
High-Speed Links

Vladimir Stojanovic


(with slides from M. Horowitz, J. Zerbe, K. Yang and W. Ellersick)

Agenda : High Speed Links


- High-Speed Links, What, Where?
- Signaling Faster - Evolution
 - » Circuits
 - » Channel
- System-level design
 - » Channel designer's view
 - » IC designer's view
- Demo

What Makes a Link?

 - Signaling: sending and receiving the information



 - Clocking: Determining which bit is which



Spanning A Broad Space

- Inverter.....to.....DSL modem
- Metrics
 - » Speed
 - » Latency
 - » Electrical environment
 - » Power & area
 - » Volume

Increasing Chip I/O Bandwidth

- Computers:

 - Main memory:

 - SDRAM100 (100 Mbps) ➔ RDRAM (0.8-1.1 Gbps)

 - Peripherals:

 - PCI (66 Mbps) ➔ Infiniband (2.5 Gbps)

- Networks:


 - Physical Front End:

 - LAN: Fast-Eth (100 Mbps) ➔ Gigabit-Eth (1Gbps)
 - WAN: OC-12 (625 Mbps) ➔ OC-192 (12.5 Gbps)

 - Switch Fabric:

 - 625 Mbps ➔ 2.5 Gbps


Inside the Router

 

- Regardless of where the links are, there is a constant desire to signal faster and with less power

Serial Link Signaling Over Backplanes - Past

- Channel was not an issue up to 2-3Gb/s

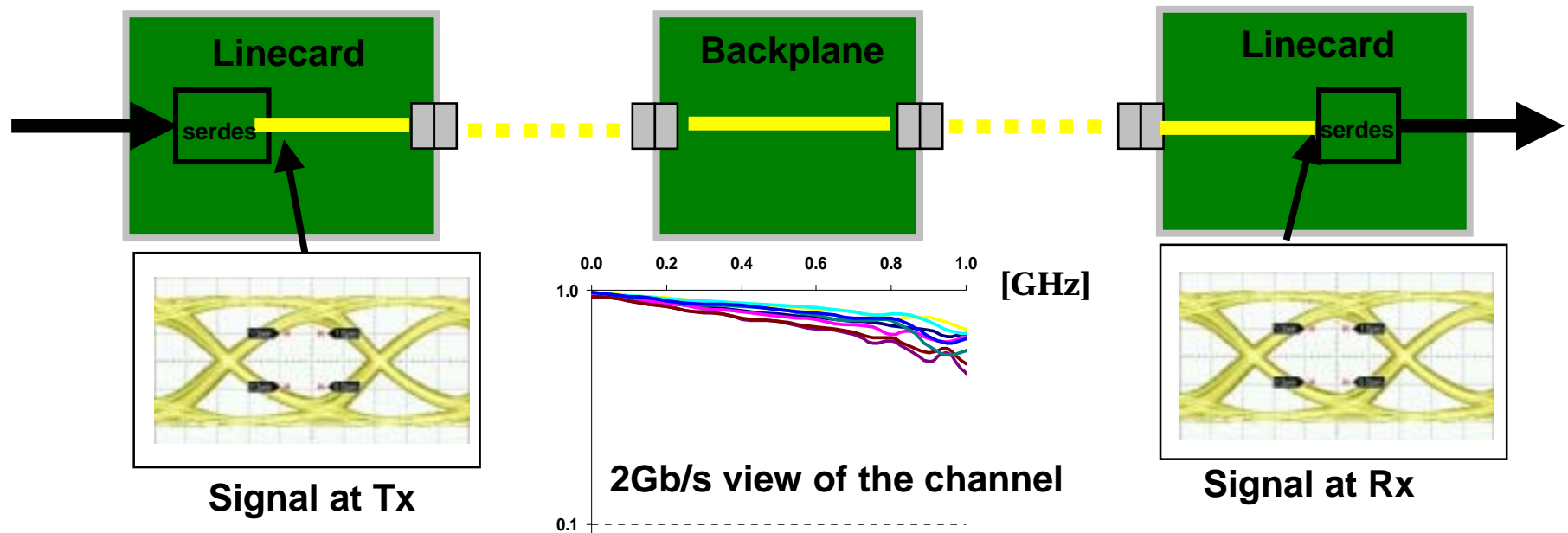


- Designs were limited by transmitter & receiver speed
- Clever circuit design – no communications/SI background needed

Signaling


	<i>Low Impedance</i>	<i>High Impedance</i>
<i>Single Ended</i>		
<i>Differential</i>		

Transmitter Design

 

- Critical components: Sync, Mux, Tx
- Design issues:
 - » Slew rate control vs ISI, jitter
 - » Output current and impedance control
- Clock and Driver power dissipation



Output Drivers

 

- On-chip clock speed limited to $6-8F_{O4}$
- Need to send more bits/clock – multiplex data



Simple Transmitter

  - DDR: send a bit per clock edge
- Critical issues:
 - » 50% duty cycle
 - » $T_{bit} > 4 \cdot FO4$




Fastest Transmitter

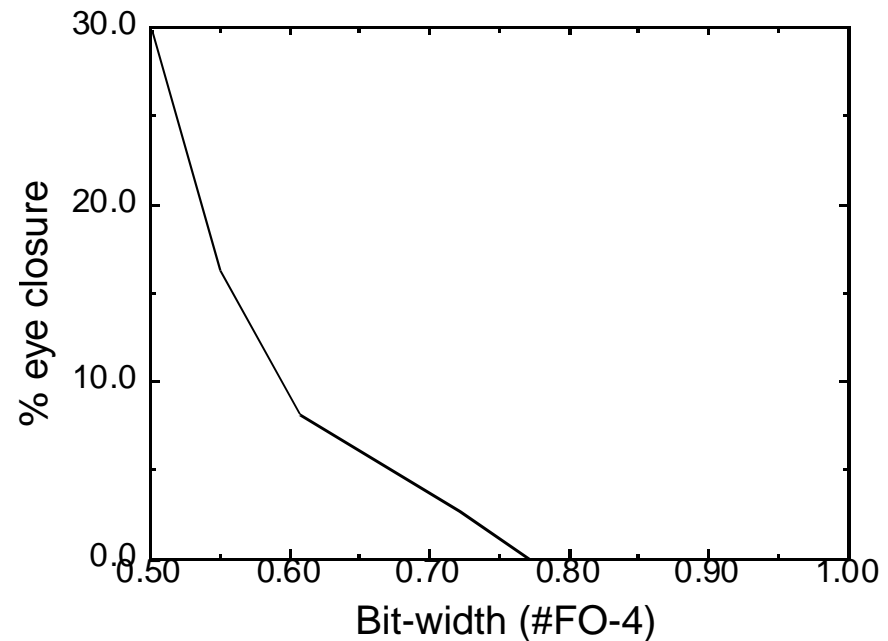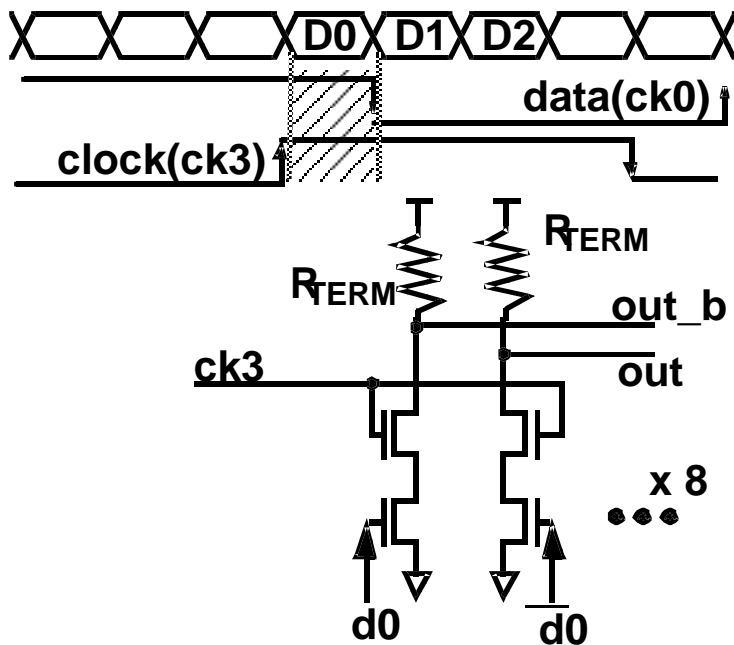- » Off chip time constant smaller than on chip:
 - Generate current pulse at the output
- » Limited only by the output capacitance





- » Limiting time constant $25-\Omega * C_{pad}$
- » $C_{pad} = 8 * C_{driver} + C_{esd}$

Simple Receiver

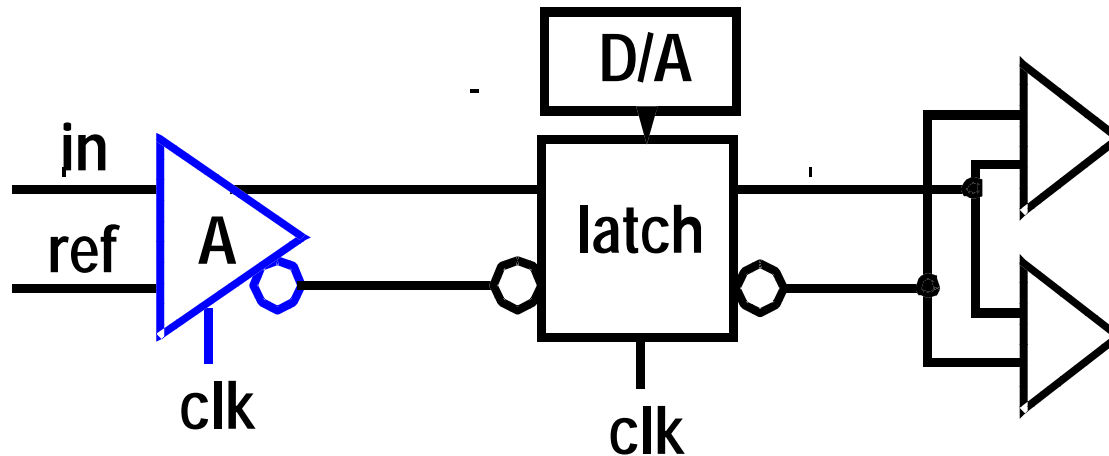


- Regenerative latch has highest gain-bandwidth product of all amplifiers (gain exponential with time – just need to wait long enough)
- Preconditioning stage: filter/integrate/rectify CM
- Latch makes decision (4-FO4)
- DAC can be used to compensate offsets

Fastest Receiver

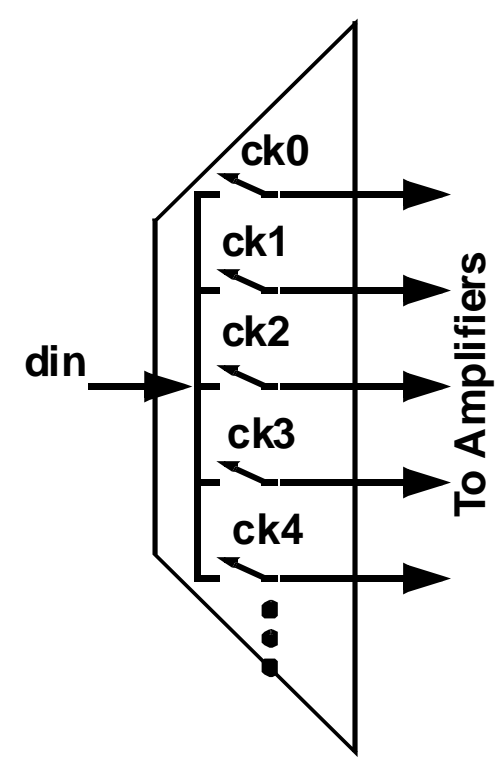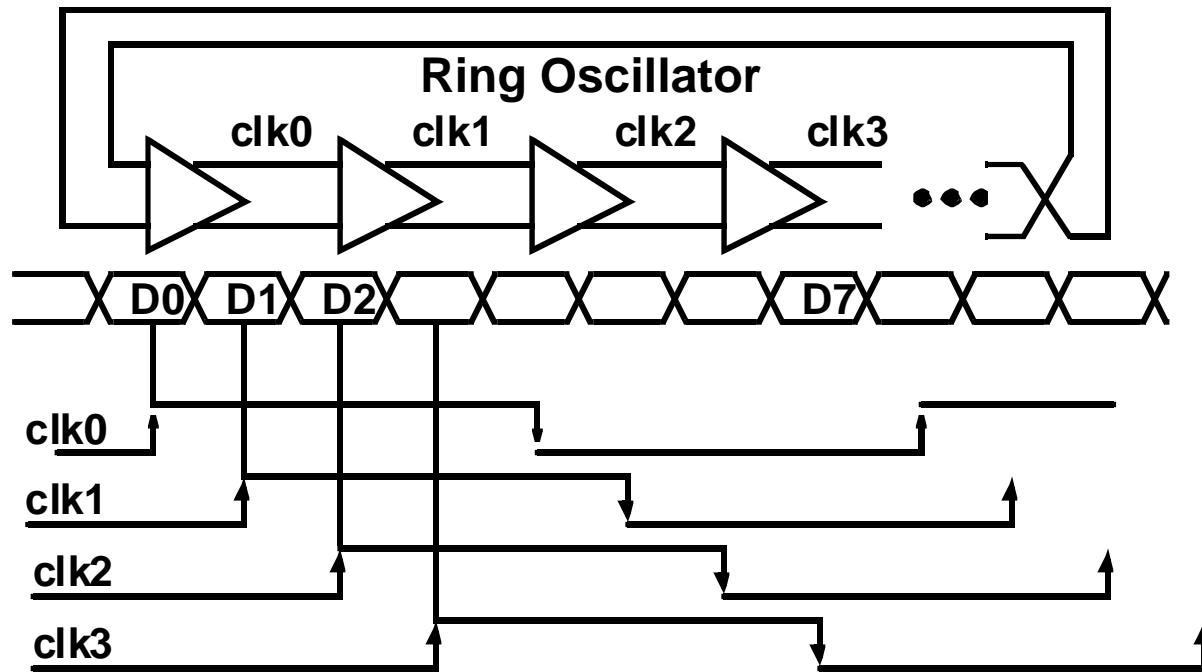


- Use multiple input receivers
 - › Simplest 2, more complex 4-8
 - › Decouples Tbit from latch resolution
 - › Leverage high input impedance amplifiers

Serial Link Signaling Over Backplanes

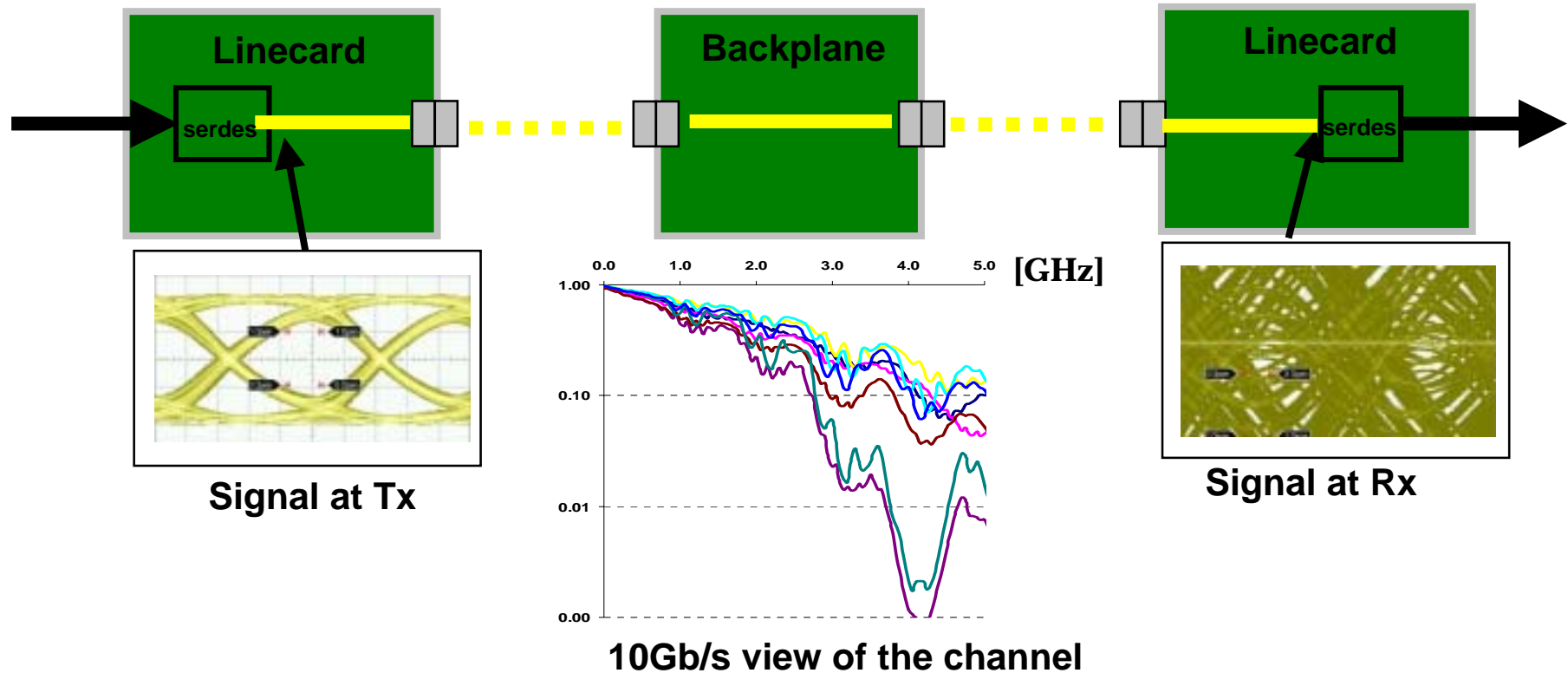



- Now that we've made the fastest Tx & Rx look what happens with the eye
- Need to look more closely into the channel as that seems to be the problem

The Backplane Environment

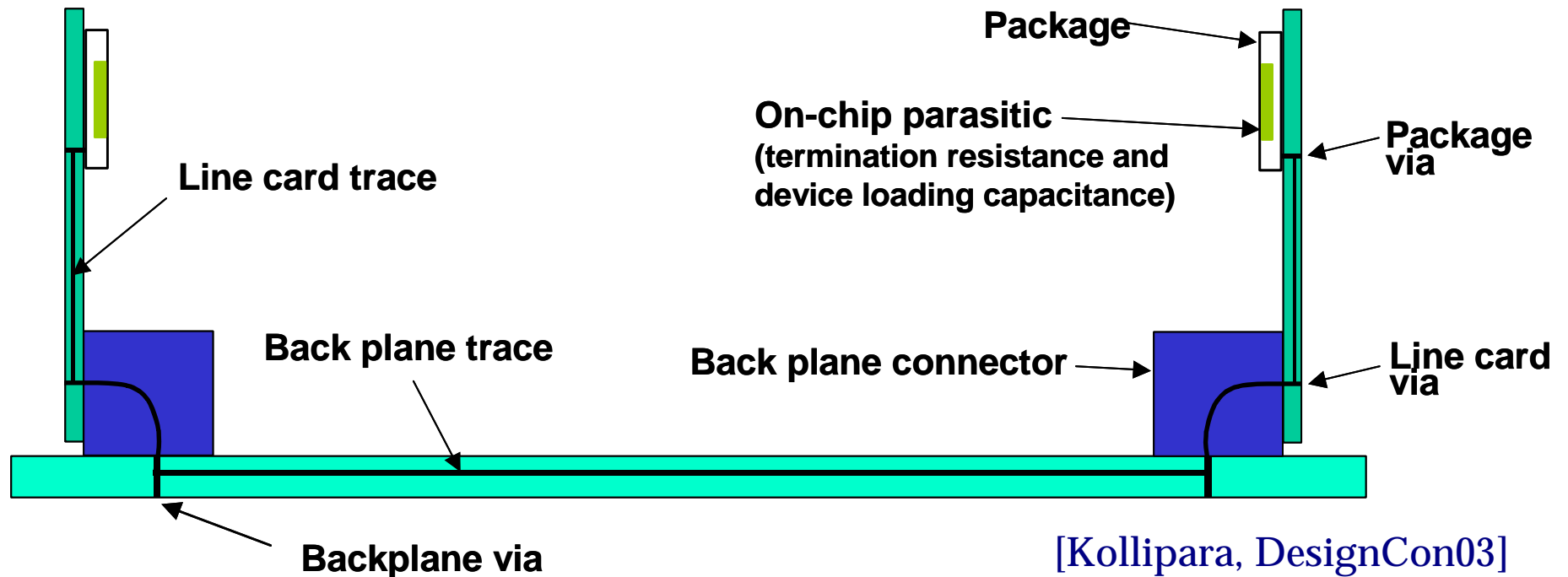


- The problem is there are many sources of Z
...and thus many possible sources of signal degradation
- Interference
 - » Intersymbol (dispersion, reflections)
 - » Co-channel (crosstalk)

Interference

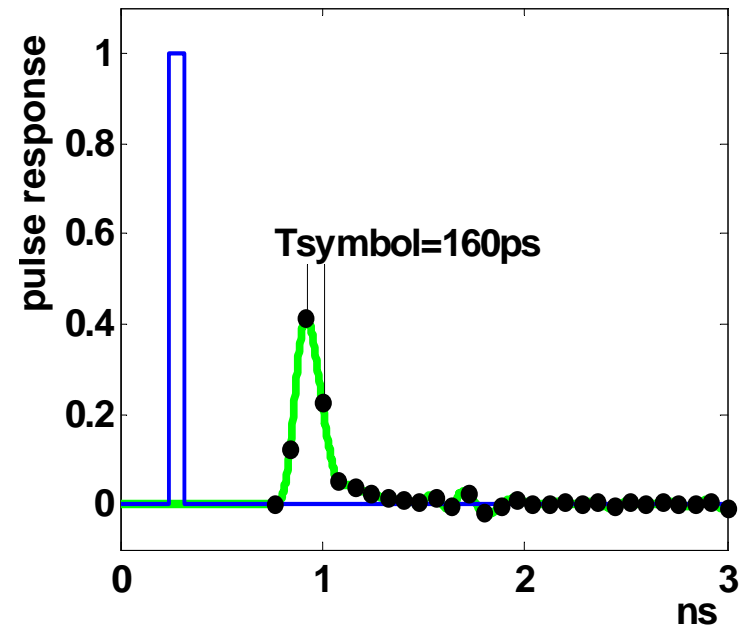 


- Inter-symbol interference
 - » Dispersion (skin-effect, dielectric loss) - short latency
 - » Reflections (impedance mismatches – connectors, via stubs, device parasitics, package) – long latency
- Co-channel interference (Far-End & Near-End Crosstalk)

Dispersion: Material Loss

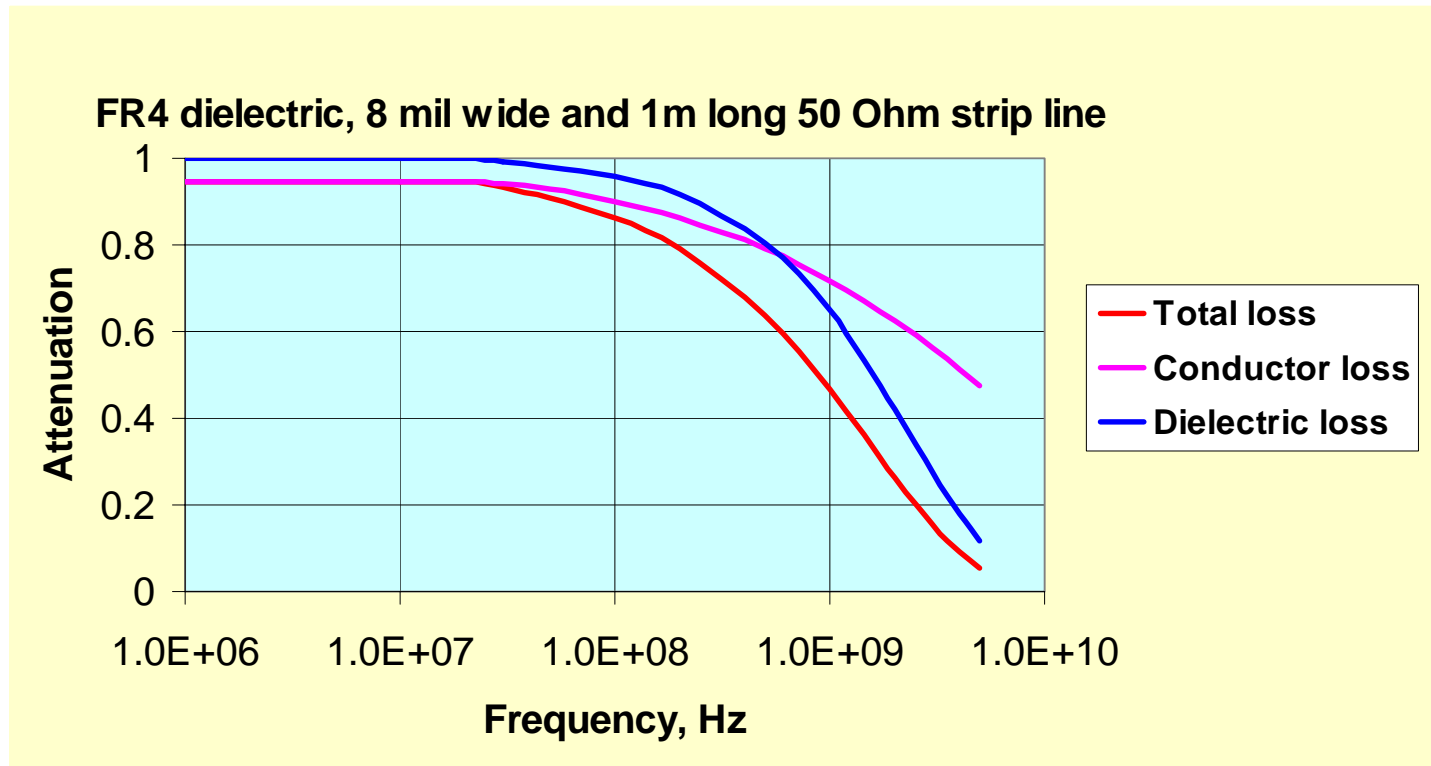


- PCB Loss : skin & dielectric loss
 - » Skin Loss $\propto \sqrt{f}$
 - » Dielectric loss $\propto f$: a bigger issue at higher f

Reflections: Z - Discontinuities


 


Energy flow into junction = transmitted + reflected energy

 - Sources of Reflections : Z - Discontinuities
 - » PCB Z mismatch
 - » Connector Z mismatch
 - » Vias (through) Z mismatch
 - » Device parasitics - effective Z mismatch




Reflections From Via Stubs

  

- Additional sources of reflections : stubs
 - » Vias - particularly on thick backplanes
 - » Package plating stubs


Reflections and Crosstalk

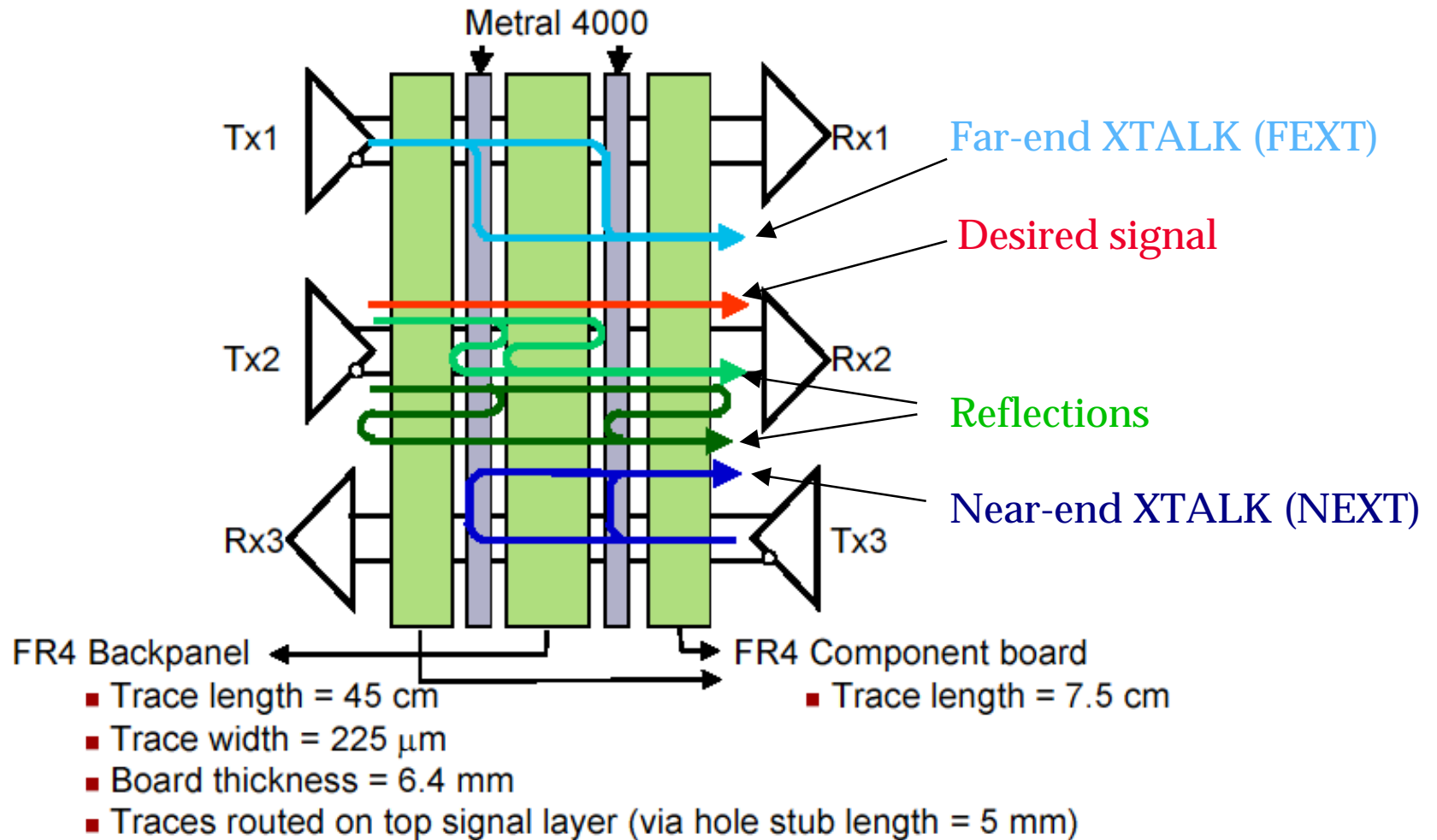


[Sercu, DesignCon03]

Crosstalk

- Many sources
 - » On-chip
 - » Package
 - » PCB traces
 - » Inside connector
- Differential signaling can help
 - » Minimize xtalk generation & make effects common-mode
- Both NEXT & FEXT
 - » NEXT very destructive if RX and TX pairs are adjacent
 - Full swing-TX coupling into attenuated RX signal
 - Effect on SNR is multiplied by signal loss
 - » Simple solution : group RX/TX pairs in connector
 - » NEXT typically 3-6%, FEXT typically 1-3%

 


A Complex System

 

Signaling Faster – System Level Improvements

- Channel designer's view (passive techniques)
 - » Try to make Z-discontinuities go away
 - » Reduce cross-talk (EM isolation)
- IC designer's view (active techniques)
 - » Design circuits that compensate/eliminate interference


 
Equalization For Loss : Goal is to Flatten Response



- Channel is band-limited
- Equalization : boost high-frequencies relative to lower frequencies



Receive Linear Equalizer

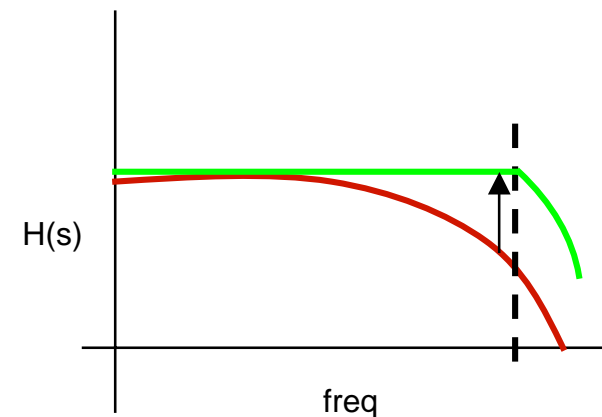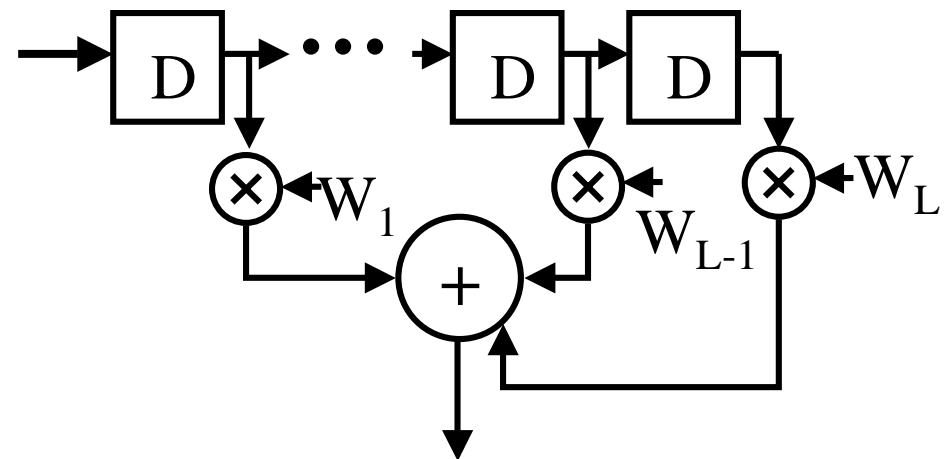- Amplifies high-frequencies attenuated by the channel
- Pre-decision
- Digital or Analog FIR filter
- Issues
 - » Amplifies noise
 - » Precision
 - » Tuning delays (if analog)
 - » Setting coefficients
 - Adaptive algorithms such as LMS




Transmit Linear Equalizer

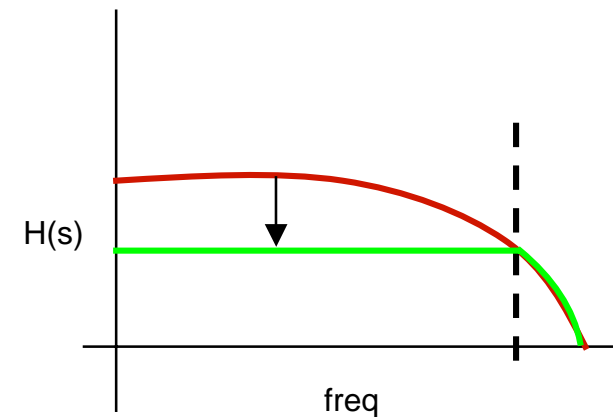 
- Attenuates low-frequencies
 - » Need to be careful about output amplitude : limited output power
 - If you could make bigger swings, you would
 - EQ really attenuates low-frequencies to match high frequencies Also FIR filter : D/A converter
- Can get better precision than RX
- Issues
 - » How to set EQ weights?
 - » Doesn't help loss at f



 
Transmit Linear Equalizer: Single Bit Operation



Example : 5Gbps over 26" FR4

 


no equalization

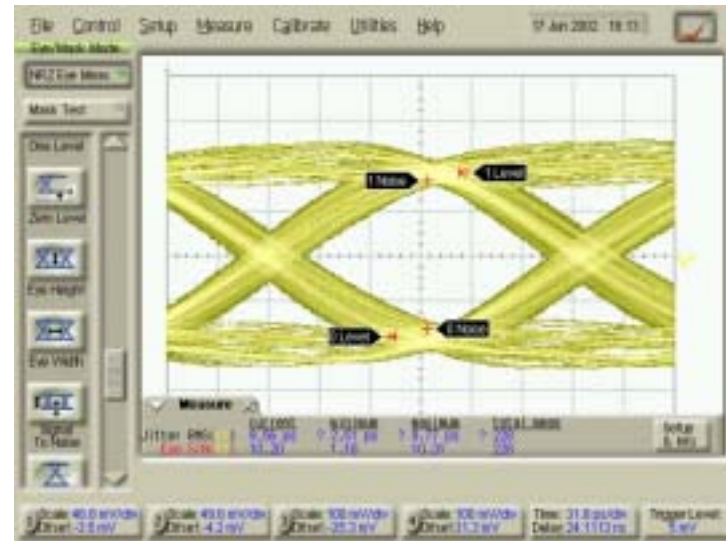


with Tx linear equalizer

Decision Feedback Equalization

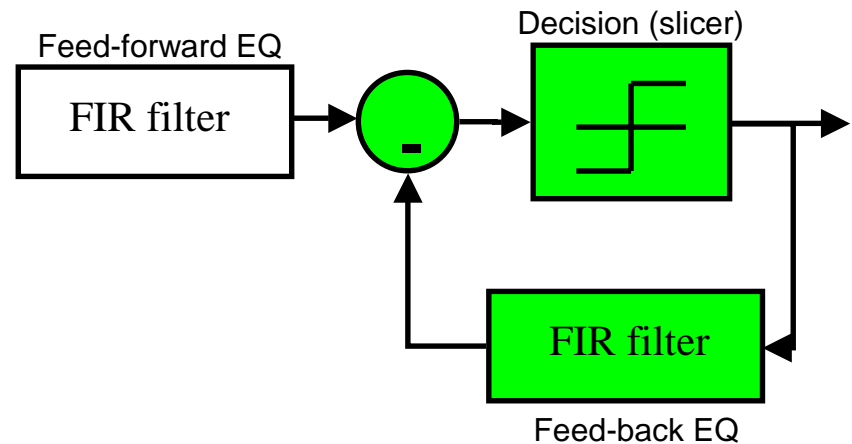- Don't invert channel... just remove ISI
 - » Know ISI because already received symbols
 - » Doesn't amplify noise
 - » Has error accumulation problem
 - Less of an issue in links where random noise small
- Requires a feed-forward equalizer for precursor ISI
 - » Reshapes pulse to eliminate precursor




Transmit and Receive Equalization

 

- Transmit and receive equalizers are combined to make a range restricted DFE
 - » Tx equalizer functions as the feed-forward filter
 - » Rx equalizer restricted in performance of loop


Tx & Rx Equalization Ranges

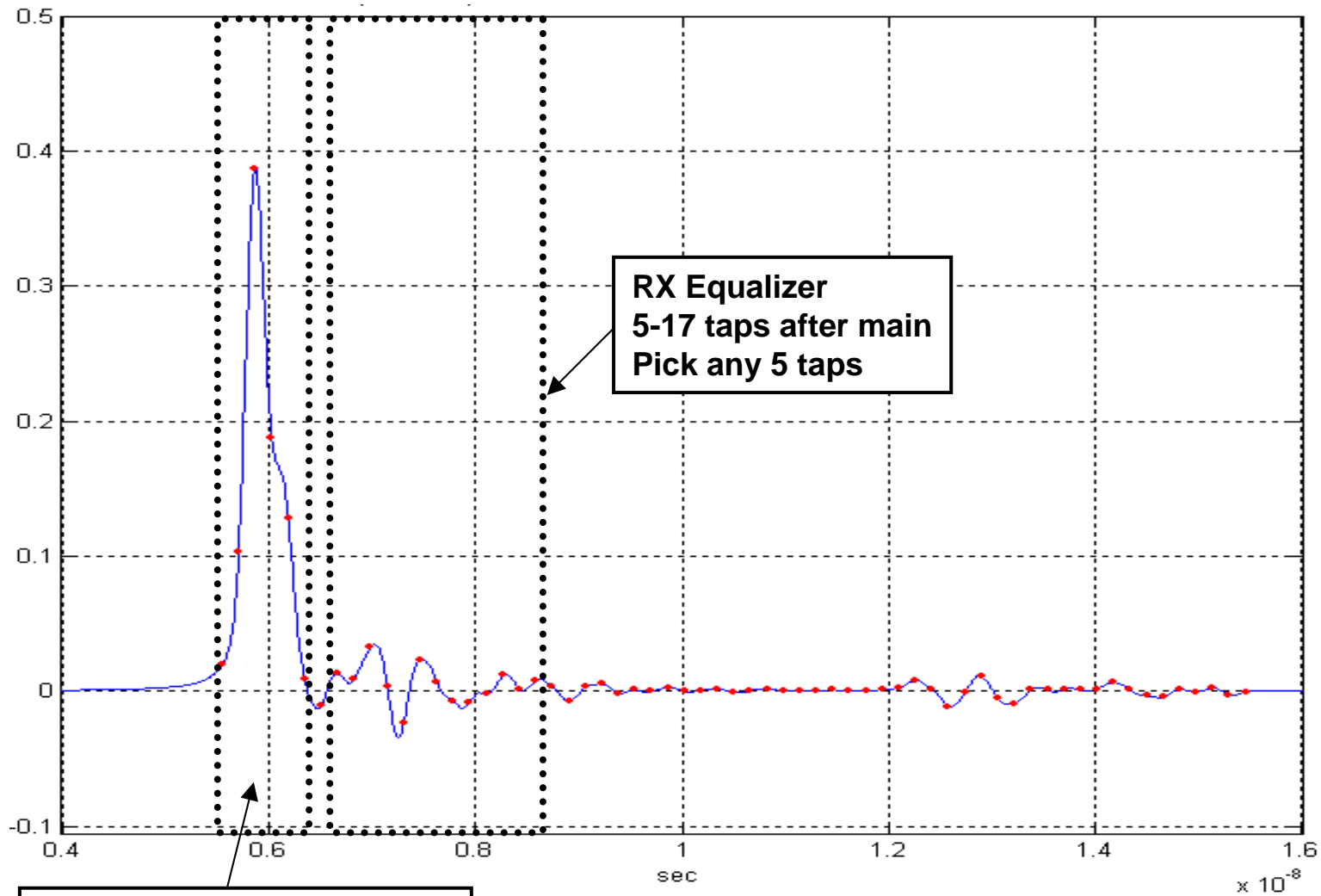


**TX Driver/Equalizer : 5 taps
1(pre)+1(main)+3(post)**

Minimizing Reflections : The Vias

 - Minimizing via stubs
 - » Thinner PCBs are better... but sometimes impossible
 - » Counter-boring
 - » Blind vias
 - » SMT technology
 - » All are costly
1.1x - 2x





Vias : Effect of Counter-boring

 


- Counter-boring top layer takes it from highest-loss to lowest-loss & reduces resonance

  Minimizing Reflections: Termination Design





(a)

 

(b)

- On-chip termination
 - » Bondwire & pad capacitance part of the channel
... instead of a stub (which rings)

Minimizing Reflections: FET Terminations

 
 


IV-characteristic
of two-element resistor

[Dally]






Alternate Approaches: Multi-Level Signaling

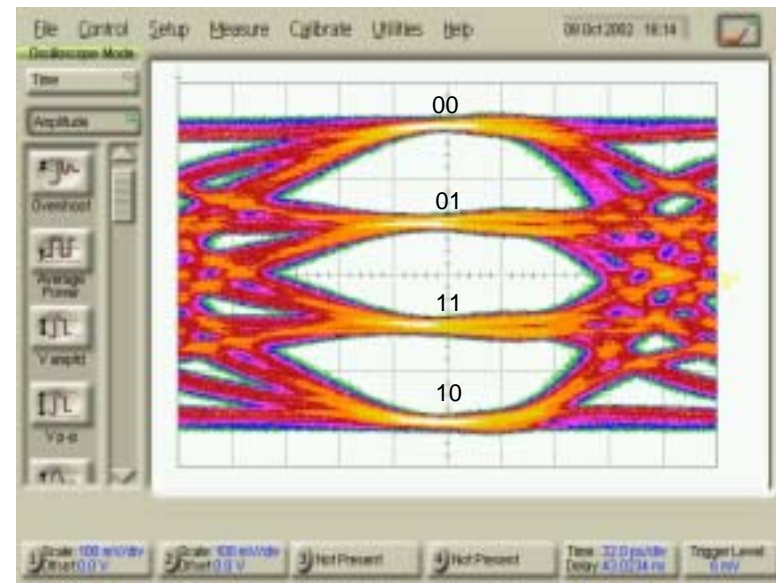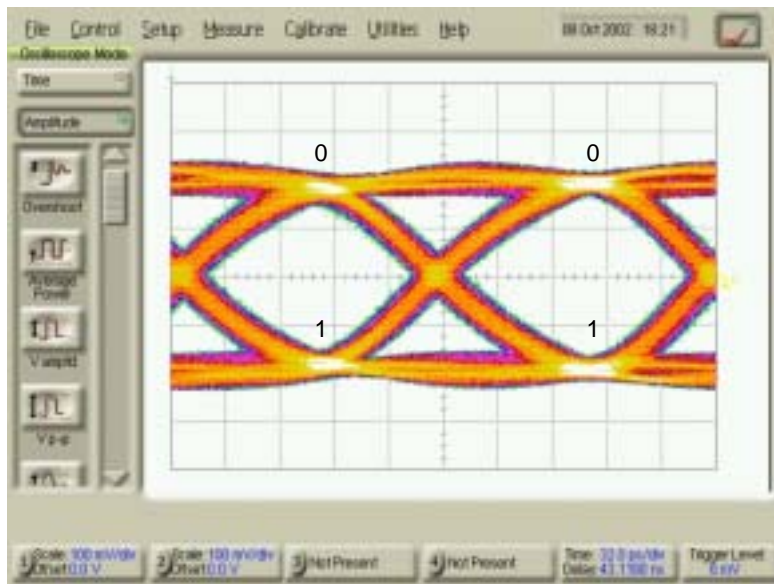- Binary (NRZ) is 2-PAM
- 2-PAM uses 2-levels to send one bit per symbol
- Signaling rate = 2 x Nyquist
- 4-PAM uses 4-levels to send 2 bits per symbol
- Each level has 2 bit value
- Signaling rate = 4 x Nyquist




Note : both can be either single-ended or differential

When Does 4-PAM Make Sense?

     


- First order : slope of S21
 - » 3 eyes : 1 eye = 10db
 - » loss > 10db/octave : 4-PAM should be considered

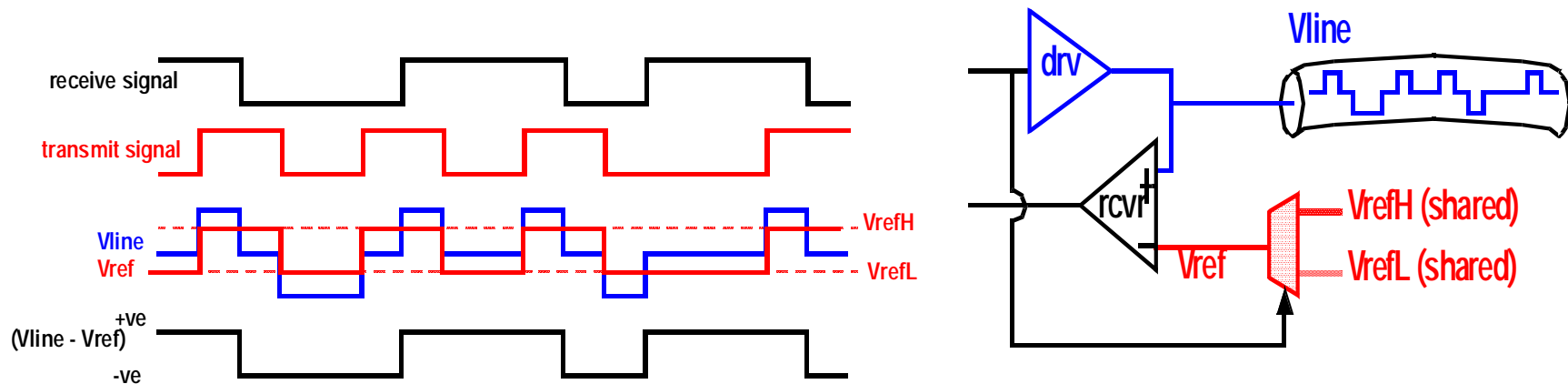Alternate Approaches: Simultaneous BiDirectional



 - Two signals at half speed
 - ›› Makes sense if b/w need equal in both directions
- Issues
 - ›› Getting ideal timing between TX & RX is tough



Characterization System

- Multiple
 - » Connectors
 - » Backplane materials
 - » Trace lengths
 - » Layers/via lengths
 - » Via technology
- These slides
 - » 20" Trace length
 - » FR4 non counter-bored
 - » Nelco 6000 2-step counter-bored
 - » Top & bottom layers




- Will show the Rambus 10Gb/s backplane SerDes demo on Friday

An attempt to shift the problem to DSP side


- 8-way DAC (8bit) and ADC (4bit)
- 8GSa/s
- A lot of power (not even including the DSP section)
- DACs and ADCs complex – a lot of parasitic filtering – channel degradation
- Still people are moving in that direction – check out K. Poulton's 20GSa/s 8-bit ADC paper at ISSCC03

Time-Interleaved DACs

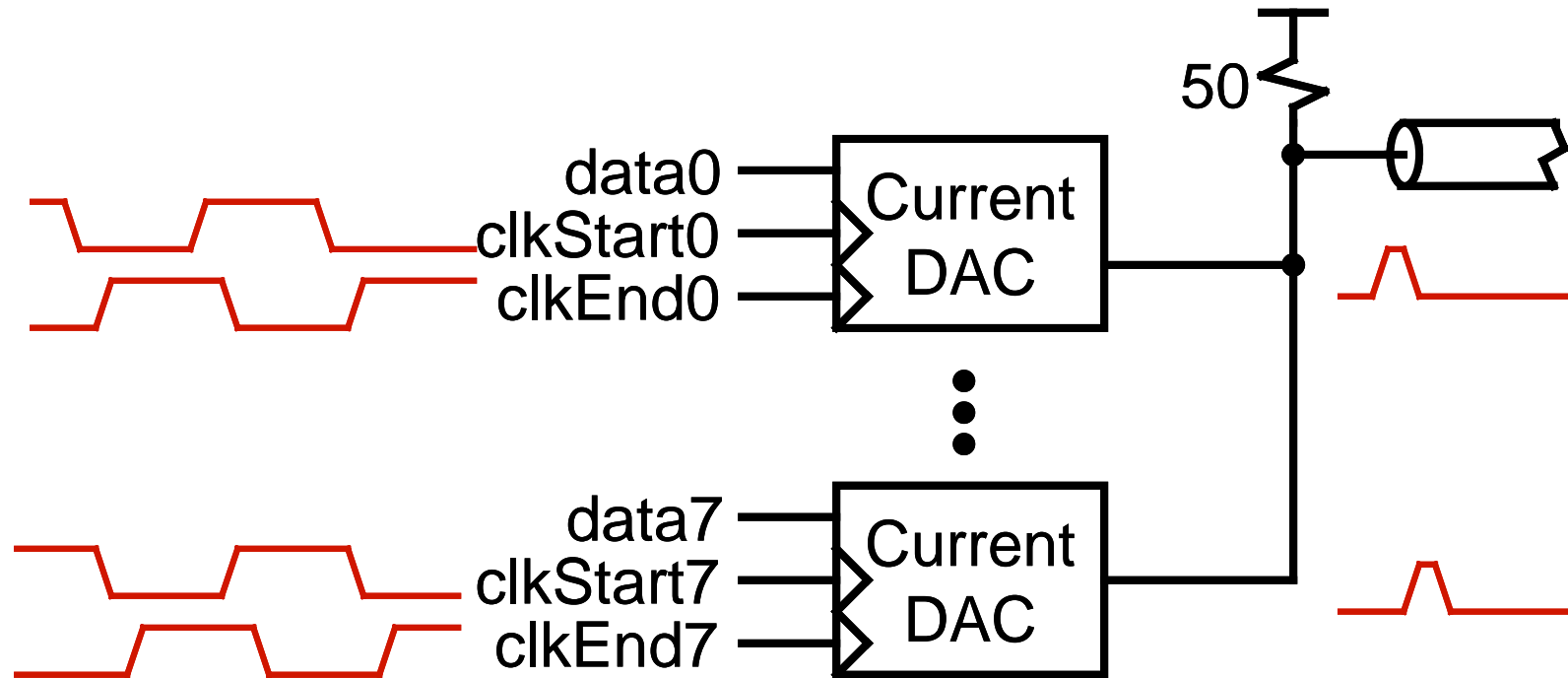

- DACs enabled by overlap of two 1 GHz clocks
 - » Need precise clocks: $3\%_{pp}$ phase noise \Rightarrow $24\%_{pp}$ symbol
 - » Fast clocks (period of 8 gate delays) limit interleaving
 - » Capacitance of all 8 DACs loads output

Transceiver Inductors and Clocking

 


- Phase adjusters correct LC delay, static errors
 - » Adjuster: clock mux, 1/16th-symbol clock interpolator
 - » 8 ADC phase adjusters + 1 for timing recovery
 - » 16 DAC phase adjusters (2 clocks for each DAC)

Next Challenges


- Improving PSR of all circuits in the path
- Integration of many links
 - » Low power, area, portable solutions
- Control of complex architectures
 - » Deal with loss, reflections and crosstalk
- Offset and mismatch
 - » Both voltage and time

- Lots of opportunity for design!


Measured S21's: FR4 no C-Bore

 


26" FR4 Bot 3.125Gbps, 2P w/EQ

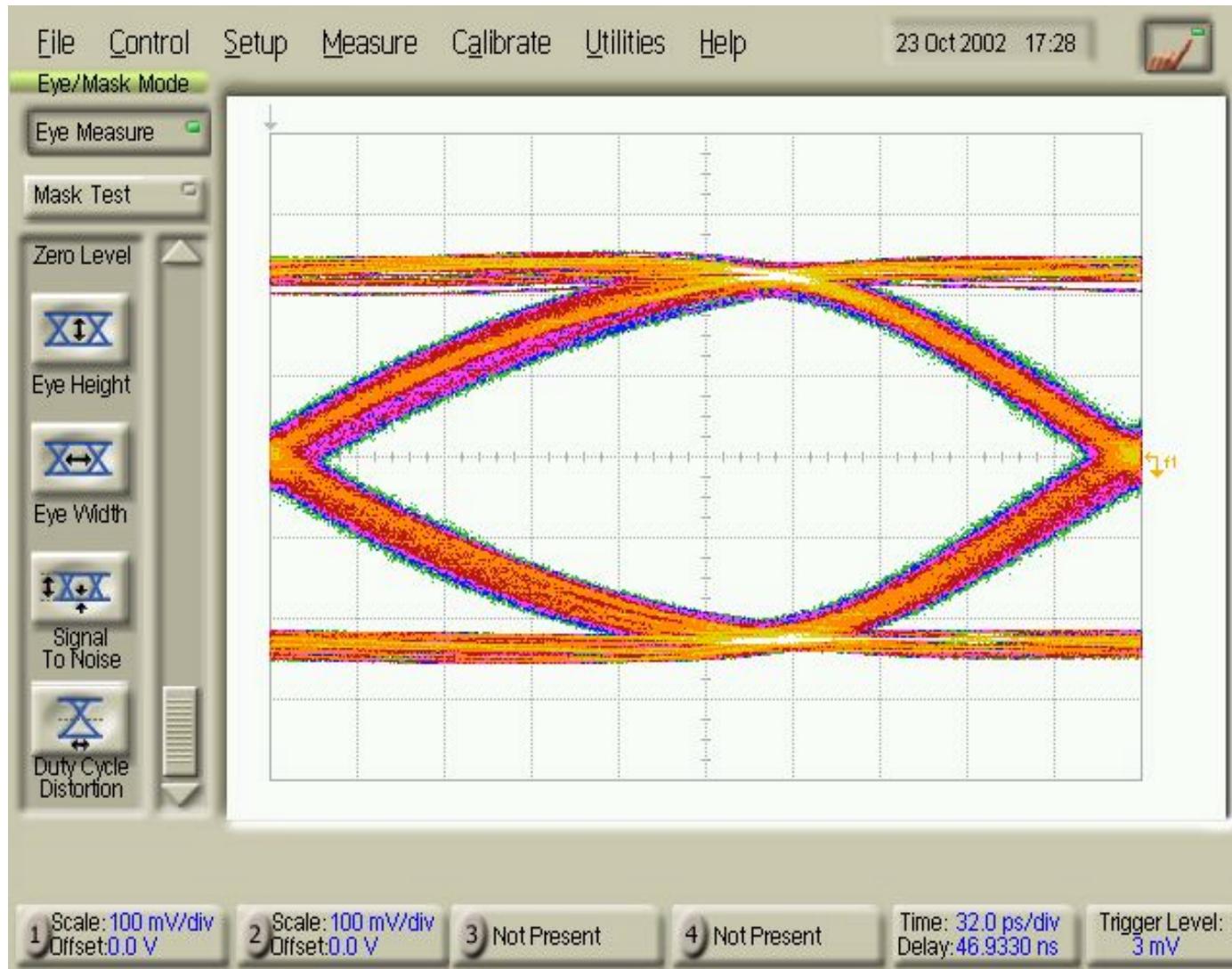


26" FR4 Bot 6.4Gbps, 2P w/EQ

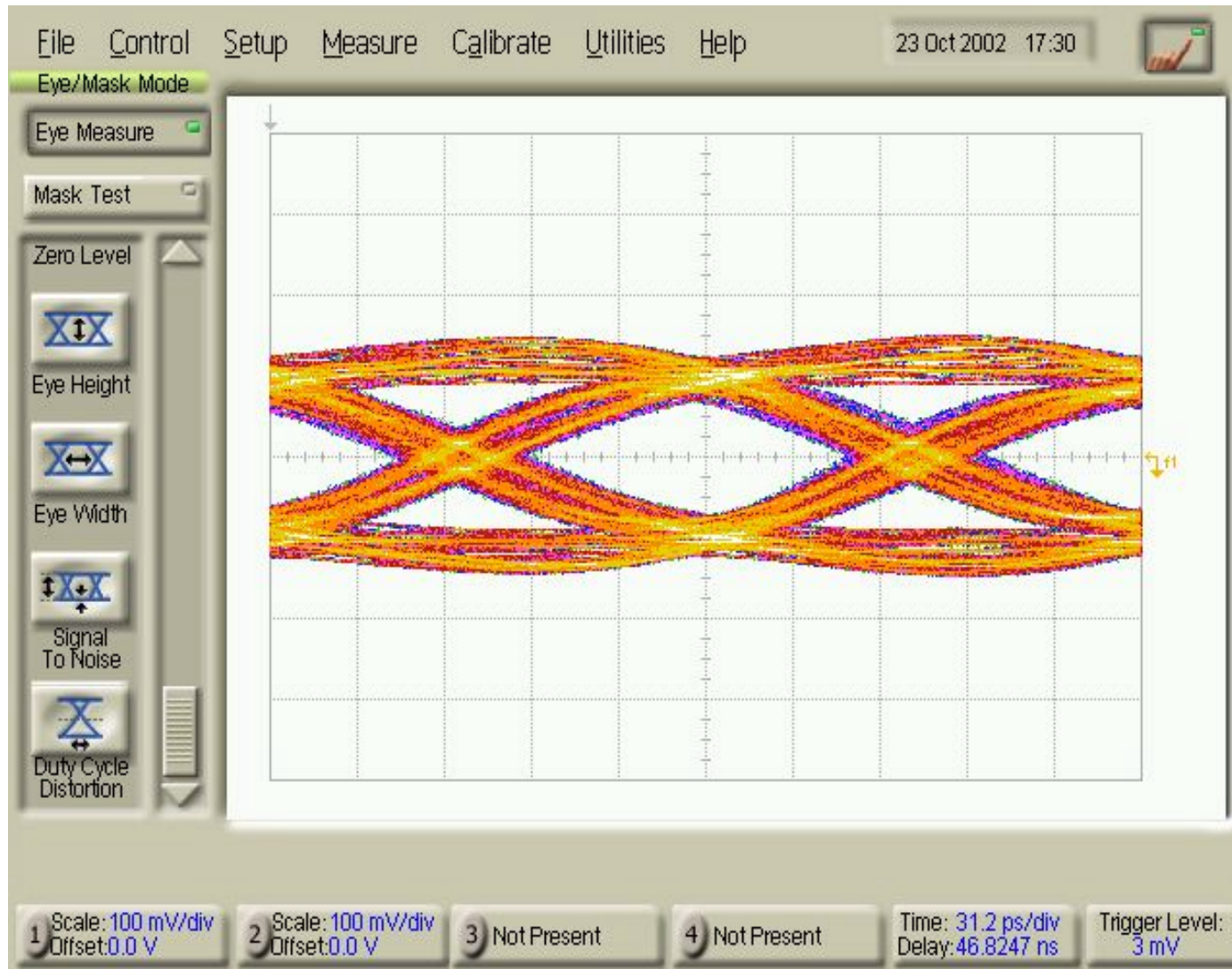


26" FR4 Top 6.4Gbps, 2P w/EQ

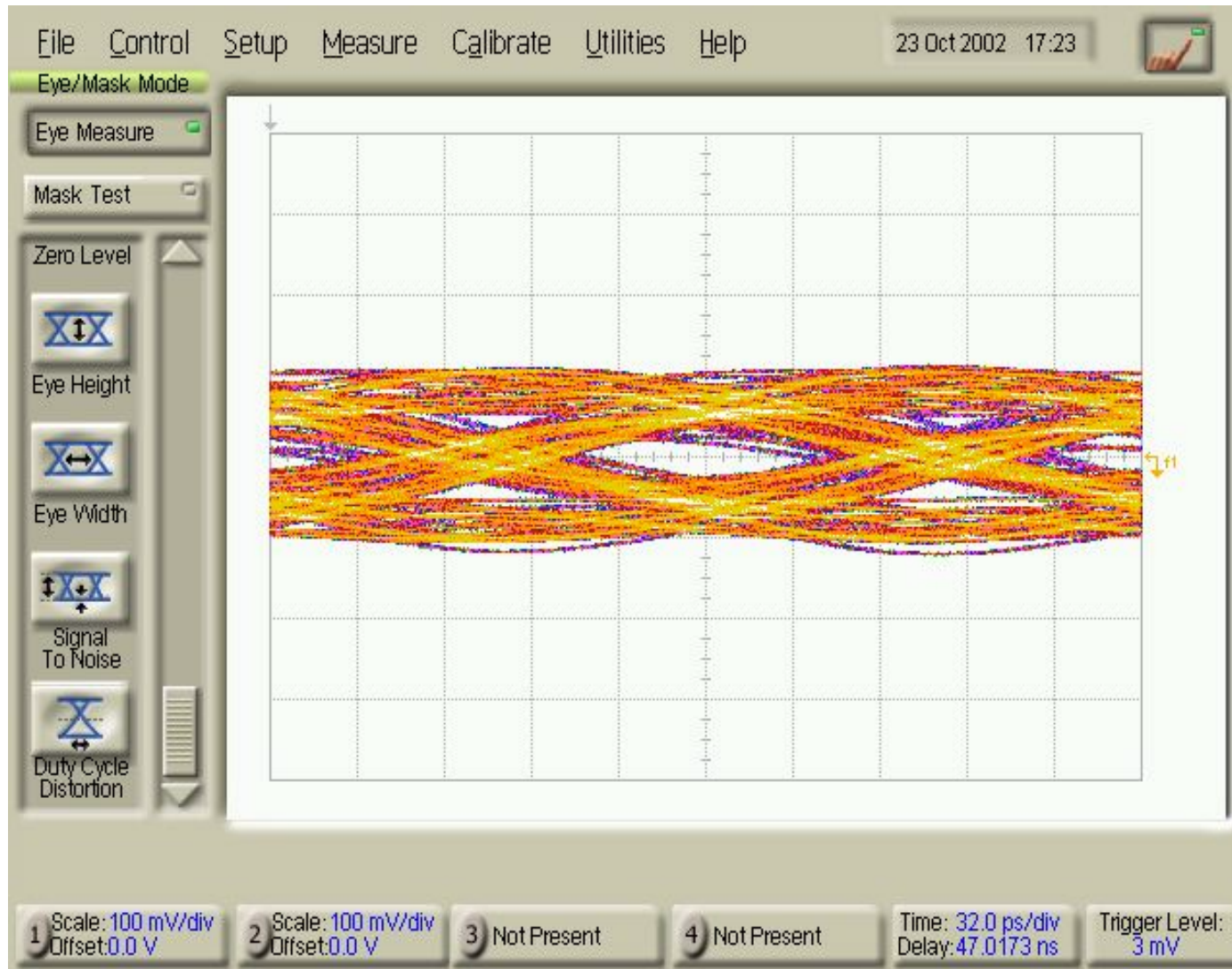


26" FR4 Top 6.4Gbps, 4P w/EQ

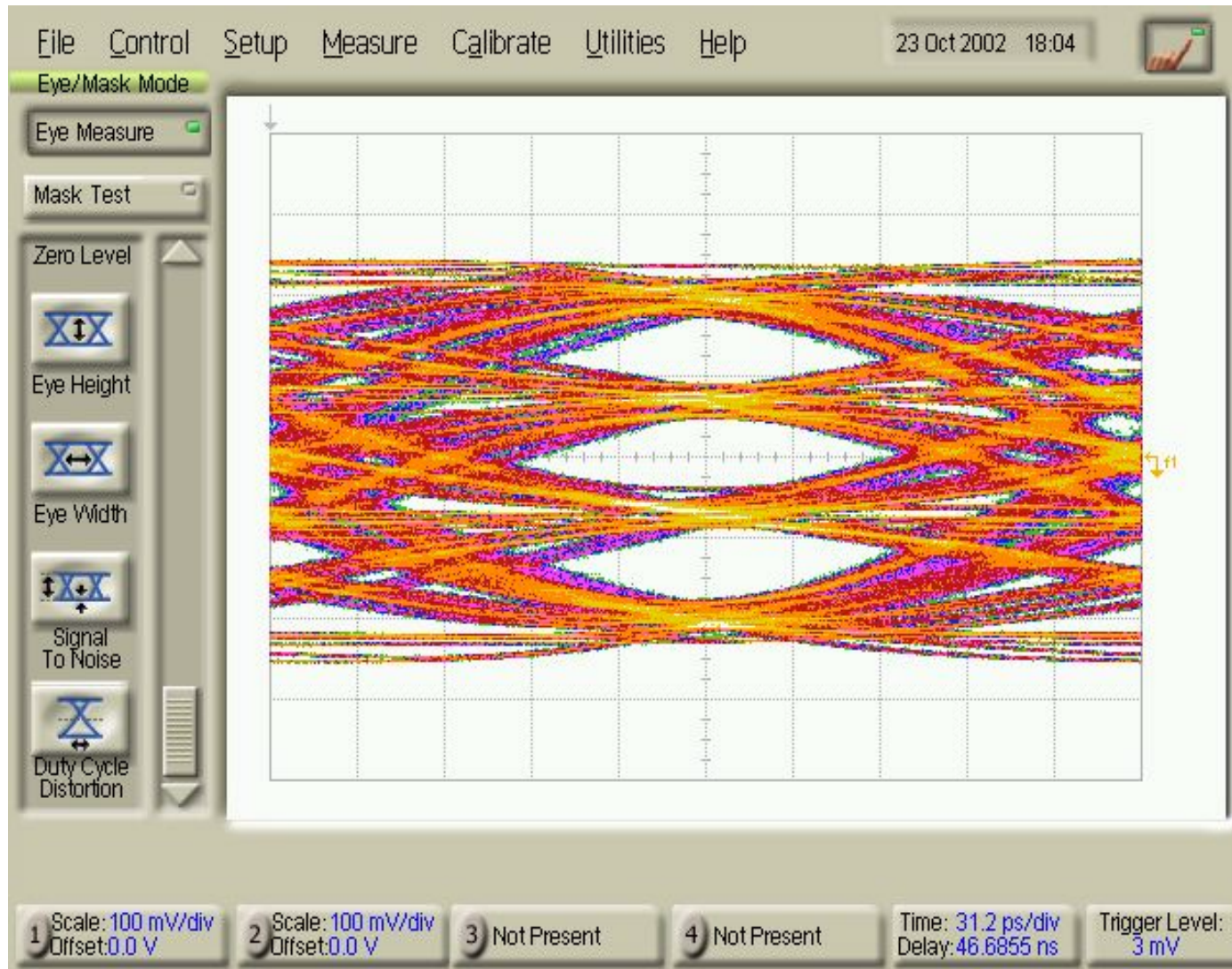


Measured S21's : N6k C-Bore

 

26" N6k-cb Top 6.4Gbps, 2P

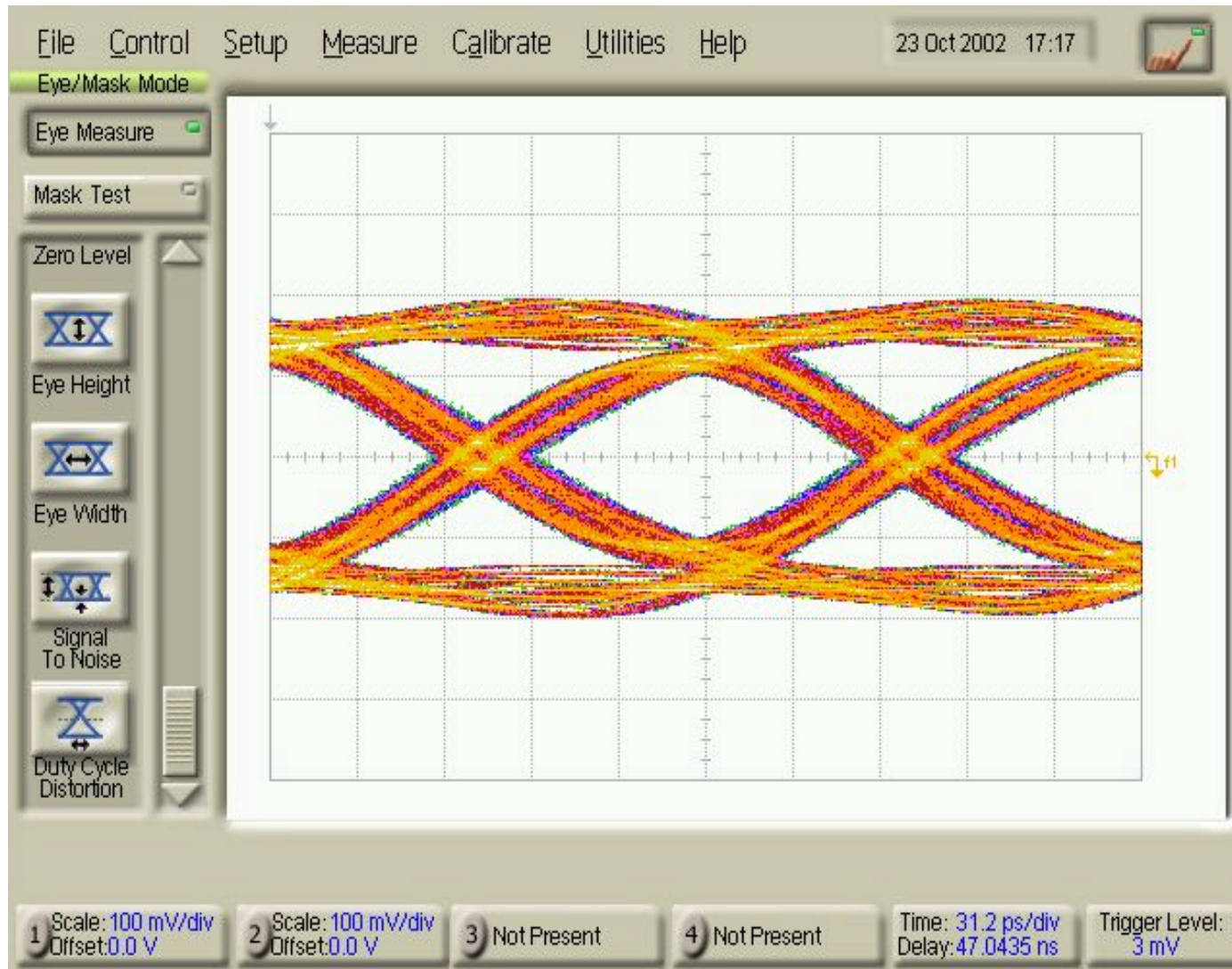


10G Eyes & System Margin Shmoos

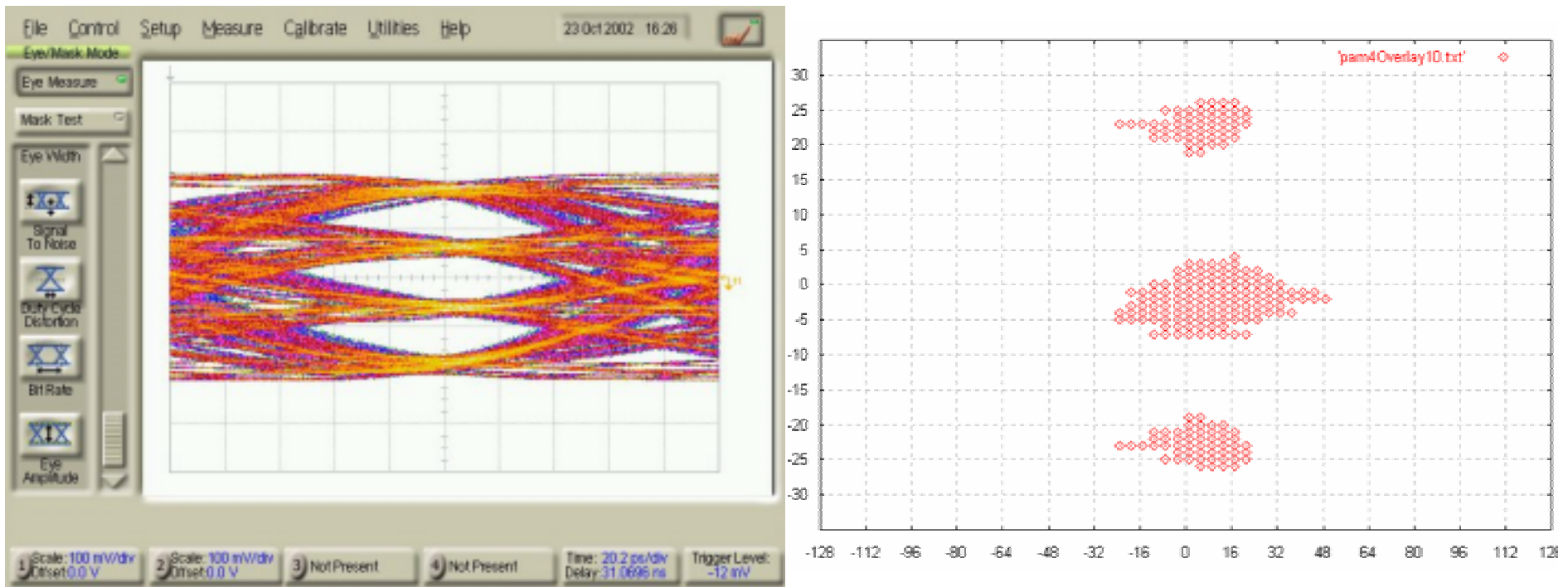


- $3''/20''/3'' = 26''$ Trace + 2 Connectors
- Tested to $BER < 10^{-15}$

Link Performance vs. Time

 

Link Efficiency: Gb/W, Gb/mm²

TX/RX Gb/W and Gb/mm²

 

(ISSCC'92-2001)

Walker'02