

---

## Lecture 9:

# Clocking for High Performance Processors

Computer Systems Lab

Stanford University

horowitz@stanford.edu

Copyright © 2001 Mark Horowitz

---

EE371

Lecture 9-1

Horowitz

## Overview

---

### Reading

Bailey	Clocking on the Alpha
Stojanovic	Evaluation of different latches
Harris	Skew tolerant domino design

### Introduction

In addition to the design of the circuits on a chip, clocking and flop/latch design has a large influence on the circuit's power and performance. As was discussed in EE271, the role of the clocks is to keep signals correlated in time. There are many approaches to this problem, some even that don't require clocks. If clocks are used, it is critical to minimize the overhead caused by the clocks, which includes clock skew, and latch/flop overheads. This lecture looks at the sequencing issue and explores a couple of approaches to this problem including eliminating clocks (self-timing). The next lecture will look at flop and latch design in more detail. We start with a brief look at history of clock design.

---

EE371


Lecture 9-2

Horowitz
 
# History

---


- Clocking was critical issue in early 80's
  - nMOS design
  - Needed fast but low power buffers
  - Name of the game was bootstrapping


 
# History, cont'd

---

- CMOS changed the rules
  - Solved the clock buffer problem



- Clock circuitry became less interesting
  - Until the 90's ...
- Clocks once again are a difficult circuit issue

# Overview of Talk

---


- Background:
  - Role of clocks
  - Why clocks are bad (clock overhead)
- Self-timed design
  - Why no clocks are bad
- Real world - (how to live with badness)
  - Clock distribution issues
  - Skew tolerant designs
- Summary

## Common View of Clock's Function

---


Clocks work with Latch or Flip-Flop to hold state

 - Latch
  - Stores data when the clock is low
- Flip-Flop
  - Stores In when clock rises


 
## Another View


If the delay of every path **was EXACTLY** the same



- I would not need clocks
  - The 'state' is stored in the gates and the wires.
- Signals stay naturally correlated in time
  - (wave pipelining)
- Impossible to do in practice, so ...

 
## Clock's Function:

Keep values in a system correlated in time



Keep signals from racing ahead of others


- Slow down signals that arrive too fast

 

- A flop is almost always built from two latches back to back
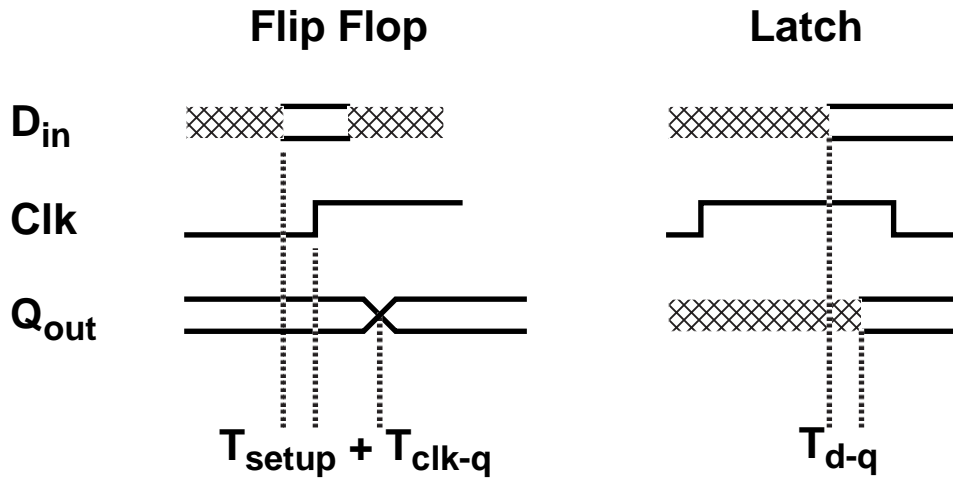
# Clock Overhead

Unfortunately, clocks delay slow paths too



# Clock Skew

Not all clocks arrive at the same time


• Two problems:

- Adds more overhead:<sup>1</sup>

$$T_{\text{cyc}} = T_d + T_{\text{setup}} + T_{\text{clk-q}} + T_{\text{skew}}$$

- Can get the wrong answer:
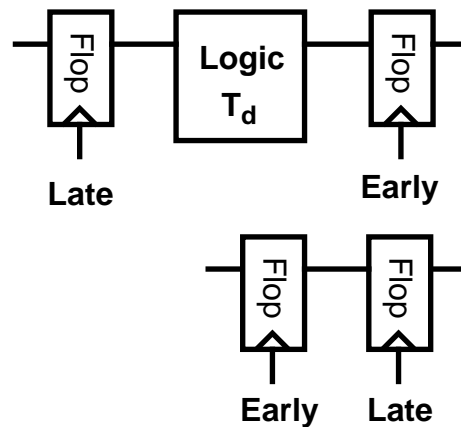
$$T_{\text{skew}} < T_{\text{clk-q}} - T_{\text{hold}}$$



Low overhead -> Fast latches, low clock skew

1. As one of the reading points out, it is hard to break the flop delay into a setup and clk-q delay, since the clk-q delay can increase when the setup time is small. We will ignore this type of issue until we talk about fops in the next lecture

# Microprocessors

---

To understand why clock design is getting harder, all we need to do is look at a couple of processor designs over the past 20 years.

- Take a look at a few different processors
  - 8086 (1978)
  - R2000(1986)
  - 21064(1992)
  - 21164(1995)
  - 21264(1998)
- Getting Larger
  - 30mm<sup>2</sup>, 80mm<sup>2</sup>, 220mm<sup>2</sup>, 300mm<sup>2</sup>, 300mm<sup>2</sup>
- Getting Faster
  - 5 MHz, 16MHz, 150MHz, 300MHz, 600MHz
  -

## Processor Trends


---

Performance:

- Part of speed increase is technology
  - Technology from 3 $\mu$  nMOS to 0.25 $\mu$  CMOS
  - CMOS FO4 gate delay is roughly 0.5ns/ $\mu$  L
- Part is better circuit design
  - 200, 50, 20-25, 20 FO4 inv delays/cycle


Bottom Line:

 - Cycle time getting shorter, even in # of gates
  - One FO4 delay is a larger % of cycle time
- Die size is growing
  - More capacitance on clocks (nF)
  - More resistance in clock lines







# Simple Self-Timed Pipeline

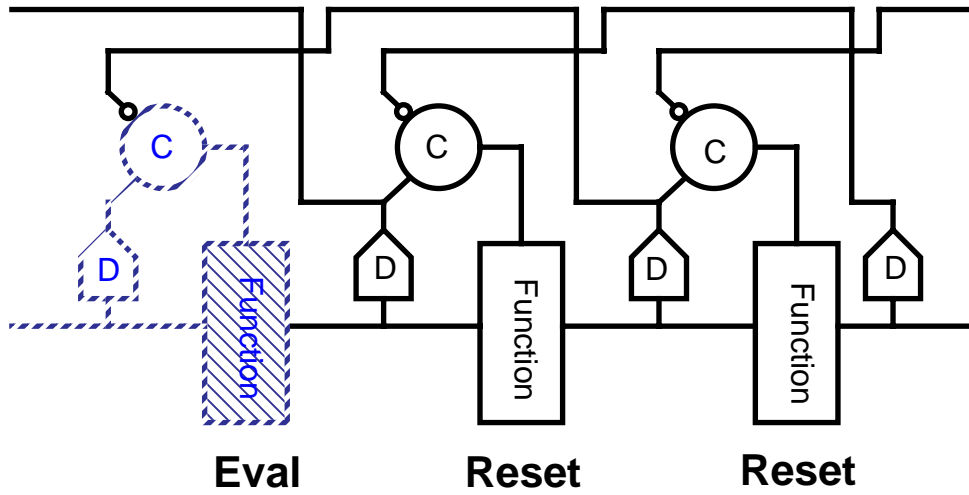


# Simple Self-Timed Pipeline

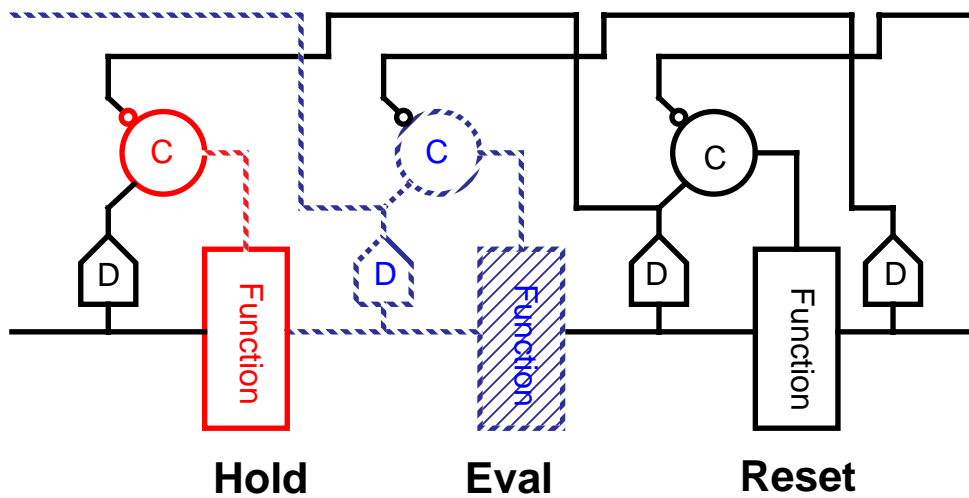

# Simple Self-Timed Pipeline

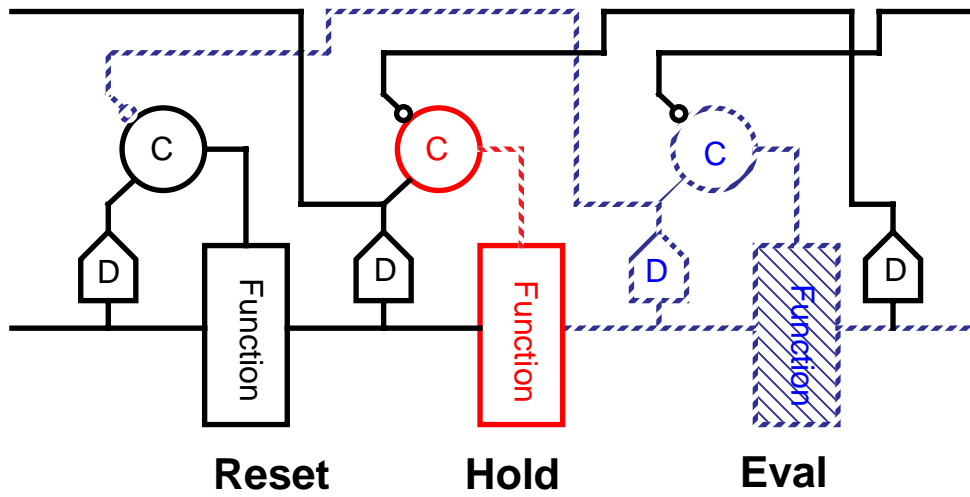

# Simple Self-Timed Pipeline

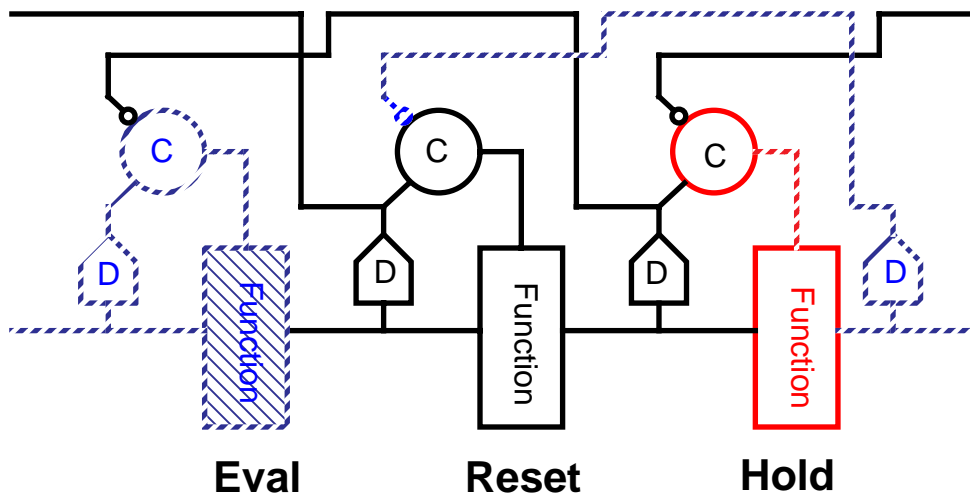

# Self-Timed Sequencing

Advantages:


- No global clock
- No clock skew
- No worst-case operation constraint
- Speed depends on operating conditions
- Cycle not limited by worst possible case

Disadvantage:

- Lots of overhead!

Cause of the overhead:

 
- Eliminated clock, not need for sequencing
  - Control generated from local signals
  - And that takes time
- Note: This is added delay not skew


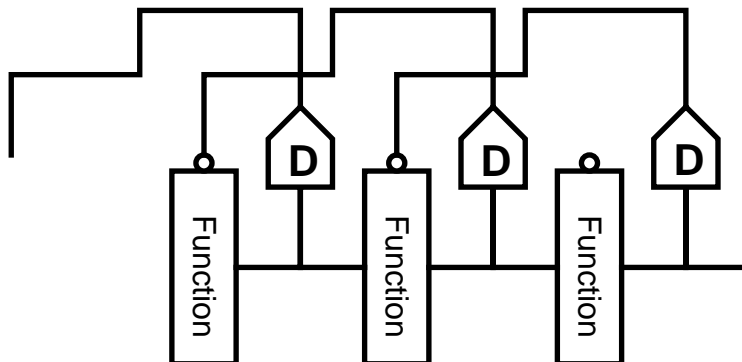
# Reducing Overhead

Make SMALL assumption about timing

- Remove D from forward path
- Data starts evaluation



## More Problems

---

In these kinds of systems there are three constraints that might be a problem

- Forward constraints (data movement)
  - This is the topic we were looking at, how fast can a data token flow forward
- Backward constraints (bubble movement)
  - This is the constraint on how fast the bubbles flow backward, or how fast does the unit reset after having data. If this is slow, you can have many bubbles for each data so this is not a constraint, but it lowers the pipeline rate.
- Loop constraints (min cycle time)
  - How fast can a function unit reset to be able to start another evaluation

These constraints have large delays in them:

- $t_D$  - completion detection tree,  $t_C$  - buffer delay to drive datapath control
- $t_D + t_C$  can be 1/2 cycle

Have fork, join issues too

## Self-Timed vs. Clocked Systems

---

Went to self-timing to get rid of skew

- Got rid of skew and worst-case limits
- But got control overhead too
  - Control overhead is larger than clock skew
- Can be hidden (in theory) but complicated
  - Little tool support

So need to choose badness

- Most designers choose clocks

# Goal

---

**Be paranoid:**

**Make clock skew as small as possible**

**AND**

**Make your circuit insensitive to skew**

## Clock Distribution


---

Need to reduce the skew on distributing the clock

- This requires us to reduce the wire delay, and the buffer delay
  - But we can't reduce the delay to the required levels (100ps) so
- Make the effective delay small, by balancing the delays of all the paths
  - Change a total delay problem to a matching problem
  - Make  $\Delta T$  much smaller than  $T_{drive}$


Use a clock trees

 - Match the delay on different branches of tree
  - If the buffer delay matches
  - If the wire delay matches
  - Skew will be zero
- Obvious question:
  - How well can you match delays?


 
# H Trees

Space filling pattern that matches wire delays



Lots of papers on these things, but not real issue


## Real Matching Issues

There are function blocks on chip, that mess up your nice abstract H-tree

- Wiring and buffers will need to fit
- Buffers eventually need to drive latches
  - Load of a latch is data dependent, since the source voltage can change

Gate loading depends on whether channel is formed

 Variation depends on technology, but is around 2:1 in capacitance



- Chip environments are not perfect
  - IR drops on the power supply lines
  - Temperature gradients across the chip
- Fabrication is not perfect
  - proximity effects / process tilt

# Wire Load Matching

---

Each wire has a different mix of components

- Not only gate-cap vs. wire cap
- Also % M1 - M2, M1 - M1, M1 fringe, etc.
- Need to find the worst-case skew

Process corners don't help

- Don't vary wires relative each other, don't account for data dependence

No real tools to help

- Problem for simulating matching of any kind, you need to simulate the worse-case for the matching, and this might not be either the slow or fast case.

Buffer Matching

- Buffer delay depend on Vdd, can vary over a chip due to IR drops (over 10%)
- Fabrication matching -- process tilt and proximity effects

## Process Tilt and Proximity Effects


---

Chips are large (2cm on a side), and transistors features are small

- Inverters on different sides on chip will be different
  - Difference is not in corner files, since corners make all transistors the same
    - This data is not usually given to designers
    - It is essential for simulating clock skew
- Proximity Issues
  - Poly width sets channel length / speed of circuit
  - Current gate lengths are  $0.25\mu$ , Poly control must be a few  $0.01\mu$
  - Local poly environment affects etching rate, so it affects channel width
  - Matched inverters, need matched layout, and matched environments
    - (region around buffer needs to be same -- add dummy buffers)
 
# Single Clock Distribution - 21064

- Thick metal layer for clocks, M3 - 2 $\mu$  thick
- Large clock buffer (entire vertical height of the chip)
  - Use a tree to balance the delay in this direction



- Shorted together all the local clock wires
  - Main difference with a conventional tree; reduces the effects of mismatches
  - Especially effective for reducing local skew
- More recent processors have more clock buffers to keep skew small


## Local Skew

Important for race-through

- Can get the wrong answer:
  - $T_{skew} < T_{clk-q} - T_{hold}$

Only occurs if delay is less than skew

- Delay is small only when elements are close
  - So only occurs when local skew is large
  - Shorting clocks together can reduce local skew
    - But also limits your design
    - Only have one clock and it is on all the time
    - Not the lowest power solution
    - Can avoid this problem by not having short paths
  - Need to have tool to check (and fix) min-delay
    - (Easy, make all your flops with the ability to have a long clk-q delay)

 


# Global Skew

---

Still have long path problem

 - Skew adds more overhead:
  - $T_{cyc} = T_d + T_{setup} + T_{clk-q} + T_{skew}$



So don't use flops!

- The situation with latches is a little different

# Clocking Design

---

- Trade off between overhead / robustness / complexity

Constraints on the logic


vs.

Constraints on the clocks

- For performance, you need to worry about
  - Overhead of the sequencing
    - Delay through the latches/flops
    - Wasted time from clock-skew
- Look at a number of different clocking methods:
  - Edge triggered clocking
  - Pulse mode clocking
  - Two phase clocking (might only have one clock)
 
# Edge Triggered Flop Design

- Most popular design style (comes from old TTL designs)
- Used in many ASIC designs (Gate Arrays and standard Cells)
- Using a single clock, breaks every cycle with a flip-flop



- Timing Constraints

$$t_{dmax} < t_{cycle} - t_{setup} - t_{clk-q} - t_{skew}$$

$$t_{dmin} > t_{skew} + t_{hold} - t_{clk-q}$$


- If skew is large enough, you have two sided timing constraints

# Flop Design

Flops introduce hard timing boundaries in to the circuit


- Data must setup before the clock edge
- Output does not change until after the clock edge
  - Any uncertainty in clock, or data is wasted
  - Need to know precisely when the data will arrive

 If some section of logic will be done early, to use that extra time, you need to move the clock to the flop early, so the next cycle has more time (and you had better check the hold time of the following flop)


 
# Latch Based Design

- Break flop into its two latches, and place logic between the latches.




- There are no hard boundaries in latches
  - Pass data when clock is high
- Latching event is the load to hold transition
  - If data arrives early it is passed through
  - Can borrow time naturally, and
  - Is insensitive to clock skew, for critical paths, data sets the timing (well generally)

# Pulse Mode Clocking

Two requirements:

- All loops of logic are broken by a single latch
- The clock is a narrow pulse

 It must be shorter than the shortest path through the logic



Clock is usually generated inside the latch

- Timing Requirements

$$t_{dmax} < t_{cycle} - t_{d-q} - t_{skew}$$

$$t_{dmin} > t_w - t_{d-q} + t_{skew}$$

# Pulse Mode Clocking

---

- Used in the original Cray computers (ECL machines)
- Advantage is it has a very small clocking overhead
  - One latch delay added to cycle
- Leads to double sided timing constraints
  - If logic is too slow OR too fast, the system will fail
  - But there is some flow time when the latch is enabled (softer edge)
- Pulse width is critical
  - Hard to maintain narrow pulses through inverter chains
- People are starting to use this type of clocking for MOS circuits
  - Pulse generation is done in each latch.
  - Clock distributed is 50% duty cycle
  - CAD tools check min delay
  - Called a glitch flop, but it is not a flop, it is a glitch latch!

# Thinking About Timing


---

Imagine your arranging your netlist on a sheet where all the flops at the top

- The gates distance from the top indicates the settling time of its output
- Gates at the end of long paths would be at the bottom of the sheet
- Some of the outputs are the inputs to the flops, so we roll the sheet
- Forms a cylinder, where the circumference is equal to the cycle time

With flops, the input has to settle before its clock rises, and the output can't change until its clock falls so

 - To guarantee operation, need to waste skew time
- Hard edge is the problem



# Latches

---

Are hard to analyze, since the timing of the output is not completely set by clock

- Output is valid clk-q delay after clock rises
  - If input was valid when clock was low
- Output is valid a d-q delay after input
  - If input becomes valid when clock is high


Skew changes the relative timing of clock and data

- Since latches are soft barriers it does not change the output arrival time!
- Latch based system can tolerate skew

$$= T_{\text{cyc}} - T_{\text{max}}$$

$$T_{\text{cyc}} = \text{cycle time}$$
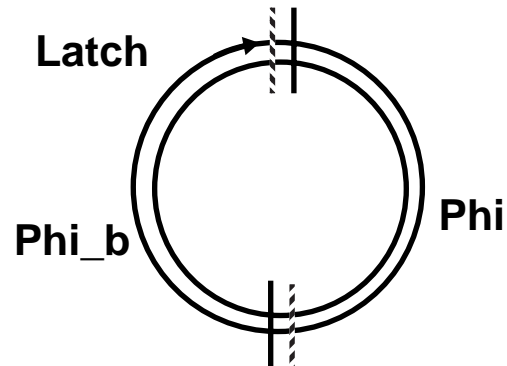
$$T_{\text{max}} = \text{Max delay between latches}$$



# Summary

---

Clocks have skew

- Today skew is caused by mismatches of balanced paths
  - Simulating matching is VERY HARD since need data that is not available
  - Need your our simulation environment since assuming perfect matching gives you get best-case skew
- I believe that keeping skew under 200ps is hard
  - Can do better than that over smaller regions (for fixed functionality, skew should roughly scale with inverter speed)
- Need to have circuits that deal with skew
  - Need to prevent race-through by padding short paths (and min. local skew)
  - Prevent cycle-time impact by using latch based design techniques
    - Use skew tolerant domino (but that is another lecture)

If you are careful clocks will work fine for chips running at GHz rates.