

VLSI Power Delivery

David Ayers

Outline


- Die power delivery
 - Die power goals
 - Typical processor power grid
 - Transistor power noise
 - SSN noise and control (decoupling)
 - Package connections
 - Large di/dt's
- System power delivery
 - Compents: VR's; MB; Socket; Package
 - Capacitor arrays
 - Frequeuncy analysis and resonance
- Related topics
 - Signal return path and cross-talk
 - IO power delivery
 - Filtered supplies for sensitive circuits
 - Scaling

Die Power Delivery

Goals of the Die Power Network

- Do's
 - Deliver power from the package to the transistors with little voltage drop
 - Deliver charge from die capacitances to transistors to control noise spikes
 - Provide signal return and shielding
- Don'ts
 - Network should not wear out from electromigration and self-heating
 - No onerous layout requirements
 - Area usage should be minimized
- Designer must balance the competing objectives
 - For example, small voltage drop competes with minimizing area (metal) usage
- Typical solution has a regular grid in the upper layers

6 Layer Power Grid Example -- CBD

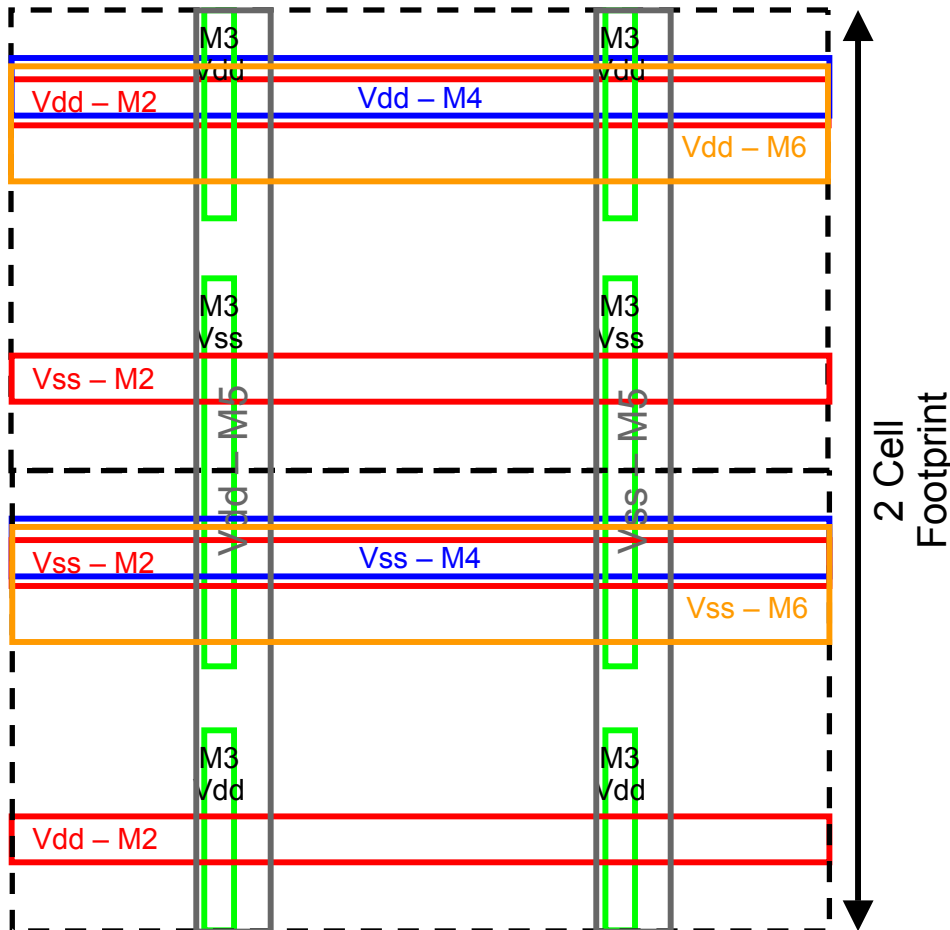


- Representative power grid design for 6 layer CBD shown
 - Custom layout may not be as regular at M2 & M3
- M2 is mirrored for well abutment
- M3 power shares tracks to limit metal usage and increase via counts
- Vias located at all next layer crossings
- Power metals are stacked as much as practical to simplify via stacks
 - Provides short access to thick upper layers
 - Thick and wide upper layers dominate the structure

Local Layout Considerations

- Transistor technology trends
 - Trend towards single poly direction for Optical Proximity Correction and Phase Shift Mask generation
 - Leg length being limited by increased poly resistance
 - Though fully silicided gates are being reported [3], [4]
 - Simplifies power layout and limits M1 leg lengths
 - Makes full gridding more practical
 - Vertical flow becomes very important, even dominate
 - Must consider vias in chip power models
 - High current density driving the need for high via counts for EM and voltage drop
 - May need more or wider power stripes to accommodate vias
 - Via counts should be in proportion to via resistance
 - Example: $V5 = 1 \text{ Ohm}$, $V1 = 3 \text{ Ohms}$ → should have 3x as many V1's
 - May need to push for larger size power vias

Transistor Behavior

 
- Graph of current vs. time from simulation of a repeater segment in 90 nm technology
- Behavior and local decoupling need is independent of clock frequency!
- Charge needed can be computed by integrating the current waveform
- Decoupling capacitance needed can be estimated by $Q/\Delta V$
 - ΔV is the budgeted voltage drop



White (middle wave) = moderate load, FO ~ 4

Transistor Behavior (Cont'd)

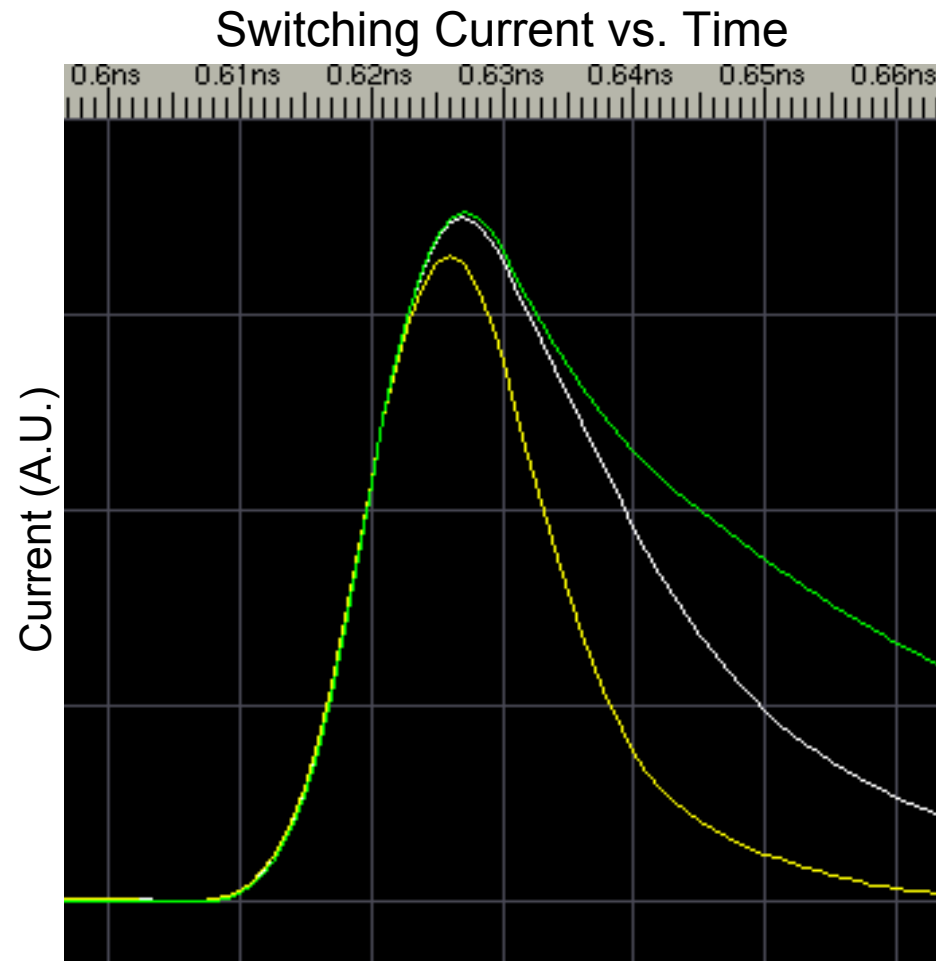
- The worst IR drop point is at the peak
 - Worst $L di/dt$ drop is at the inflection point halfway up the ramp
- The rising edge is nearly identical regardless of the load!
- Note that the transistor current is very fast -- peaks in < 20 ps
- Decoupling must be located close enough to be reached in time
 - Must beat current peak
- Package capacitors way too slow (nanosecond tau's)



White (middle wave) = moderate load, FO ~ 4
Green (upper wave) = heavy load, FO ~ 7
Yellow (lower wave) = light load, FO ~ 2.5

Impact on Nearby Logic


- Very fast transistor switching means very fast noise spikes
- Random block of logic is usually not a big noise concern
 - Thousands of scattered small transistors fire at various times in a clock cycle
 - Not enough 'stuff' firing at once to cause a serious disturbance
 - More like white noise
 - Bad case will be bank of synchronous drivers (like repeaters)
 - 64-256 large drivers firing synchronously
- Wave shown is from a power model repeater bank simulation with 90 nm technology
 - Spike droops up to 19% of Vdd
 - But droop only exceeds 5% of Vdd for < 25 ps

 

- With a clock cycle > 200 ps, there is minimal delay impact to nearby logic from one spike
 - Is extra decoupling really needed?
 - Noise spikes have the greatest speed impact on the repeated signal itself

Drop vs. Decap Distance and Die Metal

 - Simulations from 180 nm technology node
 - Capacitors placed at various distances from noise source
- Note noise increase as capacitors are placed further away
- Substantial improvement with increasing power metal use



Grid Propagation


- Die propagation is slow since resistance dominates
 - Typical top layer resistivity of 25-30 mOhms/sq
 - About 6-8x that (~ 200 mOhms/sq) for a single direction if half the layer is used for power wires
 - Factor of 2 each for half of a layer, half to Vdd or Vss, half line and space
 - Typical circuit capacitance density is ~ 1 nF/mm² (90 nm node)
 - RC time constant is ~ 200 ps/mm one way!
 - Most droops are in the 10-20% range (not $1/e = 63\%$ droop for an RC time constant)
 - Thus 10-20% droop propagates in the ~ 30 ps/mm range
 - Need to travel both to and from capacitance
 - Plus there is non-quasi static delay in decoupling cells of several ps
- This limits the useful distance at which decoupling capacitors can be placed to a few hundred μ m or less
 - 30 ps/mm limits decoupling distance to ~ 200 μ m to respond to a 20 ps current spike

Capacitance Density

- Package planes have 30-100 μm separation
 - $< 0.001 \text{ fF}/\mu\text{m}^2$
- Die metals have $\sim 0.5 \mu\text{m}$ of separation
 - $\sim 0.07 \text{ fF}/\mu\text{m}^2$ (about 4x this value for 8 metal layers)
- MOS cap has $\sim 2 \text{ nm}$ of separation (90 nm node)
 - $\sim 18 \text{ fF}/\mu\text{m}^2$
- Current MIM (metal-insulator-metal) capacitor technologies are reaching $\sim 1 \text{ fF}/\mu\text{m}^2$ (see the summary table in [1])
 - $1 \text{ fF}/\mu\text{m}^2$ is probably not very useful for bulk decoupling, need about 10x that
 - A higher density with a single mask was recently reported [2]
- MOS type caps remain as the main source of supplemental decap on die at 90 nm
 - Leakage is limiting usefulness – may need special structures

Decoupling Capacitor Design

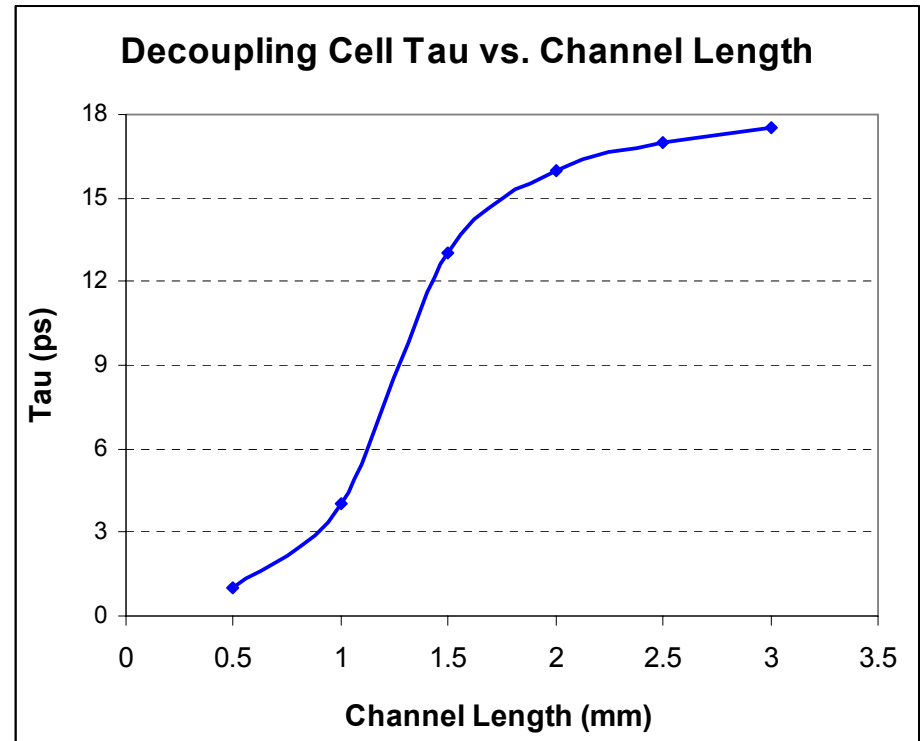- Want high capacitance density and low resistance for fast response
 - High density achieved by maximizing the poly gate oxide area
 - Low resistance achieved by limiting the distance between contacts to $\sim 1\mu\text{m}$
- Decoupling added for global di/dt changes (1st droop) can have longer distance between contacts




NMOS Transistor Style Capacitor
Simulated in 130 nm Technology

Decoupling Capacitor Design (Cont'd)


- Cell type can be important
 - NMOS faster than PMOS inversion cells
 - PMOS accumulation cells can be faster than inversion but require wells which eat up space
 - Gate oxide leakage concerns may force accumulation cells
 - Work function shift reduces leakage
 - But capacitance rolls off at lower voltages (see graph)
 - Not well suited for analog circuit applications

Capacitance Density vs. Voltage

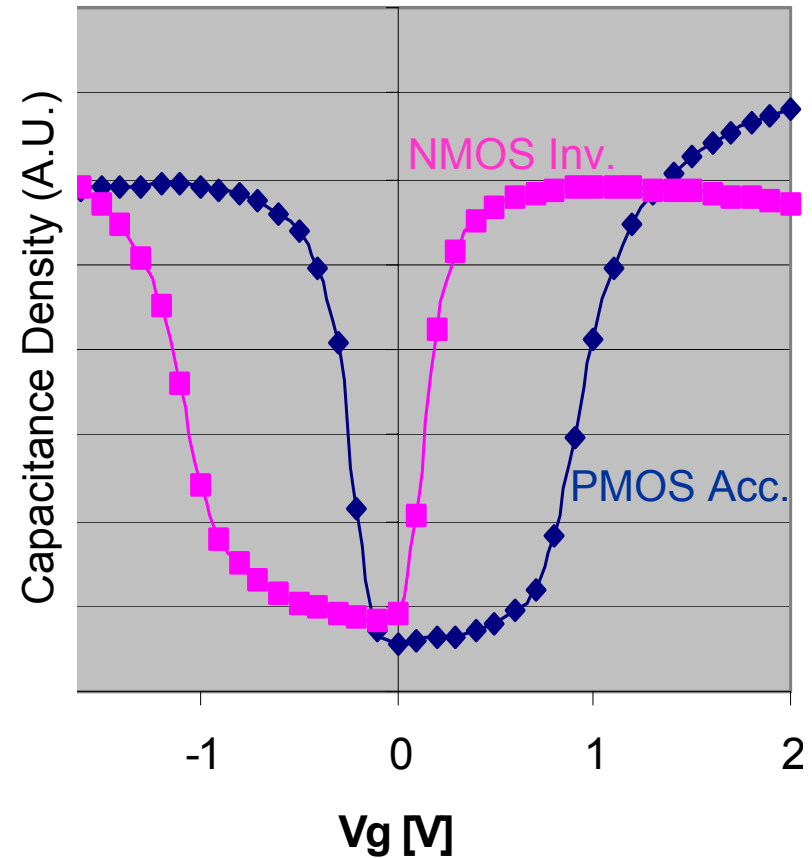

Dense Capacitor Layout Example

 - NMOS 'waffle' type layout shown
 - Poly in green, M1 in red
- Essentially a sheet of poly
 - Non-minimum openings for the silicon contacts (Vss)
 - Field oxide bumps for the poly contacts (Vcc)
- Achieves very high capacitance density with good contact spacing for low resistance and tau




Decoupling Capacitor Design (Cont'd)

- Must be aware of defects and planarity impacts
 - High poly and M1 density may increase the variation in nearby devices
 - Lower poly density means less capacitance per unit of area
 - Need to make trade-offs
 - May have millions of cells
 - Use greater than minimum spacing to reduce defect risk
- Need unit cells which can be easily built into arrays by tools

Package Connection

- C4 bump pitch has not been scaling as fast as transistor technology while current density is scaling
 - Result is increasing current per bump which will stretch reliability limits
- Note that only a few small areas have the highest current
 - Technology and uarch solutions are likely to be needed
- Increased top and second layer metal resources will also be needed

C4 Bump Current Density for a Processor

 


Large di/dt Swings

- So far we have mostly discussed local die noise
- Today's processors use extensive clock gating to reduce power consumption
 - Clocks and clocked elements consume about 50% of active (non-leakage) power
 - A largely inactive processor can have very low active power consumption
 - Can be less than 50% of peak power
- Processors can transition from a low power state to a peak power state as fast as the pipelines can fill
 - For the 90 nm generation, this can be less than 20 cycles (<5 ns) for some processors
 - Processors are approaching 100 W
 - Can have di's as high as 50 A
- Since leakage prevents much decap from being added, such swings will overwhelm die decap very quickly

System Power Delivery


Typical Power Delivery System

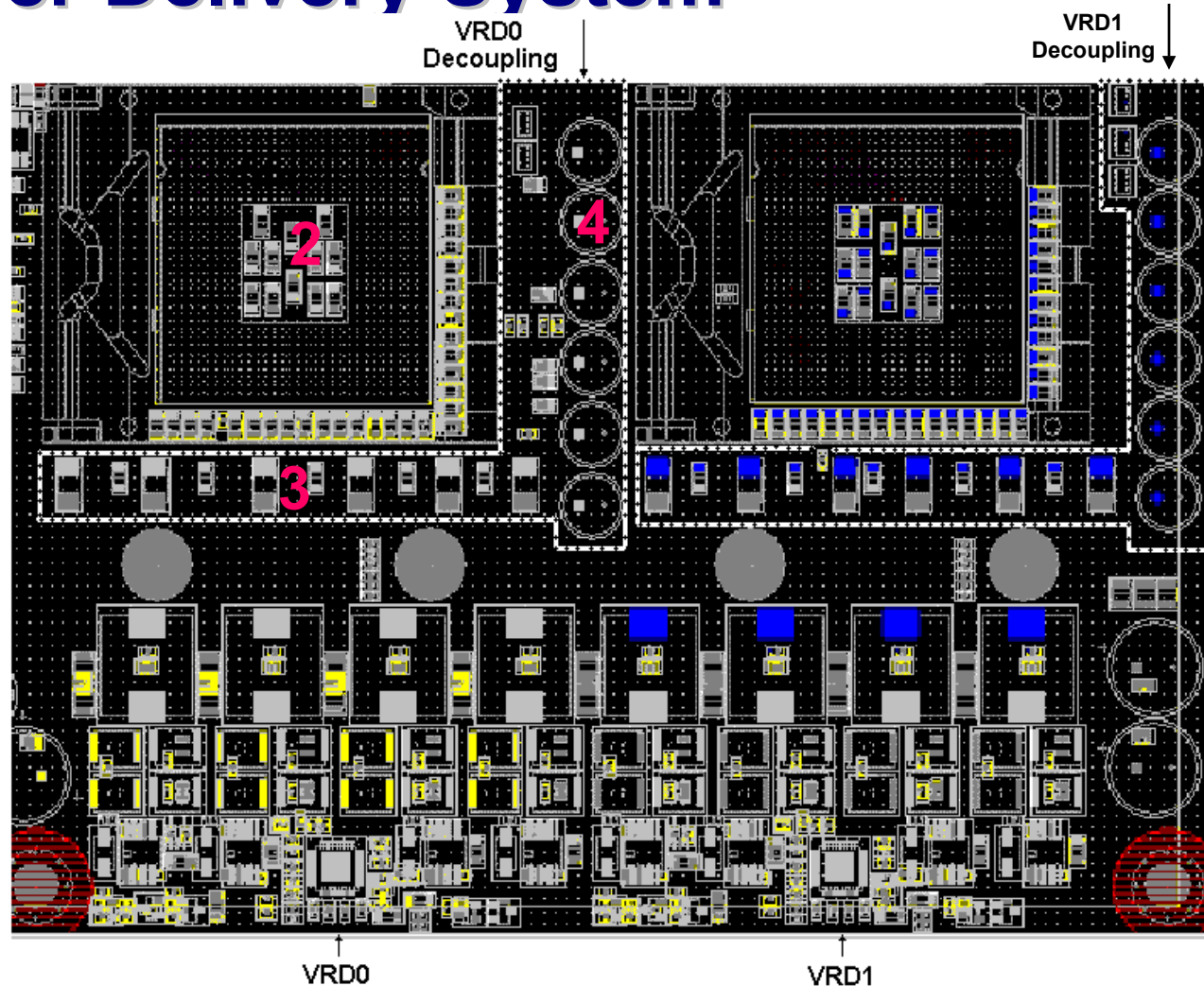- 2 processor MB design shown
- VR current brought in to processors on ~2 sides
- Note the levels of decoupling
 1. Die (MOS)
 2. Back of package
 3. High speed MB
 4. Low speed MB
- VR current brought in to processors on 2 sides to reduce impedance
- VR located close to processor




Packaging Cross-Section

- A sample processor cross-section is shown below
 - May or may not have a heat spreader
 - May have die side capacitors as well as land side
 - Package may have 4-14 layers depending on number of signals and cost structure of market (low-end desktop to high-end server)
 - May have an additional layer of package (interposer) for space transformation and for housing additional components
- Power must penetrate through the socket and package

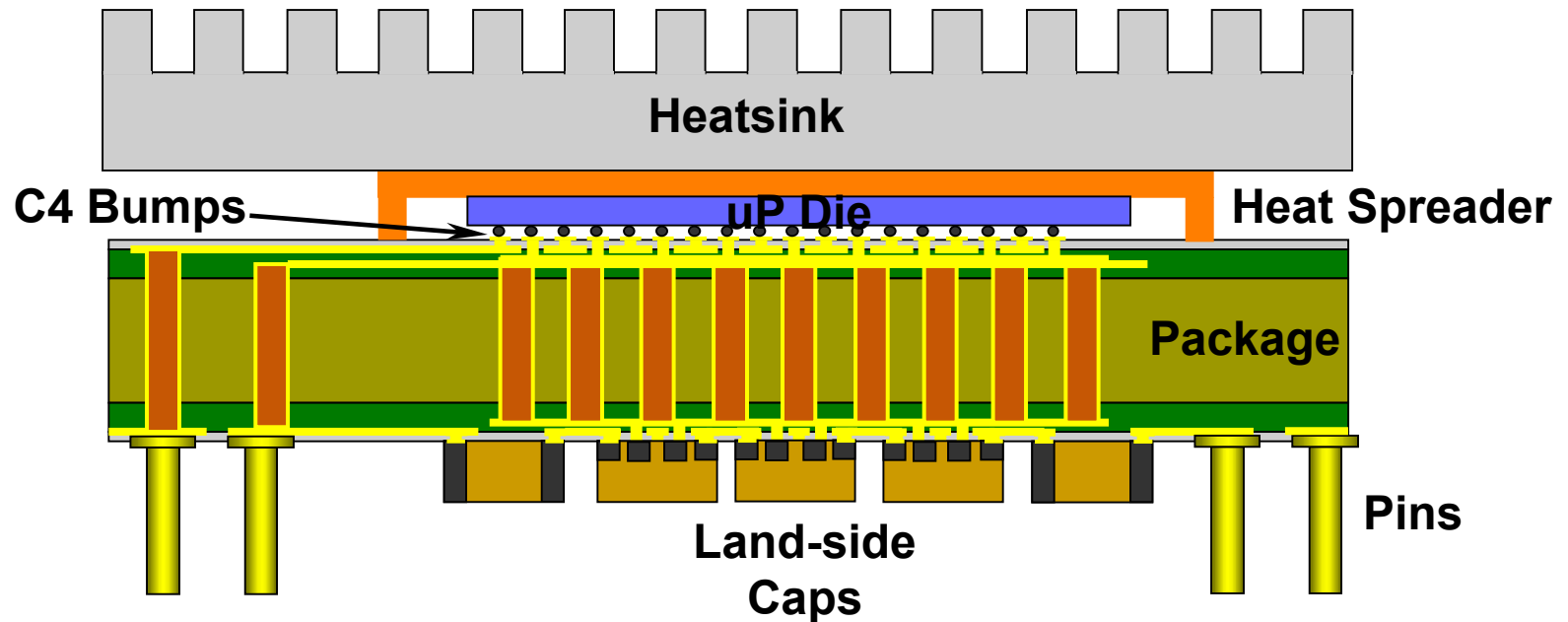


Factors in Determining Decoupling

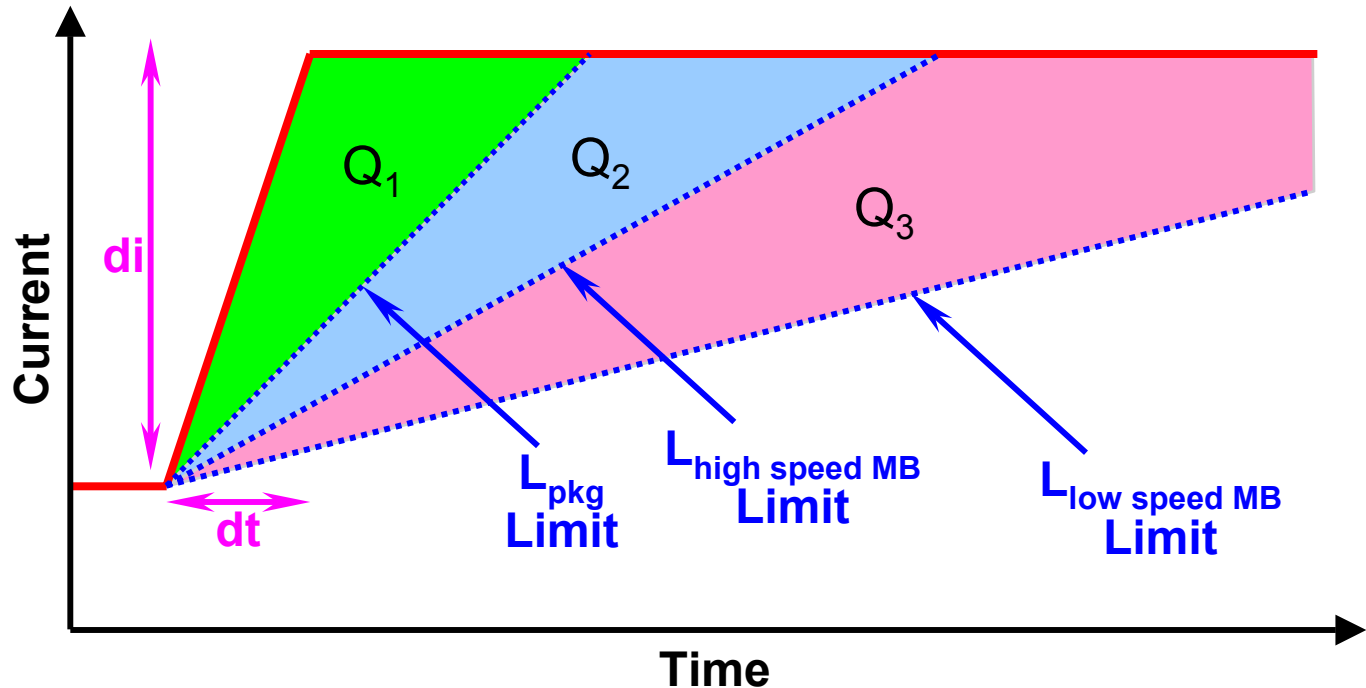


- The area of triangle Q_1 determines the need for die capacitance
 - $C_{die} = Q_1 / \Delta V$; determined by di , dt , L_{pkg} , and the voltage drop target
- The area of triangle Q_2 determines the need for package capacitance
 - $C_{pkg} = Q_2 / \Delta V$; determined by di , L_{pkg} , L_{HSMB} , and the voltage drop target
- The area of triangle Q_3 determines the need for board capacitance
 - $C_{board} = Q_3 / \Delta V$; determined by di , L_{HSMB} , L_{LSMB} , and the voltage drop target

Power Delivery Implications -- dt

 


- Picture shows dt decreased by 2x from previous page -- small impact
- Capacitances are proportional to triangle areas
 - Note that the area of the Q_1 triangle (die capacitance) increases by less than 2x
 - Area of the other triangles (other capacitors) are unaffected
 - See [6] for a treatment of di/dt control

Power Delivery Implications -- I_{max}

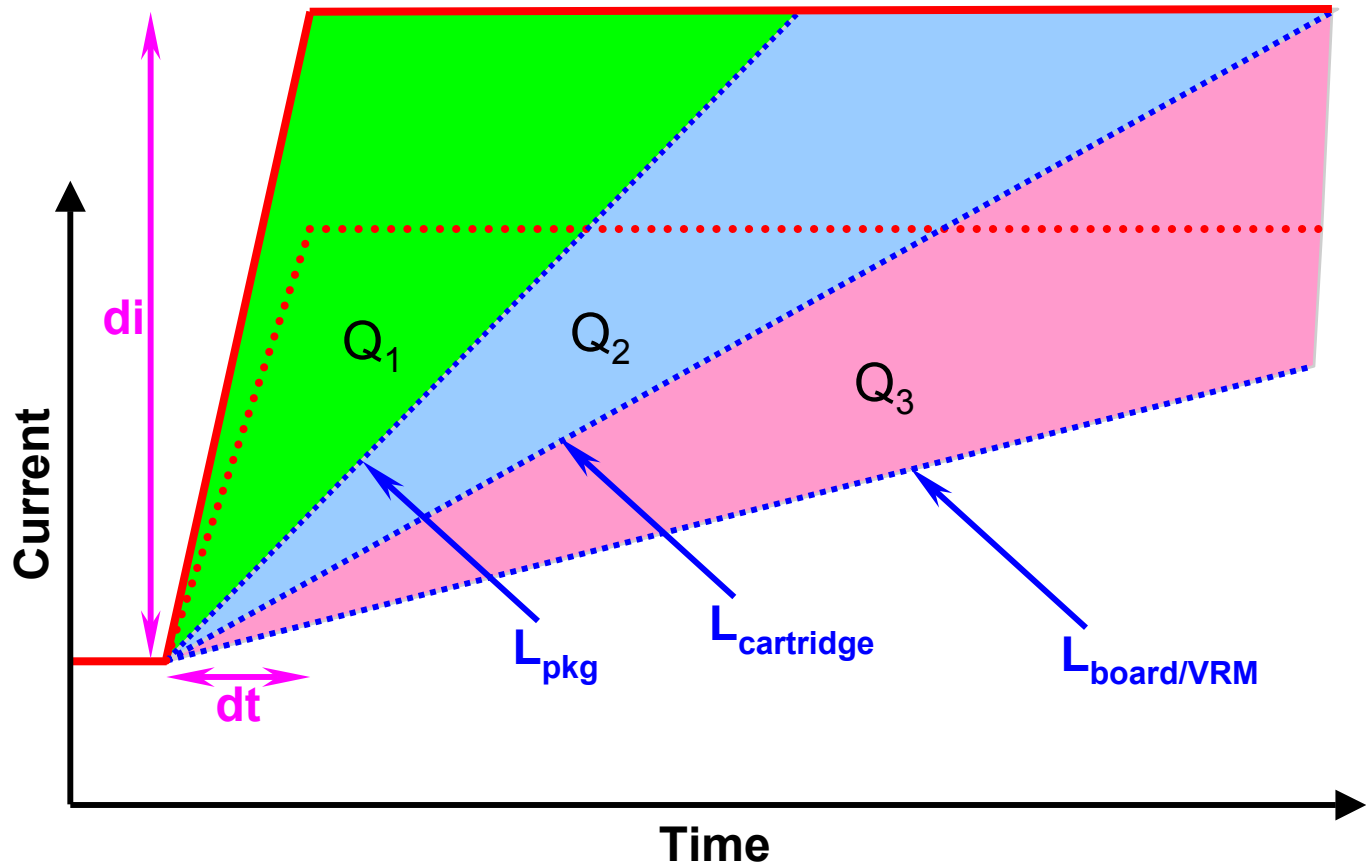



- An increase in d_i has a big impact on all the capacitances each of which is proportional to the triangle areas
 - Square relation for area: 2x increase in d_i increases the triangles by 4x!
 - Even greater increase for Q_1
- Reducing d_i is most effective for voltage control

Capacitor Current Example – 4 Levels

 


- Local voltage minima will be reached at each cross-over point
- Ideal design would have these minima equal
 - More cap levels would allow us to approach a flat impedance vs. frequency curve

Time Response

  

- Graphs shows a simulated voltage response for a system with die, package, board, and VR (bulk) capacitor arrays
- One droop for each cross-over in source of current
 - Example: 1st droop reached when main source passes from die cap to package cap

Frequency Domain System Modeling

 


- Graph of power delivery impedance vs. frequency shown
 - Peak at the resonant frequency of the package/die system
 - Up slope caused by an inductance (ωL)
 - Down slope results from a capacitor ($1/\omega C$)
- Want to move the up slope right (by reducing the inductance)
- Or, move the down slope left (by increasing the capacitance)
 - May be at odds with cost targets!
- Otherwise, may need special techniques to overcome or live with the resonance
 - Clamps, charged pumped capacitors, etc., [5]

Related Topics


Global Layout and Signal Return

- Power grid also supplies return path for signals
- Wide busses (~128b) can switch over an Amp of peak current
- Without adequate return path, inductive noise spikes can disturb signals
 - Additive to capacitive noise for certain patterns
- May need additional power wires to control inductive cross-talk
 - Example: half-shielded scheme shown below
- Robust thick upper metal power gridding can provide return path for lower layer signals
 - Can focus on signal density on lower layers

 

IO Power Delivery


- IO supplies (V_{tt}) are often separated from core power
 - Buffers on processor and chipset run off the IO supply
 - Signals usually referenced to V_{ss} as much as practical
 - Avoids needing to decouple *between* supplies to establish a low impedance return path
- IO supply will need adequate decap and routing
 - Similar analysis to core power
 - Will also need frequency analysis
 - SSN analysis especially important
 - Will need partial (or full) package planes for V_{tt}
 - May need full V_{ss} planes to shield the IO signals

 

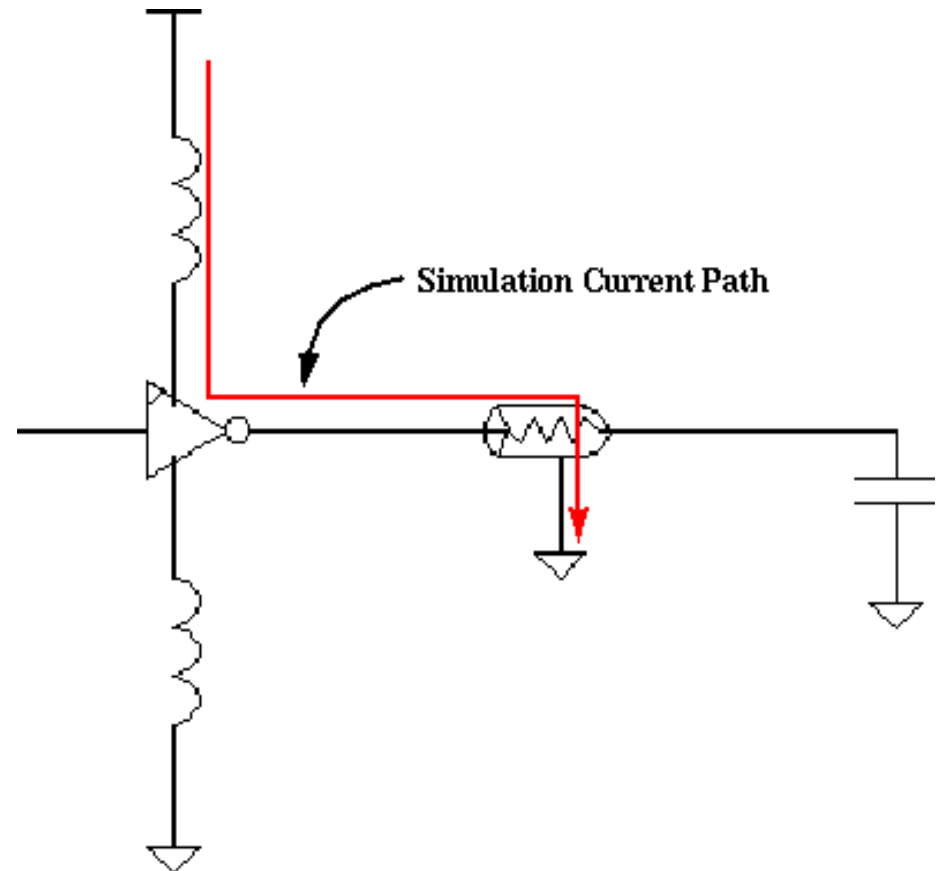Example of Package IO Routing (Crow's Flights)

IO Power Issues

- Simplified models (like the one shown) have a path to ideal ground
 - This is non-physical
- Models must reflect true path including signal return path in the Vss network
 - Only way to properly reflect the interaction of Vdd (core supply) and Vtt (IO supply)
 - IO signaling will inject noise into the core Vss (and vice-versa)
- SSN will probably need control
 - Edge rate control
 - Die and package Vtt decoupling
 - Careful via and bump layout to keep inductive loops small
 - Data inversion to avoid more than 50% 0-1 or 1-0 transitions



Die Power Delivery Scaling

- Transistor current scales on the time axis with channel length (actual, not drawn)
 - Current ramp will speed up by more than 0.7x per generation
- Capacitance density increases by about 1.4x per generation
- Wire resistance per unit length increases by $\sim 2x$ per generation for scaled wires
 - Narrow wire width effects are making this worse
 - Retaining large dimensions for the top 2 layers (or adding layers) needed to offset this problem
 - Ensure good connectivity to top layer power
 - Otherwise RC delay for charge sharing will degrade
- RC per unit of length of power grid is fairly constant
- Unfortunately, RC path delay scaling is forcing more repeaters and increased sizes which exacerbates the problem
 - Bus width increases also compound the issue

Current Density Scaling

- Current density is $C/\text{Area} \cdot fV(\text{AF})$
- C/Area goes up $\sim 1.4x$
- Voltage has been trending down $\sim 0.85x$
 - Future decreases (beyond 90 nm) may be less ($0.9 - 0.95x$) due to leakage limitations
- Processor frequencies have been going up $\sim 1.8x$
 - Less for other types of IC's
 - Less in the future ($\sim 1.6x$)?
- Leakage is increasing total current $\sim 1.1x$
- Activity factors \sim constant in worst areas
 - Decreasing on a full chip basis as cache area increases
- Overall current density increasing by $\sim 2x$
 - Forcing power metal needs to increase each generation

References

- [1] Ng, et al., Table 1, paper 9.6, IEDM 2002
- [2] Ishikawa, et al., paper 9.7, IEDM 2002
- [3] Kedzierski, et al., paper 10.1, IEDM 2002
- [4] Krivokapic, et al., paper 10.7, IEDM 2002
- [5] Ang, et al., "An On-chip Voltage Regulator using Switched Decoupling Capacitors." paper 26.7, ISSCC 2000
- [6] Grochowski, E.; Ayers, D.; Tiwari, V. "Microarchitectural Simulation and Control of Di/Dt-Induced Power Supply Voltage Variation". *Proceedings of the Eighth International Symposium on High Performance Computer Architecture, 2002*. Page(s): 7-16.