

High Speed Circuits That Work: The Road From Ideas to Products


EE 371 Lecture 15
Sam Naffziger
Hewlett Packard Co.

Overview

- Goal: Provide some insight into the design process for high speed circuits taken from concept to customer ship
- I'll use a block on the soon-to-ship McKinley (Itanium® 2) microprocessor as a case study
 - What motivated and supported some of the circuit innovation (\$\$)
 - What the design process involved (blood, sweat and tears)
 - Some of the issues that arose (weeping and gnashing of teeth)
 - How the silicon actually behaved (very un-SPICE-like)
- The 1st level data cache (L1D) is a great example
 - 16KB, 4 way set associative, physically tagged, 1 cycle load to use (0 cycle penalty)
- But first, some background on the microprocessor

McKinley Overview

 - .18 μm bulk, 6 layer Al process
- 8 stage, fully stalled in-order pipeline
- Symmetric six integer-issue design
- IA32 execution engine integrated
- 3 levels of cache on-die totaling 3.3MB
- 221 Million transistors
- ECC / parity protection on all memory arrays
- 130W @1GHz, 1.5V



McKinley vs. other 64b .18 μ m processors

(sources provided in final slide)


	McKinley	USIII	EV7	Power 4 (2 cores)
Frequency (GHz)	1.0	1.05	1.0-1.2	1.3
Pipe stages (mpb)	8 (6)	14 (8)	9 (~11)	12 (~11)
Sustainable Int BW	6 / cycle	3 / cycle	4/cycle	3/cycle
FP units	2/cycle	2/cycle	2/cycle	2/cycle
On chip cache	3.3MB 4 arrays	96KB 2 arrays	1.8MB 3 arrays	1.7MB 2.5 per core
D Cache read BW	64GB/s	16.8	19.2	41.6 / core
Die size (mm ²)	421	244	397	400 est.
Core size (no IO, only lowest level caches)	142	206	115	100 est.
Power (Watts)	130	75	125	125

Background

- Memory access is a very important aspect of processor design
 - Bandwidth must support full instruction streaming
 - Latency must be low enough to minimize pipeline stalls
 - Contemporary processors have a 1-2 cycle load to use penalty for the 1st level cache. I.e. **LD addr→A** followed by **Add A,B** incurs a stall
- Lately, most microprocessors have embraced out of order execution (PA, Power4, Alpha, Pentium)
 - Can do useful work even if the main pipe is stalled
 - Can significantly mitigate cache latency impacts
 - Witness the PA8700 with a 1.5MB *first level* data cache. Latency is 3 cycles, but more than offset by the benefits of the large cache
- BUT, the Itanium architecture is resistant to out of order implementations
 - The whole template based instruction format
 - Worse, ubiquitous predicates – any instruction can be predicated off

Background: Predication

Traditional Architectures

 


IA-64




- Removes branches, converts to predicated execution
 - Executes multiple paths simultaneously
- Increases performance by exposing parallelism and reducing critical path
 - Better utilization of wider machines
 - Reduces mispredicted branches

Background

- Customers don't care about my chip's architectural handicaps, they just pay for performance (and cause my company to pay for my lab!)
- So, if we can't use out of order execution to help with the memory latency problem *and* we still need a GHz+ processor design, the only option is to innovate
 - A six-issue machine makes the load-to-use penalty problem even *more* acute⇒
A single cycle cache would be big win
- The first big barrier was the distance issue


 


EE 371 lecture 15

 


Background

- To be truly single cycle, a cache must *receive a new address* and *deliver the dependent data* in one cycle
 - If our best repeated interconnect (for a bunch of 64b busses) is 50ps/mm, the situation in our floorplan means our *whole cycle* is consumed by wire!
- Solution: Split the caches into multiple independent arrays
 - First level instruction cache, data cache, with the floating point going directly to the larger, second level cache
 - Tight coupling between address source and data delivery
- I'll focus on the L1D cache for this talk although the L1I is similar

  


Cache Access Timing

 - High speed caches usually take the following form (only for latency insensitive or very power sensitive designs does the data array access wait on the tag)
- If a cycle time is only 20-24 FO4 inverters, this is *a lot* to get done
 - The TLB access is a problem – wide CAM + RAM access
 - 38 bits is a lot to compare
 - Just the way mux, data message and deliver is generally a full cycle ...



Cache Access Timing

- So, I set out to attack the following areas:
 - TLB access + TAG compare
 - 76 bit CAM, followed by a RAM access followed by a 38b compare
 - Then buffer up the compare result to drive the way multiplexors for a 64b datapath
 - Way mux + data message (this is *way* harder than you might think) + delivery
 - Must deliver either big or little endian data, must zero extend sub-word loads, must align subword loads, must bypass store data in and merge it with load data!
 - Data array access – speed enables a larger cache
 - Timing should match TLB/TAG plus compare
- With only a single cycle to work with, I only get *one* clock edge!
 - If I use the falling edge clock, I'm victimized by phase asymmetries, as well as clock skew which has its impact doubled for phase budgets (bad)
 - Everything must be either self-timed or dataflow => domino

 


Level 1 TLB Overview

- Takes a 64b Virtual address in, compares to stored translations and generates a physical translation
- 32 Entries, each of which stores 115 bits
 - 52 virtual address bits
 - 24 Region ID bits
 - 38 physical address bits
 - 1 Valid bit
- Fixed 4 kB page size
- 2 independent CAM ports, each with shared CAM lines for both virtual and physical address CAMs
 - This saves wires in the critical dimension
- 2-level dynamic CAM with a self timed path to create a monotonic-rising match signal.


Level 1 TLB Pulsed Bit Lines

 - The virtual address is presented to the CAM cell on a pair of dual-rail pulsed bit lines.
- Pulsed bit lines eliminate precharge drive fights and allow for the removal of clocked evaluate FETs on downstream dynamic gates.




Level 1 TLB CAM Cell

 - One write port +2 CAM ports
- CAM bit lines are pulsed
- Cell discharges match[01] when its value does not match the incoming address
- Cell layout is $27.3 \mu\text{m}^2$ ($4.8 \times$ standard RAM cell)
- Stability is not an issue, since the pass-fets only turn on during a write.
- Charge sharing is not an issue since 3 of every 4 pulldown stacks don't evaluate.




Level 1 TLB Self-Timed Path


- CAM is wide (90 address bits \times 2 pulldown stacks per cell)
- We use a full-rail hierarchical dynamic structure for speed.
6 CAM cells \rightarrow 2-input NAND \rightarrow 4-wide OR \rightarrow 2-input NAND
- The TLB calculates a monotonic-falling match signal, but the TAG needs a monotonic-rising match signal. Thus, a “dummy” self-timed path is used to create a hard edge.
- The “Johnson NOR” is used to account for PVT and clock route variations between the two halves of the TLB.
- The self-timed path consumes 20% of the path delay in margin.

 

Level 1 TLB Access

 

Next: Tag access and Compare

 

Next: Tag access and compare

- So, I can get the TLB access down to $\frac{1}{4}$ of a cycle
- For the TAG compare. I'm stuck with either:
 - Doing a true compare: xnor + 38b AND gate, or
 - Doing a precharge pulldown !compare, then either self-time it, or wait for a clock
 - Invent something new -> prevalidated the tags
- The idea is to store a one-hot vector in the tags instead of a physical address
 - This vector points to the TLB entry that contains the translation for the physical address of this tag

 


Figure 3: Prevalidated Cache Tag Design Load Critical Path


- The 38 bit compare gets replaced with a 32b (# of TLB entries) domino AND/OR gate.
- *Preserves the monotonicity* for the subsequent way mux and rotate
- Much faster and smaller

Prevalidated Tag Advantages

- Faster TLB outputs
 - No TLB RAM read is required
- Faster TAG compare
 - Dual rail compare + 38-bit dynamic AND
 - vs.
 - Dual rail miscompare + 38-bit OR + a hard clock edge
 - vs.
 - **Single rail compare + 32-bit dynamic OR**
- Less wiring in both the TLB and TAG arrays
 - 38 address bits \times 2 rails per bit
 - vs.
 - **32 bits \times 1 rail per bit**

Prevalidated Tag Array

 
- >1 kB array
 - 64 indices \times 4 ways \times (32b one-hot vector +1 valid bits)
- 2 independent read ports
- Two-level dynamic full-rail RAM read for speed
 - 8 RAM cells \rightarrow inverter \rightarrow 8-wide pulldown.
 - No sense-amp.



- SER detection is provided in several ways:
 - Cache is write-through, so spurious invalidations are OK
 - The ways are interleaved so that double-bit errors either affect two different ways or two different indices.
 - Multi-hot detector for detecting errors.

Next: Data Array Access

- For a data array access, we must take the same address bits that go to the TAG, decode them into individual word lines and column selects
 - Pull one 64b word out of the 512 in each way
- Sense the value stored in the tiny RAM cell and send it all the way across the array
 - Traditional implementations use a low swing (100-200mV) bitline which is allowed to develop for a fixed time interval and then sensed with a diff-amp
 - Too much timing overhead for the tiny budget this cache has => full swing bitlines

 


Level 1 Data Array Overview


- 16 kB of data + 2kB of parity
 - 4 ways of 4kB each
- Parity protected at the byte level to allow sub-word stores
- 2 independent load ports and 2 store ports.
- Supports 3 operations
 - Loads (8B)
 - Stores (1B - 8B)
 - Fills (64B)
- Array is approximately 50% RAM-area efficient
 - Tradeoff area for speed.
- $1280\mu\text{m} \times 1770\mu\text{m}$ in a $0.18\mu\text{m}$ process.

Level 1 Data Array RAM Cell

 - 6T-RAM cell is made dual-ported by independently controlling the word lines for the pass fets.
- Single-ended full-rail dynamic reads.
- Cell uses large NFETs for speed.
- Stability is afforded by a quick discharge of a lightly loaded bit line during a single ended read.
- Cell layout is $7.01 \mu\text{m}^2$ ($1.25 \times$ standard RAM cell)




L1D Data Array Local-Global Dump Circuit

 

Level 1 Data Array Decoder

 - Decode is performed hierarchically.
- Pulsed decoders allow for the removal of clocked-evaluate FETs in downstream dynamic logic.
- Static AND gate provides noise immunity on long pulse routes.



A domino decoder was too slow → use a self-timed “annihilation gate” for speed

 


figure 4
EE 371 lecture 15

Level 1 Data Array Decoder

- An “annihilation gate” is:
 - Fast: 1 domino gate delay for a large fan-in AND
 - Small: A single FET per input
 - Low input load
 - Scary!



 


figure 4
AGATE_SIM1 SL <858BSIM3 SCIPINFO>

 


Way Selection and Data Massage


 


Rotating Way Mux

 
- This block accomplishes 3 main tasks:
 - Way Selection
 - Byte Rotation (for sub 8B loads)
 - Little Endian / Big Endian Transformations
- A series of monotonicity-preserving static gates are used to perform the first stages of muxing.
 - Provides noise immunity
 - Allows phase stealing
- A pulse-precharged distributed pulldown network is used for the final stage.



Rotating Way Mux

  


 - Painstaking Layout is critical
- RC delay
- Coupling
- Size and features



Finally: Delivering the Data

 
- This requires careful wire engineering
 - With all the parallelism in the execution unit, we had to use every last metal 4 track
 - Since the cache data delivery is the latest arrival, we could demote a couple other tracks down to metal 2 to widen up the cache busses
 - Almost a 50ps (5% of cycle) gainer




Power

One bitslice
in the
address mux
and output
buffer circuit

Cache->Integer Bypass

 


Level 1 Cache Photo

 

Silicon Results

 - Most everything worked as expected – careful engineering pays off
 - No coupling or supply noise problems
 - No pulse width or self-timing problems
- Only significant issues had to do with unexpected processing conditions for the FETs combined with sensitive, high speed circuits




Conclusions

- There are *plenty* of opportunities to innovate in VLSI design (and get paid for doing it!)
 - As long as silicon technology keeps advancing and changing, there are new and interesting ways to exploit it
 - As long as information technology keeps driving our economy, people will pay for performance and features
- A few keys to finding the best way to contribute:
 - Study the landscape; what's been done before, the capabilities of the technology, what customers want
 - Understand the architecture and performance issues, not just circuits
 - Pick one or two strategic areas to do something truly new (it will always be more challenging than you thought)
 - For this example, we had the pre-validated tag, single-ended RAM and annihilation gates, the rest was just tenacious engineering
 - Engineer the heck out of it; leave no stone unturned searching for problems and applying airtight solutions

Backup

- Pulse generator circuit

 

Backup: Coupling Noise Solutions

- Top level cache read bitlines: 2mm, min space, precharged-pulldown, metal 4
- Anti-miller devices reduce crosstalk induced droops
- Noise margins improved significantly with a small performance penalty

