

# High Speed Circuits That Work: The Road From Ideas to Products

EE 371 Lecture 15  
Sam Naffziger  
Hewlett Packard Co.

EE 371 lecture 15

1

## Overview


- Goal: Provide some insight into the design process for high speed circuits taken from concept to customer ship
- I'll use a block on the soon-to-ship McKinley (Itanium® 2) microprocessor as a case study
  - What motivated and supported some of the circuit innovation (\$\$)
  - What the design process involved (blood, sweat and tears)
  - Some of the issues that arose (weeping and gnashing of teeth)
  - How the silicon actually behaved (very un-SPICE-like)
- The 1<sup>st</sup> level data cache (L1D) is a great example
  - 16KB, 4 way set associative, physically tagged, 1 cycle load to use (0 cycle penalty)
- But first, some background on the microprocessor

EE 371 lecture 15

2
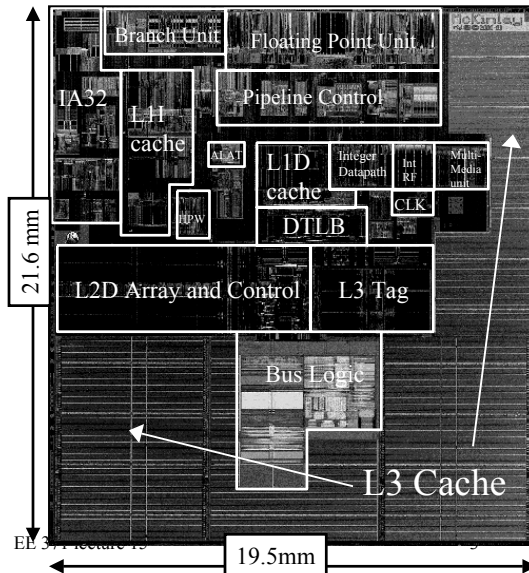
# McKinley Overview

- .18μm bulk, 6 layer Al process
- 8 stage, fully stalled in-order pipeline
- Symmetric six integer-issue design
- IA32 execution engine integrated
- 3 levels of cache on-die totaling 3.3MB
- 221 Million transistors
- ECC / parity protection on all memory arrays
- 130W @1GHz, 1.5V



## McKinley vs. other 64b .18μm processors


(sources provided in final slide)

	McKinley	USIII	EV7	Power 4 (2 cores)
Frequency (GHz)	1.0	1.05	1.0-1.2	1.3
Pipe stages (mpb)	<b>8 (6)</b>	14 (8)	9 (~11)	12 (~11)
Sustainable Int BW	<b>6 / cycle</b>	3 / cycle	4/cycle	3/cycle
FP units	2/cycle	2/cycle	2/cycle	2/cycle
On chip cache	<b>3.3MB 4 arrays</b>	96KB 2 arrays	1.8MB 3 arrays	1.7MB 2.5 per core
D Cache read BW	<b>64GB/s</b>	16.8	19.2	41.6 / core
Die size (mm <sup>2</sup> )	<b>421</b>	244	397	400 est.
Core size (no IO, only lowest level caches)	142	206	115	100 est.
Power (Watts)	<b>130</b>	75	125	125 4

# Background

- Memory access is a very important aspect of processor design
  - Bandwidth must support full instruction streaming
  - Latency must be low enough to minimize pipeline stalls
    - Contemporary processors have a 1-2 cycle load to use penalty for the 1<sup>st</sup> level cache. I.e. **LD addr→A** followed by **Add A,B** incurs a stall
- Lately, most microprocessors have embraced out of order execution (PA, Power4, Alpha, Pentium)
  - Can do useful work even if the main pipe is stalled
  - Can significantly mitigate cache latency impacts
    - Witness the PA8700 with a 1.5MB *first level* data cache. Latency is 3 cycles, but more than offset by the benefits of the large cache
- BUT, the Itanium architecture is resistant to out of order implementations
  - The whole template based instruction format
  - Worse, ubiquitous predicates – any instruction can be predicated off


## Background: Predication

 

- Removes branches, converts to predicated execution
  - Executes multiple paths simultaneously
- Increases performance by exposing parallelism and reducing critical path
  - Better utilization of wider machines
  - Reduces mispredicted branches

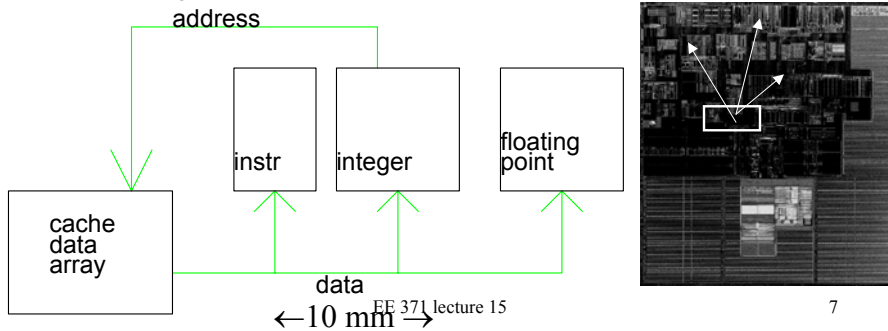
# Background

- Customers don't care about my chip's architectural handicaps, they just pay for performance (and cause my company to pay for my lab!)
- So, if we can't use out of order execution to help with the memory latency problem *and* we still need a GHz+ processor design, the only option is to innovate
  - A six-issue machine makes the load-to-use penalty problem even *more* acute⇒  
A single cycle cache would be big win
- The first big barrier was the distance issue



 
# Background

- To be truly single cycle, a cache must *receive a new address* and *deliver the dependent data* in one cycle
  - If our best repeated interconnect (for a bunch of 64b busses) is 50ps/mm, the situation in our floorplan means our *whole cycle* is consumed by wire!
- Solution: Split the caches into multiple independent arrays
  - First level instruction cache, data cache, with the floating point going directly to the larger, second level cache
  - Tight coupling between address source and data delivery
- I'll focus on the L1D cache for this talk although the L1I is similar


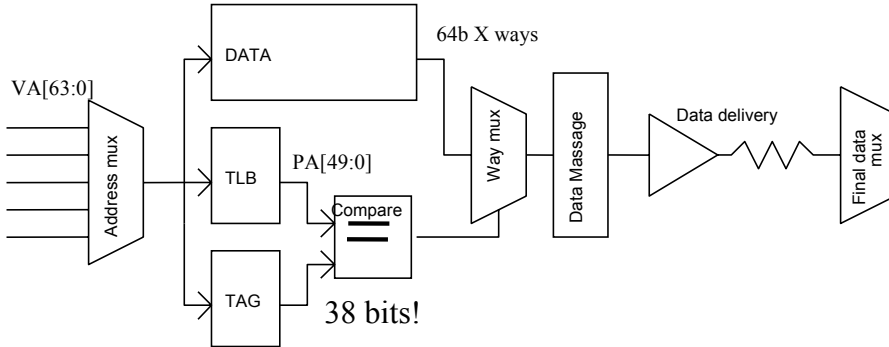
# Cache Access Timing

- High speed caches usually take the following form (only for latency insensitive or very power sensitive designs does the data array access wait on the tag)
- If a cycle time is only 20-24 FO4 inverters, this is *a lot* to get done
  - The TLB access is a problem – wide CAM + RAM access
  - 38 bits is a lot to compare
  - Just the way mux, data message and deliver is generally a full cycle ...




EE 371 lecture 15

9
 
# Cache Access Timing

- So, I set out to attack the following areas:
  - TLB access + TAG compare
    - 76 bit CAM, followed by a RAM access followed by a 38b compare
    - Then buffer up the compare result to drive the way multiplexors for a 64b datapath
  - Way mux + data message (this is *way* harder than you might think) + delivery
    - Must deliver either big or little endian data, must zero extend sub-word loads, must align subword loads, must bypass store data in and merge it with load data!
  - Data array access – speed enables a larger cache
    - Timing should match TLB/TAG plus compare
- With only a single cycle to work with, I only get *one* clock edge!
  - If I use the falling edge clock, I'm victimized by phase asymmetries, as well as clock skew which has its impact doubled for phase budgets (bad)
  - Everything must be either self-timed or dataflow => domino



EE 371 lecture 15

10

## Level 1 TLB Overview


- Takes a 64b Virtual address in, compares to stored translations and generates a physical translation
- 32 Entries, each of which stores 115 bits
  - 52 virtual address bits
  - 24 Region ID bits
  - 38 physical address bits
  - 1 Valid bit
- Fixed 4 kB page size
- 2 independent CAM ports, each with shared CAM lines for both virtual and physical address CAMs
  - This saves wires in the critical dimension
- 2-level dynamic CAM with a self timed path to create a monotonic-rising match signal.

EE 371 lecture 15

11
 
## Level 1 TLB Pulsed Bit Lines

- The virtual address is presented to the CAM cell on a pair of dual-rail pulsed bit lines.
- Pulsed bit lines eliminate precharge drive fights and allow for the removal of clocked evaluate FETs on downstream dynamic gates.




EE 371 lecture 15

12
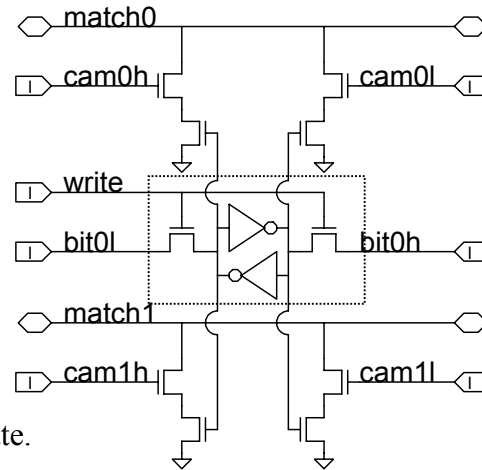
## Level 1 TLB CAM Cell

- One write port +2 CAM ports
- CAM bit lines are pulsed
- Cell discharges match[01] when its value does not match the incoming address
- Cell layout is  $27.3 \mu\text{m}^2$  ( $4.8 \times$  standard RAM cell)
- Stability is not an issue, since the pass-fets only turn on during a write.
- Charge sharing is not an issue since 3 of every 4 pulldown stacks don't evaluate.




EE 371 lecture 15

13
 
## Level 1 TLB Self-Timed Path


- CAM is wide (90 address bits  $\times$  2 pulldown stacks per cell)
- We use a full-rail hierarchical dynamic structure for speed.  
6 CAM cells  $\rightarrow$  2-input NAND  $\rightarrow$  4-wide OR  $\rightarrow$  2-input NAND
- The TLB calculates a monotonic-falling match signal, but the TAG needs a monotonic-rising match signal. Thus, a “dummy” self-timed path is used to create a hard edge.
- The “Johnson NOR” is used to account for PVT and clock route variations between the two halves of the TLB.
- The self-timed path consumes 20% of the path delay in margin.




EE 371 lecture 15

14

# Level 1 TLB Access

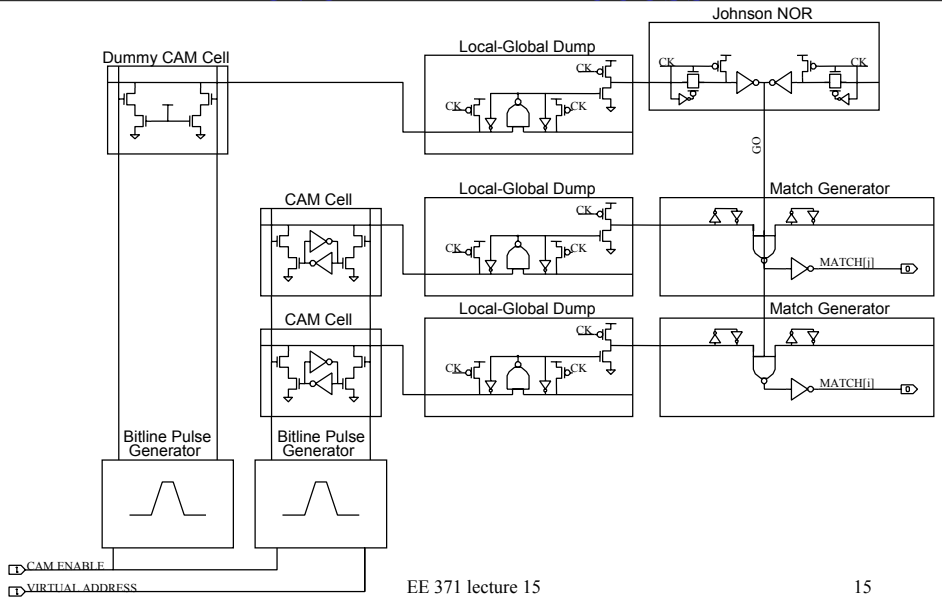

# Next: Tag access and Compare

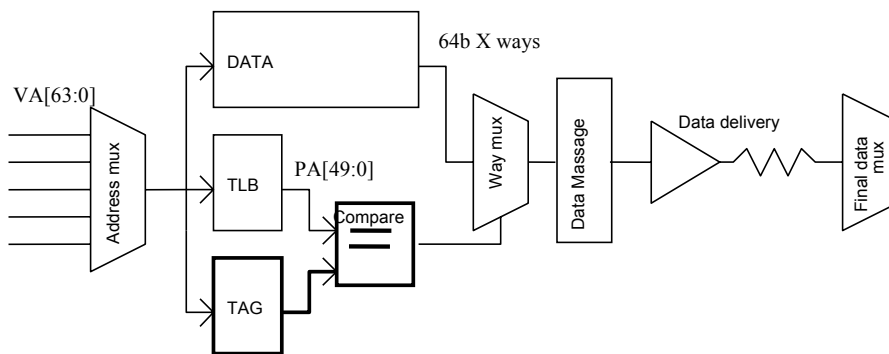

## Next: Tag access and compare

- So, I can get the TLB access down to  $\frac{1}{4}$  of a cycle
- For the TAG compare. I'm stuck with either:
  - Doing a true compare: xnor + 38b AND gate, or
  - Doing a precharge pulldown !compare, then either self-time it, or wait for a clock
  - Invent something new -> prevalidated the tags
- The idea is to store a one-hot vector in the tags instead of a physical address
  - This vector points to the TLB entry that contains the translation for the physical address of this tag

 


Figure 3: Prevalidated Cache Tag Design Load Critical Path  
EE 371 lecture 15

- The 38 bit compare gets replaced with a 32b (# of TLB entries) domino AND/OR gate.
- *Preserves the monotonicity* for the subsequent way mux and rotate
- Much faster and smaller

17

## Prevalidated Tag Advantages

- Faster TLB outputs
  - No TLB RAM read is required
- Faster TAG compare
  - Dual rail compare + 38-bit dynamic AND
  - vs.
  - Dual rail miscompare + 38-bit OR + a hard clock edge
  - vs.
  - **Single rail compare + 32-bit dynamic OR**
- Less wiring in both the TLB and TAG arrays
  - 38 address bits  $\times$  2 rails per bit
  - vs.
  - **32 bits  $\times$  1 rail per bit**

EE 371 lecture 15

18



## Level 1 Data Array Overview


- 16 kB of data + 2kB of parity
  - 4 ways of 4kB each
- Parity protected at the byte level to allow sub-word stores
- 2 independent load ports and 2 store ports.
- Supports 3 operations
  - Loads (8B)      – Stores (1B - 8B)
  - Fills (64B)
- Array is approximately 50% RAM-area efficient
  - Tradeoff area for speed.
- $1280\mu\text{m} \times 1770\mu\text{m}$  in a  $0.18\mu\text{m}$  process.

EE 371 lecture 15

21

 
## Level 1 Data Array RAM Cell

- 6T-RAM cell is made dual-ported by independently controlling the word lines for the pass fets.
- Single-ended full-rail dynamic reads.
- Cell uses large NFETs for speed.
- Stability is afforded by a quick discharge of a lightly loaded bit line during a single ended read.
- Cell layout is  $7.01 \mu\text{m}^2$  ( $1.25 \times$  standard RAM cell)




22
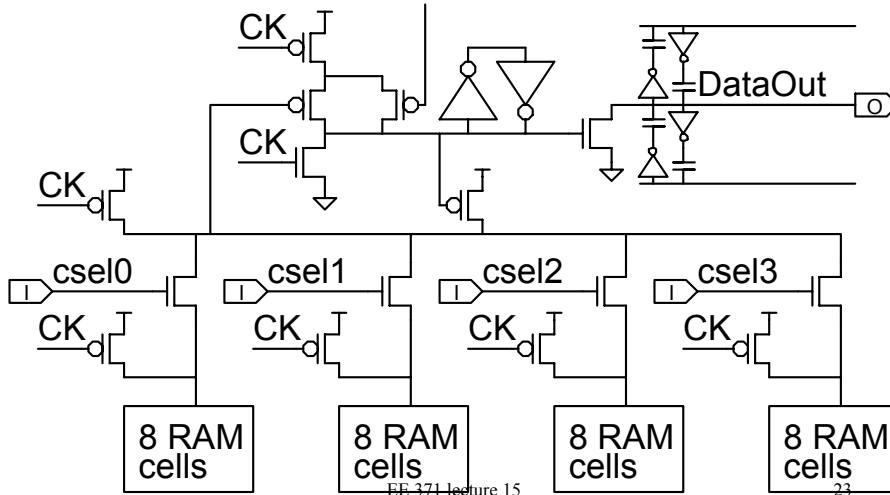
# L1D Data Array Local-Global Dump Circuit




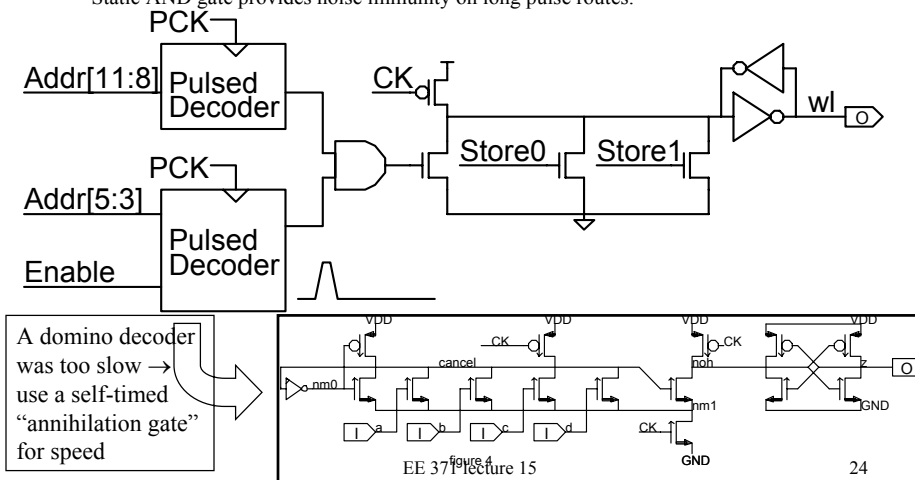
## Level 1 Data Array Decoder

- Decode is performed hierarchically.
- Pulsed decoders allow for the removal of clocked-evaluate FETs in downstream dynamic logic.
- Static AND gate provides noise immunity on long pulse routes.



  
# Level 1 Data Array Decoder

- An "annihilation gate" is:
  - Fast: 1 domino gate delay for a large fan-in AND
  - Small: A single FET per input
  - Low input load
  - Scary!




25

# Way Selection and Data Massage

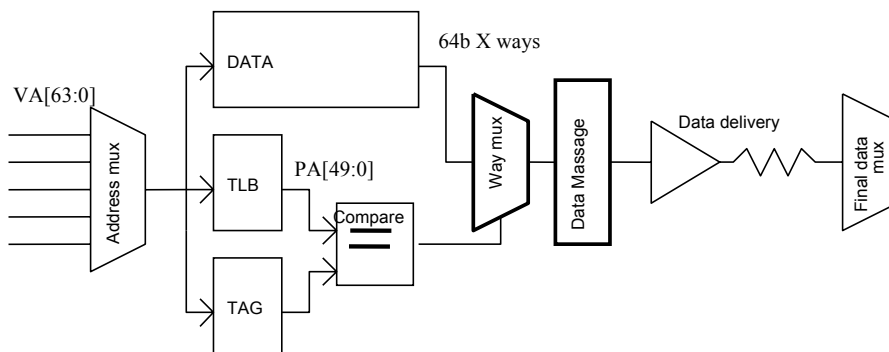

 
# Rotating Way Mux

- This block accomplishes 3 main tasks:
  - Way Selection
  - Byte Rotation (for sub 8B loads)
  - Little Endian / Big Endian Transformations
- A series of monotonicity-preserving static gates are used to perform the first stages of muxing.
  - Provides noise immunity
  - Allows phase stealing
- A pulse-precharged distributed pulldown network is used for the final stage.



EE 371 lecture 15


27

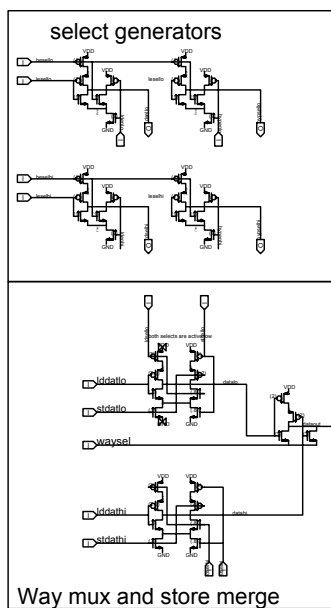

# Rotating Way Mux


- Painstaking Layout is critical
- RC delay
- Coupling
- Size and features

EE 371 lecture 15

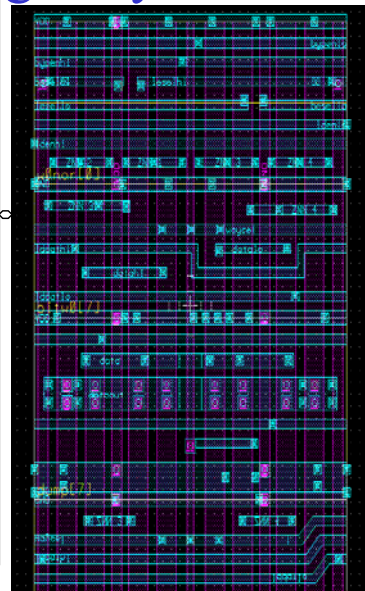

 
## Finally: Delivering the Data


- This requires careful wire engineering
  - With all the parallelism in the execution unit, we had to use every last metal 4 track
  - Since the cache data delivery is the latest arrival, we could demote a couple other tracks down to metal 2 to widen up the cache busses
    - Almost a 50ps (5% of cycle) gainer



29

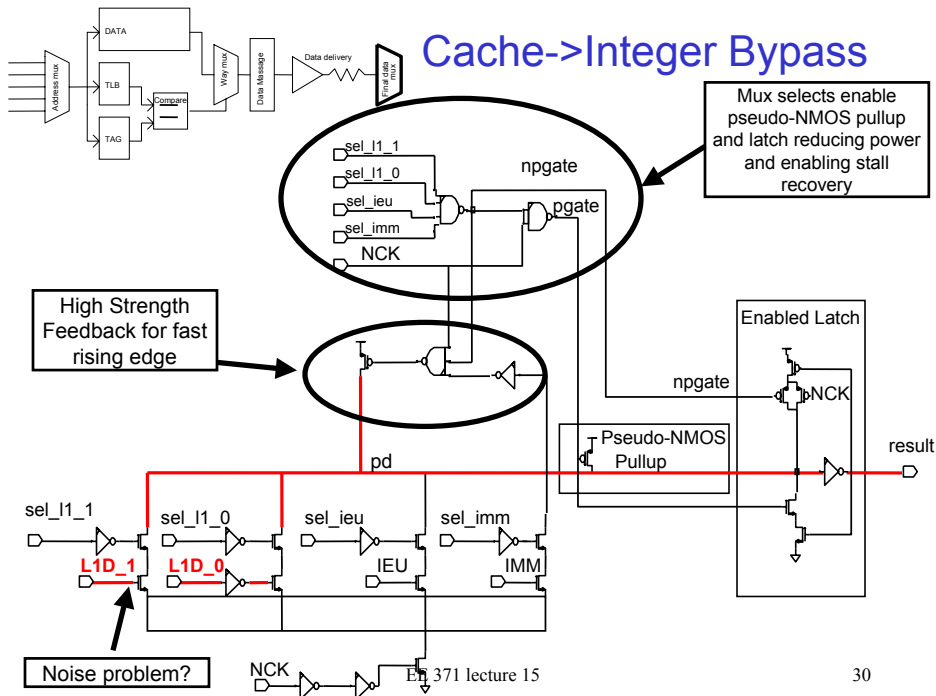


# Level 1 Cache Photo

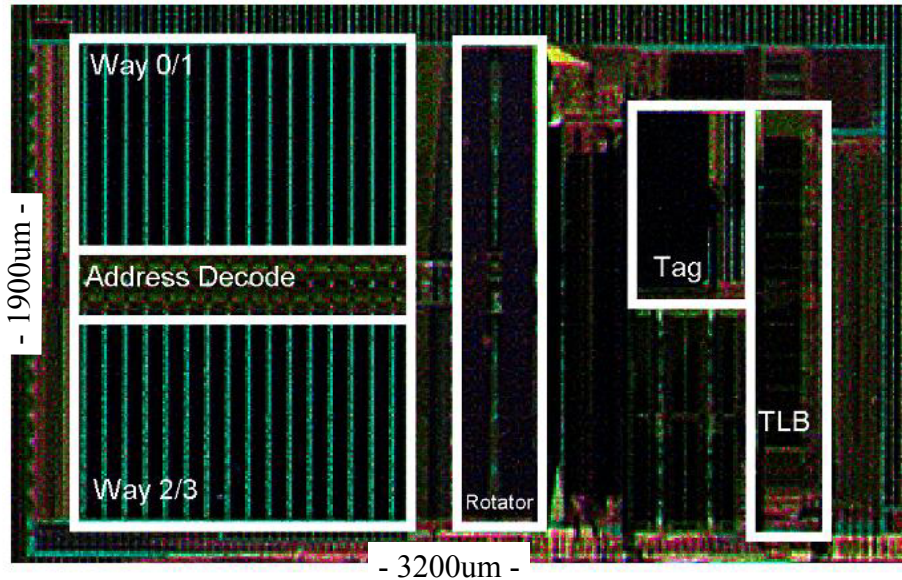
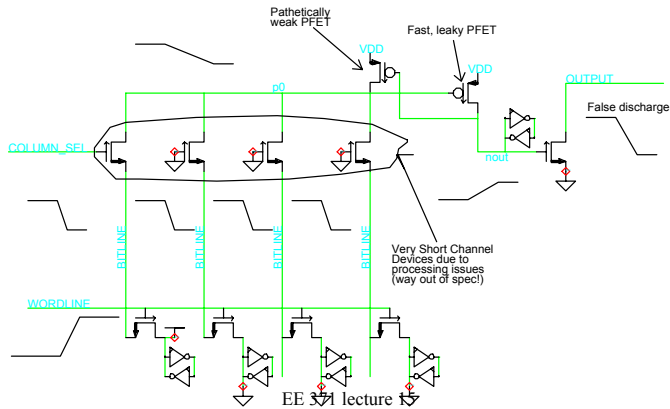
## Silicon Results

- Most everything worked as expected – careful engineering pays off
  - No coupling or supply noise problems
  - No pulse width or self-timing problems
- Only significant issues had to do with unexpected processing conditions for the FETs combined with sensitive, high speed circuits




# Conclusions

- There are *plenty* of opportunities to innovate in VLSI design (and get paid for doing it!)
  - As long as silicon technology keeps advancing and changing, there are new and interesting ways to exploit it
  - As long as information technology keeps driving our economy, people will pay for performance and features
- A few keys to finding the best way to contribute:
  - Study the landscape; what’s been done before, the capabilities of the technology, what customers want
    - Understand the architecture and performance issues, not just circuits
  - Pick one or two strategic areas to do something truly new (it will always be more challenging than you thought)
    - For this example, we had the pre-validated tag, single-ended RAM and annihilation gates, the rest was just tenacious engineering
  - Engineer the heck out of it; leave no stone unturned searching for problems and applying airtight solutions

## Backup

- Pulse generator circuit

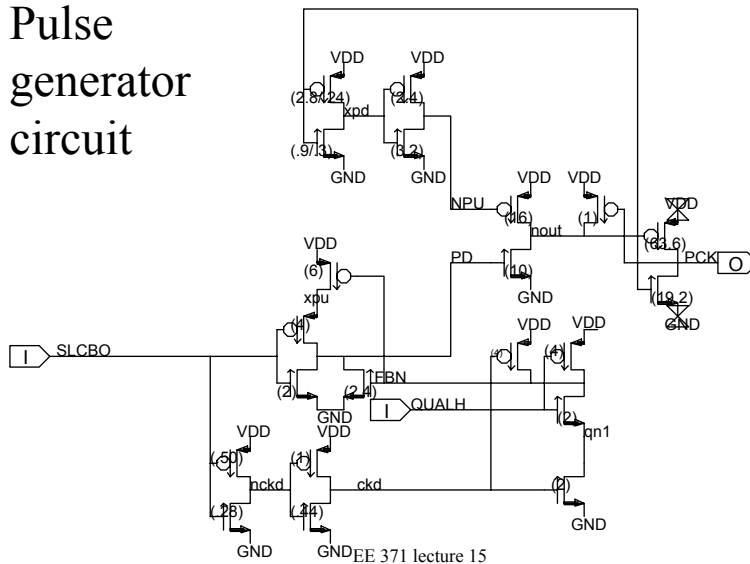

## Backup: Coupling Noise Solutions

- Top level cache read bitlines: 2mm, min space, precharged-pulldown, metal 4
- Anti-miller devices reduce crosstalk induced droops
- Noise margins improved significantly with a small performance penalty

