
EE371

Asynchronous Circuits
or
Circuits Without Clocks:
What makes Them Tick?

Jo Ebergen
Sun Microsystems Laboratories
jo.ebergen@sun.com

Copyright © 2004 by Sun Microsystems Laboratories


A Historical Perspective

- Clocked versus clockless
- The first computers: clocked or clockless?
- ENIAC('46), ACE('46), EDVAC ('46)
- Enablers for clocked design: Boolean Algebra and FSMs
- A big problem in early days: making *reliable* computers
- Clock is convenient in design and verification
- Terminology: non-synchronous, asynchronous, speed-independent, self-timed, delay-insensitive

Why No Clock?

- Speed
 - Average vs worst-case behavior
- Avoid timing problems related to clock
 - Crossing clock domains, synchronization problems
 - Clock distribution, skew, jitter
- Modularity
 - Reusability
 - Composability
 - Incremental improvement
 - Ex: “Macromodules Project” (Clark & Molnar), “Self-Timed Systems” (Seitz)

An Example: Macromodules ('66-'74)

 


More: Why No Clock?

- Low power
 - Portable electronics
 - Budget constraint: total energy, not cycle time
- Architectural freedom
 - Concurrency at any grain size
- Robustness
 - Correct operation over a large range of process, voltage, and temperature variations
- Reduced electromagnetic radiation
 - Spread spectrum versus isolated peaks


A Live Demo

 - Pipelined “food” processing
- Clocked and clockless version




Clocked “Food Processing”

 - TICK: process food
- TOCK: move plate to successor




Clockless “Food Processing”

 - Two types of plates
- Red plate = stage with data item
- White plate = empty stage
- Red plates move forward
- White plates move backward



Repeat These Actions

 - TAKE: Take RED plate from predecessor
(and give WHITE plate)
- EAT: Process food
- GIVE: Give RED plate to successor
(and take WHITE plate)




To Notice

- Clock period must be long enough for slowest person for worst food
- *Clockless pipeline adjusts speed to person and food being processed*
- Clocked pipeline spends energy with every tick or tock, even when there is no food on plate
- *Clockless pipeline spends energy only when food must be processed*
- Clocked pipeline must have the same frequency as the source and sink, to prevent overflow or underflow
- *Clockless pipeline has automatic overflow and underflow protection*

FIFOs

 
- FIFOs as a basis for pipelines
- Simple local communication



- Red plates move to the right
 - Red plates are data items
- White plates move to the left
 - White plates are often “empty stages”
 - But can be data items as well

Local Communication

 - Synchronization at each boundary
- Only one rule:
**IF (left plate is red AND right plate is white)
THEN exchange plates**




**instantaneous
event**

Many Implementations

- There are many circuits to implement this synchronization
 - Muller C-elements
 - GasP modules
 - Many others...
- Challenge is to design circuit family that is efficient and versatile
 - Small delay
 - Small area
 - Little energy consumption
 - Can do pipelines with Branch, Merge, Fork, Join
- Each circuit family has different signalling conventions
 - Bundled data: Control (clock) says when data must be valid
 - Validity embedded in data encoding

Bundled Data Signaling

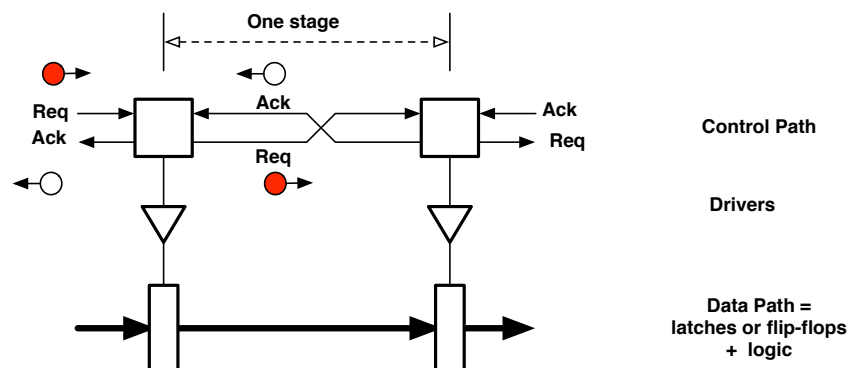- Request indicates arrival of red plate
 - Request is bundled with data
 - Request indicates validity of data
- Acknowledge indicates arrival of white plate




About Bundled Data Signaling

- Control modules produce “clock” signal
 - when needed
 - where needed
- Implementation is similar to clocked design, but with local “clocks”
 - Max and min-time constraints remain
- When data path has logic, insert extra delay in request wire that matches delay in logic
 - Often matched delay is worst-case delay
 - Matched delay may depend on data, if overhead is low
- Use of flip-flop or latch depends on signaling scheme


Two-Track Four-Phase Signalling

 - Two-track: separate wire for Request and Acknowledge
- Four-phase: four transitions in cycle
- Also known as “return-to-zero” signalling
- Fits well with standard logic gates
- Many variations exist
- Often has long cycle time




Two-Track Two-Phase Signaling

 - Two-phase: two transitions per cycle
- Also known as “transition” signalling
- Uneasy fit with standard logic gates
- Short cycle time for simple pipelines
 - Long cycle time for anything else




Single-Track, Four-Phase Signalling

 - Combines best of both worlds
 - Fits with standard gates
 - Short cycle time
- Uses one tri-state wire, which needs keeper
 - Watch out for noise issues



Kiting Delay

 - Control is usually ahead of data
 - head start is called “kiting delay”
- What matters: setup and hold constraints for storage elements






Validity Encoded in Data

- As opposed to bundled data signaling
- There is no separate signal that says when data must be valid
- Data validity is encoded in data
 - Receiver detects when new data word has arrived
 - Requires completion detection, which may add to cycle time
- Ex: m-out-of-n encoding
 - 1-out-of-2 encoding = dual-rail encoding
 - Often already present in domino gates
 - 1 transition per 2 wires for one bit of information
 - 1-out-of-4 encoding
 - 1 transition per 4 wires for two bits of information
- Can be used with two-phase or four-phase signalling


Muller C-Element

   - Also known as Rendezvous or JOIN
- David Muller (60s)
- If both inputs are 1 (0), then output becomes 1 (0)
 - If inputs differ, output remains the same
- C-element = “AND” of transitions




Synchronization with C-Element

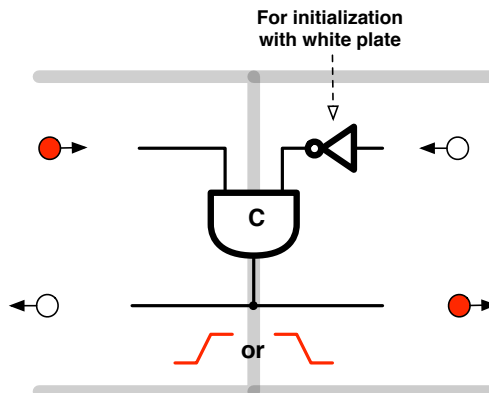- Uses two-track, two-phase signaling
- Every transition counts
- Just control:




A C-element FIFO

 - A simple micropipeline (Sutherland 88)
- Data must be stored with every transition
 - Makes data path more complex
- Cycle time is 5 gate delays
 - An optimized version has cycle time of 3 gate delays



An asP* FIFO

 
- asynchronous symmetric *Pulse Protocol*
- Simplest control consists of SR latches and AND gates
- Control produces pulses with fixed width (3, 5, 7, .. gate delays)
- Two-track, Four-phase signaling
- Storage elements may be simple latches



E = Empty
F = False
S = Set
R = Reset



GasP

 - Fast derivative of asP*, hence name
- Single-track, four-phase signaling
- Produces pulses with fixed width (3, 5, 7, .. gate delays)
- All gates have equal delay (sizing is important!)





About Speed

  - Forward latency of stage
- Reverse latency of a stage
- Cycle time of a stage: $L_f + L_r$
- Forward latency of linear FIFO: $n * L_f$
- Reverse latency of linear FIFO: $n * L_r$
- Throughput of FIFO: $1 / (L_f + L_r)$




Measuring Speed

  - Throughput of ring FIFOs
- “Token-limited”
 - Red plates never have to wait
 - Throughput determined by L_f
 - And # red plates
- “Bubble-limited”
 - White plates never have to wait
 - Throughput determined by L_r
 - And # white plates
- Limited by an interface stage
 - Interface stage acts as bottle neck
 - Throughput = throughput interface stage




Speed Example

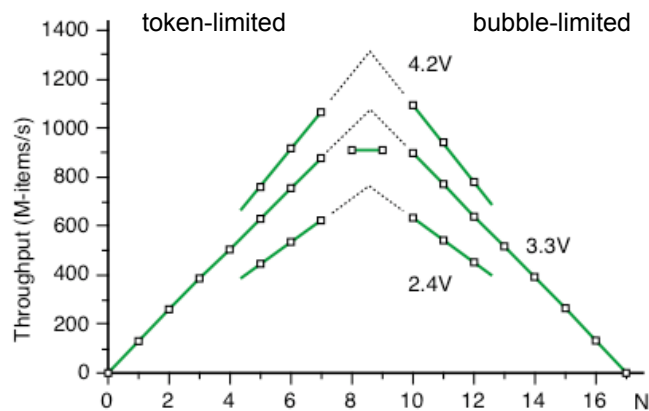- Measurement from chip, asP* FIFO (600nm, 3.3V)




Power Example

 - Measured from chip, asP* FIFO (600nm, 3.3V)
- Power proportional to throughput!



A Energy/Performance Comparison

 
Normalized Energy Versus Cycle Time (Latch Loads Only)



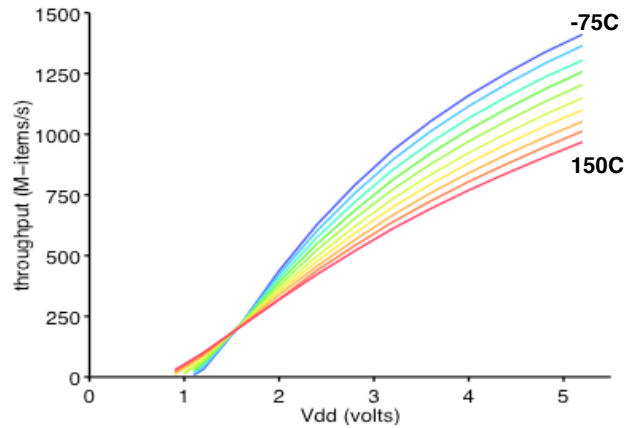1. Assumption: All gates have equal delay
2. Magic clock is infinite string of inverters with min cycle time of 6 gate delays
3. C-element FIFO has cycle time of 3 gate delays



Robustness

- Max throughput vs supply voltage and temperature
- C-element FIFO (600nm, 3.3V)




Reduced Radiation

  - Frequency spectrum of the same chip operating in sync and async mode



Average-Case Speed

 - From asP* counterflow pipeline chip (600nm, 3.3V)
- Cycle time depends on data




Architectural Freedom

- Can more freedom lead to better FIFOs?
- Better = lower power?
- Better = less latency?
- More concurrency?
- Different grain sizes (i.e. cycle times)?

A Non-Linear FIFO

- The idea:

 

- What is energy consumption?
- What is latency?
- What is cycle time of leaf cell (compared to root cell)?

Concluding Remarks

- Sun's UltraSPARCIII has async FIFOs
- Elsewhere..
 - Philips, IBM, Intel, DARPA, ..
 - Academia
 - Start-ups
- Many challenges remain
 - CAD tools
 - Education
 - Creating order in "chaos of concurrency"

Resources

- Async Design Group at Sun Labs
 - research.sun.com/async/
- Async Logic Home Page
 - www.cs.man.ac.edu/async/
- Ivan Sutherland's Turing Award lecture 1989
- "Computers Without Clocks" Scientific American, Aug. 2002
- ASYNC conference series