
Lecture 3

FIR Design and Decision Feedback Equalization

Mark Horowitz
Computer Systems Laboratory
Stanford University
horowitz@stanford.edu

Copyright © 2007 by Mark Horowitz, with material from
Stefanos Sidiropoulos, and Bora Nikolic


Readings

- Readings (for next lecture on adders)
 - Chandrakasan Chapter 10.1-10.2.10
 - Harris Taxonomy of adders (either paper on web or WH 10.2 to 10.2.2.9)
- Overview:
 - Finish up some timing issues from high-speed links
 - Your project will be the design of a decision feedback equalizer, but most of the hardware will be the same as a normal FIR filter. So the lecture will start talking about FIR filter design, and then will go into the added issues with building a DFE. **WARNING:** I am not an expert in this area, so there might be better ideas out there (and some bugs in these notes)
 - The FIR notes are from Bora Nikolic at UCB.

I/O Clocking Issues


- Remember the clocking issues:
 - Long path constraint (setup time)
 - Short path constraint (hold time)
 - Need to worry about them for I/O as well
- For I/O need to worry about a number of delays
 - Clock skew between chips
 - Data delay between chips
 - Can be larger than a clock cycle (speed of light)
 - Clock skew between external clock and internal clock
 - This can be very large if not compensated
 - It is essentially the insertion delay of the clock tree

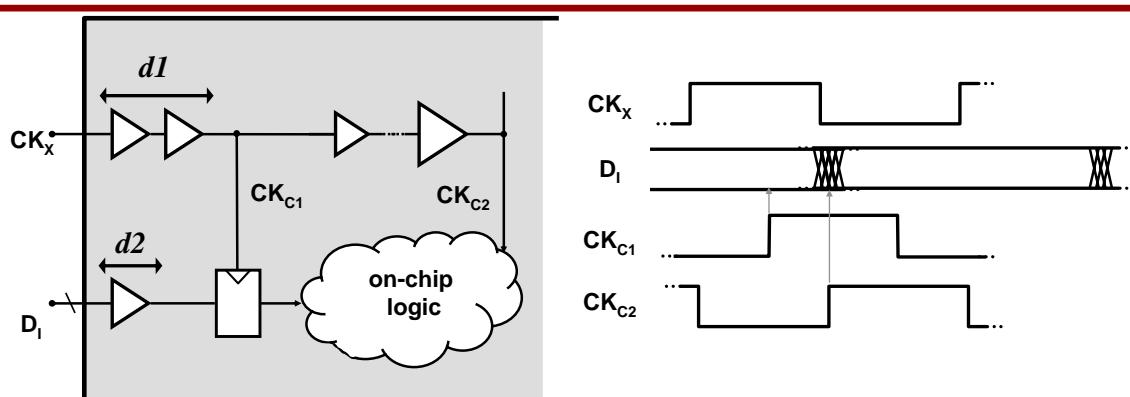System Clocking: Simple Synchronous Systems




- Long bit times compared to on chip delays:
 - Rely on buffer delays to achieve adequate timing margin

PLLs: Creating Zero Delay Buffers

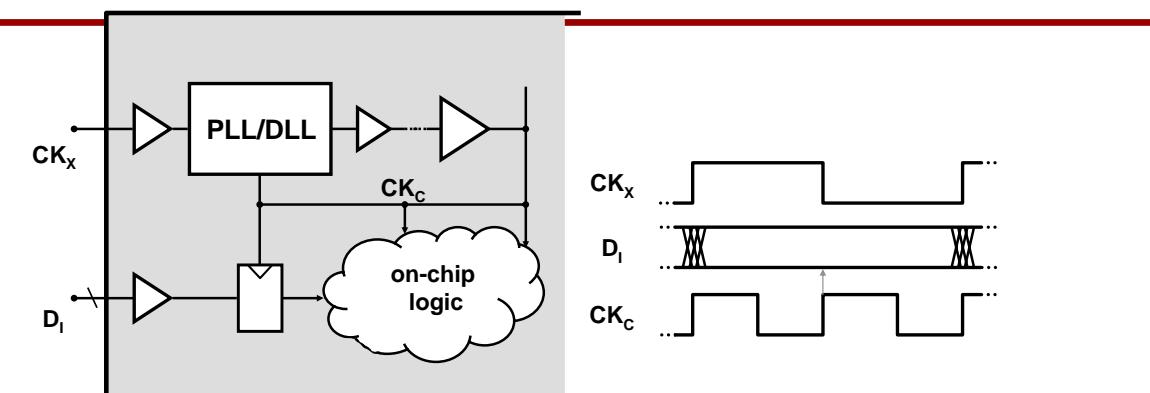

- On-chip clock might be a multiple of system clock:
 - Synthesize on-chip clock frequency
- On-chip buffer delays do not match
 - Cancel clock buffer delay

Used to Argue About PLLs vs DLLs

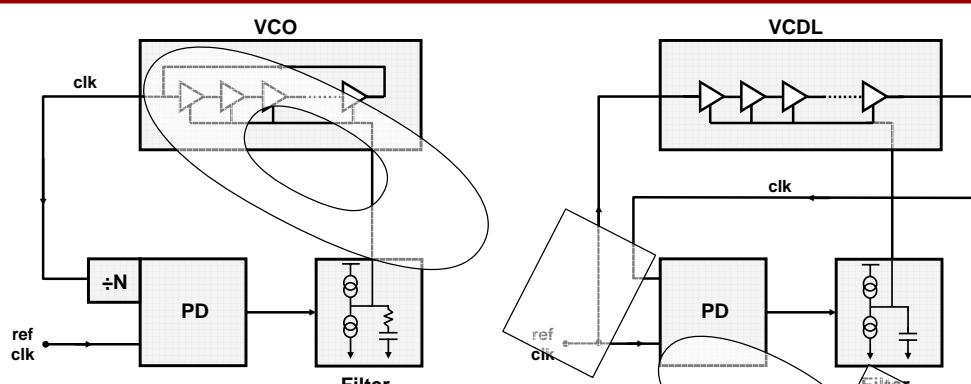


- Second/third order loop:
 - ⇒ Stability is an issue
 - ⇒ Frequency synthesis easy
 - ⇒ Ref. Clk jitter gets filtered
 - ⇒ Phase error accumulates
- First order loop:
 - ⇒ Stability guaranteed
 - ⇒ Frequency synthesis problematic
 - ⇒ Ref. Clk jitter propagates
 - ⇒ Phase error does not accumulate

After Many Years of Research


- And many papers and products
- One can mess up either a DLL or PLL
 - Each has its own strengths and weaknesses
- If designed correctly, either will work well
 - Jitter will be dominated by other sources
- Many good designs have been published
 - It is now a building block that is often reused
 - We all have our favorites, mine is the dual-loop design
- And yes, people use ring oscillators
 - Still an open question about how much LC helps (in system)

Clocking Structures

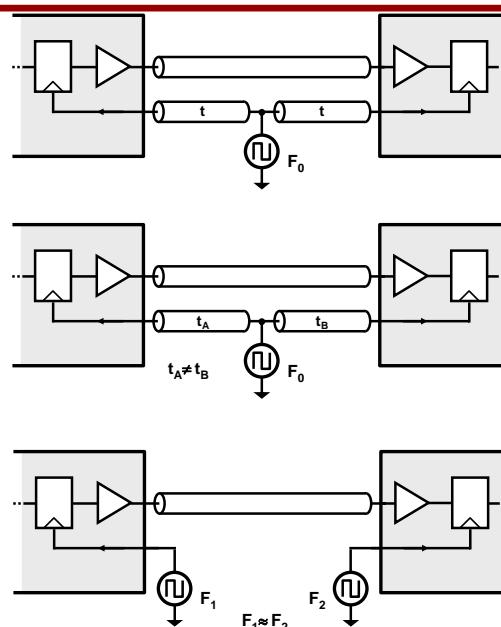- Synchronous:
Same frequency and phase
 - Conventional buses
- Mesochronous
Same frequency, unknown phase
 - Fast memories
 - Internal system interfaces
 - MAC/Packet interfaces
- Plesiochronous:
Almost the same frequency
 - Mostly everything else today




Source Synchronous Systems

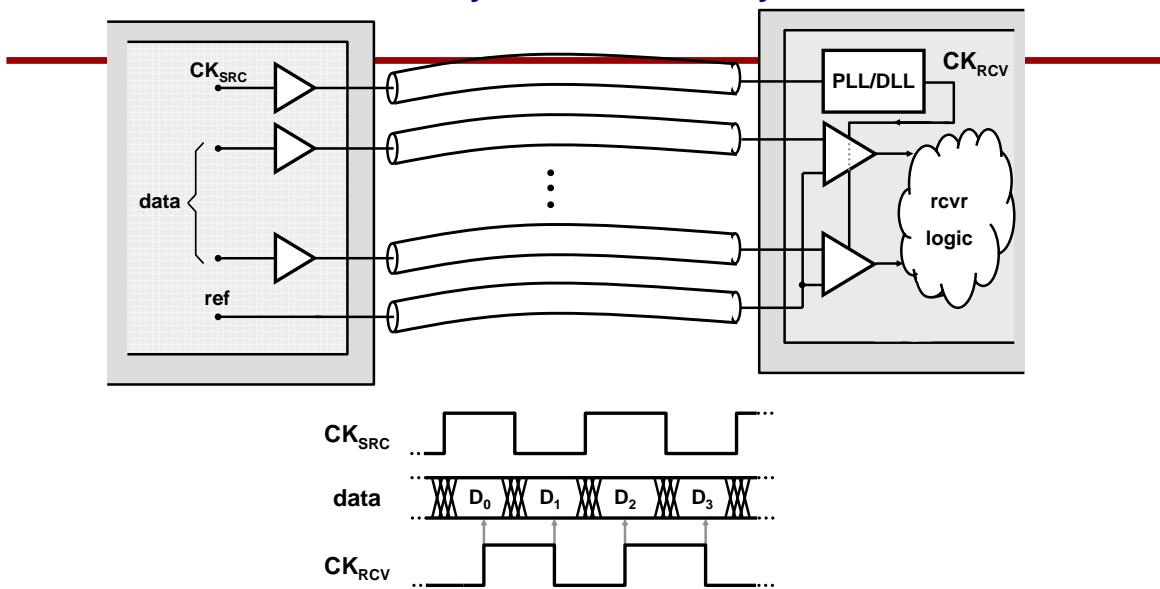

- Position on-chip sampling clock at the optimal point
i.e. maximize “timing” margin

Serial Link Circuit

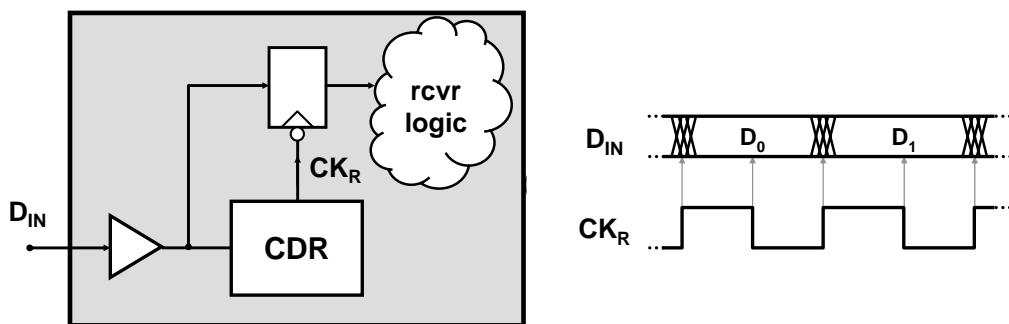


- Recover incoming data fundamental frequency
- Position sampling clock at the “optimal” point

Finite Impulse Response Filters

- In DSP filters are done in the discrete time domain
 - Instead of $x(t)$, x_n
- Filter is formed by convolution of input with filter $h(t)$
 - Output at every point is the sum:
$$y[n] = a_0 x[n] + a_1 x[n-1] + a_2 x[n-2] + \dots + a_N x[n-N+1]$$
- This is generally called an FIR filter
 - Finite impulse response filter (output depends only on input)
 - IIR filters have output depend on prior output
 - Infinite impulse response (like RC circuits)


Transversal Filter
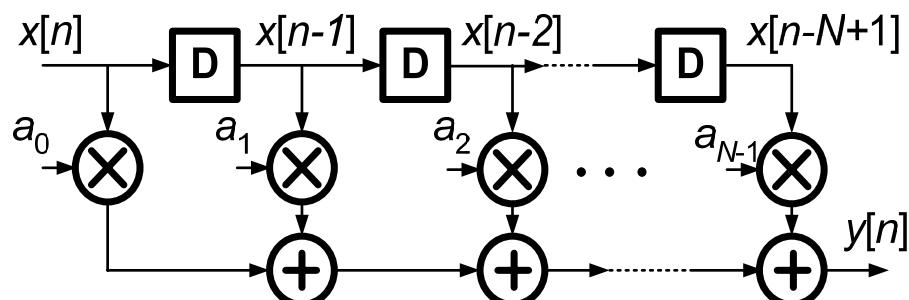
$$y[n] = a_0 x[n] + a_1 x[n-1] + a_2 x[n-2] + \dots + a_N x[n-N+1]$$



Critical Path

- Digital FIR

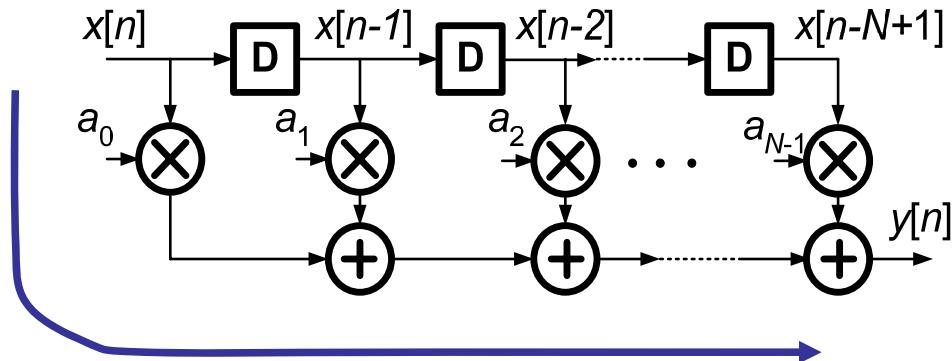

$$T = T_{mult} + (N-1)T_{add}$$

One Point To Keep In Mind


- We are working with small signal values
 - For binary (2 PAM) x is in $\{0,1\}$
 - For 4PAM x is in $\{0,1,2,3\}$
- So multiplication is generally not an issue
 - For 2 PAM it is trivial
 - For 4 PAM one shift and add
- The problem is the adds
 - While x is one or two bits, the “a” are larger
 - Generally larger than input precision
 - Since you need to add many of them up and have small quantization errors.

Pipelining

- Pipelining can be used to increase throughput
 - True for digital and mixed signal implementations
- Pipelining: Adding same number of delay elements
 - In each forward cutset (in the data-flow graph)
 - From the input to the output
- Cutset: set of edges that if removed, graph becomes disjoint
 - Forward cutset: cutset from input to output over all edges
- Plus - Increases frequency
- Minus - Increases latency and register overhead (power, area)


Pipelining

- 3-tap FIR

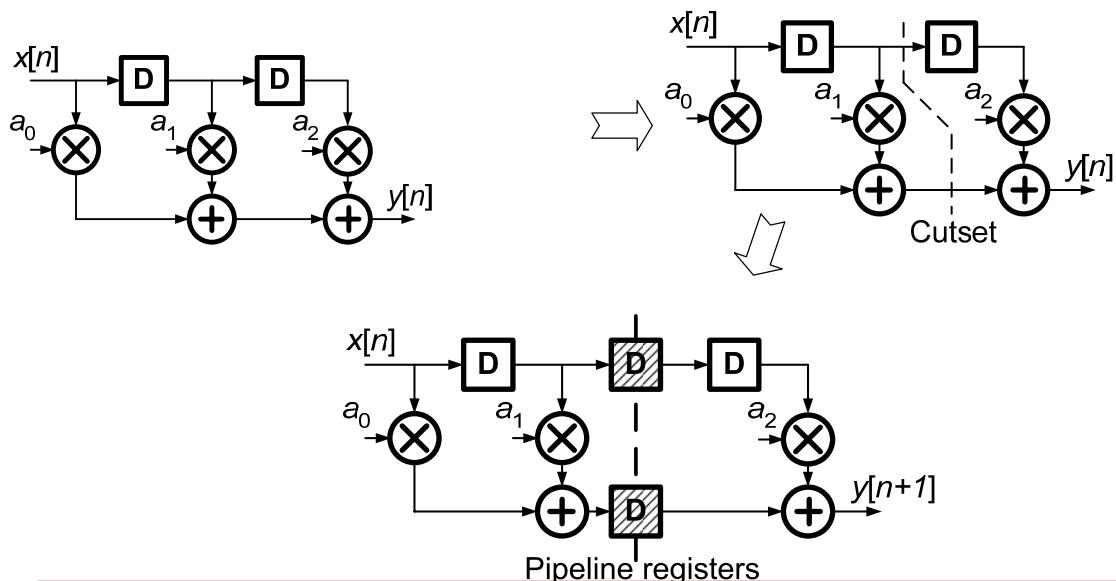

Pipelined Direct FIR


- Critical path

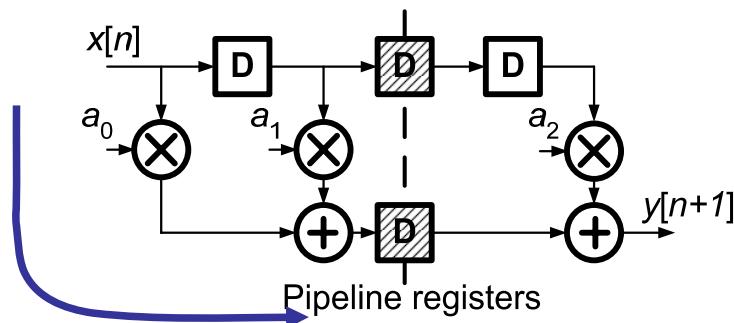

$$T = T_{mult} + T_{add}$$

Multi-Operand Addition


- Adders form a tree

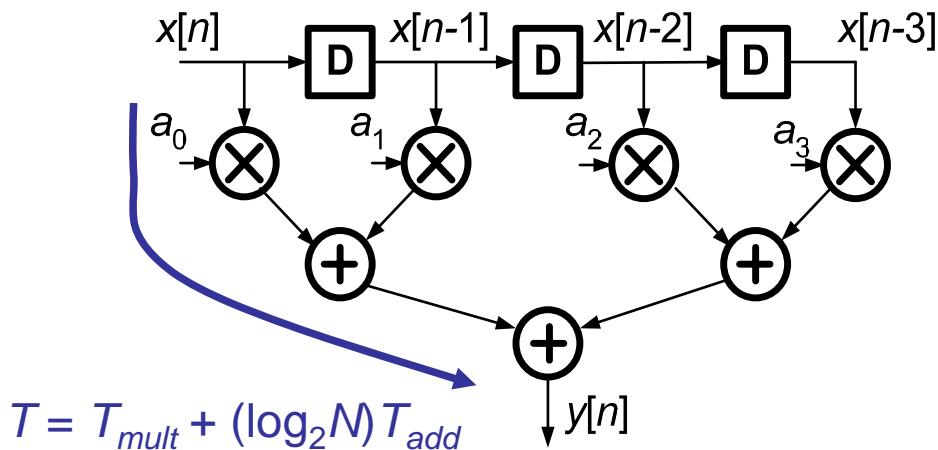

$$T = T_{mult} + (\log_2 N) T_{add}$$

Multi-Operand Addition

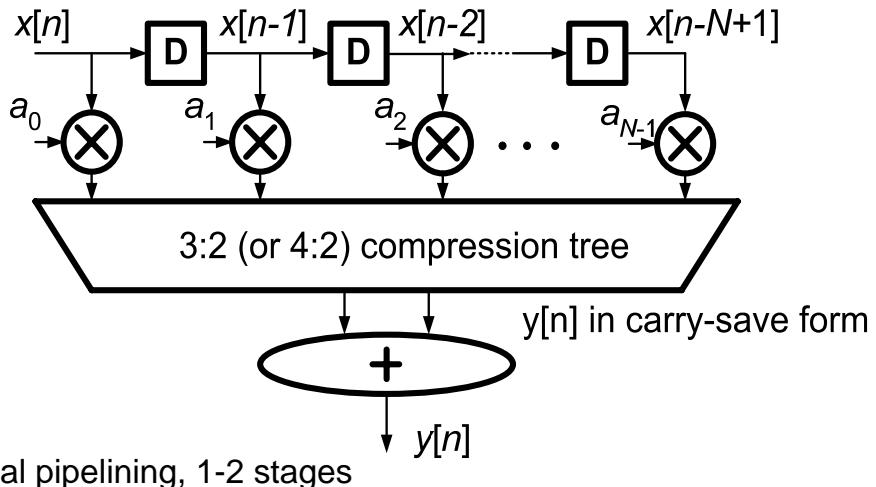- Using 3:2 or 4:2 compression
 - This is the same as a multiplier tree (in two lectures)




- Optional pipelining, 1-2 stages

Transposing FIR


- Transposition:
 - Reversing the direction of all the edges
 - In a signal-flow graph,
 - Interchanging the input and output ports
 - Functionality unchanged

Transposed FIR

- Represent as a signal-flow graph

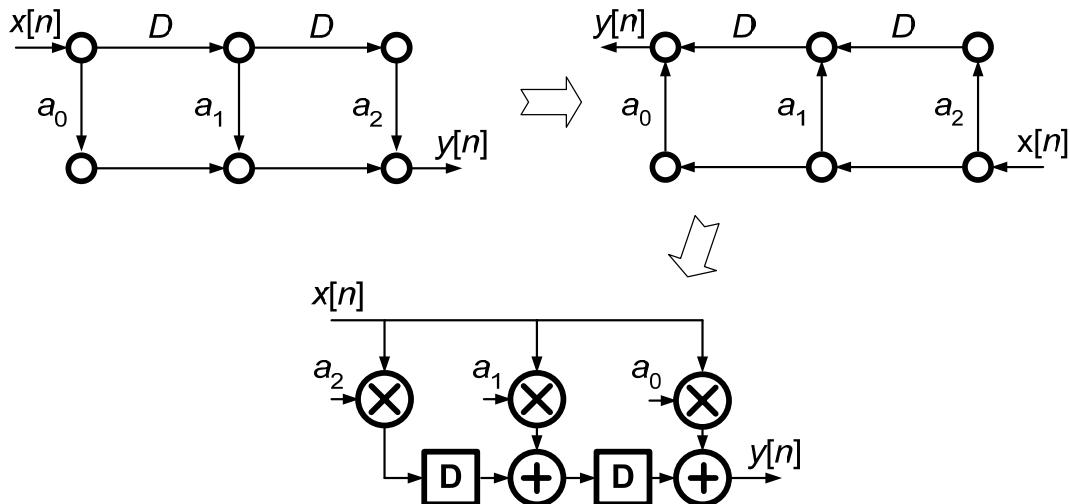


Transposed FIR

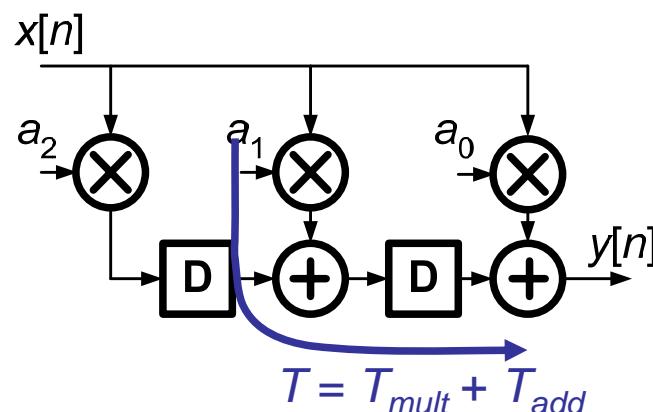

- Critical path shortened
- Input loading increased

Parallel FIR

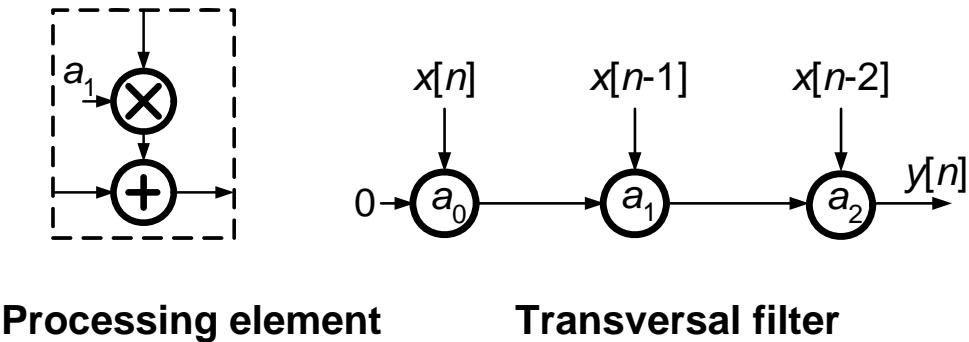- Feed-forward algorithms are easy to parallelize
- Processing element representation of a transversal filter



Parallel FIR

- Two parallel paths
- Two cycles to complete operation
- Can be extended to more


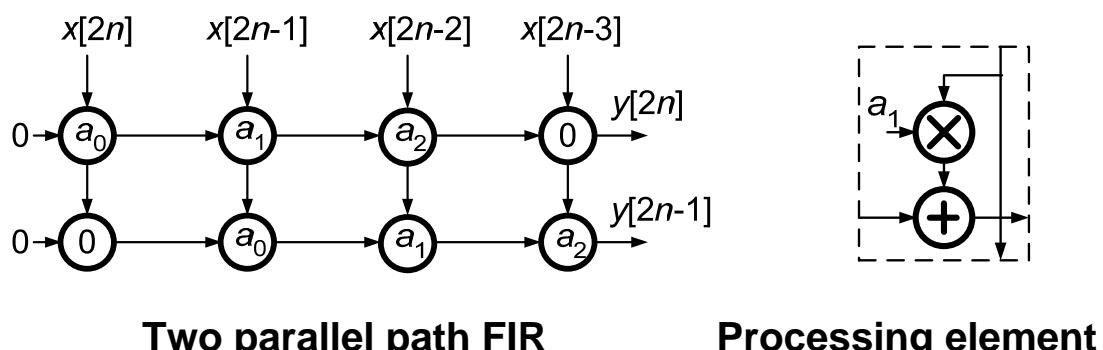


Table Lookup

- If the input data is only one or two bits
 - There are not that many input combinations
- Rather than adding the numbers together
 - Add them before hand, and just store the results in a SRAM
 - Address of SRAM is just sequence of inputs to filter
 - $x_n x_{n-1} x_{n-2} x_{n-3} x_{n-4}$
 - Values in memory
 - 00000 0 00001 a4
 - 00010 a3 00011 a3+a4
- Replaces adds and multipliers by memory
 - But it grows exponentially with number of bits needed


Decision Feedback Equalization

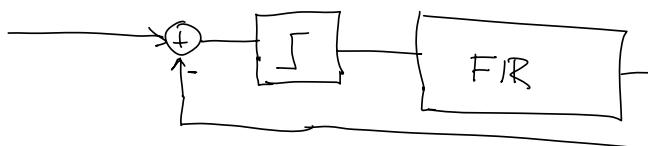

- The main problem with DFE
 - You need the output of the FIR filter NOW
 - Need it to generate the next bit
- Latency in the FIR filter is a problem


Practical Digital Equalizers

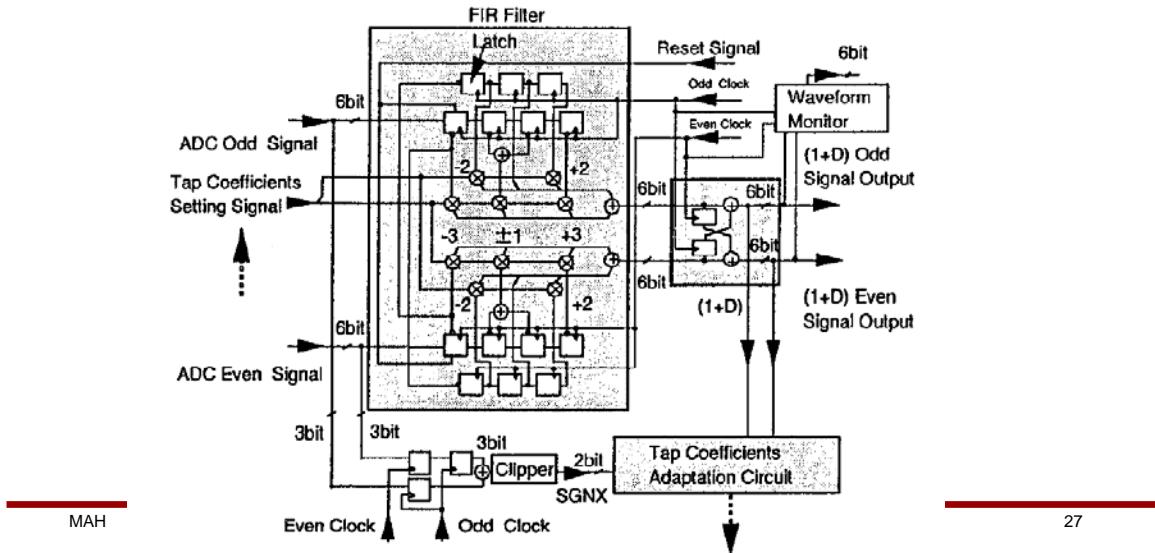- Mita, ISSCC'96, two parallel paths
- 150Mb/s 0.7μm BiCMOS




Practical Digital Equalizers

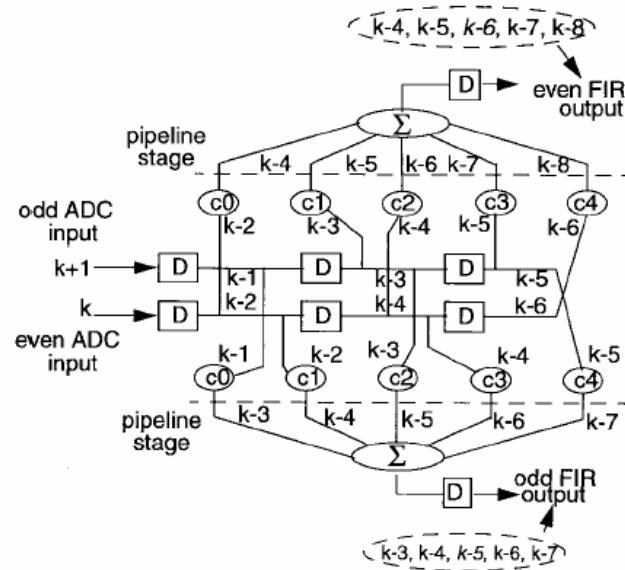- Moloney, JSSC 7/98, 2 parallel paths, 3:2 Wallace
- 150Mb/s 0.7μm BiCMOS




Practical Digital Equalizers

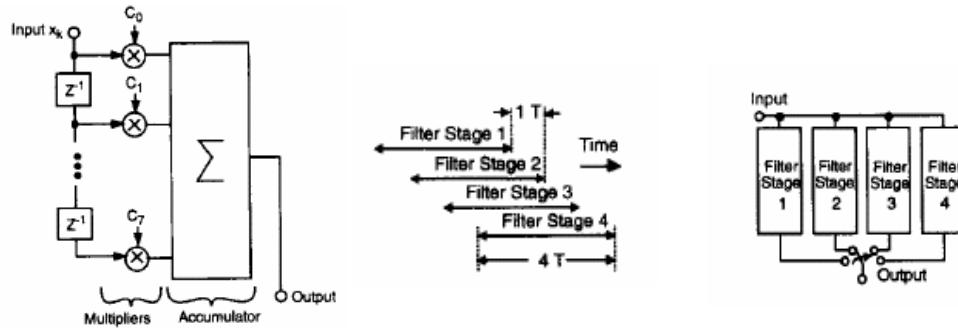- Wong, Rudell, Uehara, Gray JSSC 3/95,
4 parallel paths
- 50Mb/s, 1.2 μ m CMOS




Practical Digital Equalizers

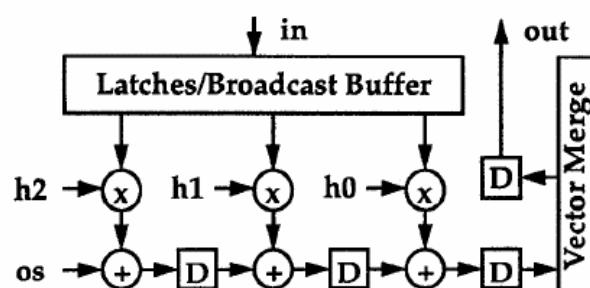- Thon, ISSCC'95
- Transposed filter, 240Mb/s 0.8 μ m 3.7V CMOS, 150mW
- Semi-static coefficients, Booth-encoded



Practical Digital Equalizers

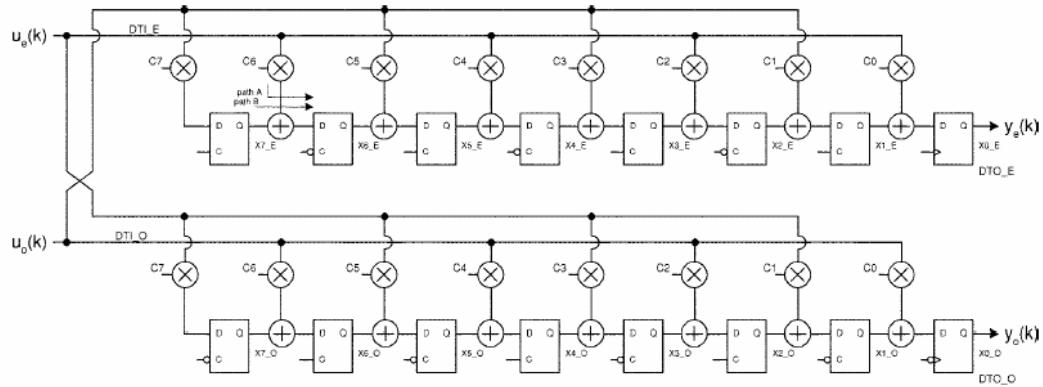- Staszewski, JSSC 8/00
- 2 parallel transposed paths, Booth encoded data
- 550Mb/s 0.21 μ m CMOS, 36mW




MAH

EE371 Lecture 3

31

Practical Digital Equalizers

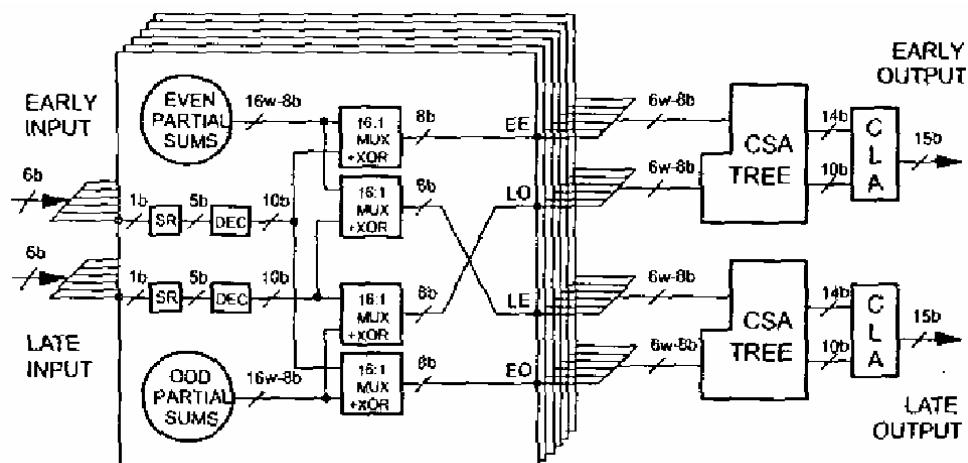- Rylov, ISSCC'01
- 2.3Gb/s, 1.2W, 0.18 μ m domino CMOS
- Distributed arithmetic




MAH

EE371 Lecture 3

32

Practical Digital Equalizers

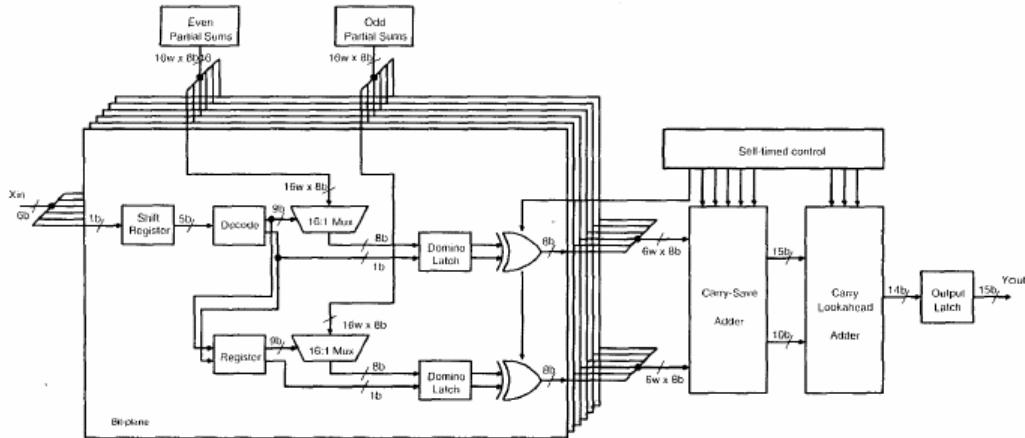- Tierno, ISSCC'02
- 1.3Gb/s, 450mW, 0.18 μ m 2.1V domino CMOS



TI DFE Design ISSCC 07

- Uses Memory lookup
 - Runs at 12Gs/s
 - Binary
- Check it out ...

References from Bora Nikolic

- R. Jain, P.T. Yang, T. Yoshino, "FIRGEN: a computer-aided design system for high performance FIR filter integrated circuits," IEEE Transactions on Signal Processing, vol.39, no.7, pp.1655-1668, July 1991.
- R.A. Hawley, B.C. Wong, T.-J. Lin, J. Laskowski, H. Samuels, "Design techniques for silicon compiler implementations of high-speed FIR digital filters," IEEE Journal of Solid-State Circuits, vol.31, no.5, pp.656-667, May 1996.
- W.L. Abbott, et al, "A digital chip with adaptive equalizer for PRML detection in hard-disk drives" IEEE International Solid-State Circuits Conference, Digest of Technical Papers, ISSCC'94, San Francisco, CA, Feb. 16-18, 1994, pp. 284 -285.
- D.J. Pearson, et al, "Digital FIR filters for high speed PRML disk read channels," IEEE Journal of Solid-State Circuits, vol.30, no.12, pp.1517-1523, May 1995.
- S. Mita, et al, "A 150 Mb/s PRML chip for magnetic disk drives," IEEE International Solid-State Circuits Conference, Digest of Technical Papers, ISSCC'96, San Francisco, CA, Feb. 8-10, 1996, pp. 62 -63, 418.
- D. Moloney, J. O'Brien, E. O'Rourke, F. Brianti, "Low-power 200-Msp, area-efficient, five-tap programmable FIR filter," IEEE Journal of Solid-State Circuits, vol.33, no.7, pp.1134-1138, July 1998.
- C.S.H. Wong, J.C. Rudell, G.T. Uehara, P.R. Gray, "A 50 MHz eight-tap adaptive equalizer for partial-response channels," IEEE Journal of Solid-State Circuits, vol.30, no.3, pp.228-234, March 1995.
- L.E. Thon, P. Sutardja, F.-S. Lai, G. Coleman, "A 240 MHz 8-tap programmable FIR filter for disk-drive read channels," 1995 IEEE International Solid-State Circuits Conference, Digest of Technical Papers, ISSCC '95, pp.82-3, 343, San Francisco, CA, 15-17 Feb. 1995.
- R. B. Staszewski, K. Muhammad, P. Balsara, "A 550-MSample/s 8-Tap FIR Digital Filter for Magnetic Recording Read Channels," IEEE Journal of Solid-State Circuits, vol. 35, no. 8, pp. 1205-1210, August 2000.
- S. Rylow, et al, "A 2.3 GSsample/s 10-tap digital FIR filter for magnetic recording read channels," IEEE International Solid-State Circuits Conference, Digest of Technical Papers, ISSCC'01, San Francisco, CA, Feb. 5-7, 2001, pp. 190-191.
- J. Tierno, et at, "A 1.3 GSsample/s 10-tap full-rate variable-latency self-timed FIR filter with clocked interfaces," IEEE International Solid-State Circuits Conference, Digest of Technical Papers, ISSCC'02, San Francisco, CA, Feb. 3-7, 2002, pp. 60 -61, 444.
