

Lecture #7: Intro to Synchronous Sequential State Machine Design

Paul Hartke

Phartke@stanford.edu

Stanford EE121

January 29, 2002

Administrivia

- Midterm #1 is next Tuesday (February 5th) in class.
 - Will not include state machines.
- Lab 3 Design Post-Mortem
 - Comments/Issues?
- Lab 4 handout
 - Due next week as normal.
- HW3 handout
 - Due Next Thursday February 7th
 - Read it over and I'll answer any questions on Thursday.

Two Types of Logic Circuits

- Combinational
 - A circuit whose outputs depend only on its current inputs
- Sequential
 - A circuit whose outputs depend not only on its current inputs, but also on the past sequence of inputs, possibly arbitrarily far back in time.

Readings


- In DDPP, Chapter 7 Intro, 7.3 (not 7.3.5), 7.4 (not 7.4.5), 7.5, 7.7
- We'll do 7.8 next time

States and State Variables

- “The state of a sequential circuit is a collection of state variables whose values at any one time contain all the information about the past necessary to account for the circuit’s future behavior.”
- The states are normally encoded as binary numbers so for n state variables, there are 2^n possible states.
 - Since there is a finite number of states, these circuits are also called finite-state machines (FSM).

Basic Sequential Element

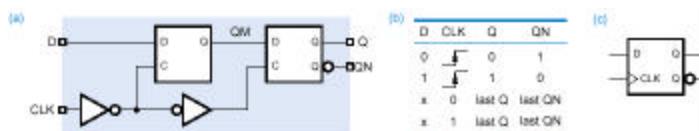- Need an element that remembers: D Flip Flop (DFF)




- Lots of ways of building this element (or an analogous one)—we’ll talk about ways later.

Simultaneous Input Changes

- Q: What if D and CLK change at the same time?
 - A: Bad things so do not change the input near the clock transition
- Setup Time: the amount of time the synchronous input (D) must be stable before the active edge of the clock.
- Hold Time: the amount of time the synchronous input (D) must be stable after the active edge of the clock.


Setup and Hold Time Diagram

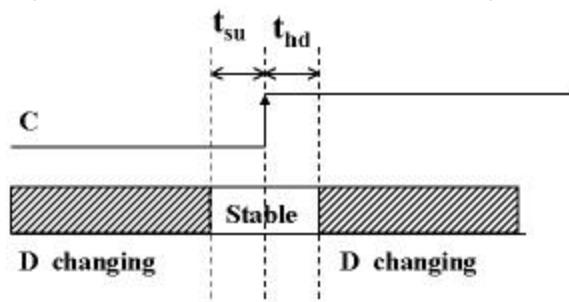- If changes on D input violate either setup or hold time, then correct FF operation is not guaranteed.
- If they are violated, metastability results.




Mealy State Machine

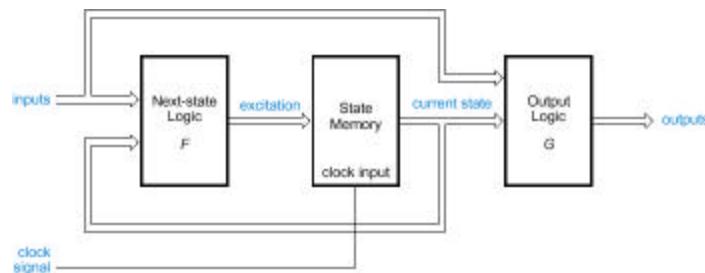- A Mealy state machine's output depends on both the state variables and the current input.



Moore State Machine

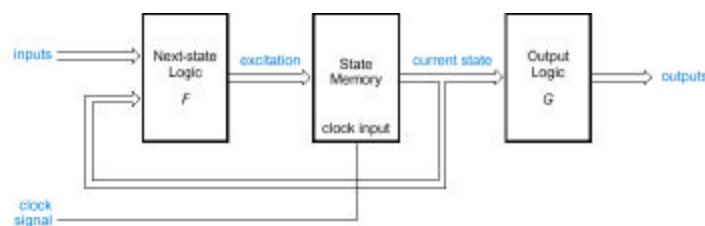- A Moore state machines outputs only depend on the state variables.



Mealy vs. Moore

- Moore machine guarantees the outputs are steady for a full clock cycle.
- However, a change at the input takes at least one clock cycle to affect the output.
- Moore machine might require more states since not dependent on the input.
- Most of the time, I use a Moore machine.

State Machine Design Process

1. Determination of inputs and outputs.
2. Determination of machine states.
3. Create State/Bubble Diagram—should this be a Mealy or Moore machine?
4. State Assignment—assign each state a particular value.
5. Create Transition/Output Table
6. Derive Next State Logic for each state element—using K-maps as necessary.
7. Derive Output logic.
8. Implement in Xilinx.


1's Counting Machine

- Design a clocked synchronous state machine with two inputs, X and Y, and one output, Z. The output should be 1 if the number of 1 inputs on X and Y since reset is a multiple of 4, and 0 otherwise.
 - Section 7.4.6 in DDPP

Machine States

- S0 → Got zero 1s (modulo 4)
- S1 → Got one 1 (modulo 4)
- S2 → Got two 1s (modulo 4)
- S3 → Got three 1s (modulo 4)

Bubble Diagram

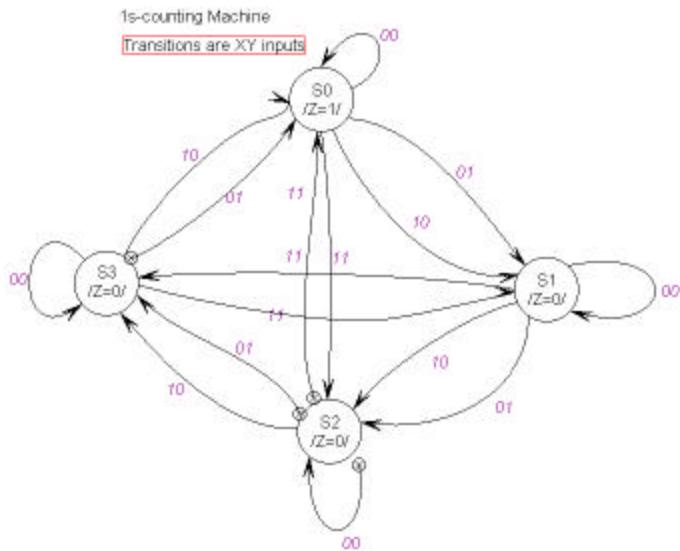

State and Output Table

- S^* is the next state given the current state and the inputs.

Meaning	S	XY				Z
		00	01	11	10	
Got zero 1s (modulo 4)	S0	S0	S1	S2	S1	1
Got one 1 (modulo 4)	S1	S1	S2	S3	S2	0
Got two 1s (modulo 4)	S2	S2	S3	S0	S3	0
Got three 1s (modulo 4)	S3	S3	S0	S1	S0	0
					S^*	

State Assignment

- Use Binary Encoding but in K-map order.
 - Requires two state elements/DFFs.
 - Semi-Arbitrary decision.
- $S_0 \rightarrow 00$
- $S_1 \rightarrow 01$
- $S_2 \rightarrow 11$
- $S_3 \rightarrow 10$

Transition/Excitation Table


- Since we will only use D-flip flops, the transition and excitation tables are the same.
 - For a DFF, $Q^* = D$

		XY				Z
Q1 Q2		00	01	11	10	
Q1* Q2*	00	00	01	11	01	1
	01	01	11	10	11	0
	11	11	10	00	10	0
	10	10	00	01	00	0

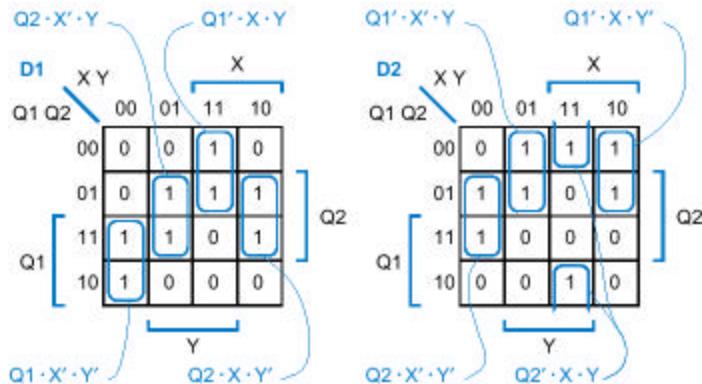Q1* Q2* or D1 D2

Derive Next State Logic

- Use a K-Map for each state register input



Logic Equations

- AKA “Next-State” Logic
- $D1 = Q2 \cdot X \cdot Y + Q1' \cdot X \cdot Y + Q1 \cdot X' \cdot Y' + Q2 \cdot X \cdot Y'$
- $D2 = Q1' \cdot X \cdot Y + Q1 \cdot X \cdot Y' + Q2 \cdot X' \cdot Y + Q2 \cdot X \cdot Y'$
- $Z = Q1' \cdot Q2'$

One-Hot Encoding

- Alternative encoding of state variables.
- Use one state element for each state variable
- $S_0 \rightarrow 0001$
- $S_1 \rightarrow 0010$
- $S_2 \rightarrow 0100$
- $S_3 \rightarrow 1000$

One-Hot Transition Table

- Same as before...

Q1Q2Q3Q4	XY=00	XY=01	XY=11	XY=10	Z
0001	0001	0010	0100	0010	1
0010	0010	0100	1000	0100	0
0100	0100	1000	0001	1000	0
1000	1000	0001	0010	0001	0

Logic Equations

- $D1 = Q1*X'*Y' + Q2*X'*Y + Q2*X*Y' + Q3*X*Y$
- $D2 = Q2*X'*Y' + Q3*X'*Y + Q3*X*Y' + Q4*X*Y$
- $D3 = Q3*X'*Y' + Q4*X'*Y + Q4*X*Y' + Q1*X*Y$
- $D4 = Q4*X'*Y' + Q1*X'*Y + Q1*X*Y' + Q2*X*Y$
- $Z = Q4$

One-Hot Value?

- One-Hot decreases the decode depth required for next state logic at the expense of more DFFs and logic.
 - Decode depth of next state logic largely determines speed of state machine.
 - Why didn't this help on this example?
- Lab 4 will have a state machine that should show the tradeoffs better.

Modified One-Hot

- In modified one-hot, the reset sequence is all zeros which transitions to the first state at the first clock edge.
- Needed for FPGAs whose FF's powerup as zeros.

Don't Forget Synchronous Resets!!

- The Xilinx FPGAs are designed so that on powerup, the DFFs initialize to logic 0.
 - We do not want to depend on that!!
- If your library supports it, use one that has a synchronous reset and tie it to the global reset pin.
- Else, explicitly design reset signal into your FSM.
- Can gate the reset signal to parts of the design on other events.