
EE108A

Lecture 1:
The Digital Abstraction
Combinational Logic
Boolean Algebra
Verilog Introduction

Administrivia

- Course Notes Chapters 1-12 (on web)
 - Read 1, 3, 6.1-6.4 for today
 - Read 6.5-6.11, 7 for Monday
- Handouts
 - Lecture slides
 - Homework 1
 - Lab 0
 - Course Policy Sheet
 - Lab/Section Questionnaire
- Web page <http://ee108a.stanford.edu>, EEClass
- E102E - writing in the major
- Photos

Today


- The Digital Abstraction
 - Representation
 - Noise
- Combinational Logic
 - Output function of current input
 - Acyclic composition
 - Representations - description, truth table, equation
 - Boolean algebra
- Verilog

1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

3

Moore's Law

 


1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis


4

Moore's Law, Broadly Defined

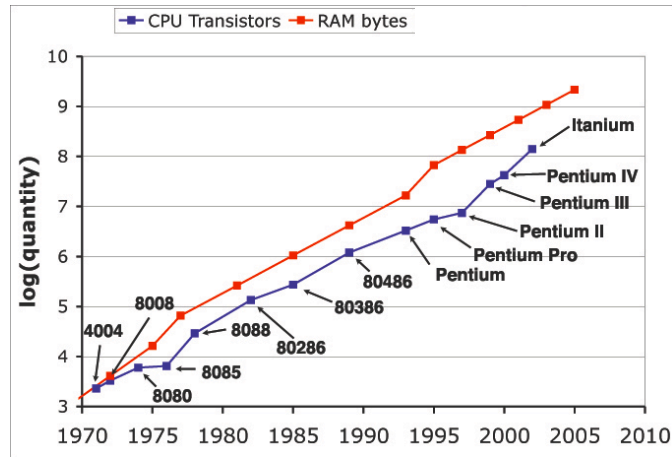

The Digital Abstraction

Voltages Ranges of Binary Signals

 

Representing Information with Digital Signals

Binary Information Light On/Off: 1/0

Element of a set

000	White	○	100	Purple	●
001	Red	●	101	Orange	●
010	Blue	●	110	Green	●
011	Yellow	●	111	Black	●

Continuous Quantities

000	68	100	76	0000000	68	0001111	76
001	70	101	78	0000001	70	0011111	78
010	72	110	80	0000011	72	0111111	80
011	74	111	82	0000111	74	1111111	82

How would you represent

- A Date ?
 - Days since Jan 1 0000 (20 bits)
 - Month, day, year (4 + 5 + 12 bits)
 - Month, day, year, day of week (4 + 5 + 12 + 3 bits)
 - This representation is _____

- A playing card ?
 - Number in deck (6 bits)
 - Suit, Number (2 + 4 bits)
 - Decoded suit, decoded number (4 + 13 bits)


- A 5-card hand ?

- Pick a representation based on operations required

 Example


- Pick representation of colors to support the operation of subtractive color mixing (e.g., red + blue = purple)
 - No colors: white
 - Primary colors: red, blue, yellow
 - Derived colors: orange, purple, green, black

- How about an additive color model?
 - No colors: black
 - Primary: red, green, blue
 - Derived: yellow, orange, purple, green, white




Effect of Noise on Analog & Digital Signals

Analog Signals

 

Digital Signals

 


1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

11

Input & Output Voltage Ranges

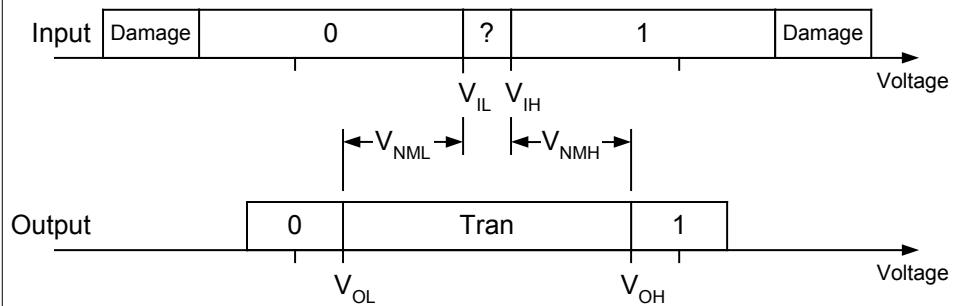


1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis


12

Restoration of Digital Signals

Noise Accumulation

 

Signal Restoration

 


1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

13

DC Transfer Curve for a Logic Module

 

1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

14

Combinational Logic


1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

15

Combinational Logic Circuit

 - Output is a function of current input
- Example – digital thermostat




1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

16

Sequential logic circuit

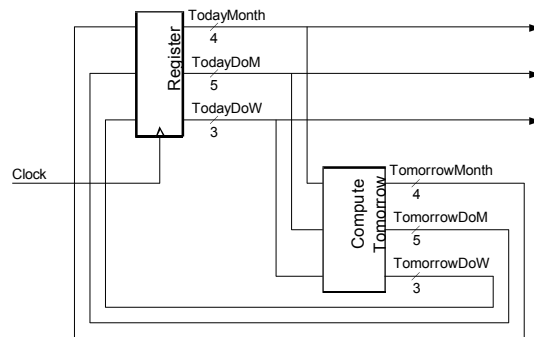- Includes state (memory, storage)
- Makes output a function of history as well as current inputs
- Synchronous sequential logic uses a *clock*
- Example, calendar circuit




1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

17

Combinational logic is memoryless

 


$$o = f(i)$$

1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

18

Can compose digital circuits

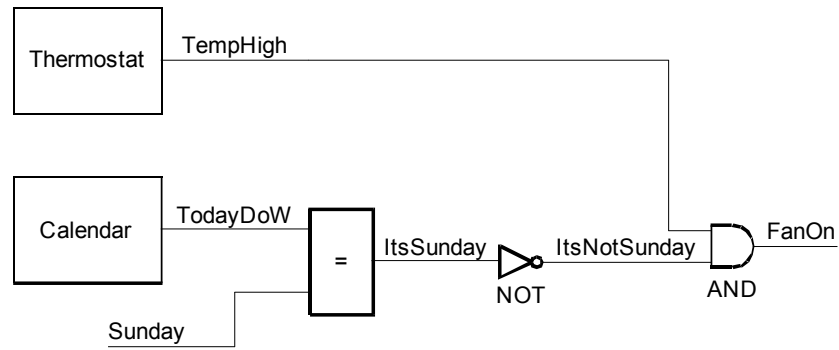


1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

19

Closure

 
- Combinational logic circuits are closed under acyclic composition.



1/9/2008


EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

20

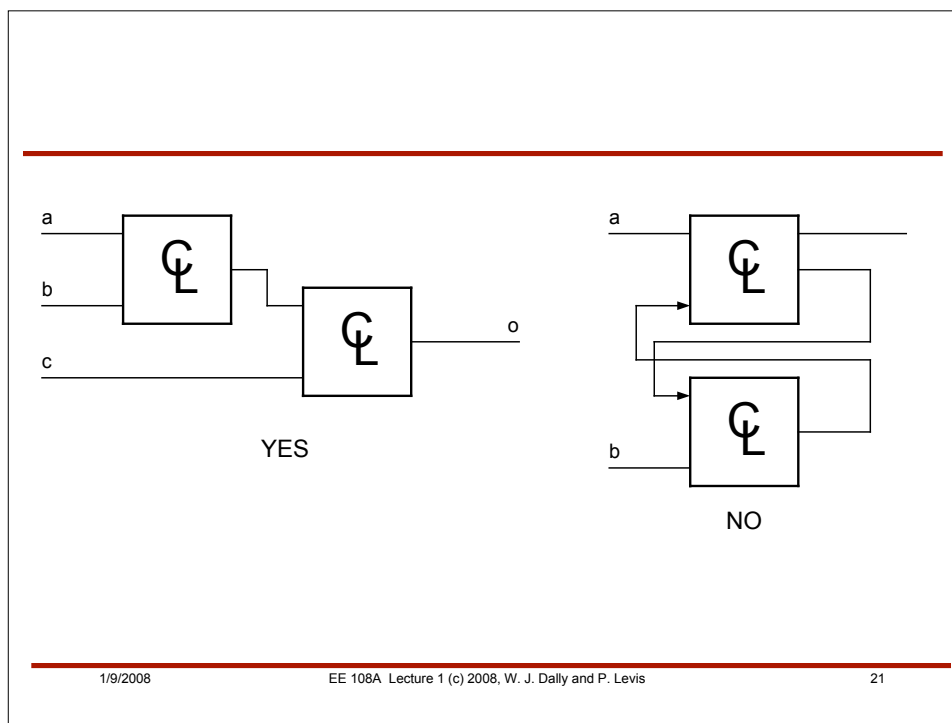

Combinational
NOT
Combinatorial

Combinational not Combinatorial

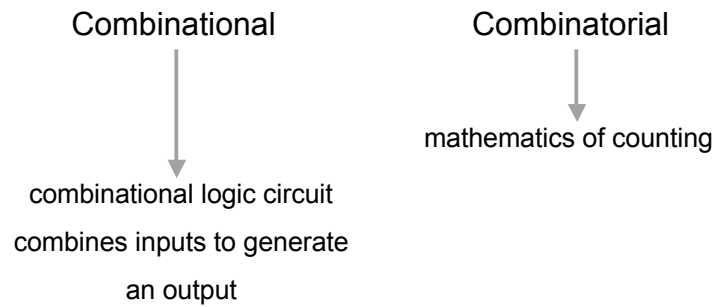

1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

23

Several ways to describe a combinational logic function

Example – Majority Circuit

1. English Language Description
 - Outputs 1 if more inputs are 1 than are 0
2. Logic equation
 - $q = (a \wedge b) \vee (a \wedge c) \vee (b \wedge c)$
3. Truth table

abc	q
000	0
001	0
010	0
011	1
100	0
101	1
110	1
111	1

1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

24

Boolean Algebra


- Boolean Algebra:
 - algebra over 2 elements: $\{0,1\}$
 - 3 operators: AND (\wedge), OR (\vee), NOT (\neg)
- AND Operation:
 - $a \wedge b = 1$ iff $a=1$ and $b=1$
- OR Operation:
 - $a \vee b = 1$ if $a=1$ or $b=1$
- NOT Operation:
 - $\neg a = 1$ iff $a=0$

a	b	$a \wedge b$	$a \vee b$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

a	$\neg a$
0	1

Note on Notation for Boolean Algebra

- For AND logic function:
 - use \wedge or $\&$
 - don't use \times or \cdot
- For OR logic function:
 - use \vee or $|$
 - don't use $+$

 

Axioms of Boolean Algebra

- *Axiom: a mathematical statement we assert to be true.*
- Identity:
 - $0 \wedge x = 0$
 - $1 \vee x = 1$
- Idempotence:
 - $1 \wedge x = x$
 - $0 \vee x = x$
- Negation:
 - $\neg 0 = 1$
 - $\neg 1 = 0$

1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

27

Useful Boolean Properties (all can be derived from the axioms)

Communicative	$x \wedge y = y \wedge x$	$x \vee y = y \vee x$
Associative	$x \wedge (y \wedge z) = (x \wedge y) \wedge z$	$x \vee (y \vee z) = (x \vee y) \vee z$
Distributive	$x \wedge (y \vee z) = (x \wedge y) \vee (x \wedge z)$	$x \vee (y \wedge z) = (x \vee y) \wedge (x \vee z)$
Idempotence	$x \wedge x = x$	$x \vee x = x$
Absorption	$x \wedge (x \vee y) = x$	$x \vee (x \wedge y) = x$
Combining	$(x \wedge y) \vee (x \wedge \neg y) = x$	$(x \vee y) \wedge (x \vee \neg y) = x$
DeMorgan's	$\neg(x \wedge y) = \neg x \vee \neg y$	$\neg(x \vee y) = \neg x \wedge \neg y$

1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

28

DeMorgan's Law

- $\neg(x \wedge y) = \neg x \vee \neg y$ $\neg(x \vee y) = \neg x \wedge \neg y$
- Proof by perfect induction



x	y	$\neg(x \wedge y)$	$\neg x \vee \neg y$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

29

DeMorgan Graphically

  

1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

30

Applying Boolean Properties

$$f(a,b,c) = (a \wedge c) \vee (a \wedge b \wedge c) \vee (\neg a \wedge b \wedge c) \vee (a \wedge b \wedge \neg c)$$

$$f(a,b,c) = (a \wedge c) \vee (a \wedge b \wedge c) \vee (\neg a \wedge b \wedge c) \vee (a \wedge b \wedge c) \vee (a \wedge b \wedge \neg c)$$

← Apply absorption property

$$f(a,b,c) = (a \wedge c) \vee (\neg a \wedge b \wedge c) \vee (a \wedge b \wedge c) \vee (a \wedge b \wedge \neg c)$$

← Apply combining property

$$f(a,b,c) = (a \wedge c) \vee (b \wedge c) \vee (a \wedge b)$$

Verilog

Verilog

- A *hardware description language (HDL)*
- Used as an input to:
 - Synthesis – implement hardware with gates, cells, or FPGAs
 - Simulation – see what your hardware will do before you build it
- Basic unit is a *module*
- Modules have
 - Module declaration
 - Input and output declarations
 - Internal signal declarations
 - Logic definition
 - Assign statements
 - Case statements
 - Module instantiations

1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

33

Example, Verilog for Thermostat

```

module Thermostat(presetTemp, currentTemp, fanOn) ;
  // temperature inputs, 3 bits each
  input [2:0] presetTemp, currentTemp ;

  // one bit, true when current > preset
  output fanOn ;

  wire fanOn ;
  assign fanOn = (currentTemp > presetTemp) ;
endmodule

```

1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

34

Example Verilog for Thermostat

```

module Thermostat(presetTemp, currentTemp, fanOn) ;
  // temperature inputs, 3 bits each
  input [2:0] presetTemp, currentTemp ;

  // one bit, true when current > preset
  output fanOn ;

  wire fanOn ;
  assign fanOn = (currentTemp > presetTemp) ;
endmodule

```

Module declaration

I/O list

Declare I/Os

3-bit wide signals

A wire is a signal set with an assign statement or connected to a module

An assign statement defines a signal with an equation

1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

35

Example, Days in Month Function

```

module DaysInMonth(month, days) ;
  input [3:0] month ; // month of the year 1 = Jan, 12 = Dec
  output [4:0] days ; // number of days in month

  reg [4:0] days ;

  always @(month) begin // evaluate whenever month changes
    case(month)
      2: days = 5'd28 ; // February has 28
      4,6,9,11: days = 5'd30 ; // 30 days have September ...
      default: days = 5'd31 ; // all the rest have 31...
    endcase
  end
endmodule

```

1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

36

Example, Days in Month Function

```

module DaysInMonth(month, days)
  input [3:0] month;
  output [4:0] days;
  reg [4:0] days;
  always @ (month) begin
    case (month)
      1: days = 5'd31; // Jan
      2: days = 5'd28;
      4,6,9,11: days = 5'd30;
      default: days = 5'd31; // all the rest have 31...
    endcase
  end
endmodule

```

Reg defines a signal set in an *always* block. It does **NOT** define a register.

Always block evaluates each time activity list changes. In this case each time *month changes*.

Case statement selects statement depending on value of argument. Like a truth table.

Can have multiple values per statement

Default covers values not listed. Always have one!

1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

37

Verilog design style – for synthesizable modules

1. Combinational modules use only
 1. Assign statements
 2. Case or Casex statements (with default)
 3. If statements – only if all signals have a default assignment
 4. Instantiations of other combinational modules
2. Sequential modules use only
 1. Combinational logic
 2. Explicitly declared registers (flip-flops)
3. Do not use
 1. Loops
 2. Always blocks except with case or casex and If
4. Do use
 1. Signal concatenation, e.g., {a, b} = {c, d}
 2. Signal subranges, e.g., a[7:1] = b[6:0];
5. Organize logic into small modules
 1. Leaf modules not more than 40 lines
 2. If it could be made two modules, it should be

1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

38

Verilog design style – for synthesizable modules (page 2)

6. Use lots of comments
 1. Comments themselves
 2. Meaningful signal names – tempHigh, not th
 3. Meaningful module names – DaysInMonth, not Mod3
7. Activation lists for case statements include **ALL** inputs
8. Constants
 1. All constants are `defined if used more than once
 2. Width of all constants is specified 5'd31, not 31
9. Signals
 1. Buses (multi-bit signals) are numbered high to low
 - e.g., wire [31:0] bus
 2. All signals should be high-true (except primary inputs and outputs)
10. Visualize the logic your Verilog will generate.
 - If you can't visualize it, the result will not be pretty

Make your code easy to read, understand, and reason about.

1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

39

Summary

- The world is digital
 - Systems are digital at their core, only analog on the edges
- Representing information
 - Binary signals, sets, continuous values
- Digital signals reject noise
 - Voltage range divided into discrete states
 - Noise margins
- Combinational logic
 - Output depends only on input (no state)
- Boolean algebra
 - Rules to manipulate logic equations
- Verilog
 - Describe hardware for simulation and synthesis

1/9/2008

EE 108A Lecture 1 (c) 2008, W. J. Dally and P. Levis

40