

---

## Lecture 8

### Simple & Pipelined Processor Designs

Christos Kozyrakis  
Stanford University  
<http://eeclass.stanford.edu/ee108b>

---

## Announcements

- Upcoming deadlines
  - HW2 due today
  - PA1 due on Thursday 2/8
- Quiz 1 review session on Friday
- Quiz 1
  - Tue 2/6, 7pm–9pm, location TBD
  - Local SCPD students must come to Stanford for the midterm
  - Covers lectures 1-7
  - Closed book, 1 page of notes + green card, calculator


---

## Review: How to Execute Instructions

- First we need to:
  - Fetch the instruction
- Then we need to:
  - Decode instruction / fetch register
- Then we need to:
  - Do the operation
- Then we need to:
  - Write the result into register-file
- Finally we need to:
  - Calculate the next instruction address

---
 
## Review: Datapath for Instruction Fetch Unit







## Control

- Since every instruction takes one cycle, control is state free!
  - It is just decoded instruction bits
- There are also few control points
  - Control on the multiplexers
  - Operation type for the ALU
  - Write control on the Instruction & Data memories
- First part of cycle does not have any control
  - Which is good, since we don't have instruction yet
- Look at setting of the control points for different instructions


## At Beginning Of Clock Cycle

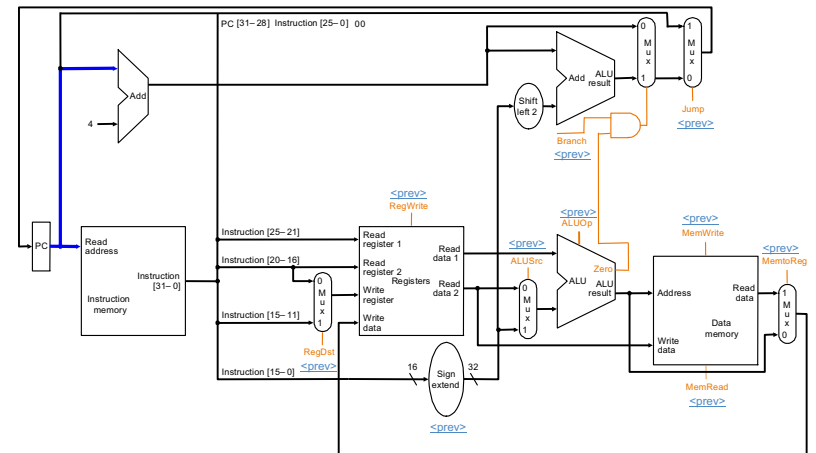


## Control for Arithmetic

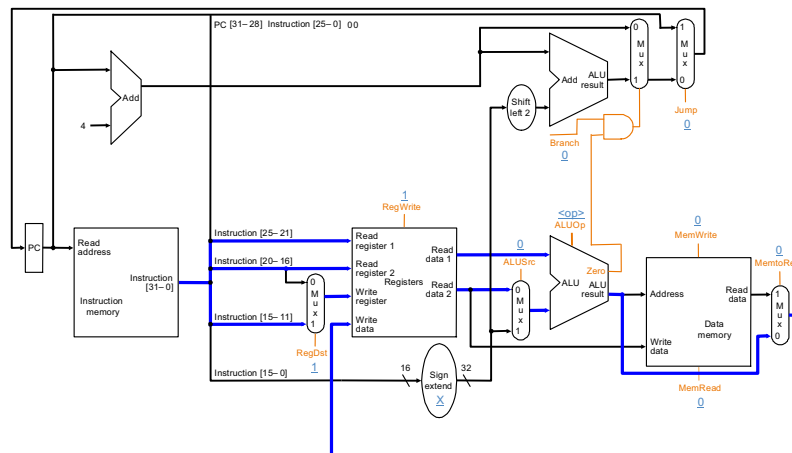

## Instruction Fetch at End

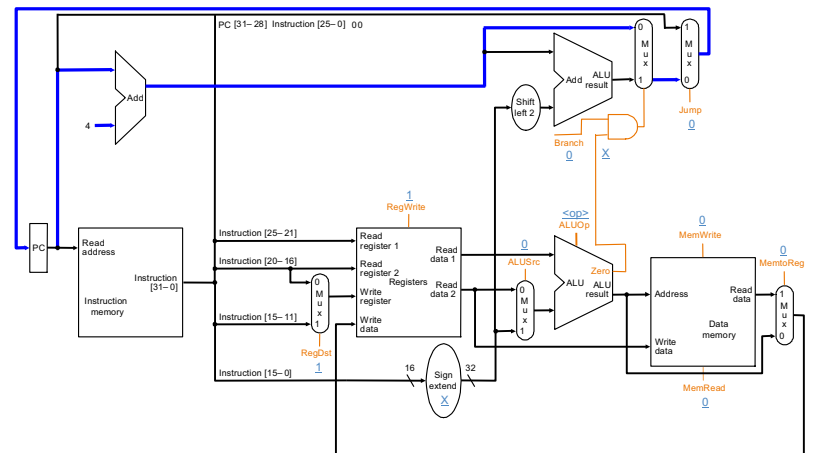

## Arithmetic Immediate (ori)

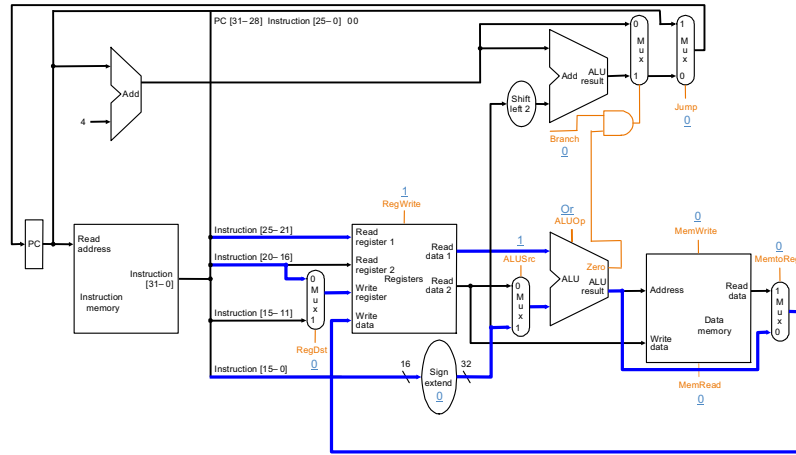


C. Kozyrakis

EE108b Lecture 8

13

## Control for Load

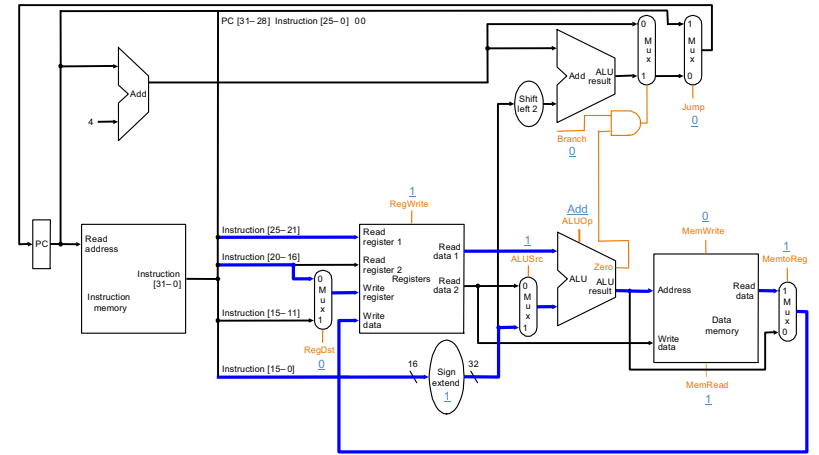


C. Kozyrakis

EE108b Lecture 8

14

## Control for Store

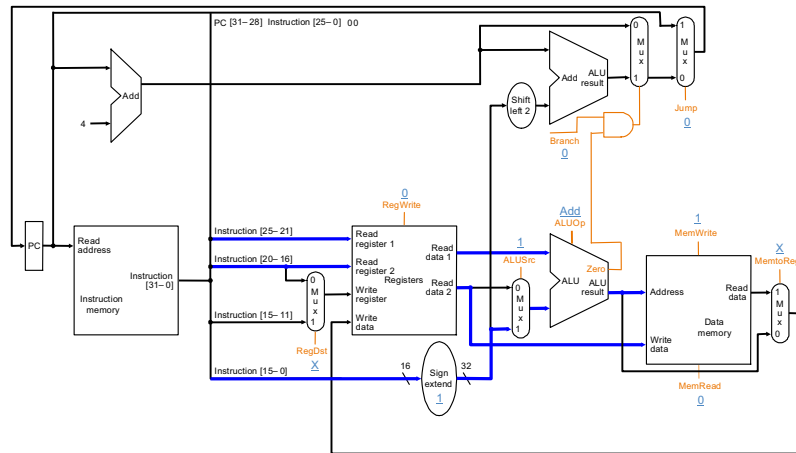


C. Kozyrakis

EE108b Lecture 8

15

## Control for Branch (beq)

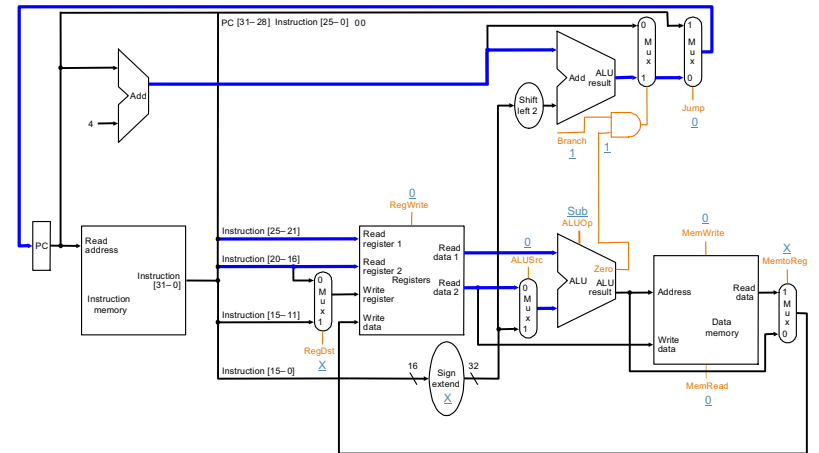


C. Kozyrakis

EE108b Lecture 8

16

## Control for Jump (j)

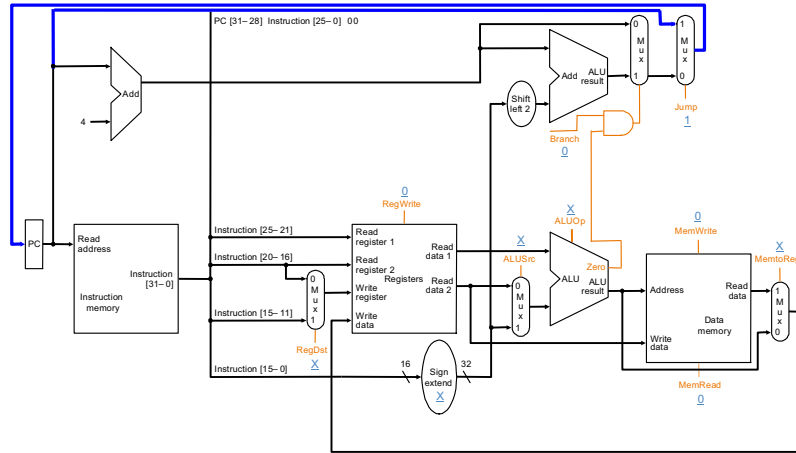


## Summary of Control Signals

func op	10 0000	10 0010	Not Important				
	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	add	sub	ori	lw	sw	beq	jump
<b>RegDst</b>	1	1	0	0	x	x	x
<b>ALUSrc</b>	0	0	1	1	1	0	x
<b>MemtoReg</b>	0	0	0	1	x	x	x
<b>RegWrite</b>	1	1	1	1	0	0	0
<b>MemWrite</b>	0	0	0	0	1	0	0
<b>Branch</b>	0	0	0	0	0	1	0
<b>Jump</b>	0	0	0	0	0	0	1
<b>ExtOp</b>	x	x	0	1	1	x	x
<b>ALUctr&lt;2:0&gt;</b>	Add	Sub	Or	Add	Add	Sub	xxx
 
## Multilevel Decoding


- Since only the ALU needs the func field
  - Pass it to the ALU unit, and have a local decoder there



## Multilevel Decoding (cont)

op	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	R-type	ori	lw	sw	beq	jump
<b>RegDst</b>	1	0	0	x	x	x
<b>ALUSrc</b>	0	1	1	1	0	x
<b>MemtoReg</b>	0	0	1	x	x	x
<b>RegWrite</b>	1	1	1	0	0	0
<b>MemWrite</b>	0	0	0	1	0	0
<b>Branch</b>	0	0	0	0	1	0
<b>Jump</b>	0	0	0	0	0	1
<b>ExtOp</b>	x	0	1	1	x	x
<b>ALUop&lt;N:0&gt;</b>	"R-type"	Or	Add	Add	Subtract	xxx

## Putting It All Together

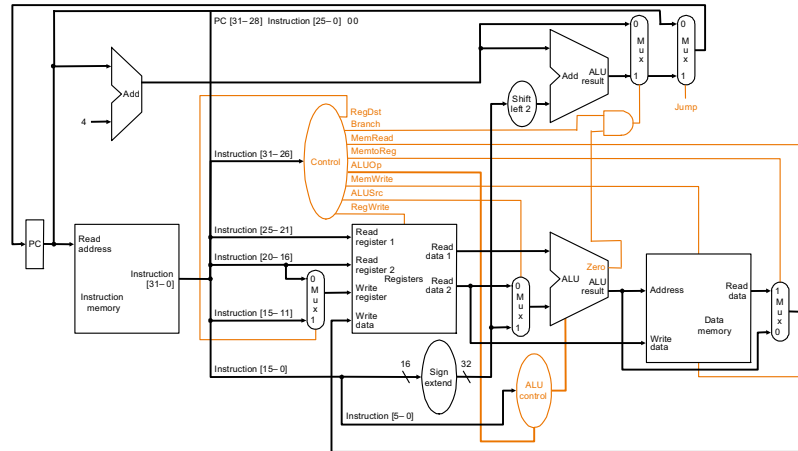

C. Kozyrakis

EE108b Lecture 8

21

## Single Cycle Processor

- Advantages
  - Single cycle per instruction makes logic and clock simple
- Disadvantages
  - Inefficient utilization of memory and functional units since different instructions take different lengths of time
    - ALU only computes values a small amount of the time
  - Cycle time is the worst case path → long cycle times
    - Load instruction
  - All machines would have a CPI of 1

C. Kozyrakis

EE108b Lecture 8

22

## Single Cycle Processor Performance

- Functional unit delay
  - Memory: 2ns
  - ALU and adders: 1 ns
  - Register file: 0.5 ns

Instruction class	Instruction memory	Register read	ALU operation	Data memory	Register write	Total
R-type	2	0.5	1		0.5	4
load	2	0.5	1	2	0.5	6
store	2	0.5	1	2		5.5
branch	2	0.5	1			3.5
jump	2					2

- CPU clock cycle = 6 ns

C. Kozyrakis

EE108b Lecture 8

23

## Variable Clock Single Cycle Processor Performance

- Instruction Mix
  - 45% ALU
  - 25% loads
  - 10% stores
  - 15% branches
  - 5% jumps

Instr. class	Instr. memory	Reg. read	ALU op	Data memory	Register write	Total
R-type	2	0.5	1		0.5	4
load	2	0.5	1	2	0.5	6
store	2	0.5	1	2		5.5
branch	2	0.5	1			3.5
jump	2					2

- CPU clock cycle =  $4 \times 45\% + 6 \times 25\% + 5.5 \times 10\% + 3.5 \times 15\% + 2 \times 5\%$   
= 4.5 ns

C. Kozyrakis

EE108b Lecture 8

24

## Increasing Parallelism

- Problem:
  - Each functional unit used once per cycle
  - Most of the time it is sitting waiting for its turn
    - Well it is calculating all the time, but it is waiting for valid data
  - There is no parallelism in this arrangement
- Making instructions take more cycles can make machine faster!
  - Each instruction takes roughly the same time
    - While the CPI is much worse, the clock freq is much higher
  - Overlap execution of multiple instructions at the same time
    - Different instructions will be active at the same time
  - This is called “Pipelining”
  - We will look at a 5 stage pipeline
    - Modern machines (Pentium 4) have order 20 cycles/instruction


## Pipelining: It's Natural and You Do It All the Time!

- Laundry Example
- Ann, Brian, Cathy, Dave each have one load of clothes to wash, dry, and fold




- Washer takes 30 minutes
- Dryer takes 40 minutes
- “Folding bench” takes 20 minutes

## Sequential Laundry

 


Sequential laundry takes 6 hours for 4 loads

## Pipelined Laundry: Start work ASAP

 

Pipelined laundry takes 3.5 hours for 4 loads

## Pipelining Lessons

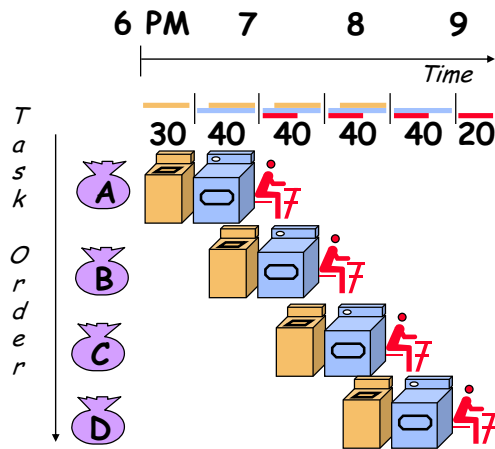


- Pipelining doesn't help **latency** of single task, it helps **throughput** of entire workload
- **Multiple** tasks operating simultaneously
- Potential speedup = **Number pipe stages**
- Pipeline rate limited by **slowest** pipeline stage
- Unbalanced lengths of pipe stages reduces speedup
- Time to "fill" pipeline and time to "drain" it reduces speedup

## Dividing Up The Execution

- Since we are going to break execution into different clock cycles
  - We want to balance the work done in each clock
  - Break into a "reasonable" number of cycles
- Imagine we are building a system and know the following:
  - Register file – 1 ns
  - ALU operation – 2 ns
  - Memory access – 2 ns
- How to divide up the cycle?
  - Make memory access one cycle, that is largest factor

 
## 5 Stage Execution

- IF: Instruction Fetch
  - Fetch the instruction from memory
  - Increment the PC
- RF/ID: Register Fetch and Instruction Decode
  - Fetch base register
- EX: Execute
  - Calculate base + sign-extended offset
- MEM: Memory
  - Read the data from the data memory
- WB: Write back
  - Write the results back to the register file



 
## Processor Pipeline

- Fetch a new instruction each cycle
  - Each stage of the pipeline is working on a different instruction


 
## Pipelining Load

- Load instruction takes 5 stages
  - Five independent functional units work on each stage
    - Each functional unit used only once
  - Another load can start as soon as 1<sup>st</sup> finishes IF stage
  - Each load still takes 5 cycles to complete
  - The *throughput*, however, is much higher




## Functional Units Are Busy


- Pipelining now keeps all the functional units busy
  - Fetch a new instruction each cycle
  - Fetch registers every cycle
  - Use the ALU almost every cycle
  - Use the Data Memory many cycles
- Instructions still take 10ns to complete
  - But start a new instruction every 2ns
  - Looks like CPI is 1 cycle

	1	2	3	4	5	6	7	8	9
I1	IF	ID	EX	MEM	WB				
I2		IF	ID	EX	MEM	WB			
I3			IF	ID	EX	MEM	WB		
I4				IF	ID	EX	MEM	WB	
I5					IF	ID	EX	MEM	WB


## Pipeline Datapath

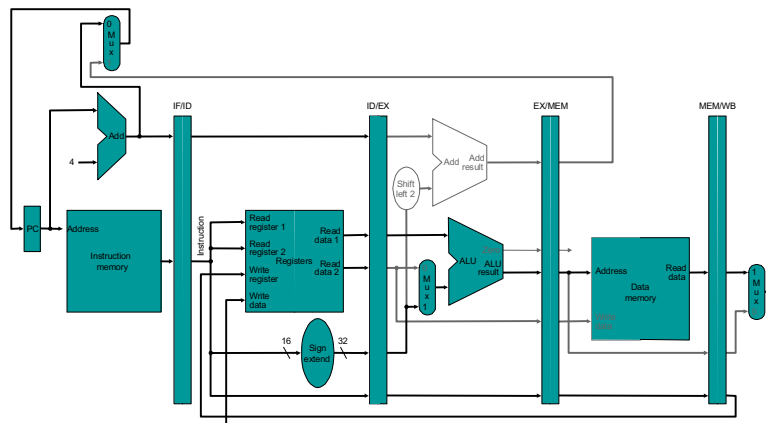


## Load Datapath: Stage 1

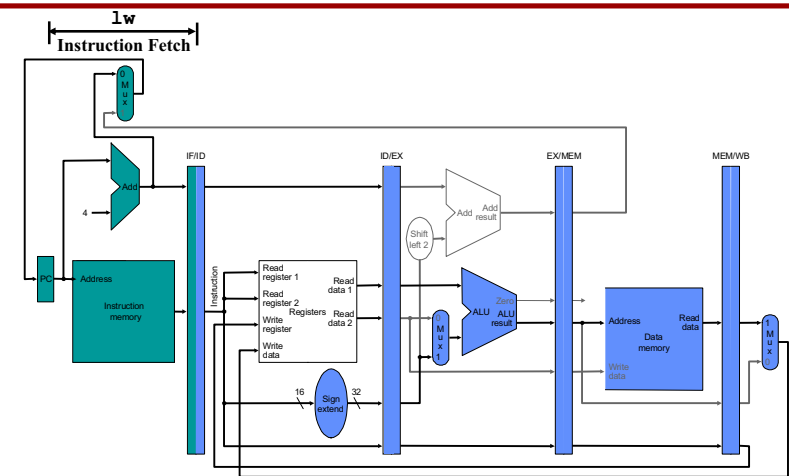


## Load Datapath: Stage 2

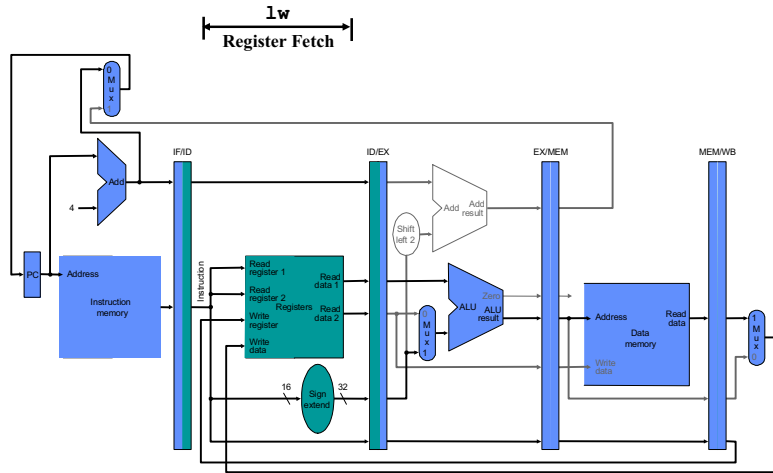


## Load Datapath: Stage 3

 

## Load Datapath: Stage 4

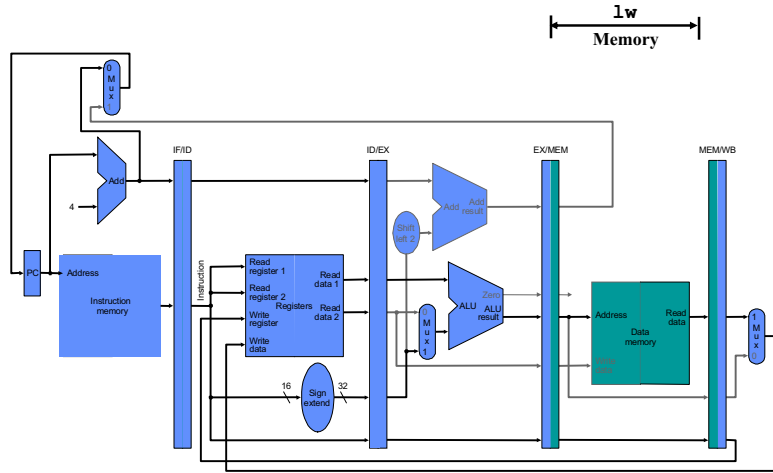


## Load Datapath: Stage 5

 



## Comparison

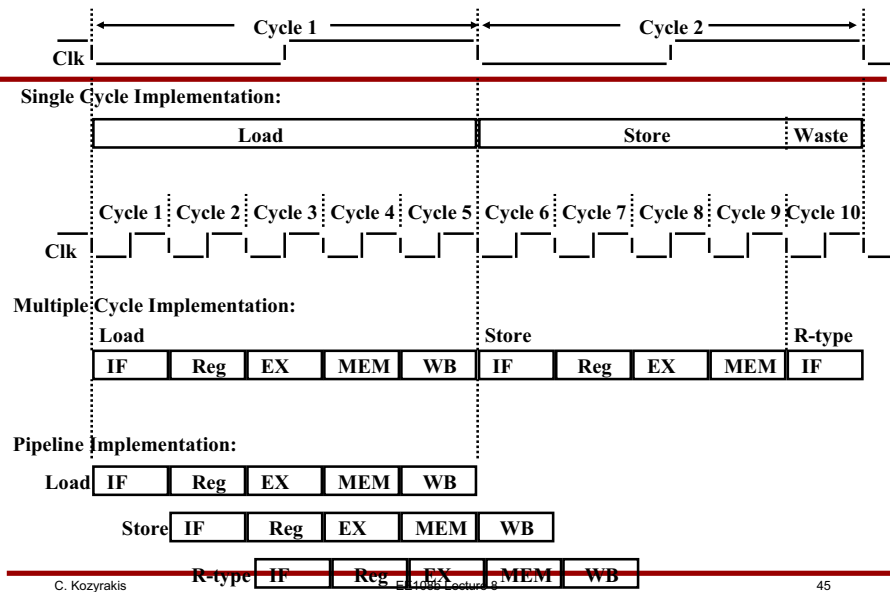

## But Something Is Fishy Here

- If dividing it into 5 parts made the clock faster
  - And the effective CPI is still one
- Then dividing it into 10 parts would make the clock even faster
  - And wouldn't the CPI still be one?
- Then why not go to twenty cycles?
- Really two issues
  - Some things really have to complete in a cycle
    - Find next PC from current PC
  - CPI is not really one
    - Sometimes you need the results from the previous instruction