

---

# Lecture 10

## Circuit Design Rules of Thumb

Zongjian Chen  
Broadcom  
Zongjian\_chen@yahoo.com

Copyright © 2004 by Zongjian Chen

Zongjian Chen

EE371 Lecture 10

1

---

## Overview

- What:
  - Sets of design guidelines, practices, numerical rules to follow when performing custom designs
- Why:
  - “Construct it right” to begin with
  - Save simulation effort spent on common cases
  - Manage design uniformity/risk
- How:
  - Methodology book
  - CAD tool checker - “If you can’t enforce it, the rule does not exist”
- Objective of this lecture
  - Get a sense of what issues are of concern in a real world design environment
  - How trade-offs are made (80/20 rules)

Zongjian Chen

EE371 Lecture 10

2

## Topics in “Rule of Thumb” Book




---

- Basics
  - Tabulated technology parameters
- Schematic design practices
- Layout design practices
   
## Basic Technology Parameters

---


- Inverter delays
  - “Intrinsic” and “fan out dependency”
- Gate cap per  $\mu\text{m}$ 
  - Various flavors of transistors
- Diffusion cap per  $\mu\text{m}$ 
  - Layout topology matters (unshared vs. shared vs. stacked)



## Basic Technology Parameters

- Wire Rs and Cs
  - Impact of width and spacing
  - 1x, 1.5x, 2x of minimum w/s typically tabulated
    - Microprocessor technology typically have “inversely scaled” interconnect technology. For example, 1x w/s for lower level, 2x w/s for intermediate level, 4x w/s for upper level
    - For a particular level (say intermediate level), the minimum w/s is  $y$  ( $y=2x$  in this example). In that layer the width and spacing of signal lines typically do not go beyond  $2y$
    - Between  $y$  and  $2y$ , increase of width/spacing bring down the resistance per length without much penalty in cap per length

Width	Spacing	Resistance (Normalized)	Ctotal (Normalized)	RC (Normalized)	Cside/(C <sub>up</sub> +C <sub>down</sub> )
$y$	$y$	2	1.1	2.2	2.1
$y$	$2y$	2	0.8	1.6	1.0
$1.5y$	$1.5y$	1.3	1	1.3	1.1
$2y$	$y$	1	1.2	1.2	1.3
$2y$	$2y$	1	1	1	0.7

 


## Schematic Design Practices

- Correctness related rules
- Efficiency (design effort) related rules
- Optimization (performance/area) related rules
- Technology migration related rules
- Power efficiency related rules
- Intertwined
  - A given rule belongs to multiple categories
  - Quantification needs to balance trade-off among several objectives
- Examples given in the following slides
  - Why, how, and scaling trends more important than absolute values
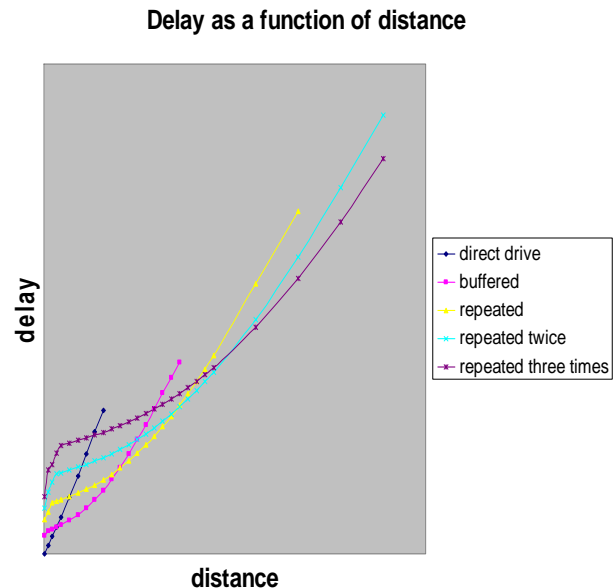
## Repeater (Buffering) & Slew Rate Rules

- Optimum repeater is a well discussed topic in EE 371
- Additional factors to account for in real life design:
  - Need to meet the coupling noise criteria
  - Current carried by the wire meets the reliability criteria
  - The slope at the end of the wire will not cause excessive “shunt” current for the target load
- Slew rate upper limit rules needs to factor in similar consideration



## Beta Ratio

- Criteria:
  - Balancing rising and falling edges
  - Delay consideration
  - Input noise margin consideration
  - Area/power consideration
- Need compromise
- Weights for objectives different between static vs. dynamic styles
- “Typical” 90 nm values
  - See the effect of velocity saturation


Gate Type	Beta (Static)	Beta (“Dynamic” - that for the static gate in a complex dynamic gate combo)
inv	2	6
nand2	3	6
nand3	3.5	6
nor2	2	5

# Transmission Gate Sizing


- Pass transistor sizing optimization (speed/power area)
  - Ratio of the pass gate vs. driving inverter
    - Optimization result sensitive to the number of inputs

•Also sensitive to the “fan out” between the load and the driver

Delay vs. Ratio of Wpassgate/Wdriver

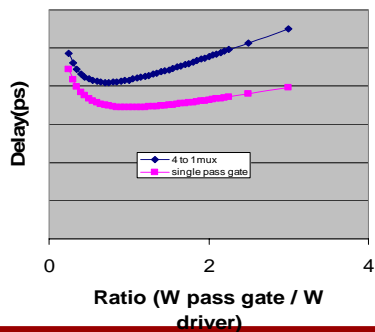

 
Delay vs. Ratio of Wpass gate/Wdriver at different fanout



# Transmission Gate Sizing

- Optimization of Beta ratio of the pass gates

Delay vs. pass gate beta

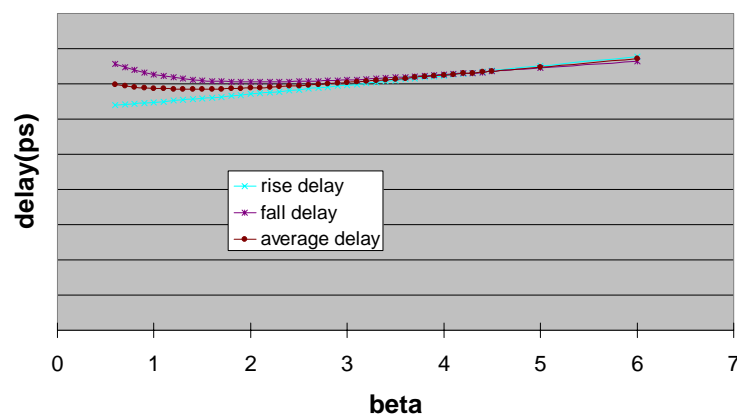


## Rules for Dynamic Circuits

- Dynamic gate:
  - Faster logic (especially for high fan-in) at the cost of design complexity and clock/power overhead
- Three tightly coupled issues:
  - Keeper sizing for leakage fighting and low delay impact
  - Charge sharing effect
  - Input noise criteria
- Other considerations:
  - Rules related to the contention current through the evaluation chain
  - Rules related to the contention current in the inverting buffers
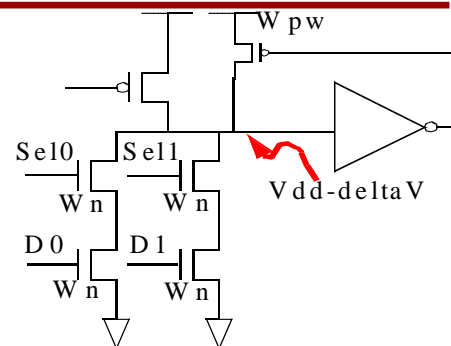
## Keeper Sizing for Leakage Fighting


- Part of dynamic node signal degradation budgeted for leakage fighting
- Need to consider the worst case: PVT corners and input topology (fast n, weak p, high V<sub>dd</sub>, high T)
- Minimum feedback pull up strength set up “leakage droop” budget
- Delay impact sets maximum limit on feedback pull up strength
- As technology migrates, the “head room” for large fan in topology gradually diminishes
- Non minimum channel and “second to fastest grade” transistor may be better choice for dynamic gate



Worst case for leakage:  
 $Se_{10}=Se_{11}=0, D_0=D_1=1,$   
 $W_{pw}/(2 \times W_n) > \text{Criteria}_1$   
 Worst case for speed:  
 $Se_{10}=D_0=0, Se_{11}=D_1=1,$   
 $W_{pw}/(W_n/2) < \text{Criteria}_2$   
 $\Rightarrow 2C_1 < (W_p/W_n) < C_2/2$   
 $C_2/C_1$  is getting worse as transistors are getting leaky

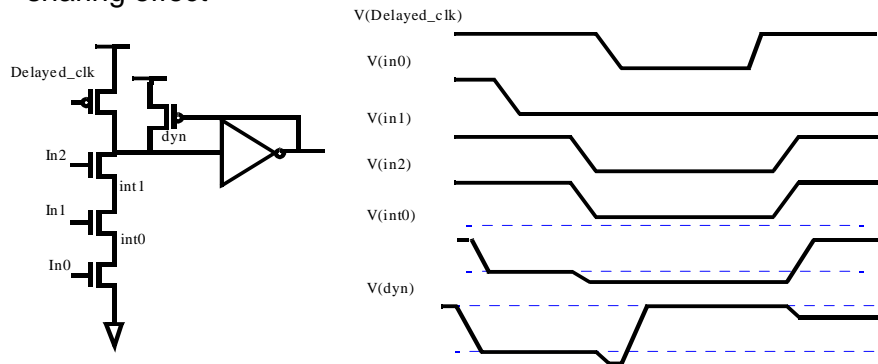
## Charge Sharing Effect in Dynamic Circuit

- Charge sharing with the dynamic node degrades signal
- The worst case sequence is worse than typically considered
- Part of dynamic node signal degradation budgeted for charge sharing effect



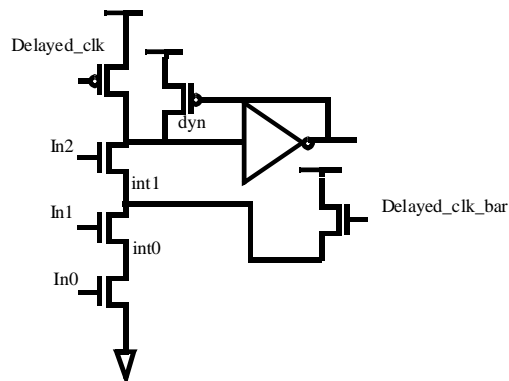
## Charge Sharing Effect in Dynamic Circuit

- Pre-charging internal node is a typically charge sharing solution
- Examples of “rule of thumb” bounding the charge sharing effect
  - Stack height has to lower than  $x$
  - Intermediate node above stack height  $y$  has to have pre-charge transistors



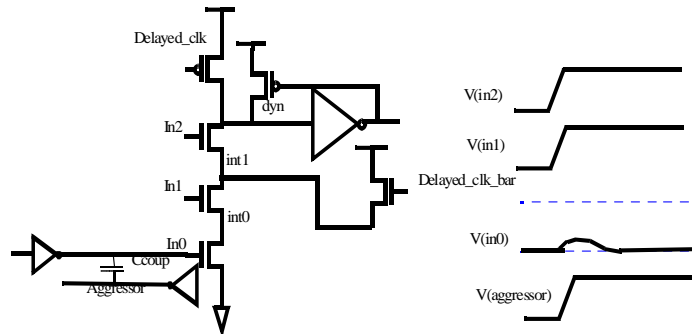
## Rules on Noise Limit for Dynamic Gate Inputs

- Portion of dynamic node signal degradation budgeted for charge sharing can be traded-off for the portion budgeted for leakage
- Input noise induced degradation shared the same “total budget”
- “Worst case additive” method no longer provides a reasonable final “degradation budgeting” plan
- Transient nature of the noise has to be taken into consideration


 
## Rules on Noise Limit for Dynamic Gate Inputs


- Beta of the static inverter is yet another input parameter
- Pass gate/Mux output as driver for dynamic gate input should be banned
- “Noise shape constraints” has to be separately checked





 
## Power Related Rules for Dynamic Gate

- Slope for pre-charging process affects “shunt” current in the inverter and needs to be limited
- “Shunt” current in the evaluation chain for “footless” domino needs to be checked
  - “Footless” domino saves clock power
  - But possible “power race” during pre-charge
  - “Power race margin” needs to be checked



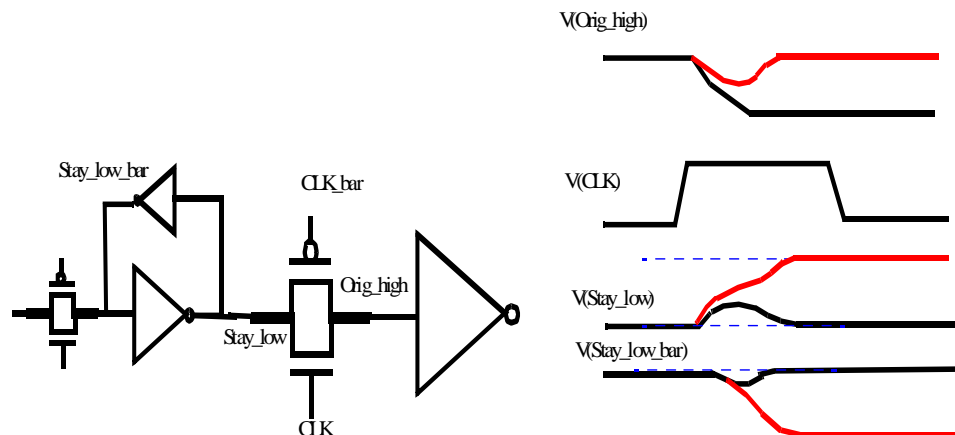
## Charge Sharing in Static Design

- Charge sharing can affect the functionality of a latch node held by static feed back


 
## Writability Rules

- Contention based circuit used for better area
- Functionality across corners are guaranteed through thorough corner simulations plus margins
- Define min. driver/keeper driving strength ratio





$$W_{\text{eff\_driver}}/W_{\text{eff\_feedback}} > \mathbf{R}_{\text{ratio\_for\_writability}}$$

For example,  $(W_n/2)/(W_{pf}/2) > 3$ , or  $W_n > 3 W_{pf}$
  
## Coupling Noise Limit

- Static gate inputs have most input noise suppression capability
- Topologies that need unique noise limit
  - Dynamic gate input
  - Pass transistor input
  - Input to static gates that drives a dynamic gate



## Rule of Thumbs on Clocks

---

- Skew budgeting
  - Amount of skew allowed at each level of clock tree
- Clock wire width as a function of per pitch clock load
  - Super linear dependency on load
  - Mandates maximum for per pitch load or size of the flop
- Via constraints at the driver side of a clock wire
  - Resistor at the driving end of a clock wire contributes disproportionately to skew
  - Modern processes have high resistive via
  - Need to jump a few layers before get to the clock wire
- Rule of thumb for datapath clock generator selection

## Inductive Noise Prevention

---

- Inductive noise can be an issue on low R (top level) wire
  - Delay and crosstalk show dependence on inductance when
  - $C_{\text{load}} \ll C_{\text{wire}}$
  - $R_{\text{wire}}/Z_0 \leq 0.5$
  - $Z_{\text{driver}} < Z_0$
- “Near return” path is a practical fix – Need “rule of thumb” for triggering threshold
-

## Scalability of the Design

---

- Full custom design need to survive multiple technology nodes to recoup design cost - scalability important
- Design implications:
  - Buffer insertion needs to be biased in the “buffer delay heavy” end vs. wire delay heavy end for the first design in a series
  - Need to bound the percentages of wire delays within a cycle (also a consideration for voltage scalability)
  - Leakage sensitive circuits – need to think ahead
- SOI “portability”:
  - Allocate area for floating body effect sensitive circuits


## Usage Limitation of Various “Flavors” of Transistors

---

- Foundries provide multiple “flavors” of transistors
  - Low  $V_t$  grade for higher speed (20%-30%), but with huge (~10X) impact on leakage power
  - Medium and high  $V_t$  grade available
  - Medium grade  $V_t$  is targeted towards a few watts of leakage power for a “large” chip
- Judicial usage of lower  $V_t$  grades are required
  - “Rationing” of faster grades of transistor specified by the methodology book
  - Past design data points needs to be taken into consideration

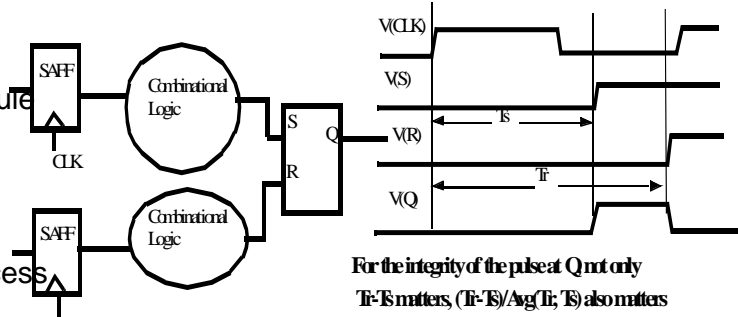
# Racing Criteria

- Minimum number of logic gates between flops
  - Not meant to be a replacement for final hold time check; more for an early feedback for hold time issues or inappropriate hold time fixes
- Minimum % difference rule between racing paths
  - Delay elements with metal option enable are typically used to deal with modeling errors
- Minimum pulse width rule
  - Dynamic gate in
  - pre-charging process
  - Nodes driven by
  - multiple tri-state drivers
- “Power races”
  - Dynamic gate in
  - pre-charging process
  - Nodes driven by
  - multiple tri-state drivers




 
# RAM Structures

- Speed estimation: bit line separation rate
- Leakage related functionality issue:
  - Pathological worse case: for a bit line of n bits, 1 bit with data active pull down, n-1 bits with data\_bar leaking
  - Max bit line length (# of bits)



  
## RAM Structures (cont.)

- Redundancy rules
  - Number of spare rows/columns per bank of x bits
- Sense Amp margin rule
  - mV of differential signal when “sense amp fires”:  $V(\text{clk}) = V_t$
- Simulation sequence
  - RAW case with opposite data typical worst case
  - Need to factor in leakage worst case
  - WAW, RAW, RAR can also be worst case depending on design


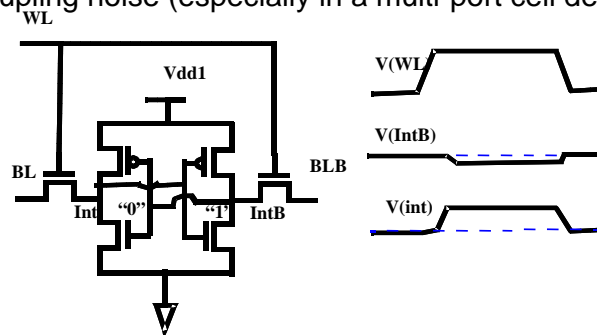
## RAM Structures (Cont.)

- Cell Stability
  - “Text book definition”
- Practical design consideration:
  - Need to consider power supply offset, and wordline/bitline coupling noise (especially in a multi-port cell design)



For read-disturb, consider  $V(\text{WL}) > V_{\text{dd1}}$   
 For writability, consider  $V(\text{WL}) < V_{\text{dd1}}, V(\text{BL}) > 0$

## Reliability Related Rules of Thumb

---

- Electromigration
  - Average current limit
  - RMS current limit: Self-heating accelerated degradation
  - Current industry flow: Post layout static analysis
  - Goal for the “rule of thumb”: reduce # of violations and # of iterations
- Current profile related to: clock rate, activity factor, load cap, fanout
- Rule of thumb characterization
  - De-rated load per “nominal” wire/via

## Rules for Better Productivity

---

- Direction of data flow
- Sizes of schematics
- Bit ordering
- Matching of hierarch between schematics and layout
- Naming convention

## Min/Max Transistor Width

---

- Min width
  - Typically the width that allows a single contact
  - Avoid dog-bone style layout and “cliff” for narrow width effect
  - Increase the channel length if “weaker” driver is desired
  - Usually want to avoid  $L > 2xL_{min}$
  - Putting transistor with same gate driver in series rather than using  $> 2xL_{min}$  if needed
- Max. width (per finger)
  - RC of silicided gate:
    - 0.1 $\mu$ m,  $W=X_{um}$ , gate RC = 10% fan of 4 delay (single sided contact)

## Datapath Pitch



---

- Function of design and interconnect technology availability
- Min. width bounded by the need to cover the per bit pitch wire routing band width
- Max. width bounded by impact on clock skew across dp
- Other considerations:
  - DP aspect ratio
  - Delay for control signals
  - Track plan



  
## Rules for Better Electrical Integrity

- Non-strapped diffusion rule
  - How often can one skip contacts
- “Poly jumper rule”
  - How long can a poly interconnect be


 
## Rules for Better Electrical Integrity

- IR drop “budgeting”
  - Global vs. local IR drop
  - Maximum distance between power strapping in non grid layers as a function of “current source distributions”



# Conclusions

---

- Rule books provides a way to
  - Ensure the functionality
  - Increase performance
  - Increase productivity
- Compromises are needed
- Dynamic change as design/process technology makes forward progress