
Lecture 4

Adders

Computer Systems Laboratory
Stanford University
horowitz@stanford.edu

Copyright © 2006 Mark Horowitz
Some figures from High-Performance Microprocessor Design © IEEE

Overview

- Readings


- Today's topics
 - Fast adders generally use a tree structure for parallelism
 - We will cover basic tree terminology and structures
 - Look at a few example adder architectures
 - Examples will spill into next lecture as well

Adders

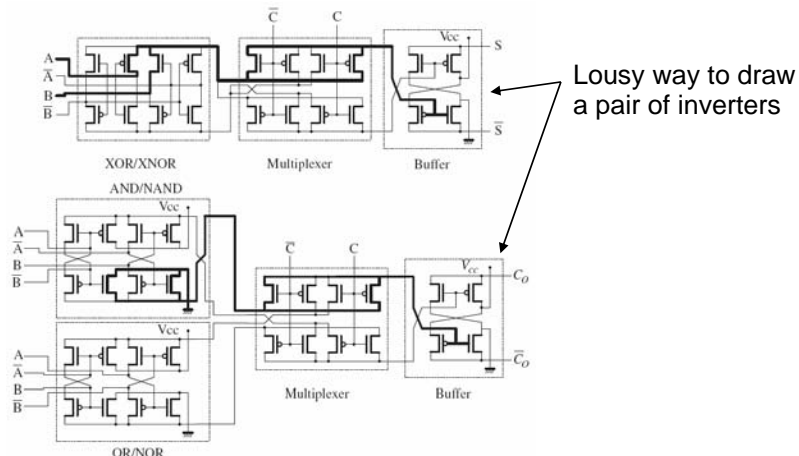- Task of an adder is conceptually simple
 - $\text{Sum}[n:0] = A[n:0] + B[n:0] + C_0$
 - Subtractors also very simple: $-B = \sim B + 1$, so invert B and set $C_0 = 1$
- Per bit formulas
 - $\text{Sum}_i = A_i \text{ XOR } B_i \text{ XOR } C_i$
 - $\text{Cout}_i = C_{i+1} = \text{majority}(A_i, B_i, C_i)$
- Fundamental problem is calculating the carry to the n^{th} bit
 - All carry terms are dependent on all previous terms
 - So LSB input has a fanout of n
 - And an absolute minimum of $\log_4 n$ FO4 delays without any logic

Single-Bit Adders

- Adders are chock-full of XORs, which make them interesting
 - One of the few circuits where pass-gate logic is attractive
 - A complicated differential passgate logic (DPL) block from the text



G and P and K, Oh My!

- Most fast adders “G”enerate, “P”ropagate, or “K”ill the carry
 - Usually only G and P are used; K only appears in some carry chains
- When does a bit Generate a carry out?
 - $G_i = A_i \text{ AND } B_i$
 - If G_i is true, then $\text{Cout}_i = C_{i+1}$ is forced to be true
- When does a bit Propagate a carry in to the carry out?
 - $P_i = A_i \text{ XOR } B_i$
 - If P_i is true, then $\text{Cout}_i (=C_{i+1})$ follows C_i
 - Usually implemented as $P_i = A_i \text{ OR } B_i$
 - OR is cheaper/faster than an XOR
 - If you are doing logic, Cout_i is still equal to $G_i + P_i C_i$
 - Just beware that $\text{Sum}_i \neq P_i \text{ XOR } C_i$

Using G and P

- We can combine G_i and P_i into larger blocks
 - Call these “group generate” and “group propagate” terms
- When does a group Generate a carry out? (e.g., 4 bits)
 - $G_{3:0} = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0$
- When does a group Propagate a carry in to the carry out?
 - $P_{3:0} = P_3 P_2 P_1 P_0$
- We can also combine groups of groups
 - $G_{i:j} = G_{i:k} + P_{i:k} G_{k-1:j}$
 - $P_{i:j} = P_{i:k} P_{k-1:j}$



Linear Adders Using P,G

- Simple adders ripple the carry; faster ones bypass it
 - Better to try to work out the carry several bits at a time
- Best designs are around 11FO4 for 64b
 - Useful for small adders (16b) and moderate performance long adders
- Example of carry bypass from the text


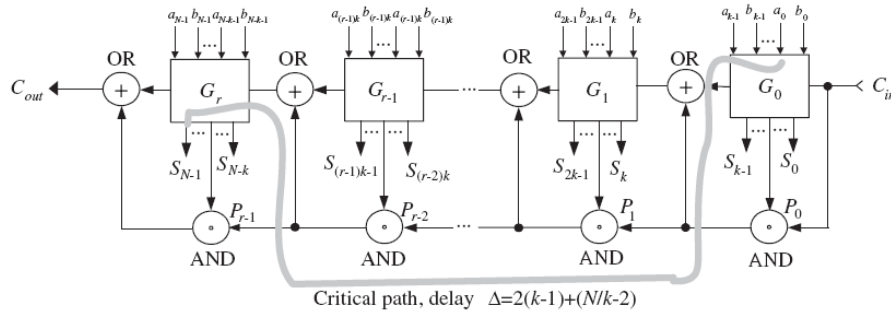


Figure Is Not Quite Right

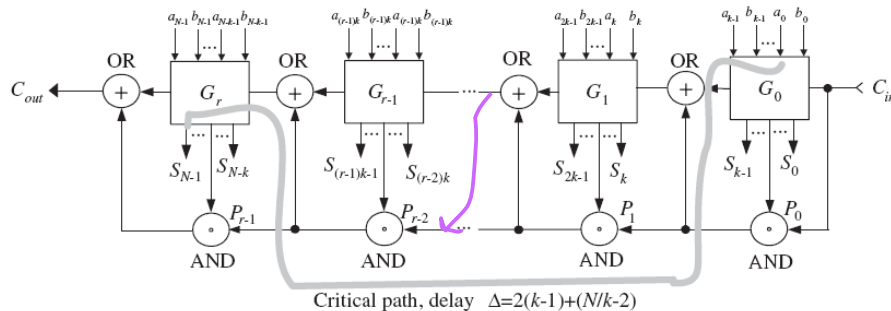- How does the drawn critical path go **down** from the OR gate?!
 - Fix: The OR gate output is the true input to the next group
- Subtle point: Each block spits out a G term for the OR
 - Not simply a C_{out} term
 - Avoids a nasty critical path ($11\dots 1 + 00\dots 0 + C_{in}$; C_{in} goes $1 \rightarrow 0$)




Faster Carry Bypass (or Carry Skip) Adders

- We see the basic idea is to form multi-level carry chains
 - Break the bits into groups
 - Ripple the carry in each group, in parallel
 - Ripple the global carry across the groups
- How big should each group be? (N bits total, k bits per group)
 - If ripple time equals block skip time then delay = $2(N-1) + (N/k - 2)$
- Would groups of different sizes be faster? (yes)
 - Middle groups have longer to generate carry outs; should be larger
 - Early and late groups have ripples in critical path; should be shorter
 - Called “Variable Block Adders”

Carry Select Adders

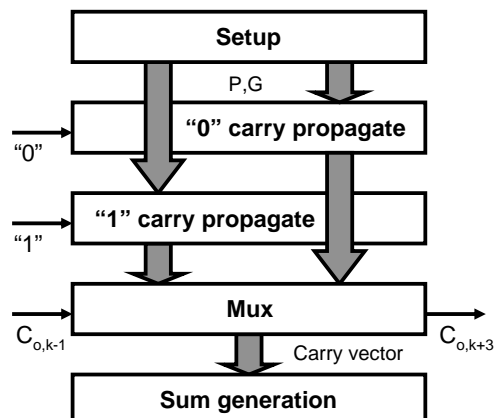- Why wait for the carry in? (If you can't find parallelism, invent it!)
 - Calculate answers for a group assuming $C_i = 1$ AND $C_i = 0$
 - Use two adders, and rely on the fact that transistors are cheap
 - Don't do this on the full adder (too expensive), just the MSBs



Many Papers on These Adders

- But no one builds them anymore
 - Or rather, nobody publishes papers on them (or gets PhDs on them)
- These are all clever improvements on adders
 - That tend to optimize transistors along with performance
 - Or are best for narrow-width operands ($n=64$ is slow)
- But scaling is pushing these adders to the wayside
 - We have very wide-word machines (media applications)
 - We have more transistors than we know what to do with
- Question: As power density questions increase...
 - ... will these “simpler” adders make a comeback?

Logarithmic, or Tree, Adders

- Fundamental problem: to know C_i , we need C_{i-1}
 - So delay is linear with n , and this dominates for wide adders ($n>16$)
 - Can we lookahead across multiple levels to figure out carry? Yes.
 - Called “prefix computation” – turns delay into logarithmic with n
- Notation is always an issue; everybody does it differently
 - Here, $A_{i:j}$ means the signal “A” for group the i^{th} to j^{th} position
 - P = propagate (A+B)
 - G = generate (AB)
 - C = CarryIn to this bit/Group position

Logic Stages For Logarithmic/Tree Adders

1. Compute single bit values

$$0 \leq i < n \quad G_i = A_i B_i \quad P_i = A_i + B_i$$

2. Compute two-bit groups

$$0 \leq i < (n/2) \quad G_{2i+1:2i} = G_{2i+1} + G_{2i} P_{2i+1} \quad P_{2i+1:2i} = P_{2i+1} P_{2i}$$

3. Compute four-bit groups

$$0 \leq i < (n/4) \quad G_{4i+3:4i} = G_{4i+3:4i+2} + G_{4i+1:4i} P_{4i+3:4i+2} \quad P_{4i+3:4i} = P_{4i+3:4i+2} P_{4i+1:4i}$$

4. ...Go down tree for G&P, then go back up for Cin...

5. Compute four-bit carries

$$0 \leq i < (n/8) \quad C_{8i+7:8i+4} = G_{8i+3:8i} + C_{8i+7:8i} P_{8i+3:8i} \quad C_{8i+3:8i} = C_{8i+7:8i}$$

6. Compute two-bit carries


$$0 \leq i < (n/4) \quad C_{4i+3:4i+2} = G_{4i+1:4i} + C_{4i+3:4i} P_{4i+1:4i} \quad C_{2i+1:2i} = C_{2i+3:2i}$$

7. Compute single-bit carries

$$0 \leq i < (n/2) \quad C_{2i+1} = G_{2i} + C_{2i+1:2i} P_{2i} \quad C_{2i} = C_{2i+1:2i}$$

An Eight-bit Example

 
- “Lines and dots” notation shows the tree structure clearly



- Takes $\log_2 n$ time to get the final carry-out ($C_{out_7} = G_{7:0}$)


An Eight-Bit Example, Redrawn

 - More common to line up the PG terms with their appropriate bits



Layout Of Our Example Tree Adder

 - Logarithmic structures have somewhat ugly layout



- Worst wire length grows as n increases ($n=64?$ $128?$)

That Was Half The Algorithm...

1. Compute single bit values

$$0 \leq i < n \quad G_i = A_i B_i \quad P_i = A_i + B_i$$

2. Compute two-bit groups

$$0 \leq i < (n/2) \quad G_{2i+1:2i} = G_{2i+1} + G_{2i} P_{2i+1} \quad P_{2i+1:2i} = P_{2i+1} P_{2i}$$

3. Compute four-bit groups

$$0 \leq i < (n/4) \quad G_{4i+3:4i} = G_{4i+3:4i+2} + G_{4i+1:4i} P_{4i+3:4i+2} \quad P_{4i+3:4i} = P_{4i+3:4i+2} P_{4i+1:4i}$$

4. ...Go down tree for G&P, then go back up for Cin...

5. Compute four-bit carries

$$0 \leq i < (n/8) \quad C_{8i+7:8i+4} = G_{8i+3:8i} + C_{8i+7:8i} P_{8i+3:8i} \quad C_{8i+3:8i} = C_{8i+7:8i}$$

6. Compute two-bit carries


$$0 \leq i < (n/4) \quad C_{4i+3:4i+2} = G_{4i+1:4i} + C_{4i+3:4i} P_{4i+1:4i} \quad C_{2i+1:2i} = C_{2i+3:2i}$$

7. Compute single-bit carries

$$0 \leq i < (n/2) \quad C_{2i+1} = G_{2i} + C_{2i+1:2i} P_{2i} \quad C_{2i} = C_{2i+1:2i}$$


An Eight-Bit Example, Finished

 - A Brent-Kung adder (1982): what's the critical path?




A 16b Brent-Kung Adder

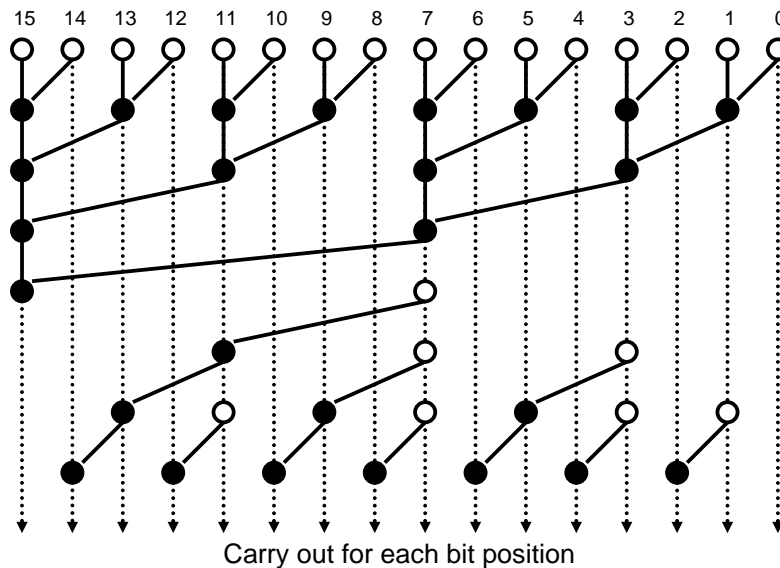- Limit fanout to 2 (can collapse some nodes with higher FO)




Many Kinds of Tree Adders

 
- We can vary some basic parameters
 - Radix, tree depth, wiring density, and fanout
- Radix: how many bits are combined in each Pgroup, Gg term?
 - Radix is generally < 4 (why not more?); prior example was 2
 - Radix- n can just compute the P $_g$ and G $_g$ terms directly



Radix-2 block

 

Radix-3 block

 


Radix-4 block


- Or it can compute the intermediate P $_g$ and G $_g$ terms as well



Radix-2 block

 


Radix-3 block

 

Radix-4 block

Building Multiple-Bit PG blocks

 
- Radix-4 Pg, Gg block that generates intermediate terms
 - Spits out “ $P_{3:0}$ ” and “ $G_{3:0}$ ” terminology
 - Also spits out P_3, G_3, P_2, G_2 and passes along P_1, G_1




- Allows for quick computation of the various carries, once we know C_{in}
- How do we build this block?

Building Multiple-Bit PG blocks, con't

 - Can we use dynamic logic to build fast blocks?
 - A Manchester carry chain can “gather” the multiple-bit G terms




 - For C , since we already have Pgs and Ggs we can do better




Dynamic Logic for 4-Bit PG Block

- Motorola design

 


32b Mixed-Radix Brent-Kung Adder

 - Vary radices at different tree levels because n may not be $(\text{radix})^k$




32b Mixed-Radix, Redrawn As Folded Tree

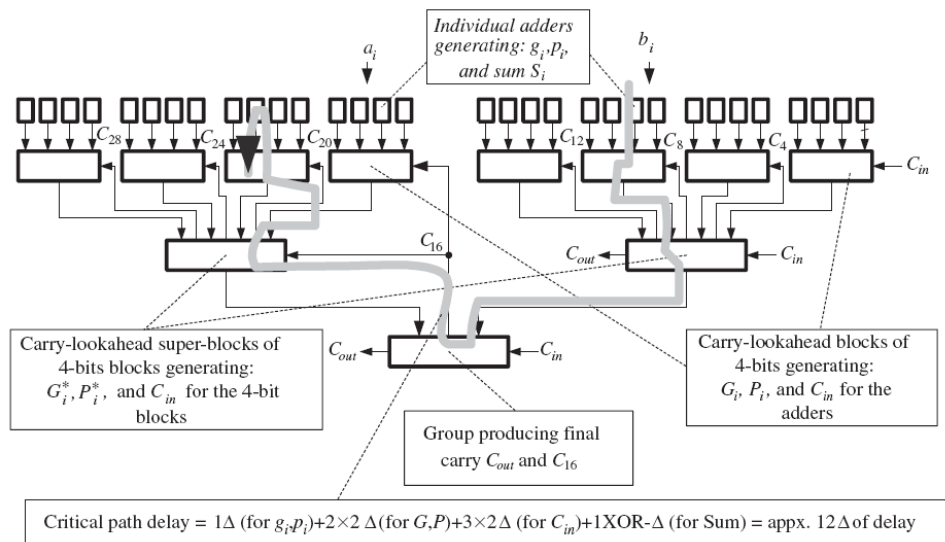- PG goes “down” and Carry goes back “up”




64b Radix-4 Brent-Kung Adder

 - Takes longer to draw in Powerpoint than it does to design!



Radix 4 PG and Carry Trees

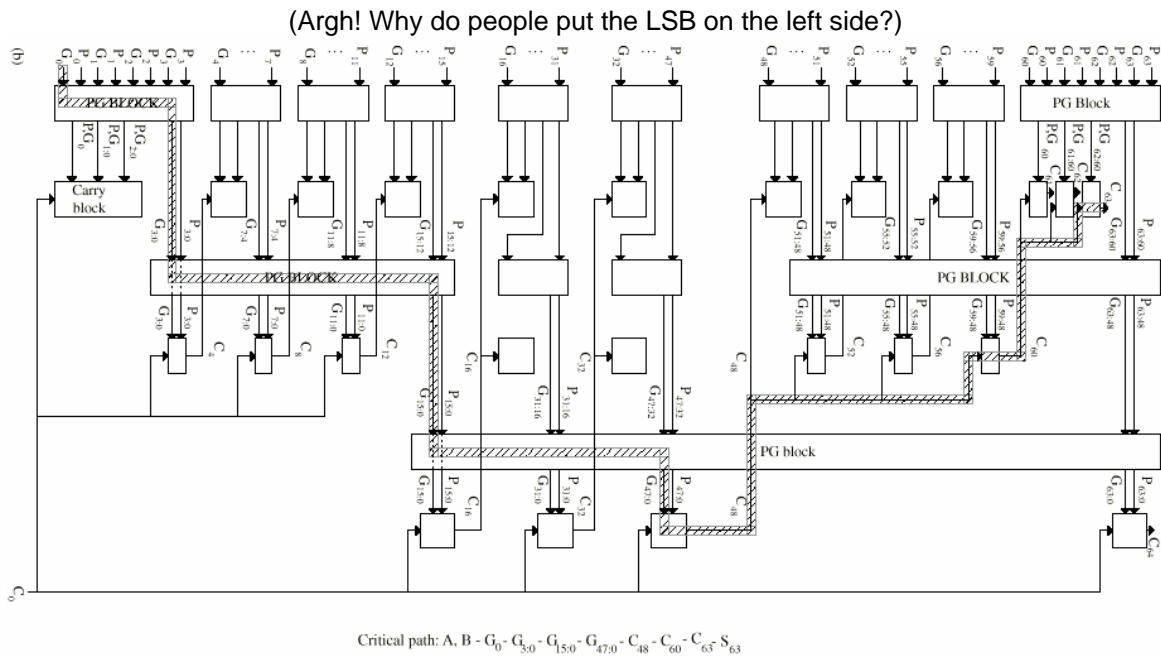


Tree Depth, Wiring Density, and Fanout

- Previous slides have all examined changing the adder radix
- We can also change the tree depth, wire density, and/or fanout
 - These usually get changed together; one affects the others
 - Density: How many wires criss-cross the tree?
 - Depth: How many stages of logic?
 - Fanout: How far is the reach of each stage?
- Reduce depth by chopping trees
 - Many adders use carry select at the final stage
 - Compute two results, and use a carry to select right result
 - Eliminate the carry tree altogether
 - Increasing wiring density or increasing fanout

A Very Dense 16b Tree

 - Eliminate the carry out tree by computing a group for each bit
 - Kogge-Stone architecture (1973)




- Lots of wires, but minimizes the number of logic levels
- We can use this for a quick swag at the minimum delay

Minimum 64b Adder Delay

- Make a few assumptions
 - Output load is equal to the load on each input
 - Use static gates; very aggressive domino logic may change results
- Simple approximation
 - Need to compute $\text{Sum}_i = A_i \text{ XOR } B_i \text{ XOR } C_i$
 - C_{in} (LSB) must fanout to all bits for a fanout of 64
 - Extra logic in chain raises effective fanout to about 128 \rightarrow 3.5 FO4
- More complicated approximation
 - At each stage, P drives 3 gates, G drives 2; effective fanout $\frac{1}{4}$ 3.5
 - Total fanout = 1.5 (first NAND/NOR) * 3.5^6 * 1-ish (final mux)
 - 5.7 FO4, not really accounting for parasitic delay correctly


Higher Radix Still Possible

 - Radix-4 Kogge-Stone tree
 - Trades off two layers of logic for lots and lots of wires
- Not a good idea in CMOS – it tends to increase stage efforts $\gg 4$
 - Not bad, though, for domino – much lower logical effort



Reduce Depth With Fanout

 - Can also reduce tree depth by increasing the stage fanouts
 - Sklansky (1960) called this a “divide-and-conquer” tree
 - Fanouts increase the further from the start you go




A Taxonomy

- Following Harris's 2003 paper
 - Assume 16b radix-2 adder families for this discussion
 - We can modify tree's depth, fanout, and wiring density
- What we've seen already
 - Brent-Kung: 7 logic levels, fanout of 2, one wiring track enough
 - Kogge-Stone: 4 logic levels, fanout of 2, eight wiring tracks
 - Sklansky: 4 logic levels, fanout of up to 9, one wiring track enough
- Formalism: Use a triplet (l,f,t) to represent the adders
 - Logic levels = $\log_2 N + l$ Brent-Kung: (3,0,0)
 - Fanout = $2^f + 1$ Kogge-Stone: (0,0,3)
 - Wiring tracks = 2^t Sklansky: (0,3,0)

Points on a plane?

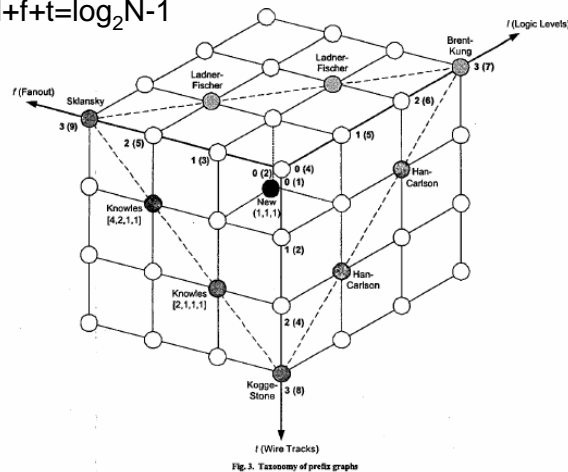
- All major adder architectures fall onto the same plane
 - Defined by $l+f+t=\log_2 N-1$




- Using this, we may expect a Han-Carlson adder to...
 - Trade off logic layers for some increased wiring

Han-Carlson Adder (1987)

 - Think of this as a sparse Kogge-Stone
 - Called a sparse tree with sparseness of 2



Adder Tradeoffs

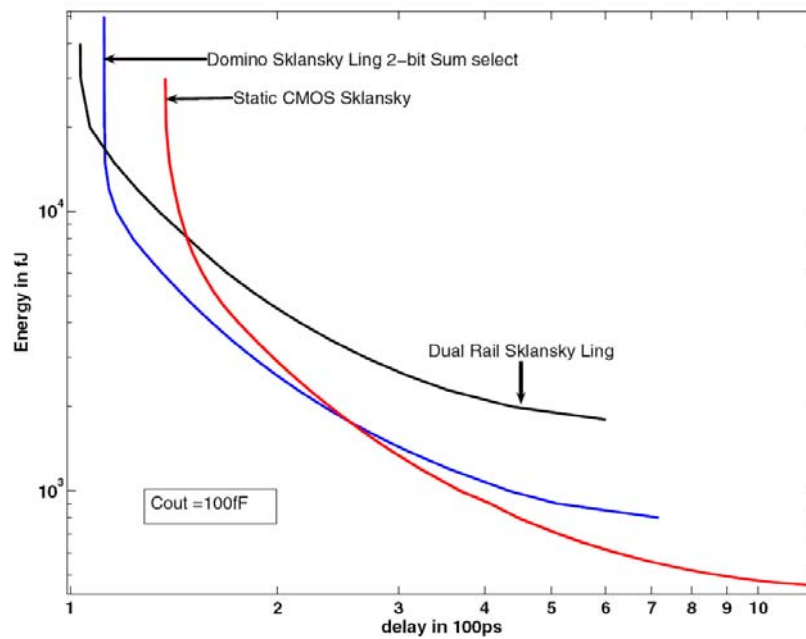

Other Sparse Trees

