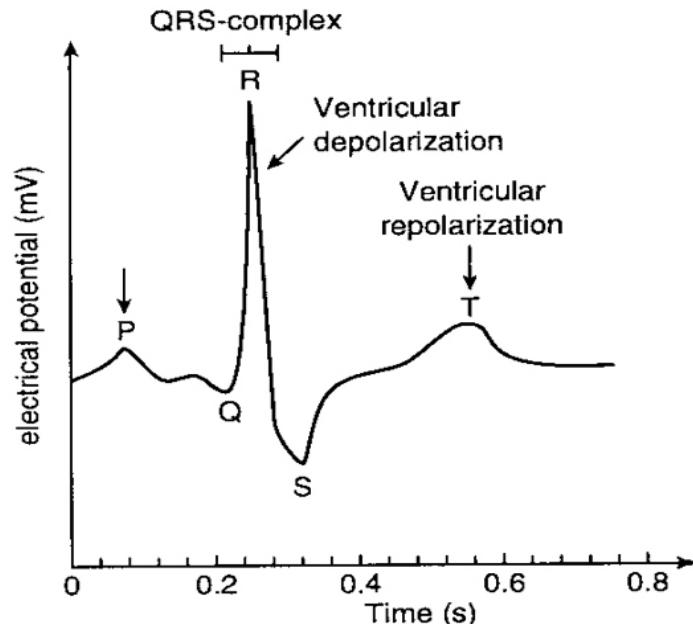


---


# E40M

## Instrumentation Amps and Noise
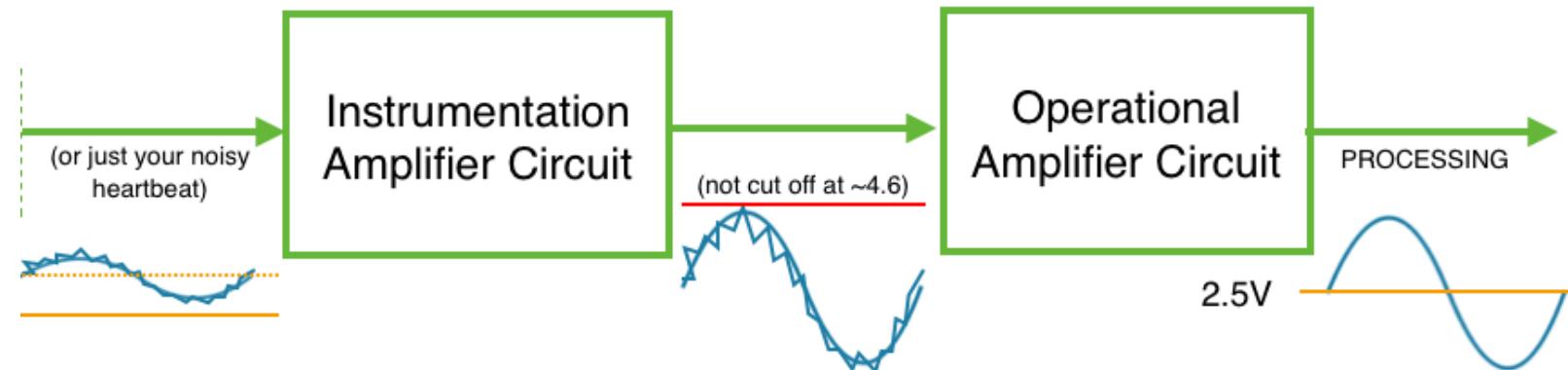
# ECG Lab - Electrical Picture




- Signal amplitude  $\approx 1 \text{ mV}$
- Noise level will be significant
- $\therefore$  will need to amplify and filter
- We'll use filtering ideas from the last set of lecture notes



---

# INSTRUMENTATION AMP
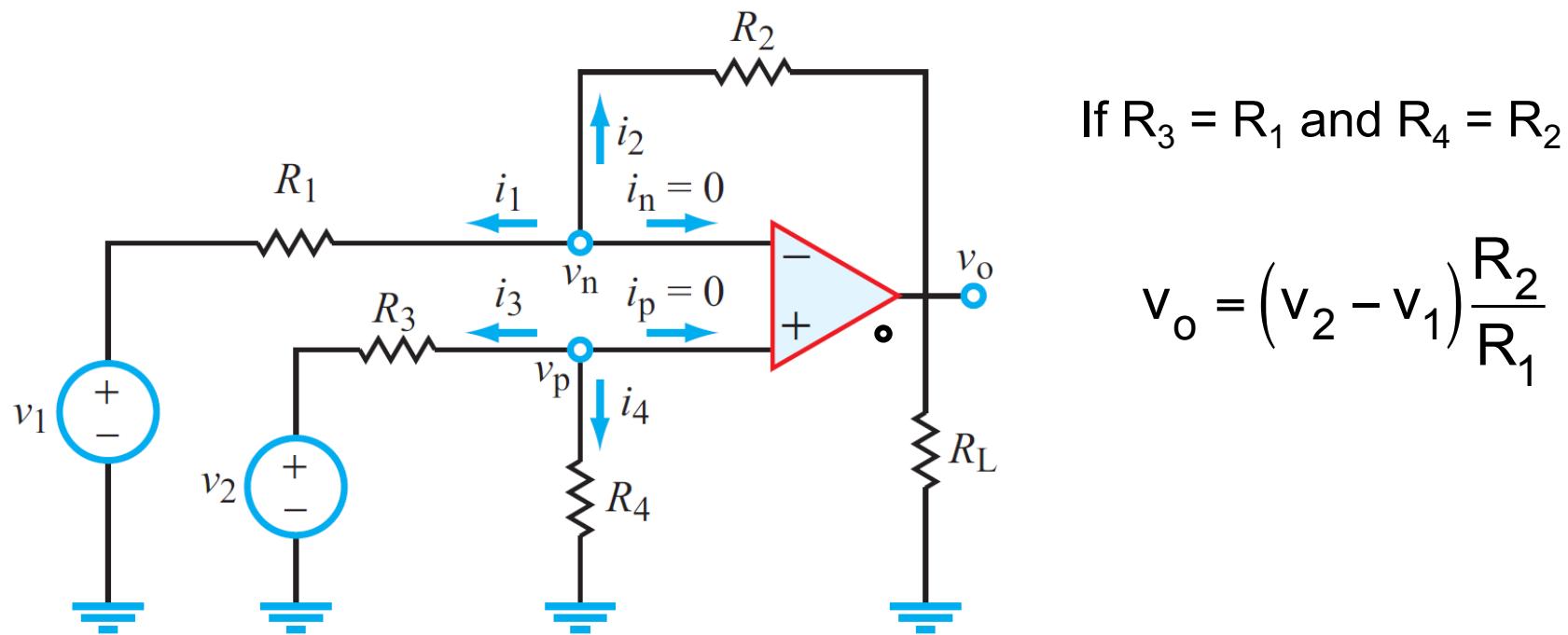
# Starting Point: Differential Amplifier 1.0



- This amplifier requires that the input voltage sources provide input currents ( $i_1$  and  $i_3$  are not zero) ... *not OK* for the ECG project or a general-purpose instrumentation amplifier.

# We Need A Differential Amplifier With No Input Current


---

- Want really want a differential amplifier with no input current
  - Make sure the input isolation resistance isn't a problem
  - This is a common situation for many types of instruments
- There is a special part for this situation
  - Called instrumentation amplifier
  - It can be thought of as 3 amplifiers
    - Two non-inverting amplifiers (so there is no input current)
    - One differential amplifiers
  - These parts are built to match very well
    - So it is better than building the circuit yourself

# Instrumentation Amp (Used in ECG Lab)


- Kind of looks like two non-inverting amplifiers
  - But they are connected together in a funny way
- Fortunately the IA can be “solved” using the Golden Rules:
  - Write KCL for ‘-’ input of the op amp
  - Find the output voltage that satisfies KCL when the voltage at the ‘-’ input is equal to the voltage on the ‘+’ input

**Simplified Schematic: INA126**

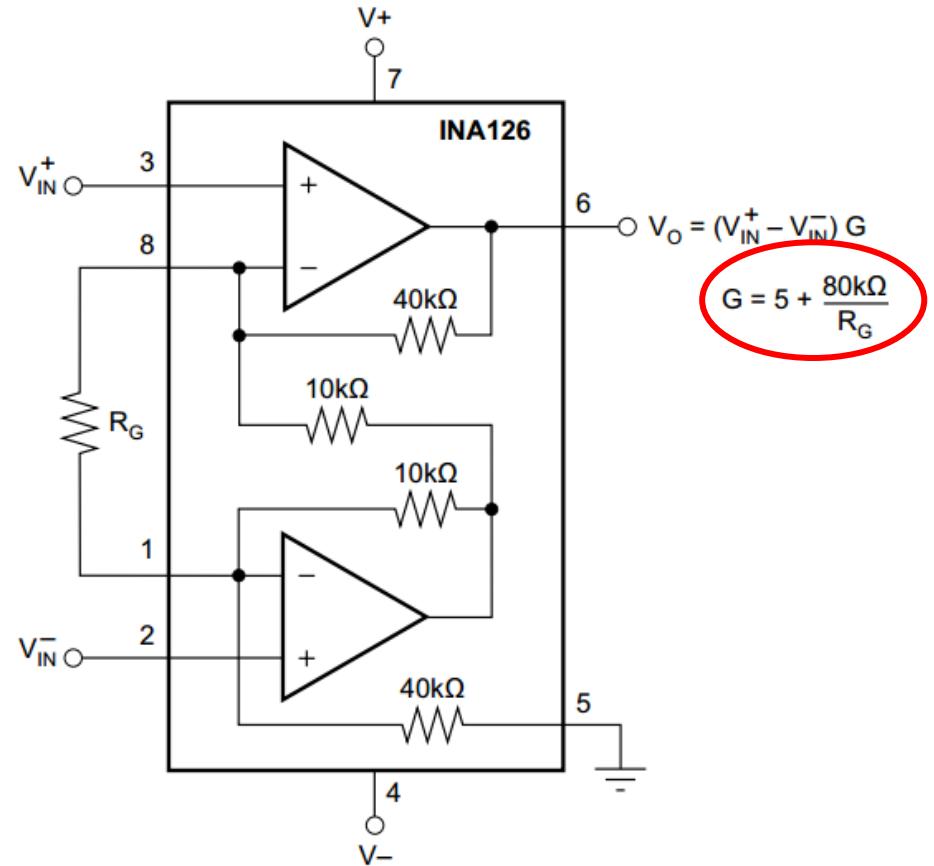

# Start with KCL at Inverting Input of Op Amp #1

**Simplified Schematic: INA126**

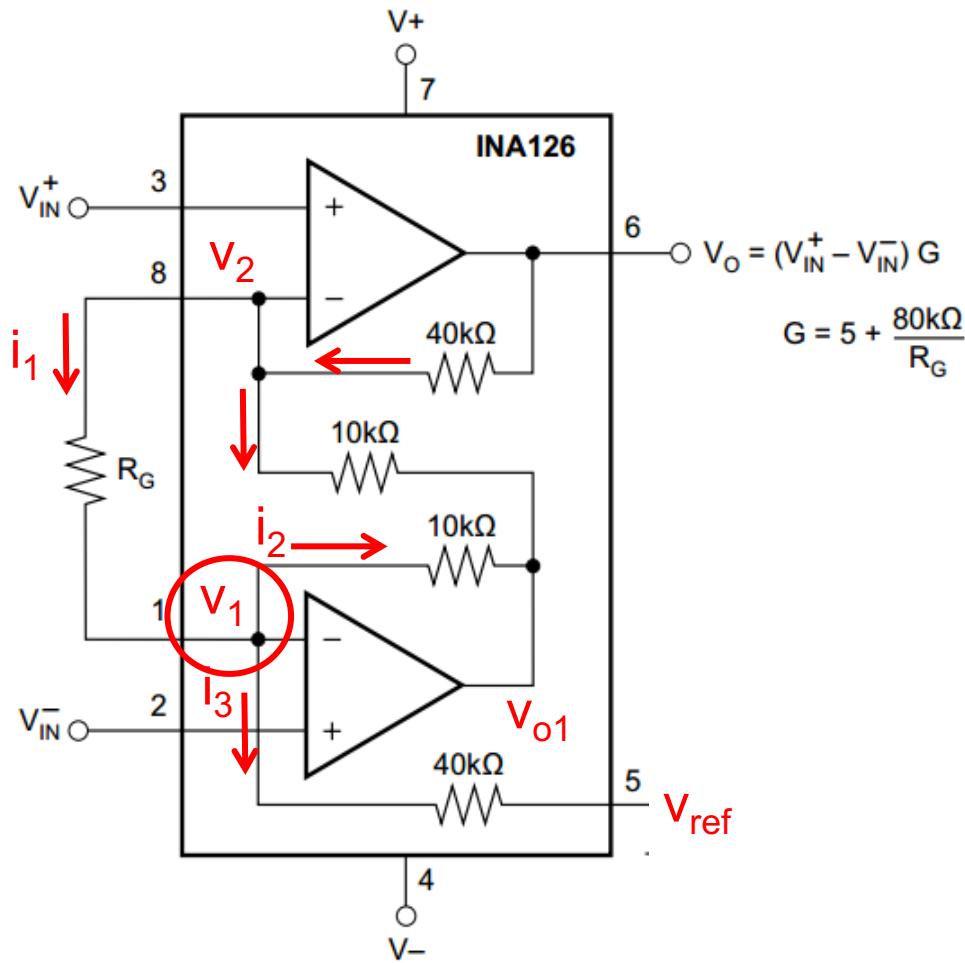

- At node  $v_1$  and assuming no op amp input current, we have

$$i_1 = i_2 + i_3$$


$$\therefore \frac{v_2 - v_1}{R_G} = \frac{v_1 - v_{o1}}{10k\Omega} + \frac{v_1 - v_{ref}}{40k\Omega}$$

- Since  $v_{IN}^- = v_1$  and  $v_{IN}^+ = v_2$

$$\therefore \frac{v_{IN}^+ - v_{IN}^-}{R_G} = \frac{v_{IN}^- - v_{o1}}{10k\Omega} + \frac{v_{IN}^+ - v_{ref}}{40k\Omega}$$

# Now Find $V_{o1}$ -- the Output Voltage of Op Amp #1

## Simplified Schematic: INA126

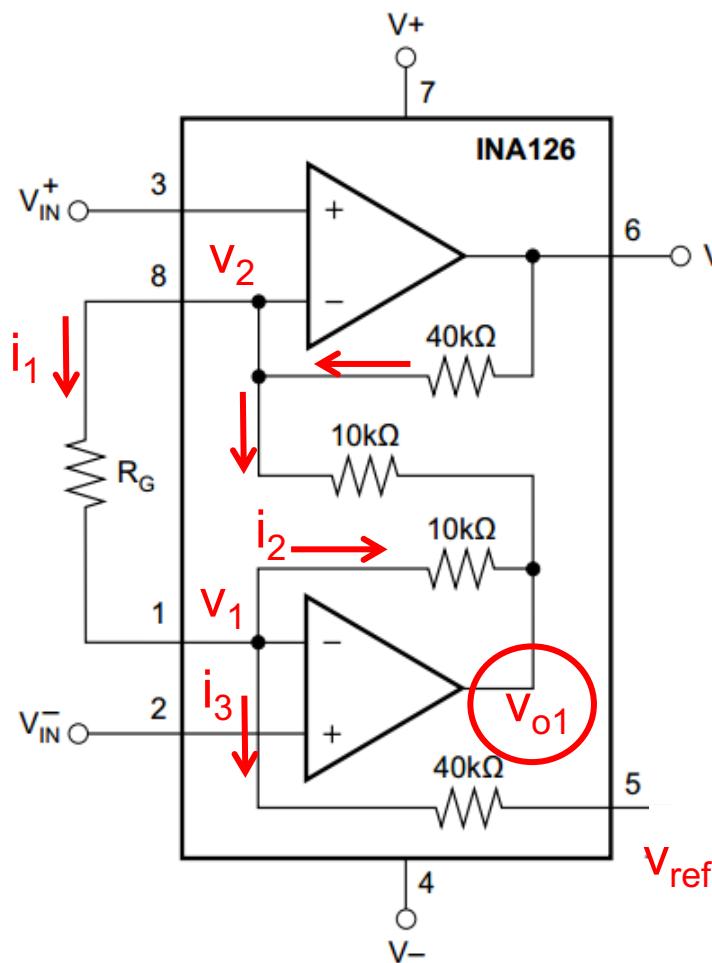

$$\therefore \frac{V_{IN}^+ - V_{IN}^-}{R_G} = \frac{V_{IN}^- - V_{o1}}{10k\Omega} + \frac{V_{IN}^+ - V_{ref}}{40k\Omega}$$


$$G = 5 + \frac{80k\Omega}{R_G}$$

$$\therefore \frac{V_{o1}}{10k\Omega} = \frac{V_{IN}^-}{10k\Omega} + \frac{V_{IN}^+ - V_{ref}}{40k\Omega} - \frac{V_{IN}^+ - V_{IN}^-}{R_G}$$

$$\therefore V_{o1} = \frac{5V_{IN}^-}{4} - \frac{V_{ref}}{4} - \frac{10k\Omega(V_{IN}^+ - V_{IN}^-)}{R_G}$$

## Next: KCL at Inverting Input of Op Amp #2

**Simplified Schematic: INA126**

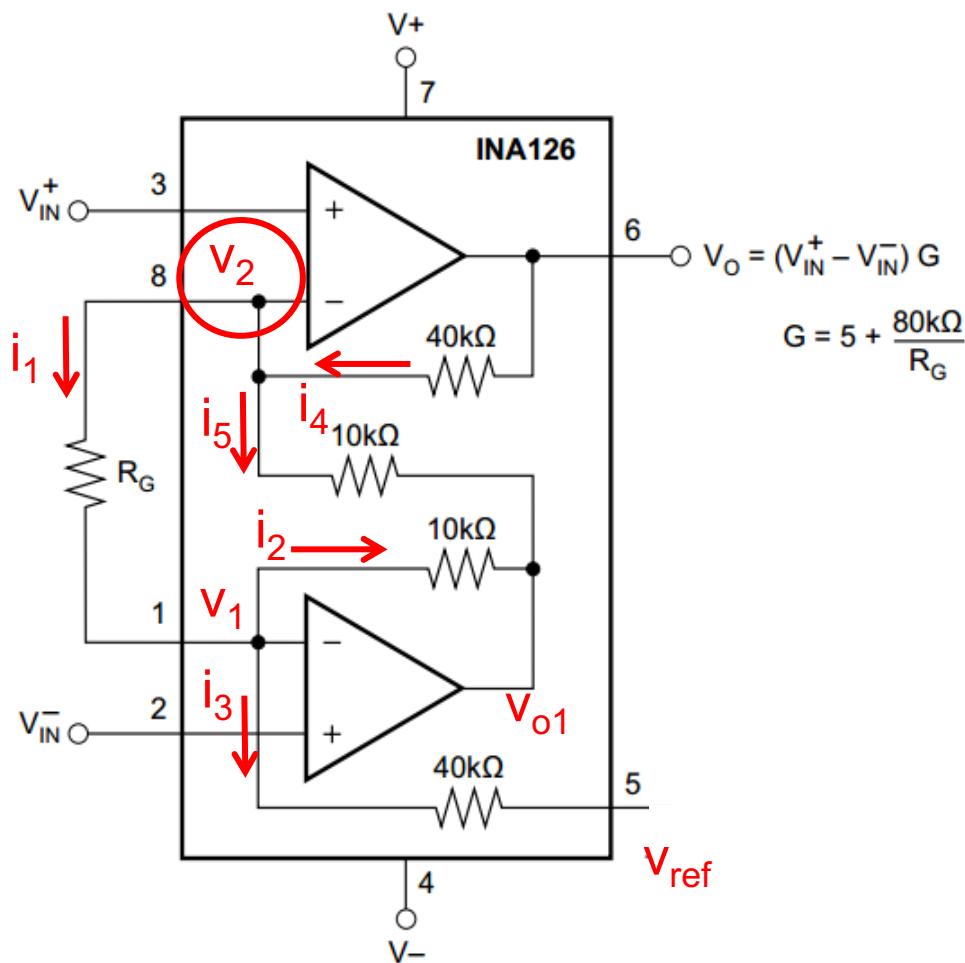

- At node  $v_2$  and assuming no op amp input i, we have

$$i_4 = i_1 + i_5$$


$$\therefore \frac{V_O - V_2}{40k\Omega} = \frac{V_2 - V_1}{R_G} + \frac{V_2 - V_{O1}}{10k\Omega}$$

- Since  $V_{IN}^- = V_1$  and  $V_{IN}^+ = V_2$

$$\therefore \frac{V_O - V_{IN}^+}{40k\Omega} = \frac{V_{IN}^+ - V_{IN}^-}{R_G} + \frac{V_{IN}^+ - V_{O1}}{10k\Omega}$$

## Step n+1: Solve for $V_o$

### Simplified Schematic: INA126

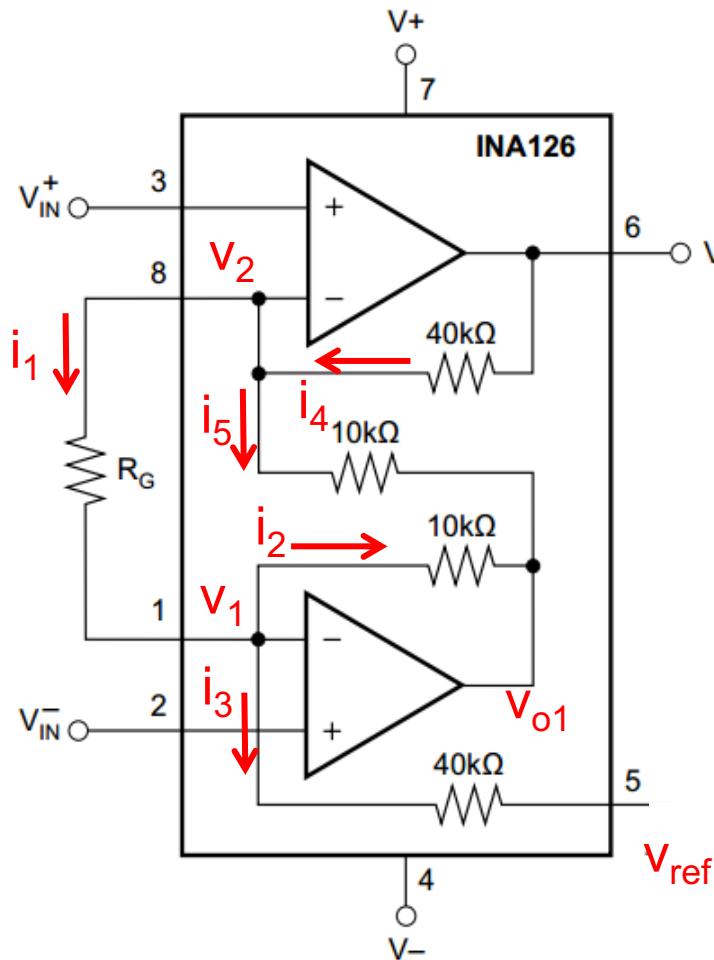

$$\therefore \frac{V_o - V_{IN}^+}{40k\Omega} = \frac{V_{IN}^+ - V_{IN}^-}{R_G} + \frac{V_{IN}^+ - V_{o1}}{10k\Omega}$$


$$G = 5 + \frac{80k\Omega}{R_G}$$

$$\therefore \frac{V_o}{40k\Omega} = \frac{V_{IN}^+}{40k\Omega} + \frac{V_{IN}^+ - V_{IN}^-}{R_G} + \frac{V_{IN}^+ - V_{o1}}{10k\Omega}$$

$$\therefore V_o = 5V_{IN}^+ + \frac{40k\Omega(V_{IN}^+ - V_{IN}^-)}{R_G} - 4V_{o1}$$

# The Finale: Combining The Results

**Simplified Schematic: INA126**

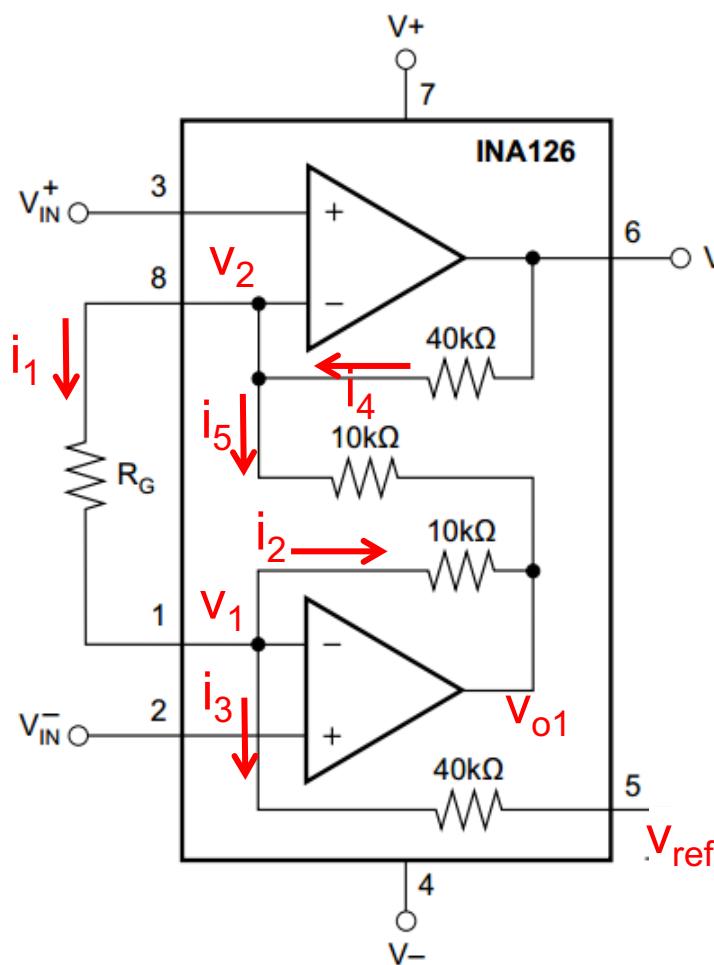

$$G = 5 + \frac{80\text{k}\Omega}{R_G}$$

$$V_{o1} = \frac{5V_{IN}^-}{4} - \frac{V_{ref}}{4} - \frac{10\text{k}\Omega(V_{IN}^+ - V_{IN}^-)}{R_G}$$

$$V_o = 5V_{IN}^+ + \frac{40\text{k}\Omega(V_{IN}^+ - V_{IN}^-)}{R_G} - 4V_{o1}$$


$$V_o = \left( \frac{80\text{k}\Omega}{R_G} + 5 \right) (V_{IN}^+ - V_{IN}^-) + V_{ref}$$

- This confirms the gain expression given in the 1NA126 data sheet! (using  $V_{ref} = 0$ ).
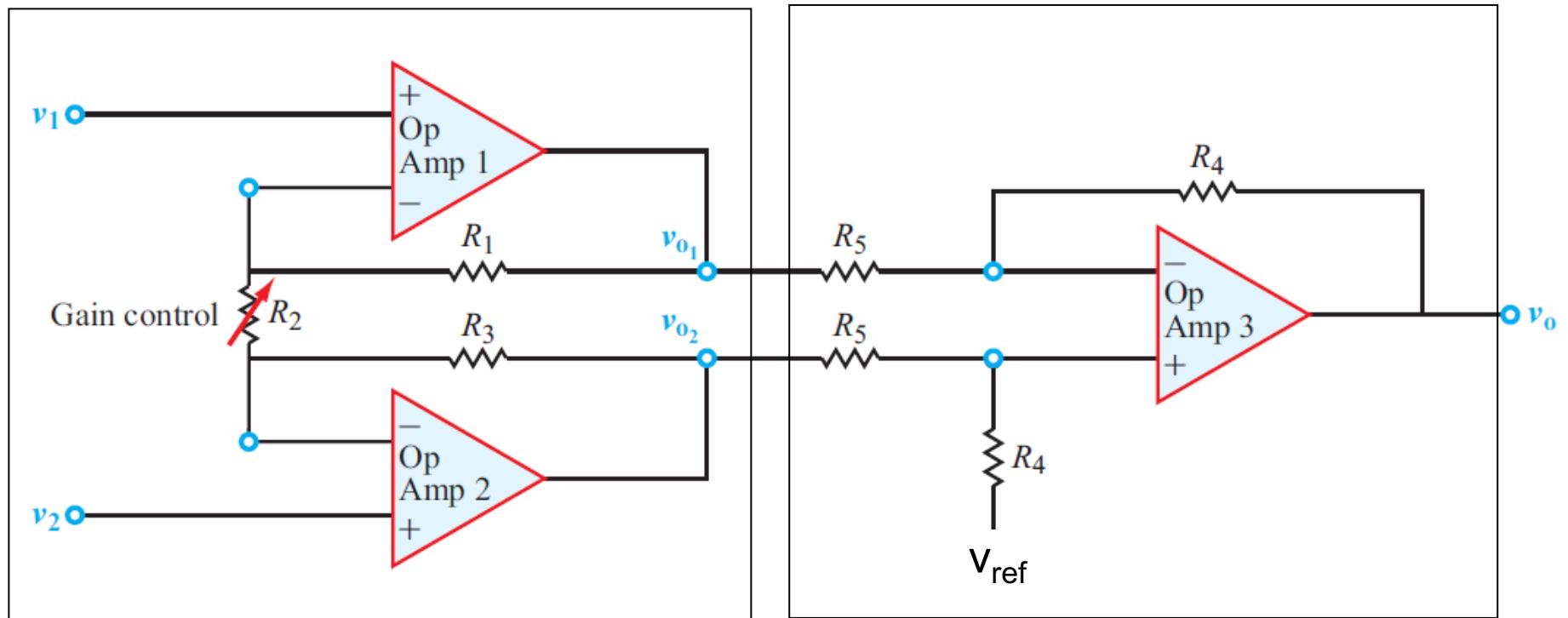
# Another Instrumentation Amplifier (Bonus)


(we are not using this architecture)

- Most instrumentation amplifiers are actually built with 3 op amps.
- The analysis is quite similar to the past few pages



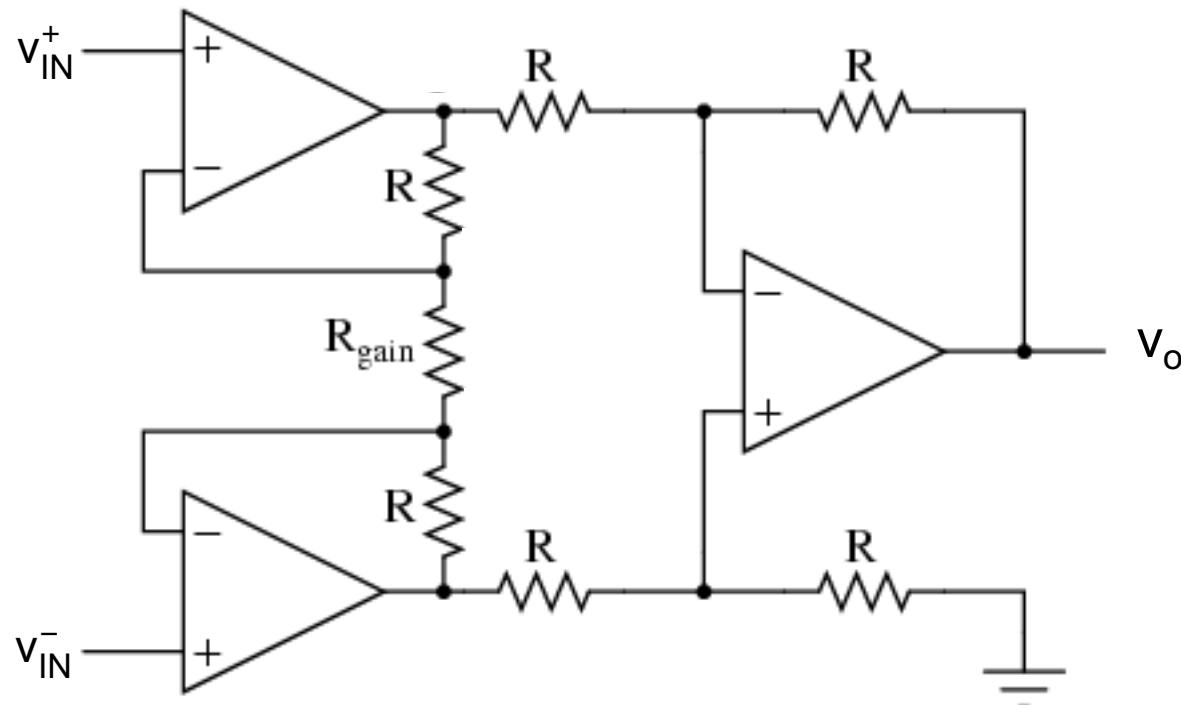
## Another Instrumentation Amplifier (Bonus)

- Consider a simplified case in which all resistors are the same (except  $R_{\text{gain}}$ ) and  $v_{\text{ref}} = 0$ .
- The analysis is quite similar to the past few pages.
- We won't cover this in class – try it yourself, you should be able to analyze this! Try it to test your understanding.


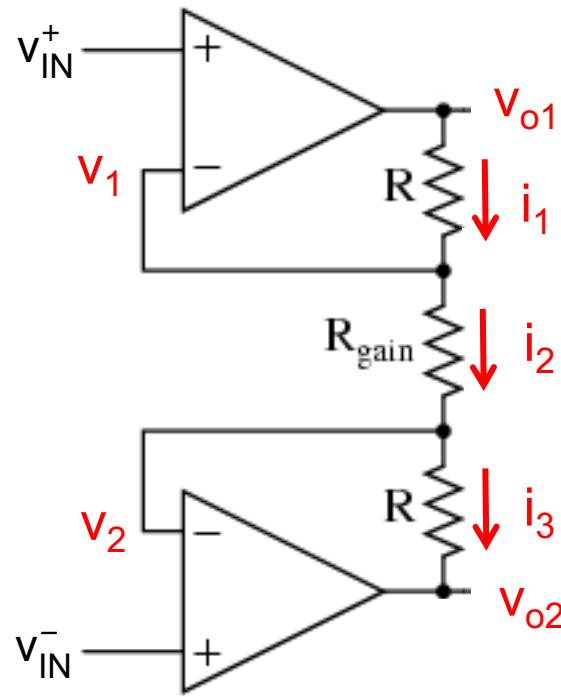
# Front End of Instrumentation Amplifier (Bonus)



- G.R. #1:  $v_{IN}^+ = v_1$  and  $v_{IN}^- = v_2$
- KCL:  $i_1 = i_2 = i_3$

$$\frac{v_{o1} - v_{IN}^+}{R} = \frac{v_{IN}^+ - v_{IN}^-}{R_{gain}} = \frac{v_{IN}^- - v_{o2}}{R}$$

$$\therefore \frac{v_{o1}}{R} = \frac{v_{IN}^+}{R} + \frac{v_{IN}^+}{R_{gain}} - \frac{v_{IN}^-}{R_{gain}}$$

$$\therefore v_{o1} = \frac{R}{R_{gain}} (v_{IN}^+ - v_{IN}^-) + v_{IN}^+$$

$$\text{Similarly, } v_{o2} = \frac{R}{R_{gain}} (v_{IN}^- - v_{IN}^+) + v_{IN}^-$$

## Back End of Instrumentation Amplifier (Bonus)

G.R. #2:  $i_4 = i_5$  and  $i_6 = i_7$

$$\frac{v_{o1} - v_3}{R} = \frac{v_3 - v_o}{R} \text{ so that } v_o = 2v_3 - v_{o1}$$


$$\frac{v_{o2} - v_4}{R} = \frac{v_4}{R} \text{ so that } v_4 = \frac{v_{o2}}{2} = v_3$$

Combining,  $v_o = v_{o2} - v_{o1}$

Using the results from the previous page,

$$v_o = v_{o2} - v_{o1} = \frac{R}{R_{\text{gain}}} (v_{IN}^- - v_{IN}^+) + v_{IN}^- - \frac{R}{R_{\text{gain}}} (v_{IN}^+ - v_{IN}^-) - v_{IN}^+$$
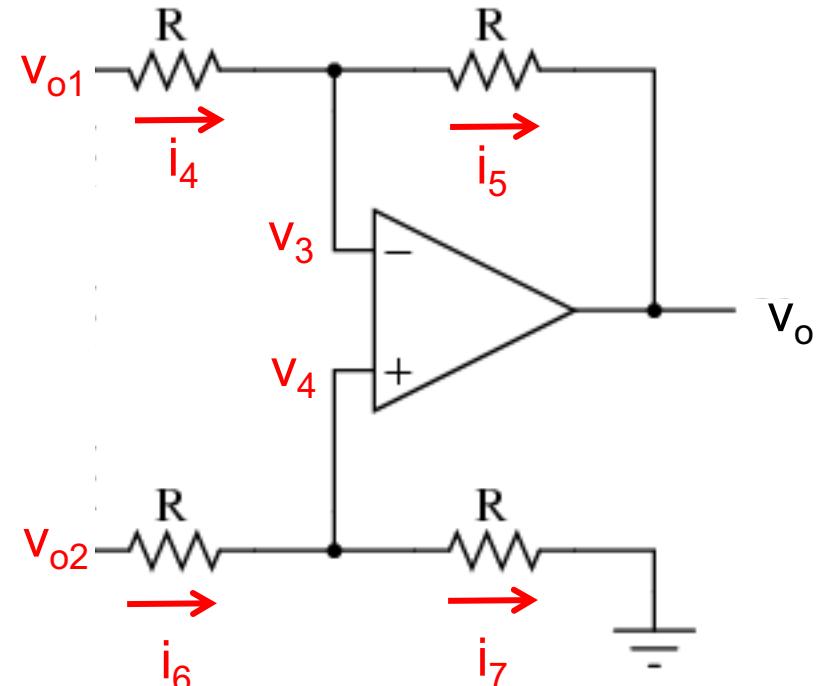
$$\therefore v_o = (v_{IN}^- - v_{IN}^+) \left( 2 \frac{R}{R_{\text{gain}}} + 1 \right)$$




---

# NOISE
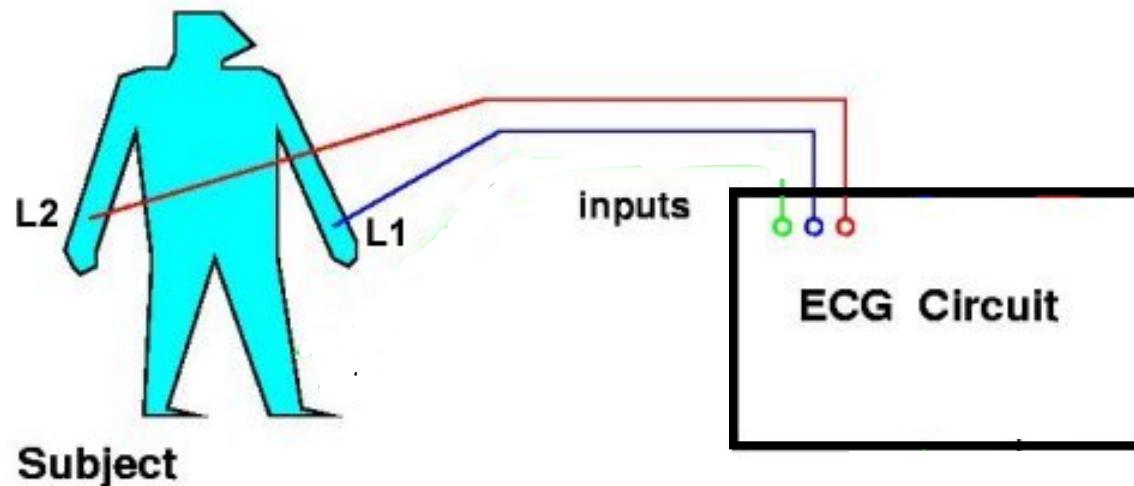
# ECG Measurement


---

- Need to measure the difference between L1 and L2
  - We think the circuit looks like



# The Circuit Really Looks Like This:

---

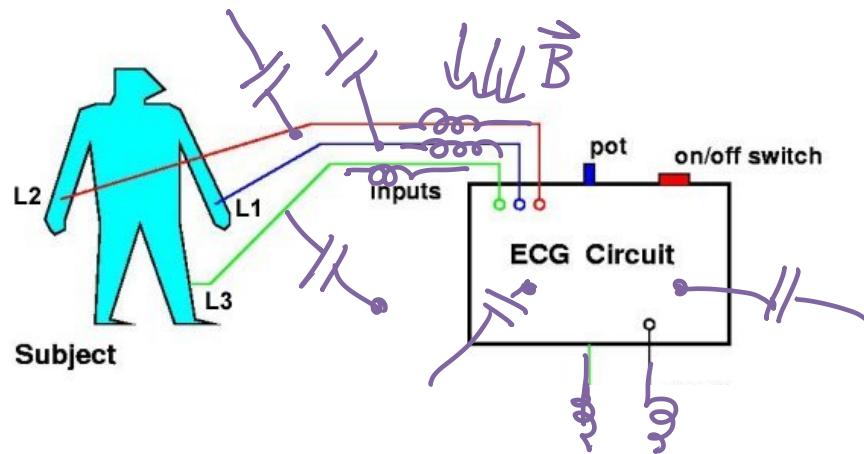

- There are many unwanted signals coupling into our circuit
  - Both capacitive (stray electric fields) and inductive (magnetic fields)
  - These signals can be larger than what we want to measure!
- How to prevent them from obscuring our signal?

# Noise Protection For Wires


---

- Shield the signal (literally cover it with metal)




[http://www.cablewholesale.com/support/technical\\_articles/coaxial\\_cables.php](http://www.cablewholesale.com/support/technical_articles/coaxial_cables.php)

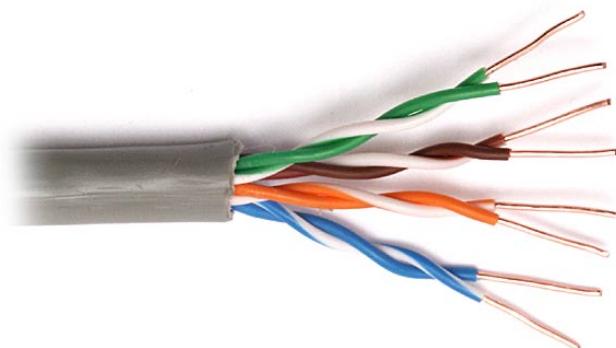- Try to make the noise common mode
  - Twist wires to each other



# Model of the Capacitive Noise (if it is common to both wires)


---

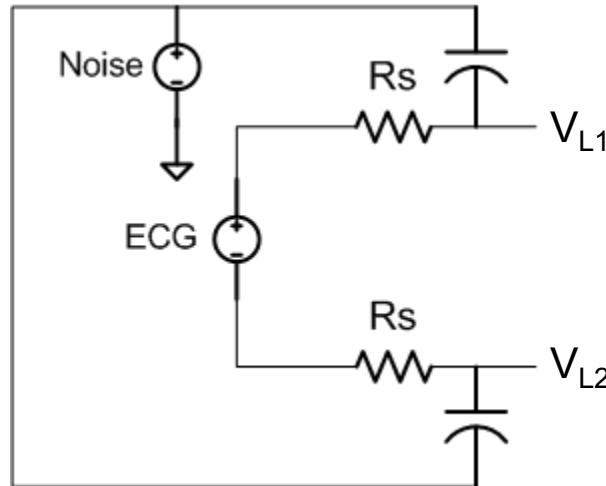

- The voltage at the two outputs will depend on ECG and Noise  
But if the capacitors and resistors are the same  
 $(V_{L1} - V_{L2})$  will not depend on noise
- This is only true if the capacitance on both wires is identical
  - Which means we need a balanced differential amplifier

# Balanced Amplifier


---

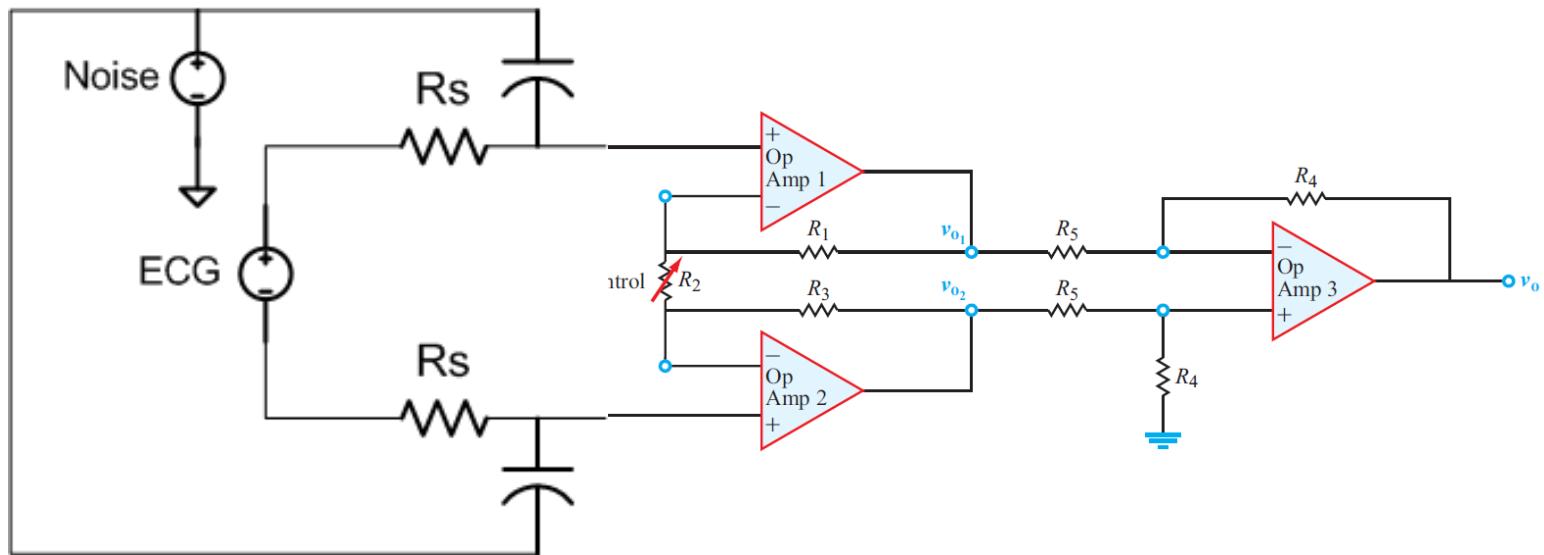

- This is a completely differential system
  - Good for reducing noise coupling

# New Problem in Our Balanced Amplifier

---

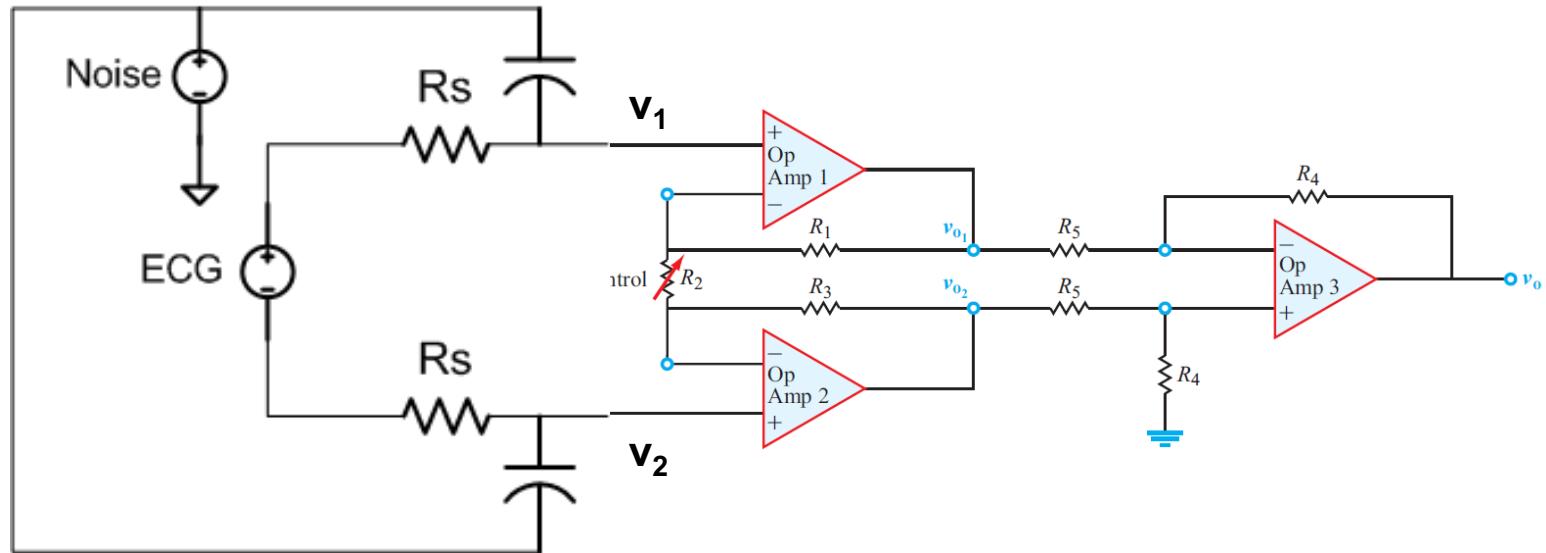


- What sets the voltage at  $v_1$ ,  $v_2$ ?
  - $V_{ECG}$  only sets  $v_1 - v_2$
  - They are not referenced to our chip's reference (Gnd)!
  - Chip won't work unless inputs are between +/- supply voltage.
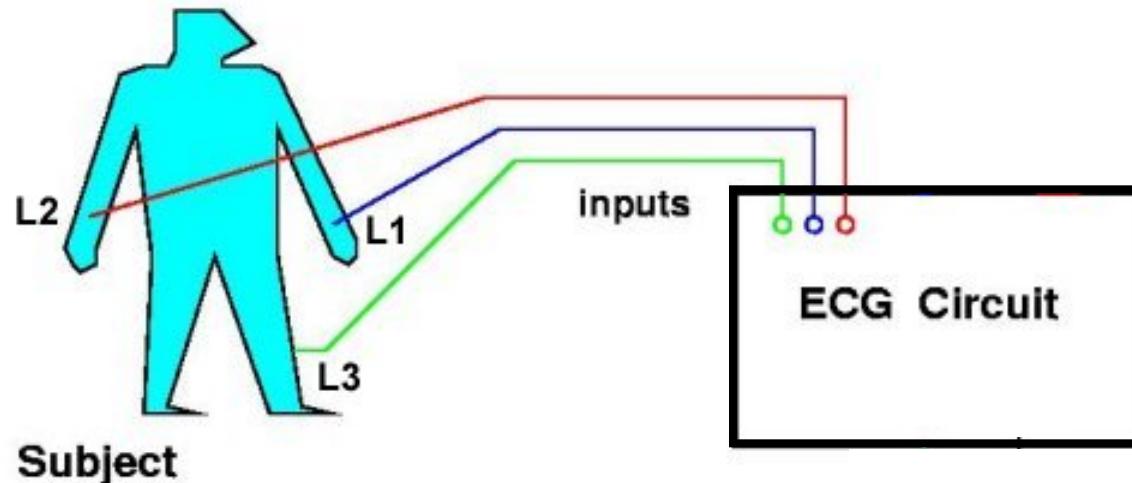
# The Reason for the Third Wire


---

- Need to measure the difference between L1 and L2
  - L3 is used to set the common-mode of the person



# Why Does the ECG Circuit Look Like This?


---

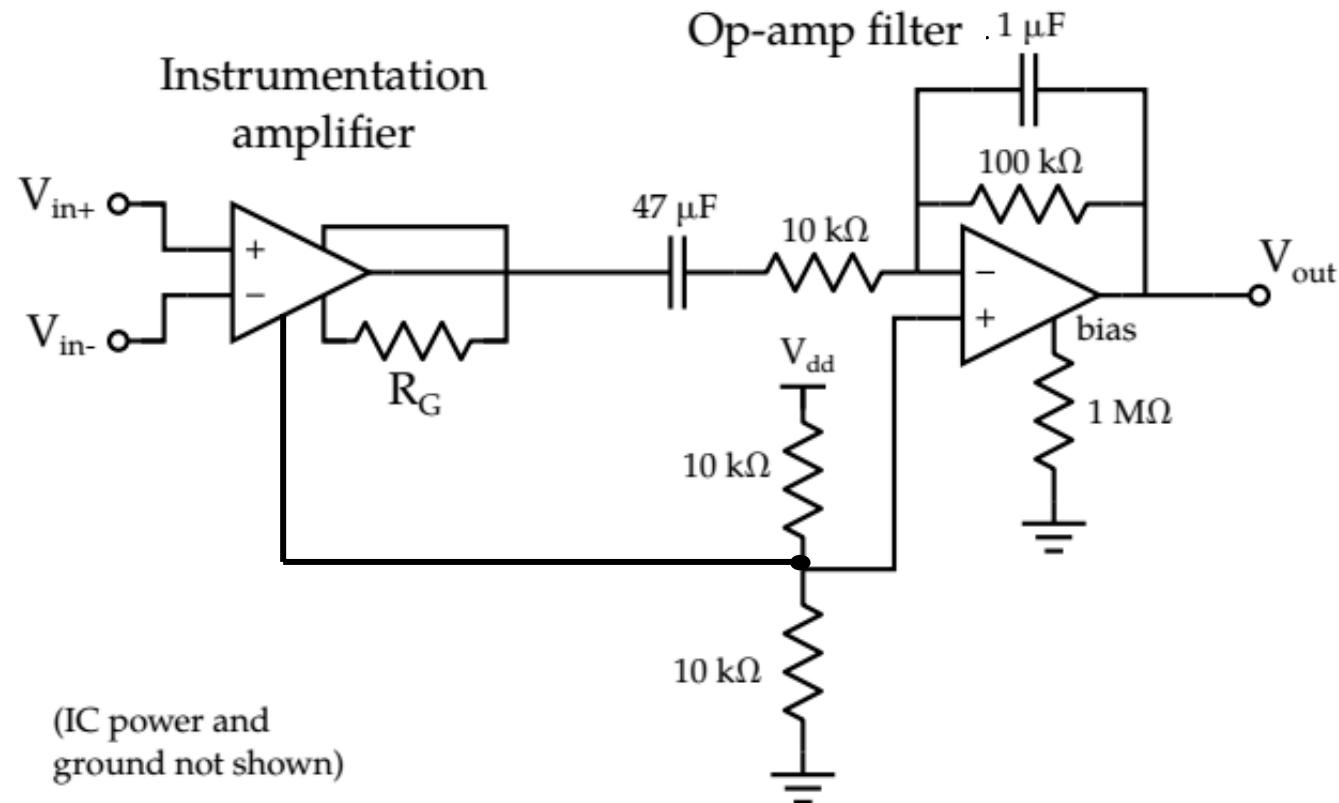
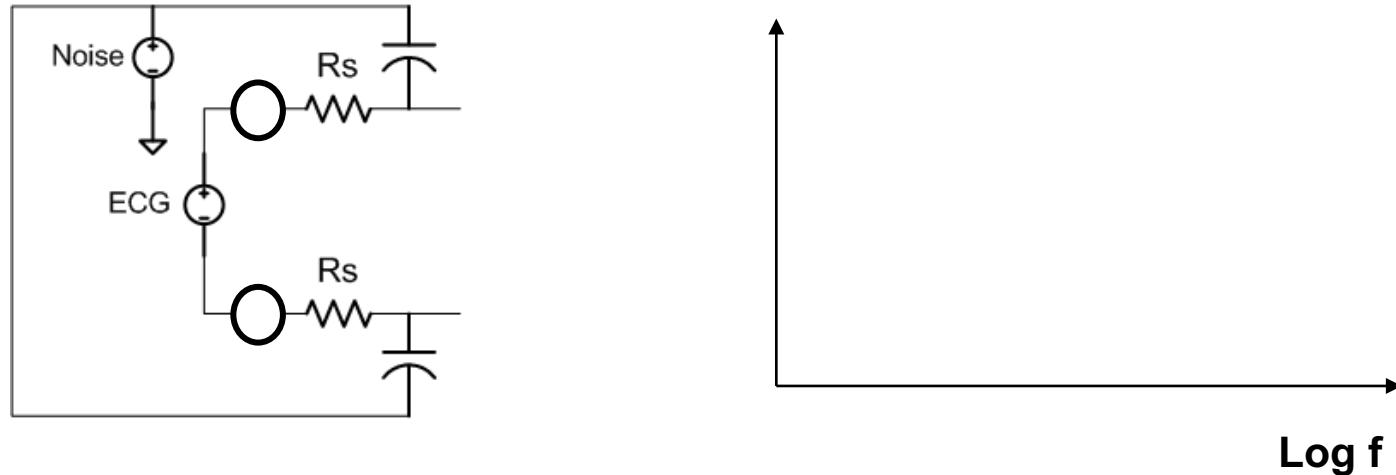
# Noise: Skin Voltage


---

- A voltage forms when metal contacts skin
  - The size of the voltage depends on the skin condition
- This means if the conditions at the two electrodes differ
  - You can generate a voltage
    - This voltage will change very slowly with time



# Why Does the ECG Circuit Look Like This?


---

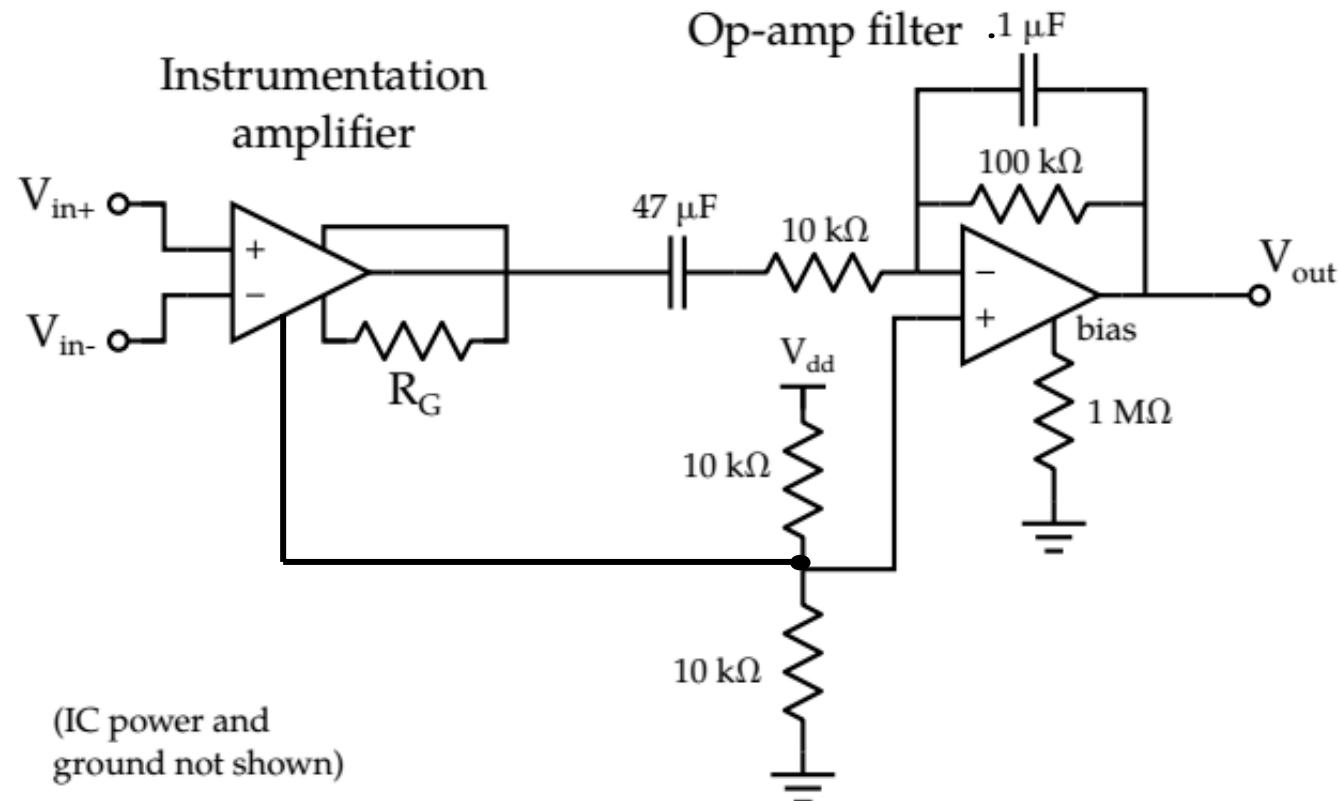
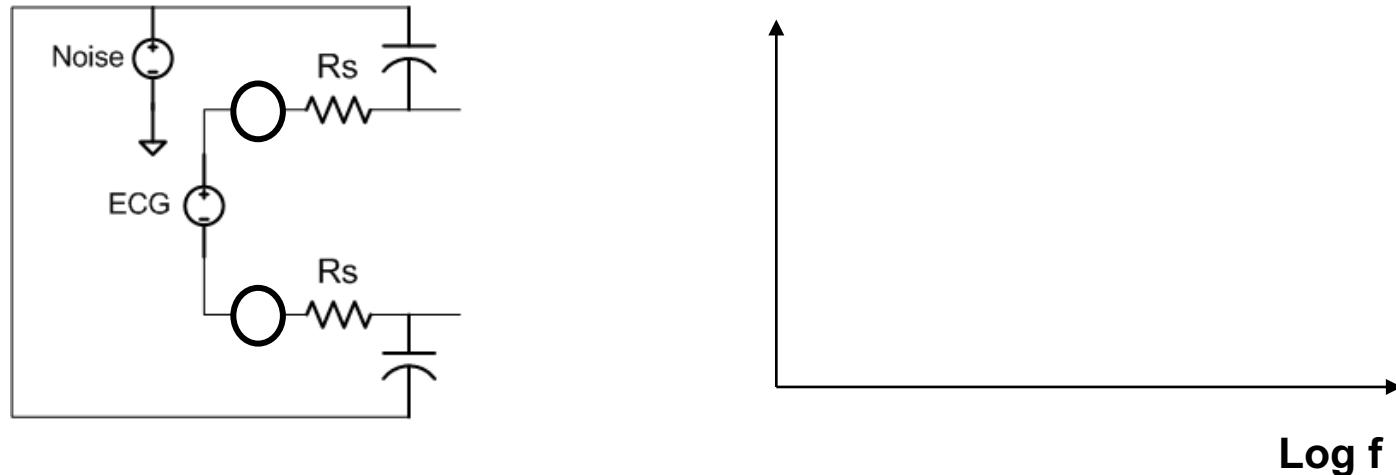
# Noise: 60Hz Wall Voltage


---

- The main capacitive noise comes from AC power
  - 120 to 240V, 60 Hz
  - This signal can be quite large (Volts!)
    - 1000x your signal
- Differential circuit cancels most of it out
  - But some will still get through due to imperfect symmetry



# Why Does the ECG Circuit Look Like This?

---

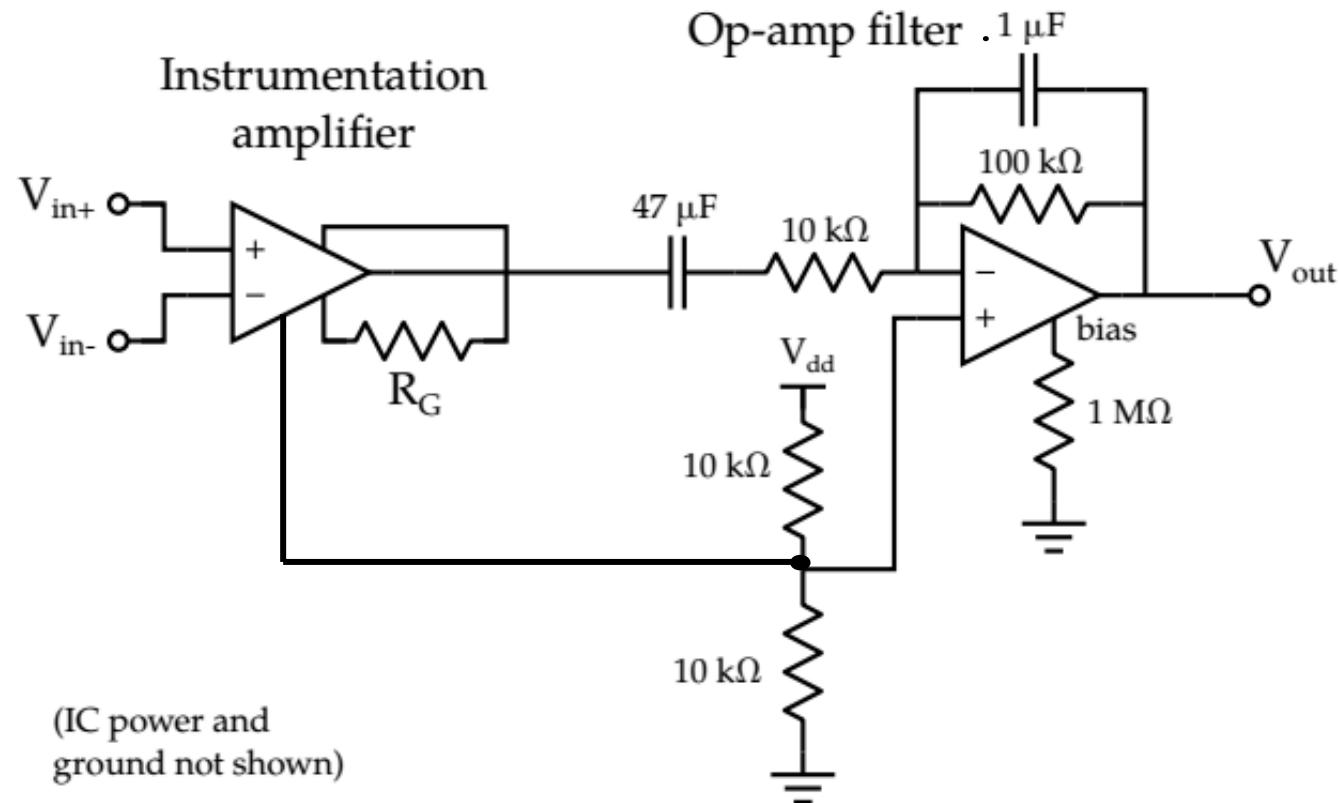

# Learning Objectives

---

- Understand how an instrumentation amplifier works
  - And how to set its gain through resistor selection
- Understand what noise is
  - Other electrical signals that you don't want on your wires
  - And how to minimize their effects on your circuit through differential amplifiers and filtering
- Understand the design philosophy behind our E40M ECG circuit