

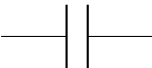

Capacitors and inductors

ENGR 40M lecture notes — July 21, 2017

Chuan-Zheng Lee, Stanford University

Unlike the components we’ve studied so far, in *capacitors* and *inductors*, the relationship between current and voltage doesn’t depend only on the present. Capacitors and inductors *store* electrical energy—capacitors in an electric field, inductors in a magnetic field. This enables a wealth of new applications, which we’ll see in coming weeks.

Quick reference

	Capacitor	Inductor
Symbol		
Stores energy in	electric field	magnetic field
Value of component (unit)	capacitance, C (farad, F)	inductance, L (henry, H)
I–V relationship	$i = C \frac{dv}{dt}$	$v = L \frac{di}{dt}$
At steady state, looks like	open circuit	short circuit

General behavior

In order to describe the voltage–current relationship in capacitors and inductors, we need to think of voltage and current as *functions of time*, which we might denote $v(t)$ and $i(t)$. It is common to omit (t) part, so v and i are implicitly understood to be functions of time.

The voltage v across and current i through a capacitor with capacitance C are related by the equation

$$i = C \frac{dv}{dt}, \quad \begin{array}{c} C \\ + \quad | \quad | \quad - \\ \quad \quad v \end{array} \quad \begin{array}{c} i \\ \rightarrow \end{array}$$

where $\frac{dv}{dt}$ is the rate of change of voltage with respect to time.¹ From this, we can see that an sudden change in the voltage across a capacitor—however minute—would require infinite current. This isn’t physically possible, so a capacitor’s voltage *can’t change instantaneously*. More generally, capacitors *oppose* changes in voltage—they tend to “want” their voltage to change “slowly”.

Similarly, in an inductor with inductance L ,

$$v = L \frac{di}{dt}, \quad \begin{array}{c} L \\ + \quad \text{---} \quad \text{---} \quad \text{---} \quad - \\ \quad \quad v \end{array} \quad \begin{array}{c} i \\ \rightarrow \end{array}$$

An inductor’s current can’t change instantaneously, and inductors oppose changes in current.

Note that we’re following the *passive sign convention*, just like for resistors.


¹That is, the derivative of voltage with respect to time. If you haven’t studied calculus, think of this as the slope of the curve at a given time t , if you draw a graph of voltage against time.

Combinations in series and parallel

Inductors combine similarly to resistors:




$$L_s = L_1 + L_2$$

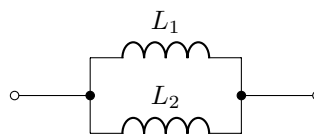


$$L_p = \left(\frac{1}{L_1} + \frac{1}{L_2} \right)^{-1} = \frac{L_1 L_2}{L_1 + L_2}$$

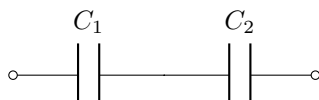Capacitors, however, are the other way round:


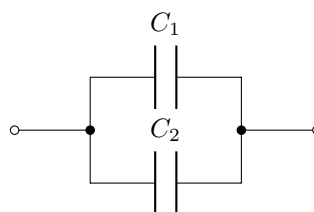
$$C_s = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1} = \frac{C_1 C_2}{C_1 + C_2}$$




$$C_p = C_1 + C_2$$

Steady state analysis

Steady state refers to the condition where voltage and current are no longer changing. Most circuits, left undisturbed for sufficiently long, eventually settle into a steady state. In a circuit that is in steady state, $\frac{dv}{dt} = 0$ and $\frac{di}{dt} = 0$ for all voltages and currents in the circuit—including those of capacitors and inductors.

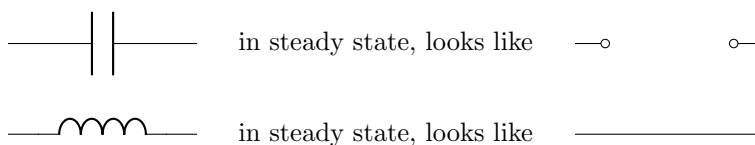Thus, at steady state, in a capacitor, $i = C \frac{dv}{dt} = 0$, and in an inductor, $v = L \frac{di}{dt} = 0$. That is, in steady state, *capacitors look like open circuits*, and *inductors look like short circuits*, regardless of their capacitance or inductance.




(This might seem trivial now, but we'll use this fact repeatedly in more complex situations later.)

Practical matters


Manufacturers typically specify a *voltage rating* for capacitors, which is the maximum voltage that is safe to put across the capacitor. Exceeding this can break down the dielectric in the capacitor.

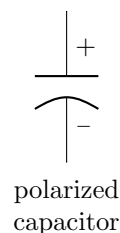Capacitors are not, by nature, *polarized*: it doesn't normally matter which way round you connect them. However, some capacitors *are* polarized—in particular, electrolytic capacitors, where the insulator is a very thin oxide layer that would be depleted if a negative voltage is applied. In schematics, if a capacitor is polarized, we use a special symbol for it, as shown right.




Examples

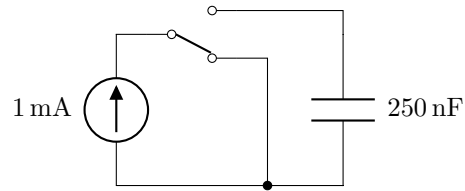
Example 1. In the (contrived) circuit below, at $t = 0$, the voltage across the capacitor is 0 V . The switch begins on the lower throw, moves to the upper throw at $t = 0\text{ ms}$, then moves back to the lower throw at $t = 1\text{ ms}$. Draw a graph of the voltage across the capacitor as a function of time.




Example 2. In the (contrived) circuit below, at $t = 0\text{ ms}$, $v_a = 10\text{ V}$. The switch begins on the lower throw, and moves to the upper throw at $t = 0\text{ ms}$. When does the capacitor's voltage reach 0 V ?

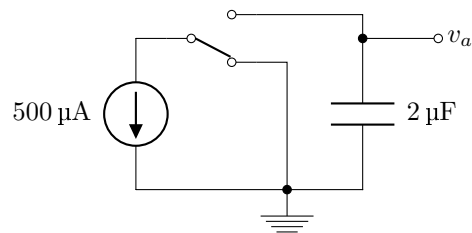

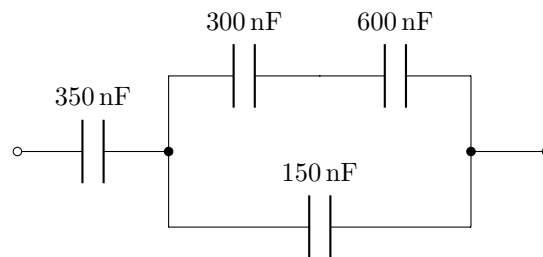
Example 3. You wish to replace the following network of capacitors with a single capacitor. What should its value be?




Example 4. In the (contrived) circuit below, at $t = 0$, the current through the inductor is 100 mA *upwards*. The switch begins on the lower throw, moves to the upper throw at $t = 0\text{ ms}$, then moves back to the lower throw at $t = 1\text{ ms}$. Draw a graph of the current through the inductor i_L , *with reference direction going downwards*, as a function of time.

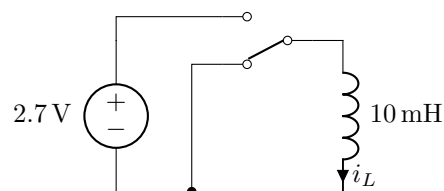

Example 5. Find the total inductance of this inductor network.

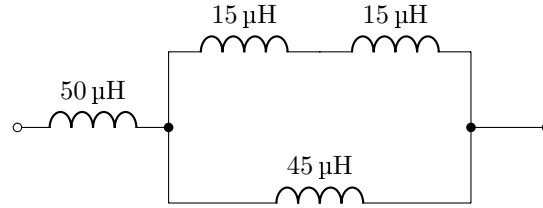


Example 6. The circuit below has reached steady state. What is the voltage v_x ?

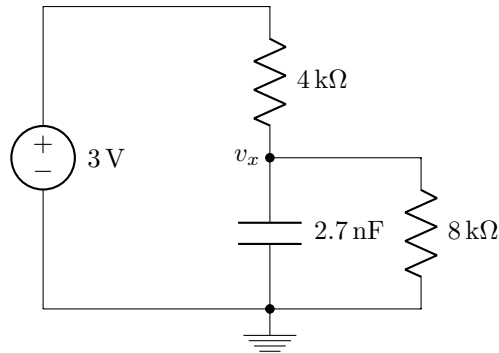

Example 7. The circuit below has reached steady state.

- What is the voltage v_x ?
- What is the voltage across the capacitor? (Be sure to specify the direction.)

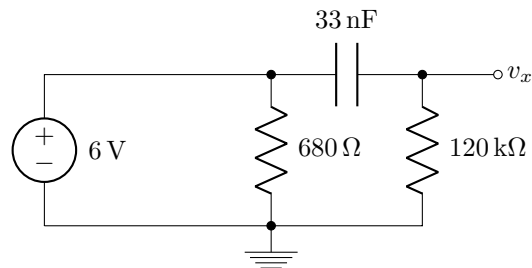

Example 8. The circuit below has reached steady state. What is the voltage v_x ?

