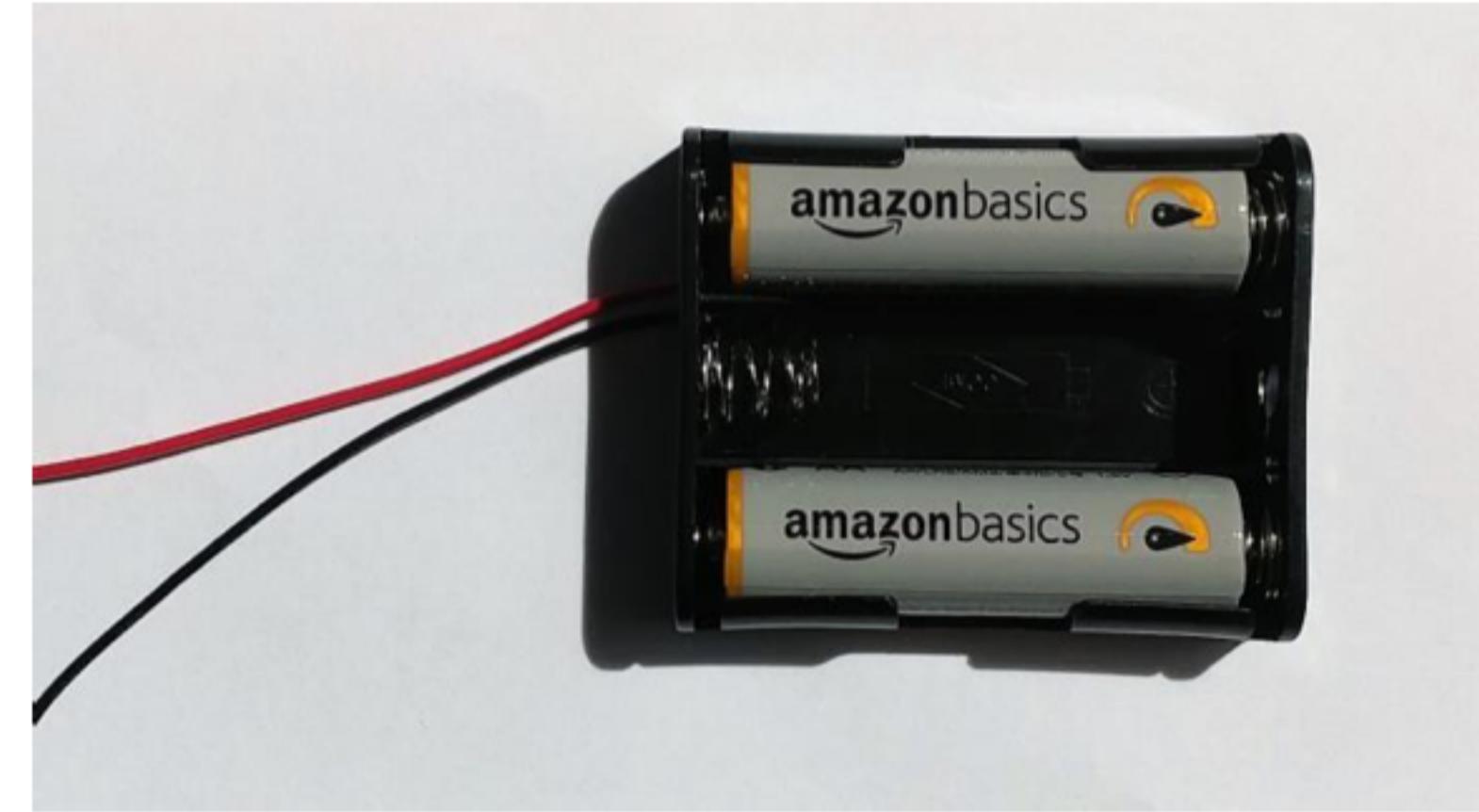


Happy Friday!


Do this now:

Take all three AA batteries out of your kit, and put (only!) **two** of them in the holder.

(Keep the third one handy.)



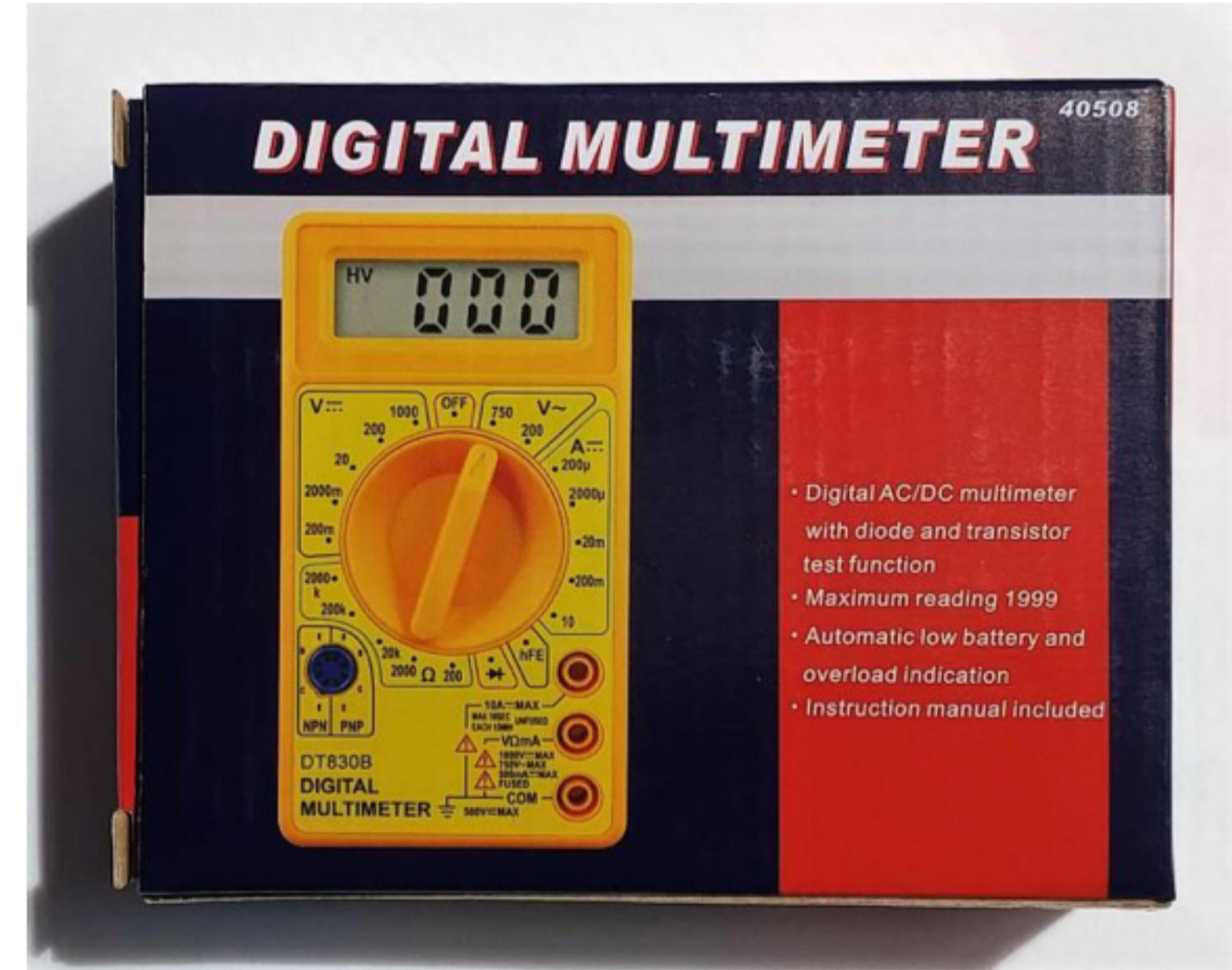Take your digital multimeter out of its packaging, as well as the probes in the box



Announcements

- **Homework 1** is due now
- **Prelab 1** (which we'll do today) is due 24 hours before your lab next week
- **Lab 0** reflections due before your lab next week
- **Homework 2** is due next Friday 3pm

All submissions are on Gradescope, the class code is on the website (it's 973RZ9)

Lab 1


Solar-powered USB charger

Using your multimeter

ENGR 40M
Chuan-Zheng Lee
Stanford University
14 April 2017


Open circuit and short circuit

Open circuit

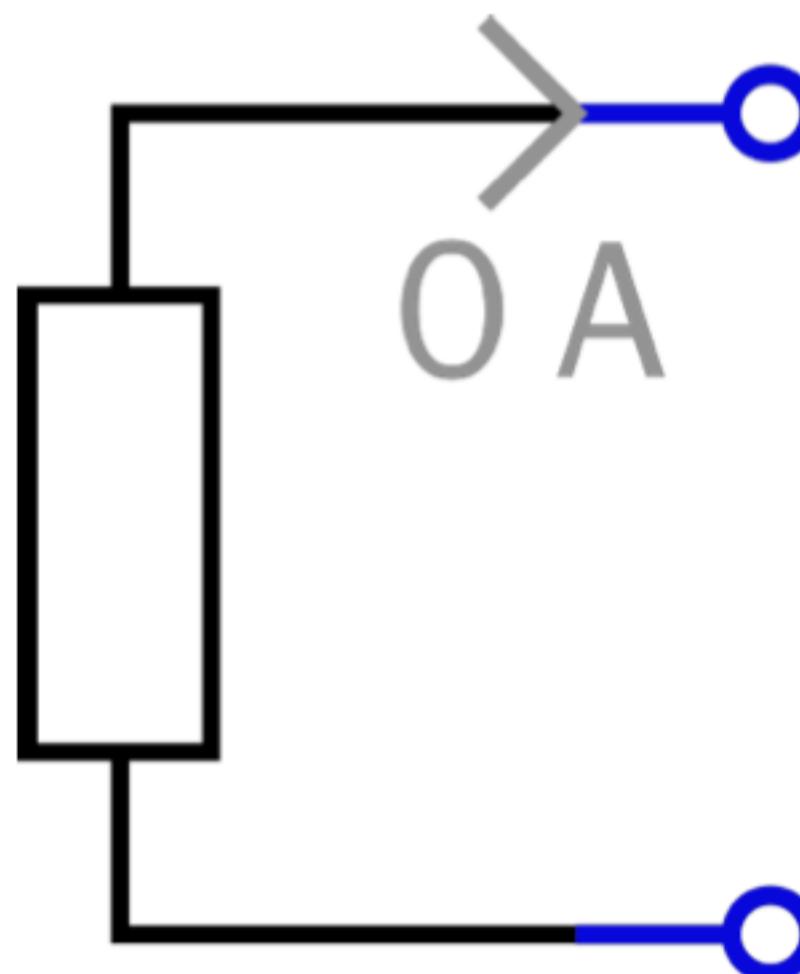

open
circuit

Short circuit

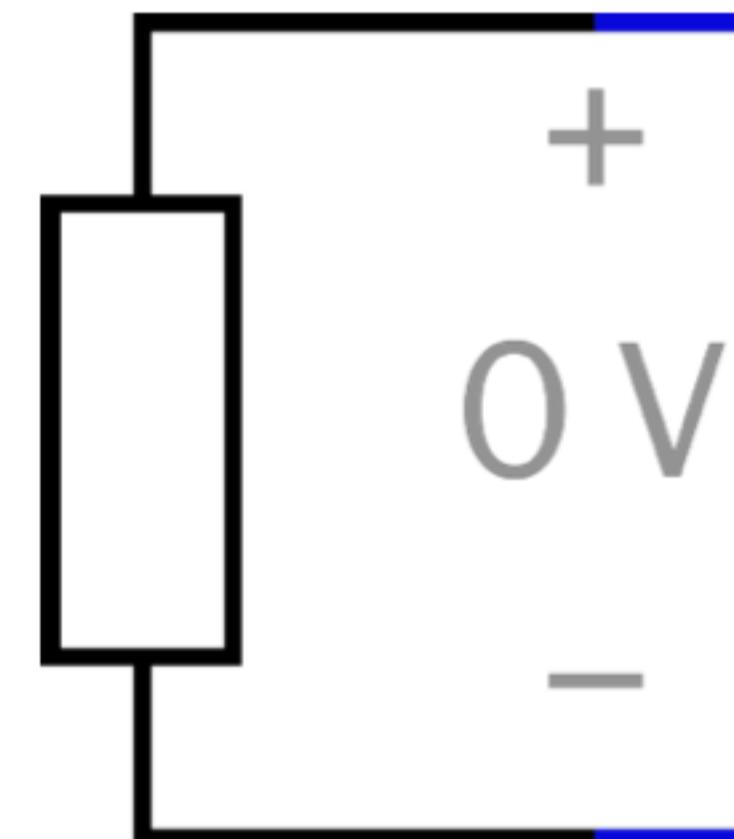


short
circuit

- No connection
- Infinite resistance
- Current can't flow ($i = 0$)


- Direct connection
- Zero resistance
- No potential difference ($v = 0$)

Modes of your digital multimeter (DMM)

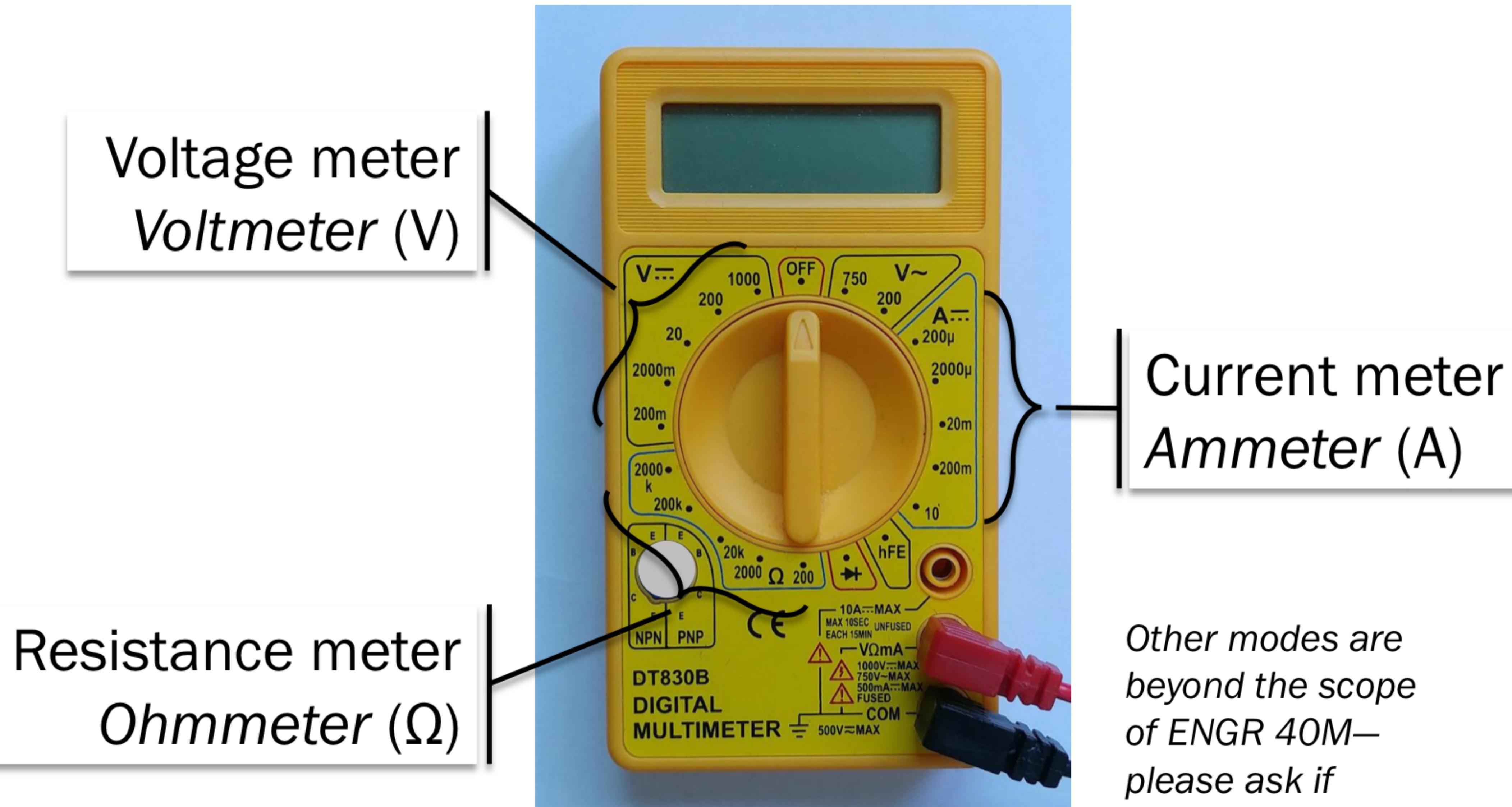

Connecting your multimeter's probes

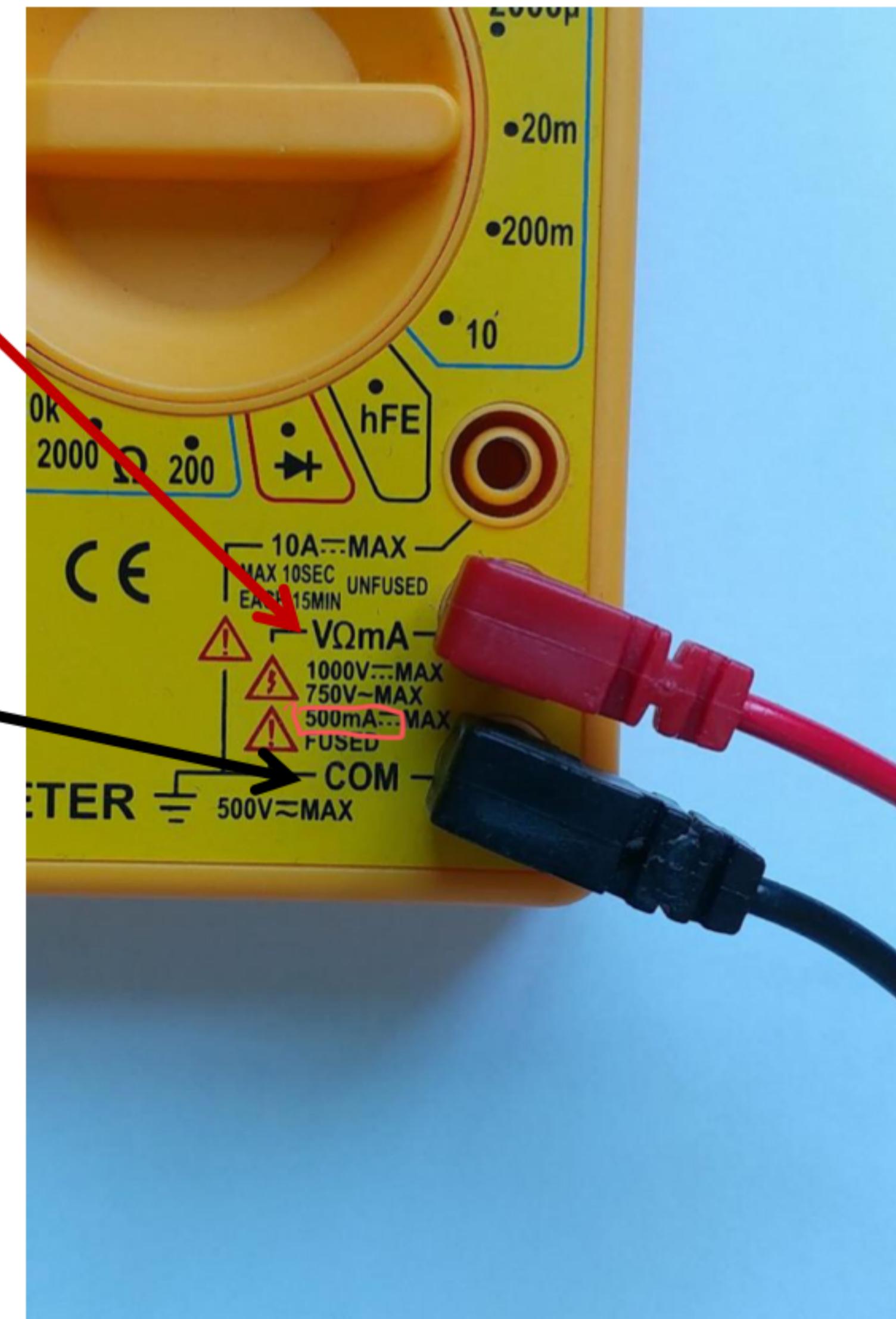
- Red probe → $V\Omega mA$, normally
 - “Volts, ohms and milliamps”
- Black probe → COM
 - “Common”
- 10A(DC) is used for higher current



Using your voltmeter (1)

Do now:

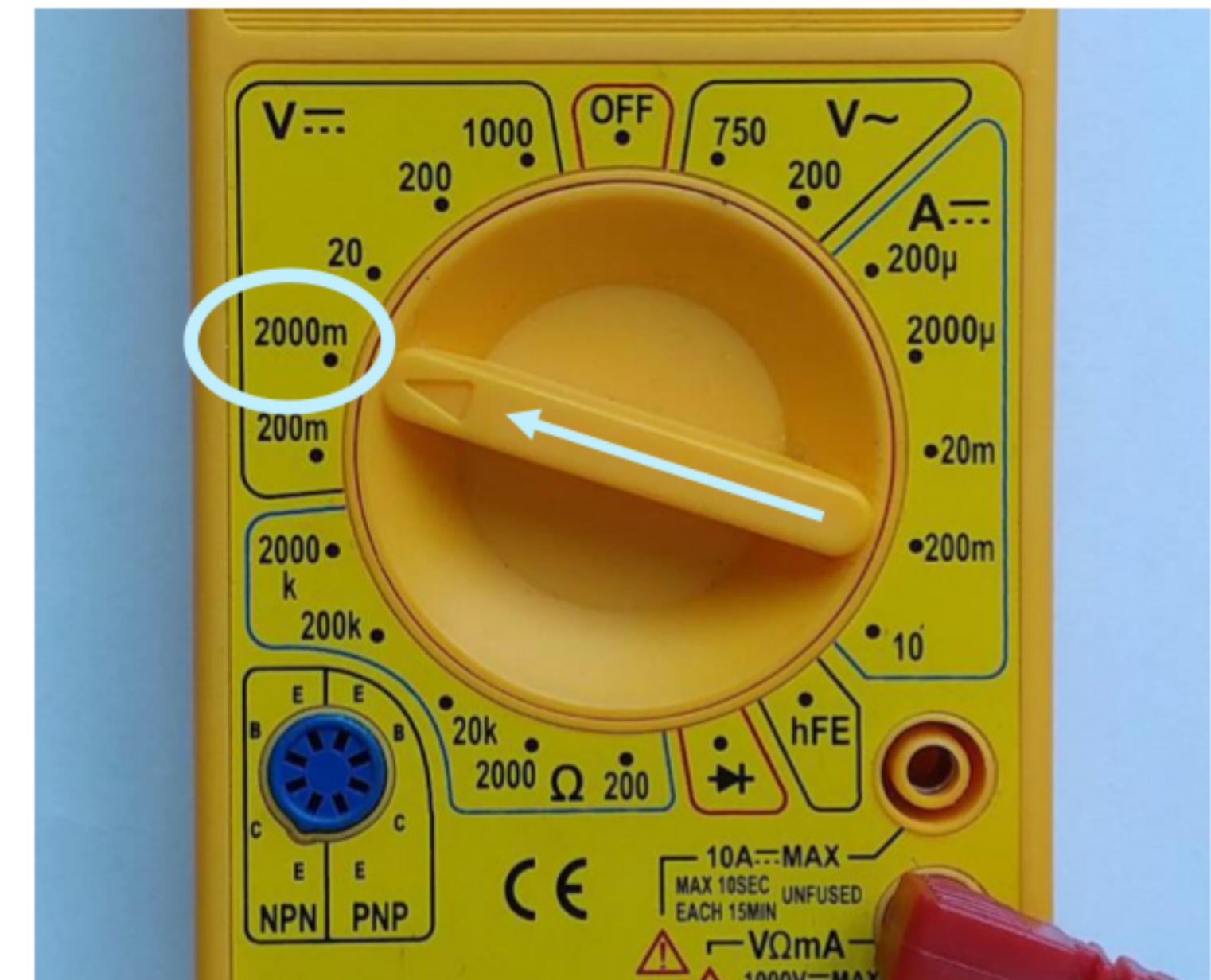- Use the 2000mV scale
- Grab an AA battery
- Put one probe on each end of the battery
- Make firm contact!




- What happens if you get the probes the “wrong way round”?



Reference directions (voltage)

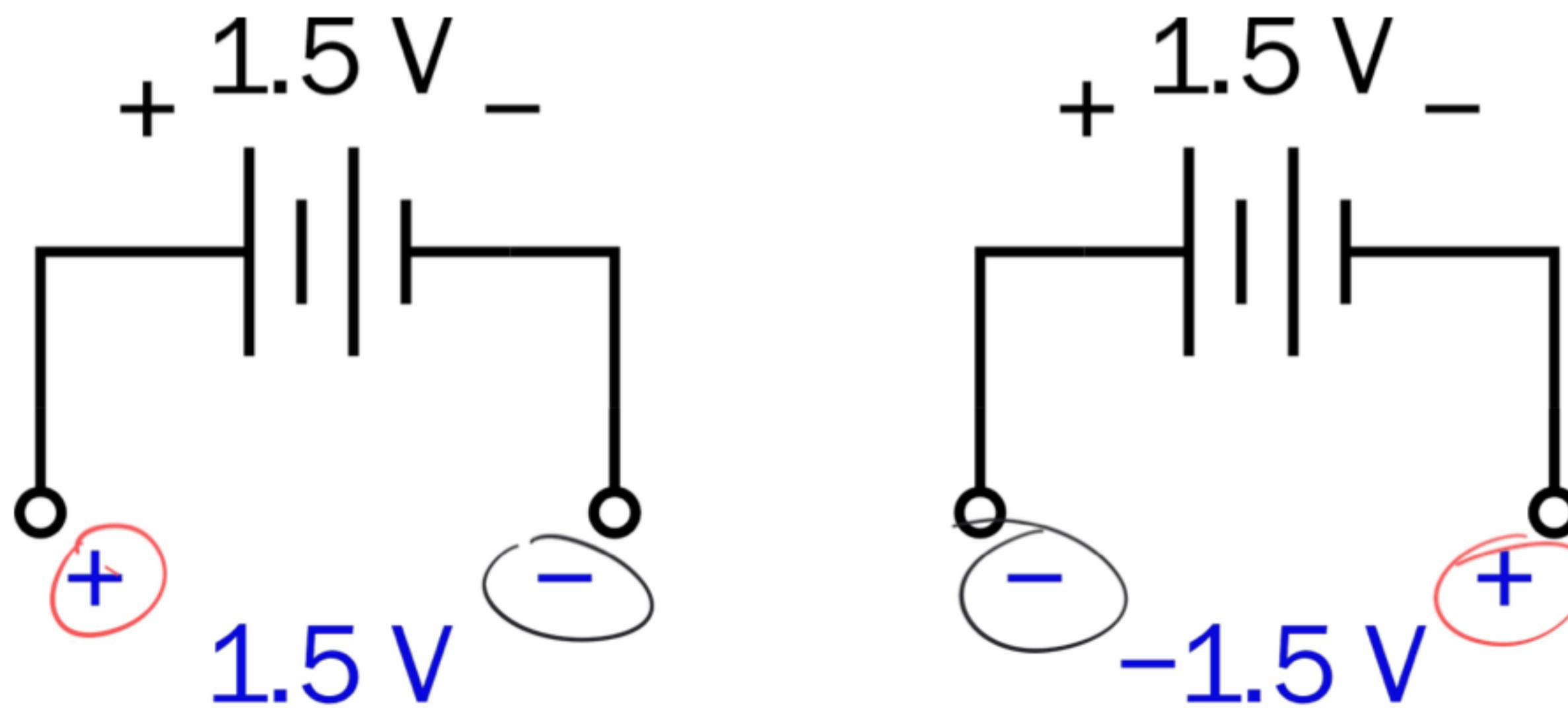- When measuring voltage, the **direction** matters
- To avoid ambiguity, we label one side of a device “**+**”, and the other side “**-**”.
- The voltage we measure is **with respect to** this reference direction. So these are equivalent:




Using your voltmeter (2)


Do now:

- Change to the 200mV scale. Measure the same battery. What does it say?
- How about on the 20V scale?

- How should you choose the scale?

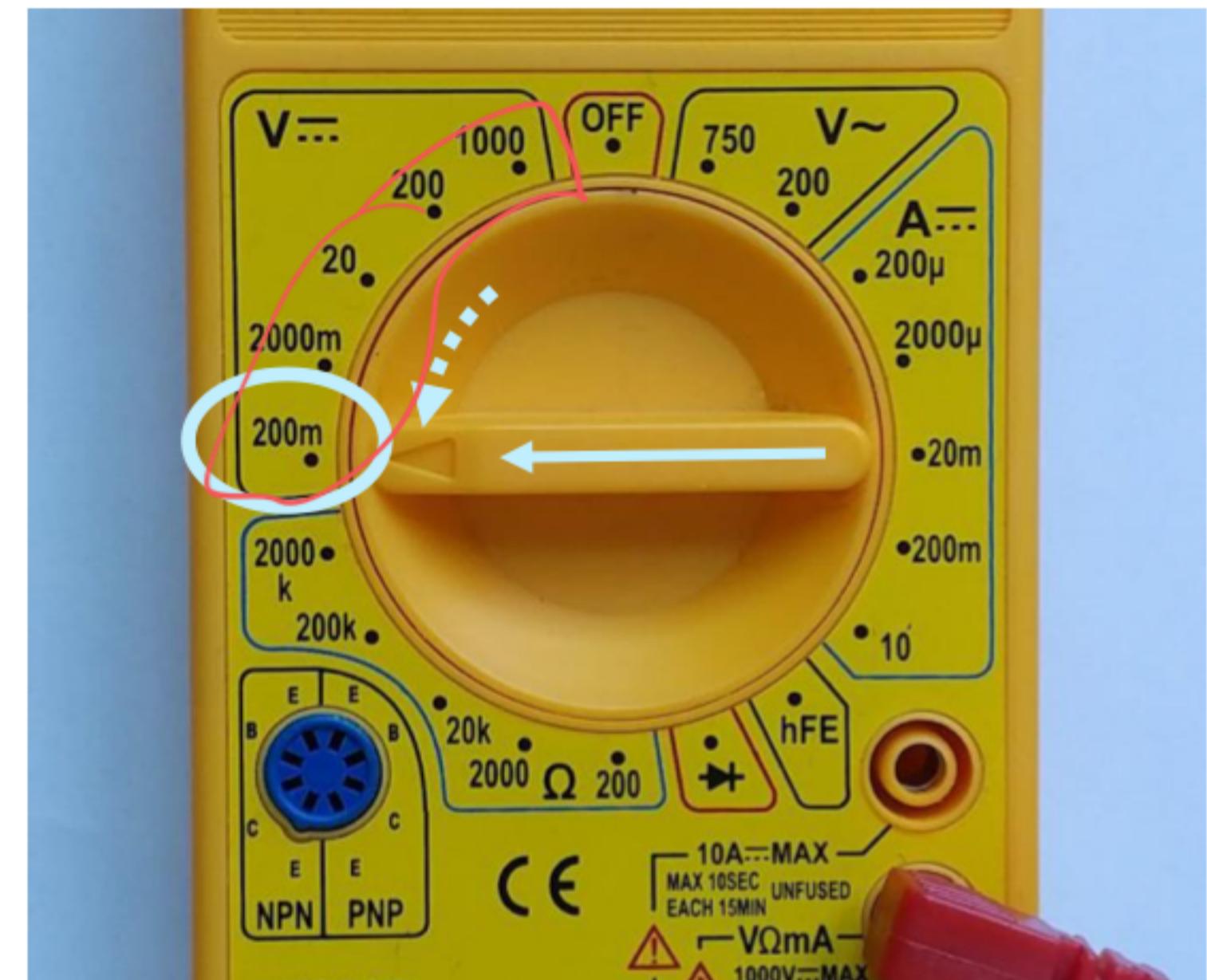

Using your multimeter: scales

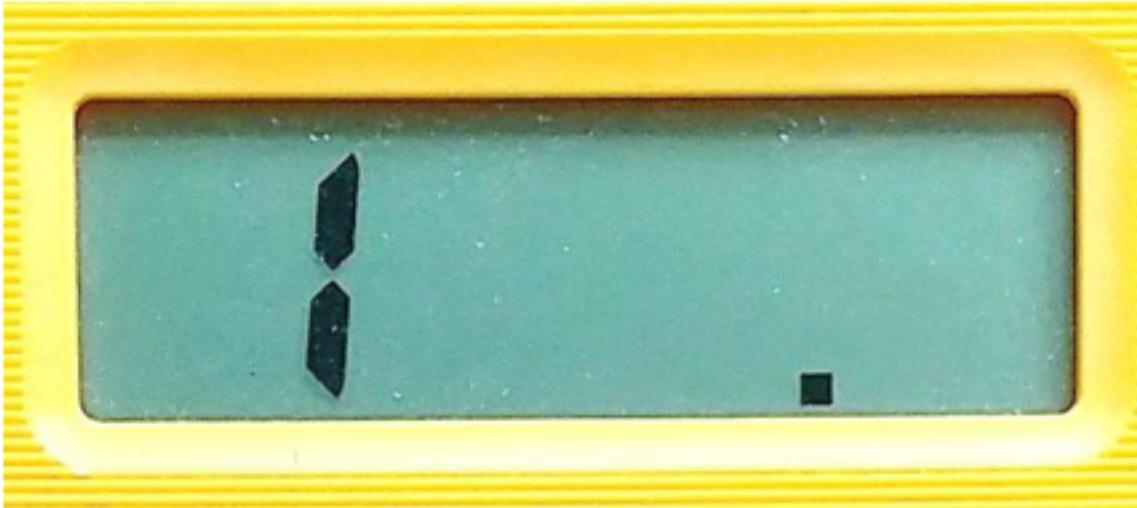
- Your multimeter has **3½ digits**: The 4th digit can only show a “1”.
- Numbers indicate the **maximum** that a scale can measure.
- If you measure something exceeding the scale, the meter shows this: 
- To maximize precision, choose the smallest scale greater than what you’re measuring.

Using your voltmeter (3)

Do now:


- Place all three AA batteries in the holder
- Don't let the holder wires touch each other
- Measure the voltage across the holder

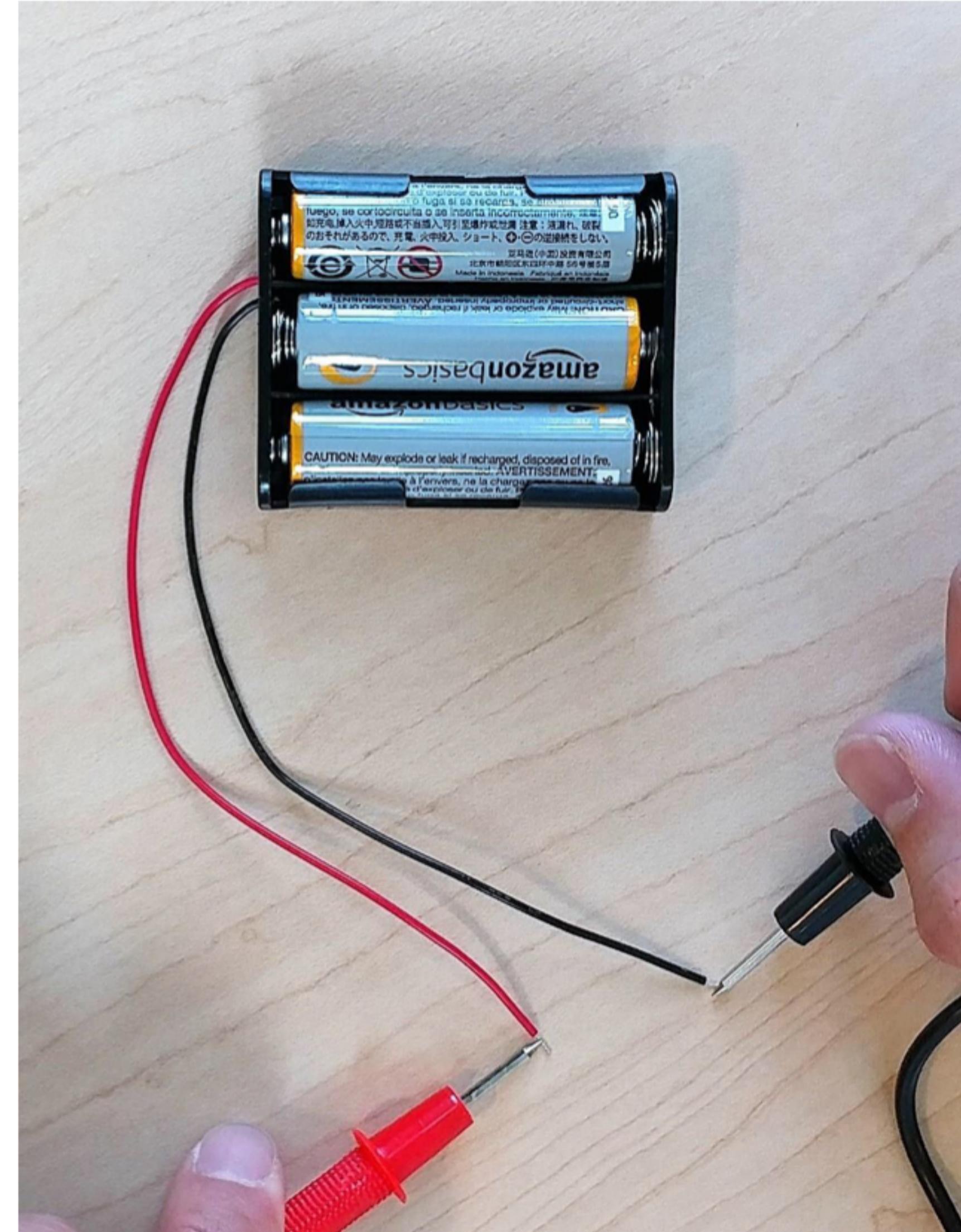- You'll need to choose the appropriate scale.
- Are the batteries in series or in parallel?



A very simple circuit

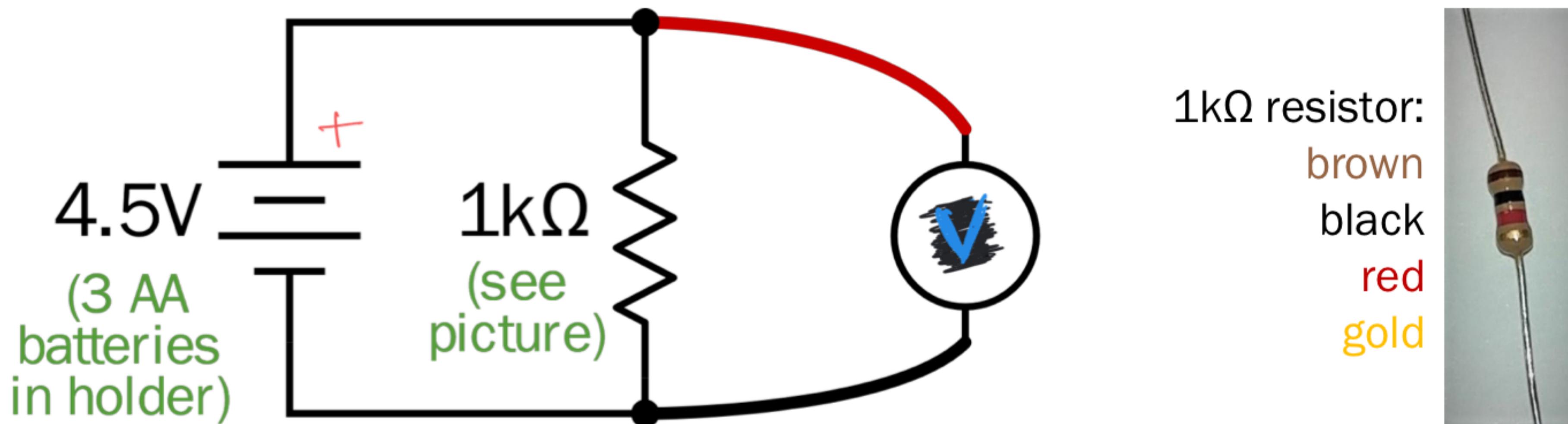
- Make this circuit using crocodile clips
- Measure the voltage across the resistor



- The voltmeter is **in parallel** with the resistor.
- How does this voltage compare to the battery's?

Voltmeters connect in parallel

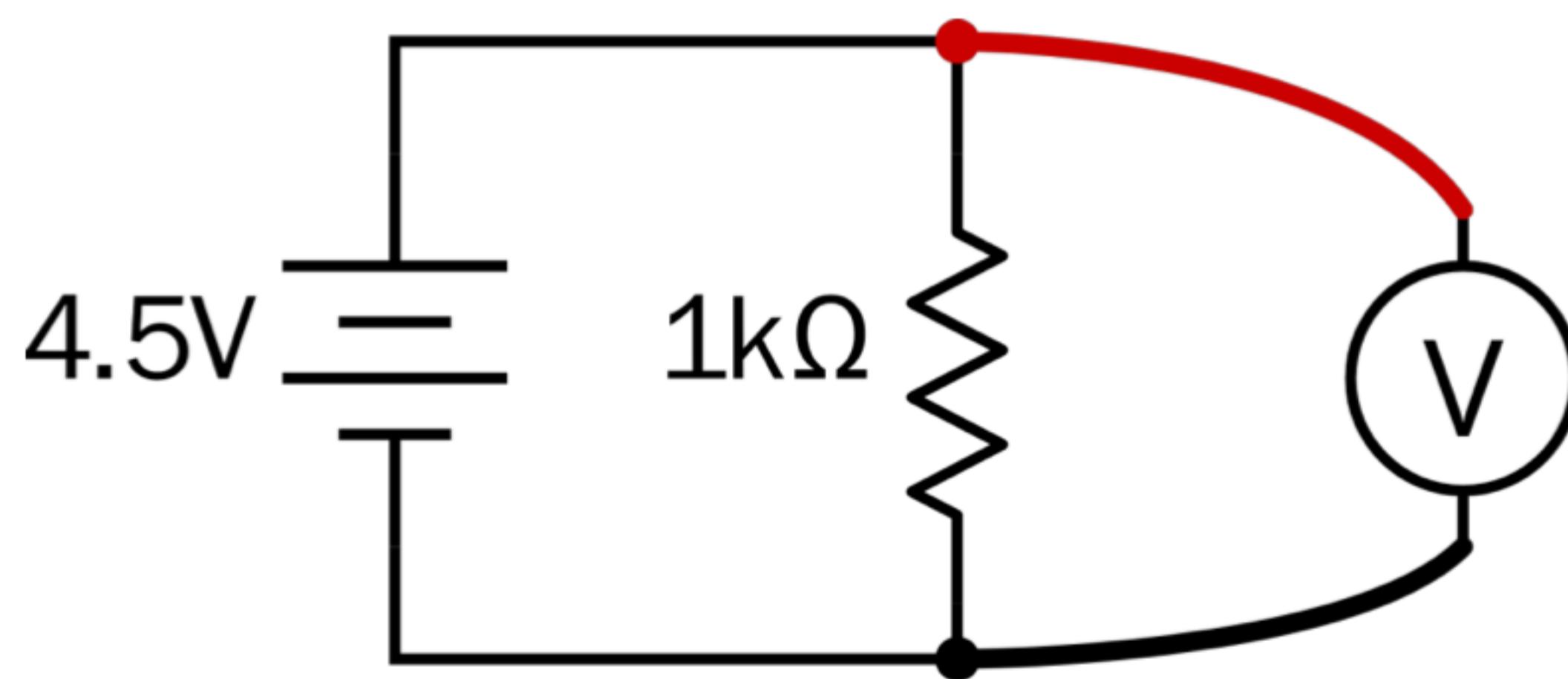
- To measure a voltage across a device, you must probe on *either side* of it.
- Therefore, voltmeters **connect in parallel**.
- In order to avoid affecting the circuit, the voltmeter takes close to zero *current*.
- We say that **the ideal voltmeter looks like an open circuit**.



Using your ammeter

Do now:

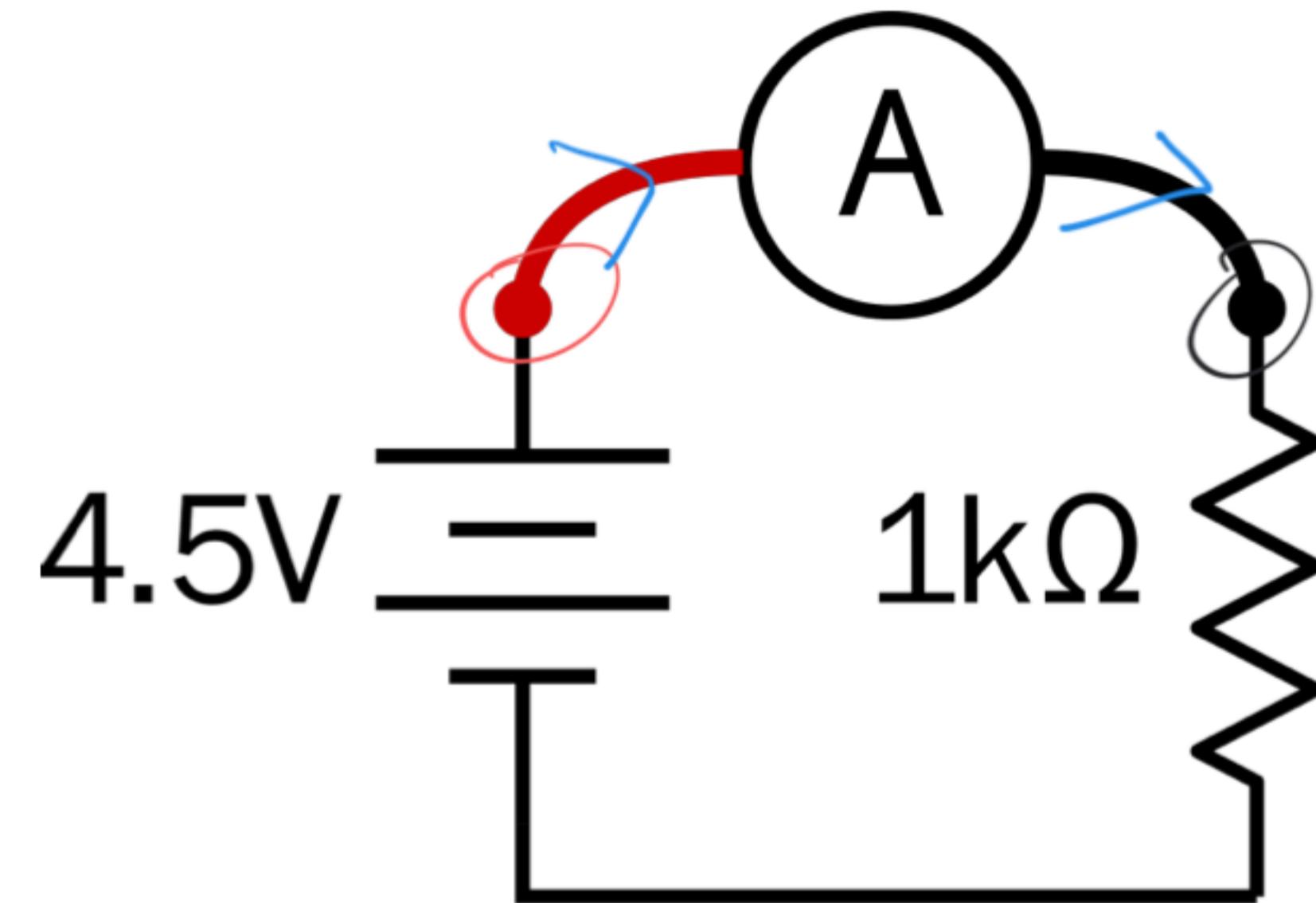- Measure the current through the resistor
- Important: The ammeter is **in series** with the resistor





- What happens if you reverse the probes?
- What is the current through the battery?



Current modes


Reference directions (current)

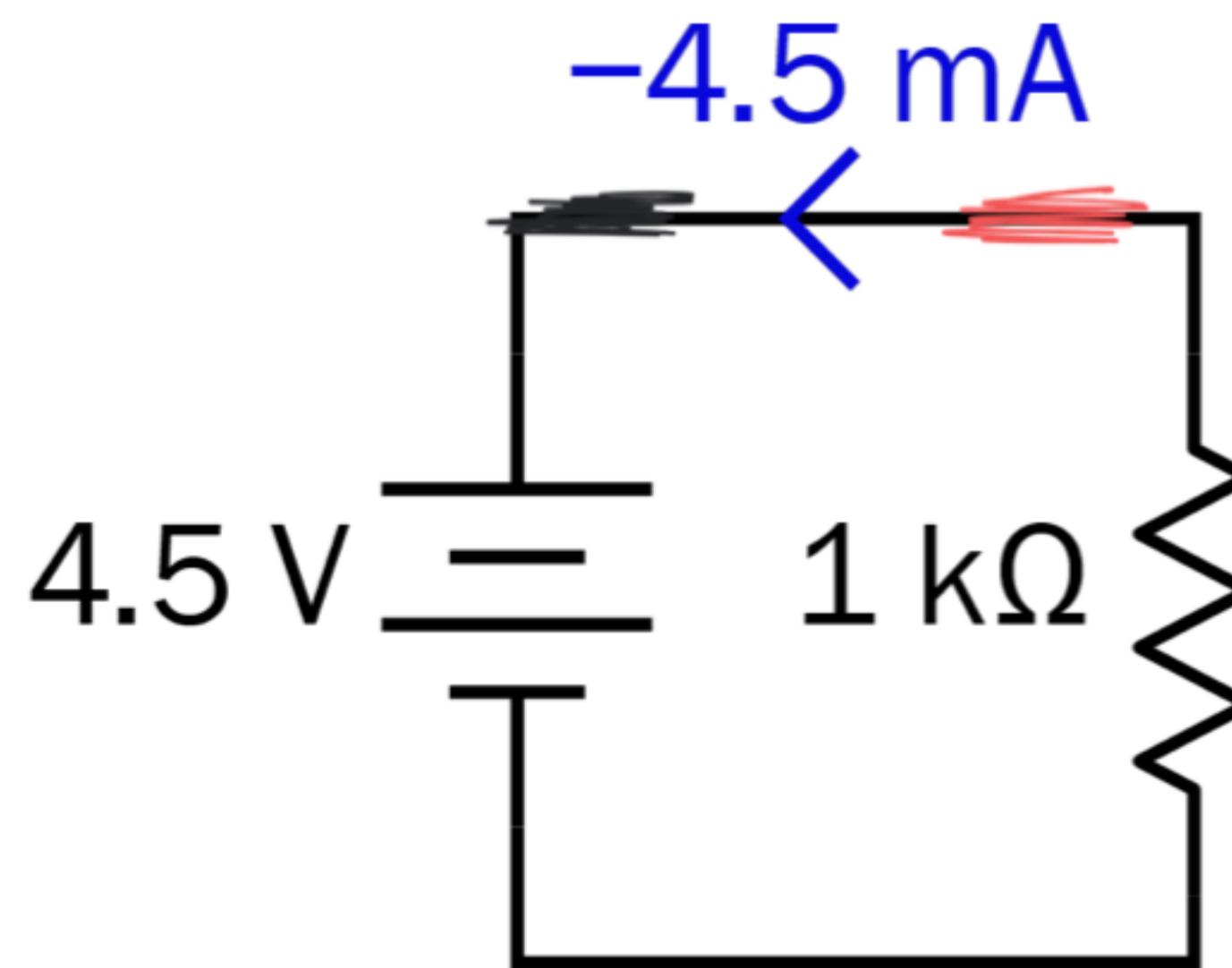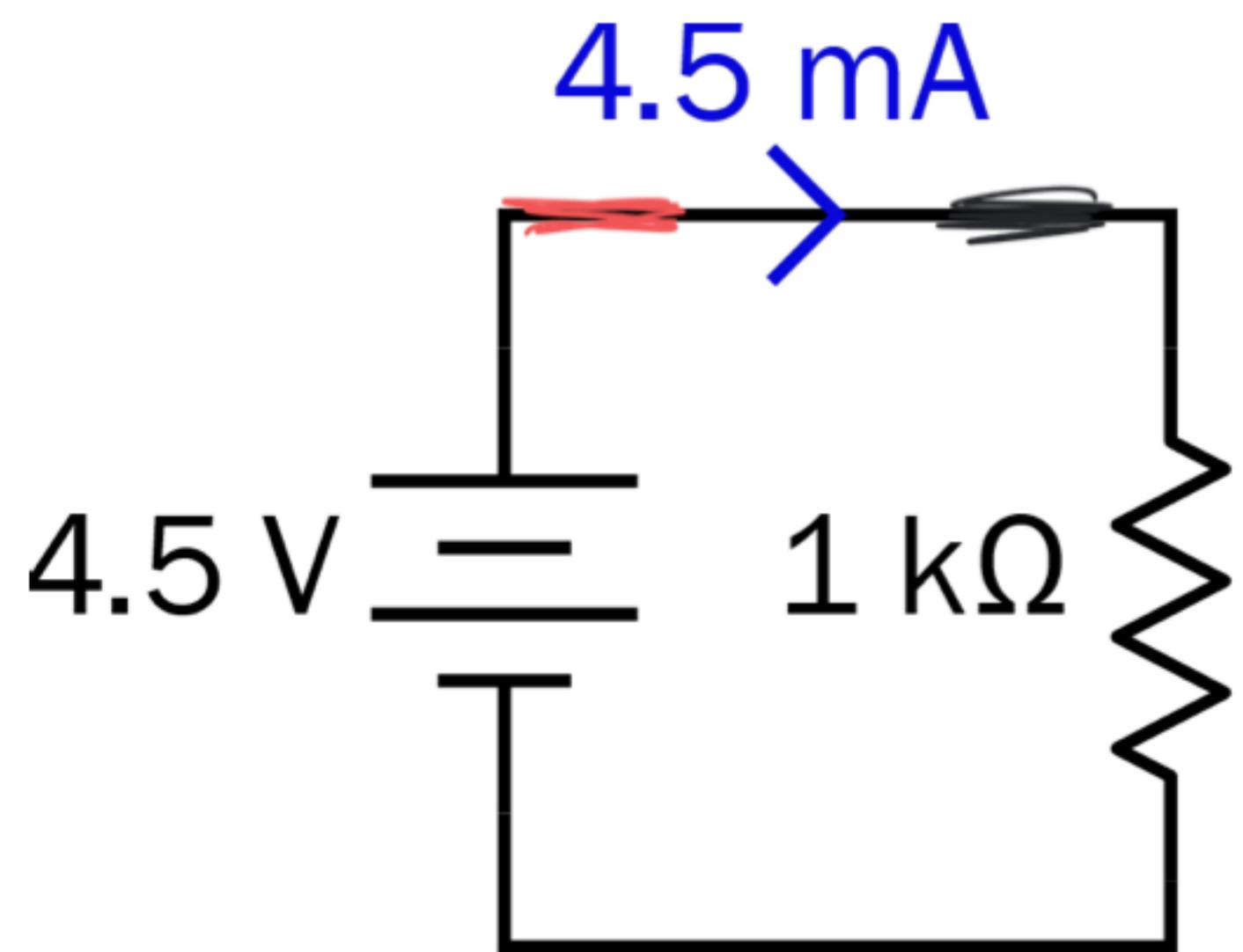- When measuring current, the **direction** matters
- To avoid ambiguity, we draw an arrow to indicate the direction we're assuming
- The current we measure is **with respect to** this reference direction. So these are the same thing:




Ammeters connect in series

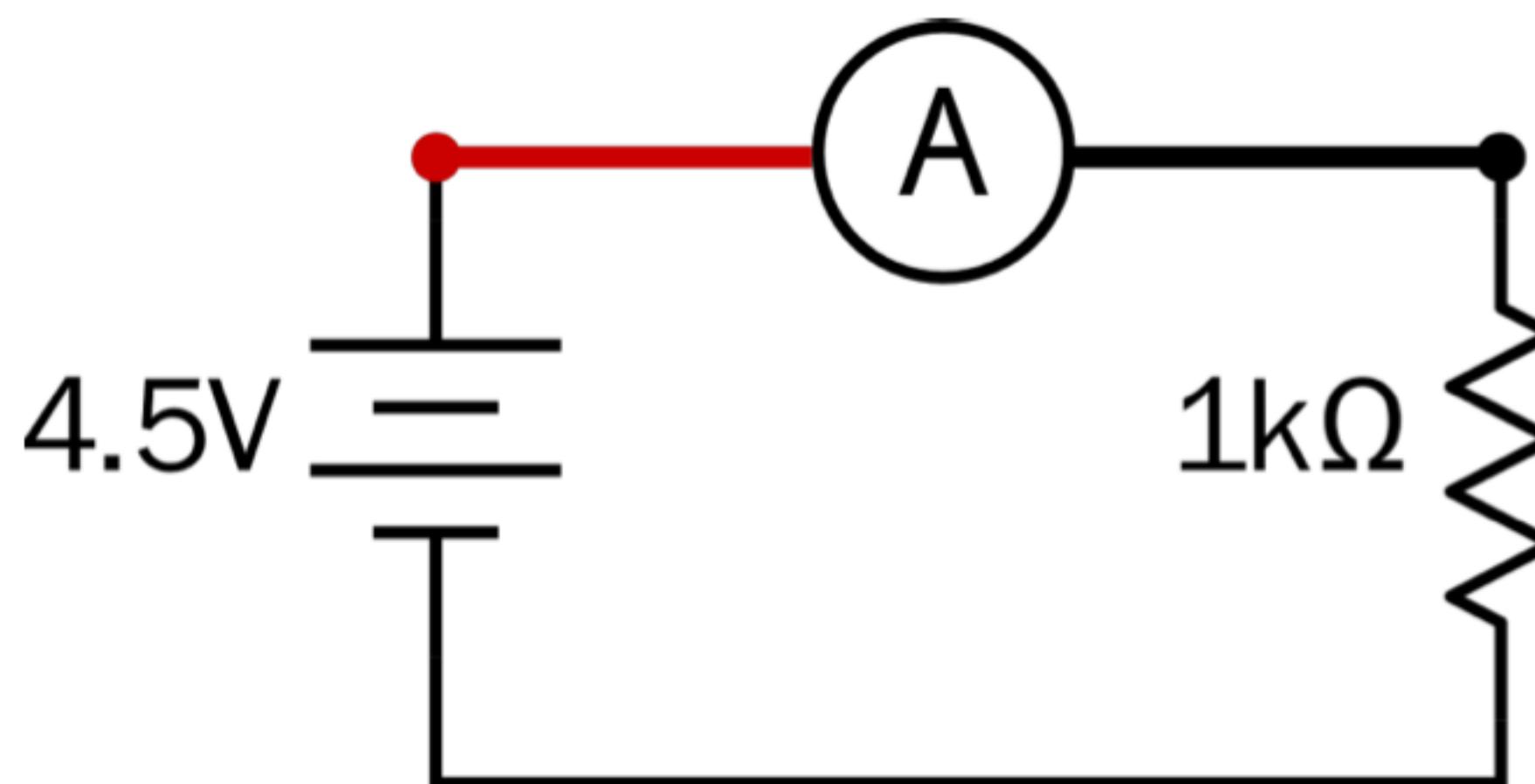- To measure current *through* a device, you must place the ammeter to have *the same current* as it.
- Therefore, ammeters **connect in series**.
- In order to avoid affecting the circuit, the ammeter takes close to zero *voltage*.
- We say that **the ideal ammeter looks like a short circuit**.




Never short-circuit a battery!

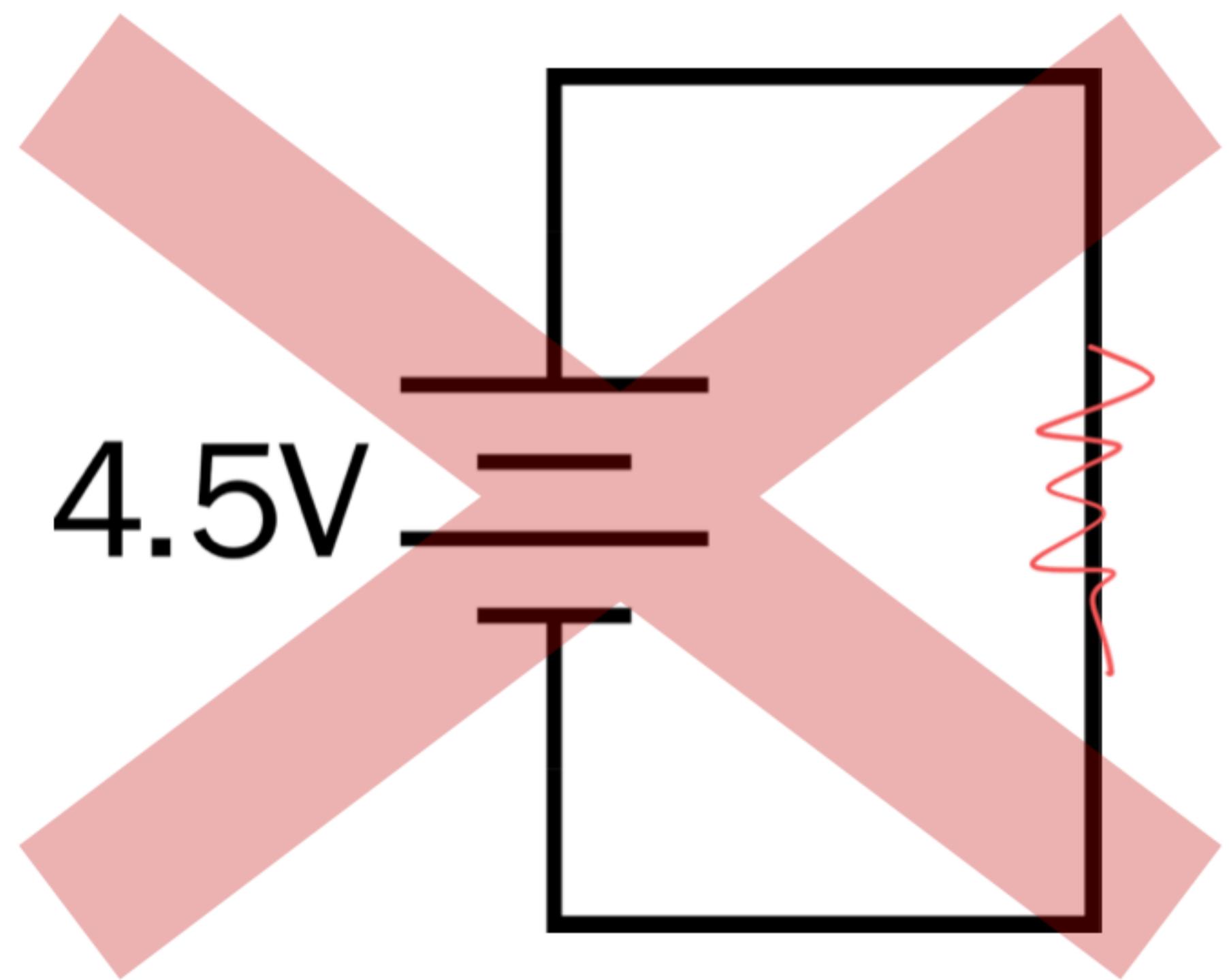- This circuit violates **Kirchoff's voltage law**
- In practice, if you do this, the wire draws a **very large current**
- **This can explode a battery!** (Or, make it very hot.)
- We call this **short-circuiting a battery**




Prevent short circuits, prevent disasters

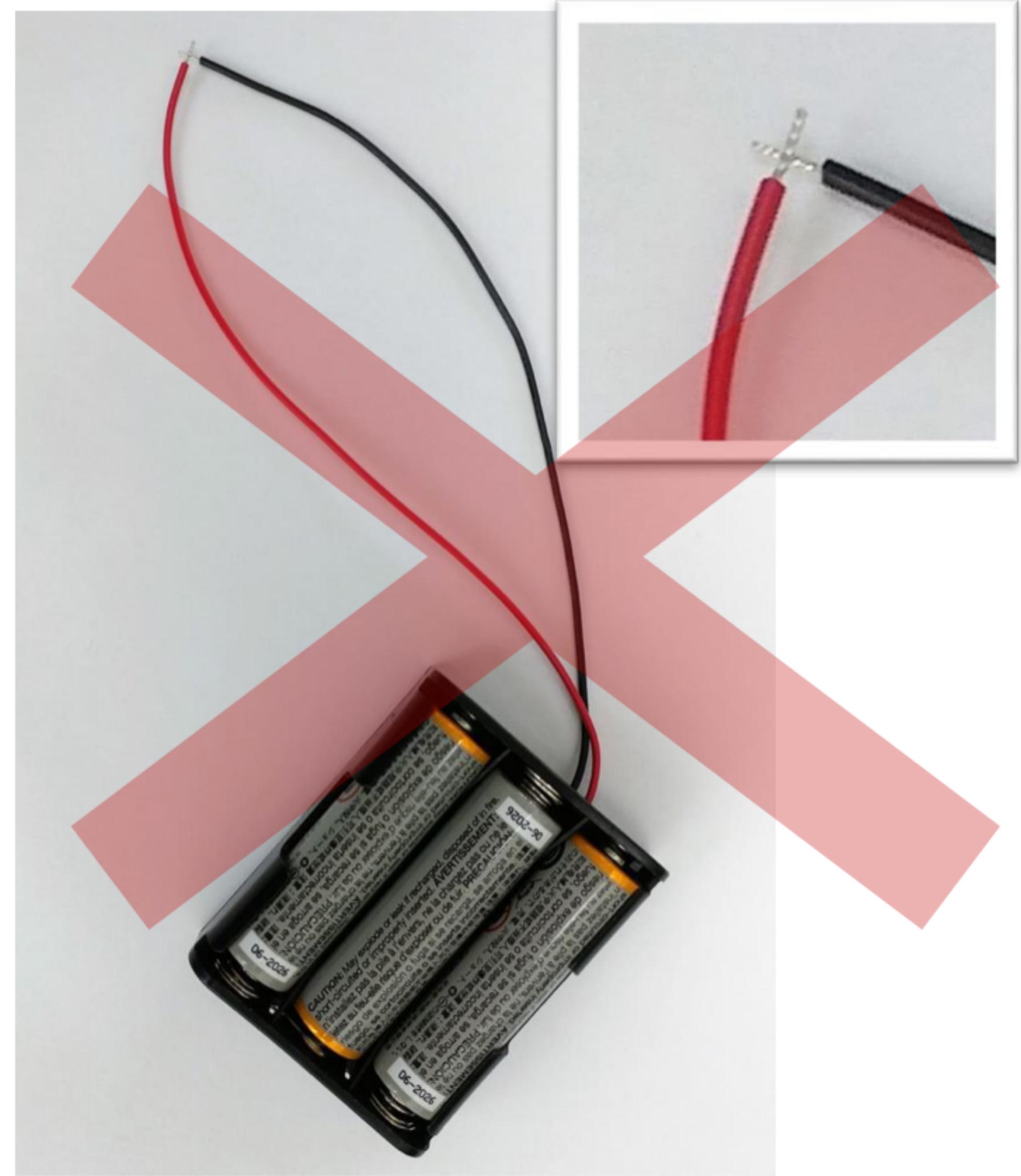- Battery (holder) leads can touch by accident, short-circuiting the battery
- Always remove a battery from the holder before putting it away
- Always make sure the leads of the lithium ion battery can't connect



Ammeters can short-circuit batteries!

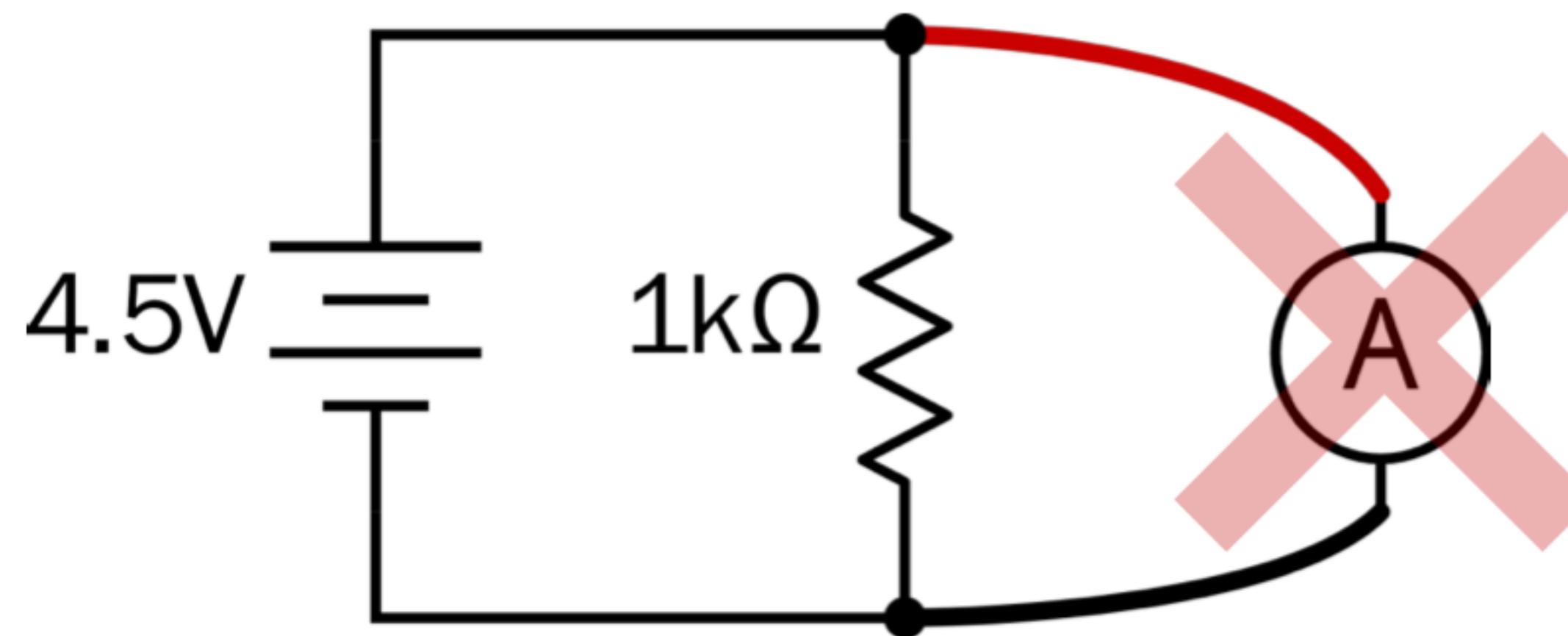- Connecting an ammeter in parallel with a battery short-circuits the battery
- This can also damage the multimeter
- **Never connect an ammeter in parallel with a battery**
- Be careful when switching from voltage to current mode!



How to read a resistor

- Resistors are marked with colored bands



- Pick your favorite resistor, and read its value

2703009
270kΩ



1000Ω = 1kΩ




0	0	Ω	($\times 10^0$)
1	1	0 Ω	($\times 10^1$)
2	2	00 Ω	($\times 10^2$)
3	3	k Ω	($\times 10^3$)
4	4	0k Ω	($\times 10^4$)
5	5	00k Ω	($\times 10^5$)
6	6	M Ω	($\times 10^6$)
7	7	0M Ω	($\times 10^7$)
8	8	00M Ω	($\times 10^8$)
9	9		

Using your ohmmeter

Do now:

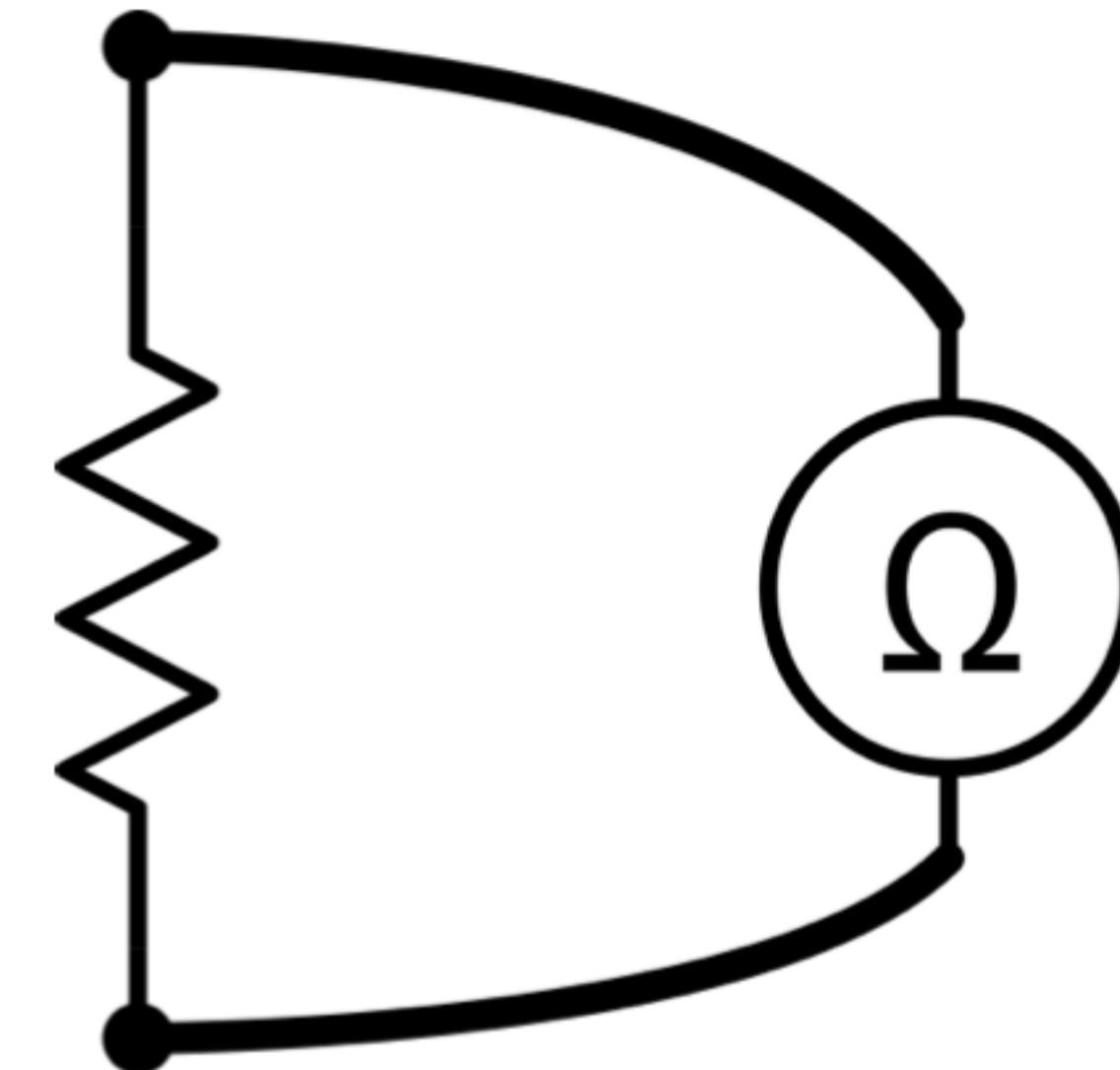- Measure the resistance of the resistor you just read
- **Note: No battery!**
- Does it match?



- Resistance is measured **without any power**
- For **resistors**, polarity doesn't matter



Resistance modes


Remember

- Voltmeters connect in parallel
- Ammeters connect in series
- Ohmmeters do not connect to a live circuit
- You need to choose the right scale
- Connecting an ammeter incorrectly can destroy your circuit, your multimeter or both

Characterizing your solar cell (1)


Open-circuit voltage

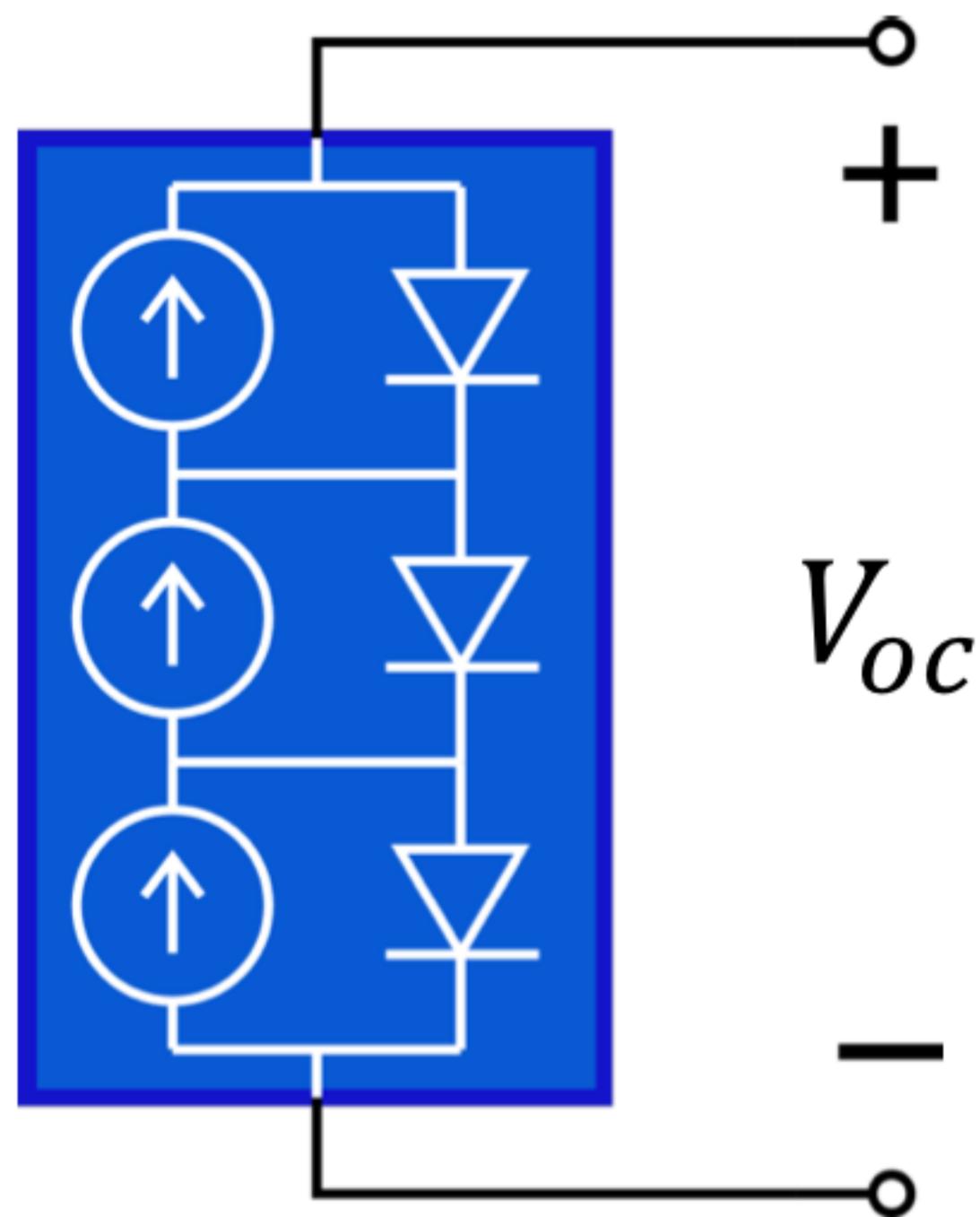- Voltage across the cell when connected to an open circuit



Short-circuit current

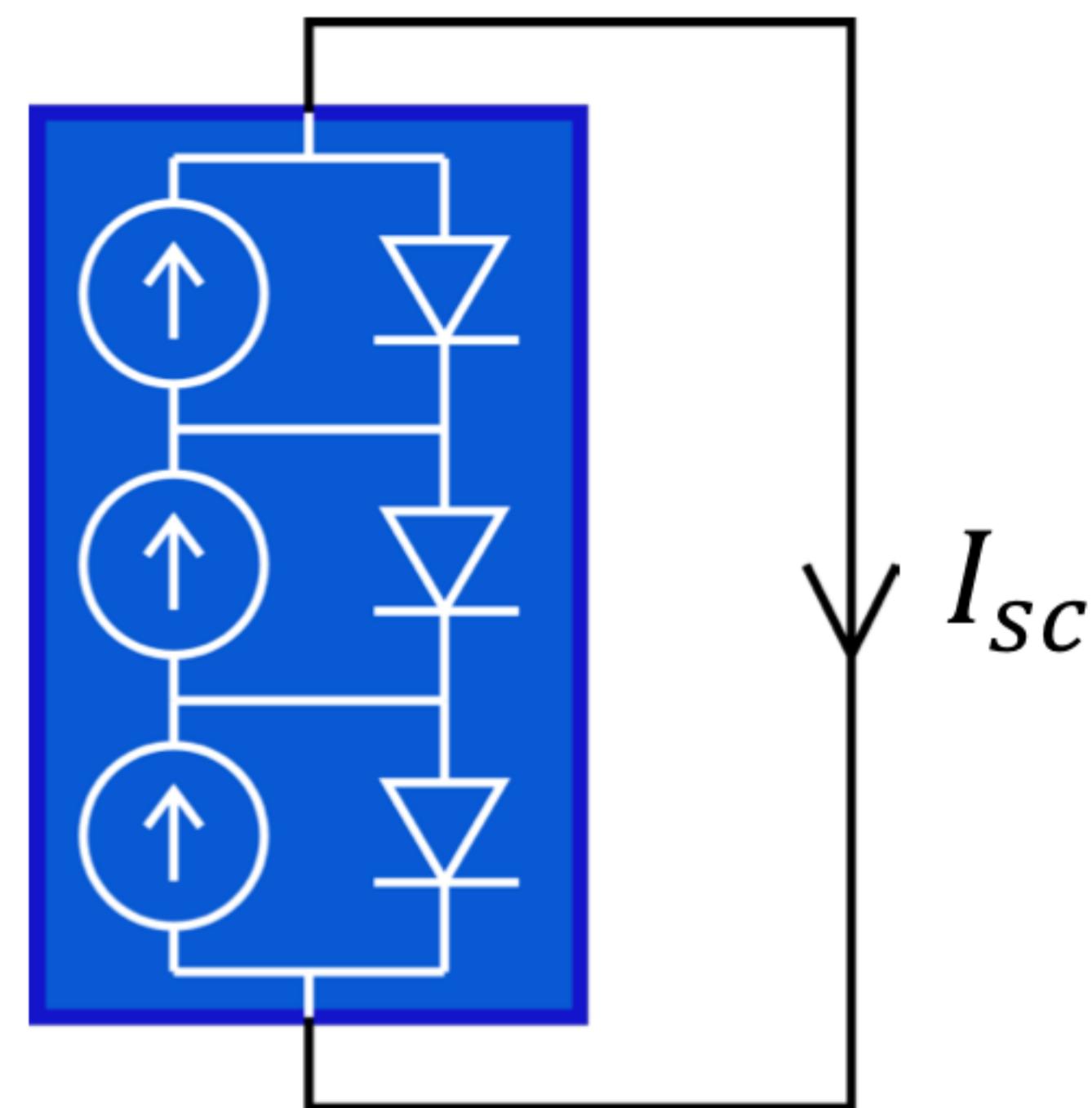
- Current through the cell when connected to a short circuit




Characterizing your solar cell (2)

- Measure the **open-circuit voltage** of your solar cell
- Measure the **short-circuit current** of your solar cell

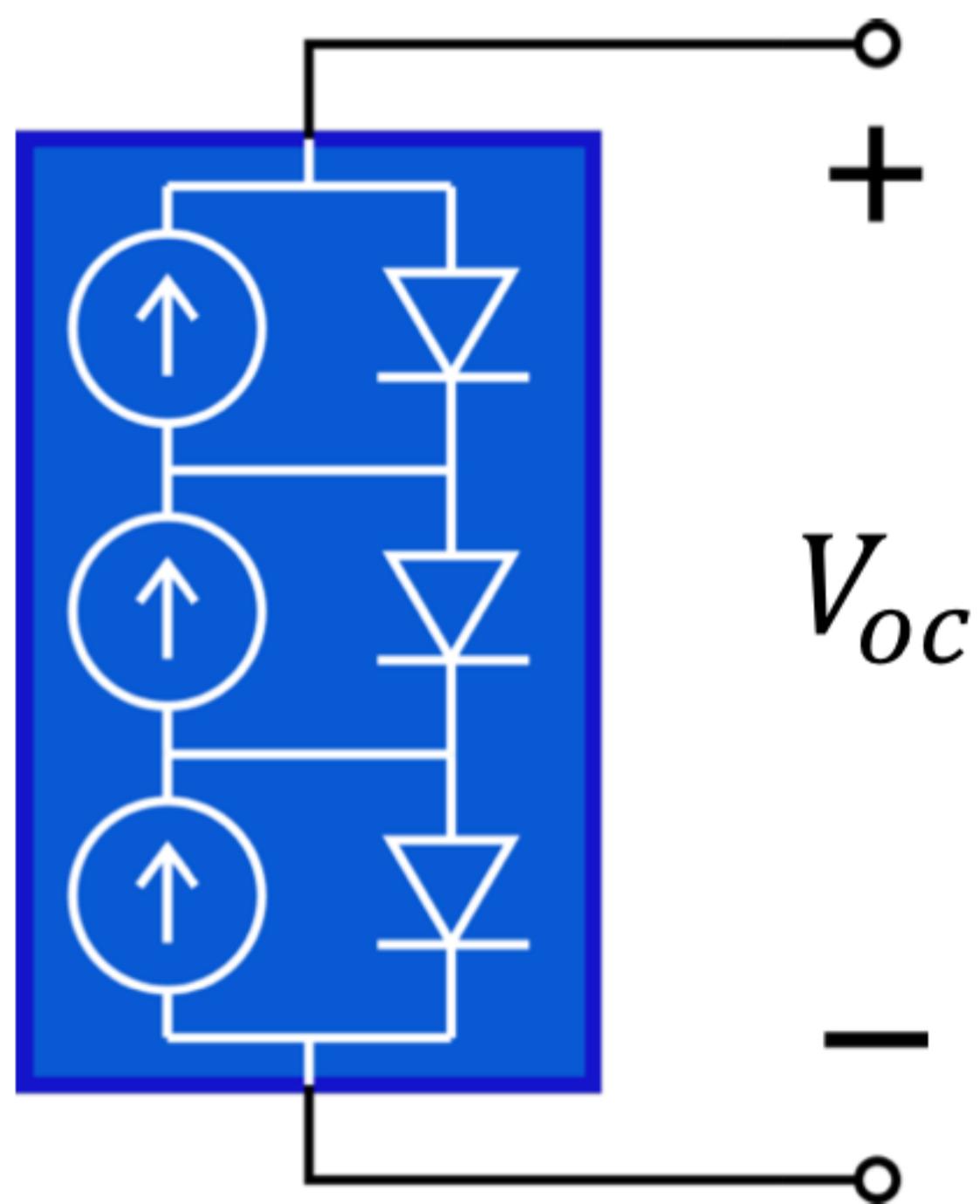Note: Doing it here is *not* the answer to your prelab question P3. Why not?






$$V_{oc}$$

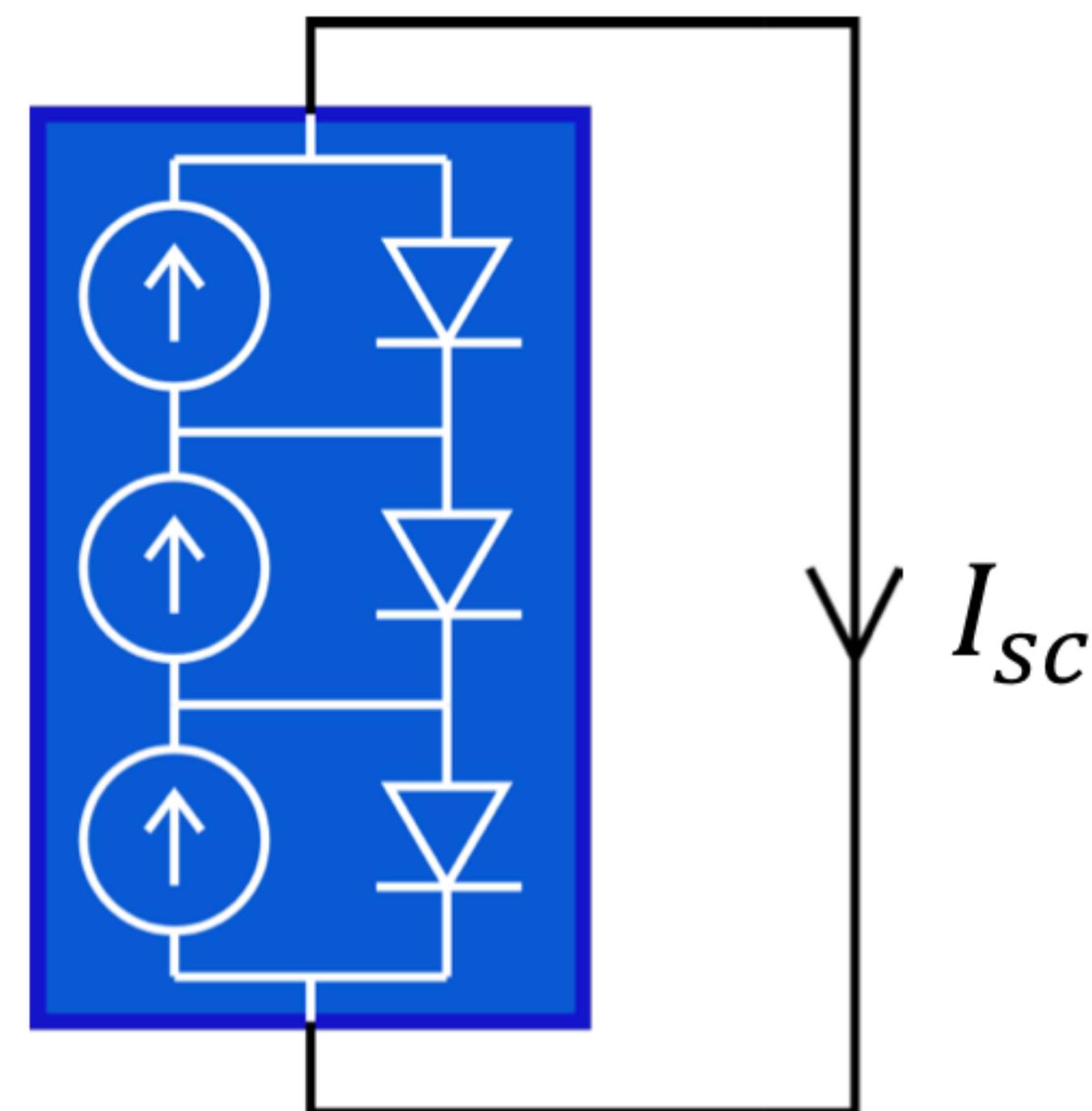


$$I_{sc}$$

Don't be fooled

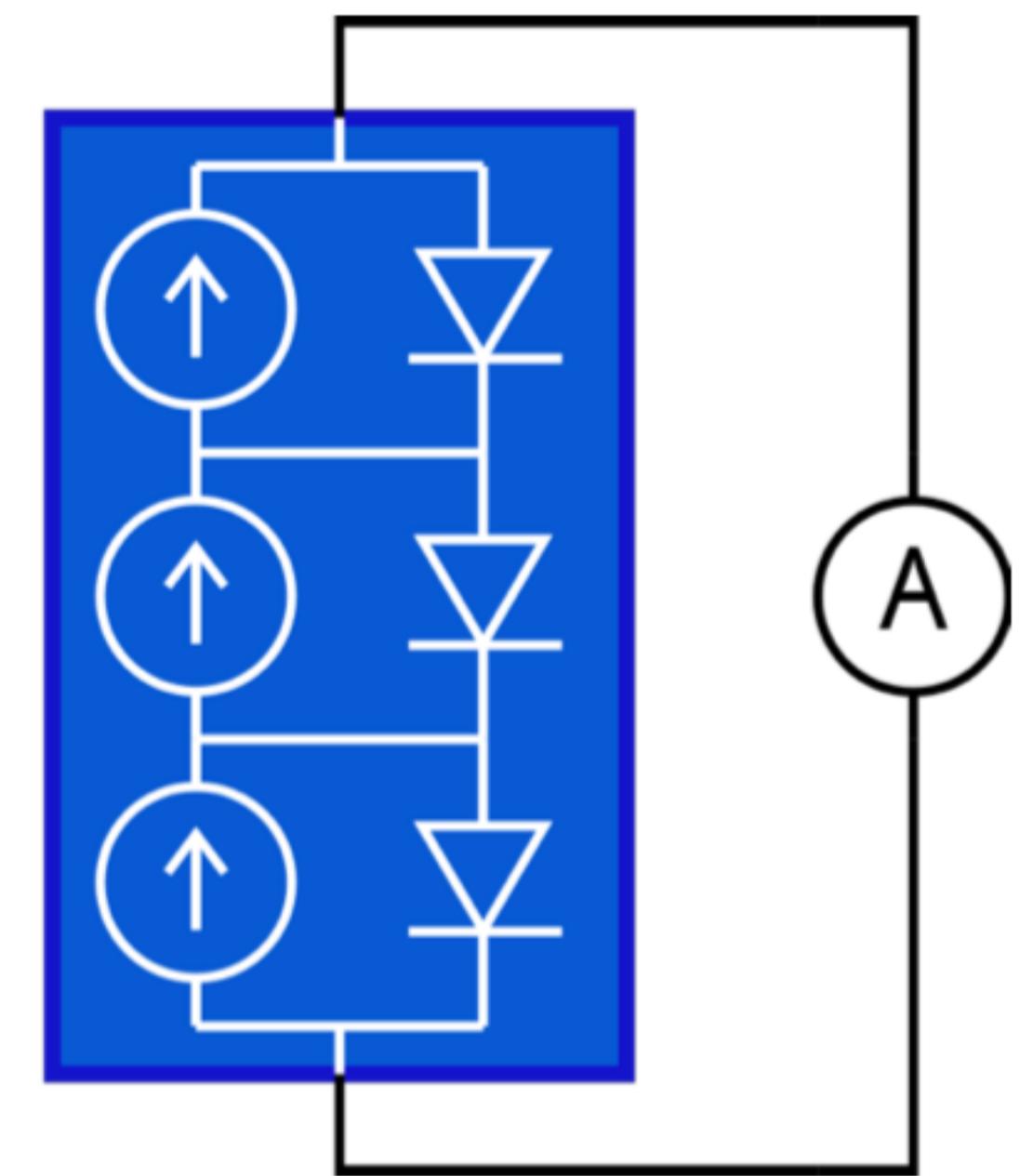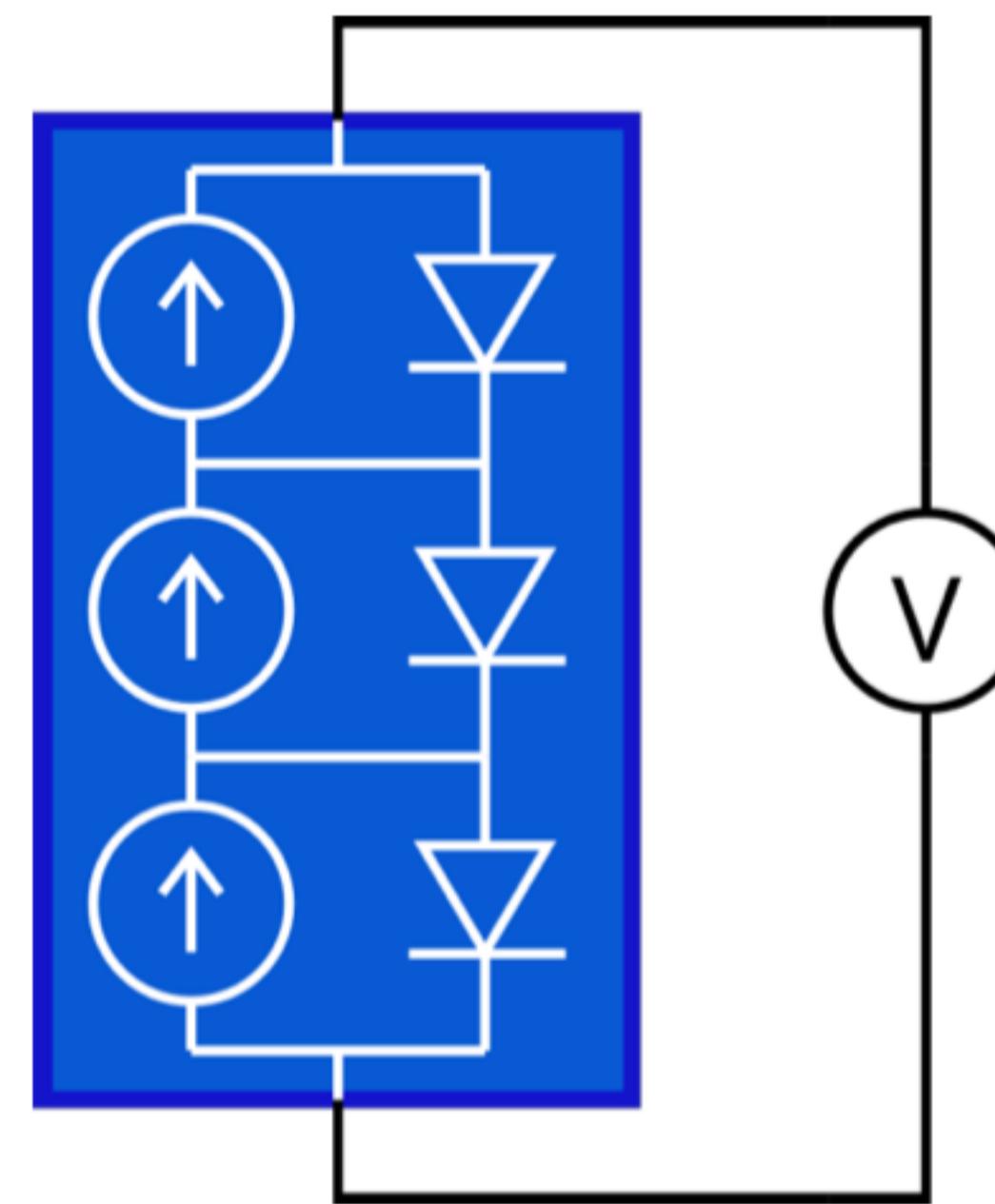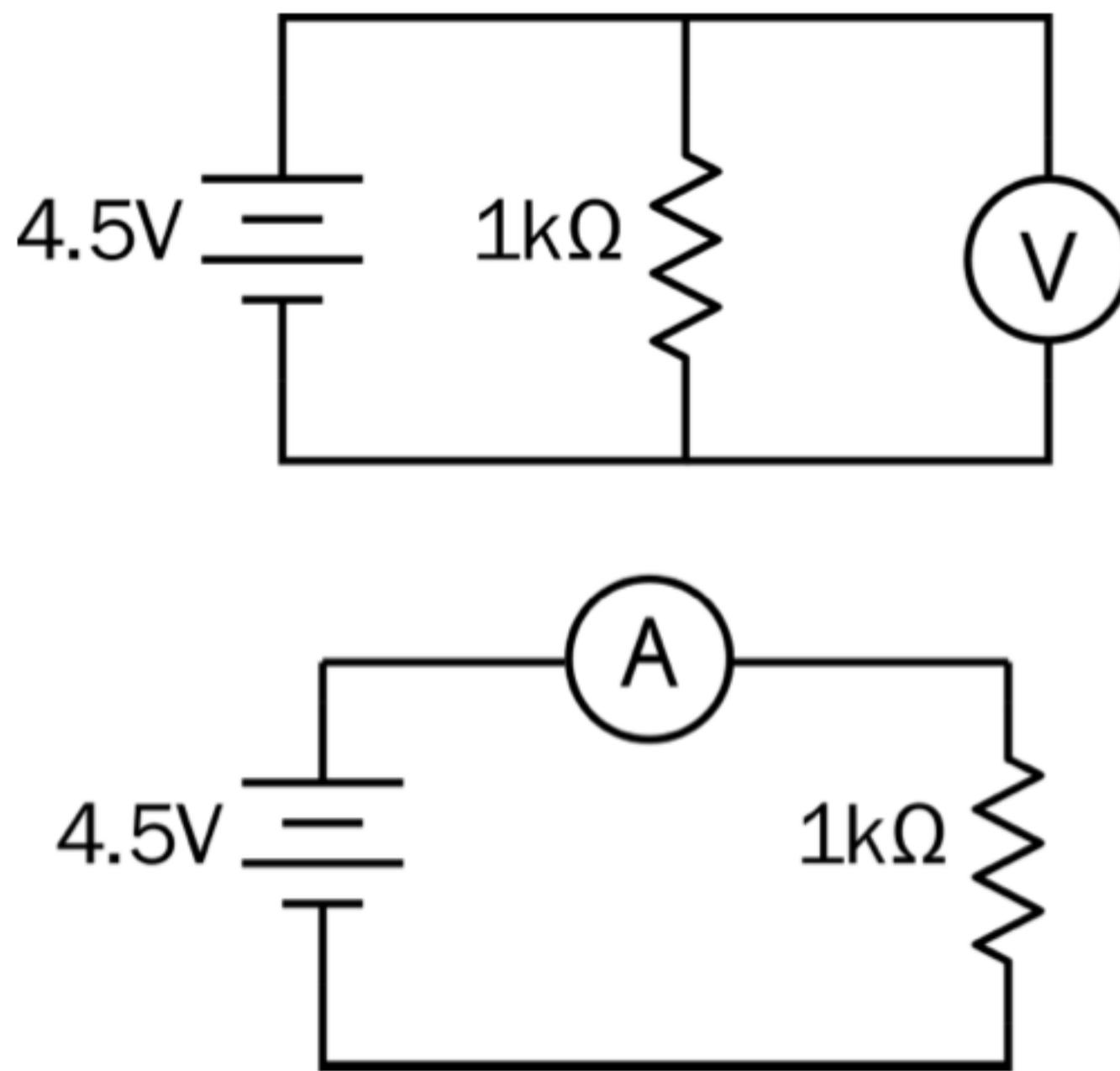
- The two meters on the left are measuring the same circuit
- The two meters on the right are measuring the solar cell in **different circuits!**




Power from I-V characteristic (1)

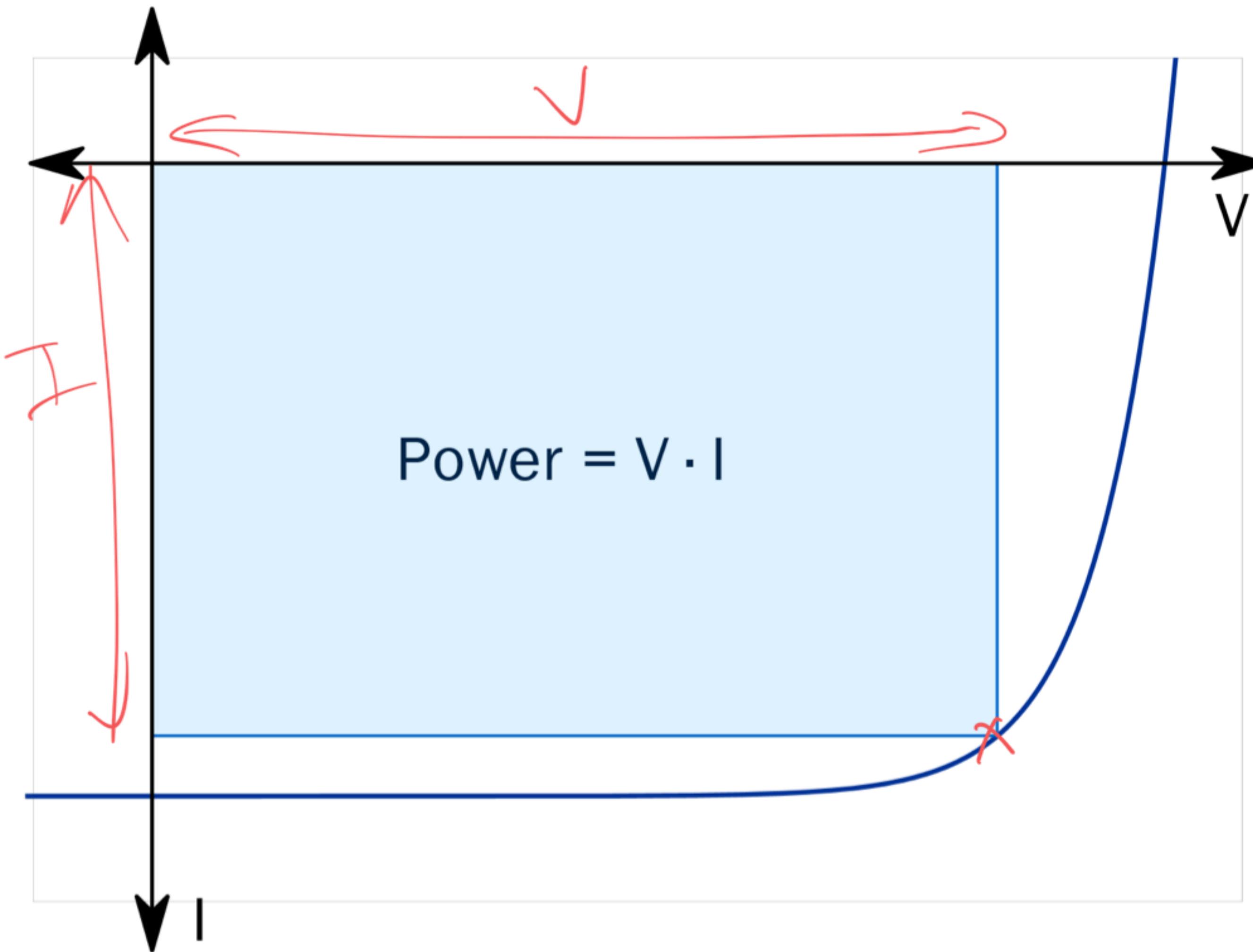

Power from I-V characteristic (2)

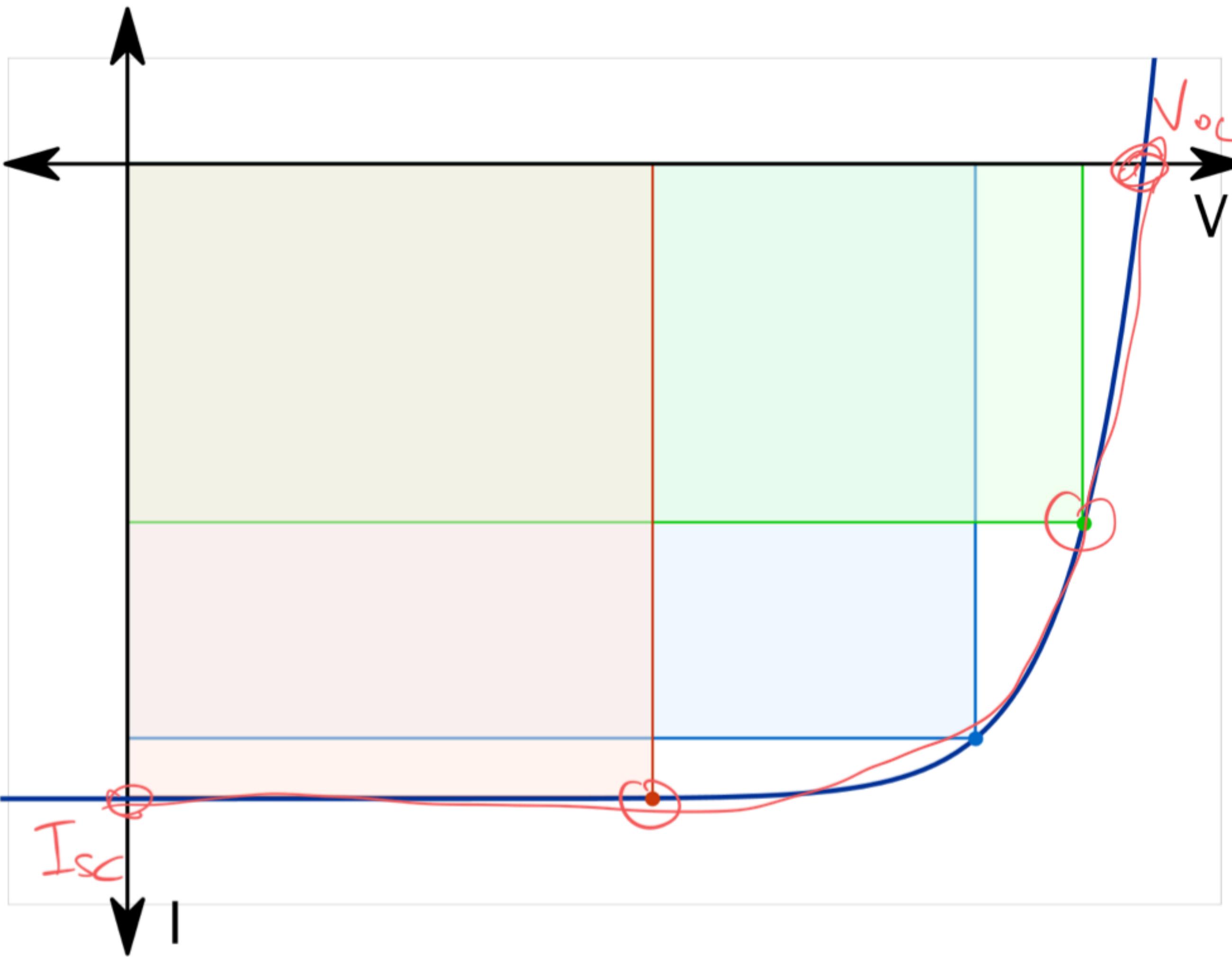


Power from I-V characteristic (3)

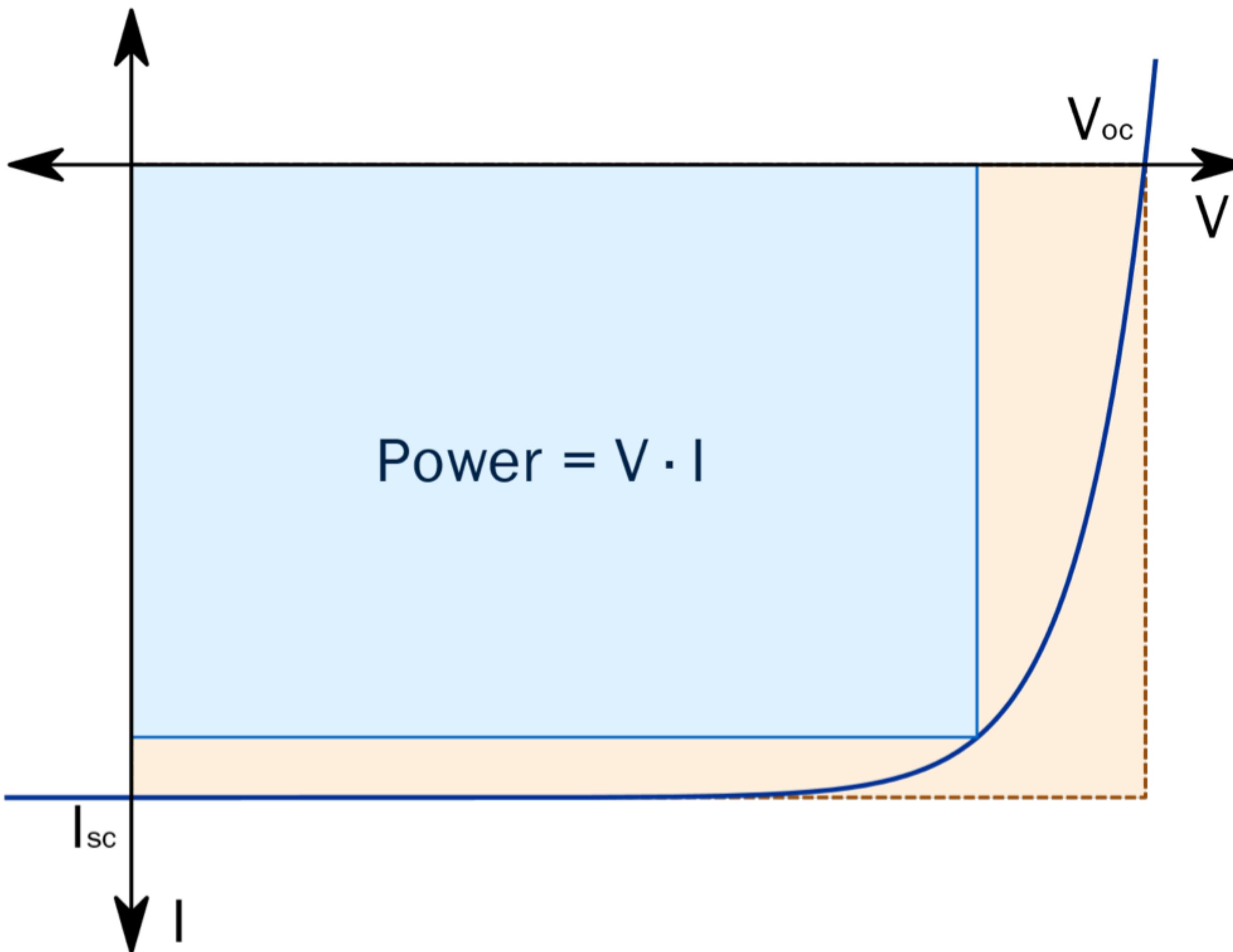

Leakage current

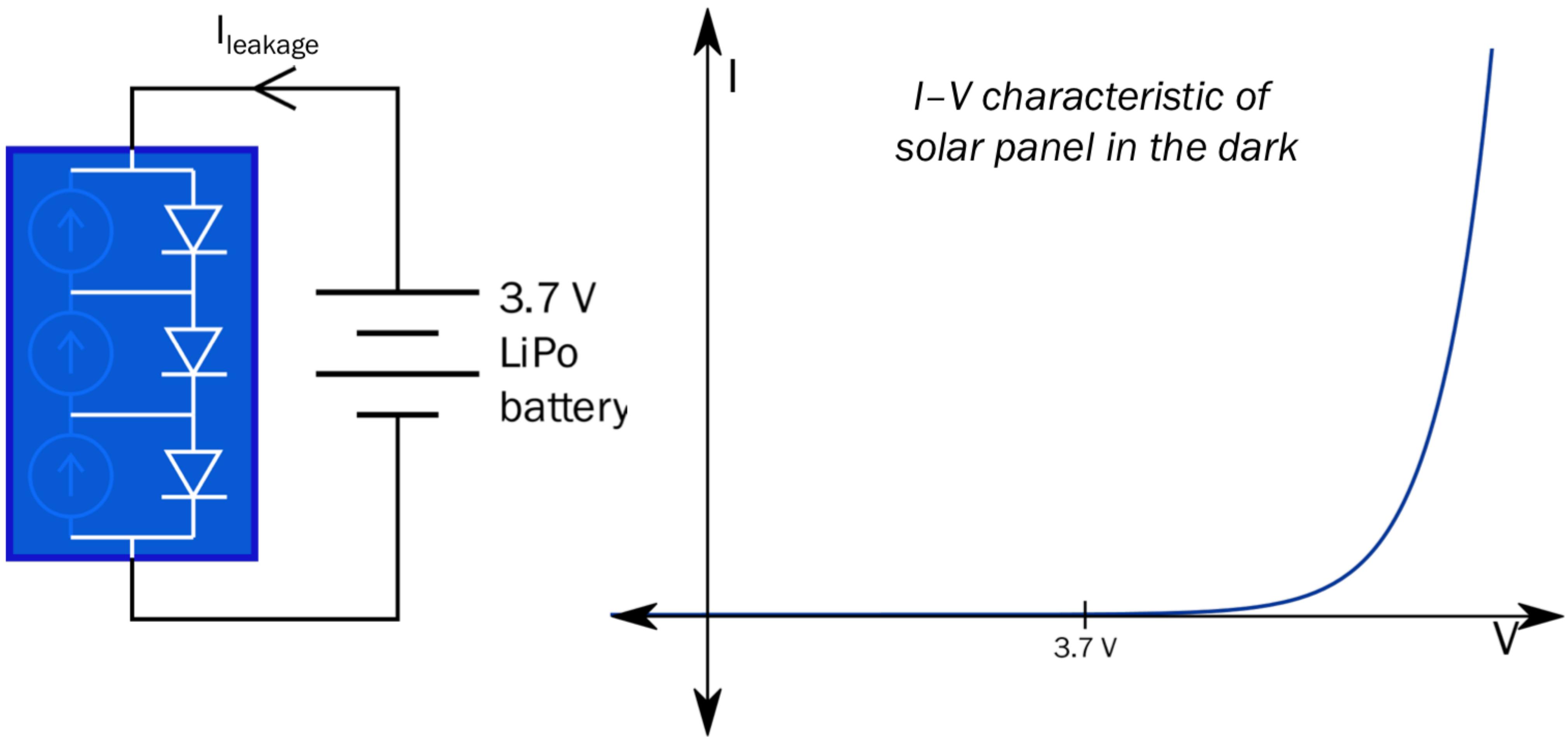In the dark, the solar panel looks like a stack of diodes



Your voltage converter

- A *voltage converter* is a circuit that takes an input supply at one voltage, and uses it to provide a different voltage to another circuit
- When the output voltage is greater than the input voltage, we call it a **boost converter**
- Your converter will take any voltage less than 5V, and output 5V to its USB port



Voltage converter efficiency

- Conservation of energy implies that the output power cannot be more than the input power

$$V_{\text{in}}I_{\text{in}} = P_{\text{in}} \geq P_{\text{out}} = V_{\text{out}}I_{\text{out}}$$


- All real converters lose energy in the conversion. We can compute their **efficiency**:

$$\text{efficiency} = \frac{P_{\text{out}}}{P_{\text{in}}} = \frac{V_{\text{out}}I_{\text{out}}}{V_{\text{in}}I_{\text{in}}}$$

- Efficiency is generally **not** a constant. It is generally quoted under particular conditions.

Converter efficiency: Example

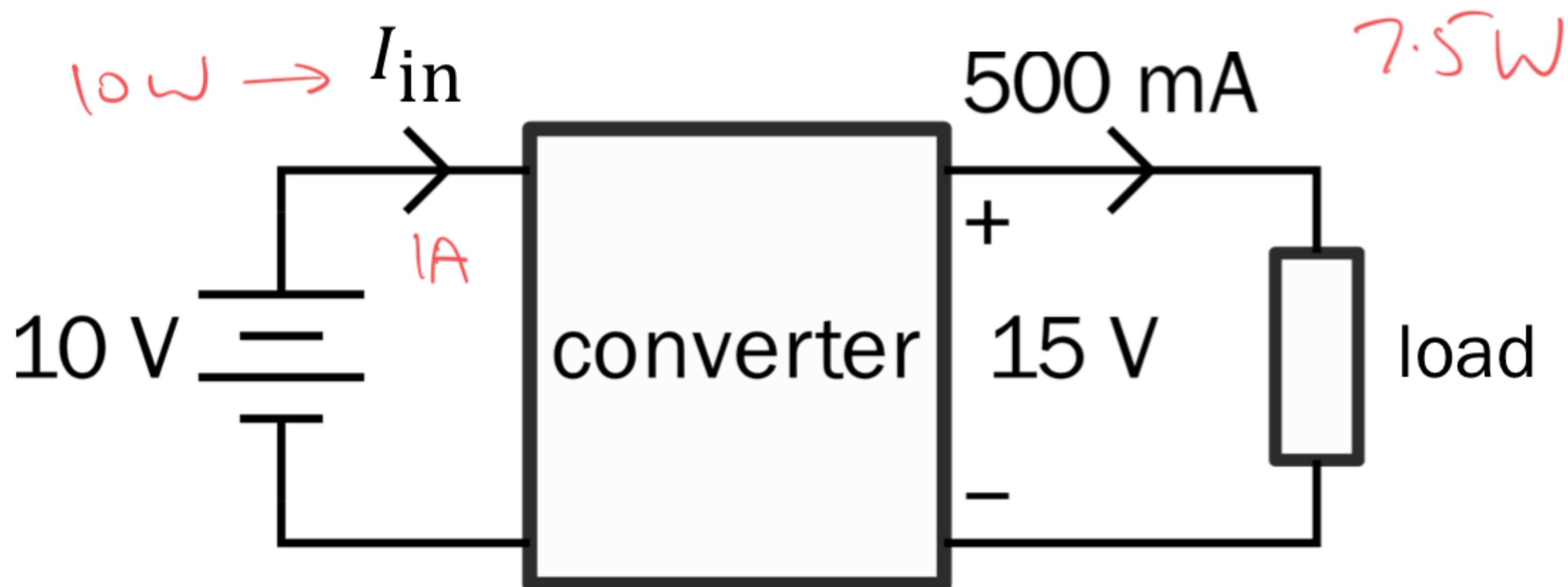
A boost converter takes an input of 10 V and provides an output of 15 V. When a load of 500 mA is placed at the output, its efficiency is 75%. What is the input current I_{in} ?



Designing a solar charger circuit

- Battery should power the converter
- Solar panel should charge battery

Your solar charger's circuit

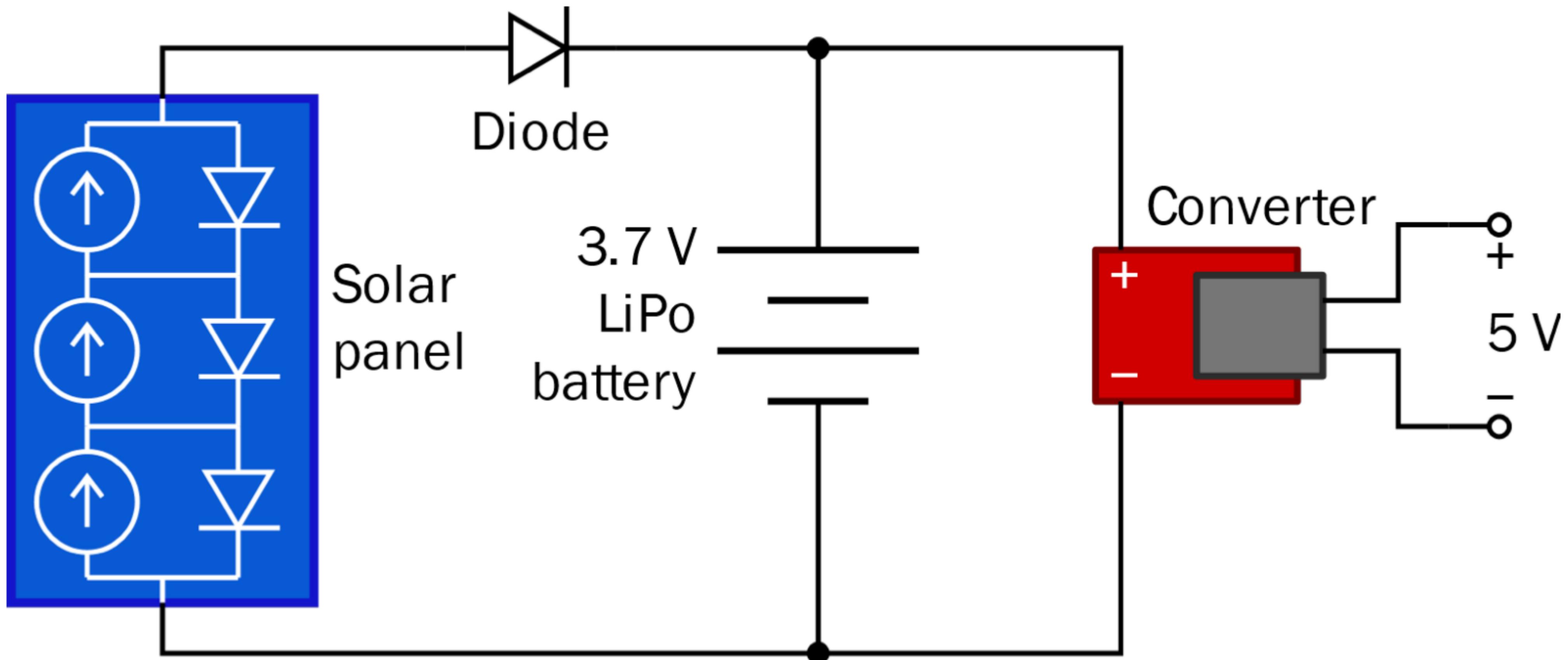

Practical matters: Wire colors

- It is convention in electronics to use
 - **black** for negative/ground, and
 - **red** for positive supply nodes.
- It is really, *really* confusing when you don't follow this convention. Please follow it.

Practical matters: Planning

- Plan your layout before you make anything permanent!
 - How long do your wires need to be?
 - Do you need to fit anything else in?
 - Soldering and tape are hard to undo
- Your LiPo battery must be well protected from the outside world, e.g., sharp objects in your bag

Practical matters: Soldering

- TAs will demonstrate soldering in labs.
- Soldering is a skill that we want you to develop. We will assess your soldering, but not in lab 1.
- You've been learning this week, hopefully!
- Your solar panel is a large heatsink, so will be a bit harder. Patience is your friend.