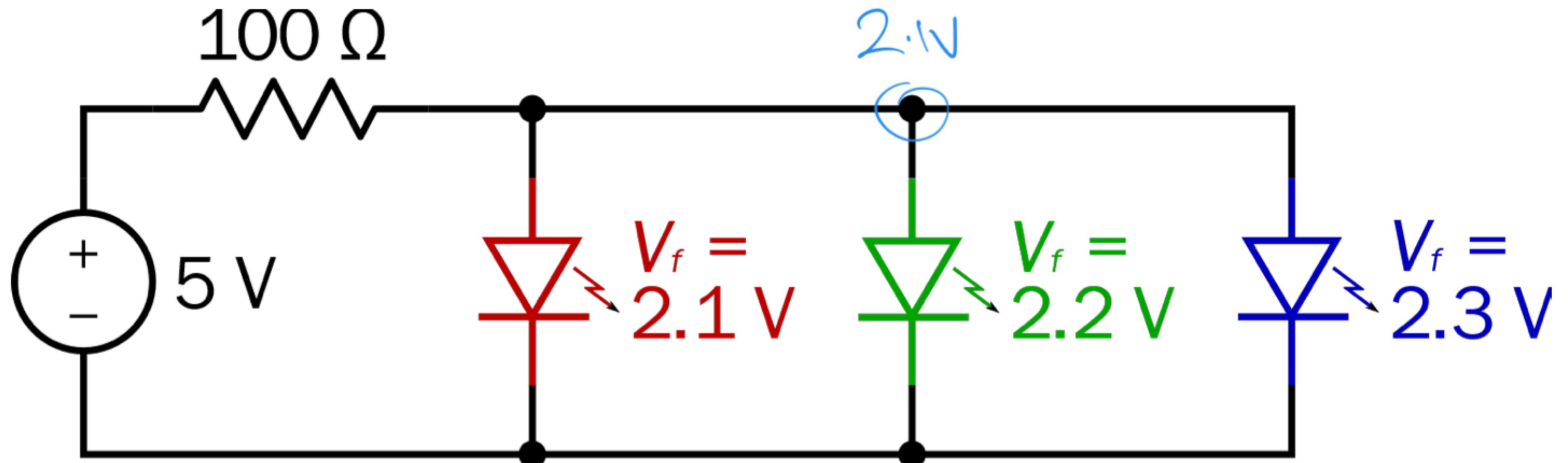


Go to [www.menti.com](http://www.menti.com) and use the code 43 60 74

Which LED(s) turn on?



# Lab 3a

## The LED cube

ENGR 40M  
Chuan-Zheng Lee  
Stanford University  
5 May 2017

# Announcements

---

- No prelab this week...
  - except to think about what color LEDs you want
  - unless you want to do a custom LED structure
- No homework next week
- Mid-quarter survey open till midnight tonight
- Midterm is next Wednesday during class
  - Covers up to lecture slides 9, lab 2b, homework 4


white  
red  
green  
blue

# Outline


---

1. Hardware to make your LEDs work
2. Getting from an  $8 \times 8$  array to a  $4 \times 4 \times 4$  cube
3. Tips for putting your cube together


# Review: Pin multiplexing

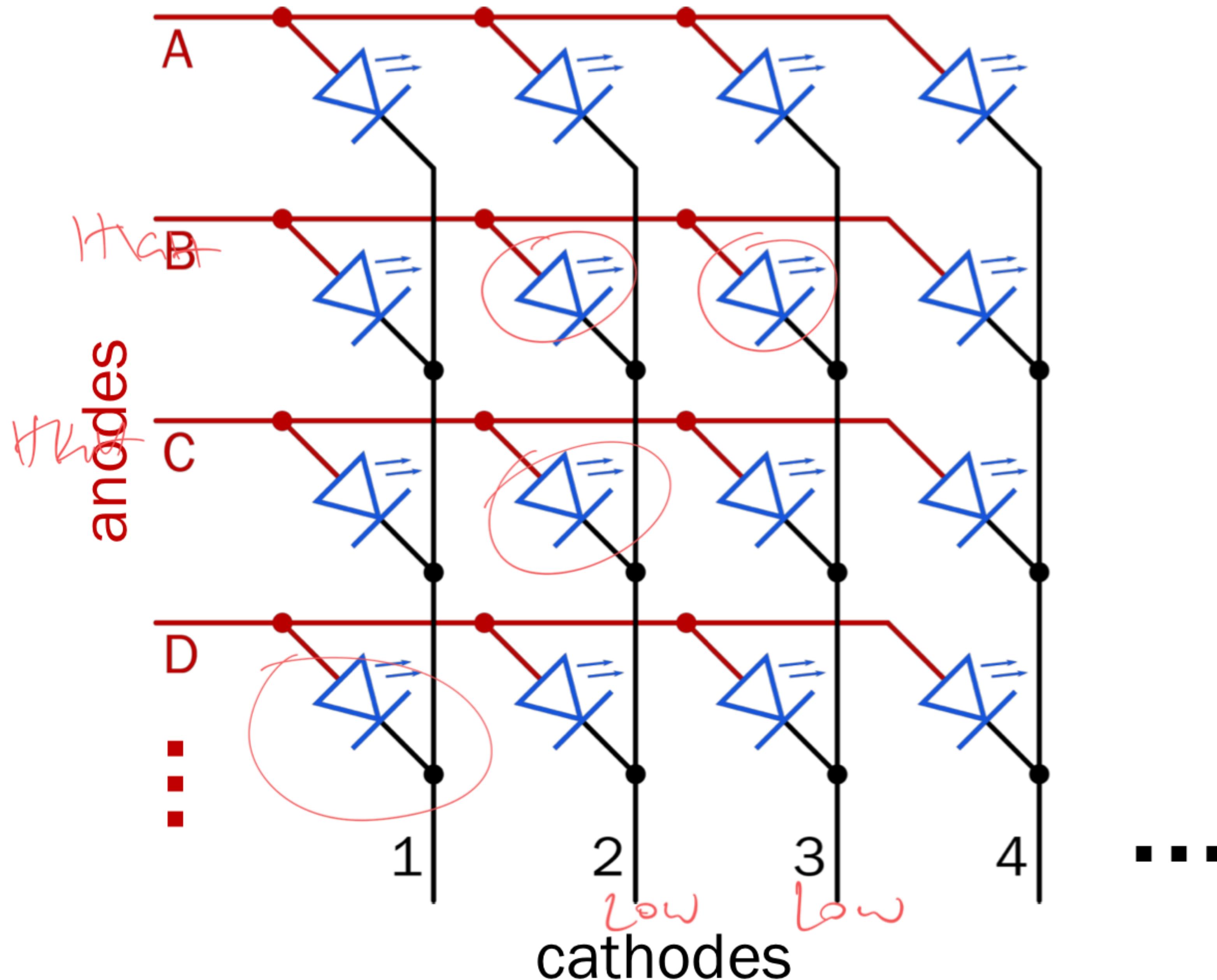


# Where should we put the resistors?

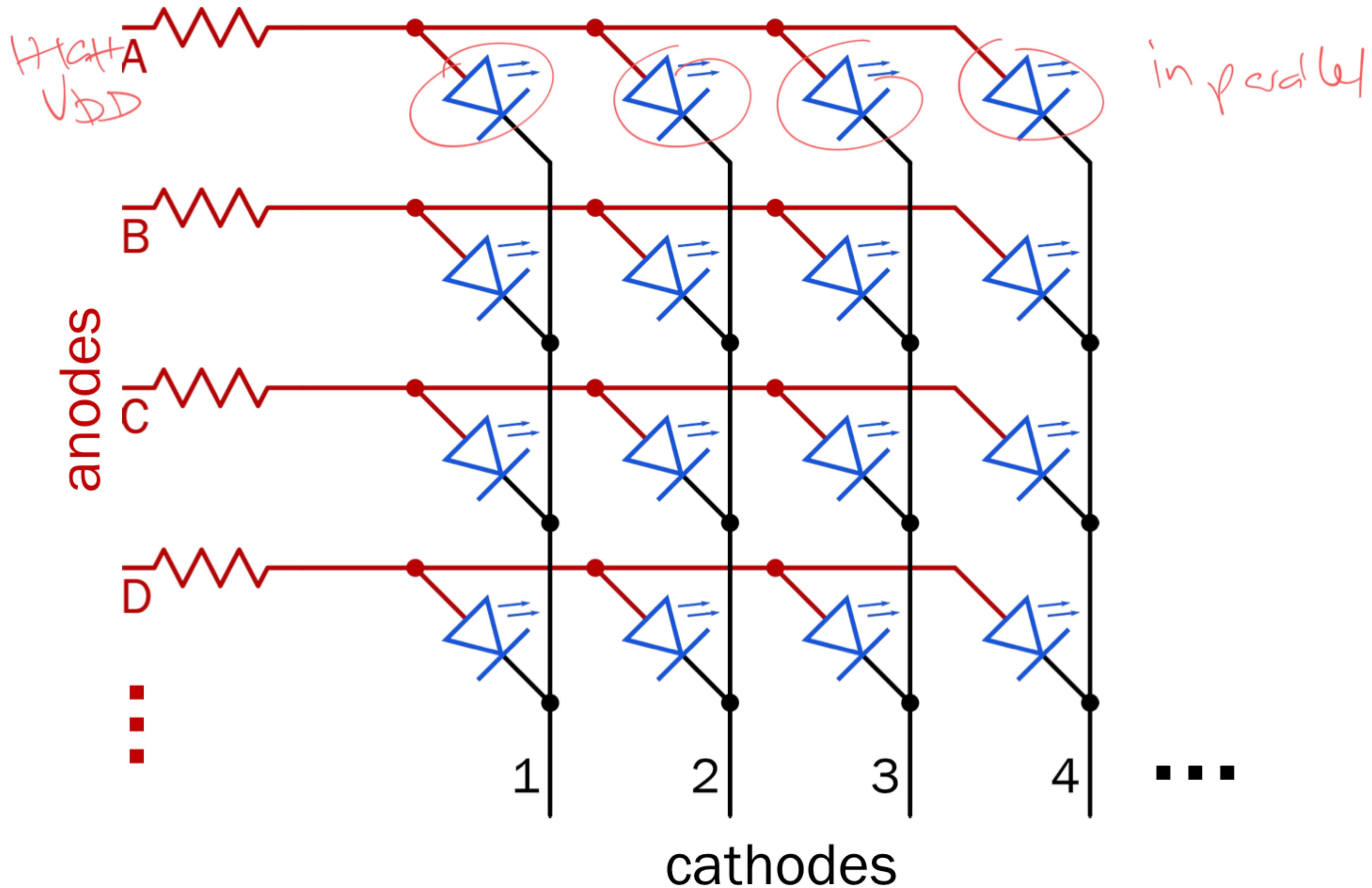


# Where should we put the resistors?

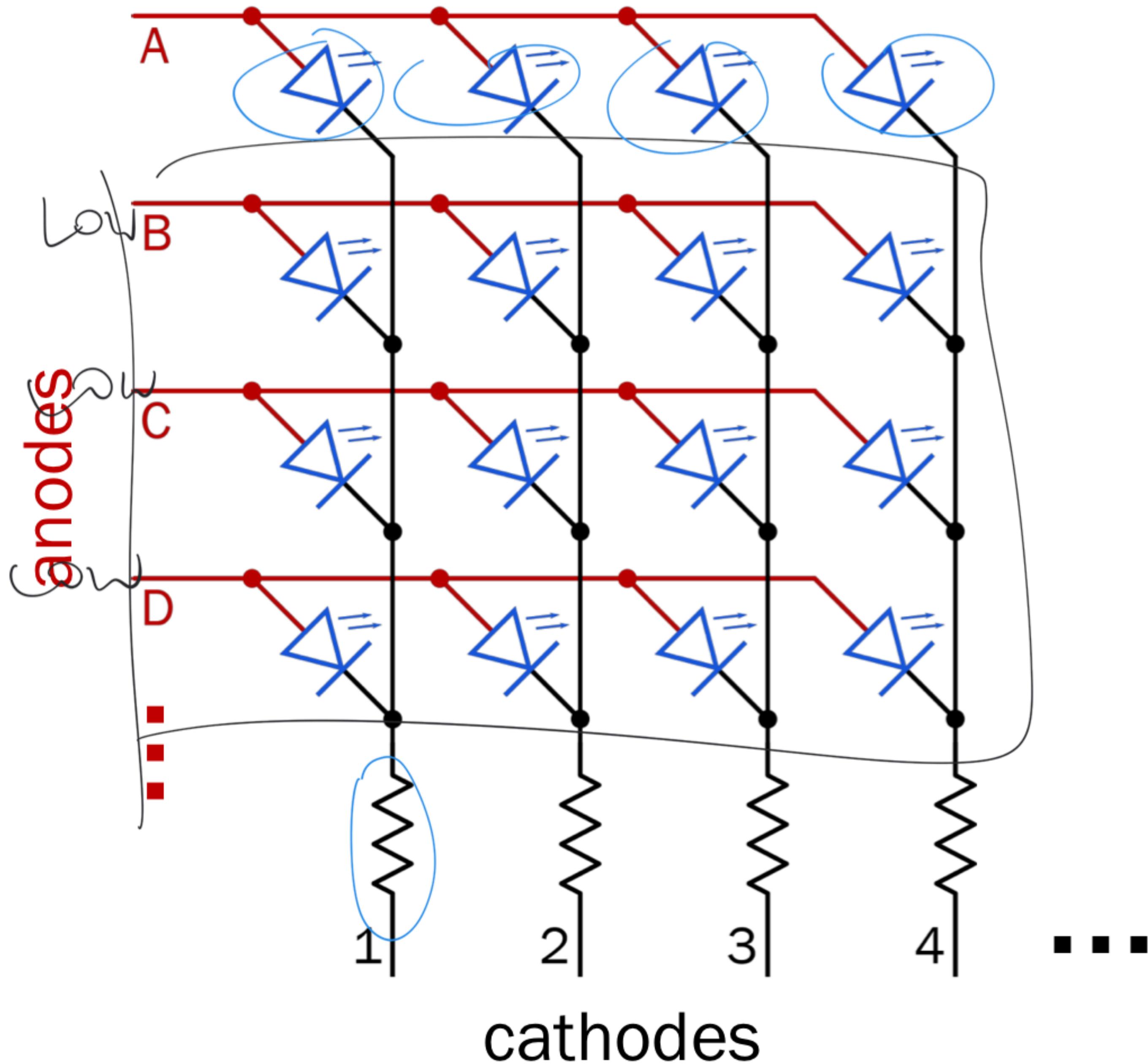

# How many LEDs could be on at once?

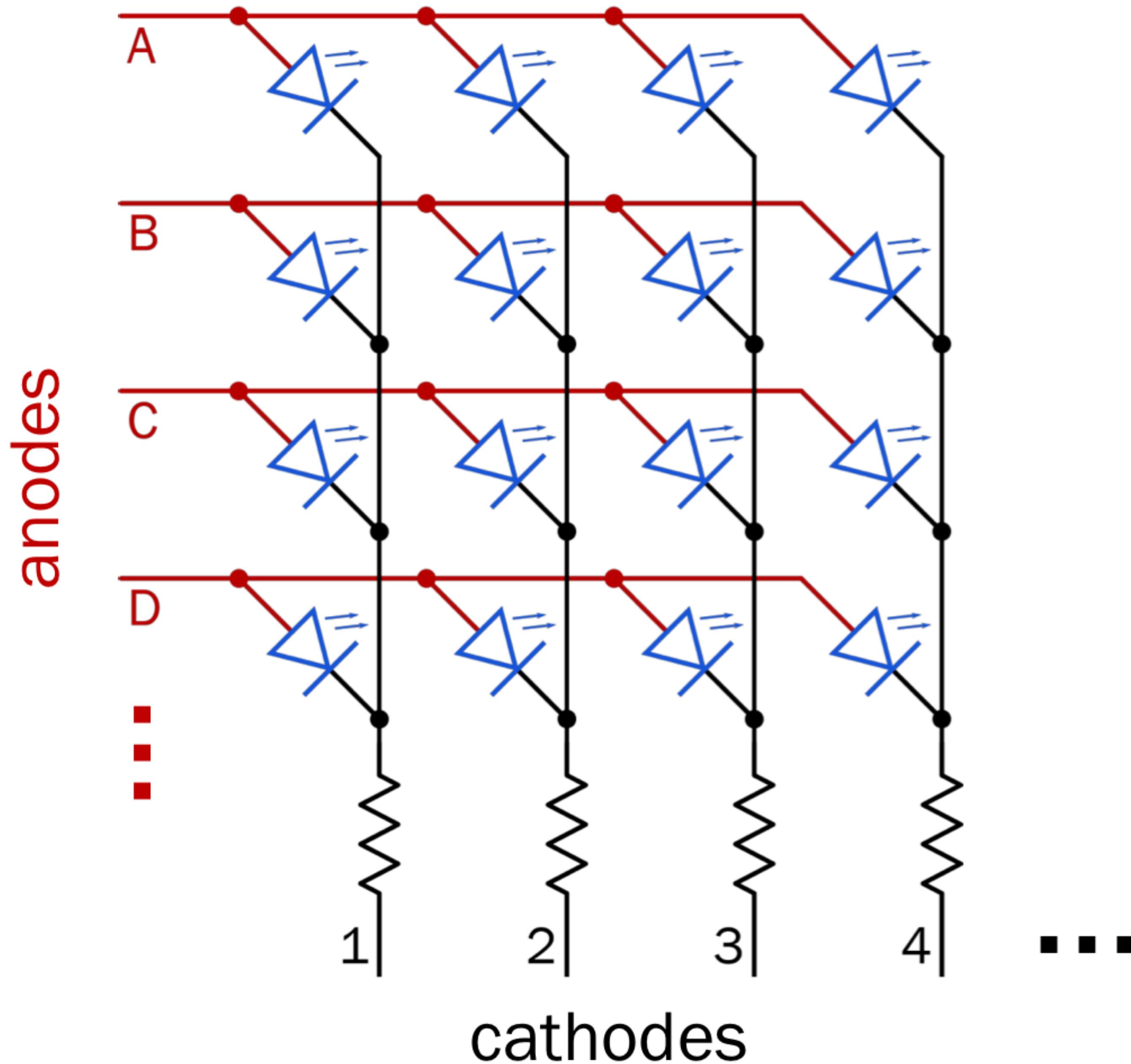

# How many LEDs could be on at once?

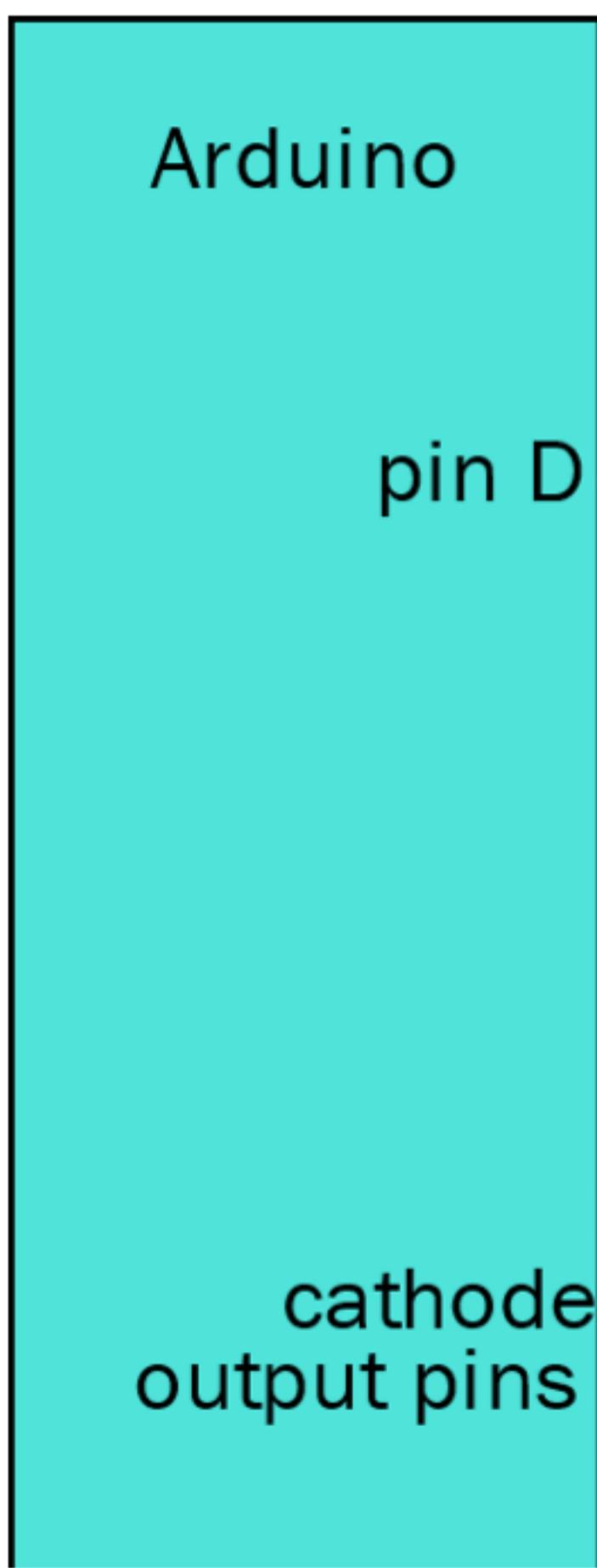


If I want each LED, when on, to conduct 10 mA, and all of the LEDs in a row are on, how much current must pin D provide?
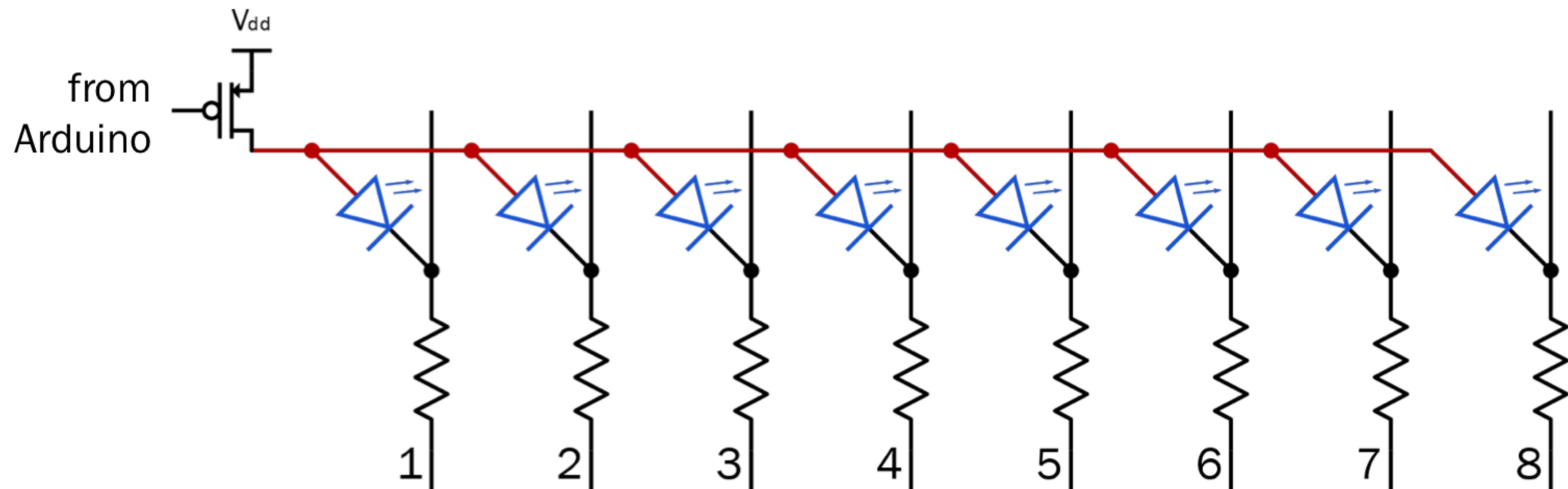
# Providing enough current


---

Use a PMOS to provide enough power to the LEDs




# Putting it all together

---

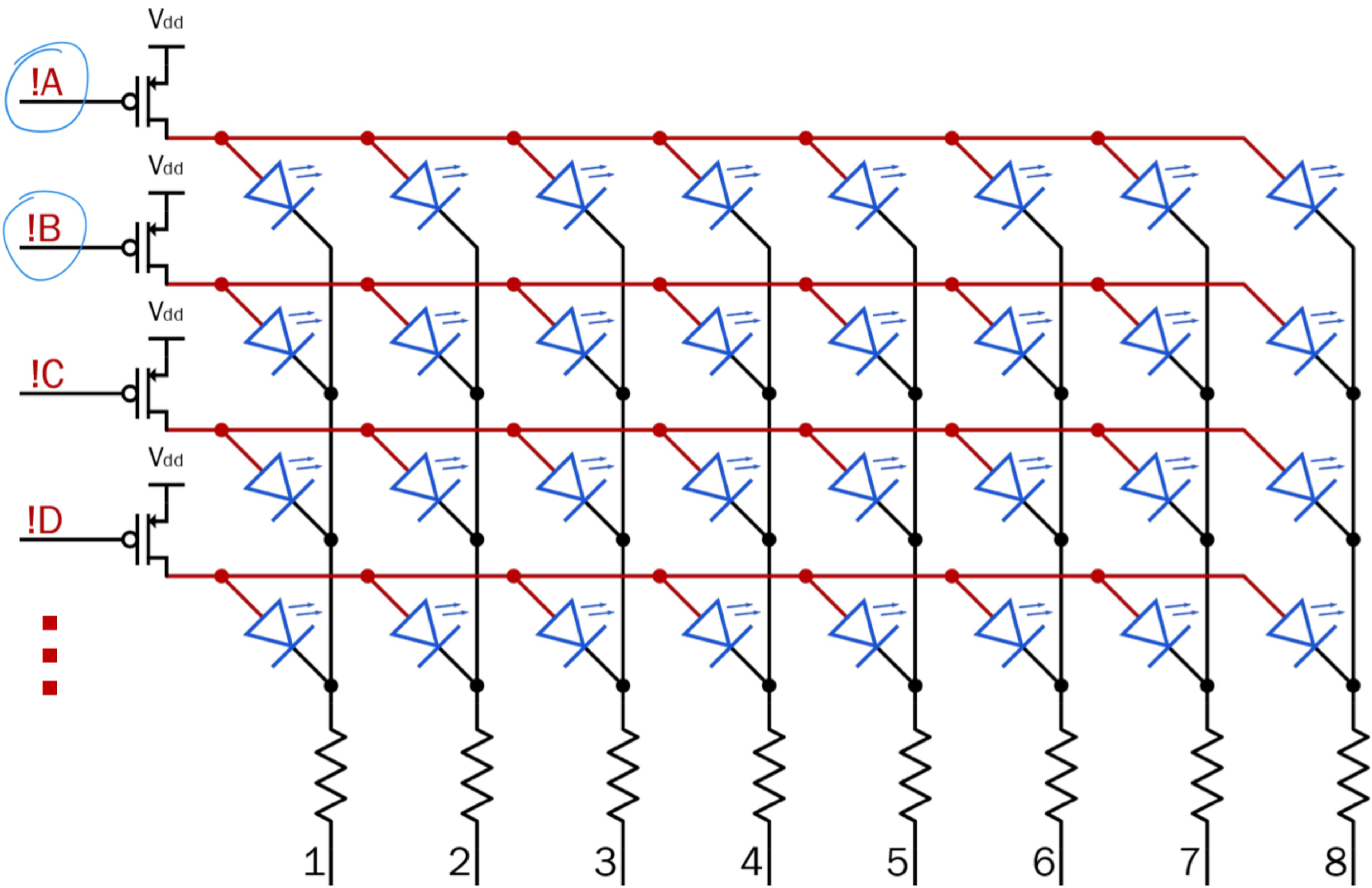

# Electrically it's an array, but physically...

---

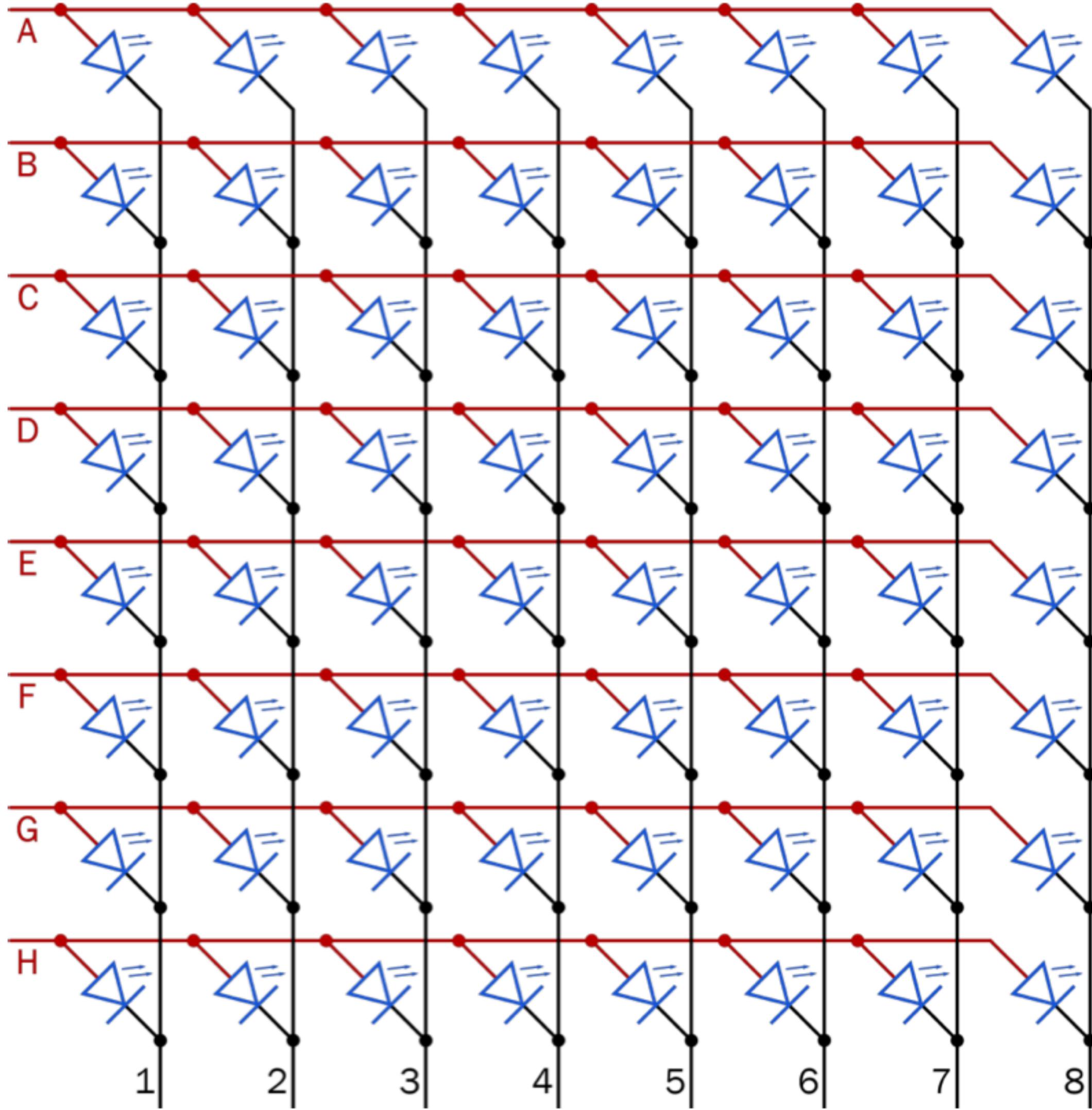


How do we  
arrange these in a  
 $4 \times 4 \times 4$  cube?

# ...it's a cube?



---



...it's a cube?

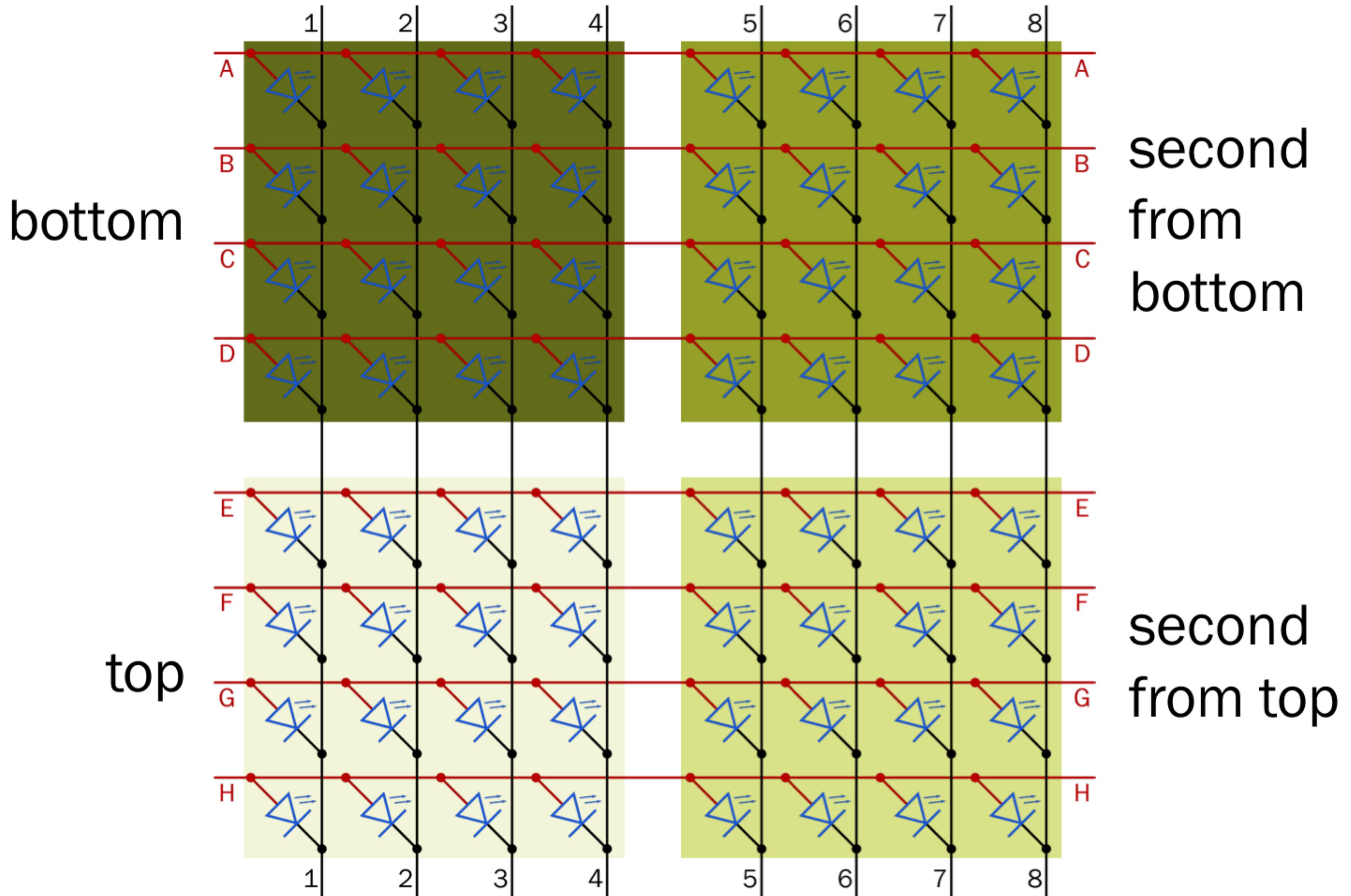

# Mapping between 2-D and 3-D

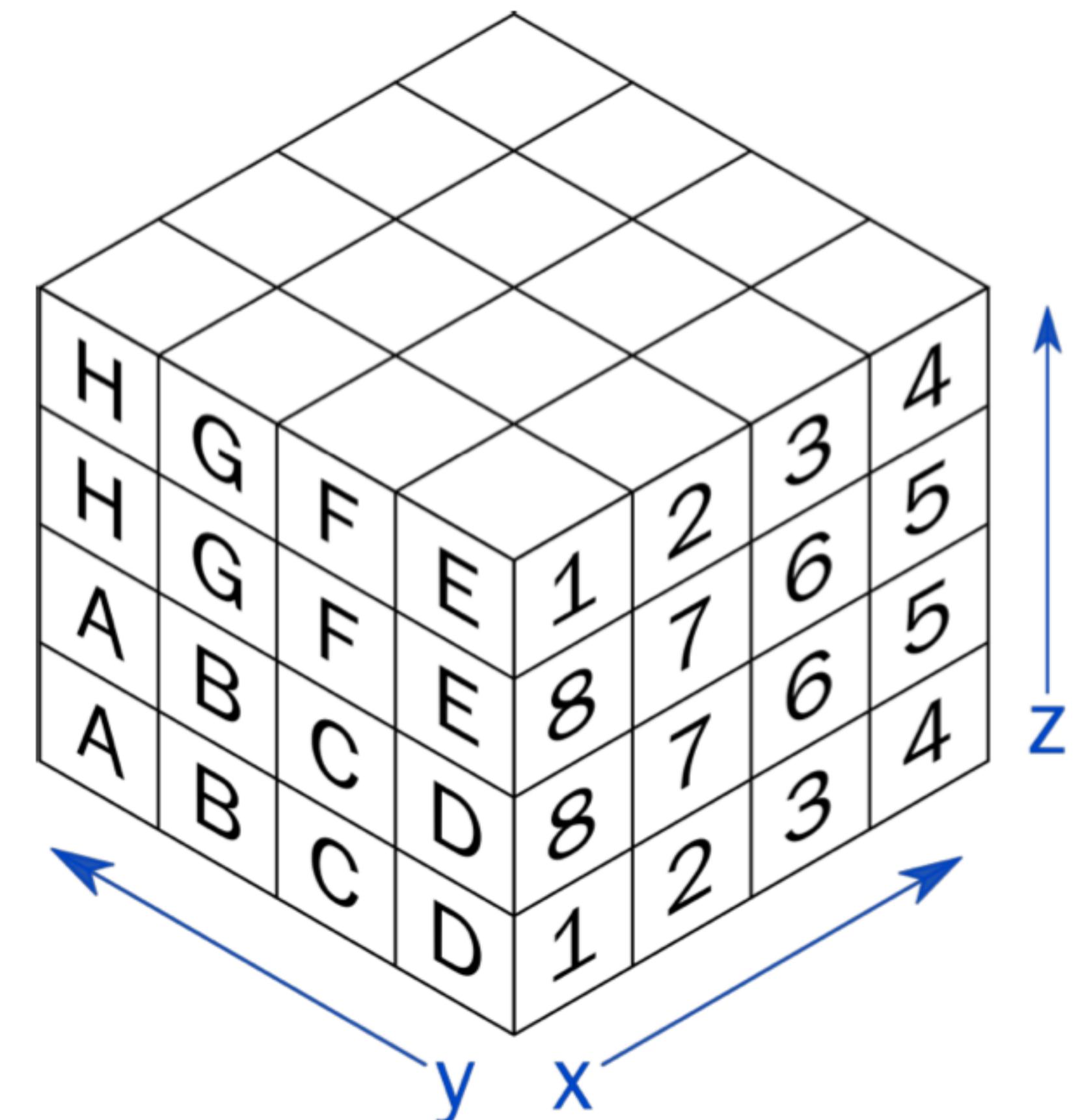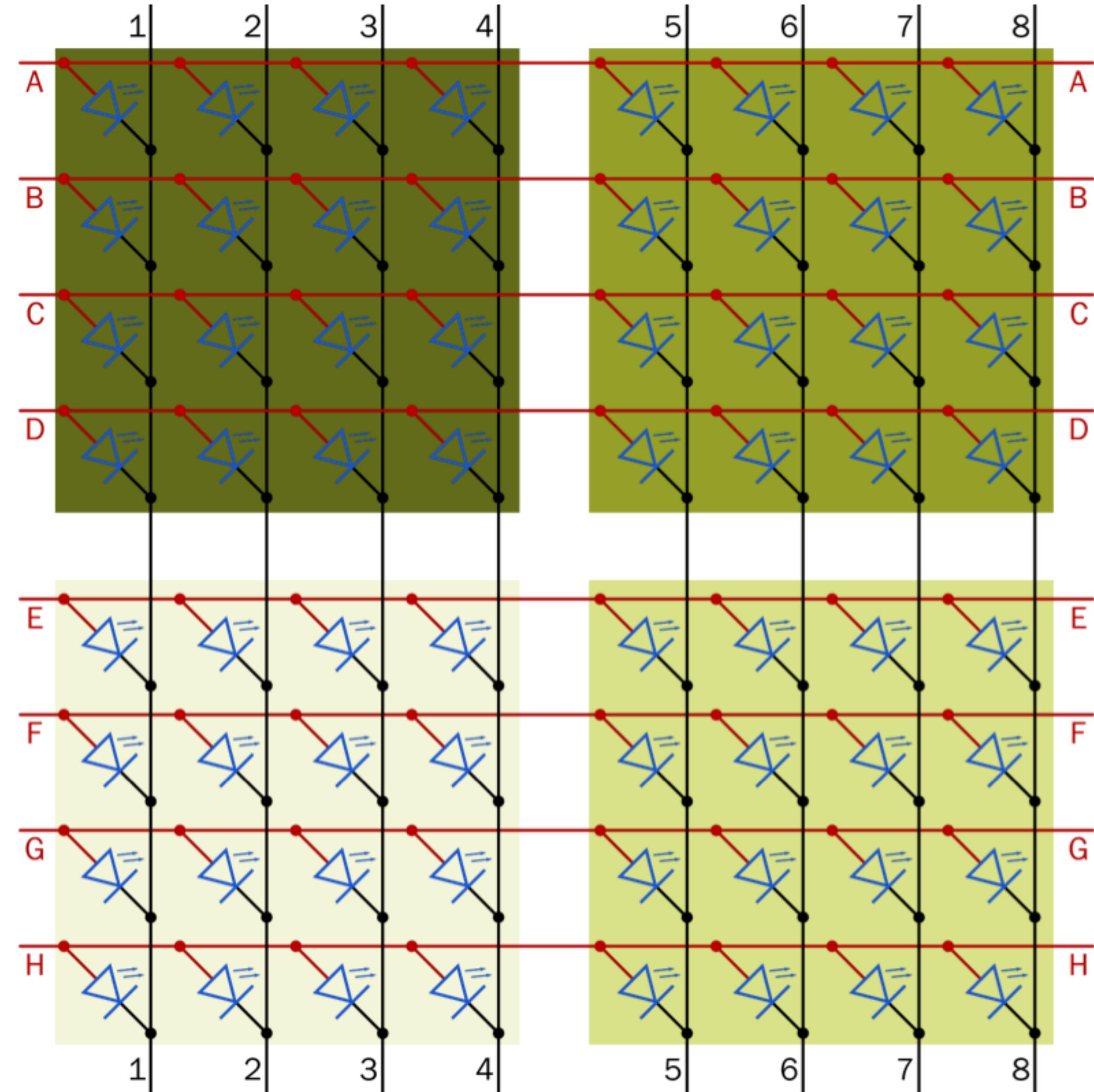


# Mapping between 2-D and 3-D

---

We want a function that  
maps

from 3D coordinates  
 $(x, y, z)$

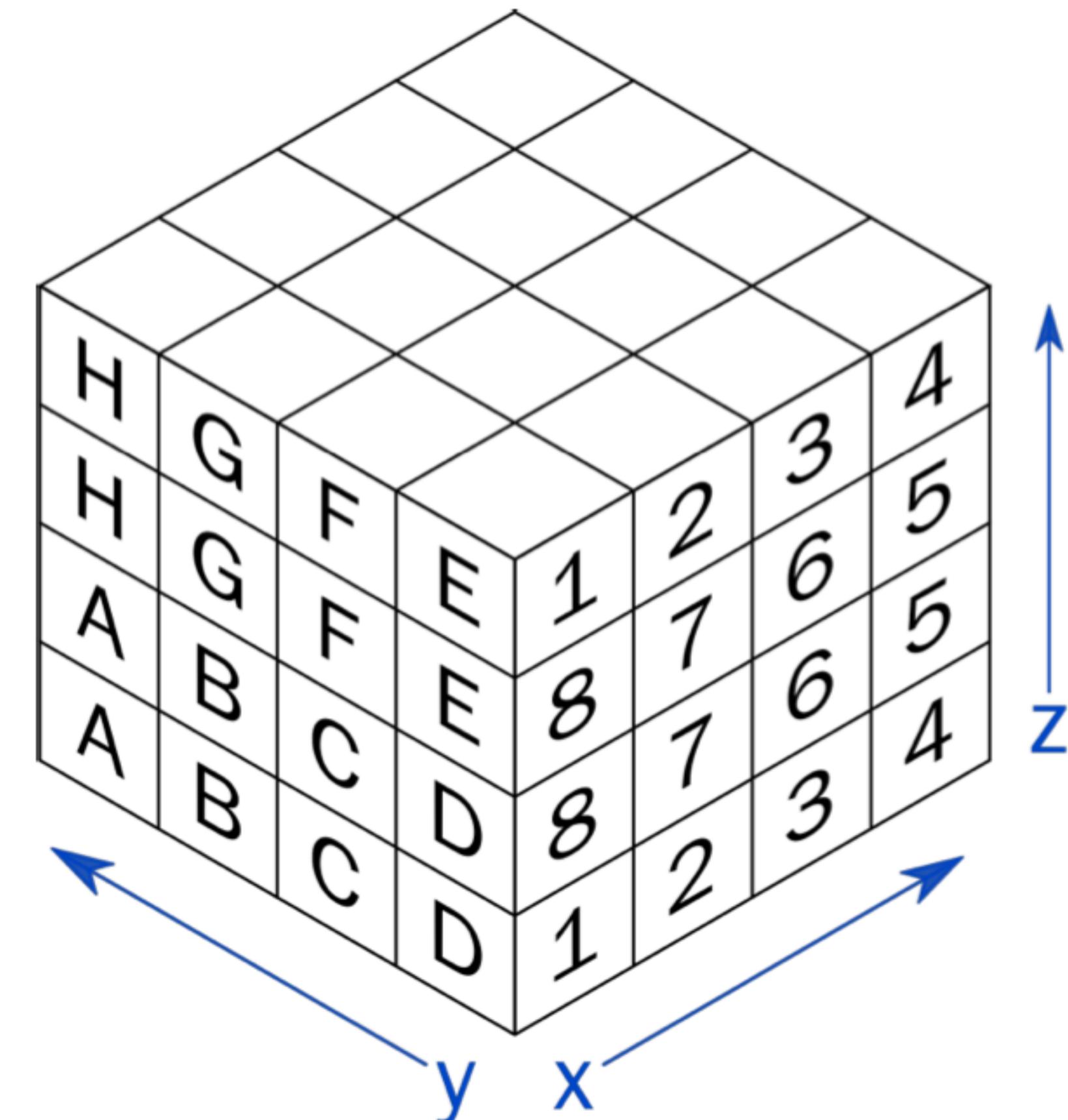
to anode/cathode pairs  
 $(a, c)$   
(e.g. “D6”)




# Mapping between 2-D and 3-D

---

**Anodes**

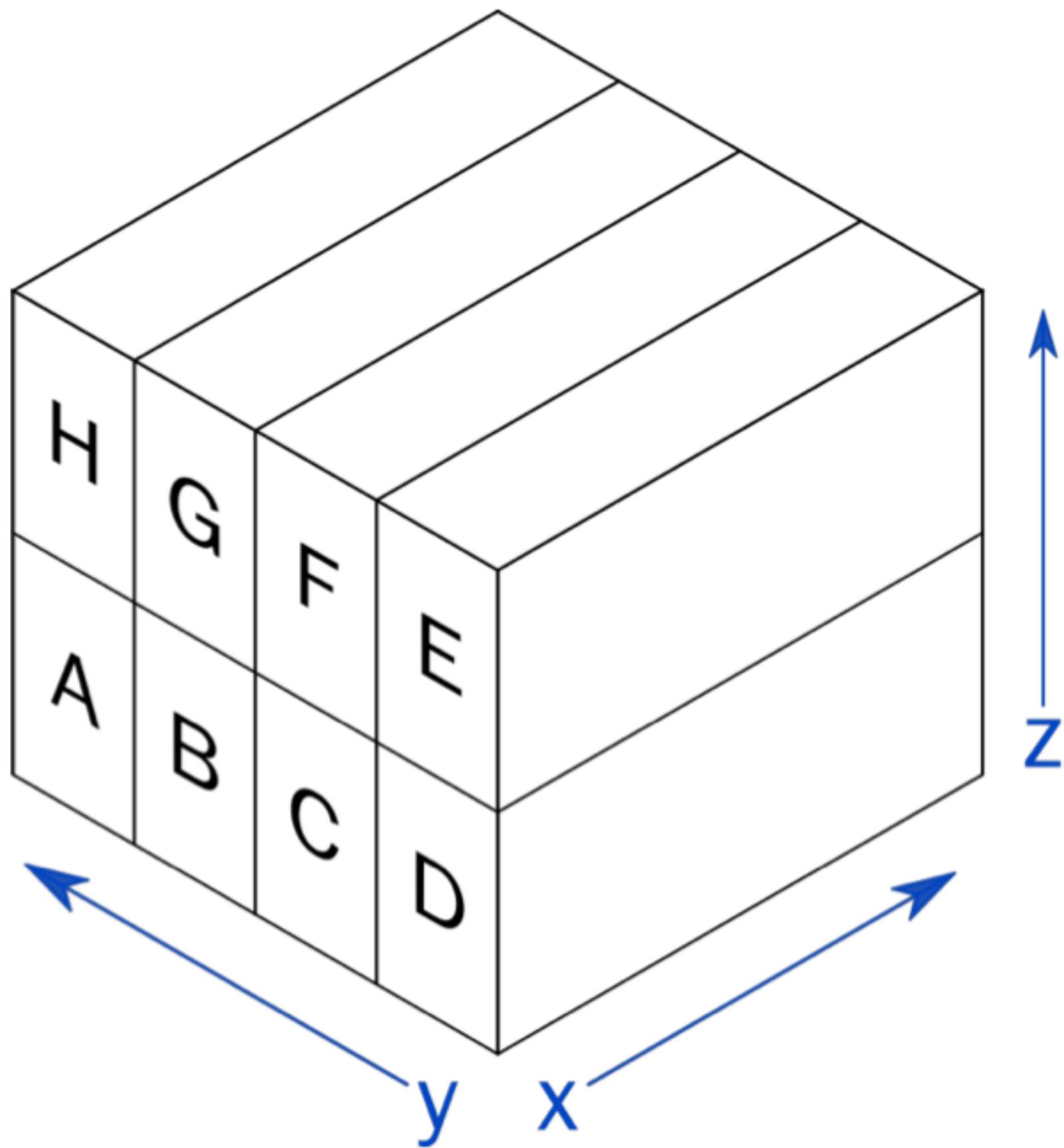


**Cathodes**

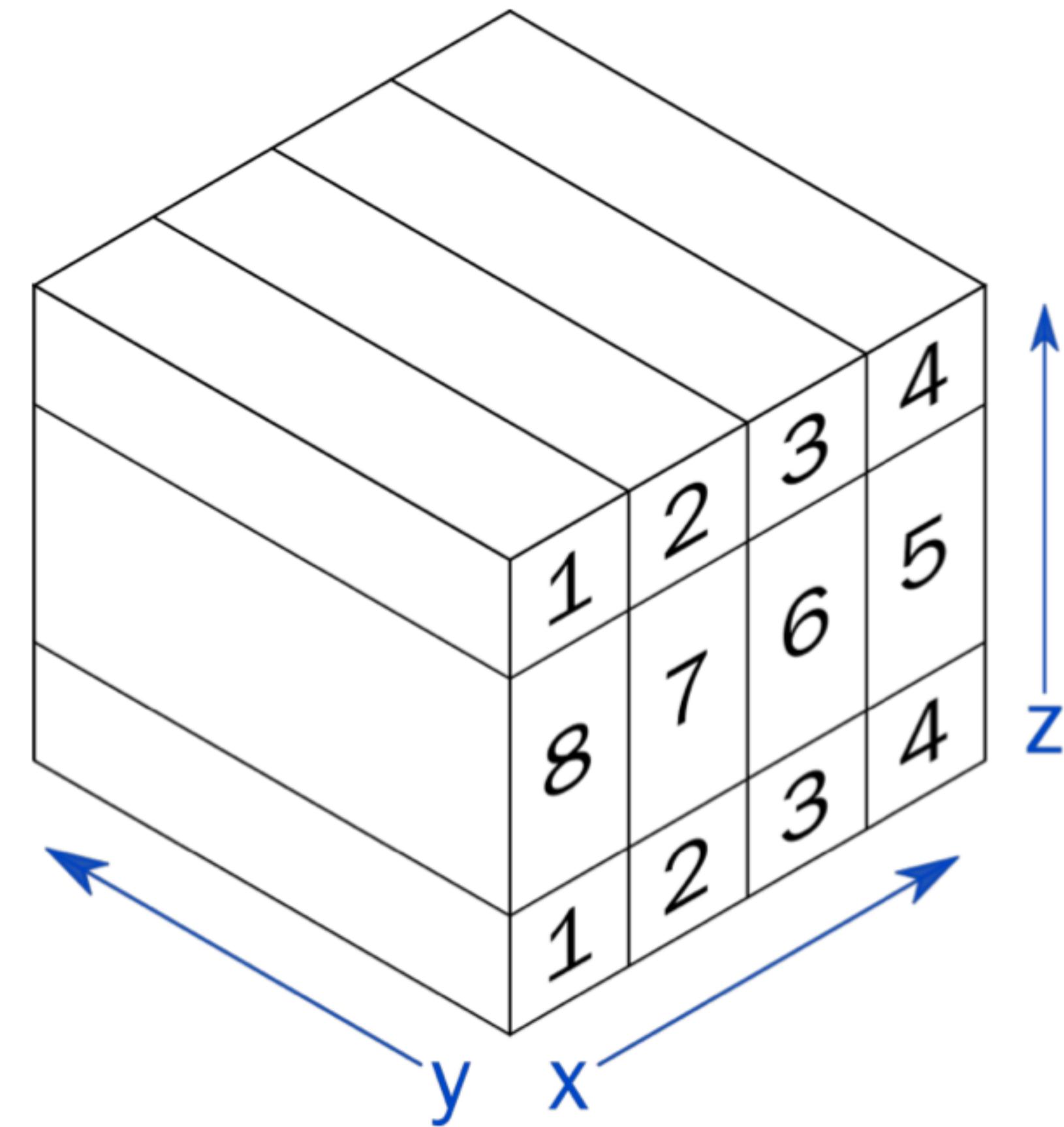

# Mapping between 2-D and 3-D

---

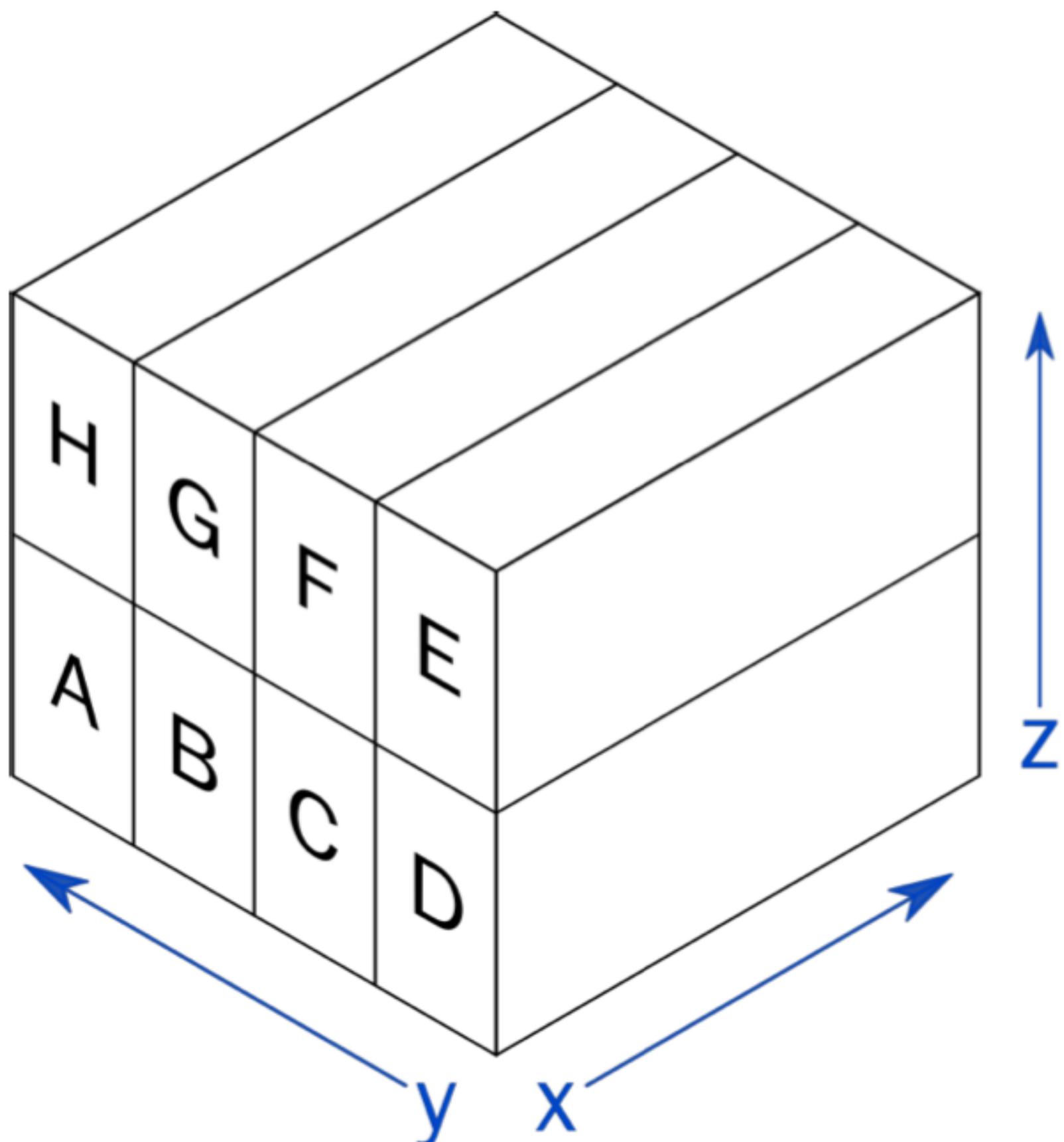

Operations we might consider using:

- **\*** (multiplication)
- **%** (modulo division)  $3 \% 2 == 1$
- **/** (integer division)  $3 / 2 == 1$
- **&** (bitwise and)
- **|** (bitwise or)
- **^** (bitwise xor)

# What do bitwise operations do?

---

- Bitwise operations apply to **each bit** in the binary representation of a number **individually**

Examples (in binary):



$$00110101 \mid 01100011 == 01110111$$
$$00110101 \& 01100011 == 00100001$$

00110101	00110101
<u>  </u>   <u>01100011</u>	<u>  </u> & <u>01100011</u>
01110111	00100001
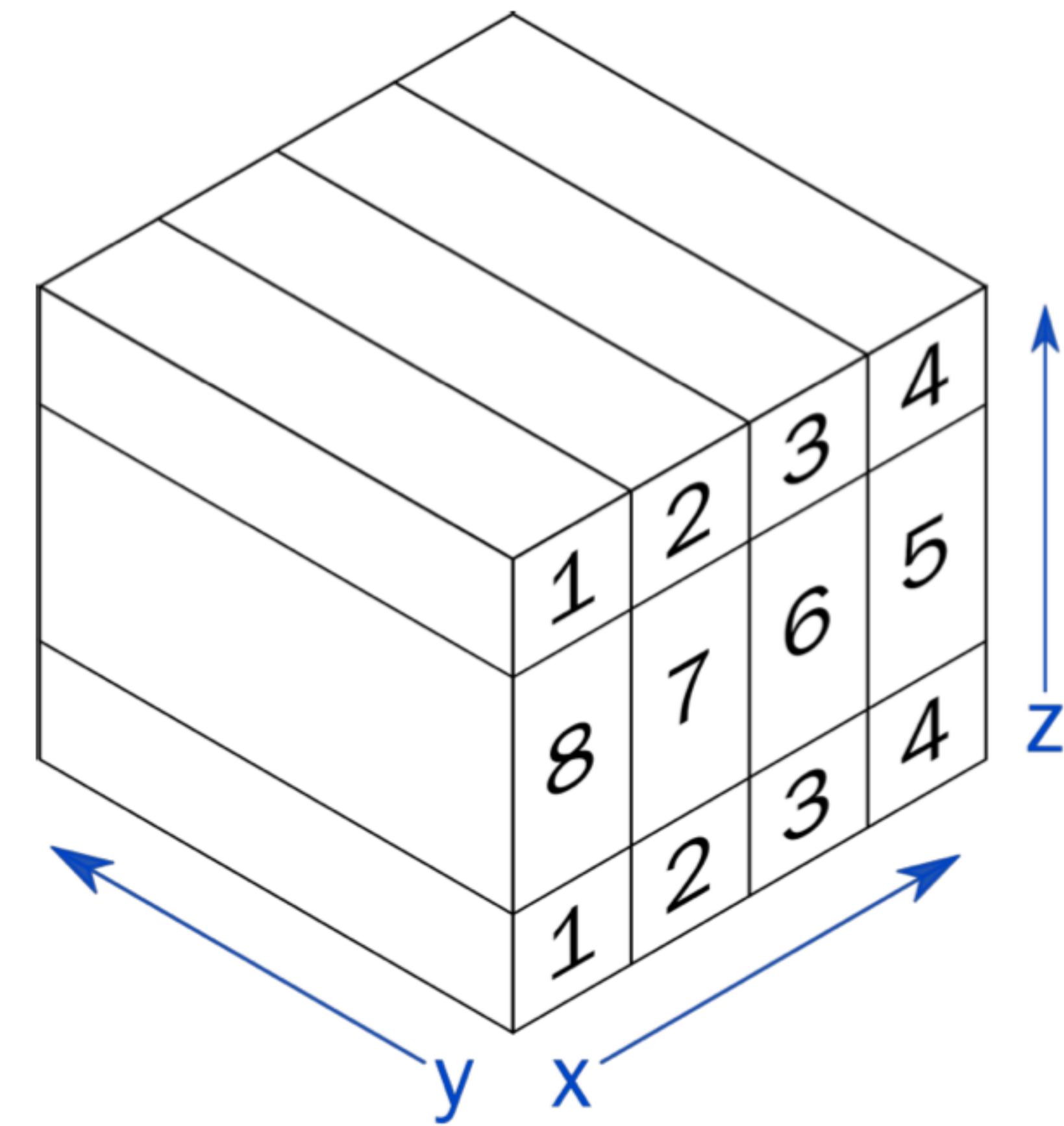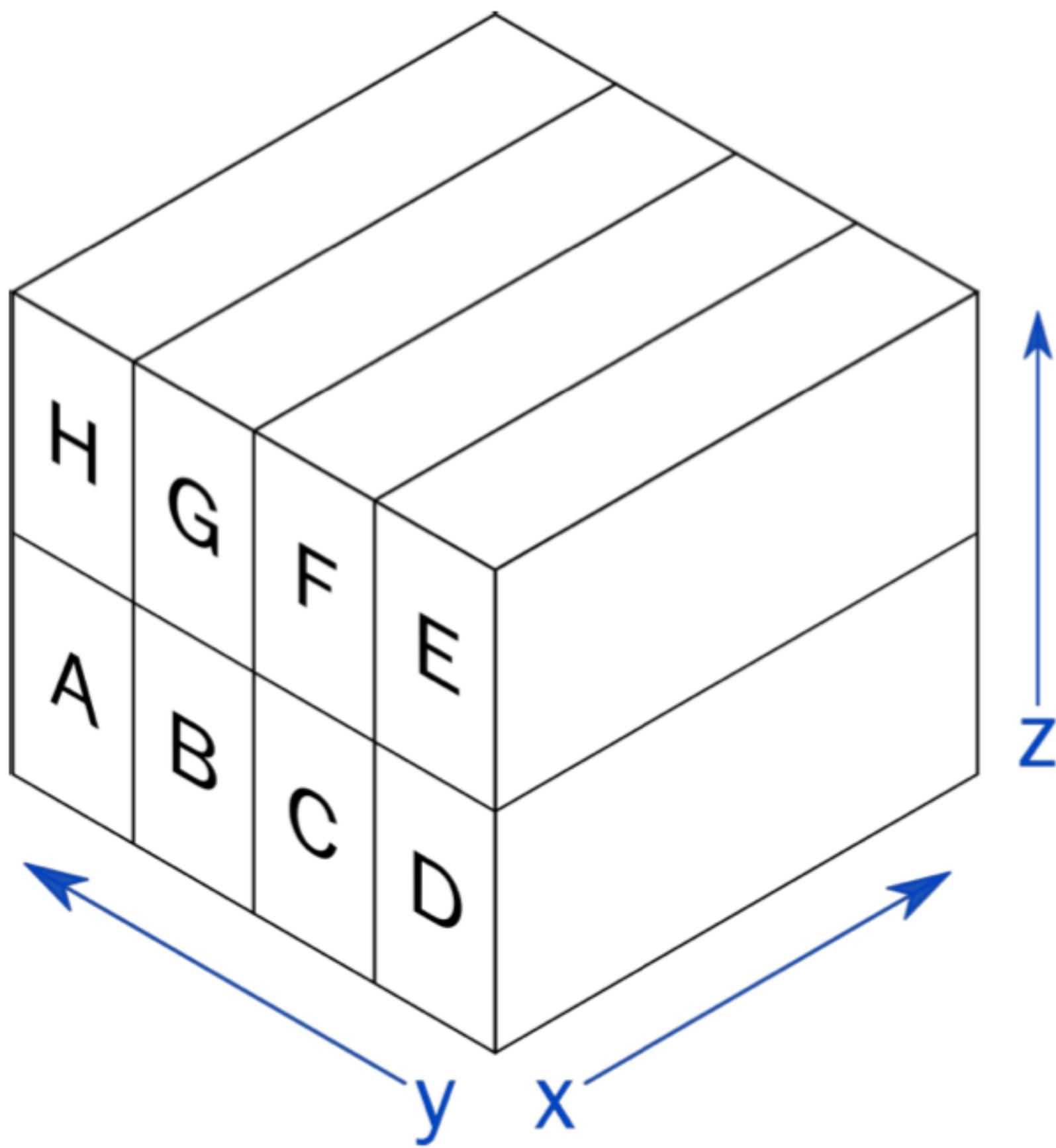
# Making the mapping function easier

---

You can reorder the anodes/cathodes however you like.  
Would a different ordering make the relationship simpler?



# Building an LED cube: Key tips

---

## Plan ahead

- Read the entire handout first

## Test often, fail quickly



- Mistakes are easier to fix earlier than later
- It helps you avoid making the same mistake twice

## Optimize repetitive tasks

- Think of procedures to make tasks easier
- Use tools effectively—you only have two hands
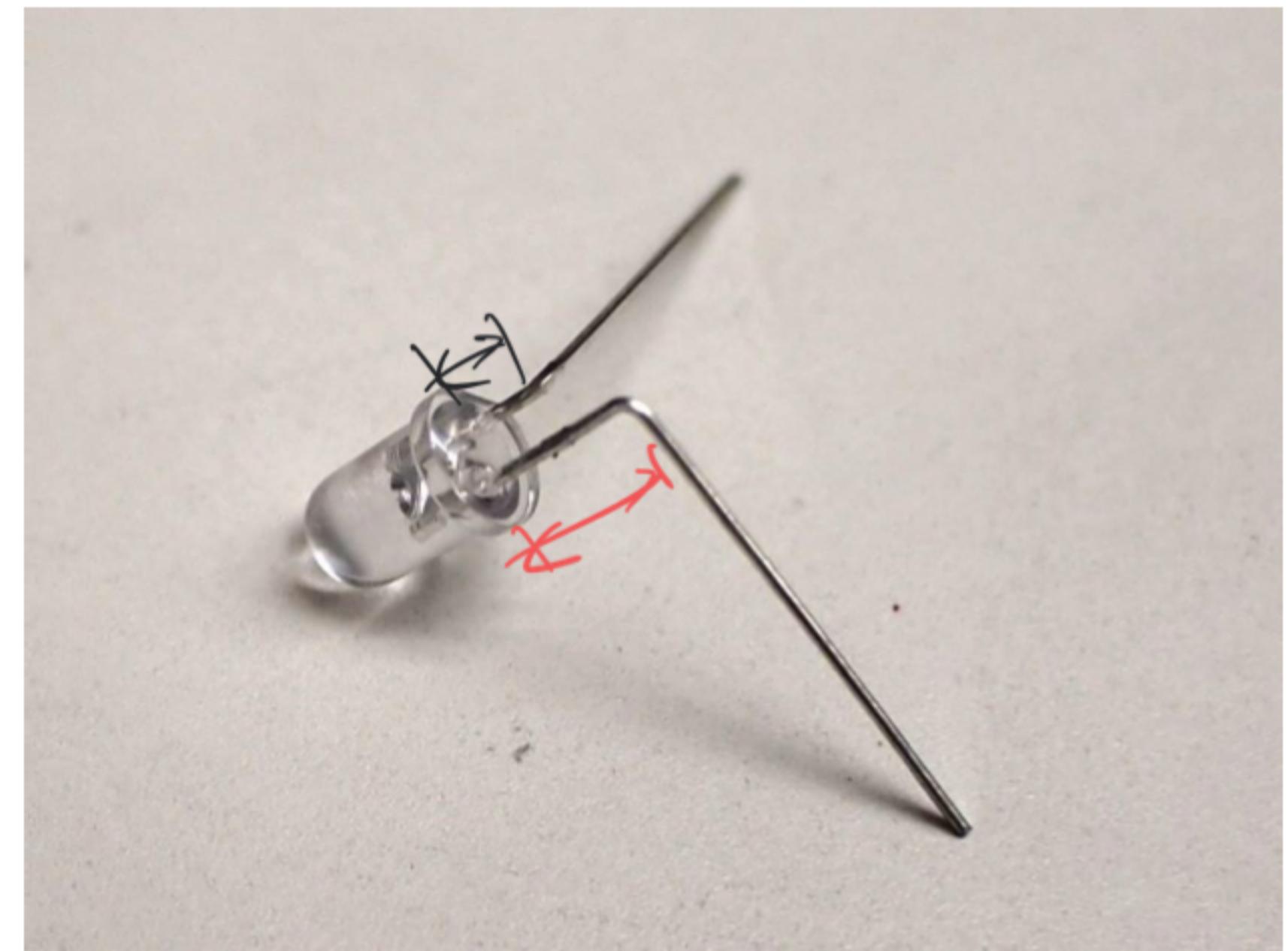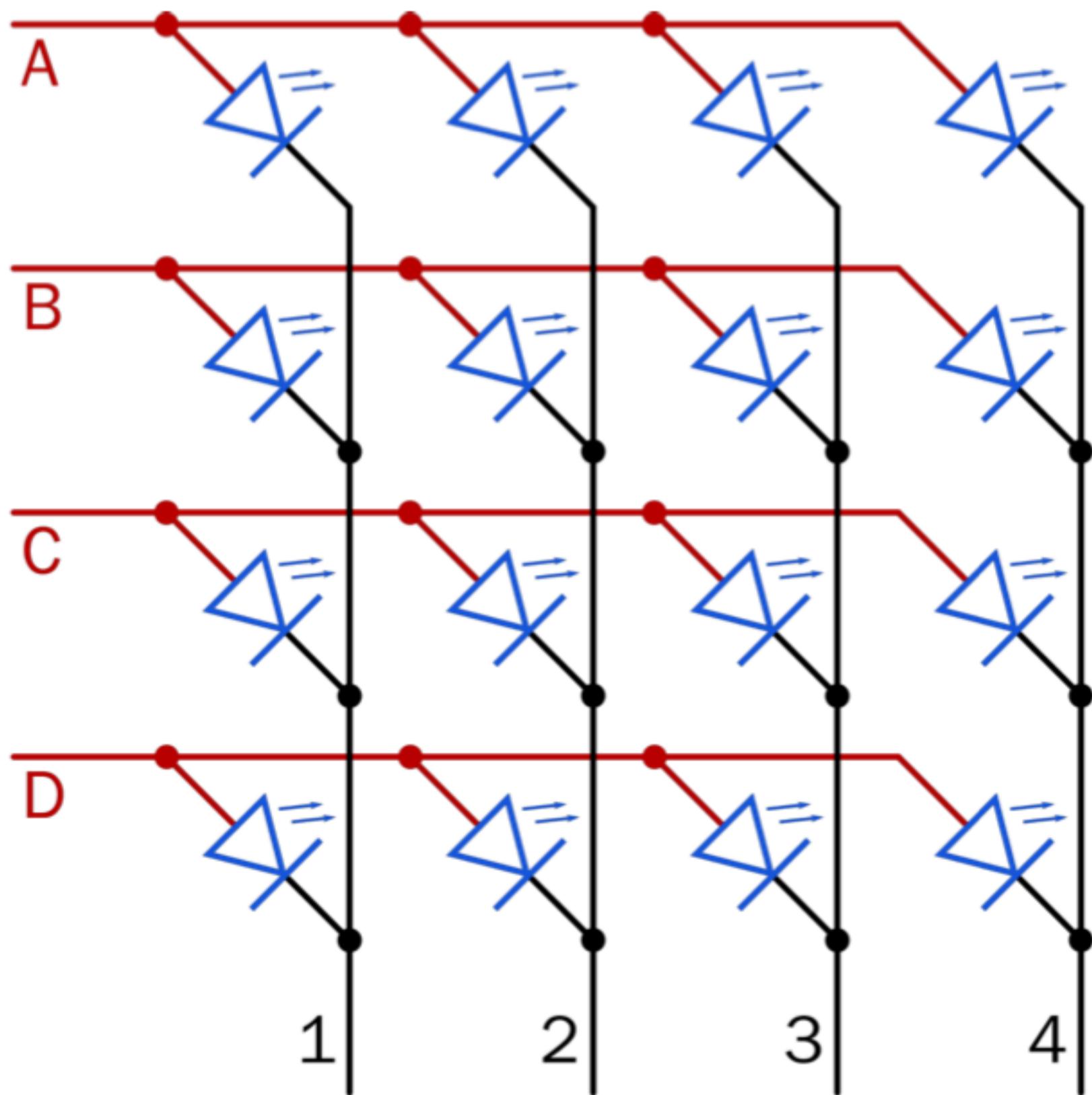
# Step 1: Build the arrays



Bend the anodes and cathodes at different heights, so they don't touch. *Use pliers, not your fingers.*


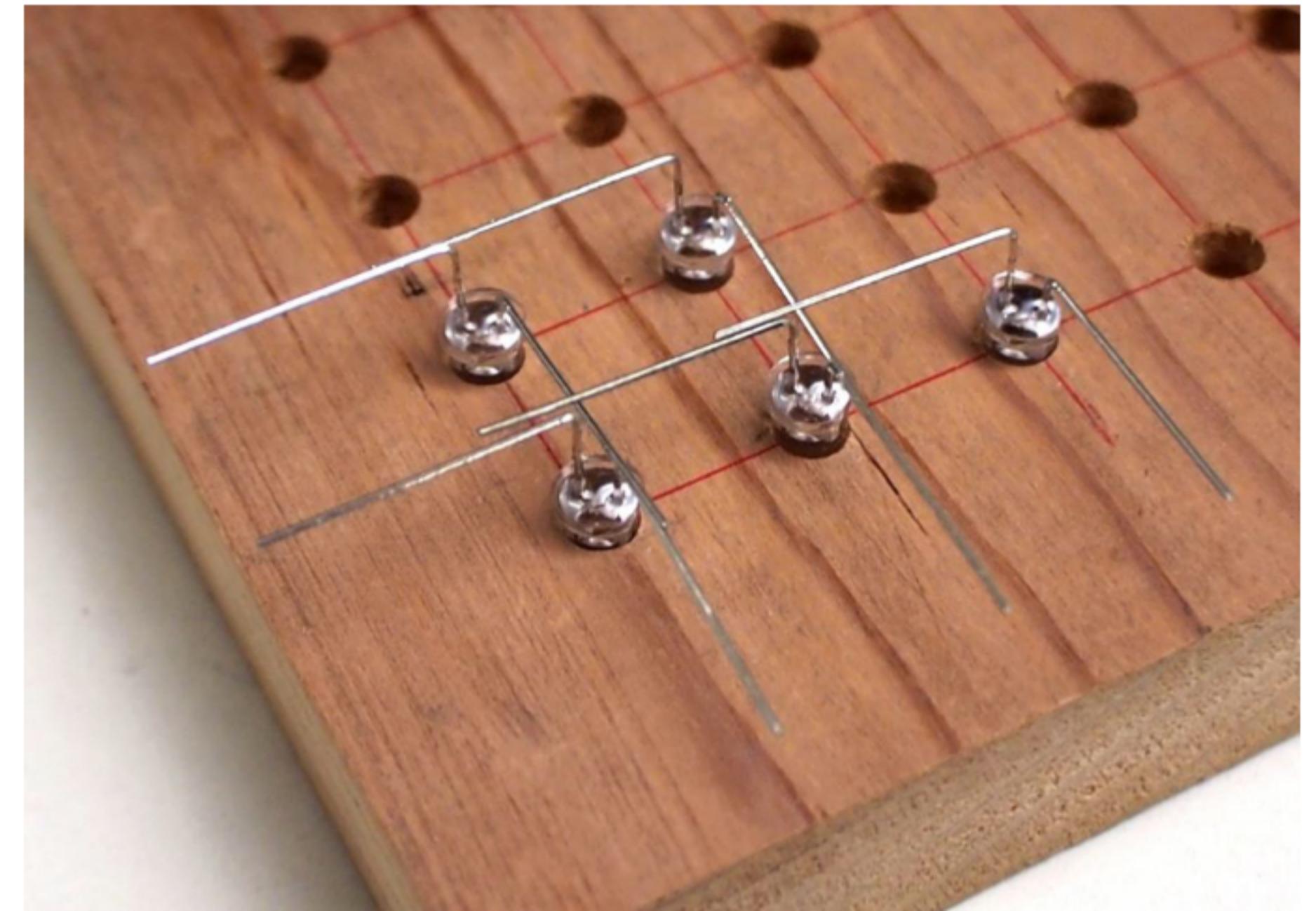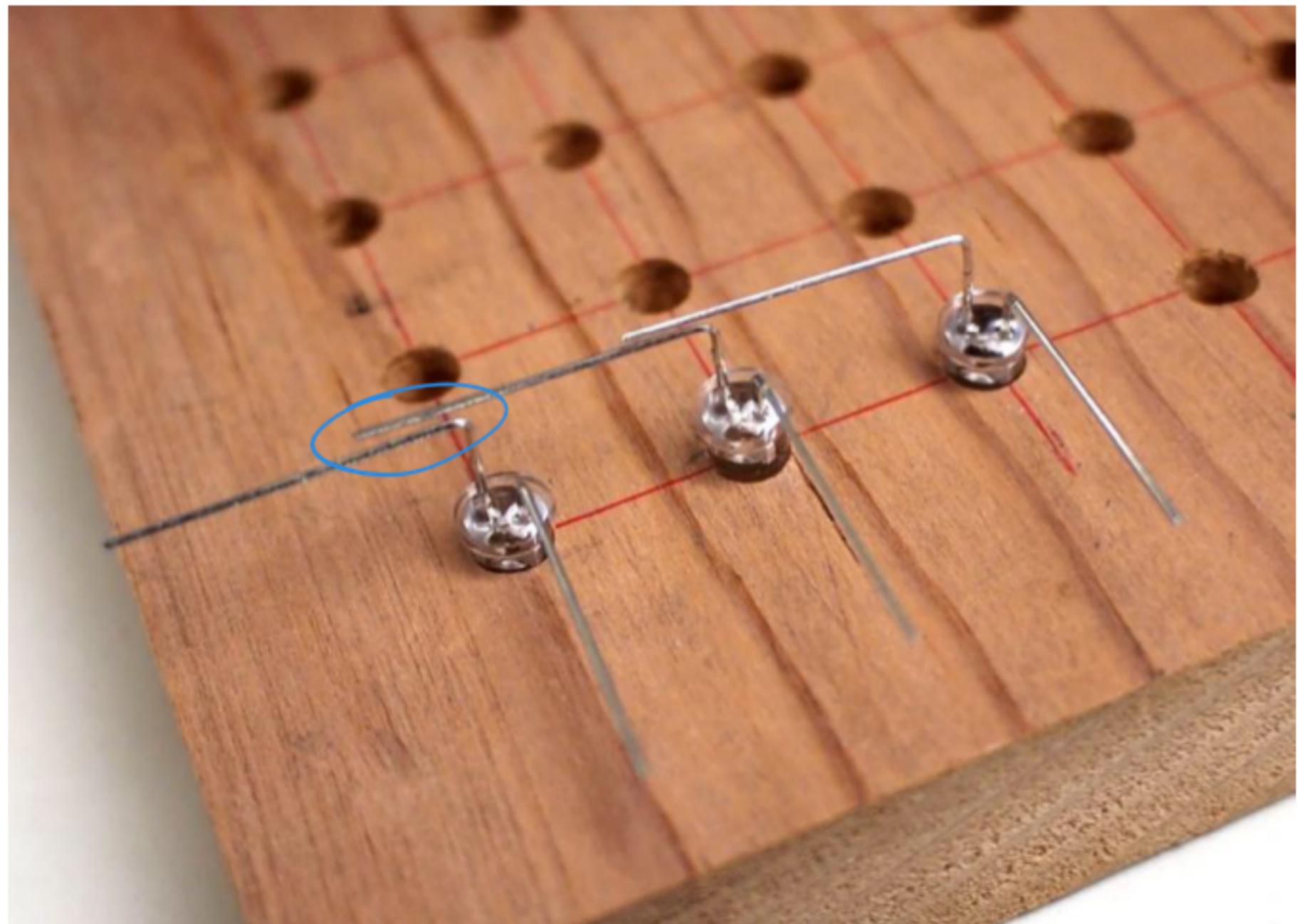
# Step 1: Build the arrays


---

Jigs will help you keep the LEDs in place.



# Step 1: Build the arrays


---

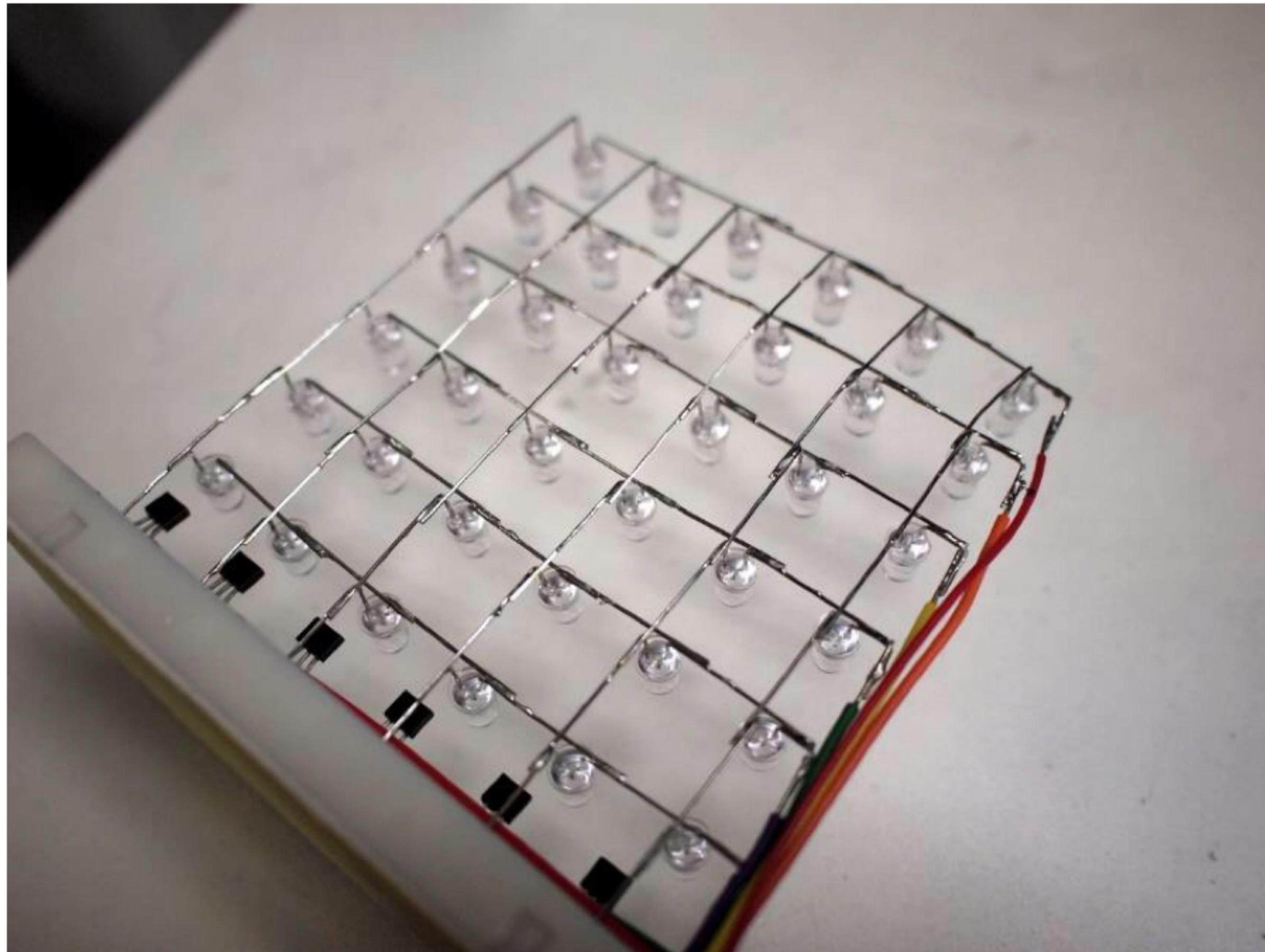

Test that the LEDs light up as you'd expect!

# Step 2: Connect the arrays together

---

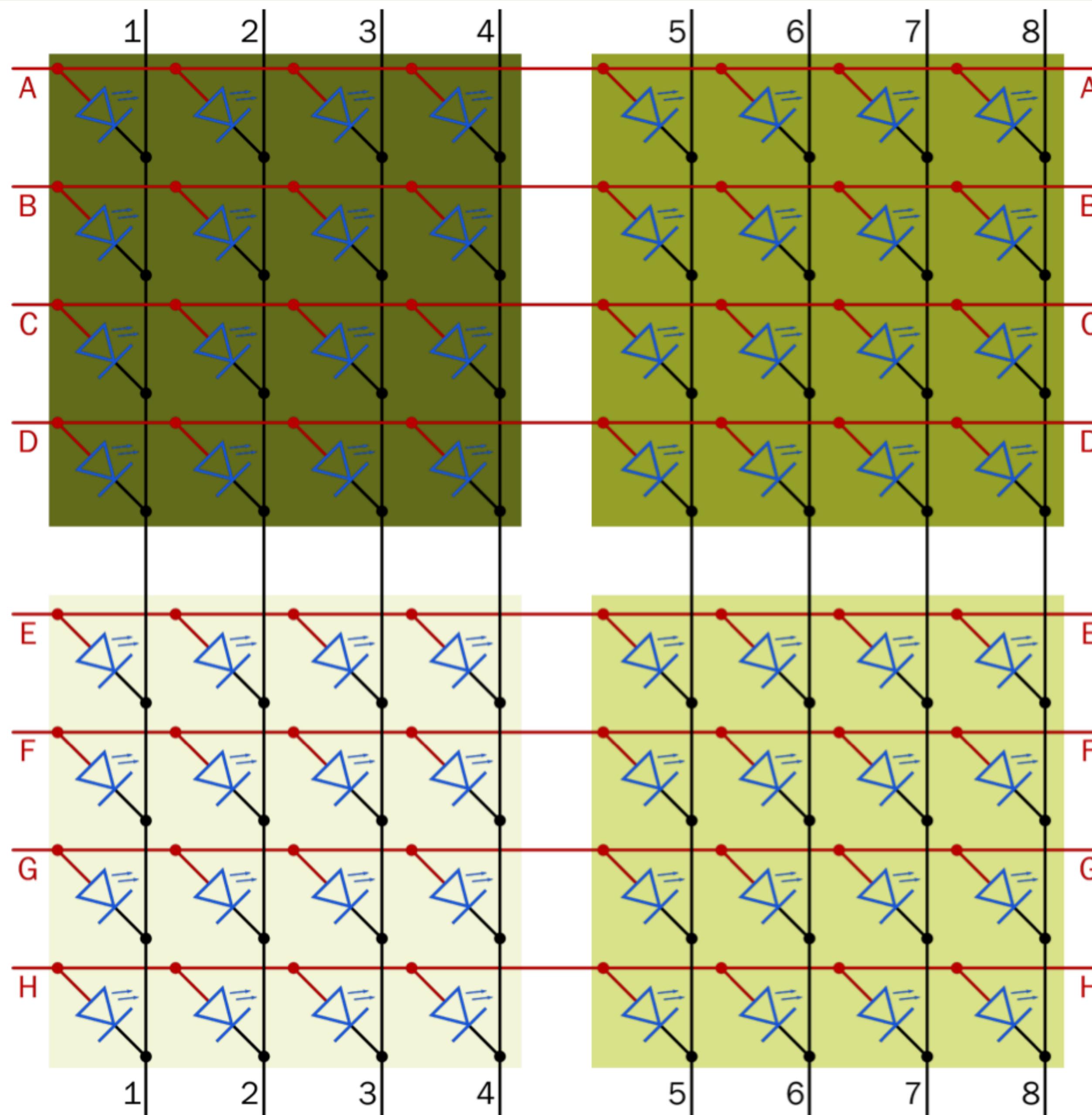

## Step 2: Connect the arrays together

---

