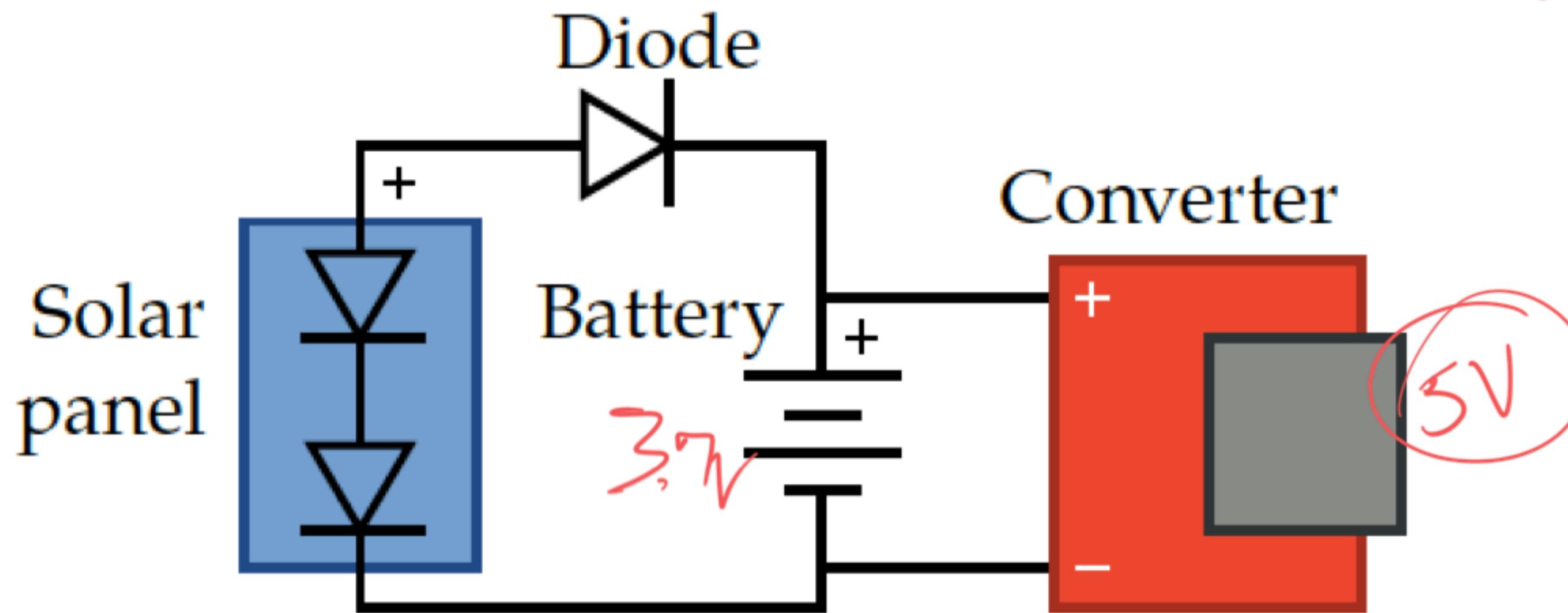

E40M

Charge, Current, Voltage and Electrical Circuits

Reading - Chpt 1
Course reader

Understanding the Solar Charger – Lab Project #1

Just in time learning



We need to understand how:

1. Current, voltage and power behave in circuits
2. Electrical devices constrain current and voltage
3. Diodes including solar cells work
4. Voltage converter works (later in the quarter). ↗

next
several
lectures


What Does It Do?

- Takes energy from sun light
- Stores it 
- Provides that energy later
 - To charge your cellphone
 - Create reading light, flashlight





How does it do that?

How Our Solar Charger Works

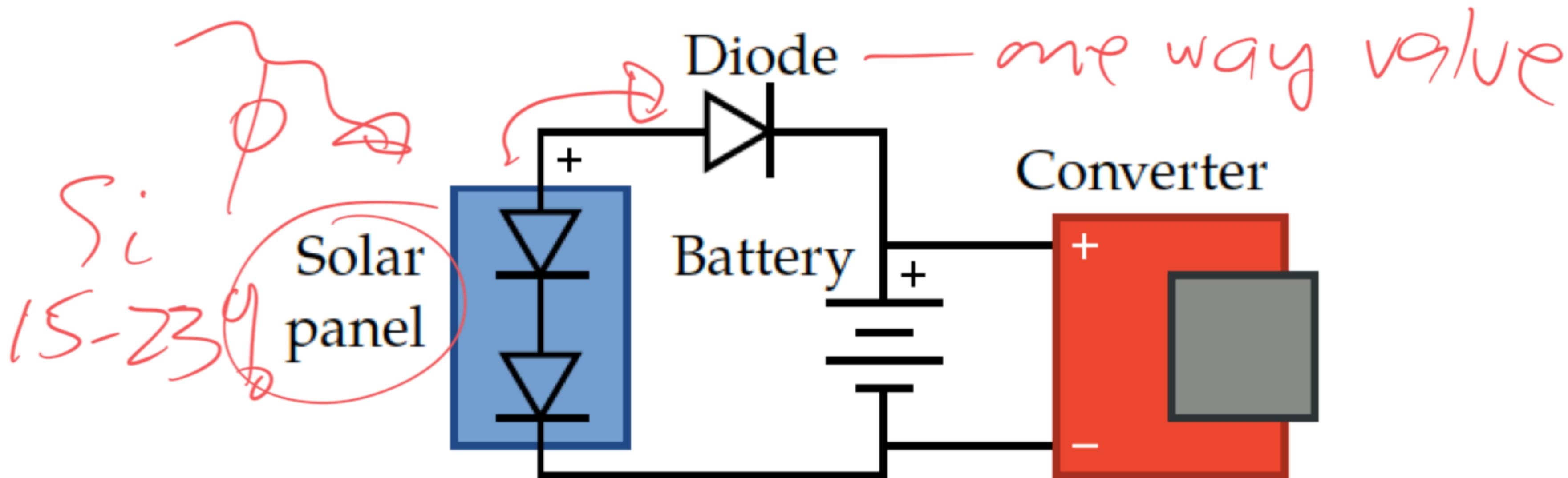




- Converts some energy from sunlight into an electrical signal
- That **electrical signal** connects to a rechargeable battery
 - So energy flows from solar cell to battery
- Another electrical signal connects the battery to the USB port
 - So energy can flow to the USB, and charge your phone
- So we need to understand electrical signals

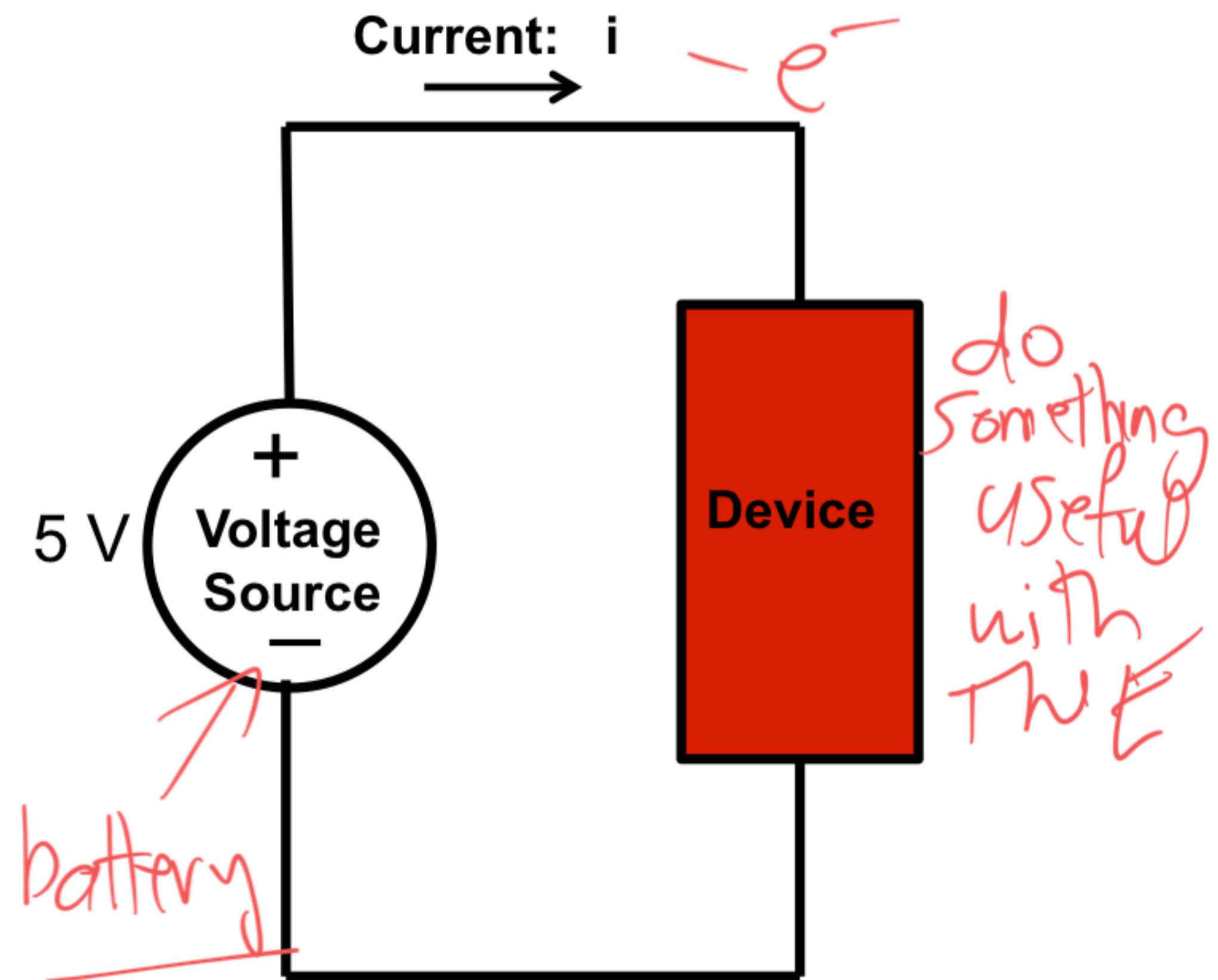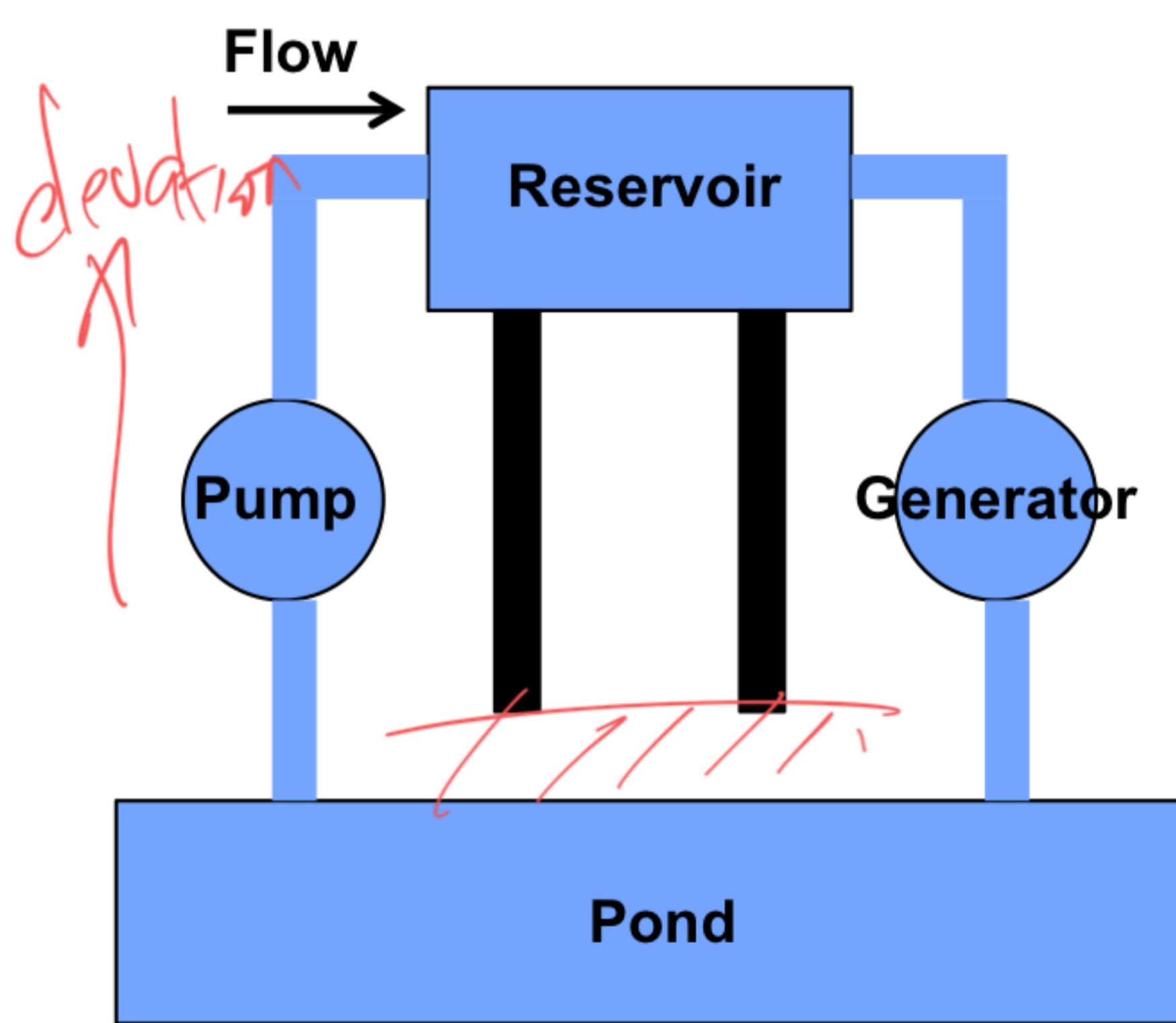Fluidic “Circuits” \approx Electrical Circuits



Electrical Charge
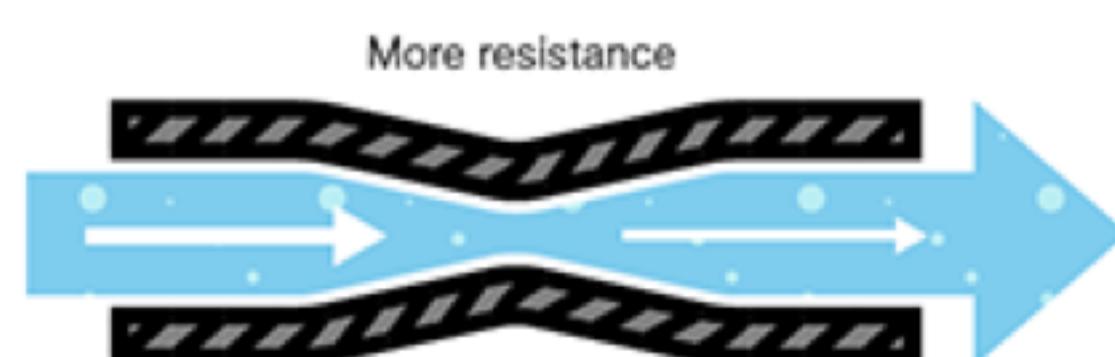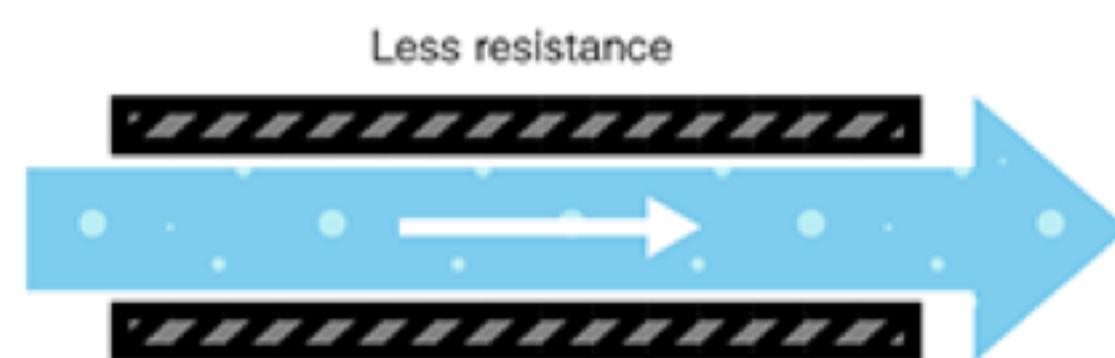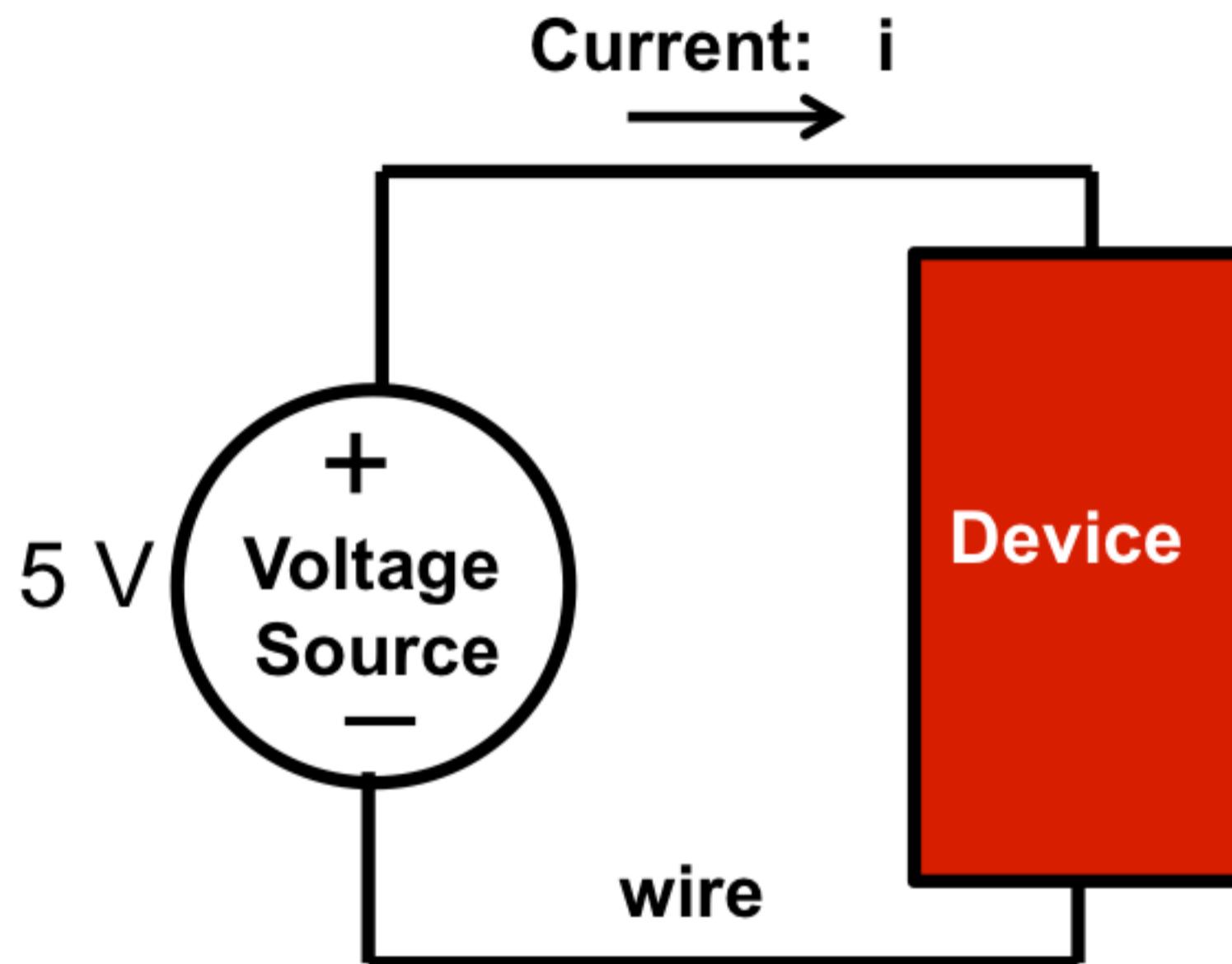
$$1 \text{ coul} = 6.25 \times 10^{18} e^-$$



- In electrical systems current is carried by charges, usually electrons
- Charge is measured in **Coulombs**
 - 1 coulomb is a *lot* of charge
 - Each electron has a charge of -1.6×10^{-19} Coulombs
- Charge can flow (move) in a material that **conducts**
 - **wires, devices** (power is dissipated if they have resistance)
- Like magnets, opposite charges attract; like charges repel.



Material Conductivity

metal

conductors

Si Ge


semiconductors

glasses

insulators


10^{25}

Electrical Current

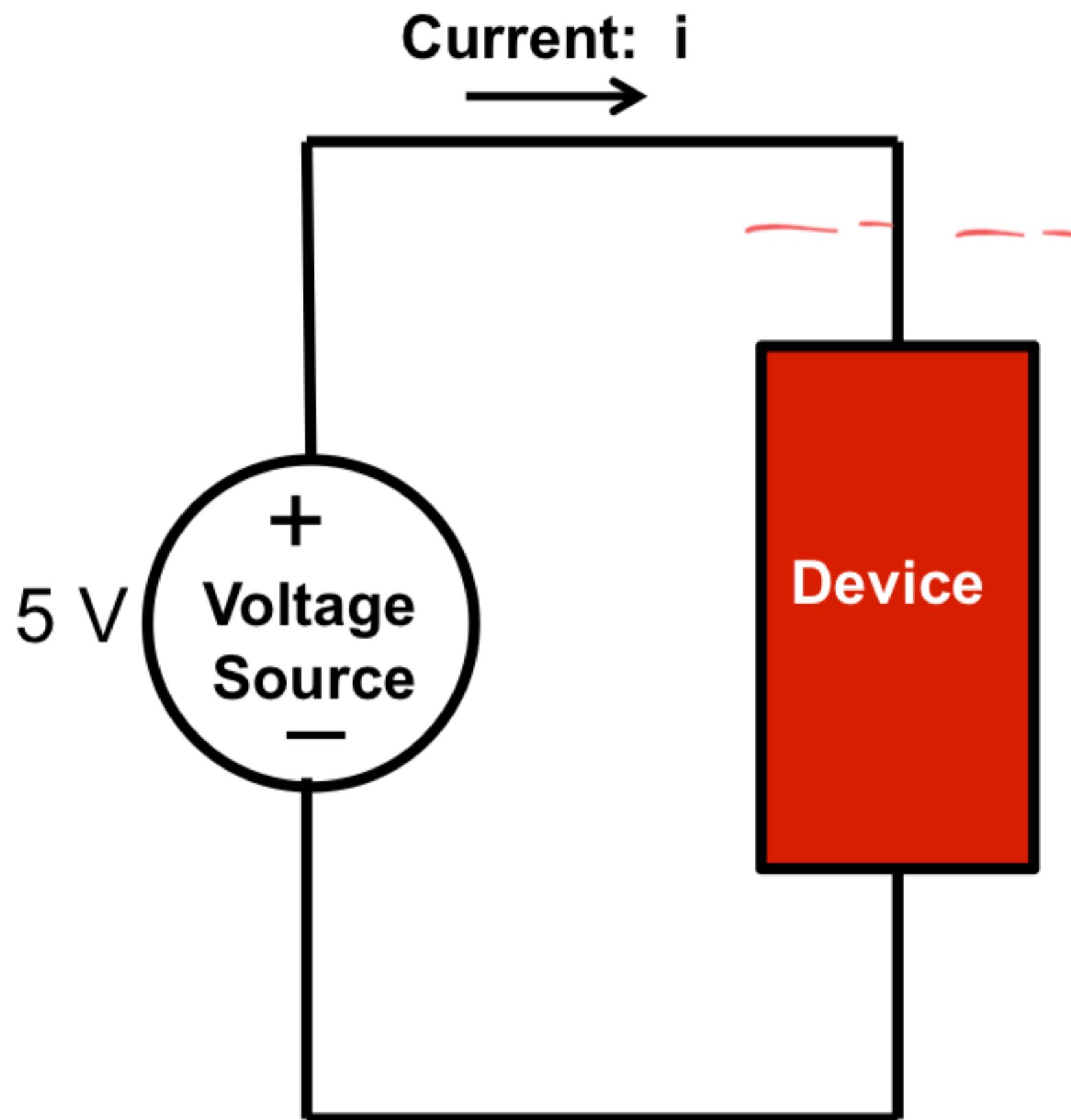

- Moving charge is called current
 - Current is the flow of charge per second
 - Past some measured point
- Its unit is the Ampere, usually called amps and abbreviated A
 - $1 \text{ A} = 1 \text{ Coulomb/sec} = 1 \text{ Cs}^{-1}$
 $6.25 \times 10^{18} \text{ e/sec}$
- The symbol for current is usually i

Electrical Current is Continuous

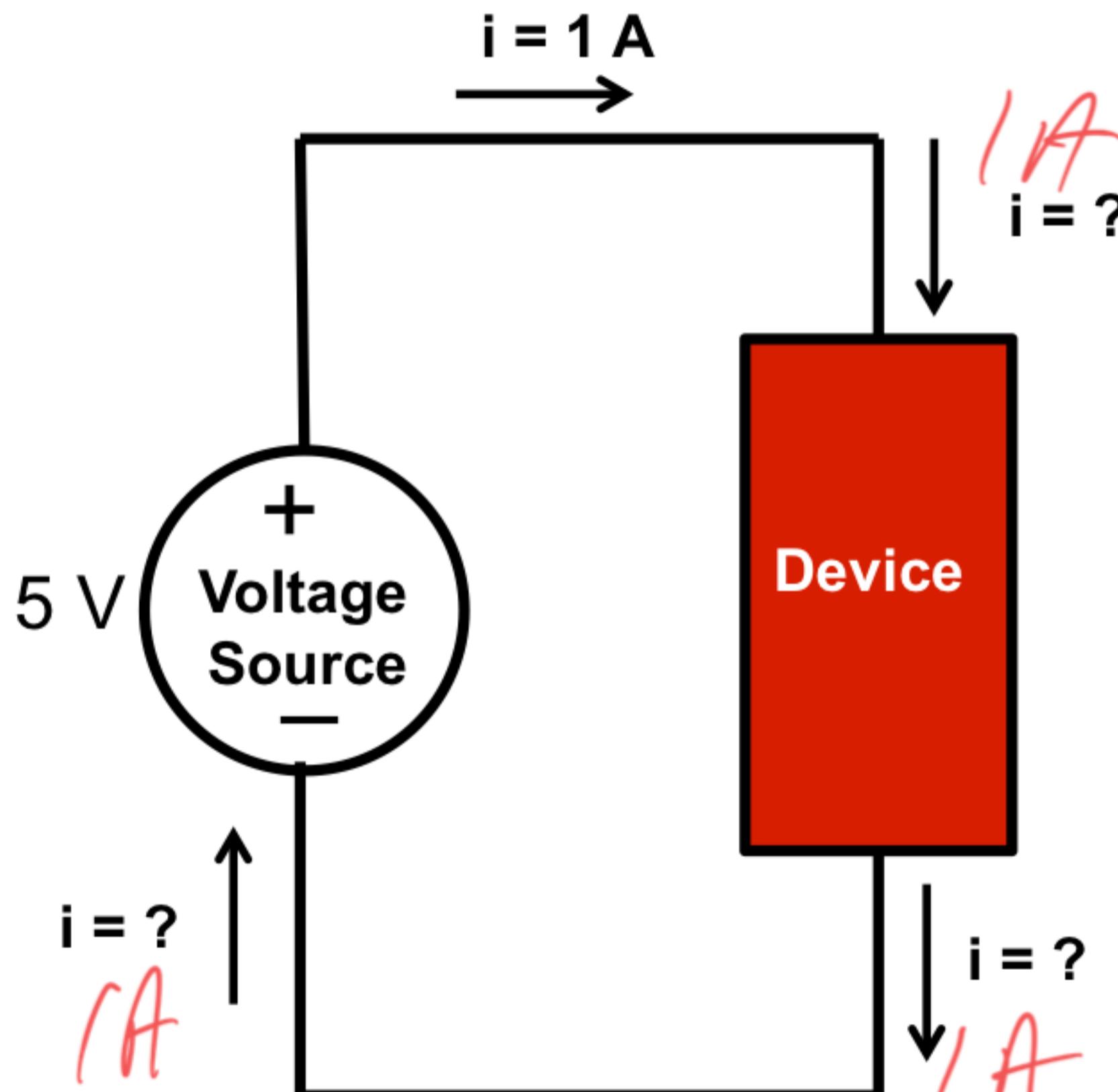


- The current flow in a wire remains the same along it, since there are no “leaks” of charge out of the wire
- The current flows in one terminal of the device and out the other
- The wires and the device are neutral (zero charge), even though current is flowing through them

FTI



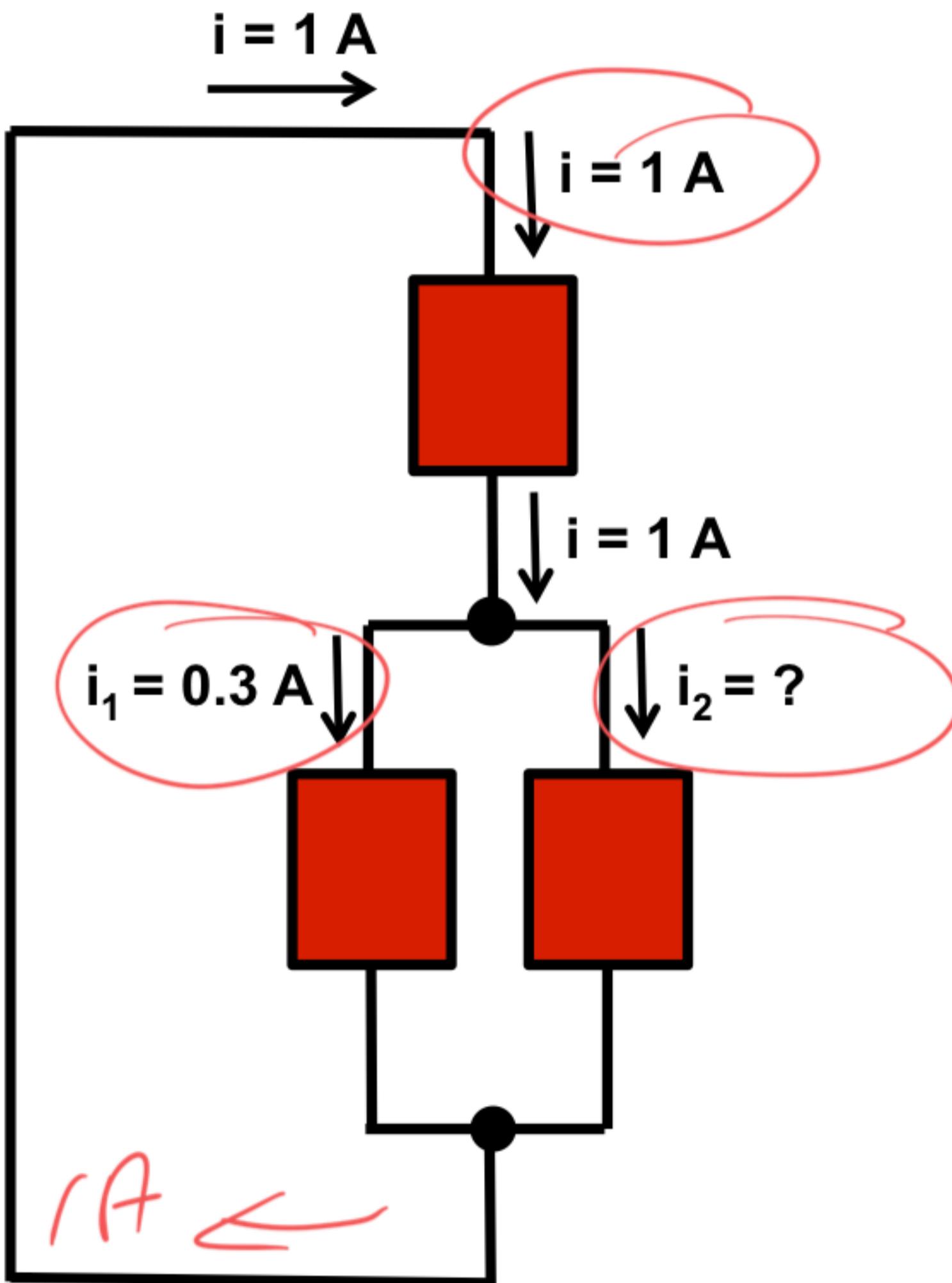
Circuits with Branches: Constraints on Currents (KCL)



- The black dot is an electrical connection between the wires
- What is the value of the current i_2 ?

$$i_1 + i_2 = 1 \text{ A}$$


If You Think of Charge as a Fluid

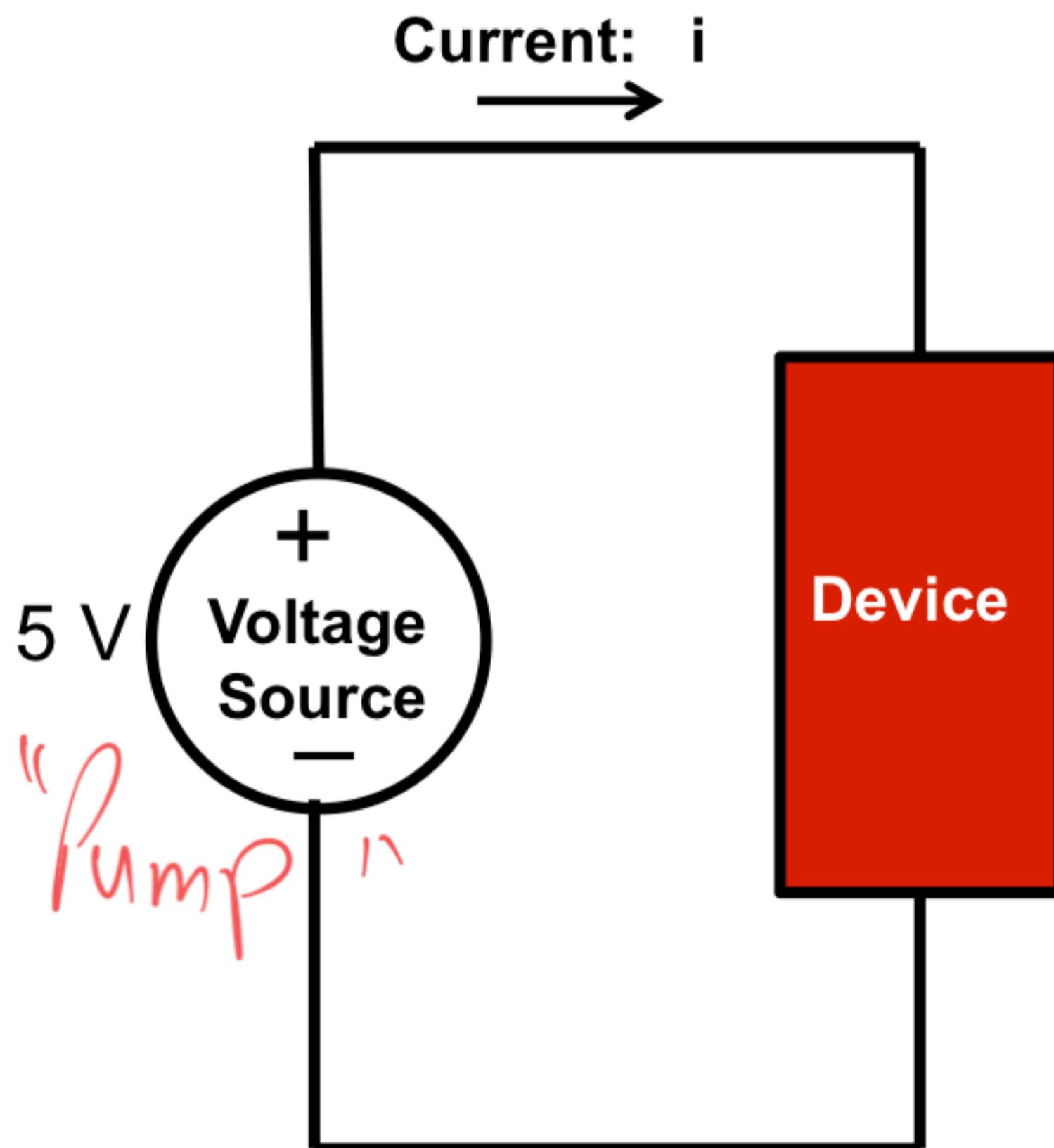

- Current is then fluid flow
- Current constraints are then about fluid conservation
 - The fluid in any object is constant
- But we know that a fluid doesn't move unless it is pushed
 - What pushes charge to make it move?

A Voltage Source

Electrical Voltage

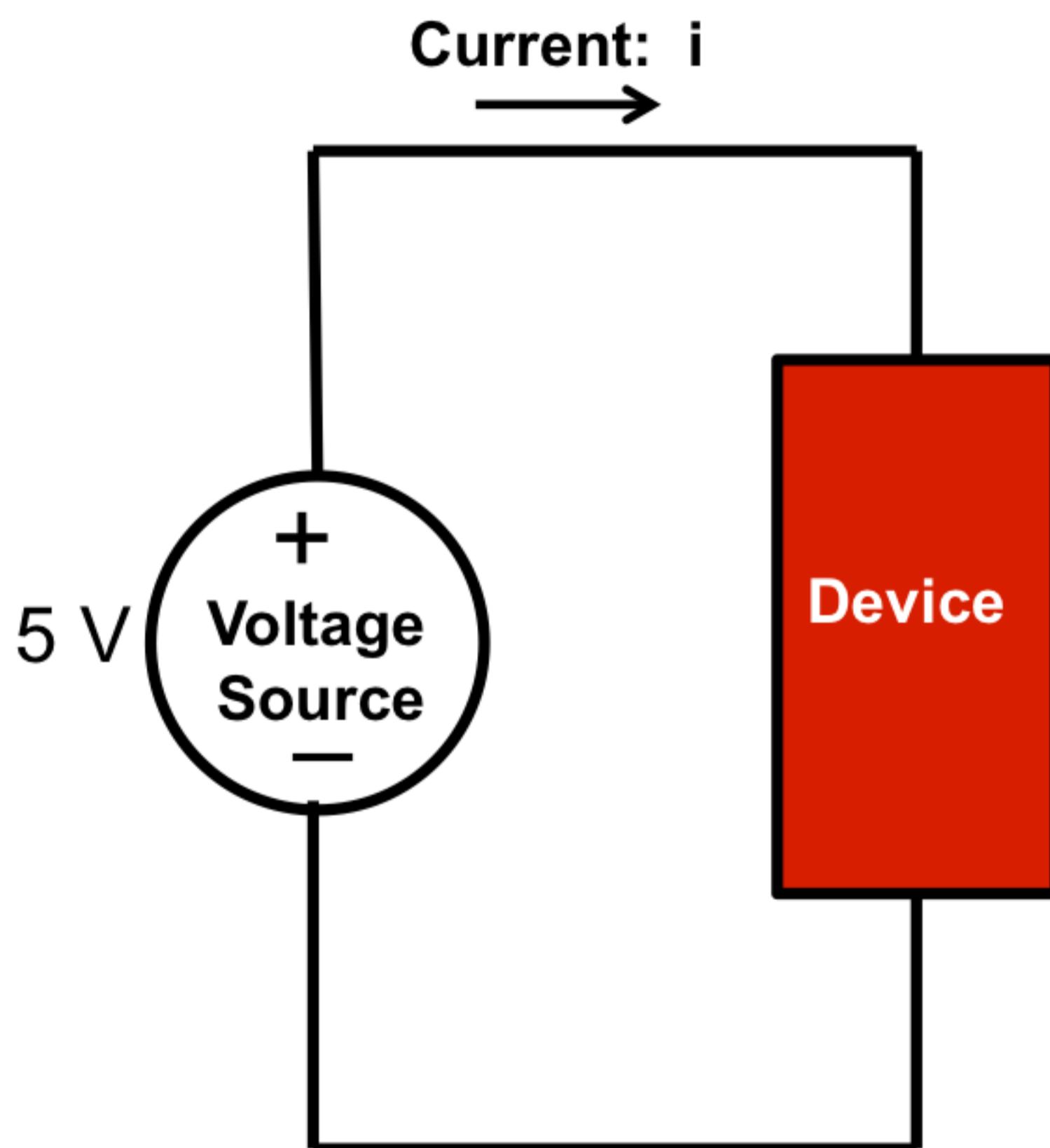


- **Voltage** is a measure of the potential energy per unit charge
 - It is measured in **Volts**
 - Which has the units of Joules per Coulomb.
- The charge on the higher energy side will move through an external path (a wire) to neutralize the negative charge on the other side of the device.
 - This causes the charge to flow in the wire, as well as through the device.

What is a Battery?

- It is a chemical pump for electrons!
 - There is a pair of chemical reactions that pump electrons from anode to cathode
 - Actually, a battery absorbs electrons at the anode and creates electrons at cathode (with ions moving through the middle), but it has exactly the same effect
 - The battery voltage is the potential energy given to electrons as a result of this pump.
- The voltage of the battery depends on chemicals
 - Generally either 1.5 V, or multiples
 - Or around 3.5 V (lithium)



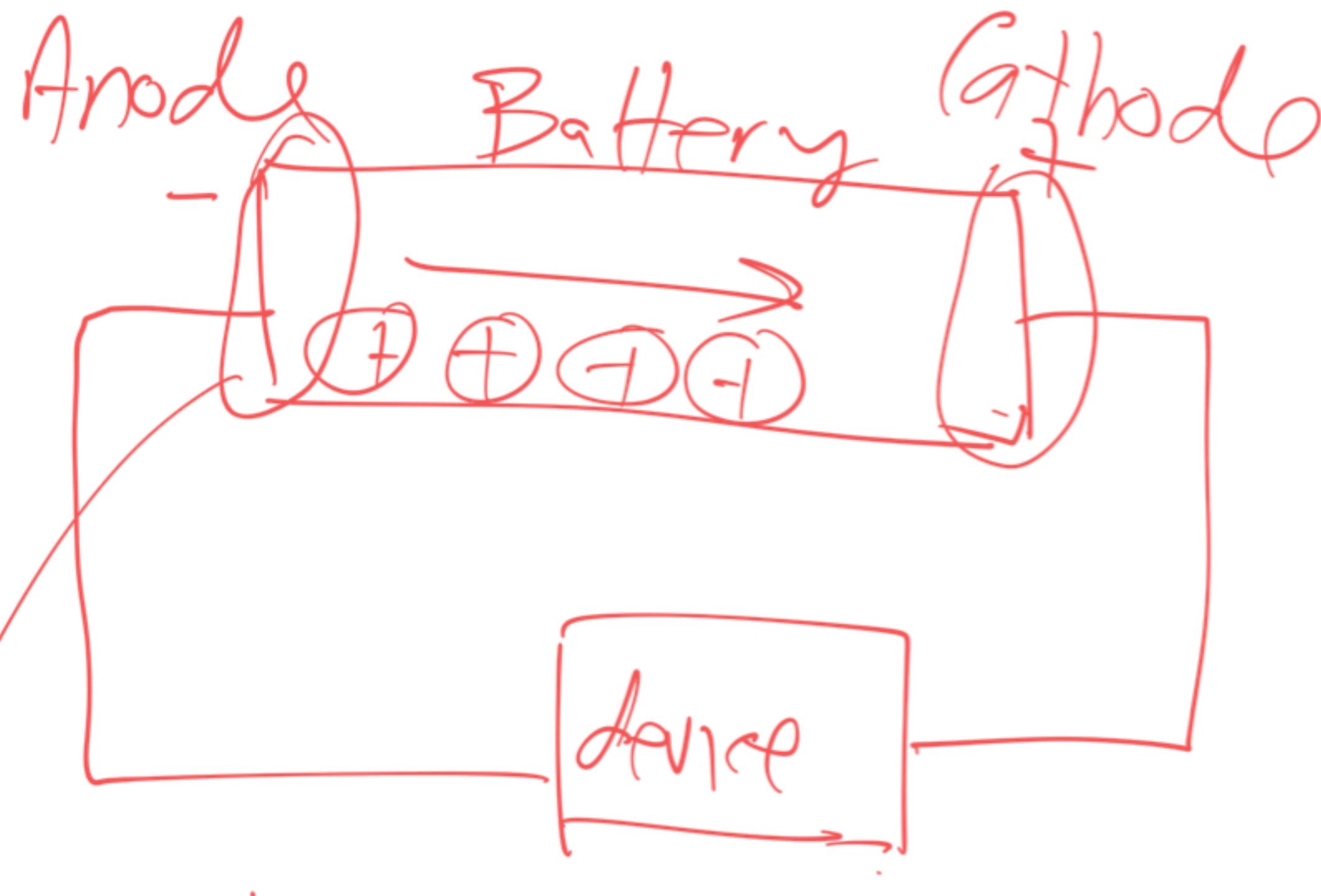


- oxidation reaction - loss of e^-
 - reduction reaction - gain of e^-

Chemical E \rightarrow Elec E


Energy and Power

Power

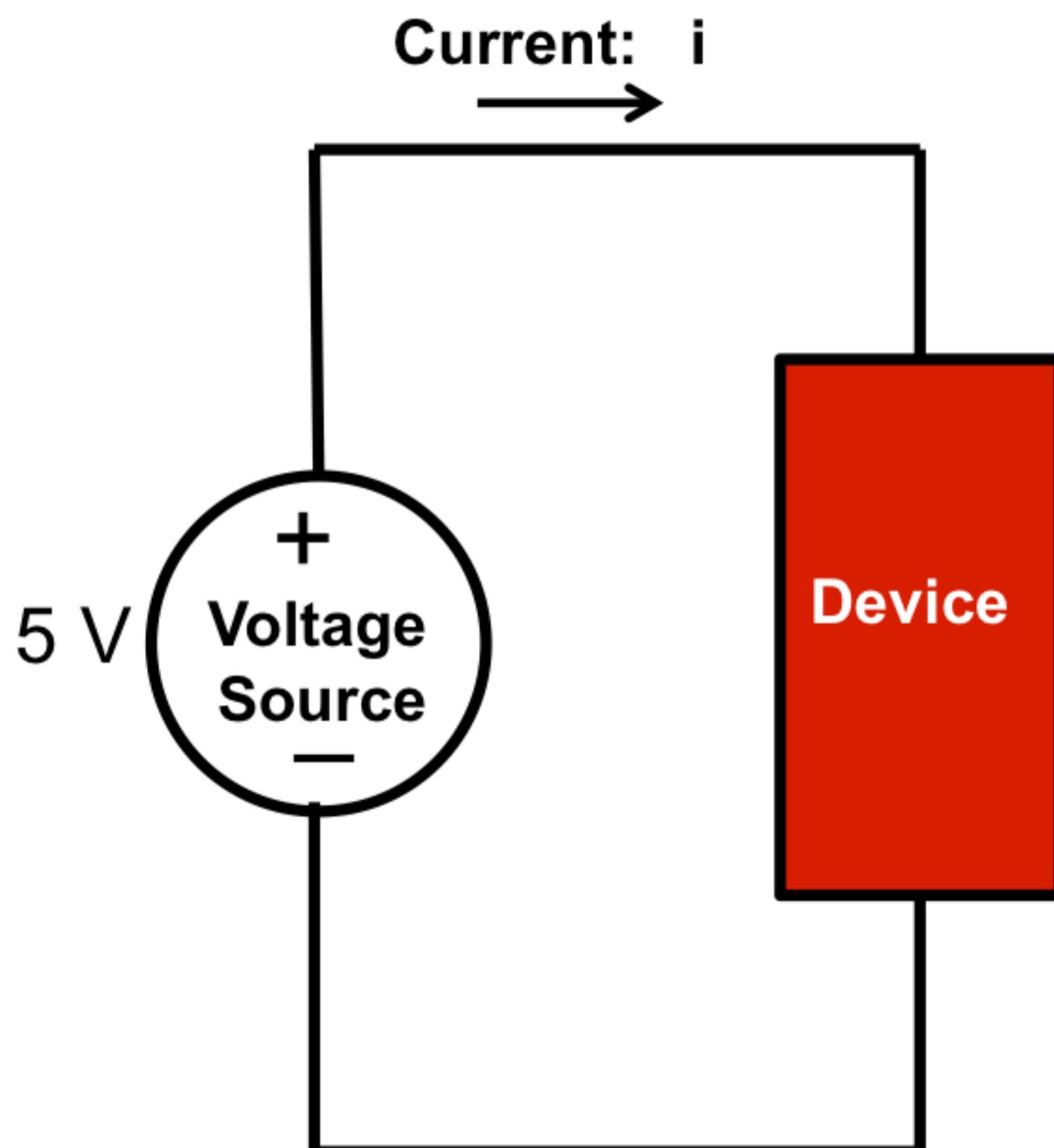

- The battery or power supply provides power to the device. ($P = i \cdot V$) $E = P \cdot t$
- Since energy is conserved, the device does something with this power
 - Resistor turns it into heat
 - LED turns it into light
 - Logic circuit computes something
 - Motor turns it into mechanical energy
 - Pump turns it into potential energy by pumping water uphill
 -

Electrical Devices

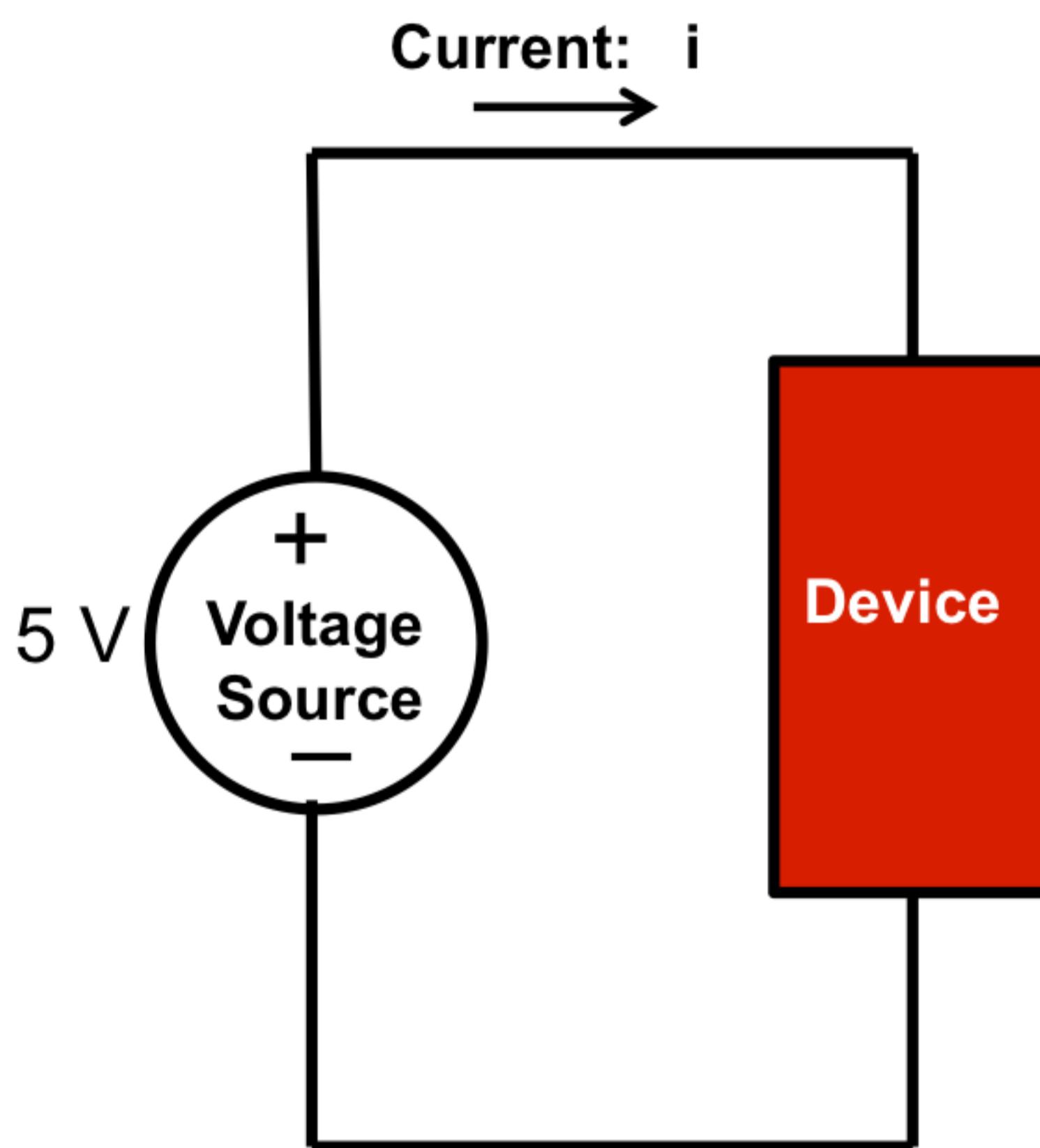


- We'll learn about many different electrical devices.



Resistors



Diodes

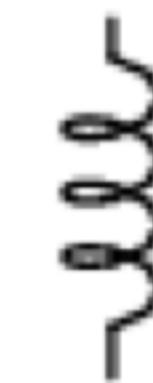


Inductors




Capacitors



Light Emitting Diodes

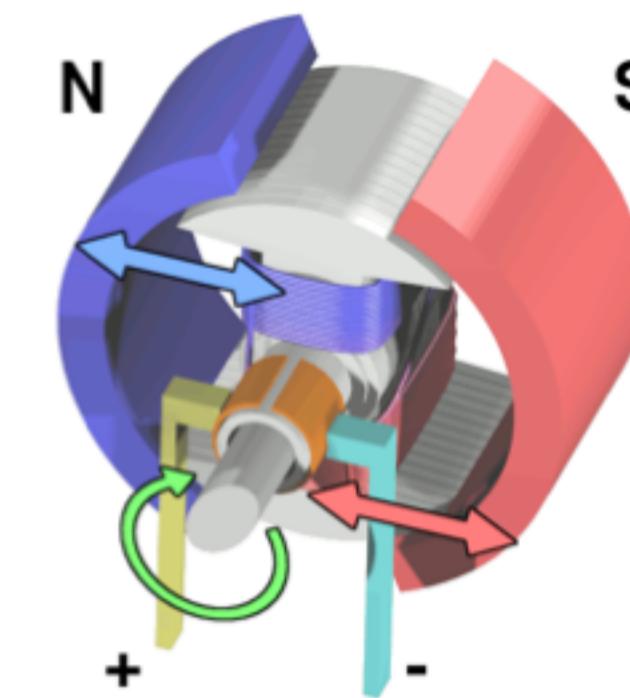


Motors

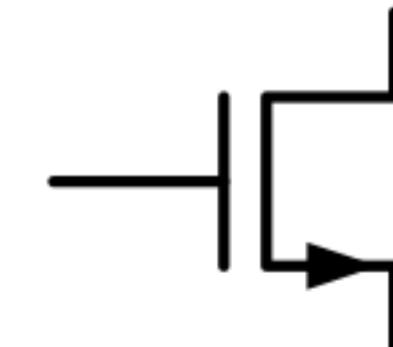


Transistors

Electrical Devices

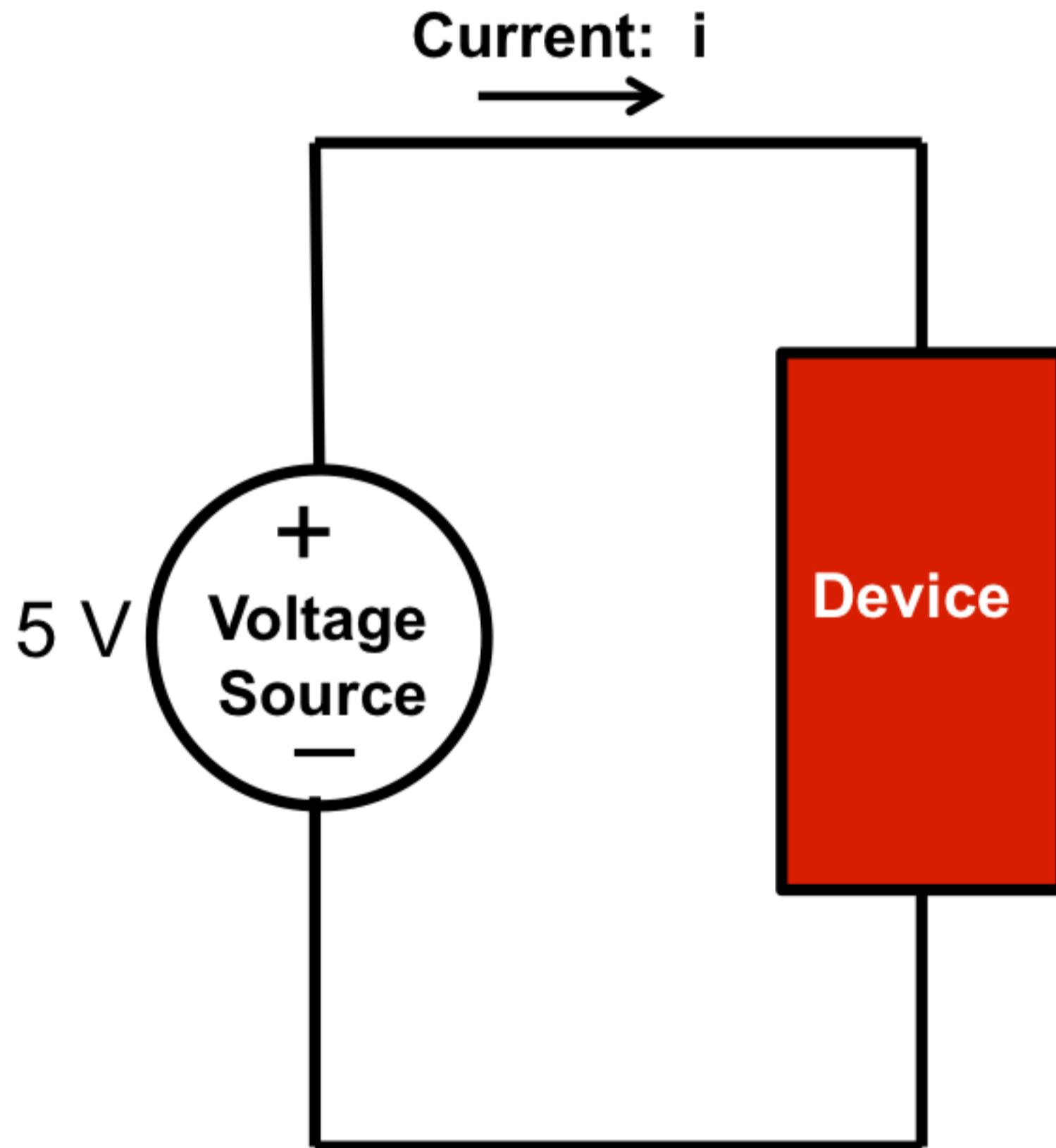



- Each electrical device responds differently to the voltage and current provided to it.
- Electrical engineers combine these devices to do interesting and useful things.
- You'll build and demonstrate several interesting examples in E40M.

Electrical Devices – Some Properties

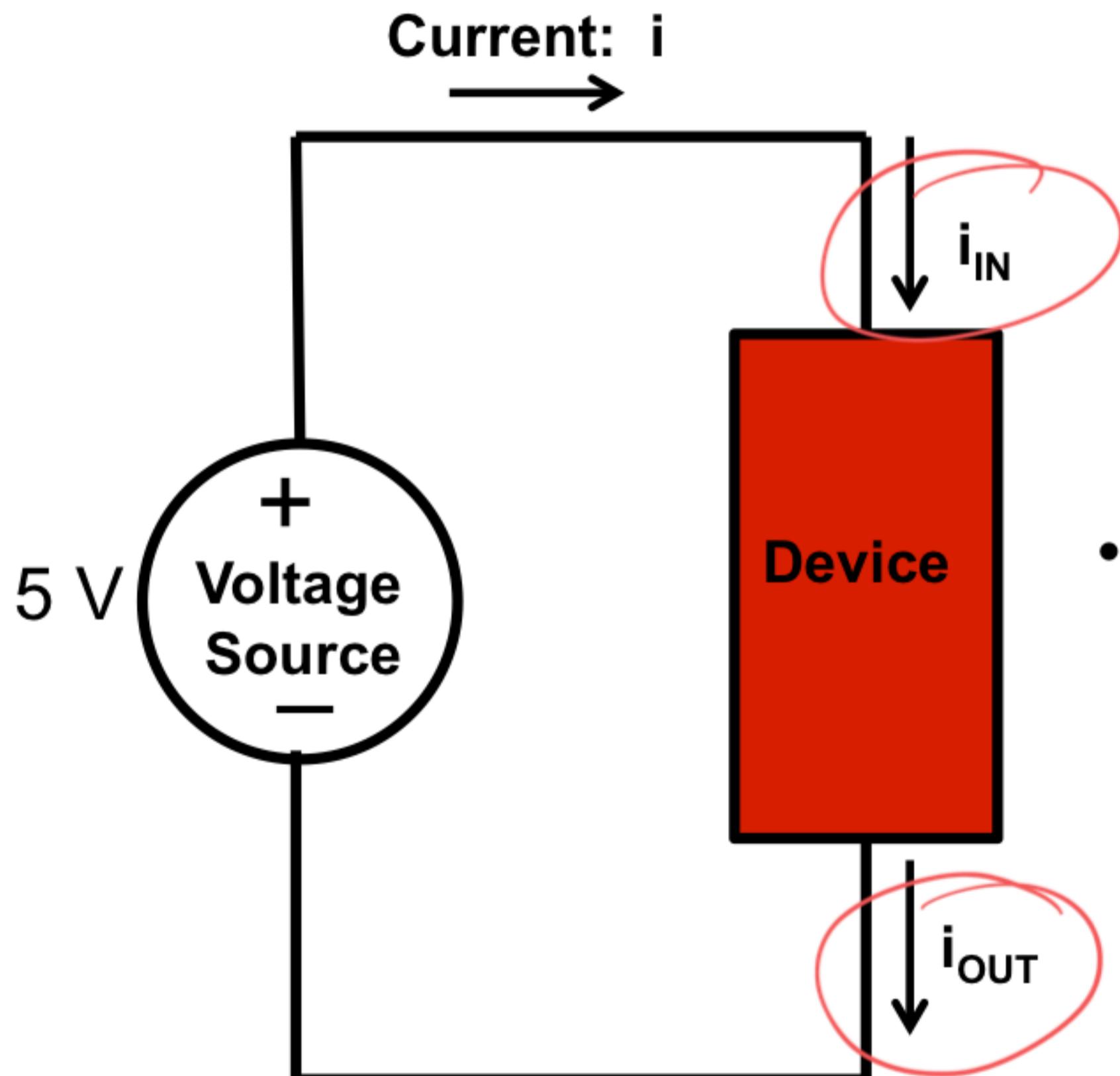


- Charge neutral; i.e., charge entering = charge leaving
 - Batteries or power supplies separate charge but the overall device is still charge neutral
- The net current into any device is **always zero**, so $i_{IN} = i_{OUT}$
 - Current that flows into one end of a wire must flow out the other
 - Often called KCL (Kirchhoff's Current Law)
- Dissipate power ($P = i \cdot V$)


Electrical Circuit Terminology

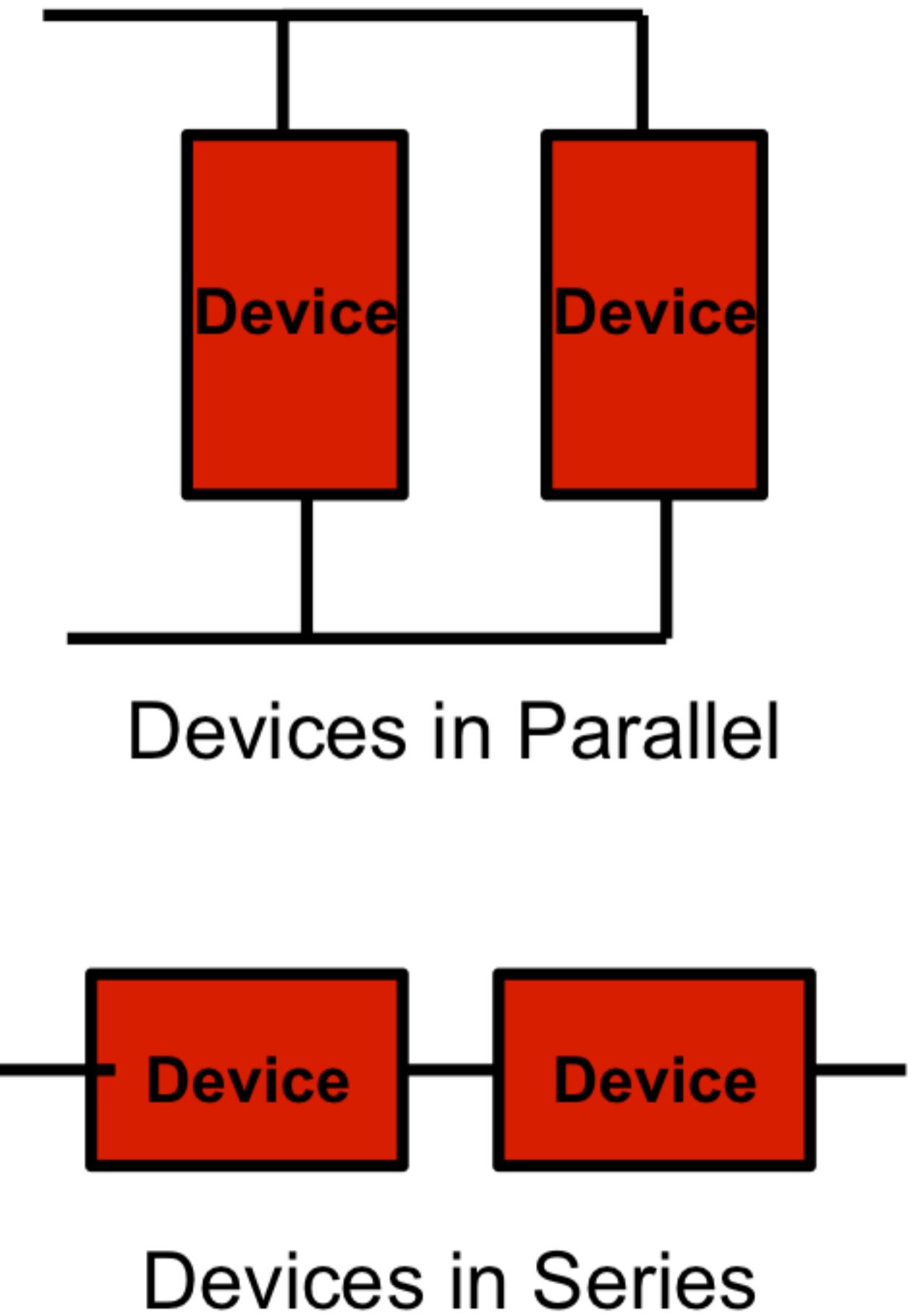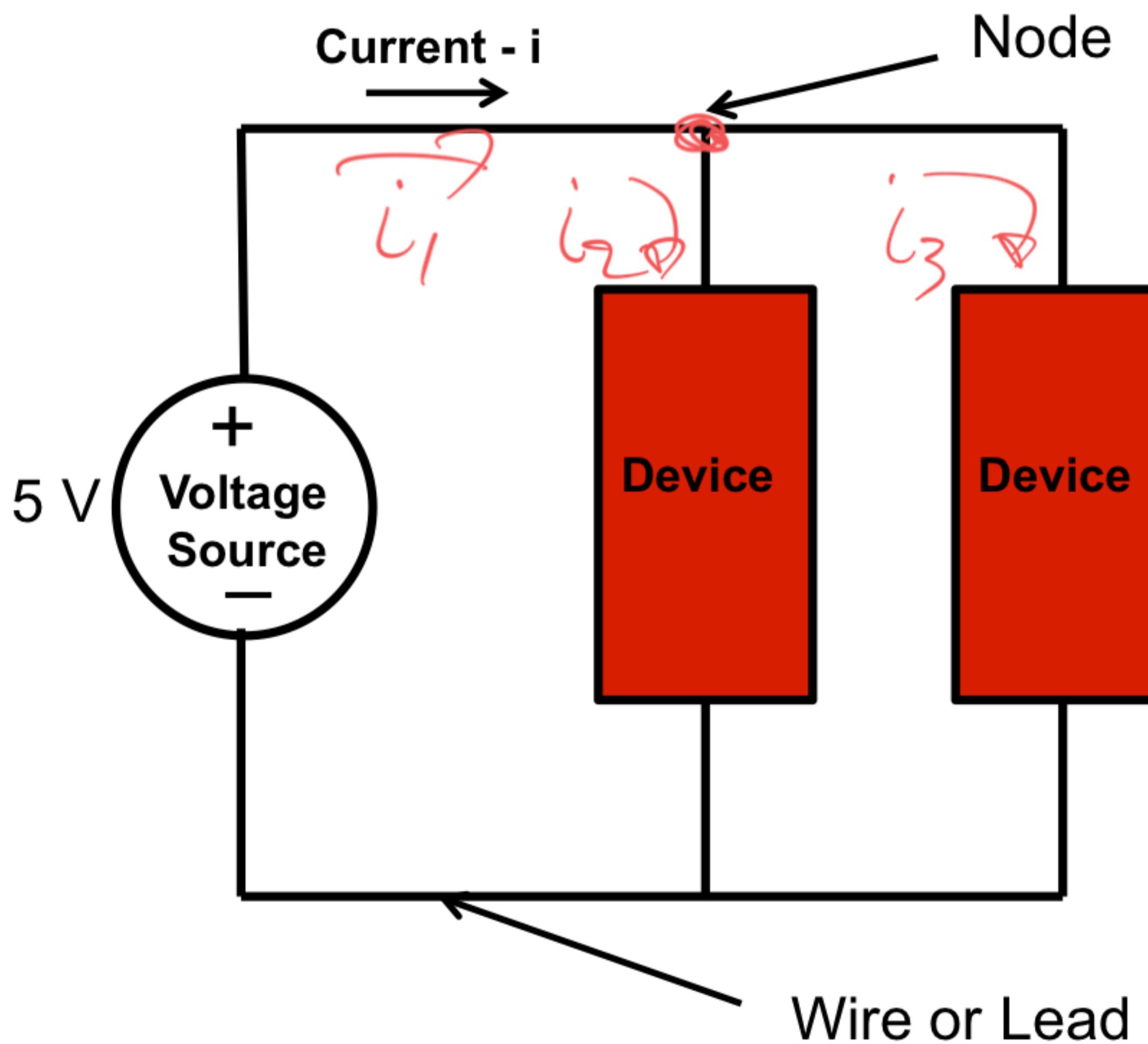

Electrical Circuit Terminology

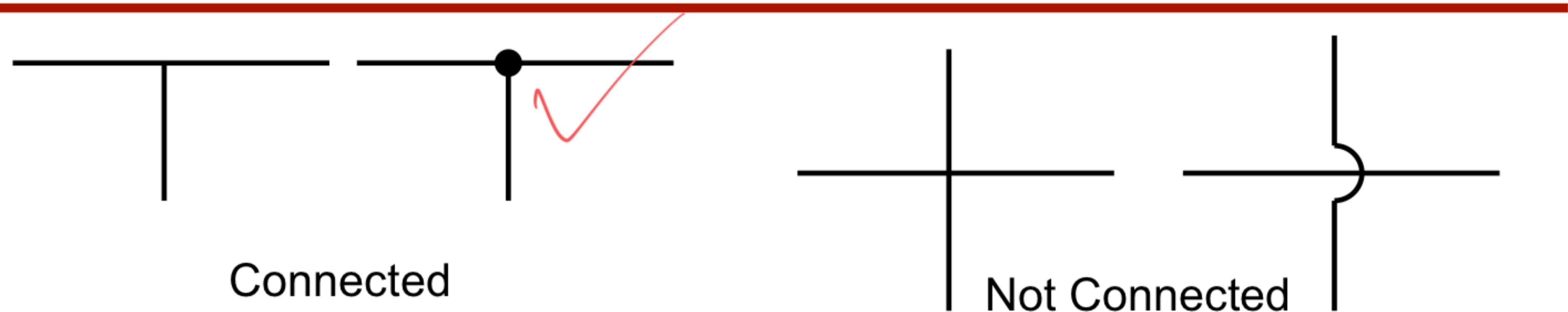

Example:

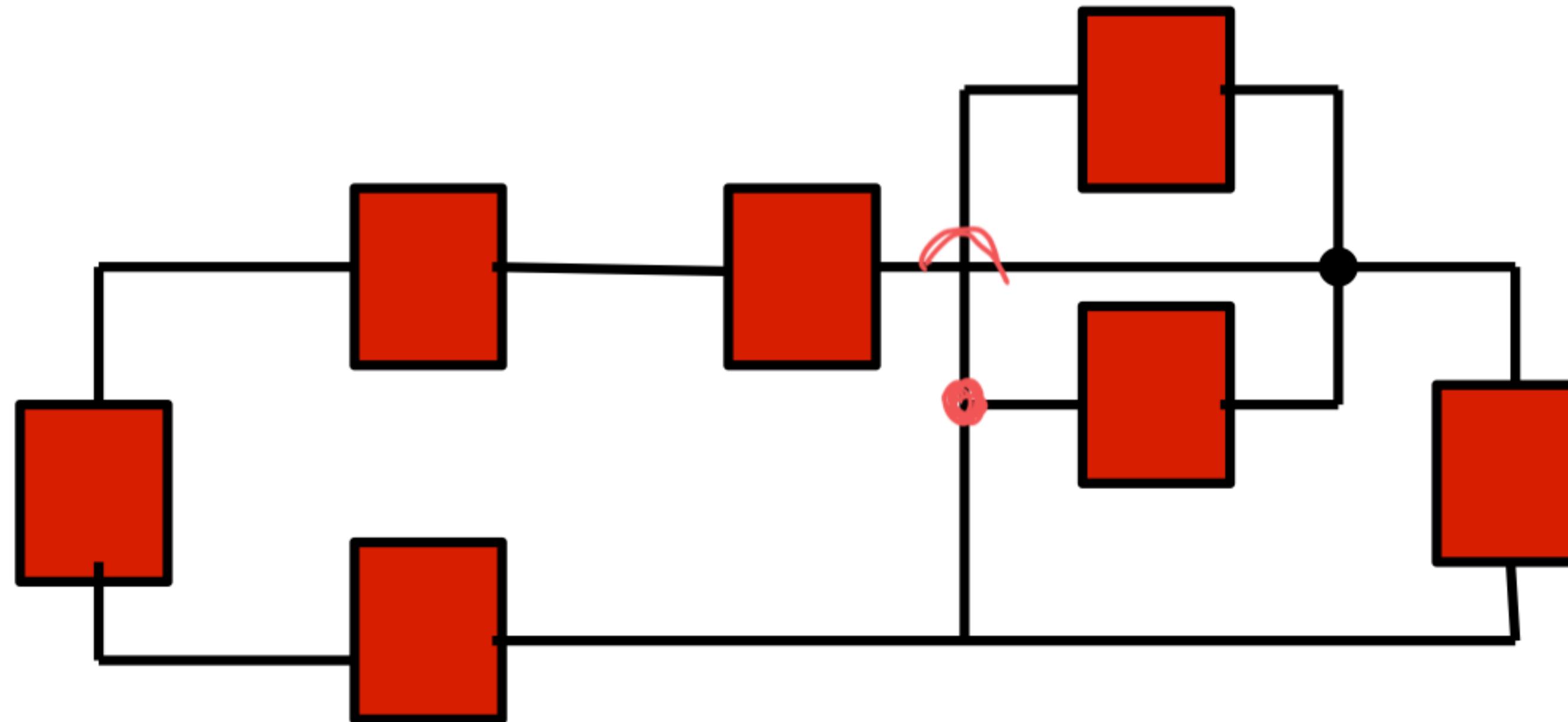

Learning Objectives – Charge, Current, Voltage, Electrical Circuits

- Understand that **charge** is what makes components electrical
 - Moving charge is called **current**, and often represented by “**i**”
 - Measured in **Amps** = Coulombs/sec
- Understand that all components and wires are **charge neutral**
 - This means that the net charge flowing into an object is 0
 - KCL - The sum of the currents into an device **or wire** = 0
- The energy that causes the charge to move is called **Voltage**
 - Measured in **Volts** = Joules/Coulomb
 - Voltage is a potential energy difference
 - Measured between two nodes