
E40M

Solving Circuits using Nodal Analysis, Part II and EveryCircuit™

The Key Idea from Last Lecture

Systematic Nodal Analysis

1. Label all the nodes (V_A , V_B , or V_1 , V_2 , etc.), after selecting the node you choose to be Gnd.
2. Label all the branch currents (i_1 , i_2 , etc.) and choose directions for each of them
3. Write the KCL equations for every node except the reference (Gnd)
 - Sum of the device currents at each node must be zero
4. Substitute the equations for each device's current as a function of the node voltages, when possible
5. Solve the resulting set of equations

Today: Reducing Circuit Complexity

- Fewer variables is better
 - Could be fewer nodes
 - Could be fewer devices
- Can we break the circuit into pieces
 - Look at a **sub-circuit**
 - Replace that sub-circuit with a simpler equivalent
- We'll look at several examples


Series Combinations

- Two resistors in series (“share a current”)
 - The voltage across the combination is the sum of the device voltages
 - The current through the devices is the same
 - So the effective resistance of the series is $R = R_1 + R_2$
- So we can replace series resistors
 - With a single equivalent resistor
 - Removes a node voltage and device from our equations!



Parallel Combinations

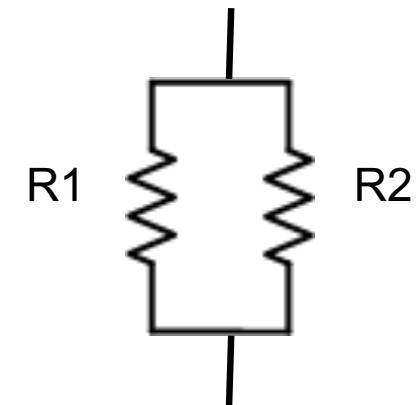
- Two resistors in parallel
 - The total current through parallel resistors is the sum of the currents through the two resistors
 - The voltage across each resistor is the same ... they “share a voltage”
 - So the effective resistance of parallel resistors is:



$$1/R = 1/R_1 + 1/R_2$$

$$R = (R_1 \cdot R_2) / (R_1 + R_2)$$

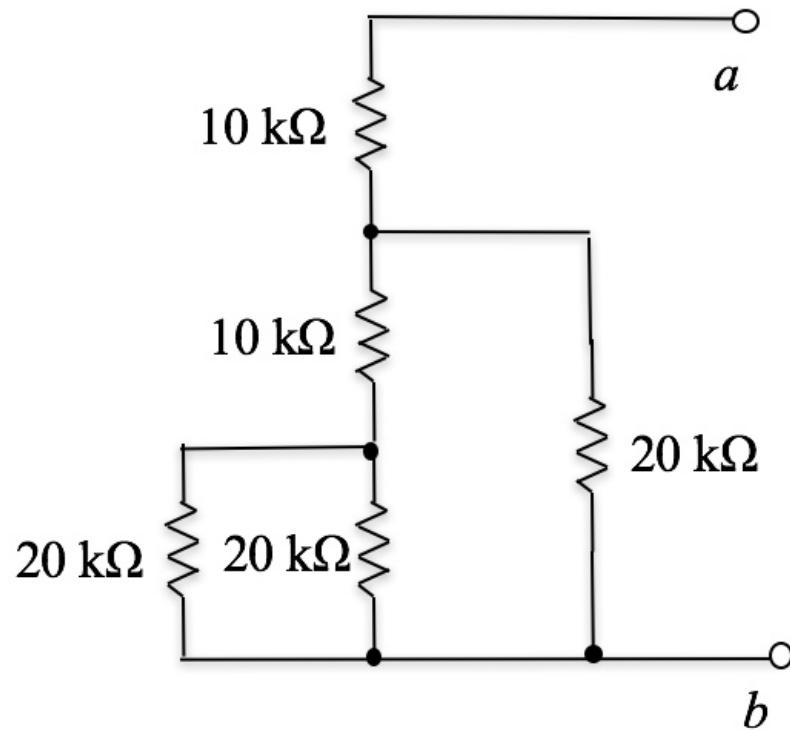
Using Series and Parallel Combinations to Simplify Circuits



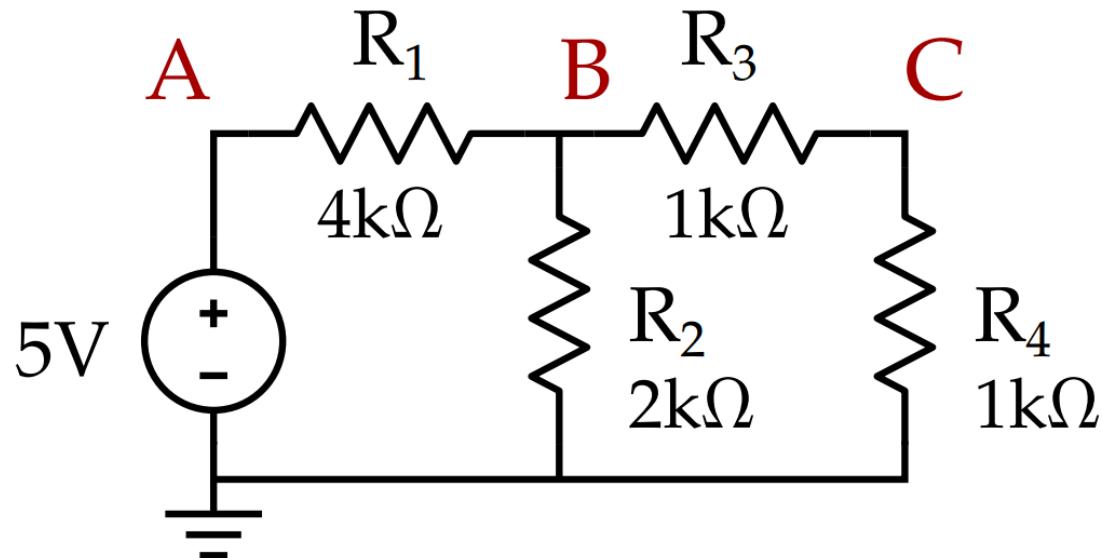
Example: Find the resistance between node a and node b

But What About This Circuit?


- R_3 and R_4 are in series
 - But I need to find the voltage at the node I will eliminate
 - “collapse and then expand”
- First eliminate the node to simplify the circuit



First Solve for the Voltage at Node B

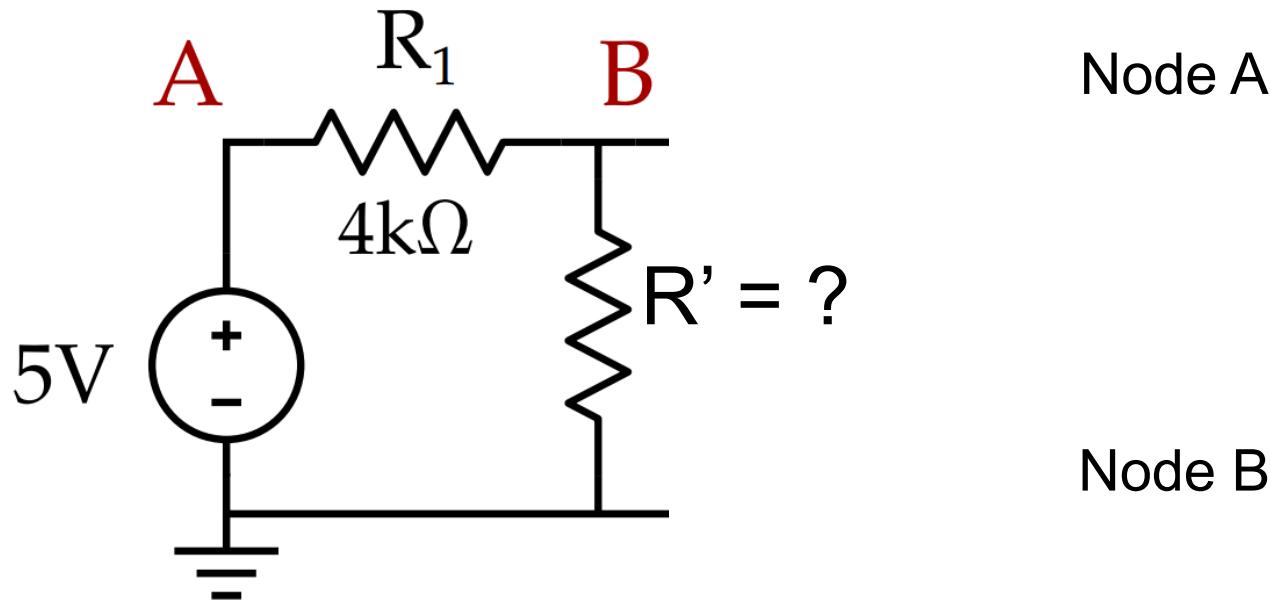


Then Solve for the Voltage at Node C

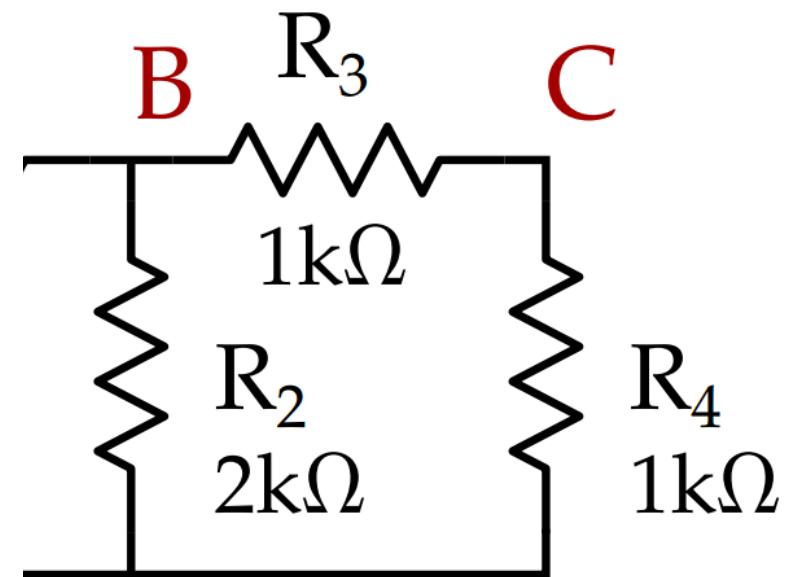

Voltage Divider

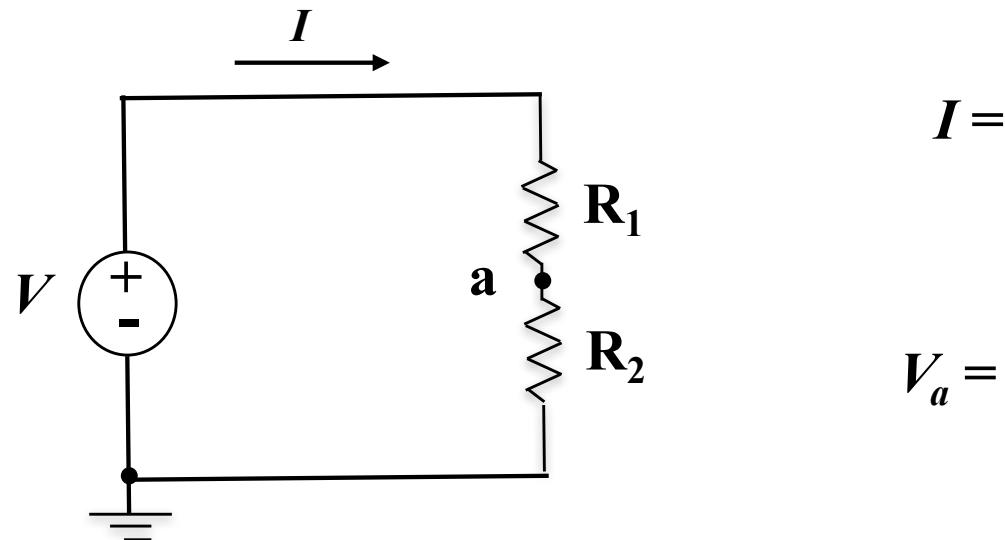- First simplify circuit to a single resistor and find the current I
- Then use the current to find the voltage V_a




$$I =$$

$$V_a =$$

Current Divider

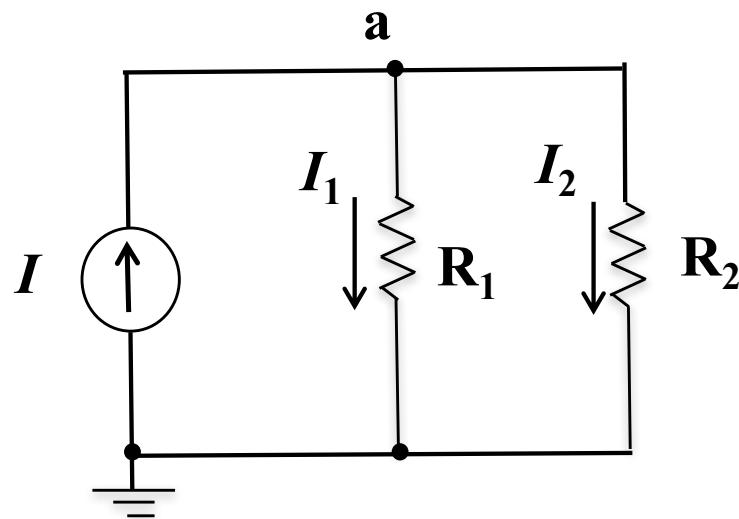- In this case simplify the circuit to a single resistor, then find voltage across each resistor and use it to find the current through each resistor



Intuition on Dividers


- Voltage divider: $R_2 = 10 R_1 \dots$ what is $V_a = V_{R2}$ in terms of V ?
- Current divider: $R_2 = 10 R_1 \dots$ what is I_2 in terms of I ?

Series-Parallel Reduction


We connect a 2 V battery between nodes 1(+) and 2(-).

What current flows through the latter?

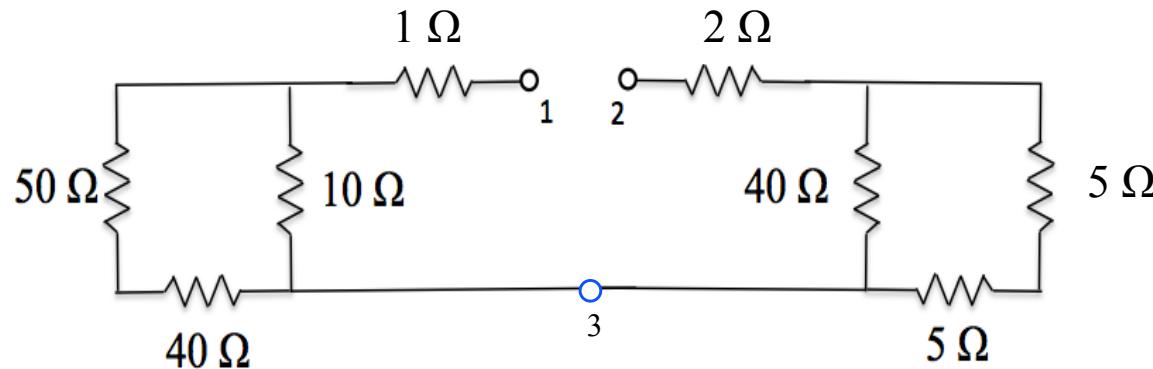What is the voltage difference between node 2 and node 3?



Series-Parallel Reduction

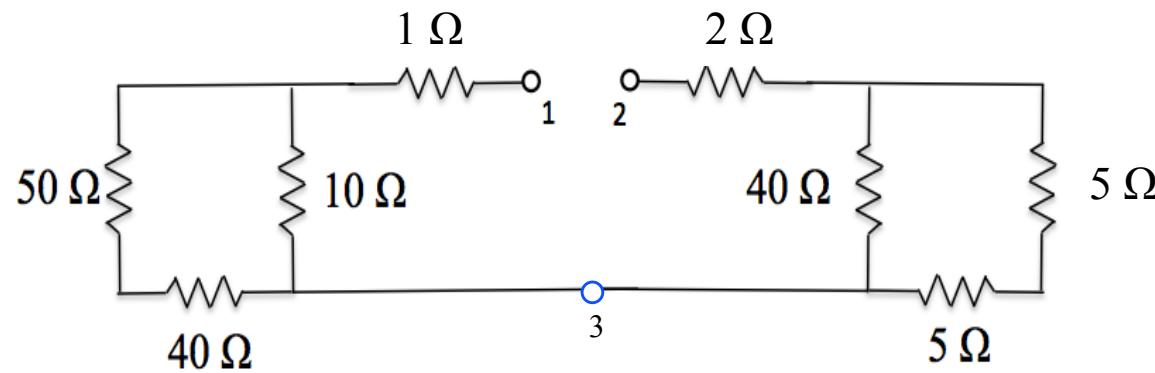


Superposition For Linear Circuits

If a circuit contains more than one independent source, the voltage (or current) response of any element in the circuit is equal to the algebraic sum of the individual responses associated with the individual independent sources, as if each had been acting alone.

- Reason:
 - Resistors, voltage, and current sources are linear
 - Resulting equations are linear
- What's the benefit?
 - Superposition enables the analysis of several simpler circuits in place of one complicated circuit


Applying Superposition

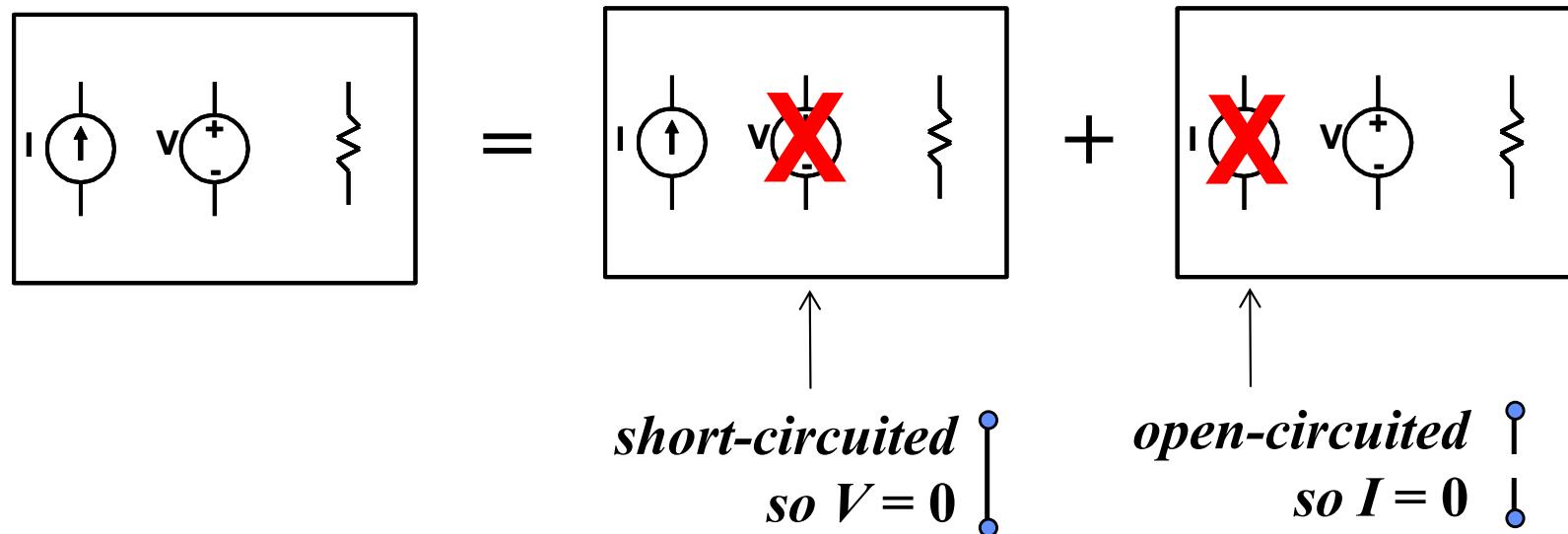- Calculate the response of the circuit for each independent source at a time, with the other's turned off
- What happens when we turn off a source?
 - Voltage sources: have 0 V (are **shorted** ... replace by a wire)
 - Current sources: have 0 current (are **opened** ... replace by a *broken* wire)



Applying Superposition


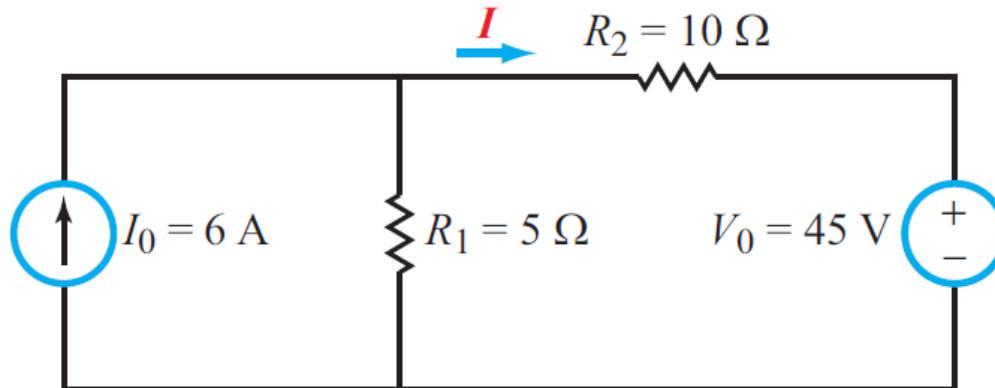
- We need to “zero-out” sources into order to find the sub-circuits (one per source)
- Find the current I



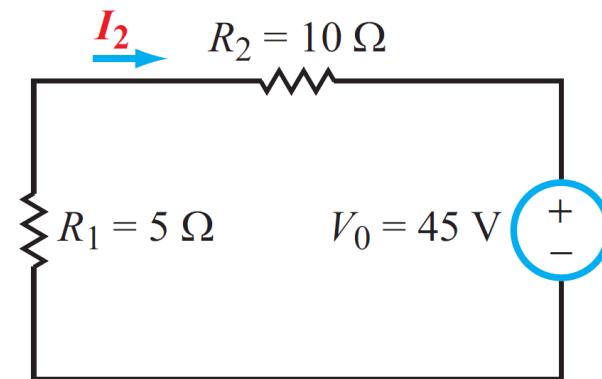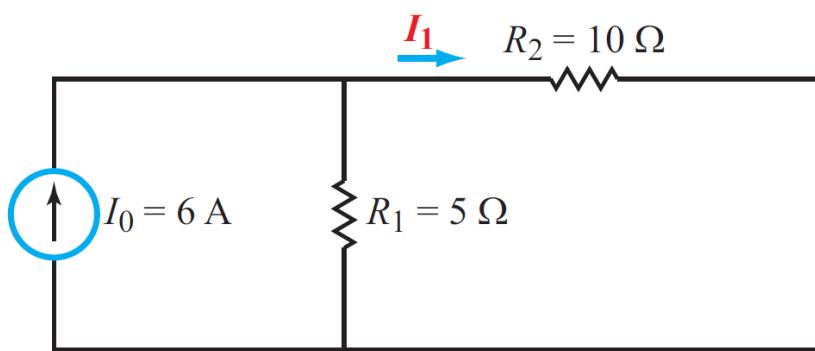F. T. Ulaby and M. M. Mahabir, *Circuits*, NSTP, 2009, p. 97.

Applying Superposition

- We need to “zero-out” sources into order to find the sub-circuits (one per source)



$$I_1 =$$

$$I_2 =$$

$$I = I_1 + I_2 =$$

F. T. Ulaby and M. M. Mahabiz, *Circuits*, NSTP, 2009, p. 97.

EveryCircuit

Circuit Debugging

- For future labs you will be building more complex circuits
 - You will build these circuits using breadboards
- These circuits will contain many different components
 - Including transistors with three connections
- Sometimes these circuits won't work the way you expect
 - Perhaps your circuit is wrong
 - Or perhaps you just connected it up wrong
 - How do you debug it in either case?

Circuit Simulator

- We create a program to estimate how our circuit will behave
- The program shows the wiring in a nice way
 - and makes it easy to probe the voltage and current
 - It has built-in voltage and current meters
- It also makes it easy to change component values
 - So you can tune/play with your circuit
- You are going to use an easy-to-use simulator: EveryCircuit

Every Circuit

<http://everycircuit.com/app/>

The screenshot shows the EveryCircuit application interface. On the left, there is a sidebar with the title "EveryCircuit" and icons for Google Chrome, Android, and Apple. Below the title are several examples with circuit diagrams and descriptions:


- Current**: Current is a flow of electric charge, such as electrons moving through a wire. It is measured in amperes (A) and.
- Voltage and ground**: Electrons have electric potential energy. An electron located at ground node has zero energy. Its energy
- Resistance and Ohm's...**: Resistance (R) of an electrical conductor is its opposition to the passage of current. Resistance is measured in
- KCL and current divider**: Kirchhoff's current law (KCL) states that the sum of currents flowing into a node is equal to the sum of currents
- KVL and voltage divider**: Kirchhoff's voltage law (KVL) states that the sum of voltages across the components in any closed
- Resistor tree**: One way to calculate an equivalent resistance of a network is to apply a known voltage across it and measure

The main workspace is a grid-based circuit editor with a toolbar at the top containing symbols for voltage, current, resistors, capacitors, inductors, and other components. To the right, there is a "Circuit details" panel for saving the circuit, with options for "PUBLIC", "UNLISTED", and "PRIVATE" (which is selected), and buttons for "SAVE" and "jdplummer". The "jdplummer" section includes fields for "Enter title" and "Enter description".

Every Circuit

<http://everycircuit.com/app/>

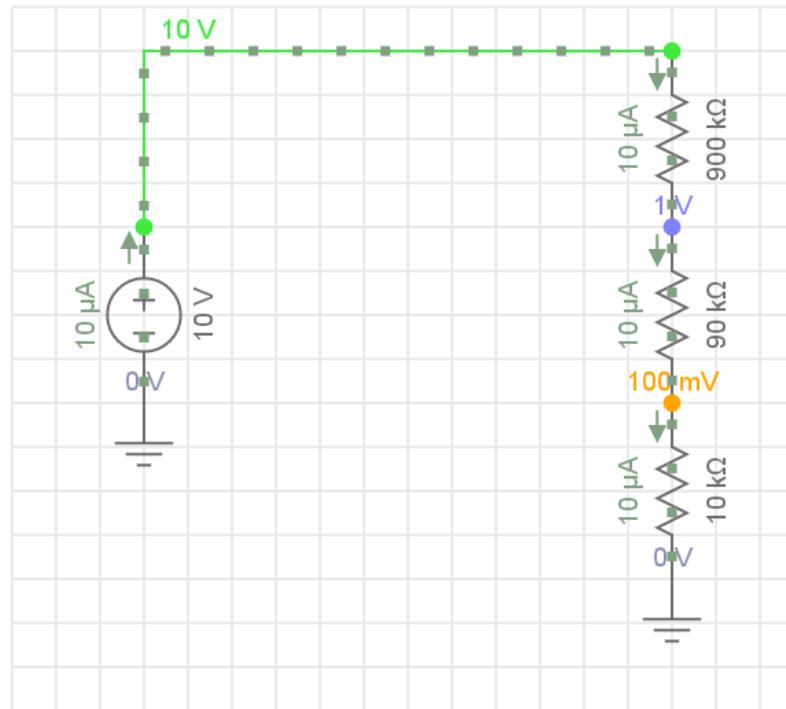- Simple simulator that we will use for circuits



Quick Use Notes

- To connect two nodes, select one node, then select another node.
- To delete a single wire in a node, select the node, then select the wire, then press Delete.
- To maximize schematic area in browser window (remove circuit explorer on the left and circuit details on the right) click the right-most icon in the menu below the schematic.

Every Circuit's Keyboard Shortcuts

- R : Rotate selected device
- F : Flip selected device
- A : Adjust parameter of a selected device
- T : Toggle selected switch
- W : Add / remove voltage of selected node or current of selected device to / from oscilloscope
- S : Adjust simulation speed
- Esc : deselect all
- Arrows : move selected component or workspace
- Plus / Minus : zoom in / out
- Space : start or pause simulation
- Delete : delete selected device or cut selected wire
- Ctrl + Z : Undo
- Ctrl + Y : Redo

Activate Your License

- <http://everycircuit.com/licensekeyactivation>

259825287547

(Good during spring quarter)

Learning Objectives

- Understand how to solve for device voltage and currents
 - First label node voltages (KVL)
 - Solve current equations at each node (KCL)
 - Called nodal analysis
- Be able to break a large circuit into smaller circuits
 - This is standard “divide and conquer” approach
- Recognize some common circuit patterns
 - Which reduce the complexity of the circuit you need to solve
 - Start with series and parallel resistors
- Superposition is a powerful tool for handling multiple sources
- EveryCircuit can solve your circuits, so you can be sure your homework and prelab answers are correct!