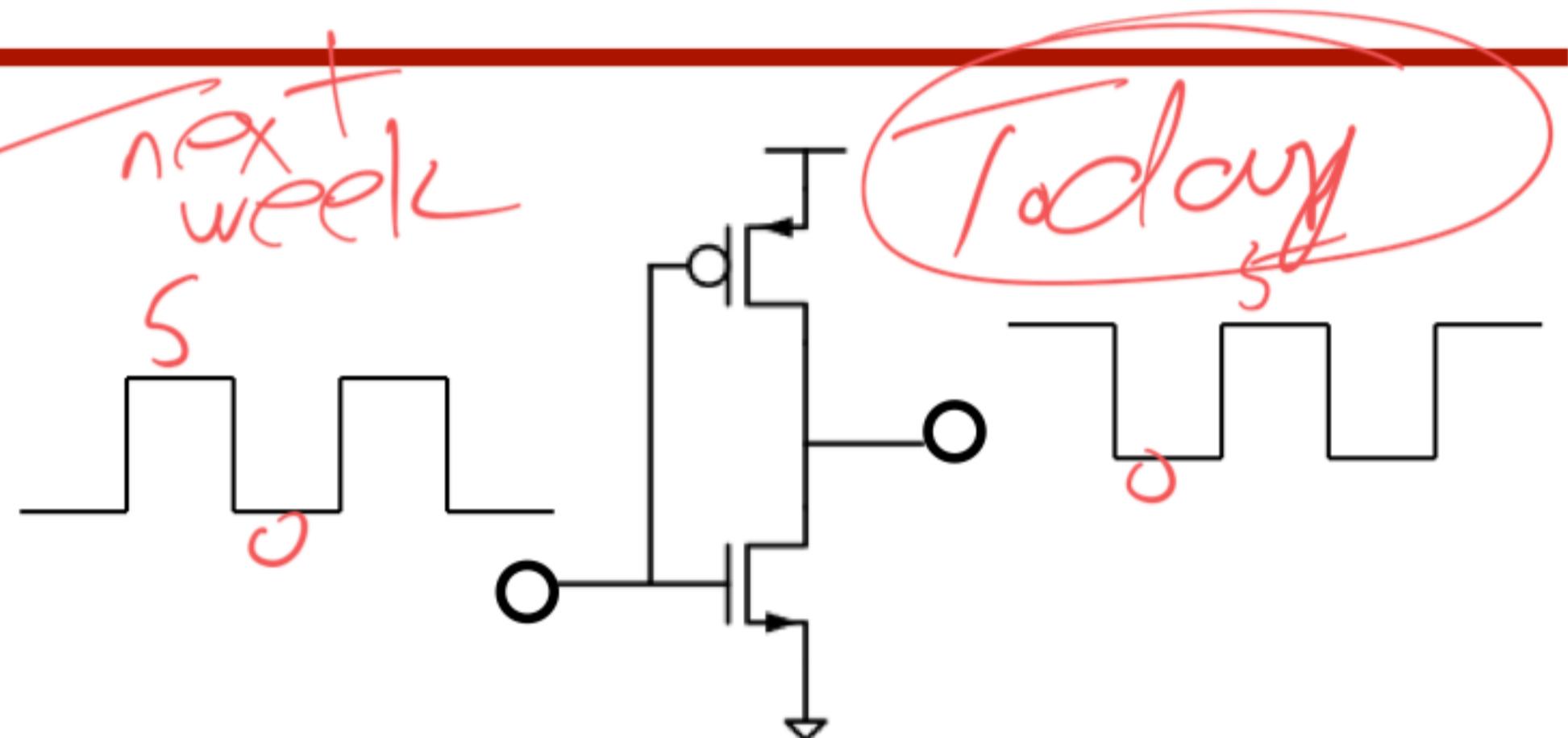
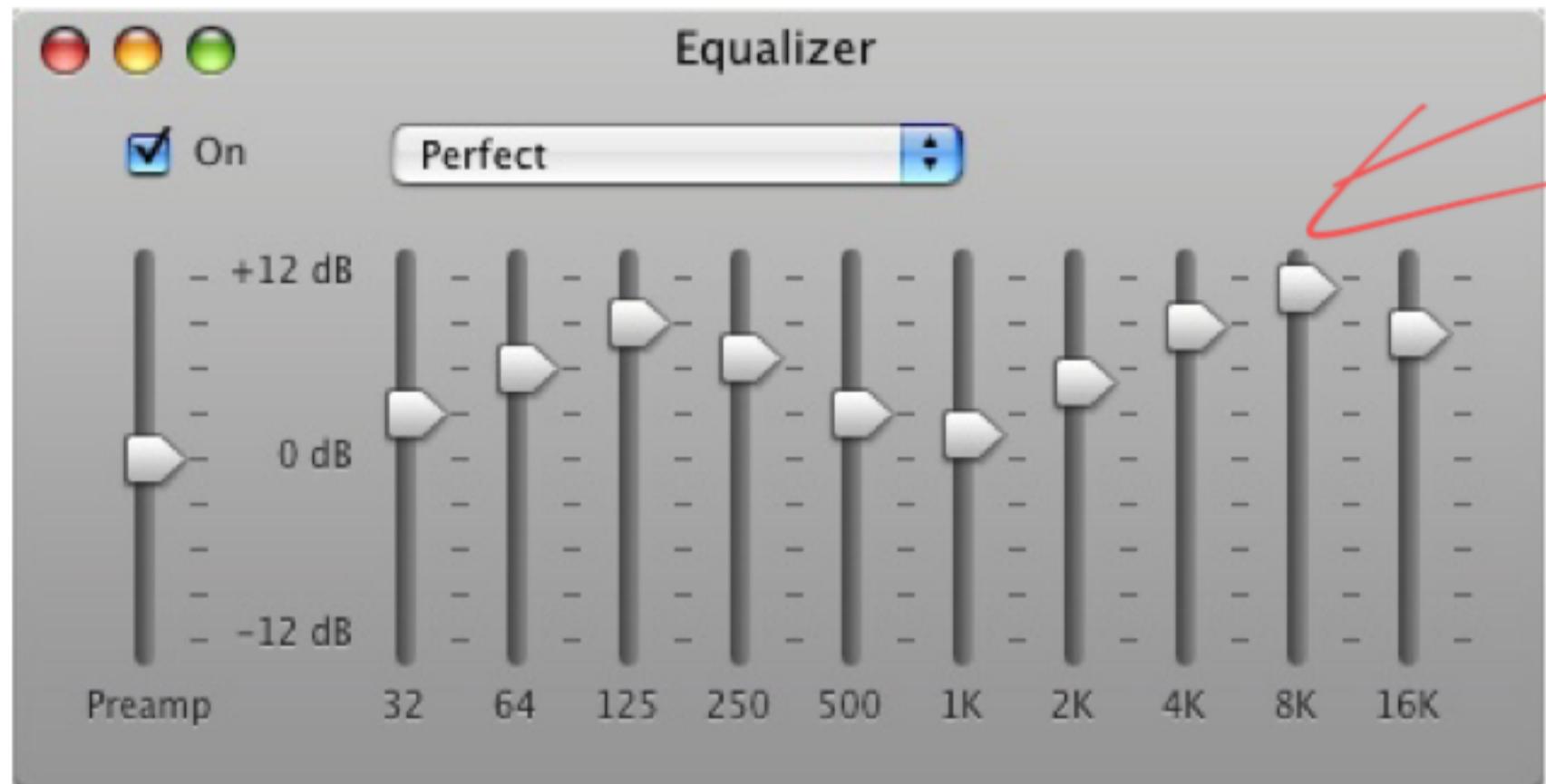

E40M Capacitors

Midterm - Wed in class, this room
Cover through lecture #9, lab 2b, HW #4

Reading


- Reader:
 - Chapter 6 – Capacitance
- A & L:
 - 9.1.1, 9.2.1

Why Are Capacitors Useful/Important?



How do we design circuits that respond to certain frequencies?

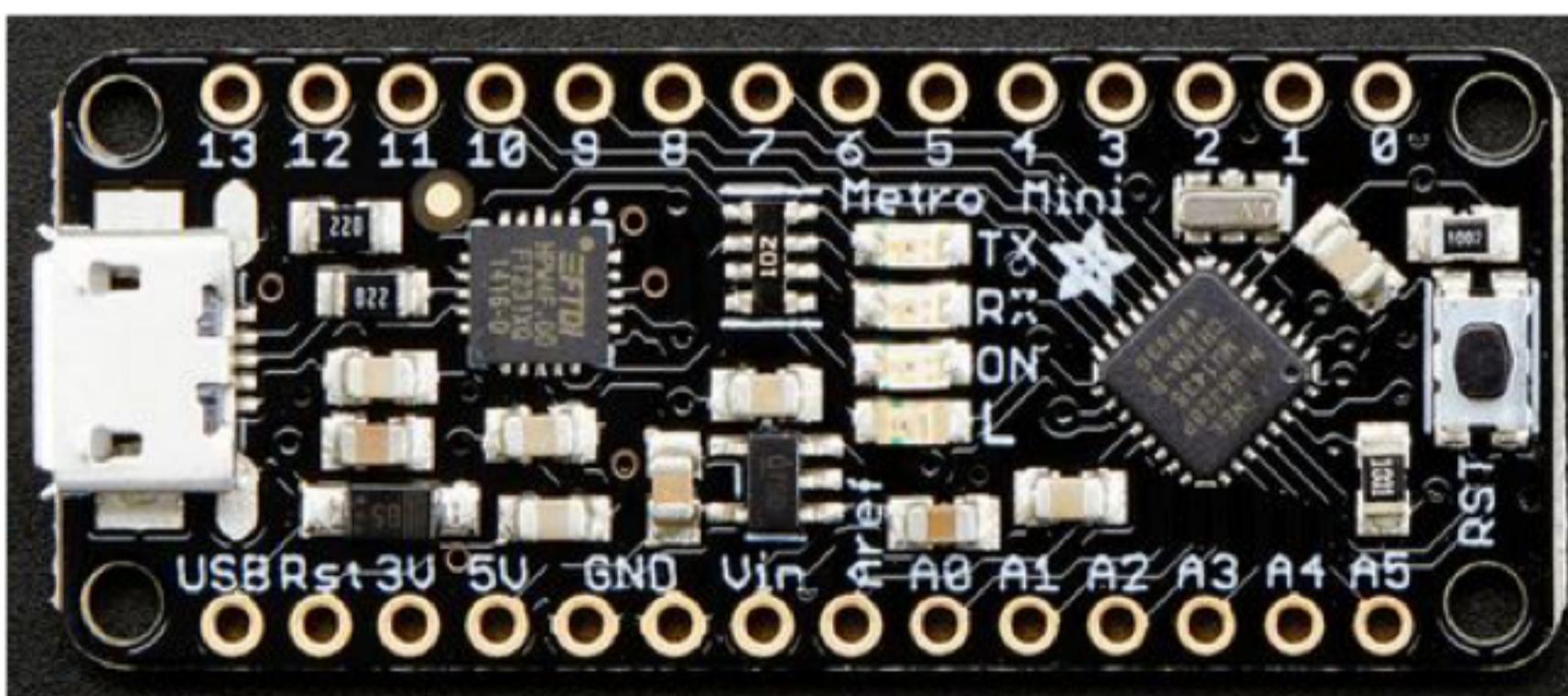What determines how fast CMOS circuits can work?





Why did you put a $200\mu\text{F}$ capacitor between Vdd and Gnd on your Arduino?


CAPACITORS


Capacitors

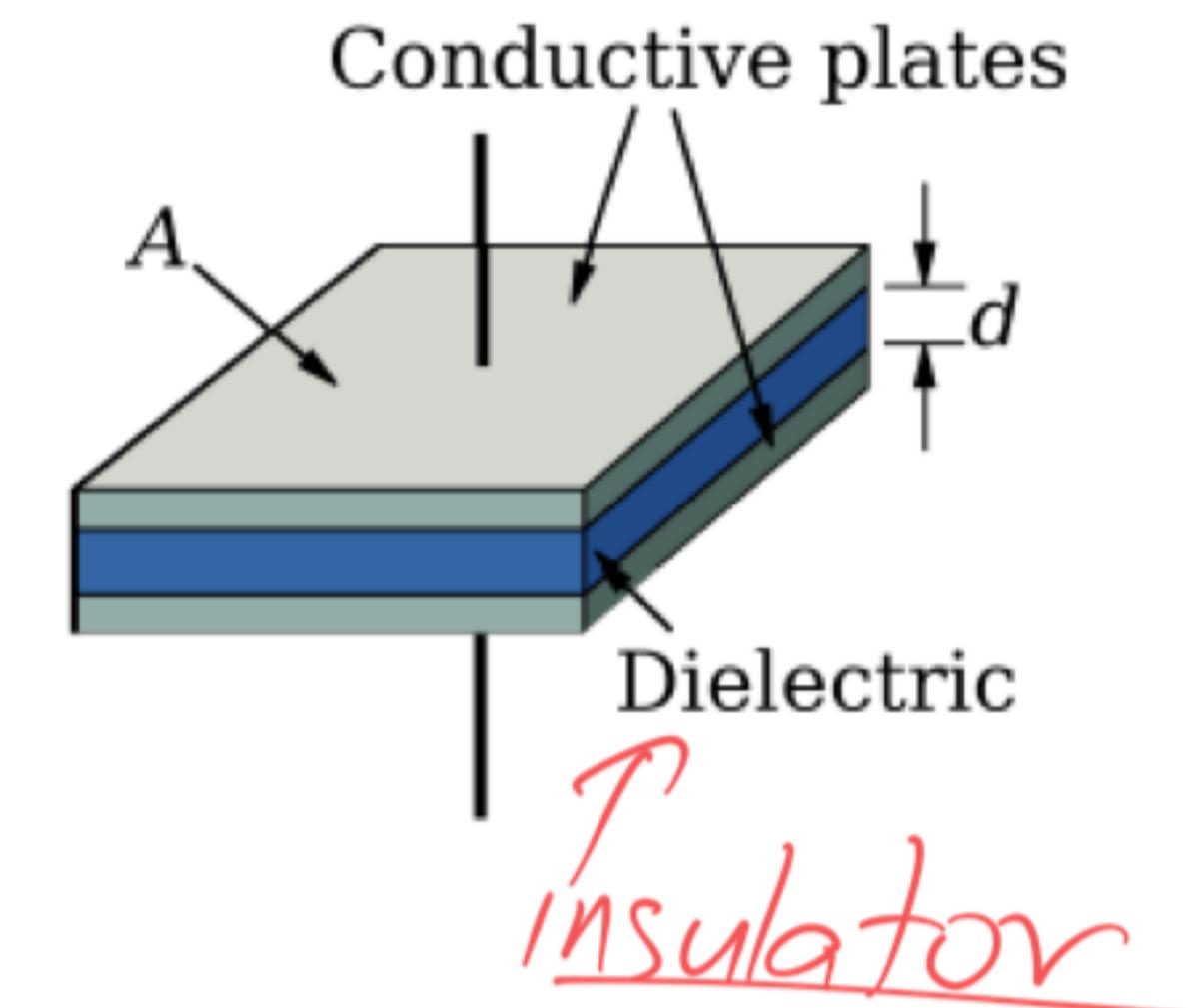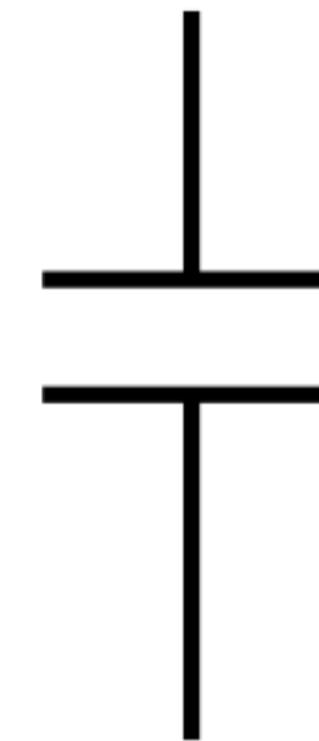- What is a capacitor?
 - It is a new type of two terminal device
 - It is linear
 - Double V, you will double I
 - We will see it doesn't dissipate energy
 - Stores energy



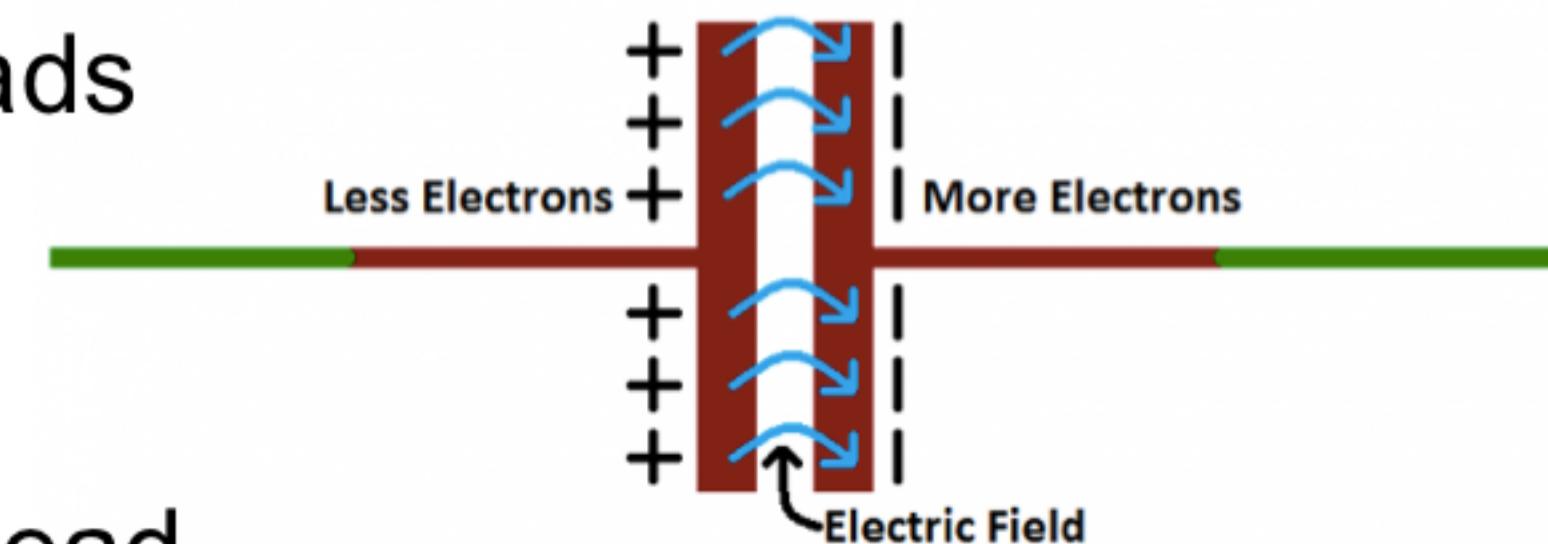- Rather than relating i and V
 - Relates Q , the charge stored on each plate, to Voltage
 - $Q = CV$
 - Q in Coulombs, V in Volts, and C in Farads
- Like all devices, it is always charge neutral
 - Stores $+Q$ on one lead, $-Q$ on the other lead




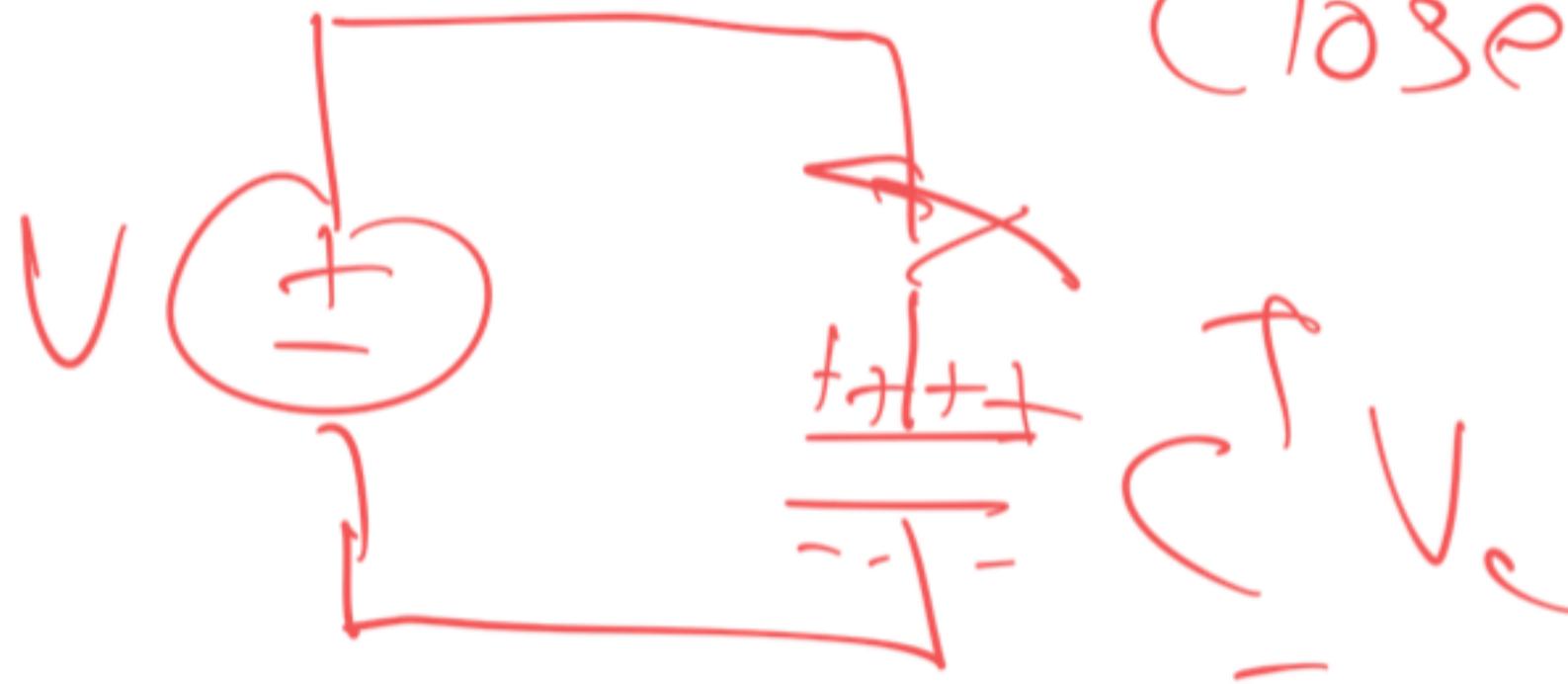

Close switch @ $t = 0$

since $V_c = V$

then $i \rightarrow 0$

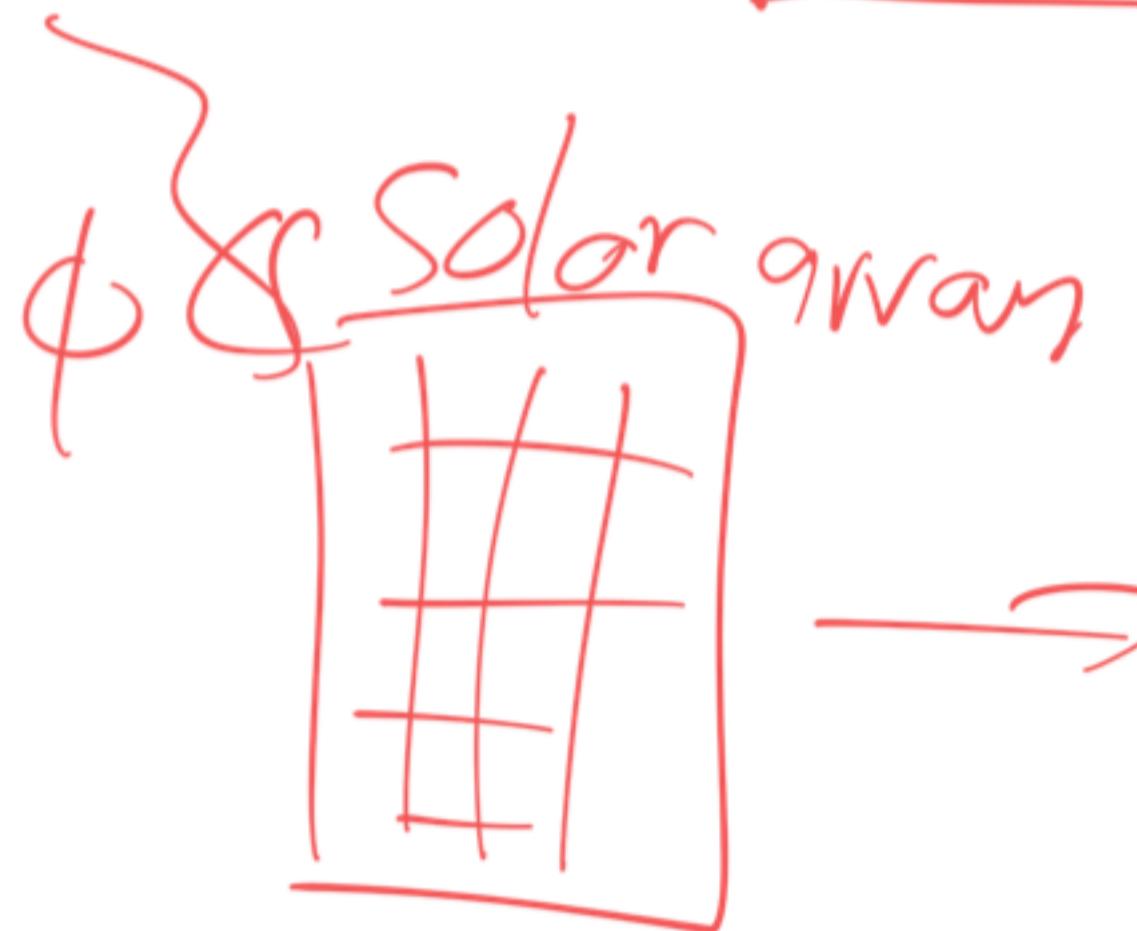

① Battery - solar cell project


② Cap

much less energy density

Capacitors have many applications
in circuits

iV for a Capacitor

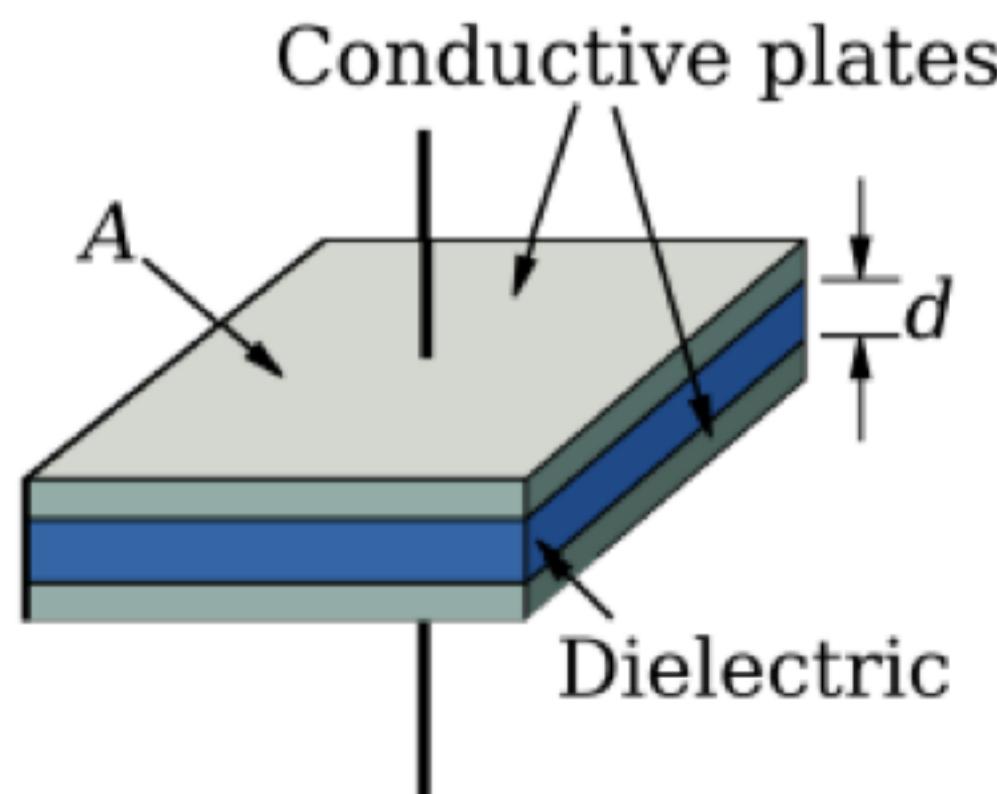- We generally don't work in Q , we like i and V
 - But current is charge flow, or dQ/dt
- So if $Q = CV$, and $i = dQ/dt$
 - $i = C dV/dt$
- This is a linear equation but between i and dV/dt . If you double i for all time, dV/dt will also double and hence V will double.




$$C = \frac{\epsilon A}{d}$$

(C↑ as A↑)
(C↑ as d↓)

where ϵ is the dielectric constant

Capacitors Only Affect Time Response not Final Values

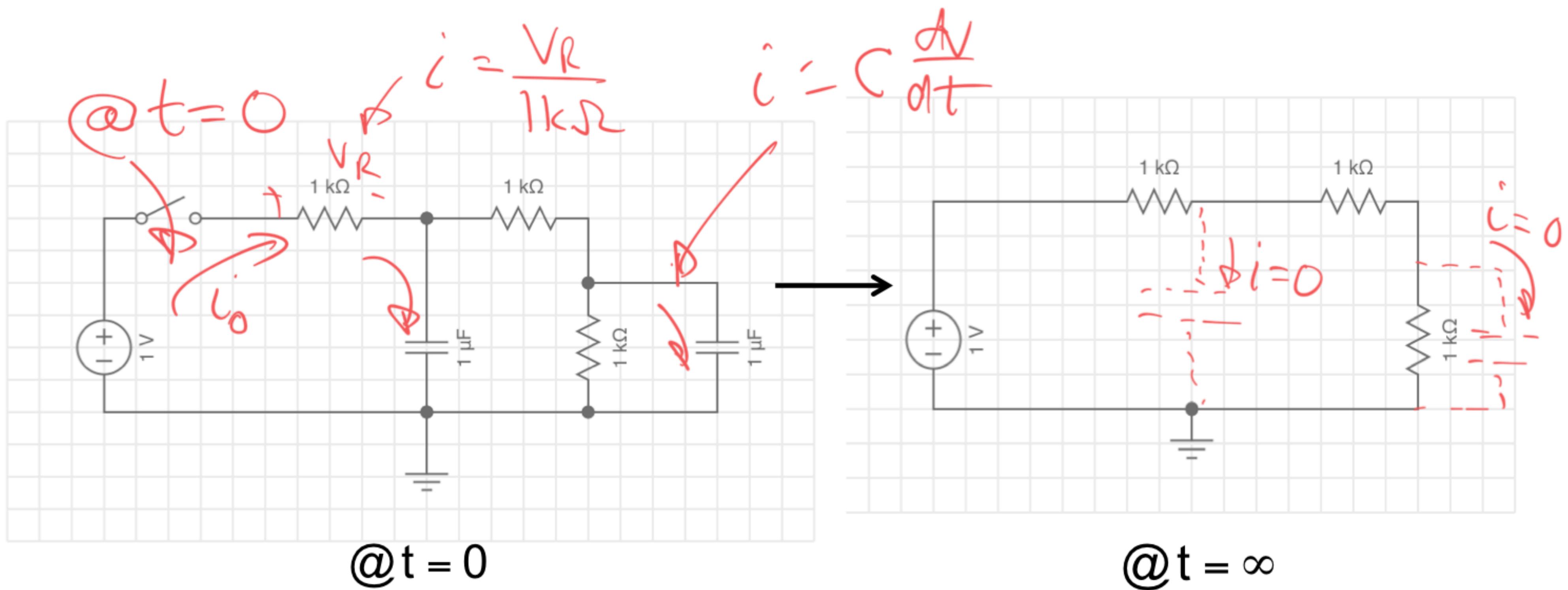
- Capacitors relate i to dV/dt
- This means if the circuit “settles down” and isn’t changing with time, a capacitor has no effect (looks like an open circuit).



So What Do Capacitors Do?

- It affects how fast a voltage can change
 - Current sets dV/dt , and not V
 - Fast changes require lots of current
- For very small Δt capacitors look like voltage sources
 - They can supply very large currents
 - And not change their voltage
- But for large Δt
 - Capacitors look like open circuits (they don't do anything)

$$i = C \frac{dV}{dt}$$

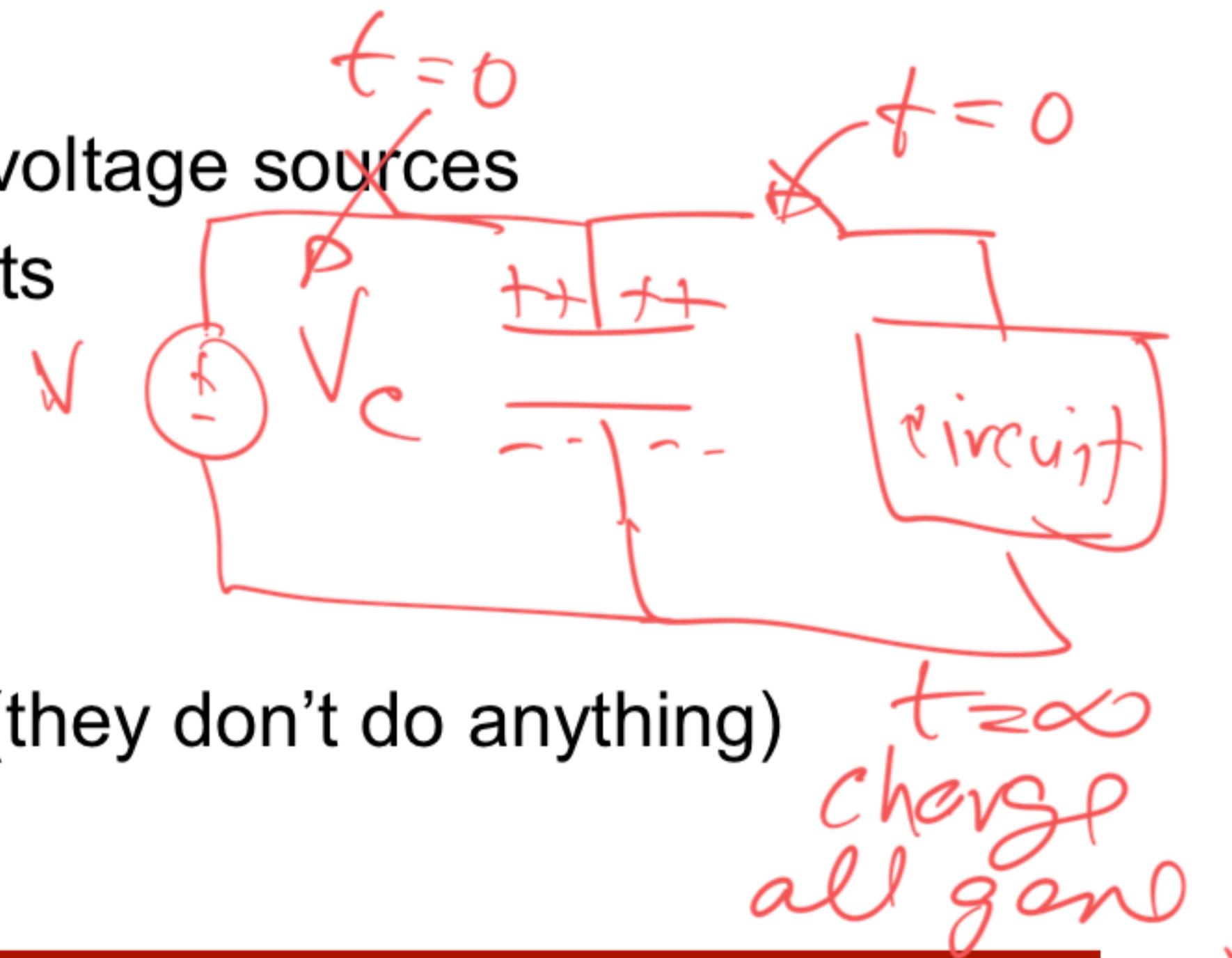

Capacitor Energy


- The Power that flows into a charging capacitor is

$$P = iV = \left(C \frac{dV}{dt} \right) V$$

- And the energy stored in the capacitor is

$$E = \int P dt$$
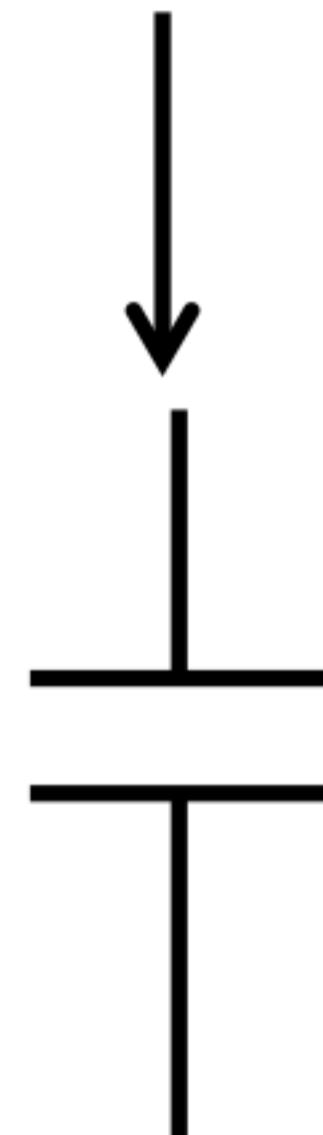
$$\therefore E = \int P dt = \int_0^V CV dV = \frac{1}{2} CV^2$$




- This energy is **stored** and can be **released** at a later time. No energy is lost.

REAL CAPACITORS

Capacitor Types


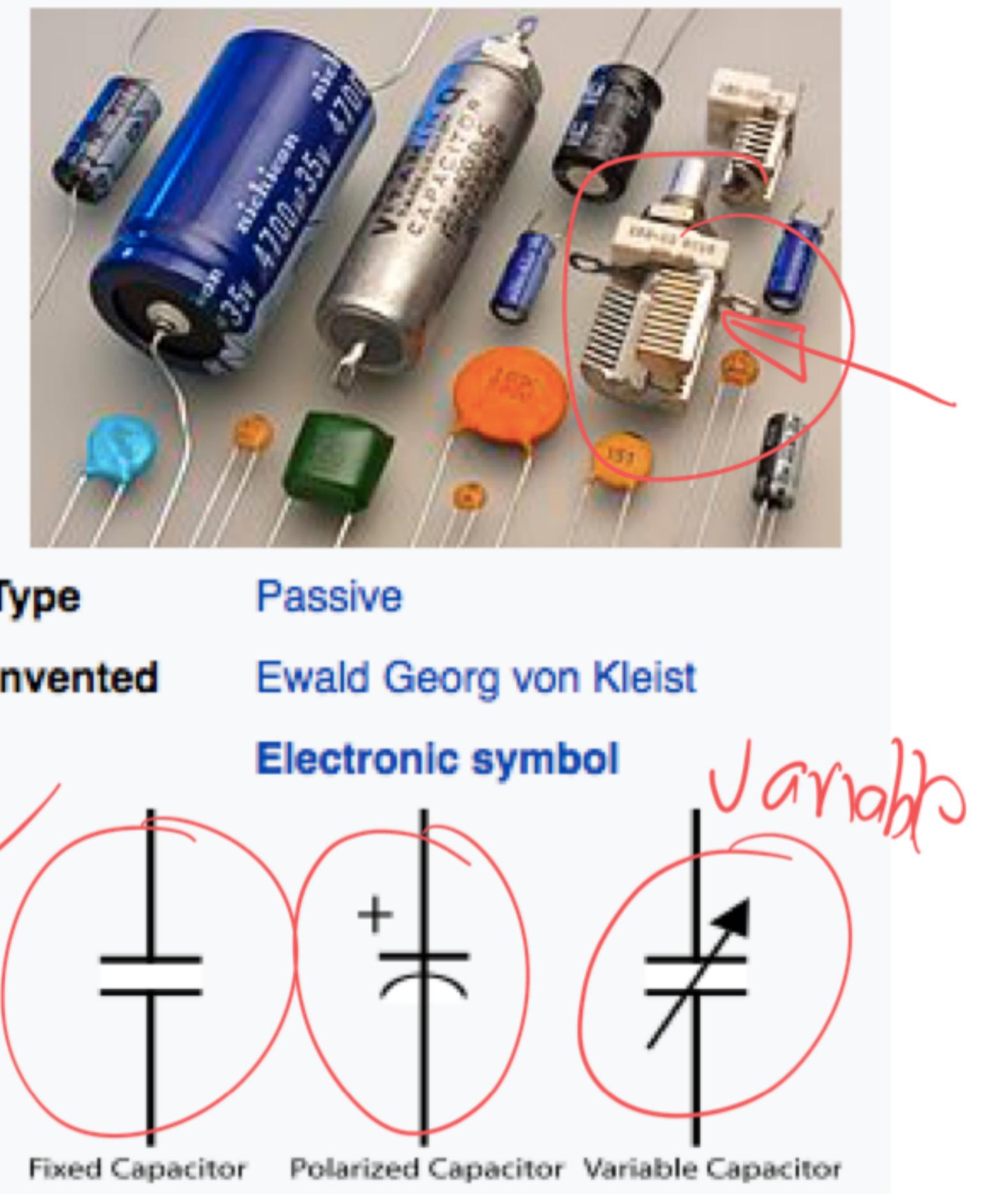
- There are many different types of capacitors
 - Electrolytic, tantalum, ceramic, mica, . . .
- They come in different sizes
 - Larger capacitance
 - Generally larger size
 - Higher voltage compliance
 - Larger size
- Electrolytic have largest cap/volume
 - But they have limited voltage
 - They are polarized
 - One terminal must be + vs. other



http://en.wikipedia.org/wiki/Types_of_capacitor



Gate of MOS Transistor

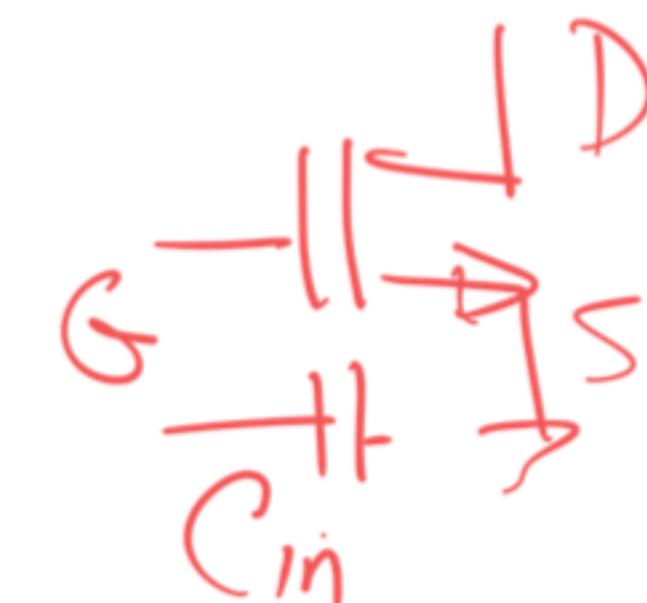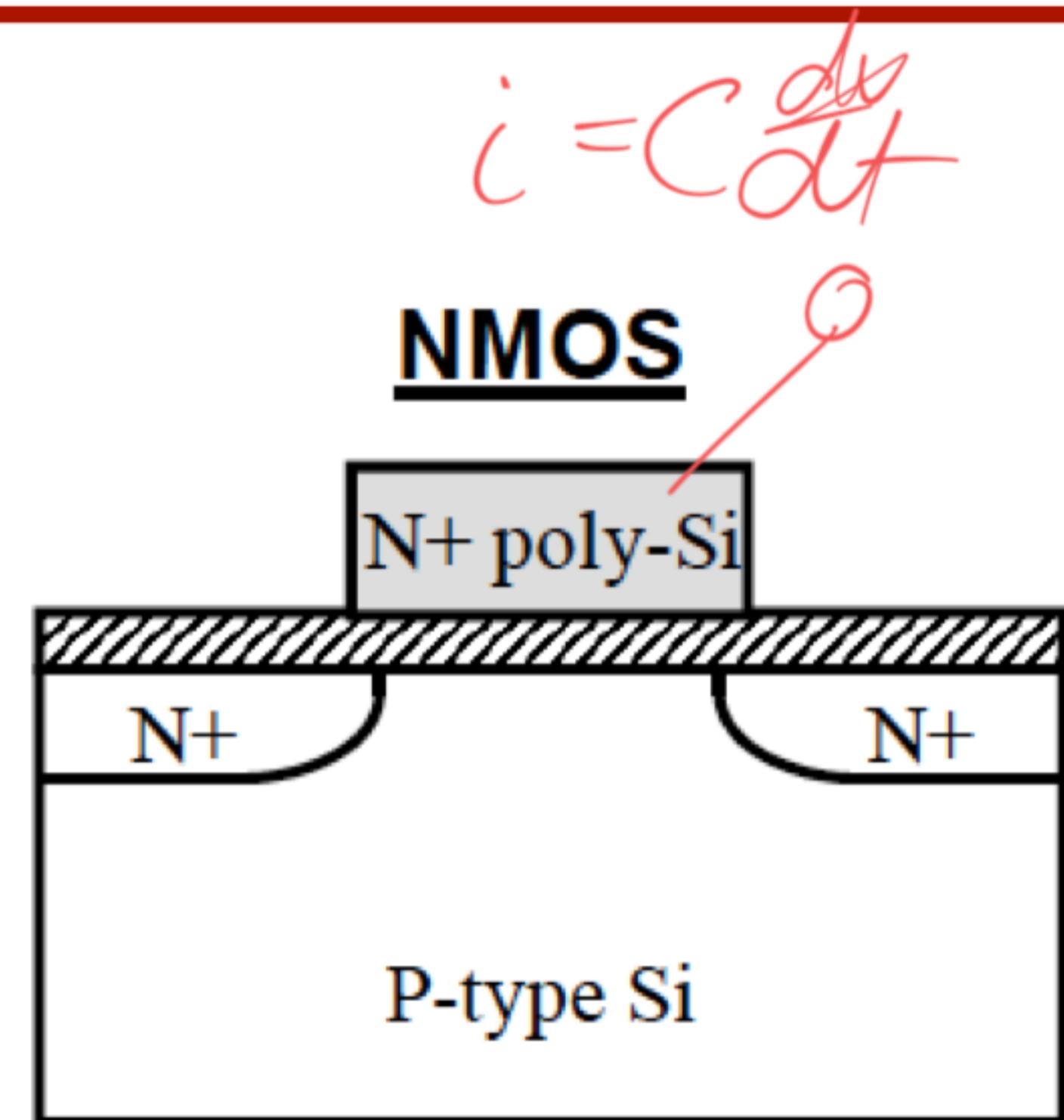
- Is a capacitor between Gate and Source
- To change the gate voltage
 - You need a current pulse (to cause dV/dt)
- If the current is zero (floating)
 - $dV/dt = 0$, and the voltage remains what it was!



All Real Wires Have Capacitance

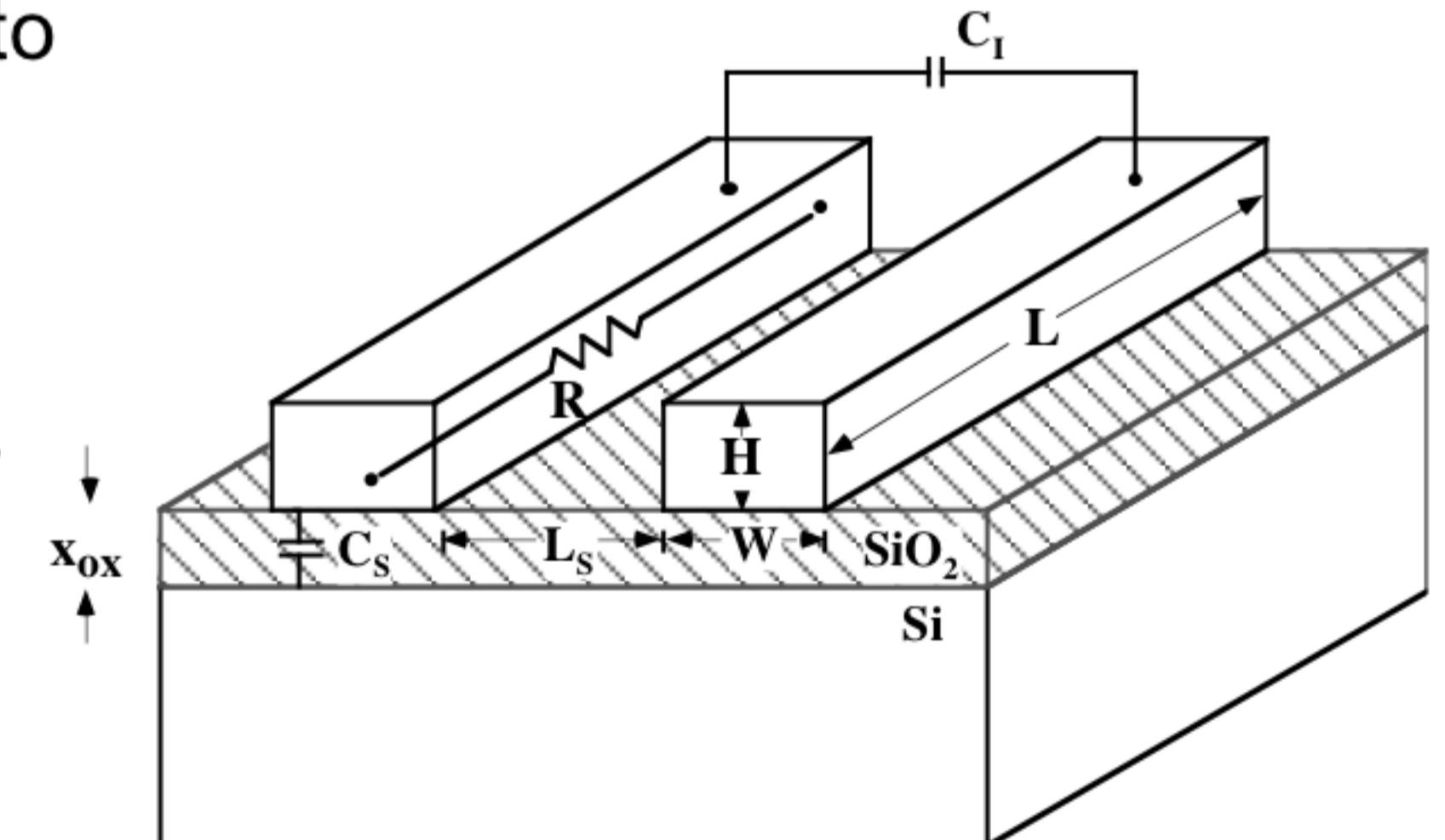
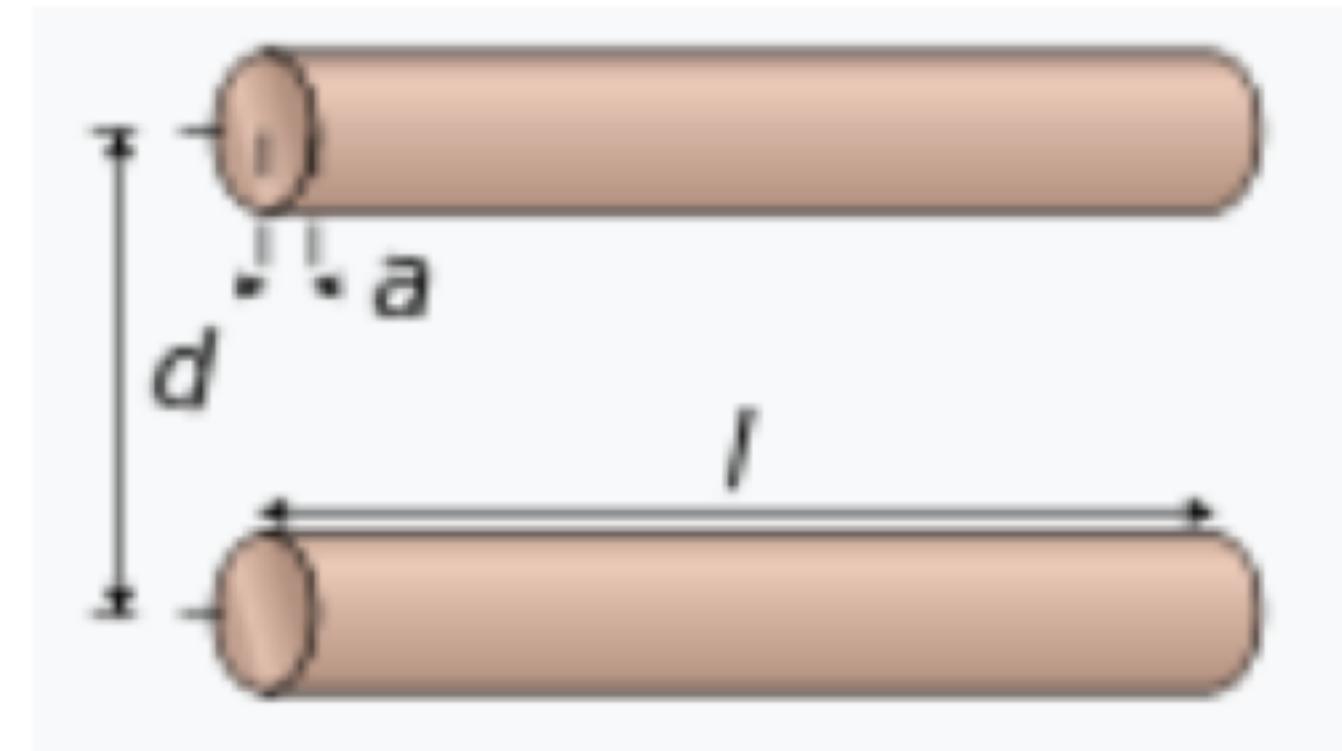
- It will take some charge to change the voltage of a wire
 - Think back to our definition of voltage
 - Potential energy for charge
 - To make a wire higher potential energy
 - Some charge has to flow into the wire, to make the energy higher for the next charge that flows into it
- This capacitance is what sets the speed of your computer
 - And determines how much power it takes!




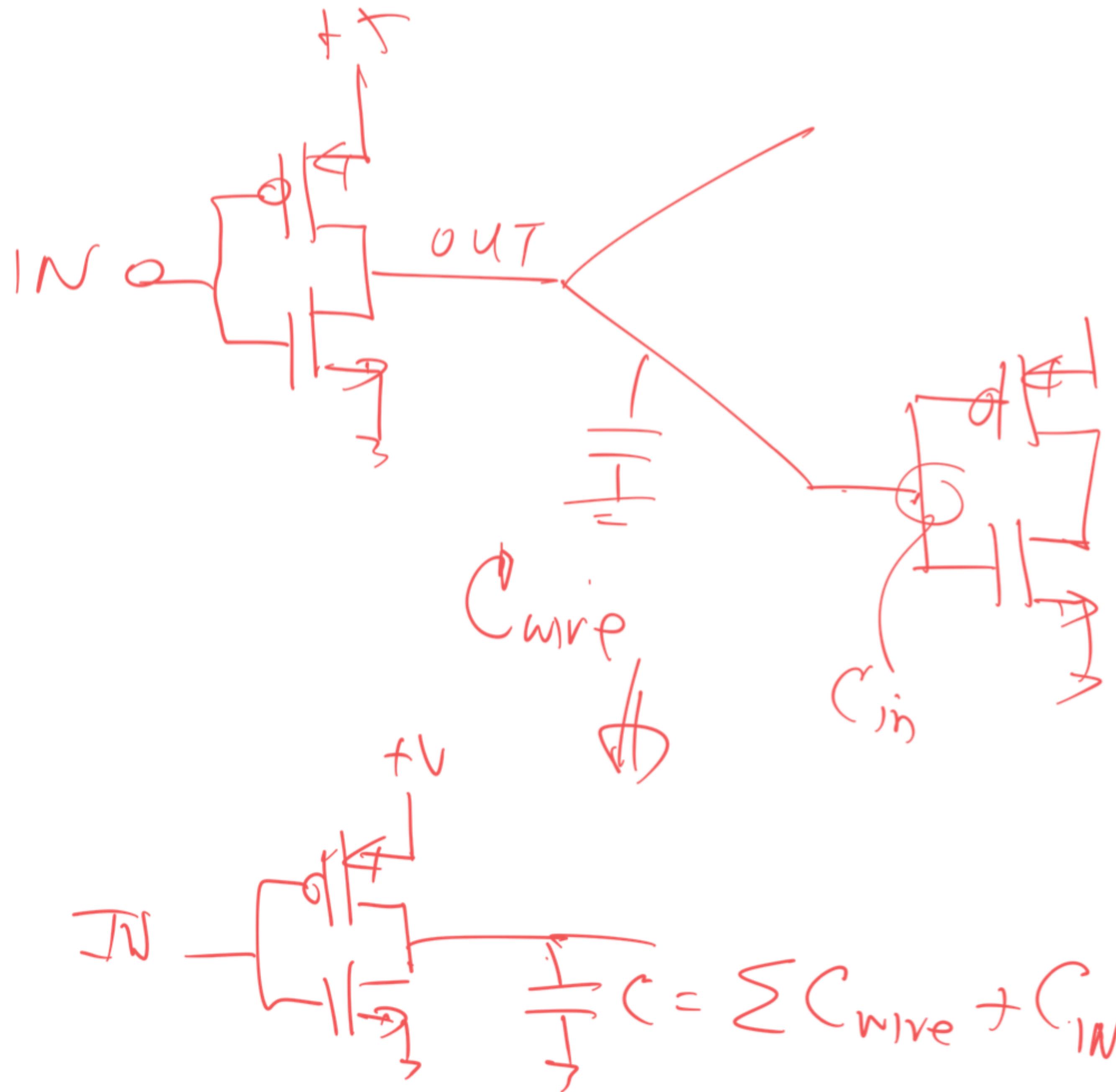


Capacitor Info, If You Know Physics E&M...

- Models the fact that energy is stored in electric fields
 - Between any two wires that are close to each other
- A capacitor is formed by two terminals that are not connected
 - But are close to each other
 - The closer they are, the larger the capacitor
- To create a voltage between the terminals
 - Plus charge is collected on the positive terminal
 - Negative charge is collected on the negative terminal
- This creates an electric field (Gauss's law)
 - Which is what creates the voltage across the terminals
 - There is energy stored in this electric field

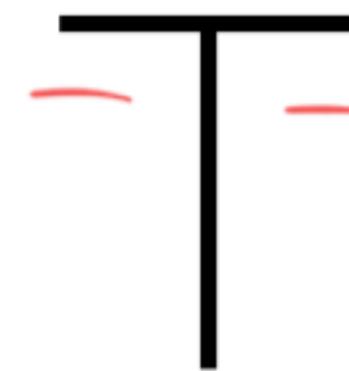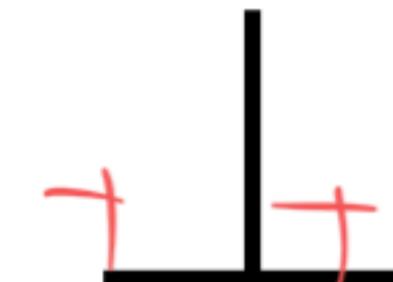

Capacitors in Parallel and Series

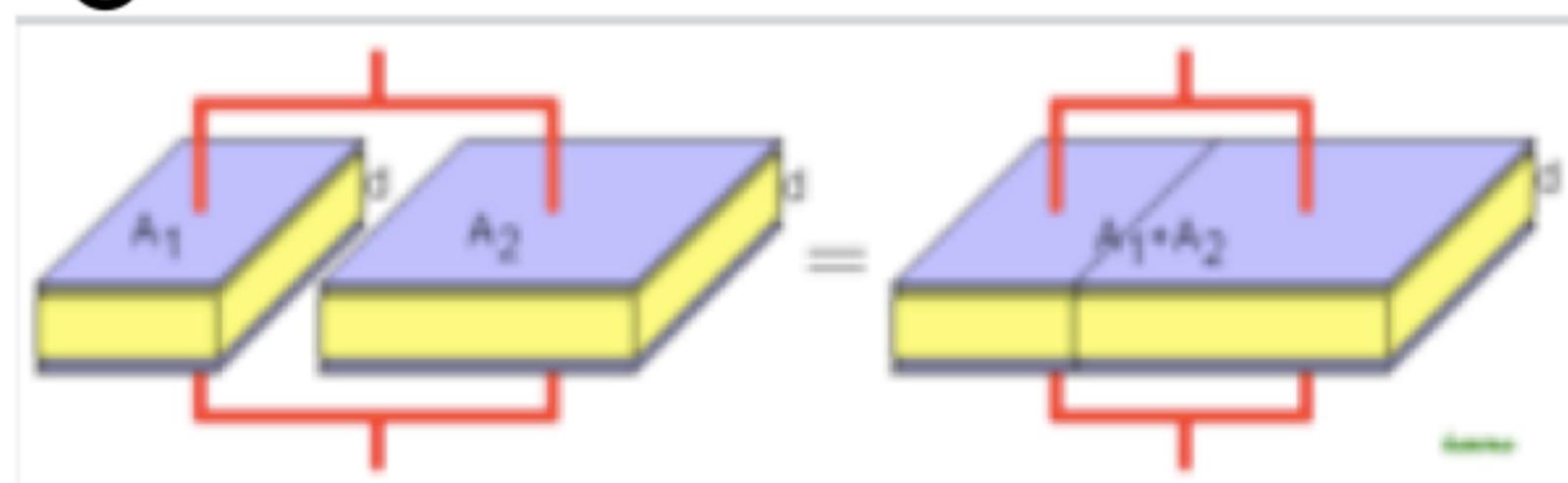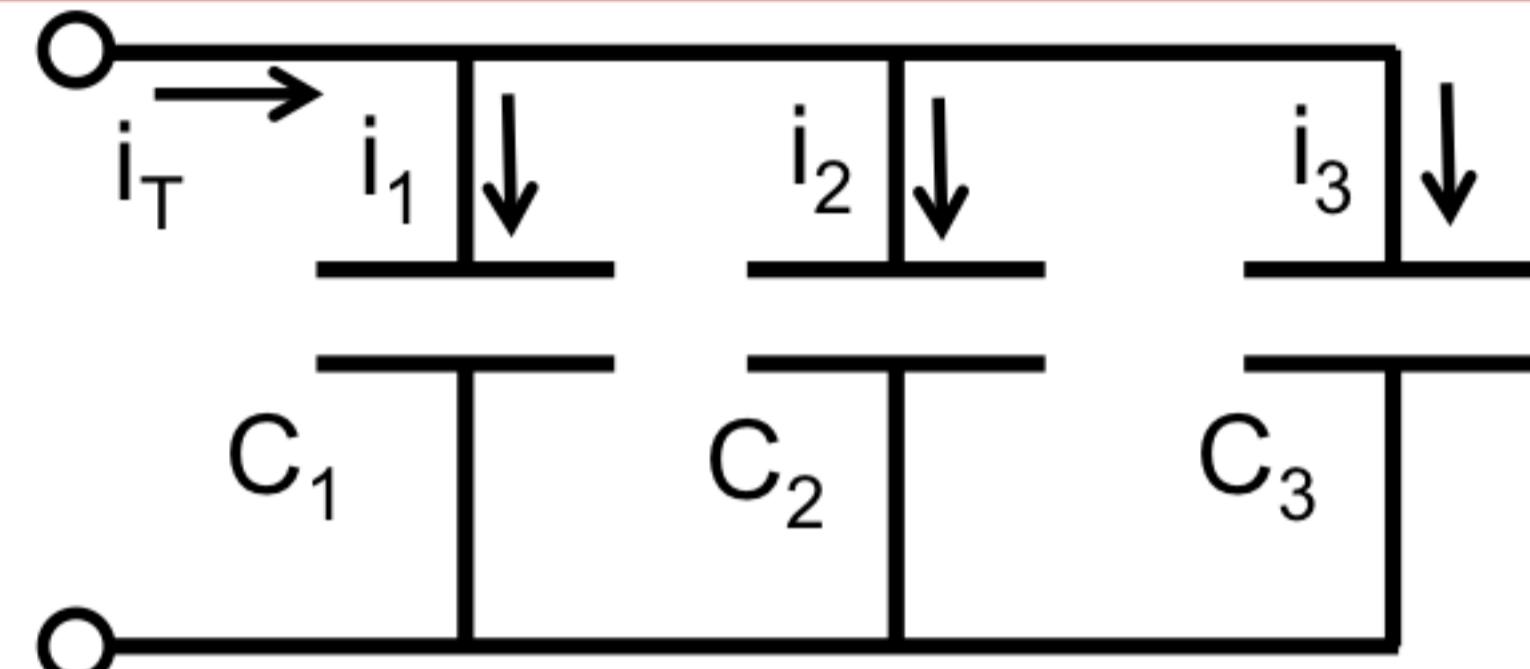

$$C = \frac{\epsilon A}{d}$$

$$\begin{aligned}i_T &= i_1 + i_2 + i_3 = C_1 \frac{dV}{dt} + C_2 \frac{dV}{dt} + C_3 \frac{dV}{dt} \\&= (C_1 + C_2 + C_3) \frac{dV}{dt}\end{aligned}$$


$$\therefore C_{\text{eqv}} = C_1 + C_2 + C_3$$

like $R's$ in series

Capacitors in Parallel and Series

$$C_{\text{eqv}} = \frac{C_1 C_2}{C_1 + C_2}$$

if 2 caps

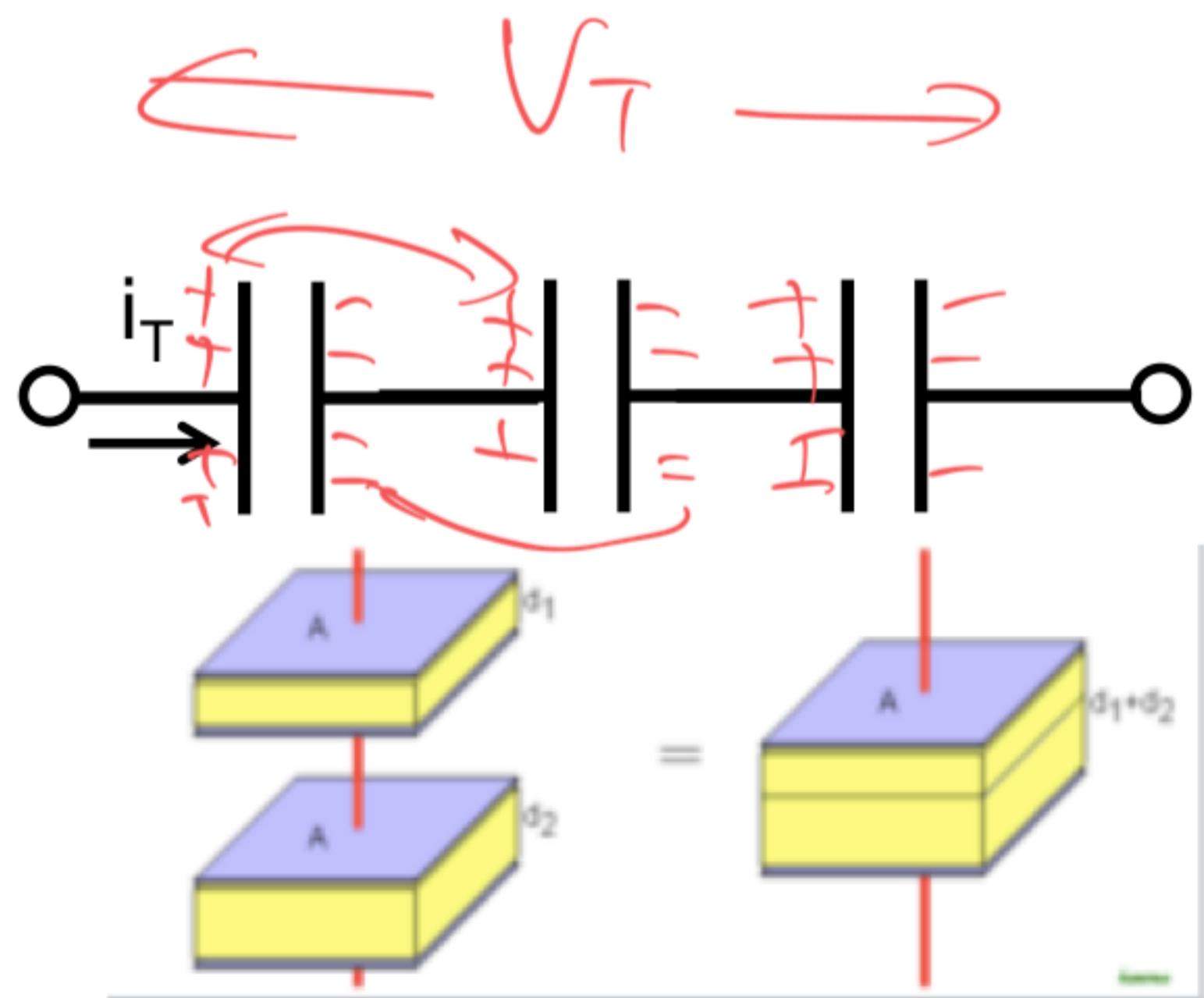


$$V_T = V_1 + V_2 + V_3 = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3} = \frac{Q}{C_{\text{eqv}}}$$

$$\therefore \frac{1}{C_{\text{eqv}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

CAPACITOR RESISTOR CIRCUITS

Capacitors and Logic Gate Speeds

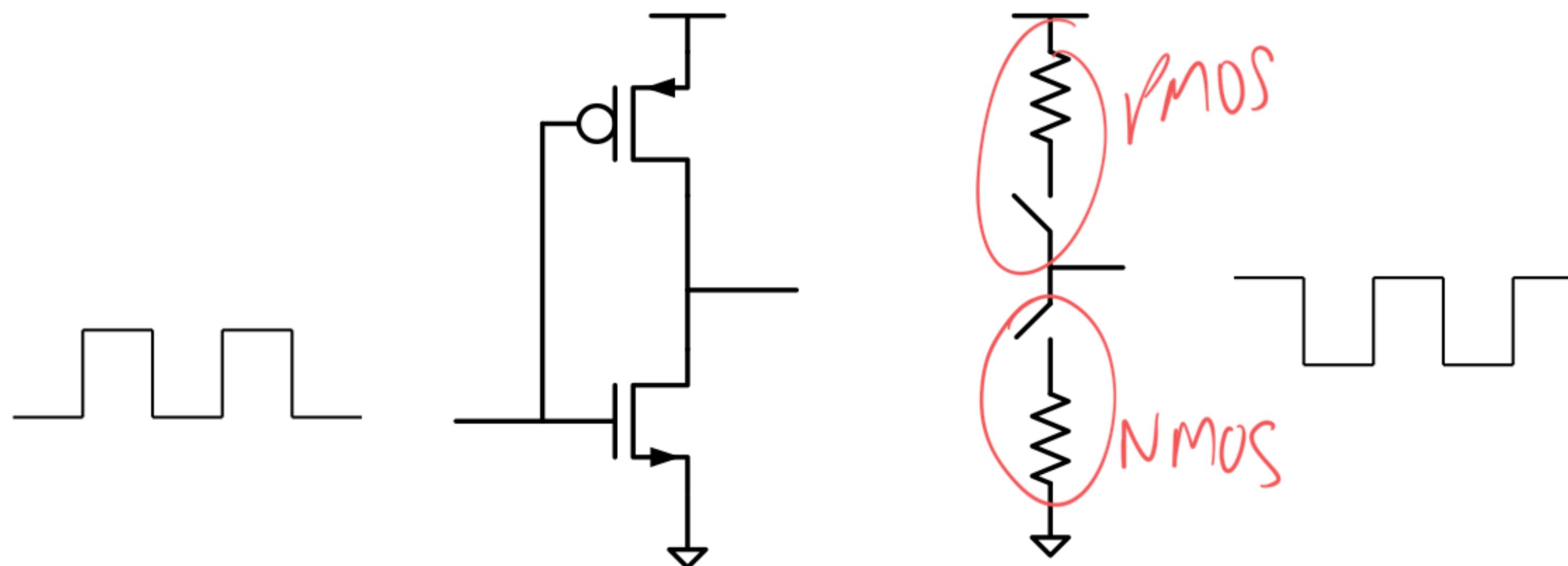- When the input changes from low to high
 - The pMOS turns off, and the nMOS turns on
 - The output goes from high to low
- But in this model
 - The output changes as soon as the input changes




Gates Are NOT Zero Delay

- It would be great if logic gates had zero delay
 - But they don't
- Fortunately, it is easy to figure out the delay of a gate
 - It is just caused by the transistor resistance
 - Which we know about already
 - And the transistor and wire capacitance

Improved Model

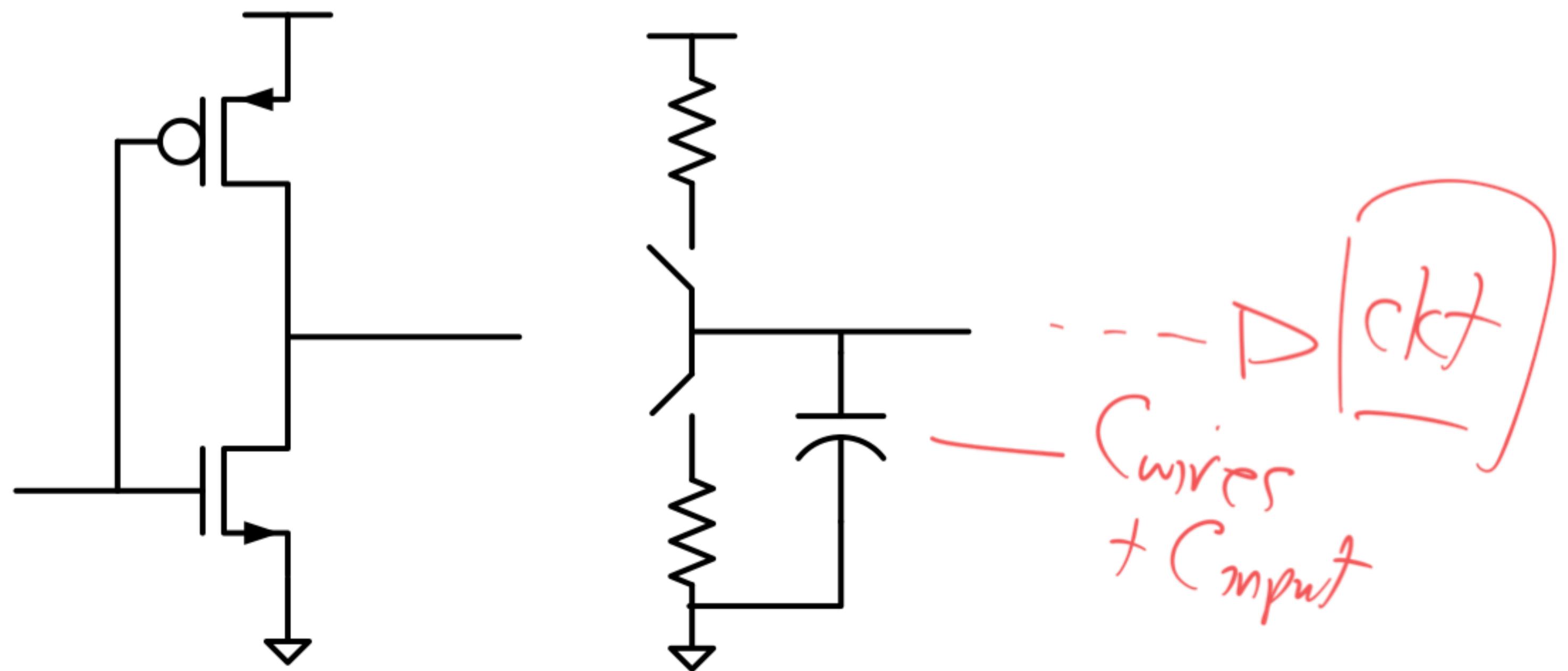- Just add a capacitor to the output node
 - Its value is equal to the capacitance of the gates driven
 - Plus the capacitance of the wire itself



RC Circuit Equation

- When the input to the inverter is low, the output will be at V_{dd}
 - Right after the input rises, here is the circuit


- Want to find the capacitor voltage versus time

- Just write the nodal equations:

- We just have one node voltage, V_{out}
 - $i_{RES} = V_{out}/R_2$
 - $i_{CAP} = CdV_{out}/dt$

- From KCL, the sum of the currents must be zero, so
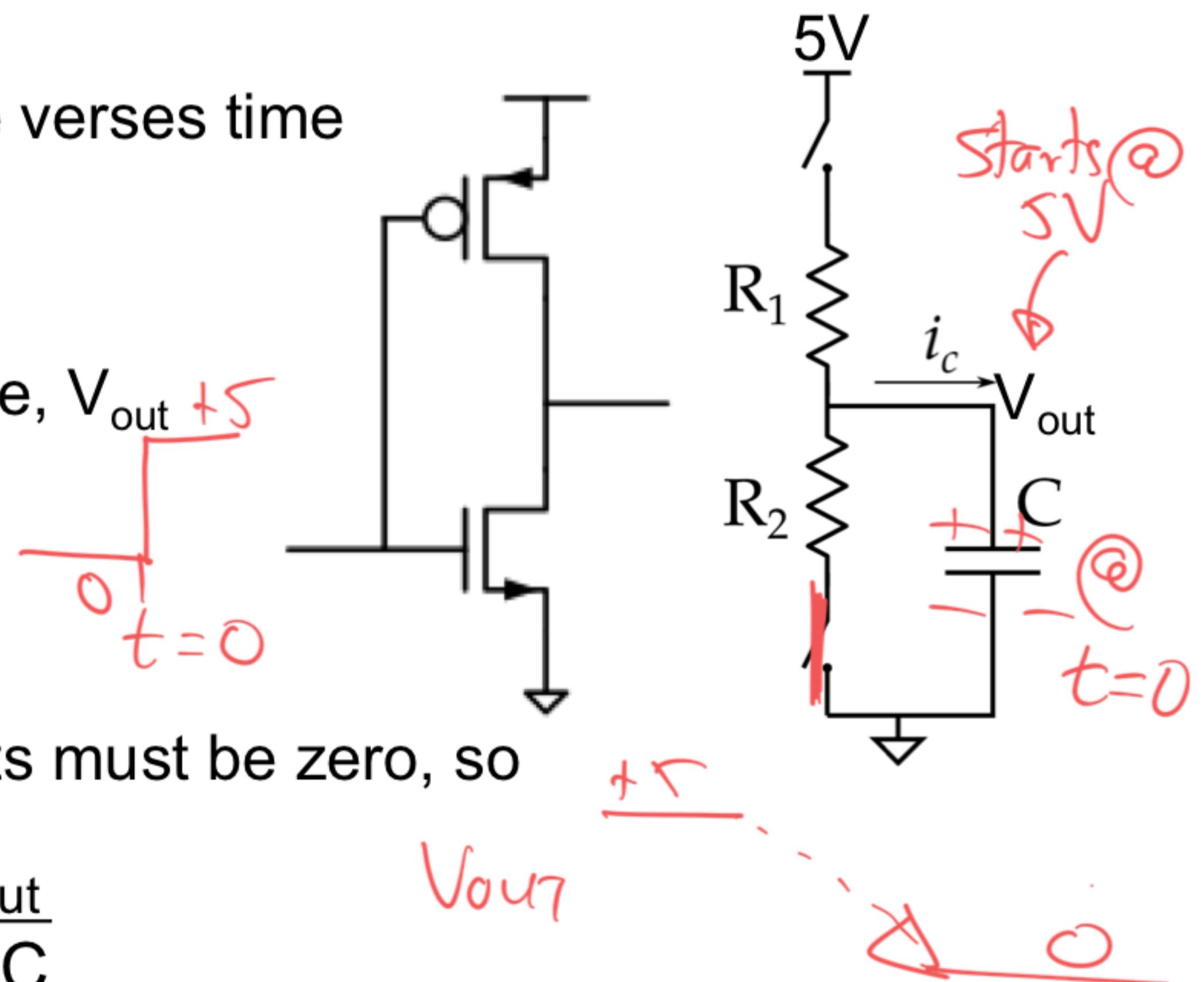
$$\frac{dV_{out}}{dt} = -\frac{V_{out}}{R_2 C}$$




RC Circuit Equations

- Solving,

$$\int \frac{V}{5} \frac{dV_{\text{out}}}{V_{\text{out}}} = - \int_0^t \frac{dt}{R_2 C} \quad \text{so that} \quad \ln(V_{\text{out}}) - \ln(5V) = -\frac{t}{R_2 C}$$

- This is an exponential decay
 - The x axis is in time constants
 - The y axis has been normalized to 1
 - Slope always intersects 0 one tau later ($\tau = RC$)
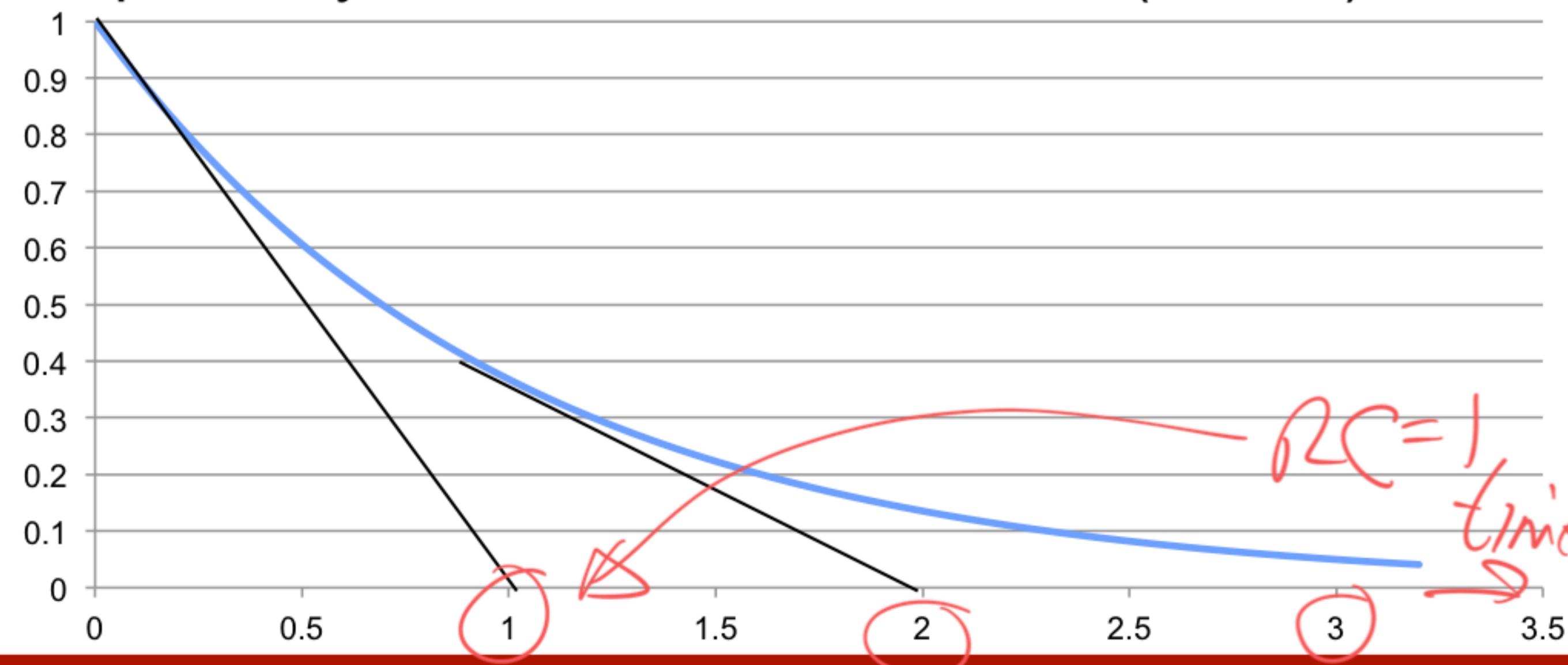
$$\therefore V_{\text{out}} = 5V \left(e^{-t/R_2 C} \right)$$



What Happens When Input Falls?

- Now the voltage across the capacitor starts at 0V

~~A~~ $i = (V_{dd} - V_{out})/R_1$

~~A~~ $dV_{out}/dt = i/C$


$$\frac{dV_{out}}{dt} = \frac{(V_{dd} - V_{out})}{R_1 C}$$


- Not quite the right form

- Need to fix it by changing variables


- Define $V_{new} = V_{dd} - V_{out}$

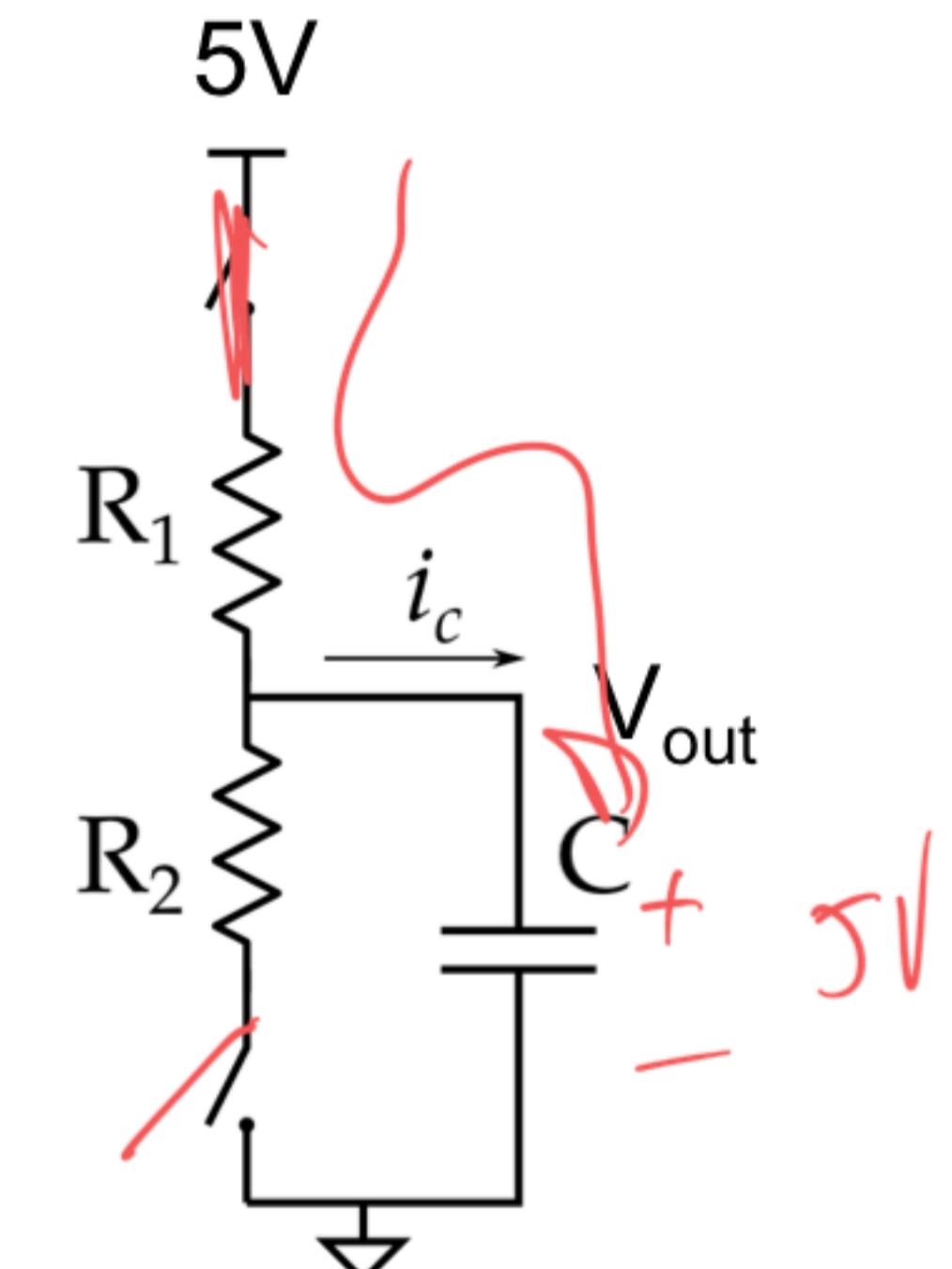- $dV_{out}/dt = -dV_{new}/dt$, since V_{dd} is fixed




$$\int_5^{\frac{V_{new}}{V_{new}}} \frac{dV_{new}}{V_{new}} = - \int_0^t \frac{dt}{R_1 C} \text{ so that } \ln\left(\frac{V_{new}}{5}\right) = -\frac{t}{R_1 C} \therefore V_{out} = 5V \left(1 - e^{-t/R_1 C}\right)$$

RC Circuits in the Time Domain

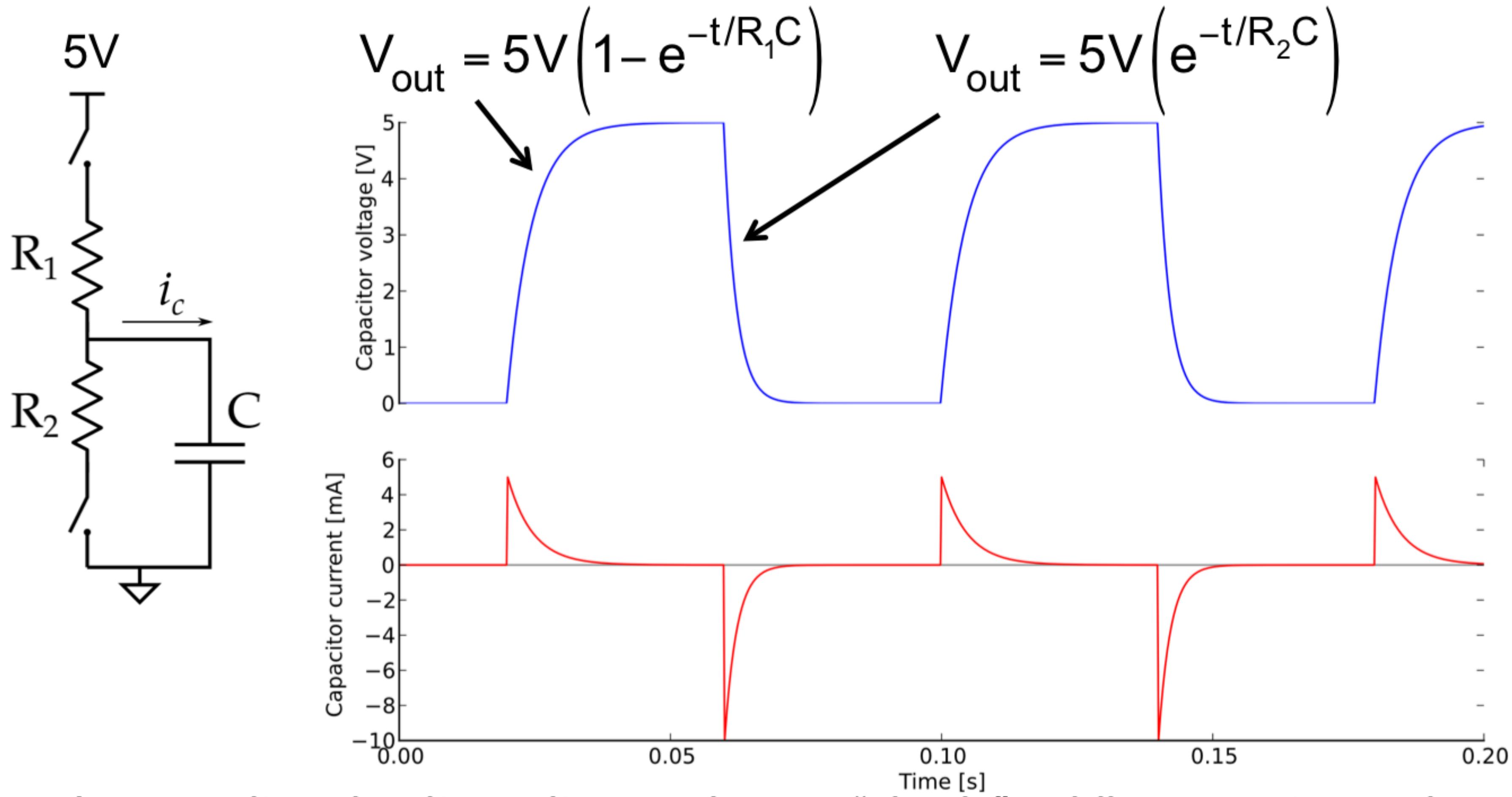



In capacitor circuits, voltages change “slowly”, while currents can be instantaneous.

Simple RC Circuit Demo

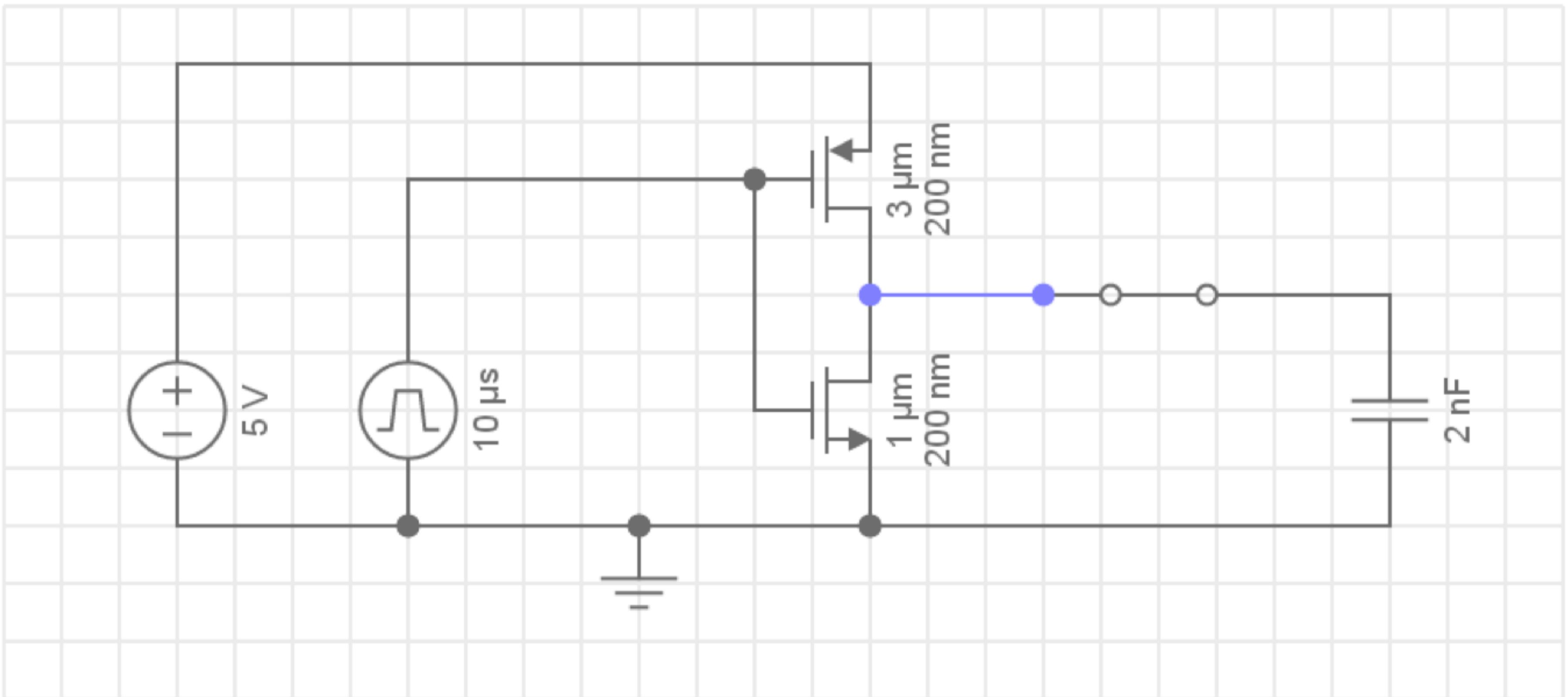


EveryCircuit Demo – CMOS Inverter

Interesting Aside

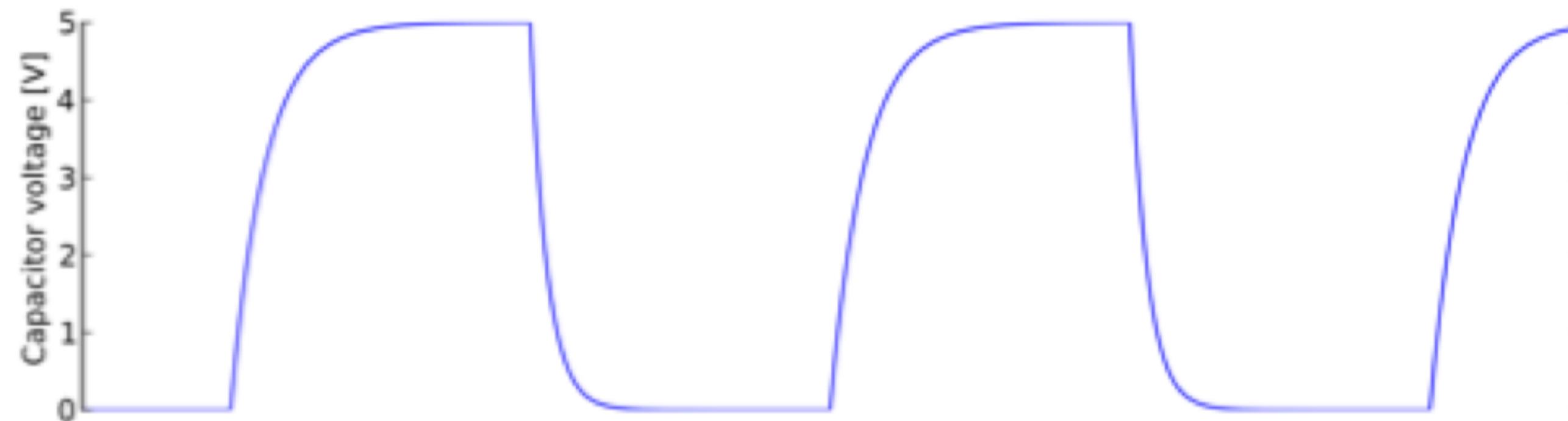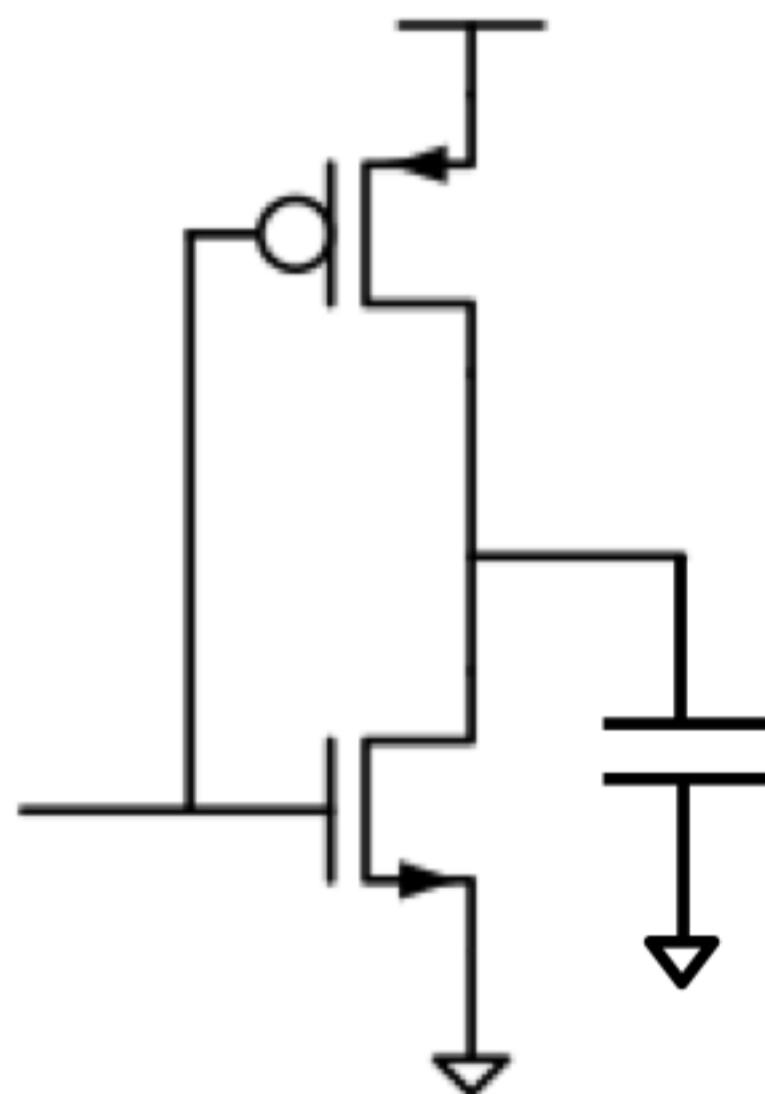

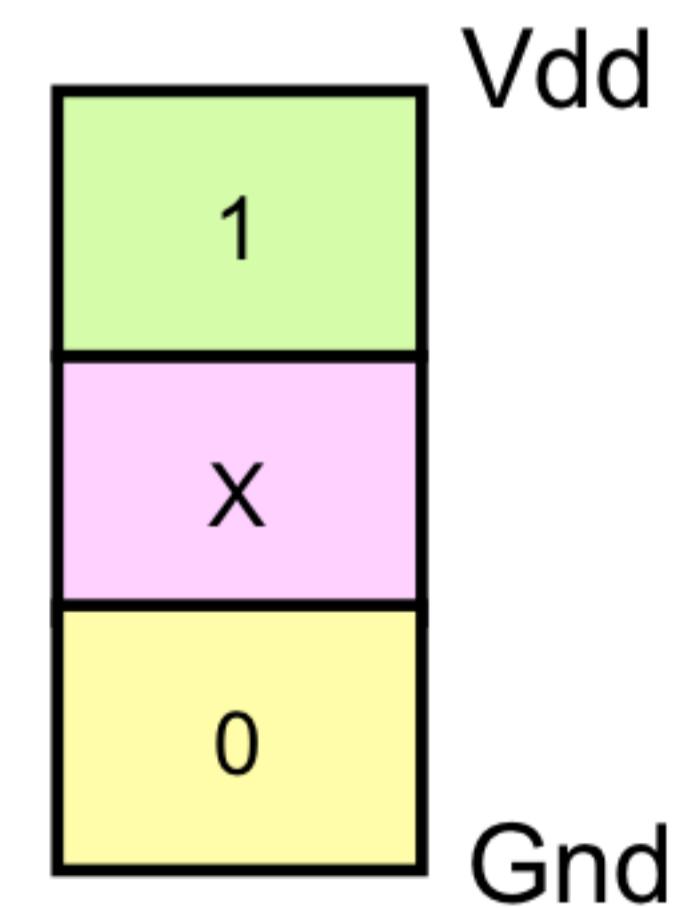- Exponentials “never” reach their final value
- So if this logic gate is driving another gate, when does the next gate think its input is 0 or 1?
- This is one of the reasons why logic levels are defined as a range of values.



Learning Objectives

- Understand what a capacitor is
 - $i=C \frac{dV}{dt}$
 - It is a device that tries to keep voltage constant
 - Will supply current (in either direction) to resist voltage changes
- Understand how voltages and current change in R C circuits
 - Voltage waveforms are continuous
 - Takes time for their value to change
 - Exponentially decay to final value (the DC value of circuit)
 - Currents can change abruptly