
E40M


Bode Plots, dB

Reading

- Reader
 - 7.1-7.2 – Bode Plots


EKG Lab

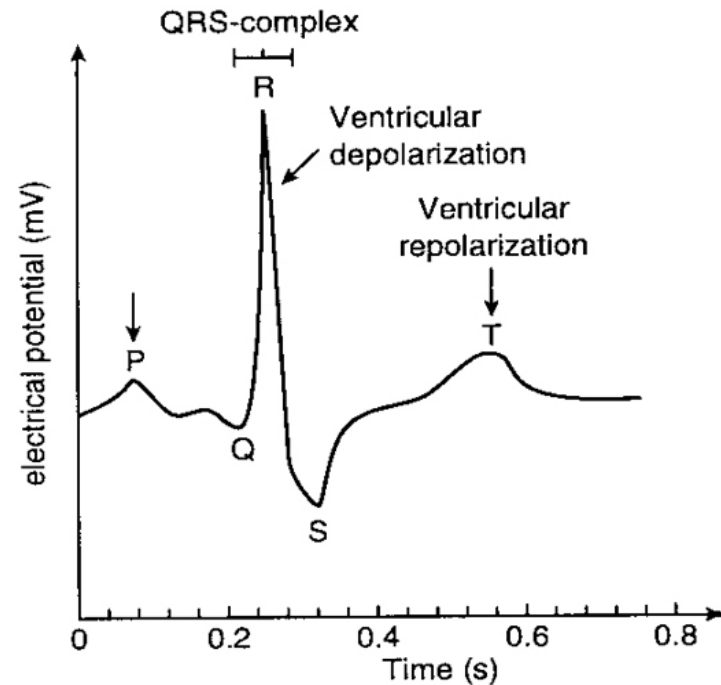- Concepts
 - Amplifiers
 - Impedance
 - Noise
 - Safety
 - Filters
- Components
 - Capacitors
 - Inductors
 - Instrumentation and Operational Amplifiers




In this project we will build an electrocardiogram (ECG or EKG). This is a noninvasive device that measures the electrical activity of the heart using electrodes placed on the skin.

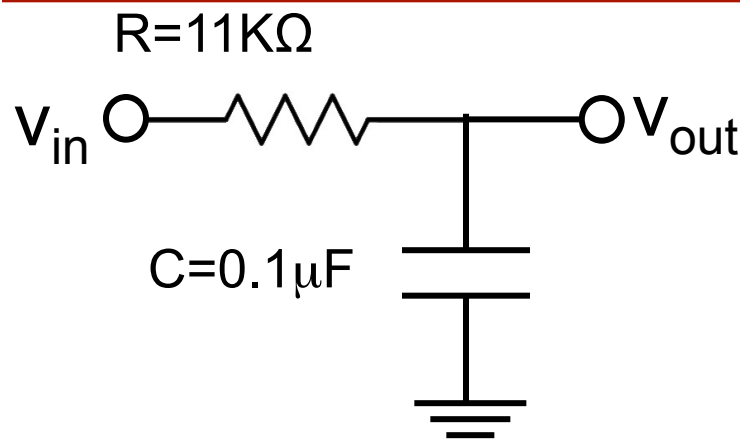Analyzing RC Circuits Using Impedance – Review (Low Pass Filter)




$$\frac{V_{out}}{V_{in}} = \frac{1}{R + \frac{1}{j*2\pi FC}} = \frac{1}{1 + j*2\pi FRC}$$

Gain vs. Freq

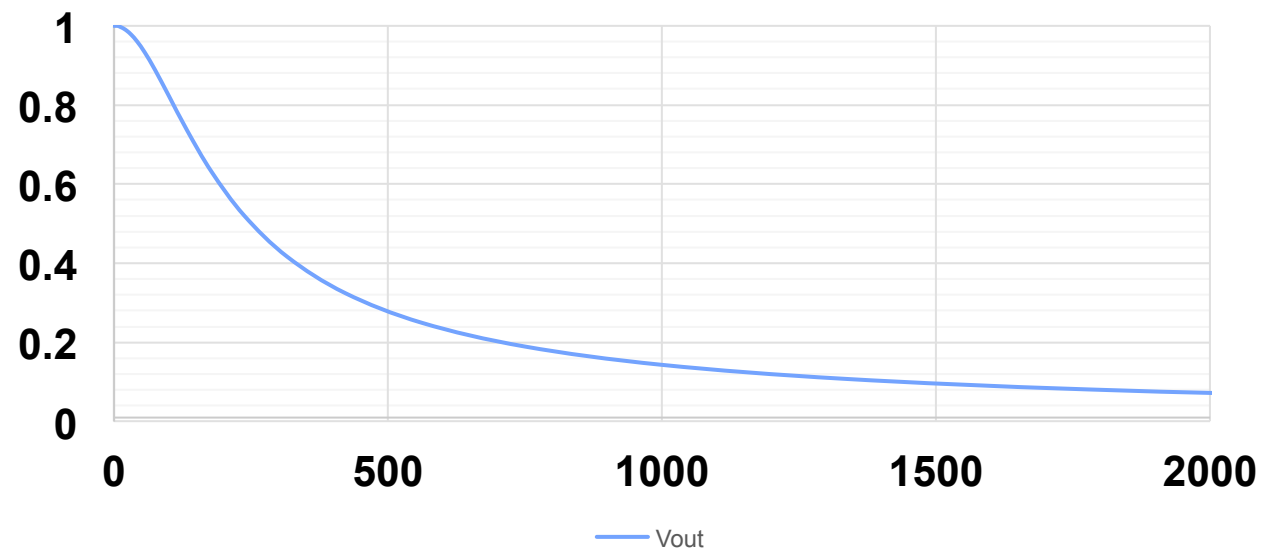

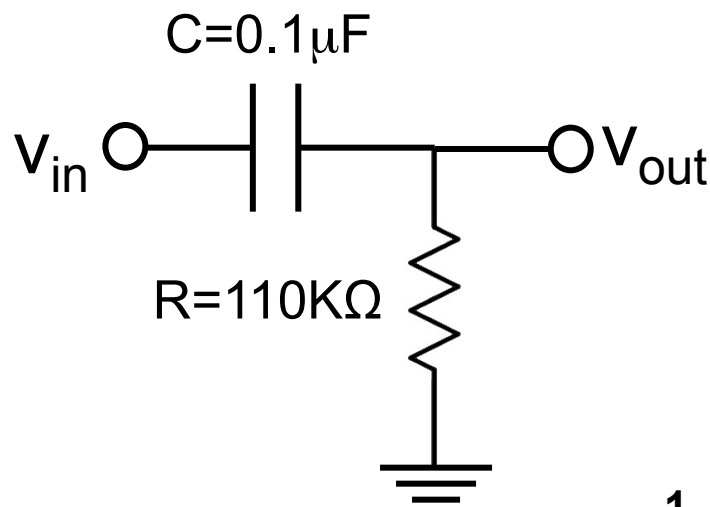
Analyzing RC Circuits Using Impedance – Review (High Pass Filter)




$$\frac{V_{out}}{V_{in}} = \frac{R}{R + \frac{1}{j * 2\pi FC}} = \frac{j * 2\pi FRC}{1 + j * 2\pi FRC}$$

$RC = 11 \text{ ms}$; $2\pi RC$ is about 70 ms

Gain vs. Freq

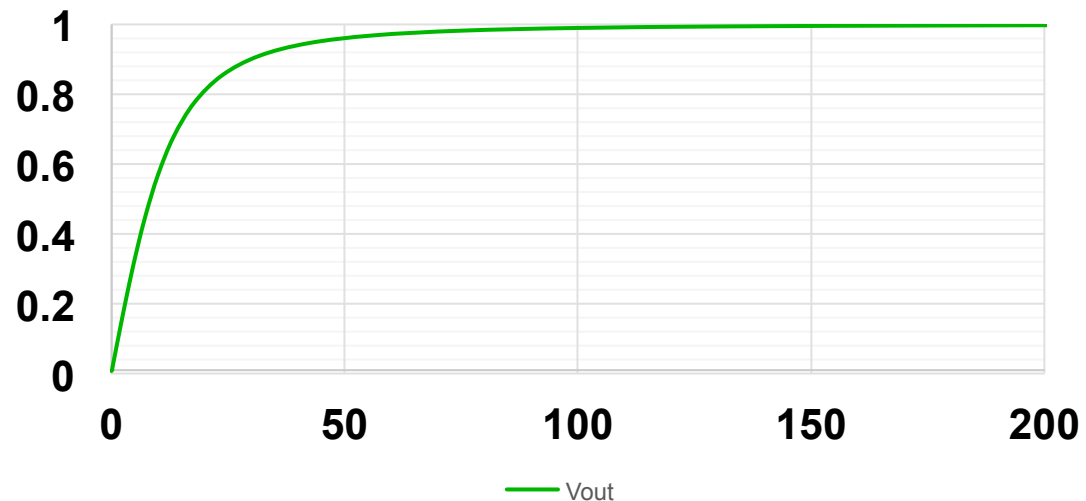


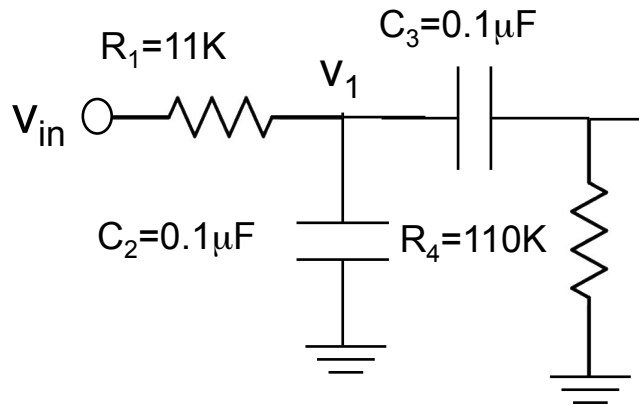Analyzing RC Circuits Using Impedance – Review (Band Pass Filter)



$$\frac{V_{out}}{V_{in}} = \frac{j * 2\pi F R_4 C_3}{1 + j * 2\pi F (R_4 C_3 + R_1 C_2 + R_1 C_3) + (j * 2\pi F)^2 R_1 C_2 R_4 C_3}$$

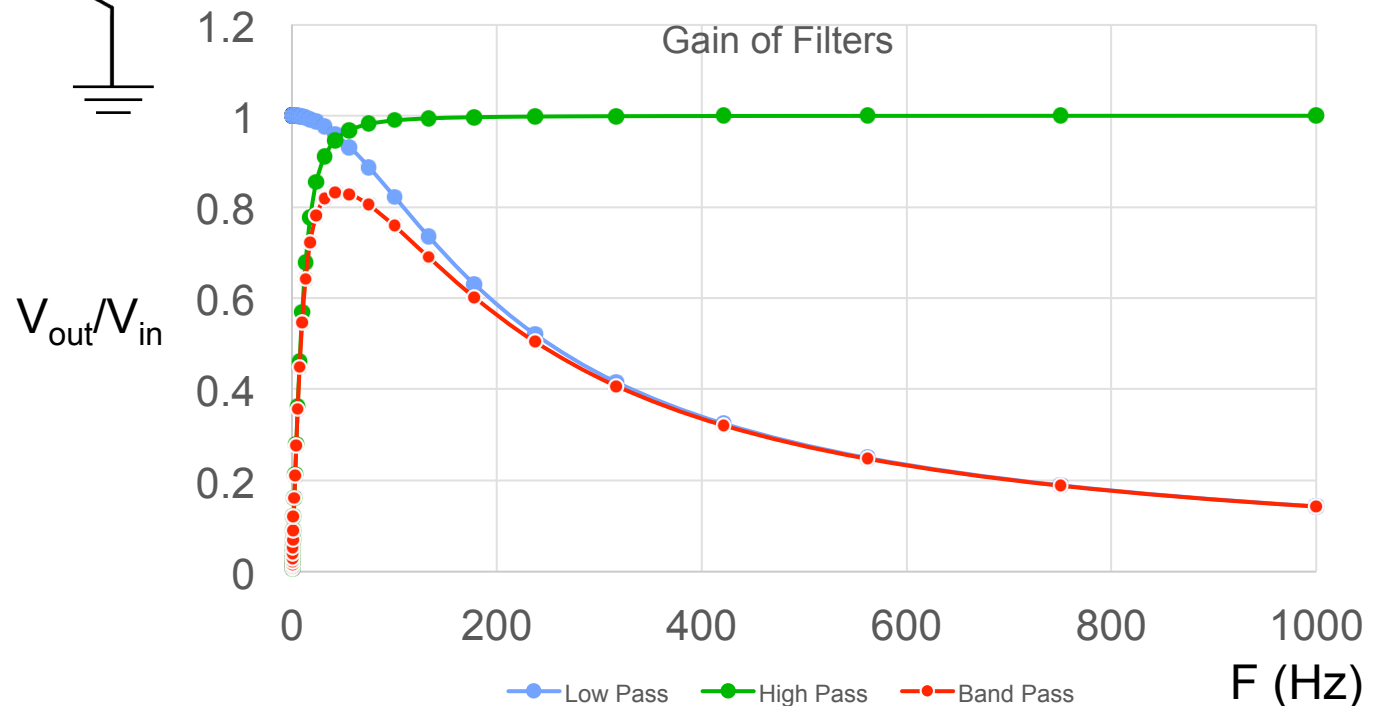
- We'll use a filter that operates like this in the ECG lab project.



BODE PLOTS


Our Plots Are Not Very Good

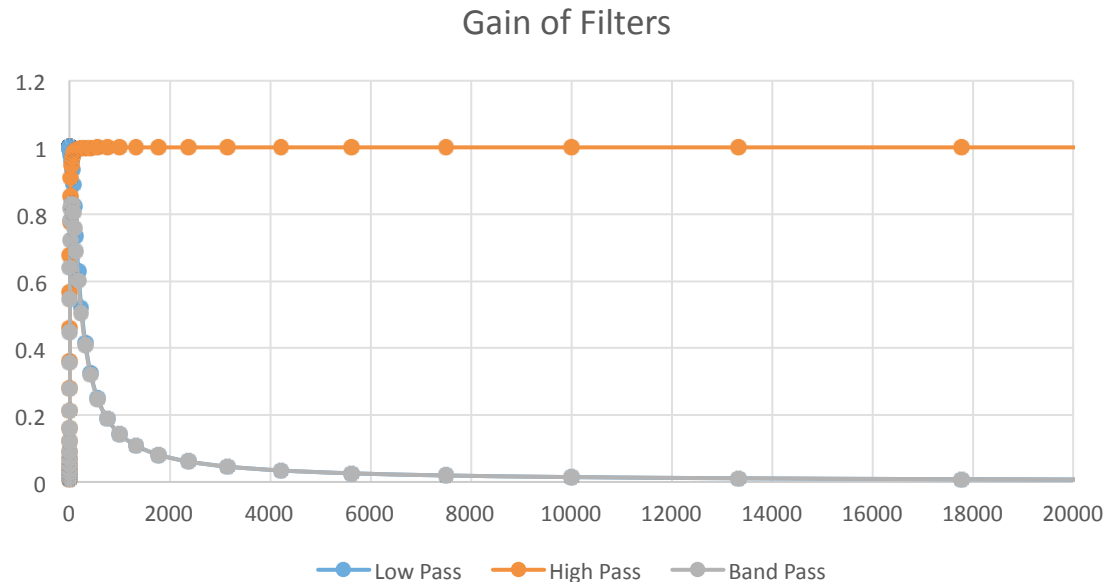- Most of the plot is for the “high frequency”
 - Your ear is very interested in each octave (2x) in freq
 - If you plot the full audio spectrum (20-20kHz)
 - 50% of the plot will be from 10-20kHz
 - And that is only one octave of ten!
 - You won't be able to see the first five octaves!




More Plot Issues

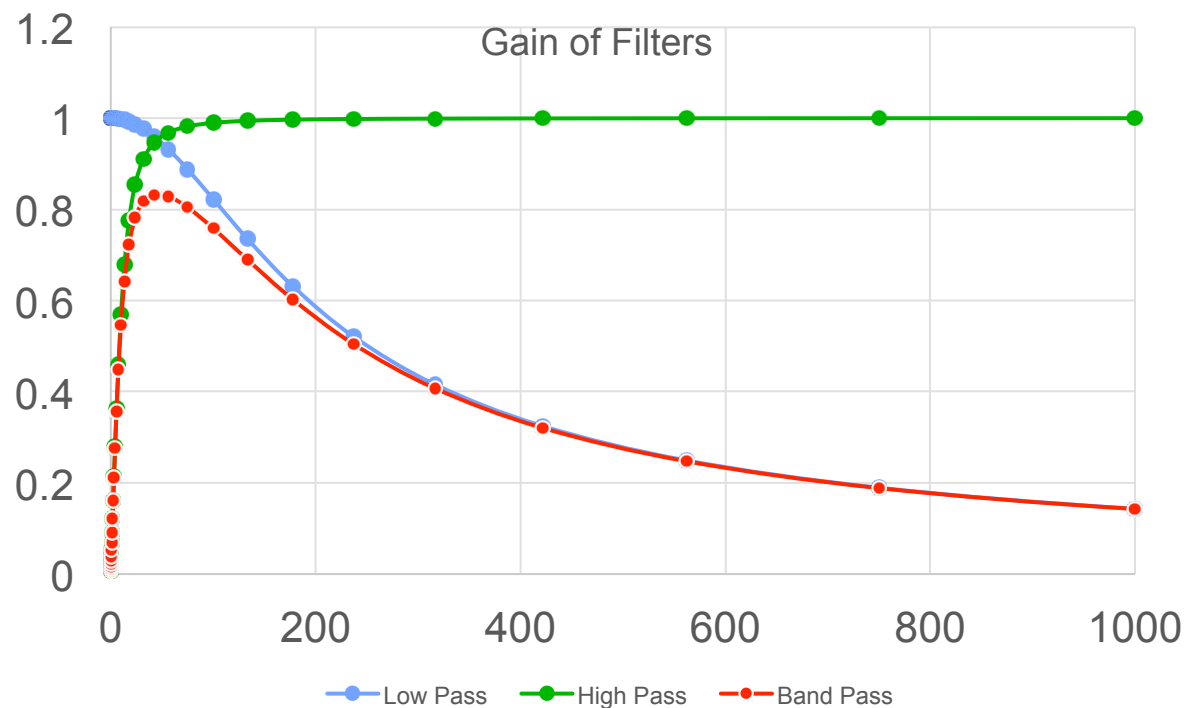- The plots usually are proportional to:
 - Constant, or F or F^{-1} or F^2 or F^{-2}
 - It would be great if these were easy to see on a plot




There is an Easy Way to Fix Both Issues

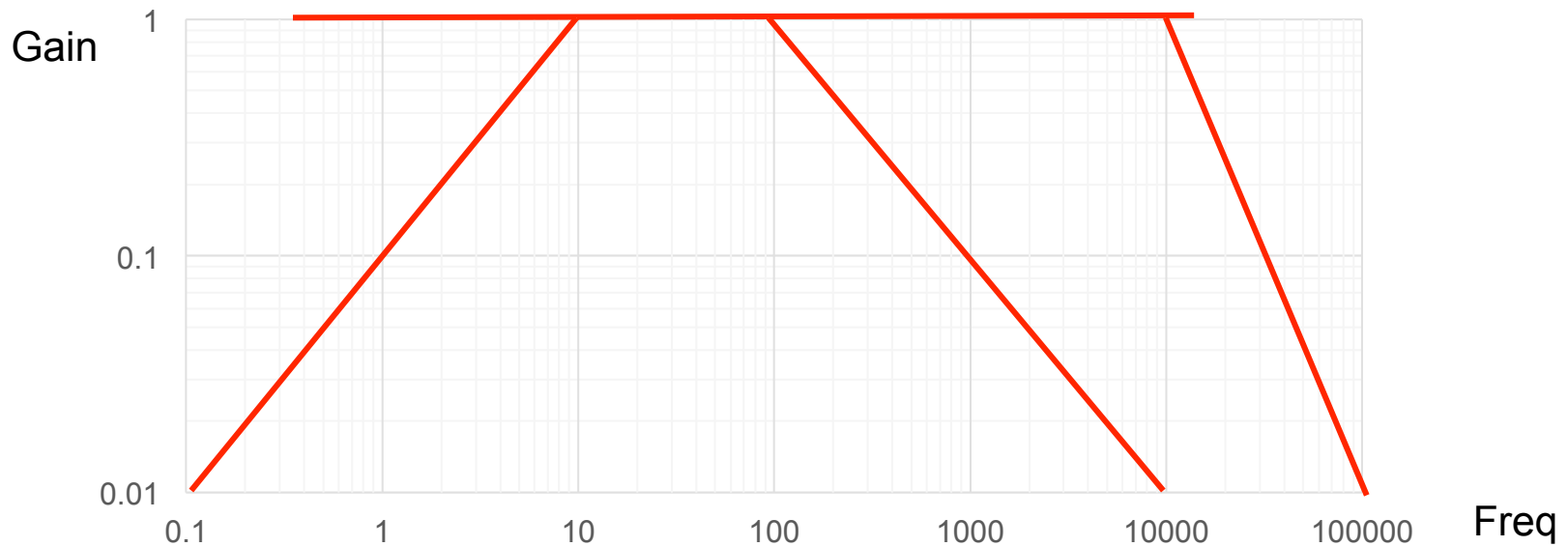- Use a log-log plot
 - That is plot the $\log(\text{Gain})$ vs $\log(F)$
 - Usually labeled with Gain and F
 - But the spacing between numbers is their log
- Any power of F is a straight line $\log(F^n) = n * \log(F)$
So the slope of the line is the power of F





Example – Low Pass Filter

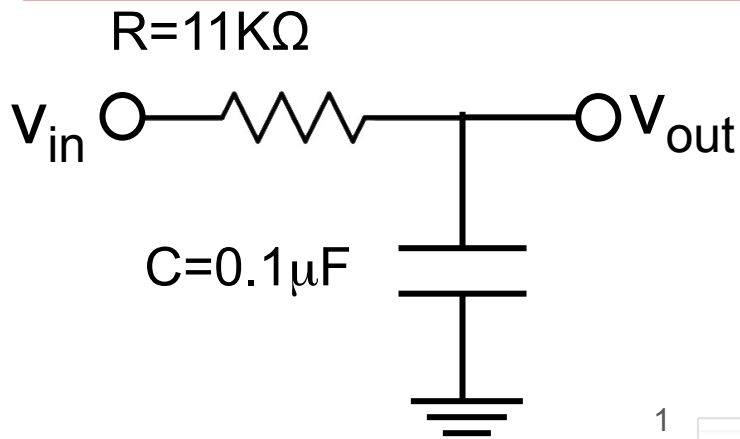


$$\frac{V_{out}}{V_{in}} = \frac{1}{R + \frac{1}{j * 2\pi FC}} = \frac{1}{1 + j * 2\pi FRC} = \frac{1}{1 + jF / F_c}$$

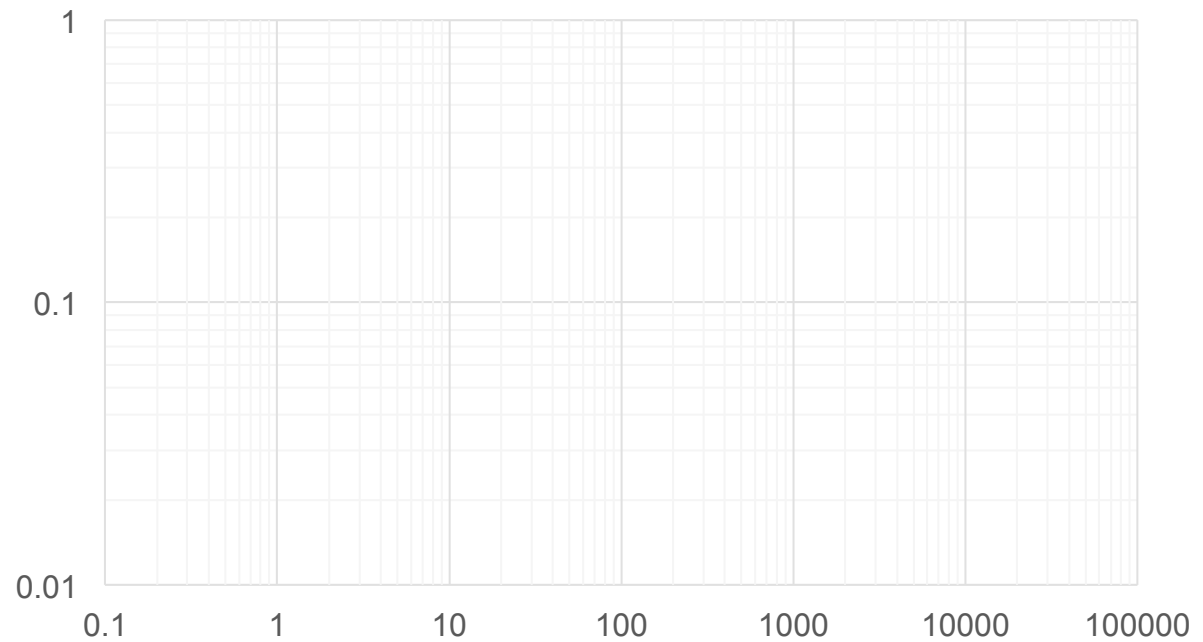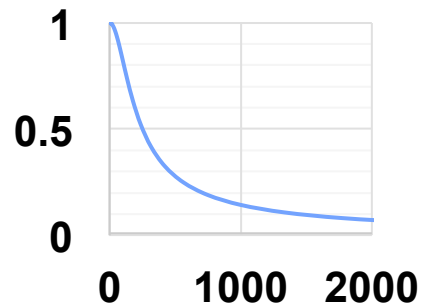$2\pi RC$ is about 7ms; $F_c = 140\text{Hz}$





Low Pass

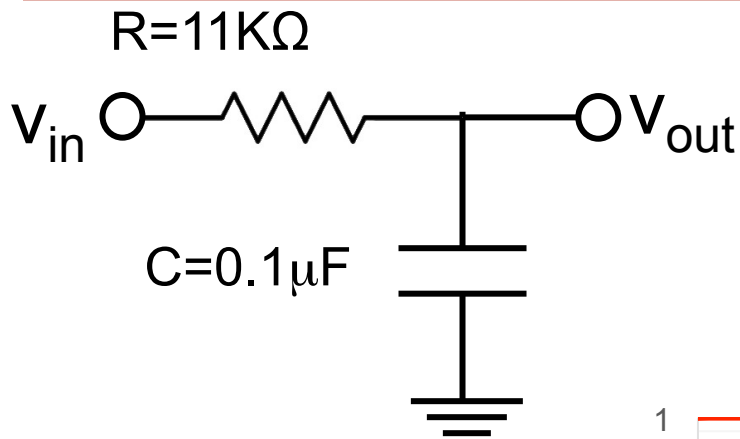


$$\frac{V_{out}}{V_{in}} = \frac{1}{R + \frac{1}{j * 2\pi FC}} = \frac{1}{1 + j * 2\pi FRC} = \frac{1}{1 + jF / F_c}$$

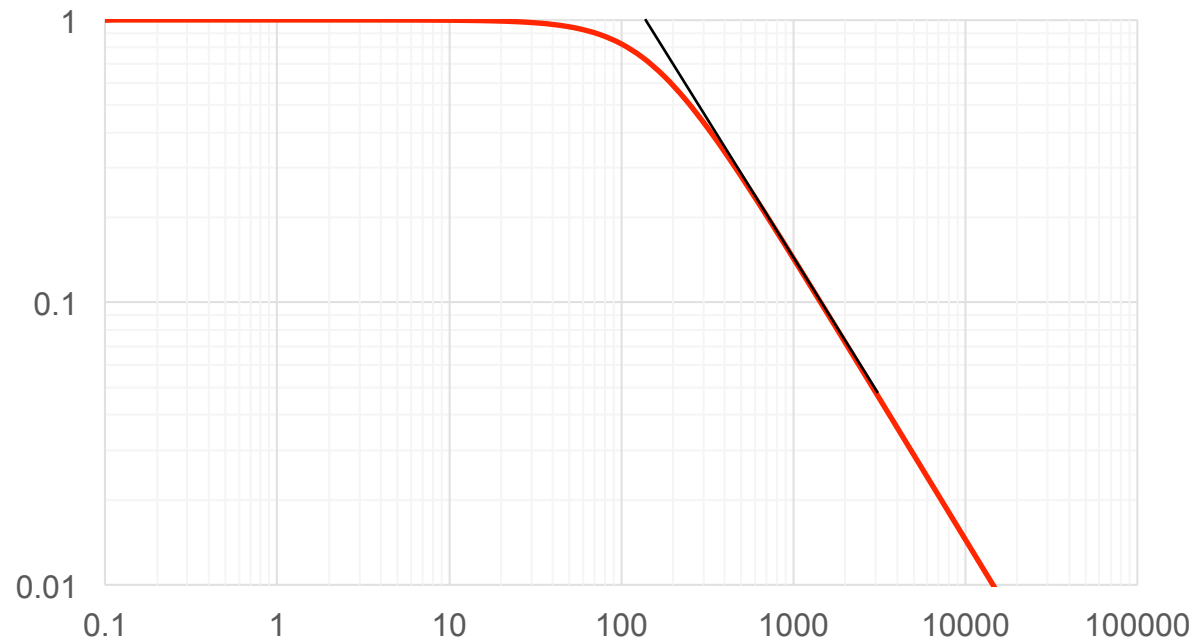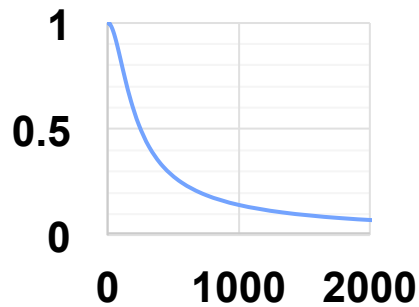$2\pi RC$ is about 7ms; $F_c = 140\text{Hz}$





High-Pass



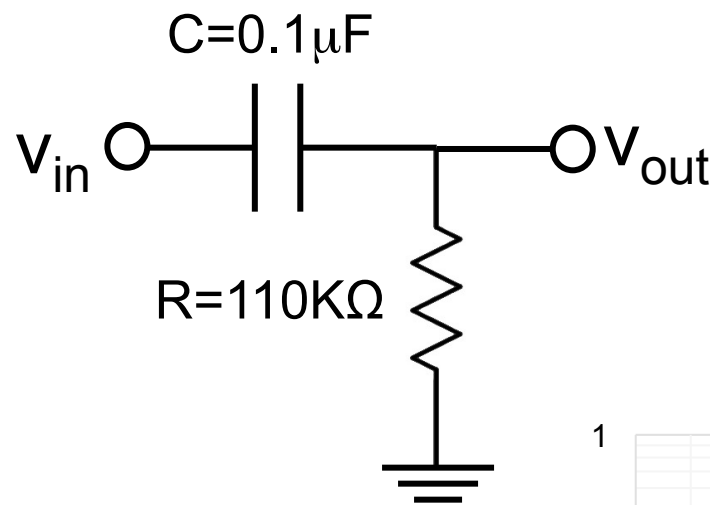


$$\frac{V_{out}}{V_{in}} = \frac{R}{R + \frac{1}{j*2\pi FC}} = \frac{j*2\pi FRC}{1 + j*2\pi FRC}$$

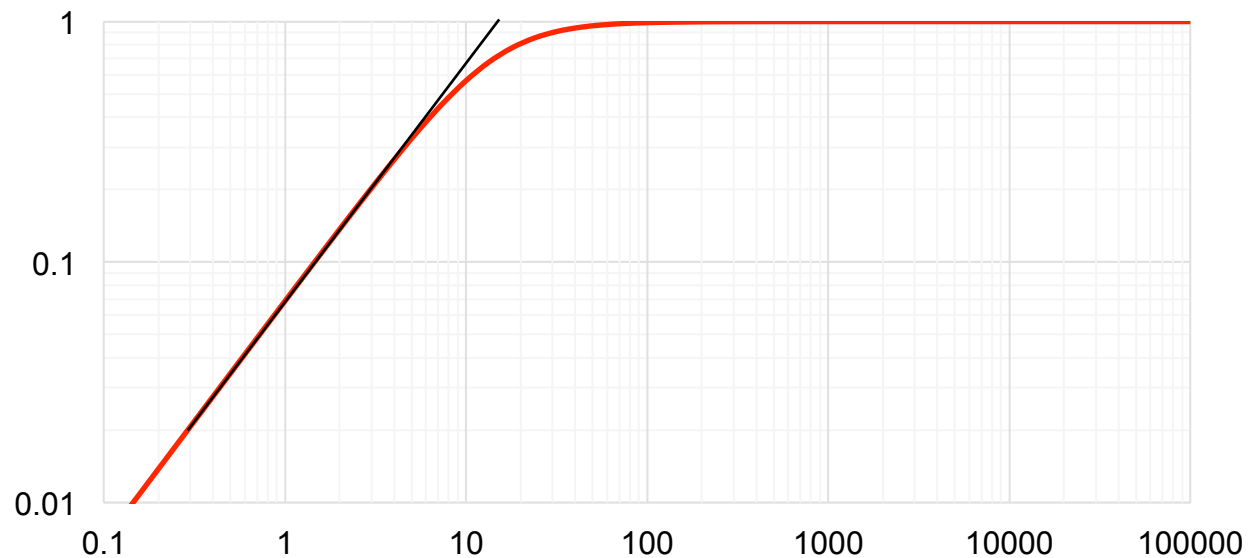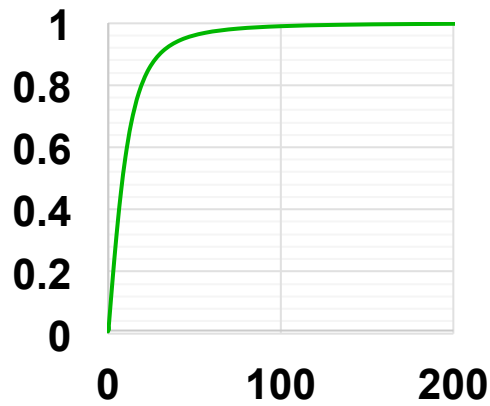$2\pi RC$ is about 70ms; $F = 14\text{Hz}$



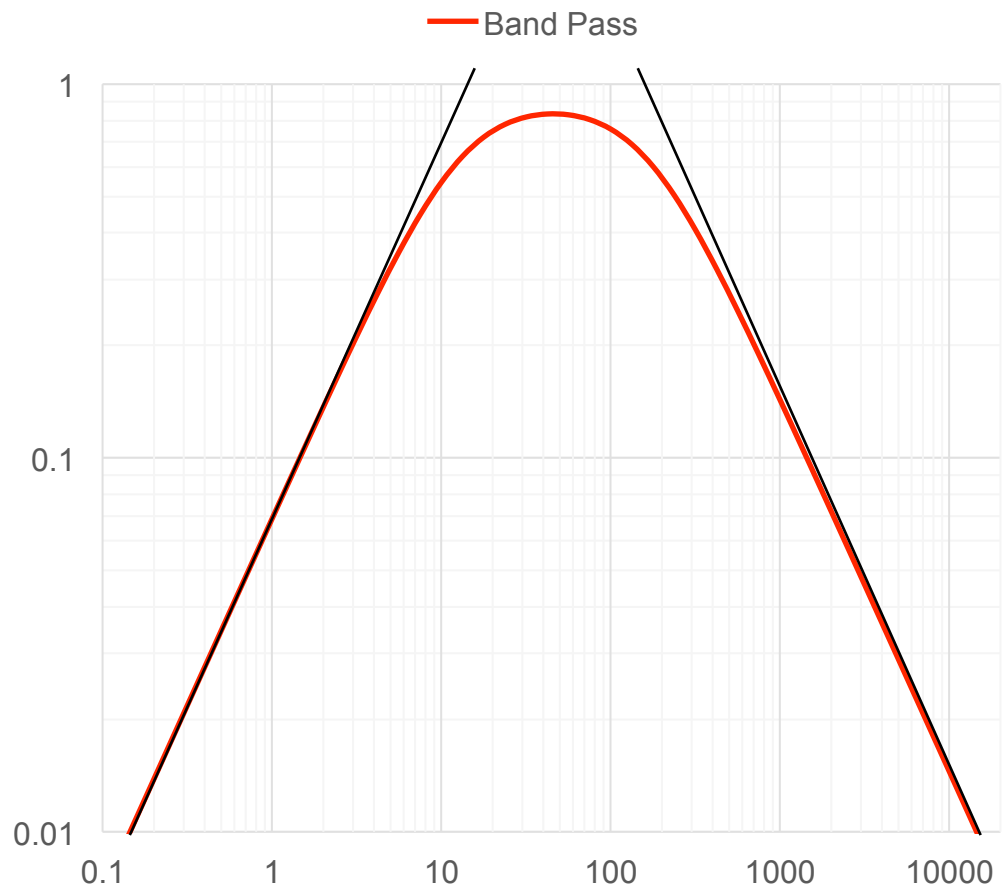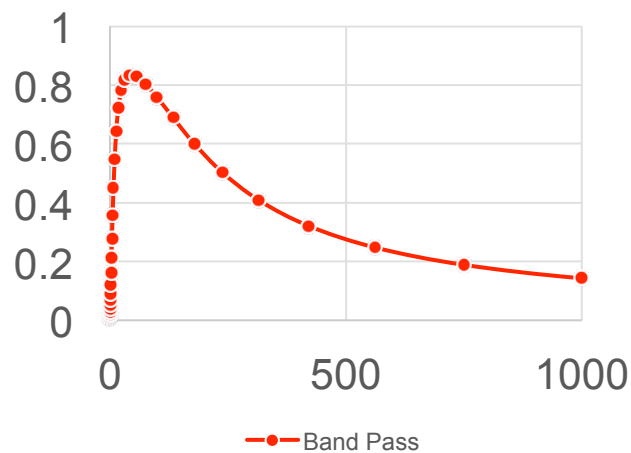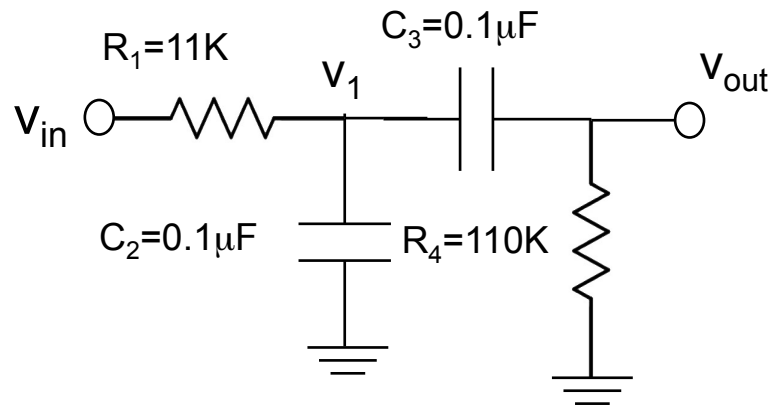Band Pass – Combining the Low and High Pass



One More Trick With Log-Log Plots


- Remember:

$$\log(A*B) = \log(A) + \log(B), \text{ and } \log(A/B) = \log(A) - \log(B)$$

- So:
$$\frac{V_{out}}{V_{in}} = \frac{j*2\pi FRC}{1 + j*2\pi FRC}$$

– Can add two lines

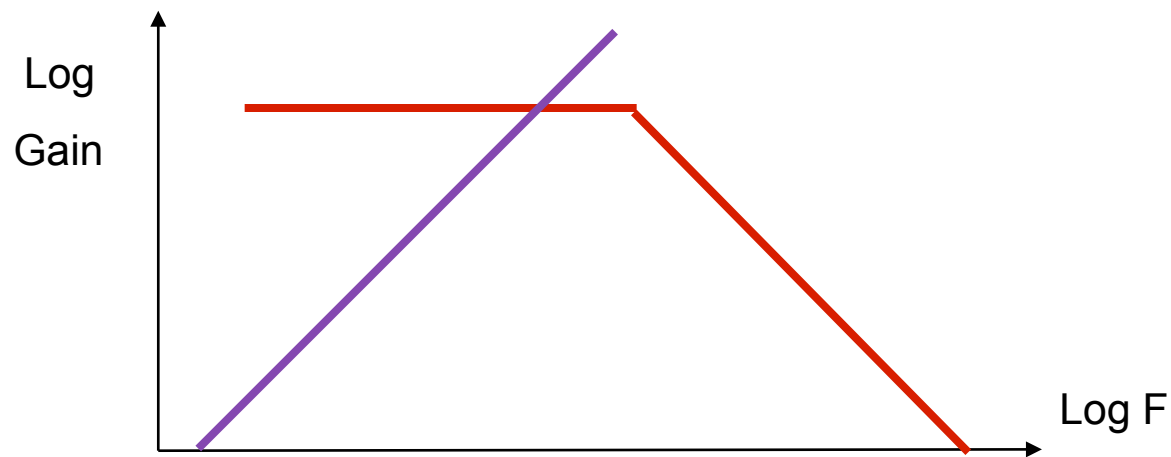- One slope +1
- One flat and then slope -1




Log-Log Plot Tricks, cont'd

- Our bandpass filter earlier had a gain function of the form

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{j * 2\pi F R_2 C_2}{1 + j * 2\pi F (R_1 C_1 + R_2 C_2) + (j * 2\pi F)^2 R_1 C_1 R_2 C_2}$$


- If we can factor the polynomial, then we can add lines as on the last slide
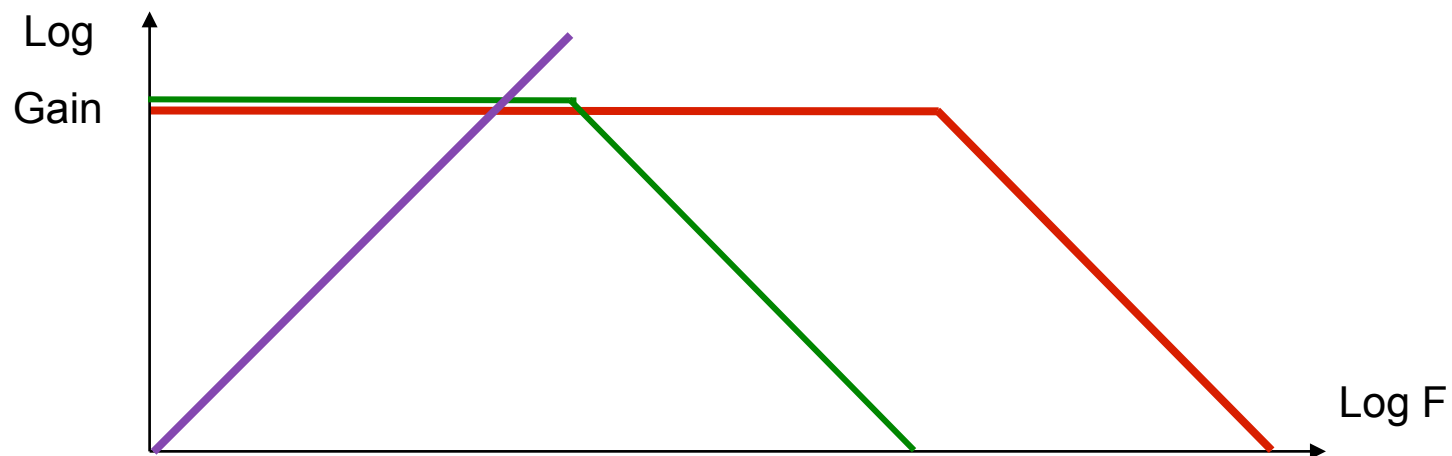
$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{j * 2\pi F R_2 C_2}{(1 + j * 2\pi F R_1 C_1) * (1 + j * 2\pi F R_2 C_2)}$$



dB

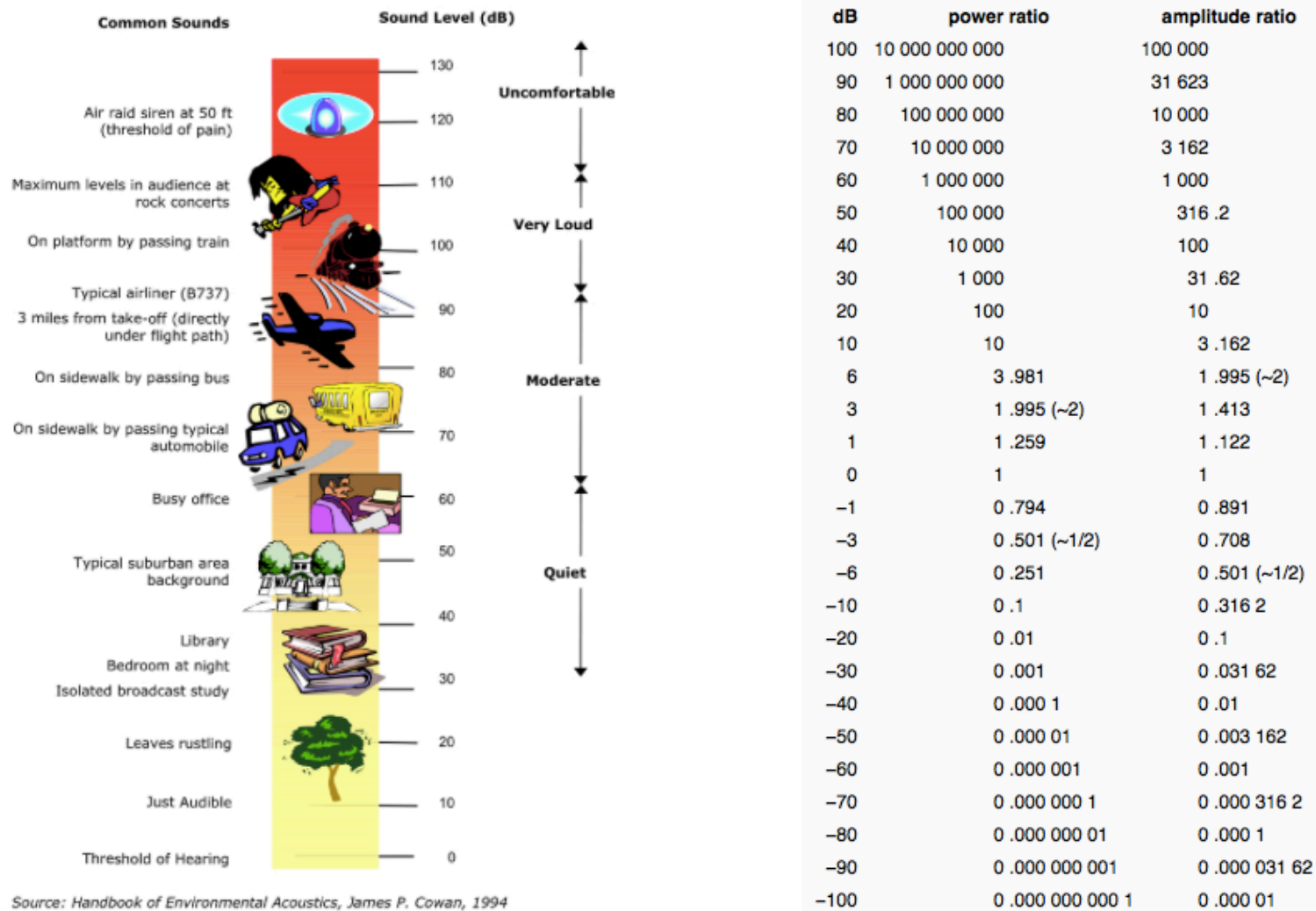Use of Logarithmic Scales to Represent Wide Ranges



dB


- In many places you will see the symbol **dB**
 - This is decibel
 - It is a logarithmic measure of power gain
 - $\text{dB} = 10 * \log (\text{Power}_{\text{out}}/\text{Power}_{\text{in}})$
- It is logarithmic so
 - 10dB is a 10x change in power
 - 20dB is a 100x change in power
 - 3dB is a 2x change in power
- Since power is proportional to V^2
 - A 10x change in voltage is a 100x change in power
 - This is a 20dB change
 - 6dB is a 2x change in voltage

Plotting Gain vs. Frequency


- Want to plot $\log(\text{gain})$ vs. $\log(\text{frequency})$
- dB is already log of the gain
 - So the plots look semilog
 - Log of frequency in the x direction
 - dB in the y direction
 - But this is the log-log plot that we want
- Please remember that dB measures power
 - 10x in voltage = 20dB

Plotting dB vs. Frequency

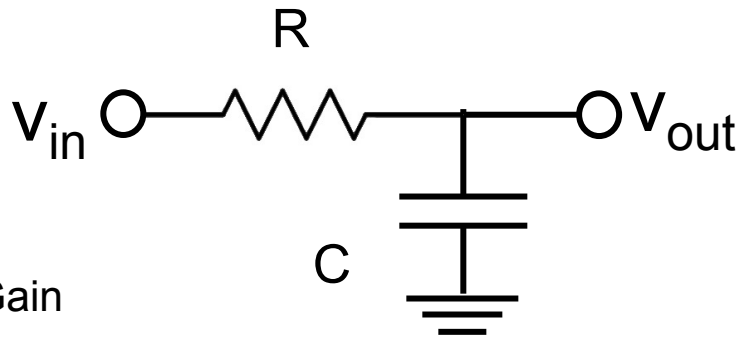- Consider the simple low pass filter we looked at earlier


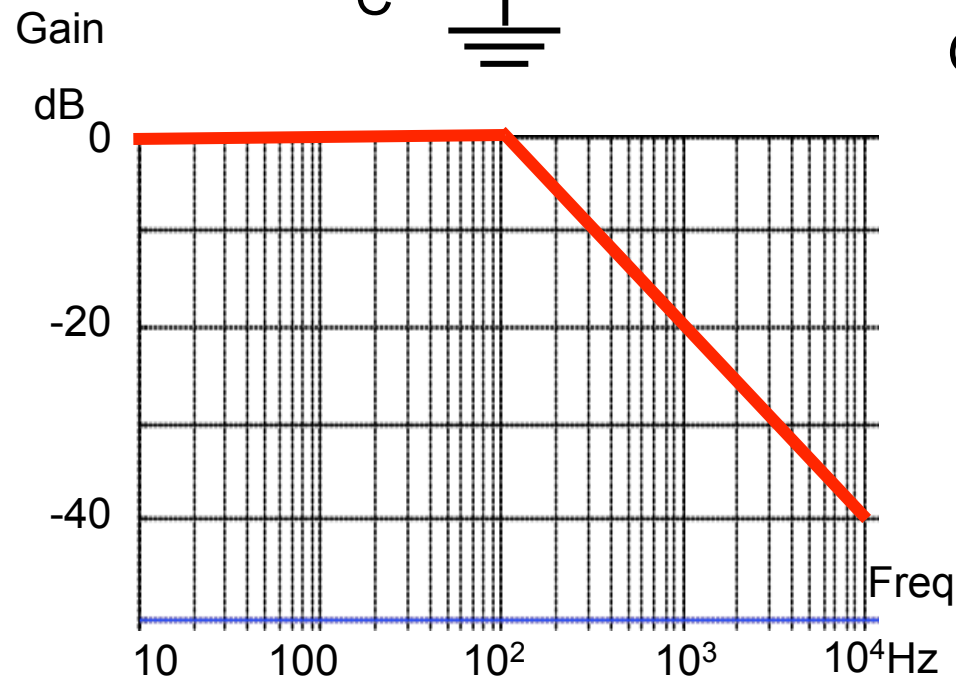
$$\text{Gain} = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{1}{1 + j * 2\pi FRC} = \frac{1}{1 + jF / F_c}$$




$$\begin{aligned}\text{Gain}_{\text{dB}} &= 20\log_{10}\left(\frac{1}{1 + jF / F_c}\right) \\ &= 20\log_{10}(1) - 20\log_{10}(1 + jF / F_c) \\ &\cong 0 - 20\log_{10}(F / F_c)\end{aligned}$$

(assuming F is large and neglecting the phase)

FYI – Hendrik Bode

Hendrik Wade Bode



Hendrik Wade Bode

Born December 24, 1905
[Madison, Wisconsin](#)

Died June 21, 1982 (aged 76)
[Cambridge, Massachusetts](#)

Residence [Cambridge, Massachusetts](#)

Nationality American

Fields [Control Systems](#), [Physics](#),
[Mathematics](#), [Telecommunications](#)

Institutions [Ohio State University](#)
[Bell Laboratories](#)
[Harvard University](#)

Alma mater [Ohio State University](#)
[Columbia University](#)

Known for [Bode plot](#), [Control theory](#),
[Telecommunications](#)


Notable awards [Richard E. Bellman Control Heritage Award](#) (1979)
[Rufus Oldenburger Medal](#) (1975)
[President's Certificate of Merit](#)
[Edison Medal](#) (1969)
[Ernest Orlando Lawrence Award](#) (1960)

- Bode (1905 –1982) spent most of his career at Bell Labs.
- He worked on control system theory and electronic filters and during WW II he worked on using radar information to direct anti-aircraft guns to try to intercept enemy aircraft and missiles like the German V2 missile.
- But today he's best remembered for inventing Bode plots used to describe the frequency behavior of linear systems.

(Wikipedia)


Plotting the Output

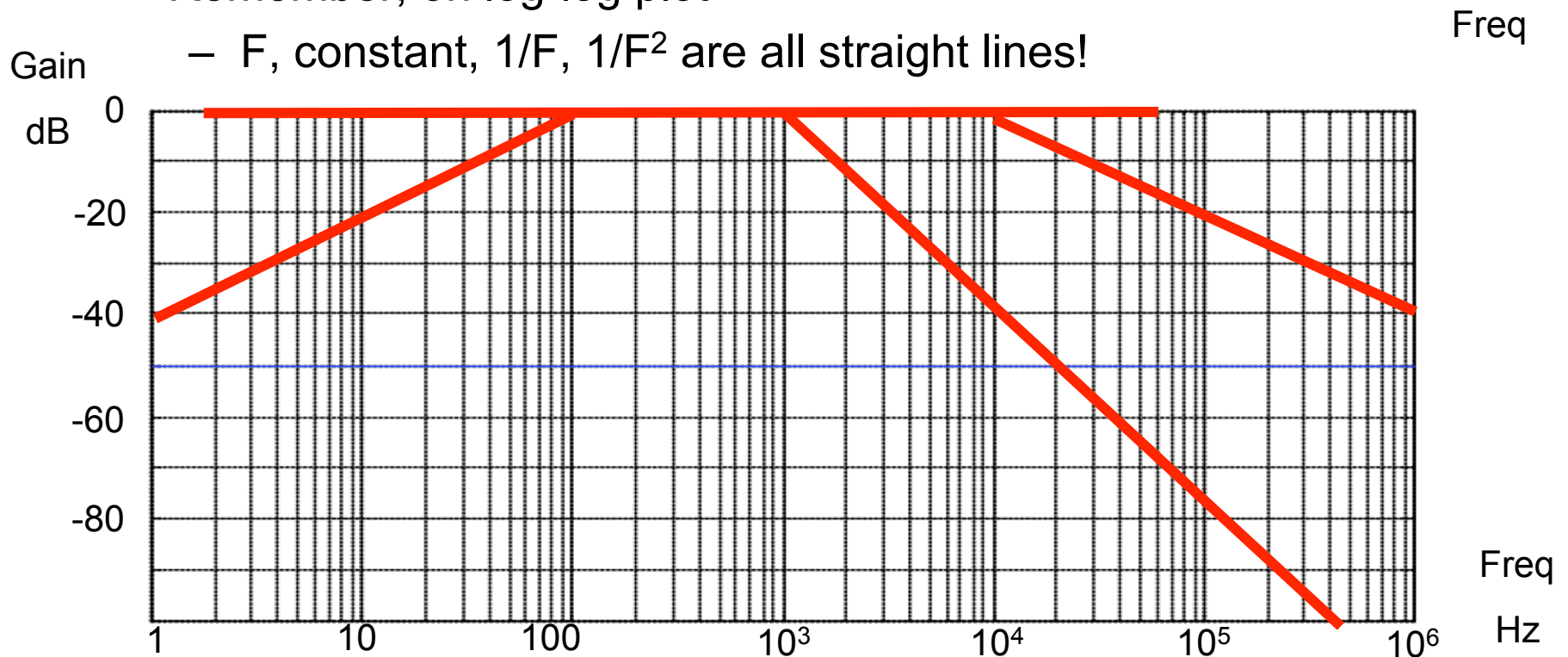- We use a Bode Plot to plot the transfer function of a circuit
 - Remember that this is the log of gain vs. log of frequency
- Remember, on log-log plot
 - F , constant, $1/F$, $1/F^2$ are all straight lines!




Circuit Bode Plots

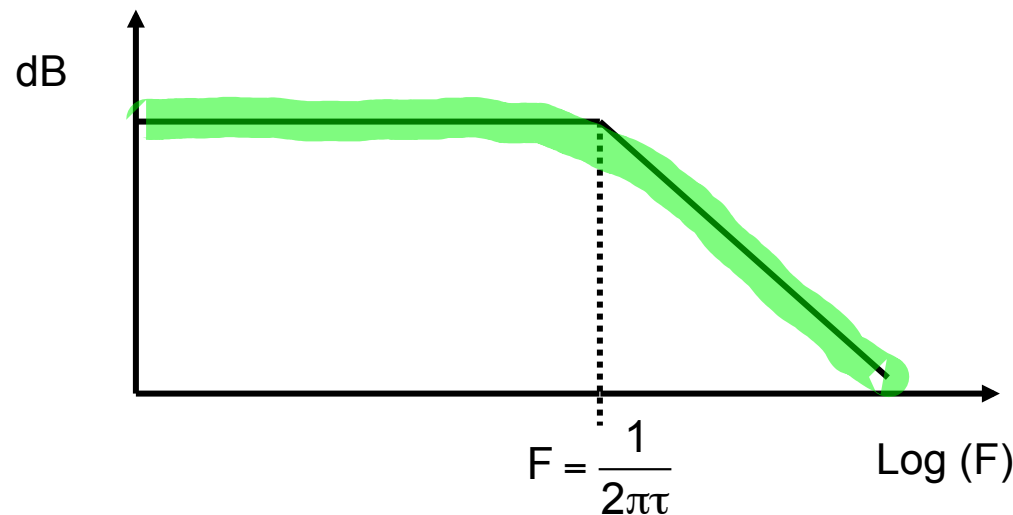- These are generally easy to draw
 - Know the slopes at different frequency ranges
 - Plot those straight lines
 - These lines will intercept at the F where the terms are equal
i.e. $F = 1/2\pi\tau = 1/2\pi RC$



- Actual curve will be close to the straight lines

Example

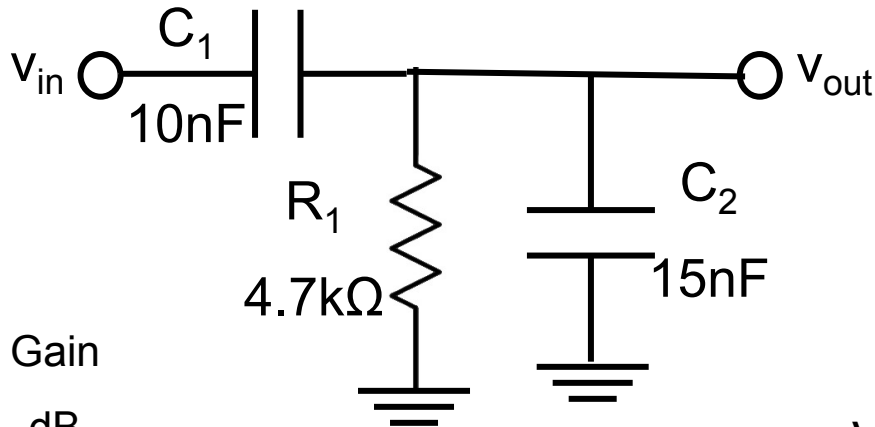


$$\frac{V_{out}}{V_{in}} = \frac{Z_{R1} \parallel Z_{C2}}{Z_{C1} + Z_{R1} \parallel Z_{C2}}$$

$$Z_{R1} \parallel Z_{C2} = \frac{Z_{R1} * Z_{C2}}{Z_{R1} + Z_{C2}} = \frac{R_1}{1 + 2\pi f R_1 C_2}$$


$$\frac{V_{out}}{V_{in}} = \frac{\frac{R_1}{1 + 2\pi f R_1 C_2}}{\frac{1}{2\pi f C_1} + \frac{R_1}{1 + 2\pi f R_1 C_2}} = \frac{2\pi f R_1 C_1}{1 + 2\pi f R_1 (C_1 + C_2)}$$

$$F_c = \frac{1}{2\pi R_1 (C_1 + C_2)} = 1.35 \text{ kHz}$$
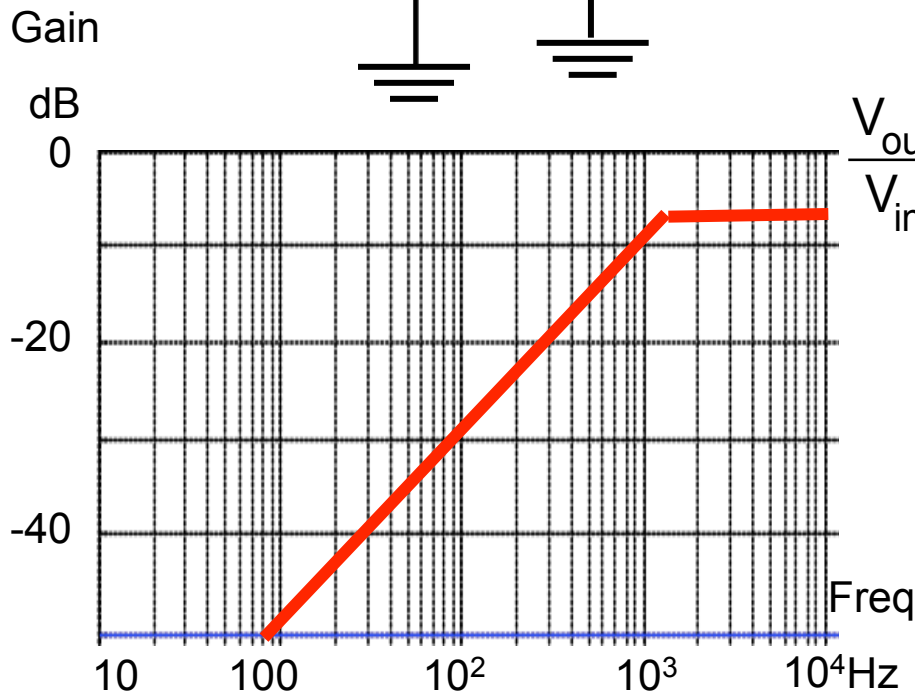
$$\text{Gain}_{dB} @ \text{HighF} = 20 \log \left(\frac{C_1}{C_1 + C_2} \right) = -7.96 \text{ dB}$$



EveryCircuit – Frequency Resonse

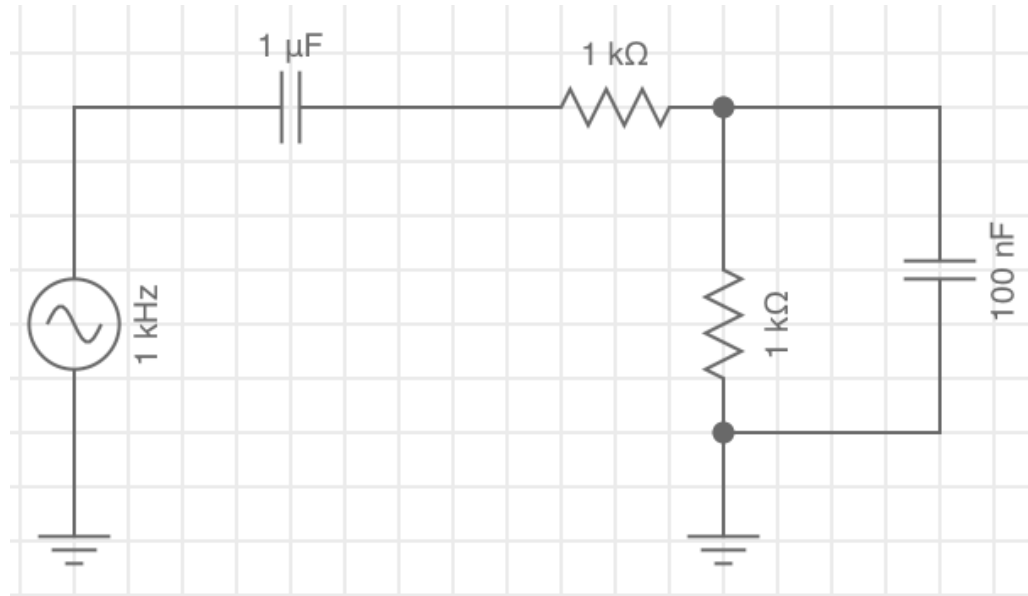


- EveryCircuit can be used to calculate and plot Bode plots for circuits. We'll demo this in class.
- This is very useful for checking answers to HW problems or for developing understanding about circuit frequency response.

Bonus Section (Not on HW, Exams)
See Class Reader For Details

**WHAT DOES $(1 + j*x)$ REALLY
MEAN?**


An Example - High Pass RC Filter

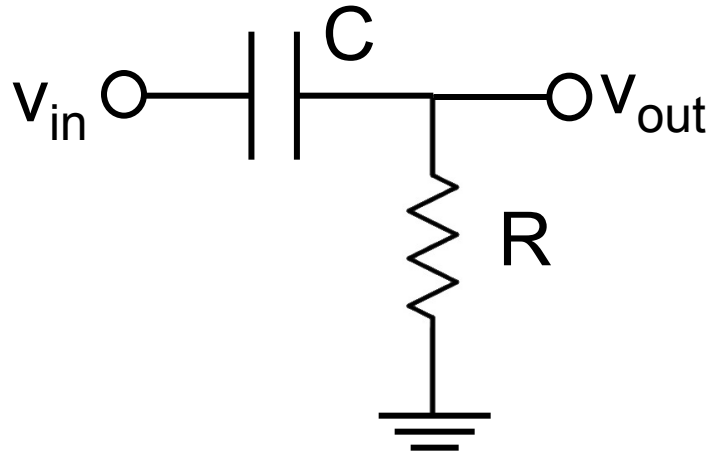Bonus Material – See Class Reader For Details



$$\frac{V_{out}}{V_{in}} = \frac{R}{R + \frac{1}{j * 2\pi FC}} = \frac{j * 2\pi FRC}{1 + j * 2\pi FRC}$$
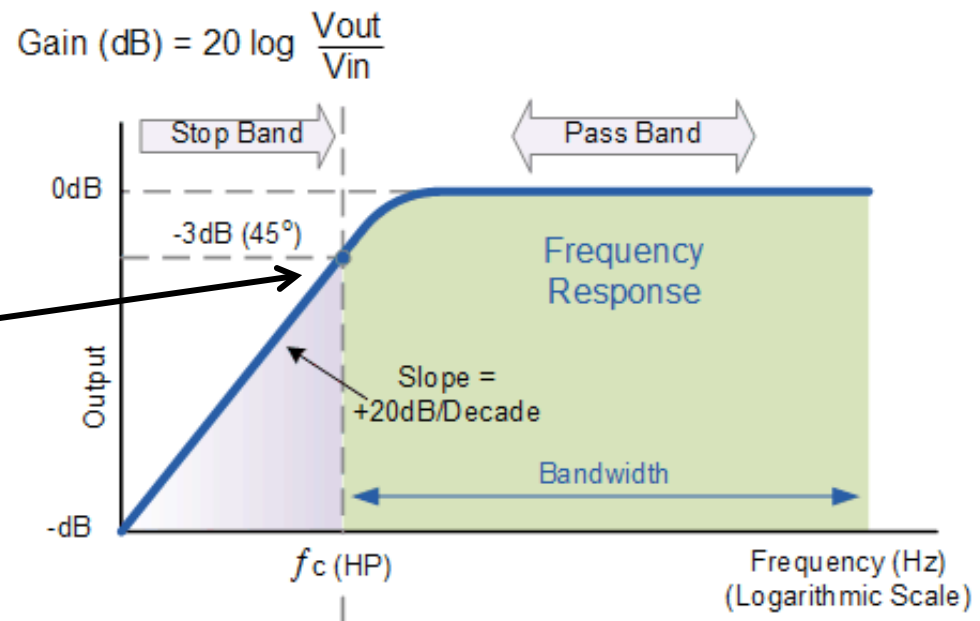
$$2\pi FRC = 1 \text{ or } F = \frac{1}{2\pi RC}$$



(Electronic Tutorials)

3dB?

Bonus Material – See Class Reader For Details

- Notice that when the two terms are the same, $F = 1/2\pi RC$
 - The overall gain is -3dB
 - This might seem right since -3dB is $1/2$, BUT
 - This is the power ratio!
 - The voltage ratio is only $1/\sqrt{2}$!
- What is going on?
- To understand, we'll need to think about what $(1 + j\omega x)$ means

Adding Sine and Cosine Waveforms

Bonus Material – See Class Reader For Details

- $1 + j*x$ means the waveform is the sum of
 - A sinewave with amplitude 1
 - With a cosine wave with amplitude “x”
- The good news is that this always results in a sinusoidal waveform
 - With some phase shift between a sin and cos (+90°)
 - So we can write

$$A \sin(2\pi Ft + \phi) = \sin(2\pi Ft) + x * \cos(2\pi Ft)$$

- And we want to find A and ϕ

The Trick

Bonus Material – See Class Reader For Details

$$C * \sin(2\pi Ft + \phi) = A * \sin(2\pi Ft) + B * \cos(2\pi Ft)$$

- This equation is always true so
 - At $t = 0$, the sine term is zero


$$C * \sin(\phi) = B$$

- At $t = 1/(4F)$, the cosine term is zero, so

$$C * \cos(\phi) = A$$

- So the amplitude of the resulting sine wave is

$$\sqrt{A^2 + B^2}$$

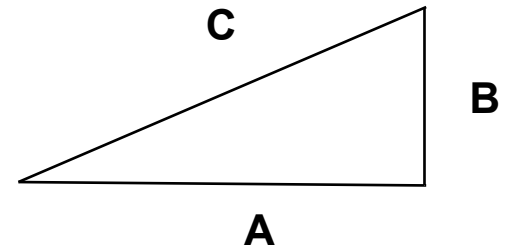

Learning Objectives For Today

- Understand how to create Bode plots for RC circuits
 - You plot two straight lines that intercept at $F=1/2\pi RC$
- (Bonus Section) Understand what an amplitude of $(1+ j*2\pi RCF)$ means
 - The result is a sum of a sine and cosine wave