

Some useful links:

- 1) <http://www.stanford.edu/class/ee133/handouts/general/vnc.pdf>  
(How to set up and run VNC)
- 1) [http://www.stanford.edu/class/ee133/handouts/general/hspice\\_tut.pdf](http://www.stanford.edu/class/ee133/handouts/general/hspice_tut.pdf)  
(Detailed tutorial about HSPICE & Mwaves)
- 2) <http://www.stanford.edu/class/ee133/spice/HSpice.pdf>  
(How to set up HSPICE in UNIX environment)
  - a) `source /usr/class/ee/DOT.cshrc`
  - b) `hspice filename.hsp > filename.lis (output)`  
`hspice filename.hsp >! filename.lis`
  - c) `mwaves filename`
- 3) [http://www.stanford.edu/class/ee133/handouts/general/spice\\_ref.pdf](http://www.stanford.edu/class/ee133/handouts/general/spice_ref.pdf)  
( 'Quick' Reference Sheet. More than you need in EE133)

```
*** -----***
*** A highly Annotated HSPICE input example file ***
*** http://www.stanford.edu/class/ee214/example.hsp ***
*** -----***
```

Remember that the first line is a title!

```
* comments are lines that begin with *
* all other lines are evaluated.

* model statement. this is an example of an include file
.include 'level3models'
* Or you may also specify the whole path.
*.include '/afs/ir/class/ee214/WWW/level3models'

* include this to use mwaves on the output!
.option post

* param statements allow you to define constants, etc.
.param cload      = 1pF

* note that beginning a line with +
* appends the time to the previous line
* (exceptions: comments cannot continue with +)
.param rout      = 10k
+   vdd      = 3V
+   delV     = 1

*circuit. This is in netlist format.

* voltage sources:
* Vname pos_terminal neg_terminal dc_val AC ac_val
vdd  vdd  gnd  vdd
vcm  cm   gnd  1.2V
vin1 in1  cm   ac   'delV/2'
vin2 cm   in2  ac   'delV/2'

* current sources:
* Iname pos_terminal neg_terminal dc_val
iss  ss   gnd  200u

* a resistor:
* Rname term1 term2 res_val
Rout ss   gnd  rout
```

```

* a capacitor:
* Cname term1 term2 cap_val
Cload      out  gnd  'cload'

* a transistor:
* Mname drain gate source bulk model_name W=width L=length
* L=Ldrawn!
.param     wn      = 25u
+         wp      = 10u
+         l       = 0.5u
mn1  load  in1  ss  gnd  nmos  w=wn  l=l
+     as='wn*3*1' ad='wn*3*1' ps='2*(wn+3*1)'  pd='2*(wn+3*1)'

mn2  out   in2  ss  gnd  nmos  w=wn  l=l
+     as='wn*3*1' ad='wn*3*1' ps='2*(wn+3*1)'  pd='2*(wn+3*1)'

mp1  load  load  vdd  vdd  pmos  w=wp  l=l
+     as='wp*3*1' ad='wp*3*1' ps='2*(wp+3*1)'  pd='2*(wp+3*1)'

mp2  out   load  vdd  vdd  pmos  w=wp  l=l
+     as='wp*3*1' ad='wp*3*1' ps='2*(wp+3*1)'  pd='2*(wp+3*1)'

* Simulation
* DC sweep from .7V to 1.5V in .01V steps
.dc  vcm  0.7  1.5  0.1

* AC sweep 10steps/decade from 1Hz to 1GHz  varying
* the output resistor from 10k to 30k in 5 evenly space steps.
.AC  dec  10  10k  10G  sweep  rout  lin  5  10k  30k

* output results
* some notes:
* when doing DC sweeps, refer to
*   voltages at nodes by v(nodename)
*   currents in voltage sources by i(voltage_source)
* when doing AC sweeps, refer to
*   voltage(mag) by vm(nodename)
*   voltage(phase) by vp(nodename)
*   voltage(magnitude in db) by vdb(nodename)

* print statements list all the values you want to see.
.print      DC    v(out)      i(vdd)
.print      AC    vm(out)

.measure  dc  gate_vol  when  i(vdd)=-0.5m
.measure  dc  drain_vol  find  v(out)  when  i(vdd)=-0.5m
.measure  ac  ugbw_frequency  when  vdb(out)=0
.measure  ac  ugbw_phase      find  vp(out)  when  vdb(out)=0
.measure  ac  ugbw_phase_margin  param='180 + ugbw_phase'

*.alter statements allow you to change a parameter and
*then rerun all of the above simulations
*syntax : .alter title
.alter      wn100
.param     wn      = 100u
+         wp      = 25u

.alter      wn200
.param     wn      = 200u
+         wp      = 50u

*remember to end the file with .end AND a carriage return.
.end

```