

LNA Stability Issues--Step 1

Briefly reviewing, the small signal hybrid- π version of the “y” parameters is as follows:

$$C_\pi = \frac{g_m}{\omega_T} - C_\mu \quad \text{or} \quad C_\pi + C_\mu = \frac{g_m}{\omega_T}$$

$$r_\pi = \frac{\beta}{g_m}$$

$$y_i = \frac{g_m}{\beta} + j\omega(C_\pi + C_\mu) = \frac{g_m}{\beta} + j\omega\left(\frac{g_m}{\omega_T}\right)$$

$$y_f = g_m - j\omega C_\mu$$

$$y_r = 0 - j\omega C_\mu$$

$$y_o = \frac{1}{r_o} + j\omega C_\mu$$

most of the “action”
will be associated with
 C_μ

Stability Criteria (the minimalist’s view)

There are two stability criteria formulae. The Stern criteria will be used here for discussion. The equations are derived in terms of network theory (and feedback) that considers conditions when the denominator of the transfer function (i.e. $A=a/[1-af]$) can become zero.

$$K \equiv \frac{2(g_i + G_s)(g_o + G_L)}{(|y_f y_r| + \text{Re}(y_f y_r))}$$

Stability for $K > 1$ or

$$2(g_i + G_s)(g_o + G_L) > (|y_f y_r| + \text{Re}(y_f y_r))$$

and in terms of hybrid- π :

$$|y_f y_r| \sim g_m \omega C_\mu$$

Bottom-line (ultra-simplified) Equation

$$\operatorname{Re}(y_f y_r) = -(\omega C_\mu)^2$$

assume that $g_o \ll G_L$

$$2\left(\frac{g_m}{\beta} + G_s\right)(G_L) \gg g_m \omega C_\mu - (\omega C_\mu)^2$$

LHS

RHS

Now, let's take some typical numbers for transistor parameters and look at the effects of:

- bias, frequency
- loading from G_s and G_L .

Assume the following values for the transistor:

$$\beta = 100$$

$$C_\mu = 0.5 \text{ pF}$$

Putting some numbers into the Equation

Assuming that $I_c = 2 \text{ mA}$, resulting in a value of $g_m = 0.077$, then the following table gives values for the two RHS terms

ω	ωC_μ	$g_m \omega C_\mu$	$(\omega C_\mu)^2$
20 MHz...	6.28×10^{-5}	4.84×10^{-6}	3.94×10^{-9}
200 MHz..	6.28×10^{-4}	4.84×10^{-5}	3.94×10^{-7}
1 GHz.....	3.14×10^{-3}	2.42×10^{-3}	9.86×10^{-6}

Assuming $g_i = G_s$ and $G_L = 10 \text{ k}\Omega$, and computing the LHS of the boxed equation gives:

$$2 \times (1.54 \times 10^{-3})(10^{-4}) = 3.08 \times 10^{-7}$$

(which for ALL frequencies would NOT satisfy the K-stability criteria).

Getting a stable amplifier

Now choosing $G_s=500\Omega$ and $G_L=1K\Omega$, again computing the LHS gives:

$$2x(7.7x10^{-4} + 2.0x10^{-3})(10^{-3}) = 5.54x10^{-6}$$

(which **does satisfy the K-stability criteria at 20MHz** (but NOT at 200MHz). In turn, this would set the voltage gain at $A_v=-g_m R_L=-77$).

Clearly, if one needs to go to higher frequencies, several things would be needed:

- Lower G_s and G_L
- Larger g_m
- A better transistor (with lower C_μ)