

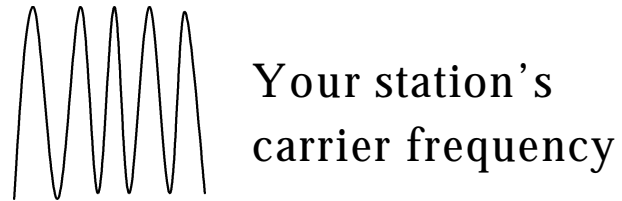



A Few Basics--Modulation, AM & FM

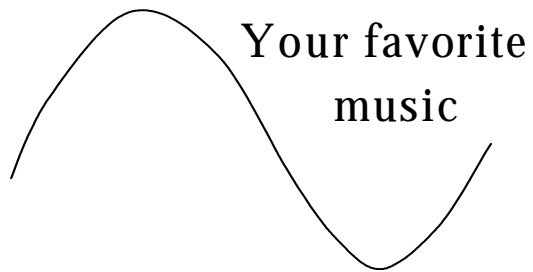

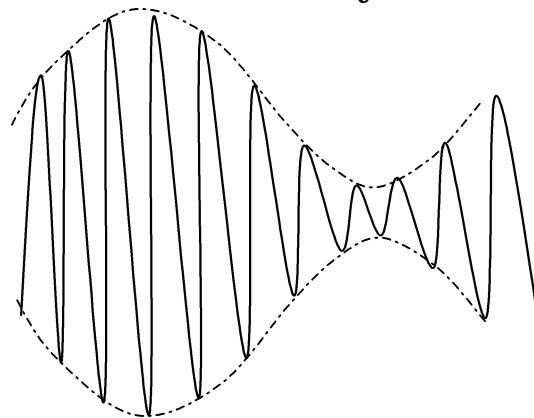
The Amplitude Modulated (AM) version of your music



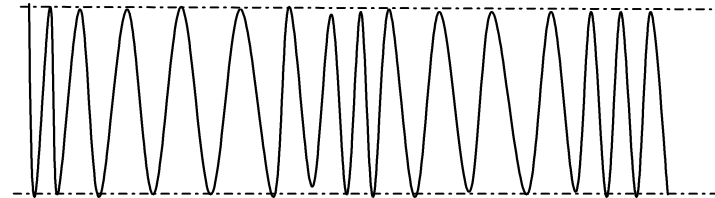
The Frequency Modulated (FM) version of your music



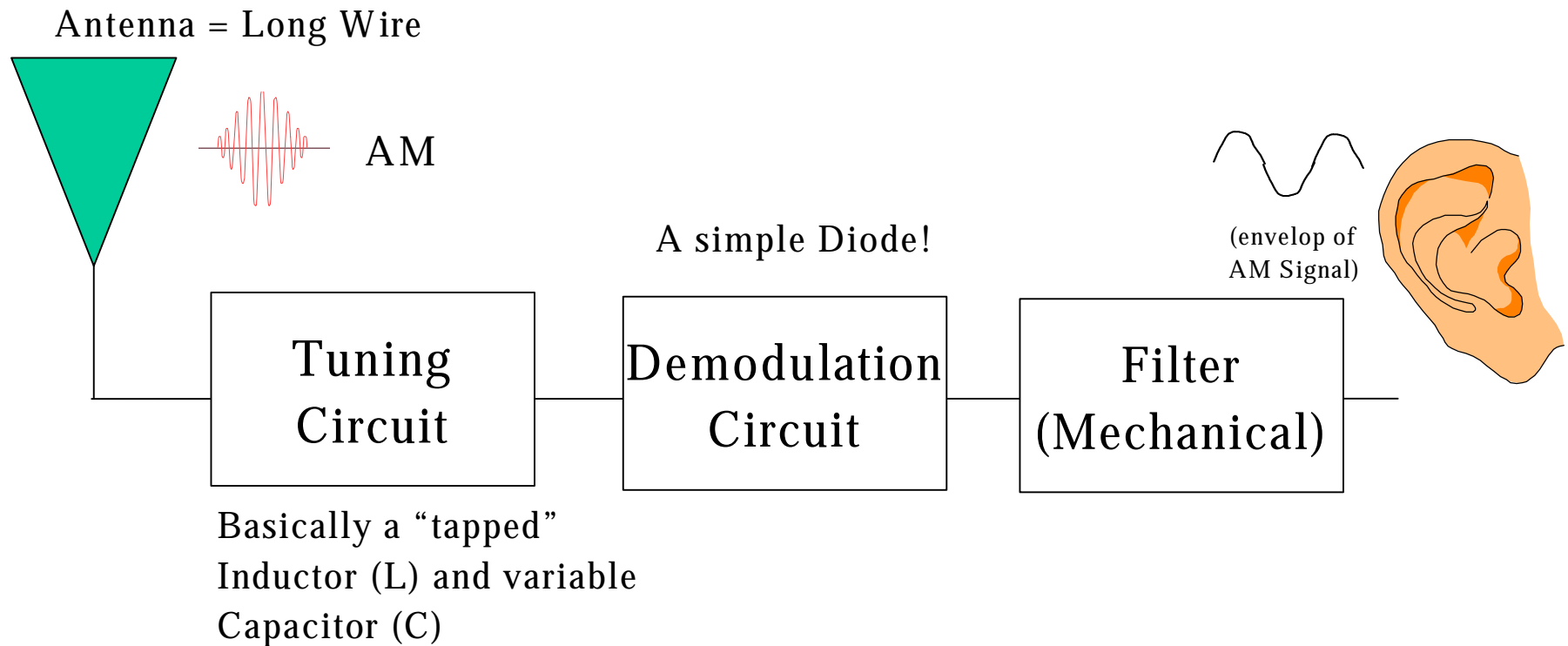
Demodulation is about recovering the original signal--Crystal Radio Example



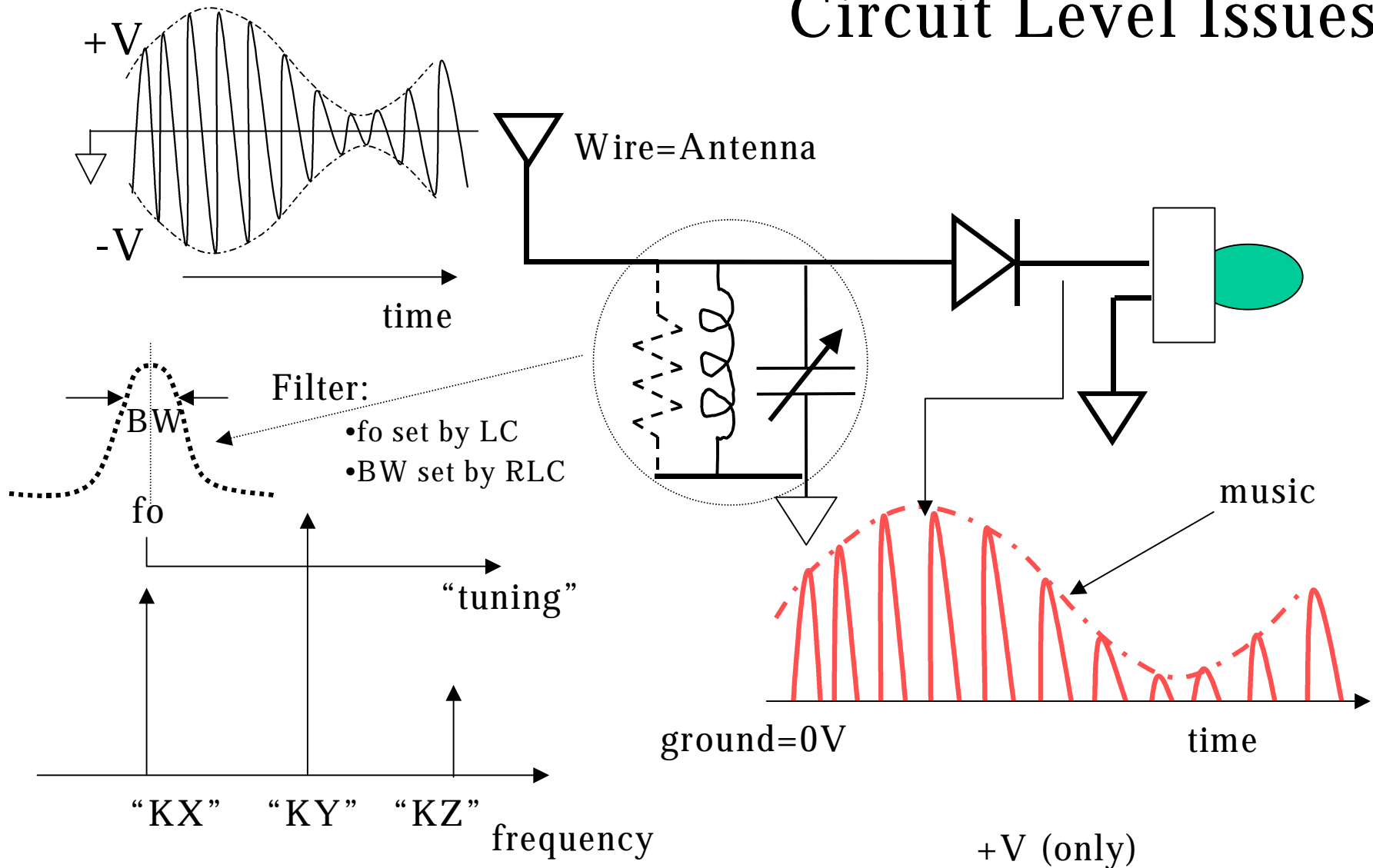Signal Flow in Crystal Radio-- Circuit Level Issues



Series Resonant “Tank” Circuit

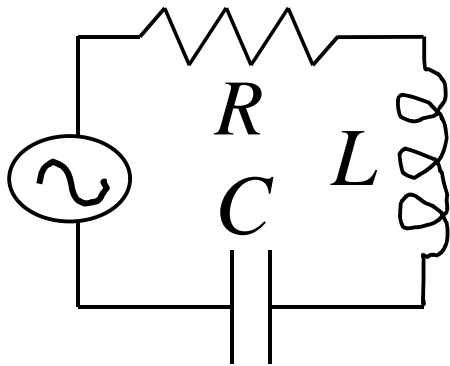


$$Z(j\omega) = R \left[1 + jQ_s \left(\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega} \right) \right]$$

where :

$$Q_s \equiv \frac{\omega_o L}{R} = \left(\frac{X_s}{R_s} \right)$$

$$\omega_o = \frac{1}{\sqrt{LC}}$$

Parallel Resonant “Tank” Circuit

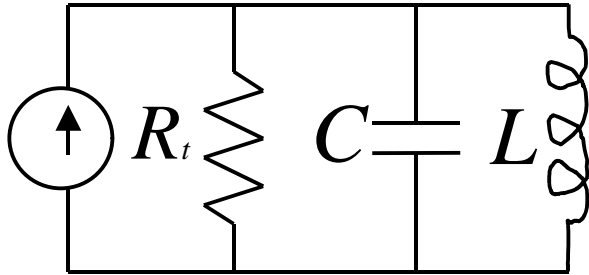

$$Y(j\omega) = G_t \left[1 + jQ_p \left(\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega} \right) \right]$$

where :


$$Q_p = \frac{\omega_o C}{G_t} = \frac{R_t}{1/\omega_o C} = \left(\frac{R_p}{X_p} \right)$$

About notation and components:

- We'll use the “p” and “s” subscripts (per text) and their definitions in terms of respective R and X values (where X is either ωL or $1/\omega C$)
- Components are NOT ideal! (see Chapter 6 reading)
- Basically, when talking about resonant circuits we want to have equivalent tank circuit (either series or parallel per above to cases)

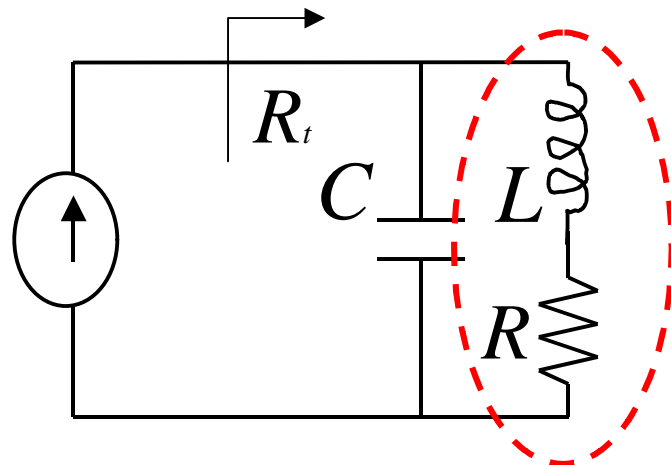Example of non-ideal Inductor

(and transforming back to equivalent tank circuit)




Conversion...series-to-parallel

$$L_p = L \left(\frac{Q_s^2 + 1}{Q_s^2} \right)$$

$$R_t = R(Q_s^2 + 1)$$

where :

$$Q_s = \frac{\omega_o L}{R}$$

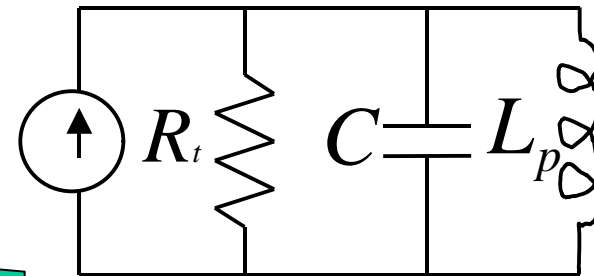

Final equivalent resonant
“tank” circuit:

- transformed L now sets resonant frequency
- let's see how these transformations work...

A bit more about “Q”

We can think about (and/or measure) the quality factor (Q) in two ways--parallel (sub_p) or series (sub_s).

As discussed in text (section 6.7.2) there is ultimately only one “Q” for the circuit, we’ll call it Q_c

The definitions of the parallel and series (component) Q’s are as follows:

$$Q_p = R_p / X_p \text{ (parallel or “shunt”)}$$

$$Q_s = X_s / R_s \text{ (series)}$$



Based on simple math, comparing the series and parallel cases for either capacitor or inductor:

$$R_p = (Q_c^2 + 1) R_s$$

$$\text{and } Q_c = Q_p = Q_s$$

We can derive all of the following relationships based on using the above relationships

Conversion Relationships--Capacitors

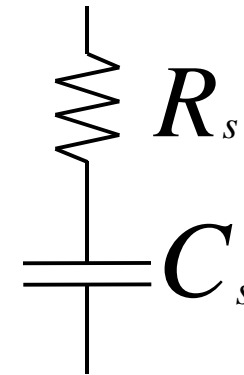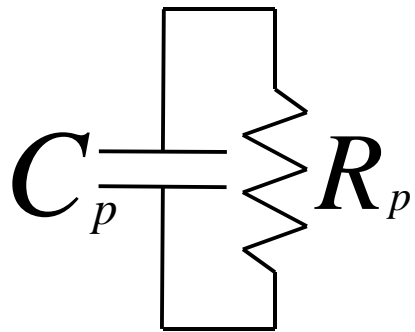

$$C_{s-eq} = C_p \left(\frac{Q_p^2 + 1}{Q_p^2} \right)$$

$$R_{s-eq} = \frac{R_p}{1 + Q_p^2}$$

$$Q_p = \frac{R_p}{X_p}$$

$$X_p = 1 / \omega C_p$$

$$C_{p-eq} = C_s \left(\frac{Q_s^2}{Q_s^2 + 1} \right)$$

$$R_{p-eq} = R_s (Q_s^2 + 1)$$



$$Q_s = \frac{X_s}{R_s}$$

$$X_s = 1 / \omega C_s$$

parallel-to-series

series-to-parallel

Conversion Relationships--Inductors

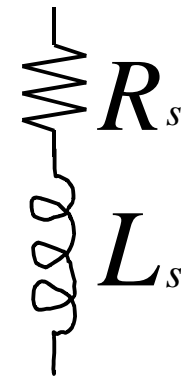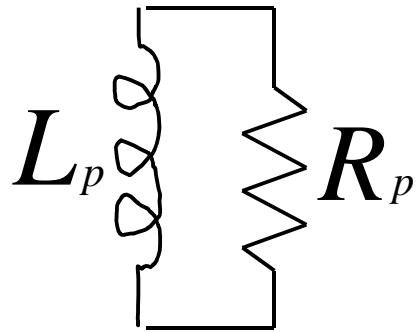

$$L_{s-eq} = L_p \left(\frac{Q_p^2}{Q_p^2 + 1} \right)$$

$$L_{p-eq} = L_s \left(\frac{Q_s^2 + 1}{Q_s^2} \right)$$

$$R_{s-eq} = \frac{R_p}{1 + Q_p^2}$$


$$R_{p-eq} = R_s (1 + Q_s^2)$$

$$Q_p = \frac{R_p}{X_p}$$

$$Q_s = \frac{X_s}{R_s}$$



$$X_p = \omega L_p$$

$$X_s = \omega L_s$$

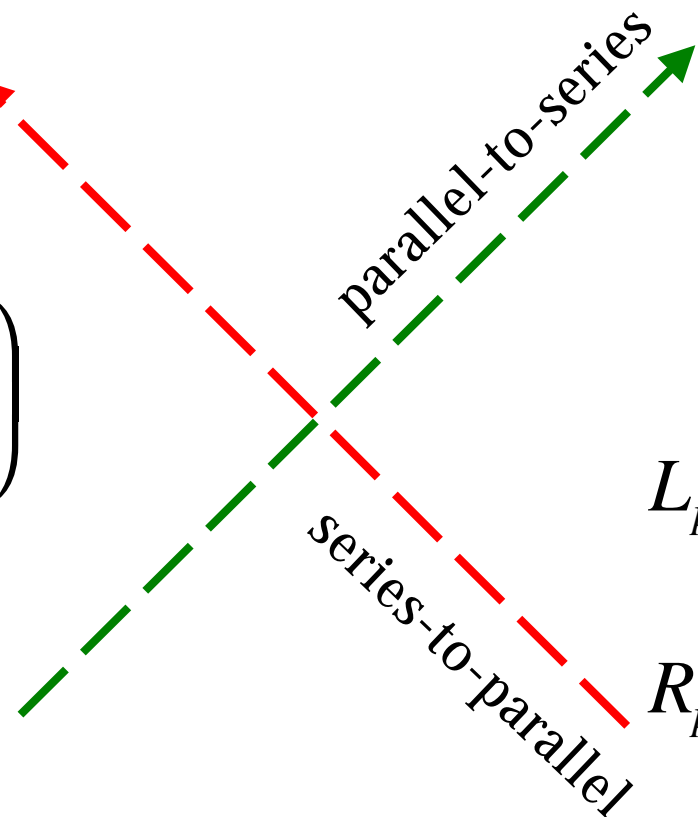

Another Example... (a.k.a. Lab 1)

original circuit...

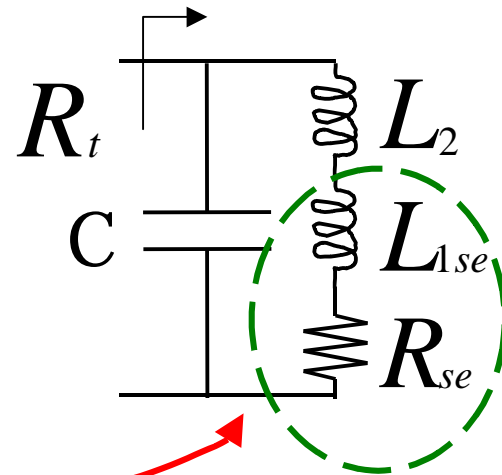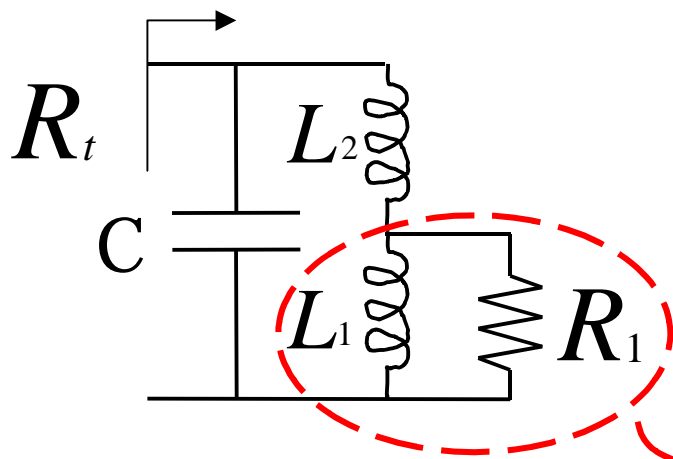

convert to series...

Following steps:

- Combine $L_1 + L_2$ (series equivalent) = $L_{(new)}$
- Convert $L_{(new)}$ & R_{se} back to parallel
- Result gives final equivalent tank circuit


Design-Oriented Example

(including use of transformer concepts* ... text (Sect. 6.8.2))

$$N \equiv \frac{L_1 + L_2}{L_1}$$

$$\frac{R_t}{R_1} = N^2$$

(*per_book_notation* :)

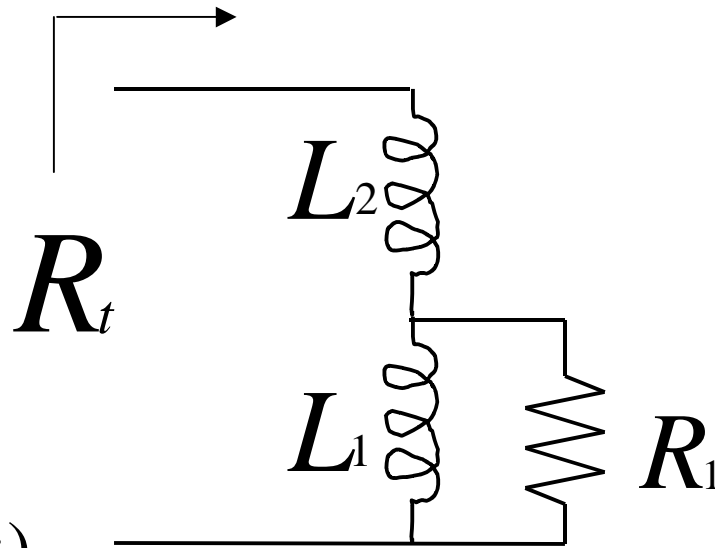

$$N = \frac{n}{n_1}$$

$$L_T = L = L_2 + L_1$$

Example:

$$R_1 = 50\Omega$$


In order to have $R_t = 2\text{K}\Omega$,

$$N^2 = 40 \text{ or } N = 6.3 = L_T/L_1$$

*caution: this simple relationship works for $Q_p > 10$, otherwise one needs to do the transformations per above example

Useful (more complete) Design Equations

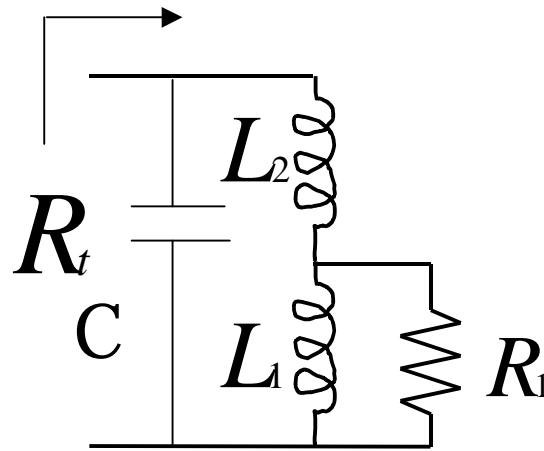(per supplemental book by Krauss... last year's text)



For $Q_c = Q_t \approx \omega_o / BW \geq 10$

$$C \approx \frac{1}{2p \cdot BW \cdot R_t}$$

$$L \approx \frac{1}{\omega_o^2 C}$$

$$N = \left(\frac{R_t}{R_1} \right)^{\frac{1}{2}}$$

For $Q_p < 10$:


$$Q_p = \left(\frac{Q_t^2 + 1}{N^2} - 1 \right)^{\frac{1}{2}}$$

$$L_1 = \frac{R_1}{\omega_o Q_p}$$

$$L_{1_se} = \frac{L_1 Q_p^2}{Q_p^2 + 1}$$

$$L_2 = L - L_{1_se}$$

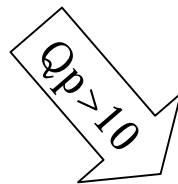$\frac{Q_t}{N} = Q_p \dots$ If $\frac{Q_t}{N} \geq 10$



For $Q_p \geq 10$:

$$Q_p = \frac{Q_t}{N}$$

$$L_1 = \frac{L}{N}$$

$$L_2 = (N - 1)L_1 = L - L_1$$