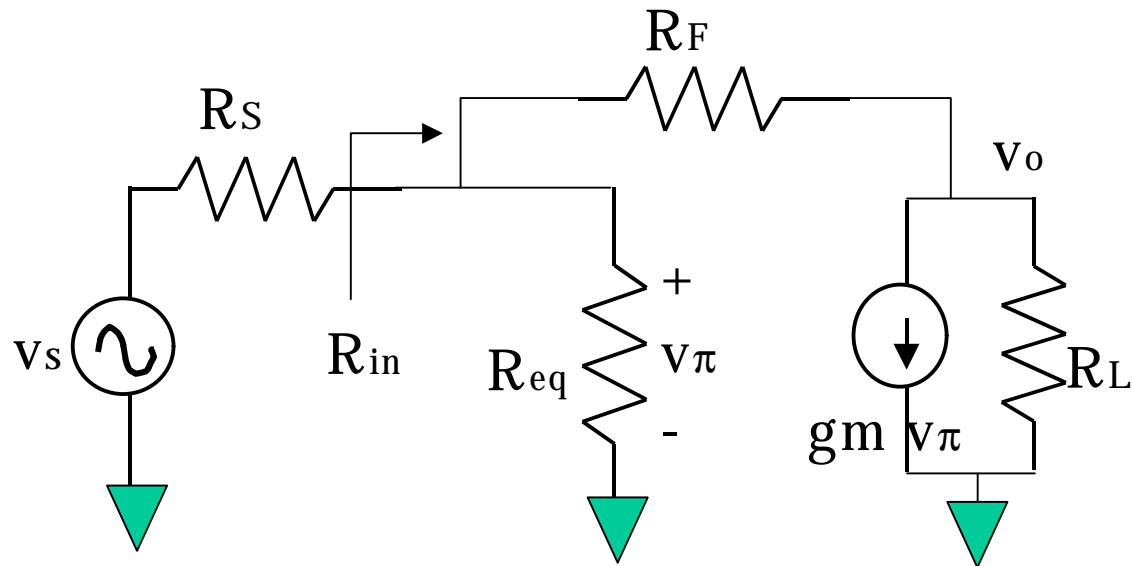


Rigorous Analysis of Shunt-Shunt Feedback Circuit

- Nodal Analysis
- One Assumption... $|g_m| \gg |g_f| \dots$ (see below)
- Results on the final pages:
 - Relationship to match R_s
 - Gain expression (both as voltage gain and trans-resistance with units “V/I”)
 - Manipulations that put results into “classical” form (ala step-by-step done in **Gray & Meyer**)



Nodal – Equations :

$$(V_s - V_p)g_s - V_p g_{eq.} - (V_p - V_o)g_f = 0$$

$$(V_p - V_o)g_f - g_m V_p - V_o g_L = 0$$

rearranged :

$$V_p (g_s + g_{eq.} + g_f) - V_o g_f = V_s g_s$$

$$V_p (g_m - g_f) + V_o (g_f + g_L) = 0$$

$\frac{V_o}{V_p}$ is:

$$\frac{V_o}{V_p} = \left(\frac{-g_m + g_f}{g_f + g_L} \right) \approx \left(\frac{-g_m}{g_f + g_L} \right)$$

assu min $g|g_m| \gg |g_f|$

Solving for $V_p = f(V_s)$:

use $\left(\frac{V_o}{V_p} \right)$ in first equation:

$$V_p (g_s + g_{eq.} + g_f) + g_f \left(\frac{g_m}{g_f + g_L} \right) V_p = g_s V_s$$

$$V_p = \frac{g_s}{g_s + g_{eq.} + g_f + g_m \left(\frac{g_f}{g_f + g_L} \right)} V_s$$

and...


$$V_s - V_p = \left(\frac{g_{eq.} + g_f + g_m \left(\frac{g_f}{g_f + g_L} \right)}{g_s + g_{eq.} + g_f + g_m \left(\frac{g_f}{g_f + g_L} \right)} \right) V_s$$

solving_for_the_input_conductance:

$$i_{in} = g_s (V_s - V_p) \text{ and...}$$

$$g_{in} = \frac{i_{in}}{V_s}$$

which_in_turn_for_a_matched_condition:

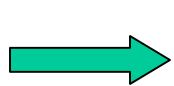

$$g_{in} = \frac{g_s}{2} =$$

Assumption
(I.e. that we want
"match" with
Rs)

$$= g_s \cdot \left(\frac{g_{eq.} + g_f + g_m \left(\frac{g_f}{g_f + g_L} \right)}{g_s + g_{eq.} + g_f + g_m \left(\frac{g_f}{g_f + g_L} \right)} \right)$$

therefore:

$$g_s + g_{eq.} + g_f + g_m \left(\frac{g_f}{g_f + g_L} \right) = 2 \cdot \left(g_{eq.} + g_f + g_m \left(\frac{g_f}{g_f + g_L} \right) \right)$$

which gives:

$$g_s = g_{eq.} + g_f + g_m \left(\frac{g_f}{g_f + g_L} \right) \leftarrow$$

solving for $\frac{V_o}{V_s}$:

$$\frac{V_o}{V_s} = \left(\frac{-g_m}{g_f + g_L} \right) \left(\frac{g_s}{g_s + g_{eq.} + g_f + g_m \left(\frac{g_f}{g_f + g_L} \right)} \right)$$

which can be rewritten as:

$$= \frac{-g_m \cdot g_s}{(g_f + g_L)(g_s + g_{eq.} + g_f) + g_m g_f}$$

this is exactly equivalent to $G \& M$ (Eqn.8.56)


Note: this equation is a specific result of having the R_{in} of *amplifier with feedback* exactly equal R_s (I.e. a matched load condition)



Design Example
Coming Soon!

Looking at equation once more, putting it into the units which are consistent with feedback theory (I.e. shunt-shunt... see EE113 notes!)
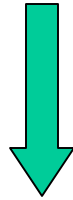
$$\frac{V_o}{V_s} = \frac{-g_m \cdot g_s}{(g_f + g_L)(g_s + g_{eq.} + g_f) + g_m g_f}$$



which can be rewritten in "standard" feedback form:

$$\frac{V_o}{V_s / R_s} = \frac{V_o}{I_s} = \frac{\frac{-g_m}{(g_f + g_L)(g_s + g_{eq.} + g_f)}}{1 + \frac{g_m g_f}{(g_f + g_L)(g_s + g_{eq.} + g_f)}}$$

← Actually, this is the exact equivalent of the G&M Eqn.8.56

$$= \frac{a}{1 + |af|}$$

← Which can be written in the classical feedback equation form...

where:

$$a = \frac{-g_m}{(g_f + g_L)(g_s + g_{eq.} + g_f)}$$

and

$$f = -g_f$$

← These are the "a" and "f" terms with natural units of: V/I and I/V respectively

solving the quadratic for g_f :

$$g_f = \frac{-(g_m + g_L + g_{eq} - g_s) \pm \sqrt{(g_m + g_L + g_{eq} - g_s)^2 + 4(g_s - g_{eq})g_L}}{2}$$

and the correct (physical) solution is:

$$g_f \approx \frac{(g_s - g_{eq})g_L}{(g_m + g_L + g_{eq} - g_s)}$$

Typical numbers based on $I_c=5\text{mA}$:

$$g_m=0.193 \text{ (mho)}$$

$$g_{eq}=g_p=0.0024 \text{ (mho)}$$

and assuming...

$$g_L=0.0005 \text{ (mho)} \rightarrow R_L=2\text{K}\Omega$$


$$g_s=0.05 \text{ (mho)} \rightarrow R_s=50\Omega$$

The above equations give:

$$g_f=5.028 \times 10^{-5} \text{ (mho)} \rightarrow R_f=19.99\text{K}\Omega$$

and using this value in the gain expression:

$$V_o/V_s = -175$$



Sounds good but...
there are still potential issues
related to stability!