
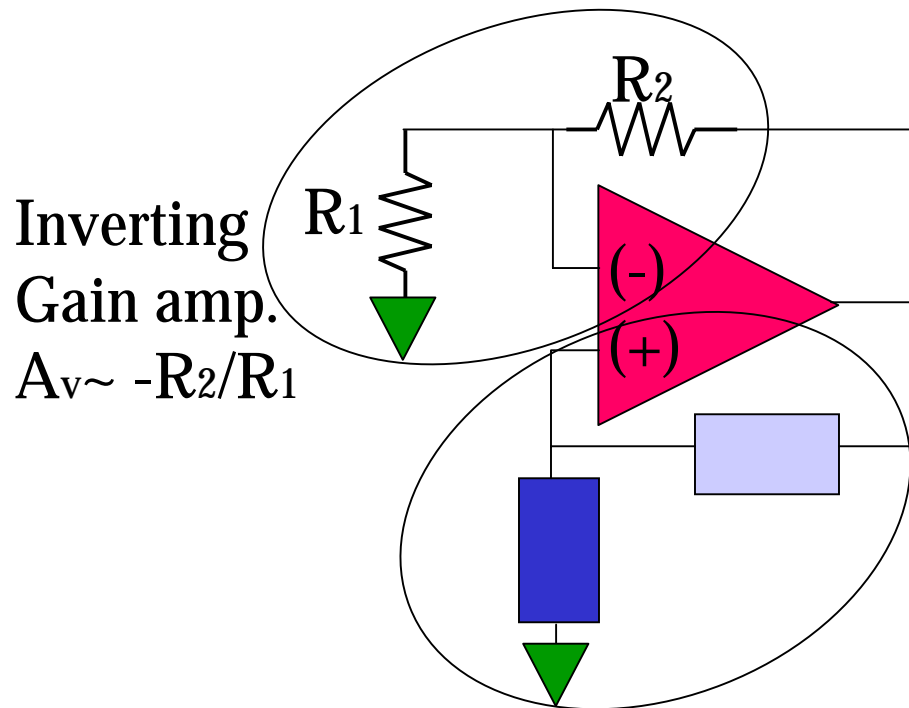


# Oscillations and Voltage-Controlled Oscillators

- Feedback perspective  $A = a / (1 - af)$ , if  $af = 1$  we get infinite gain...or oscillations
- From EE 122 the phase-shift oscillator specifically uses series-parallel RC network to:
  - Make  $|f| = 1/|a|$  and
  - Guarantee exact 0-degree phase shift
- Timing-based oscillations--this can be “ring oscillator” type or “charge-discharge” (of C) type
- Transistor level oscillations (which we’ll do now)

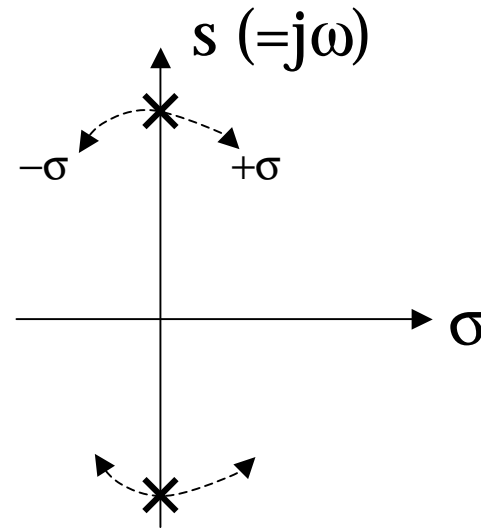Reminder about  
s-plane and poles  
moving into either  
LHP or RHP



Phase-shift  
Network  
 $\phi=0$  and  $f_0$   
and attenuating  
by  $1/A_v$


## Timer Circuits:

- Schmitt Trigger
- 555 IC
- Many others...

$$I = C \frac{dV}{dt}$$

$$\frac{C\Delta V}{I_x} = T_x$$

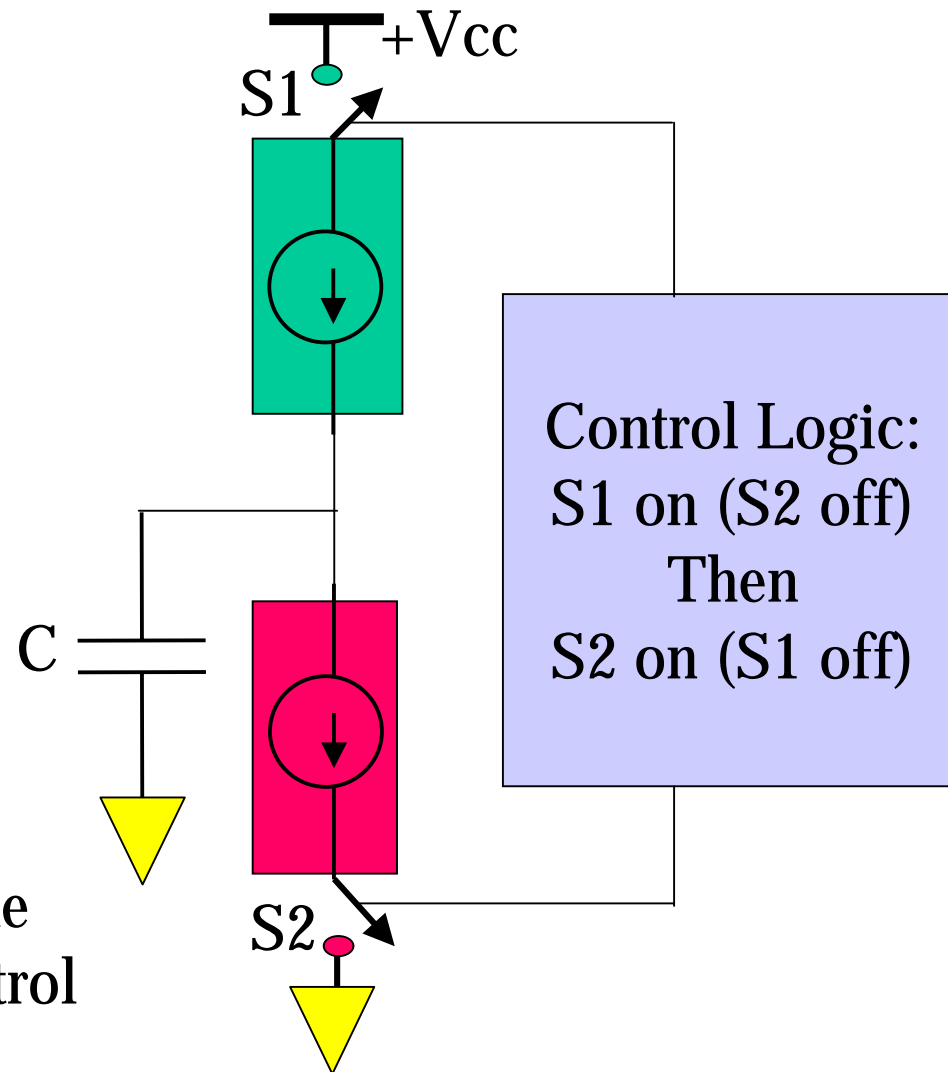“x” is the portion of the total period for which the respective “I<sub>x</sub>” is in control



## Colpitts Oscillator (Analysis and Design):

Read Chapter 5 (especially 5-5) in Krauss!

The following is a combination:


- First-order, small-signal analysis (Dutton)
- Improved “large signal” version (T. Lee)
- Discussion of Krauss’ version (ala 5-5)


### Common Base Amp.:


- Biasing like CE but!
- BIG Cap at base=ac ground
- Cap divider (ala Ch. 3) from collector back to emitter
- TANK circuit at collector
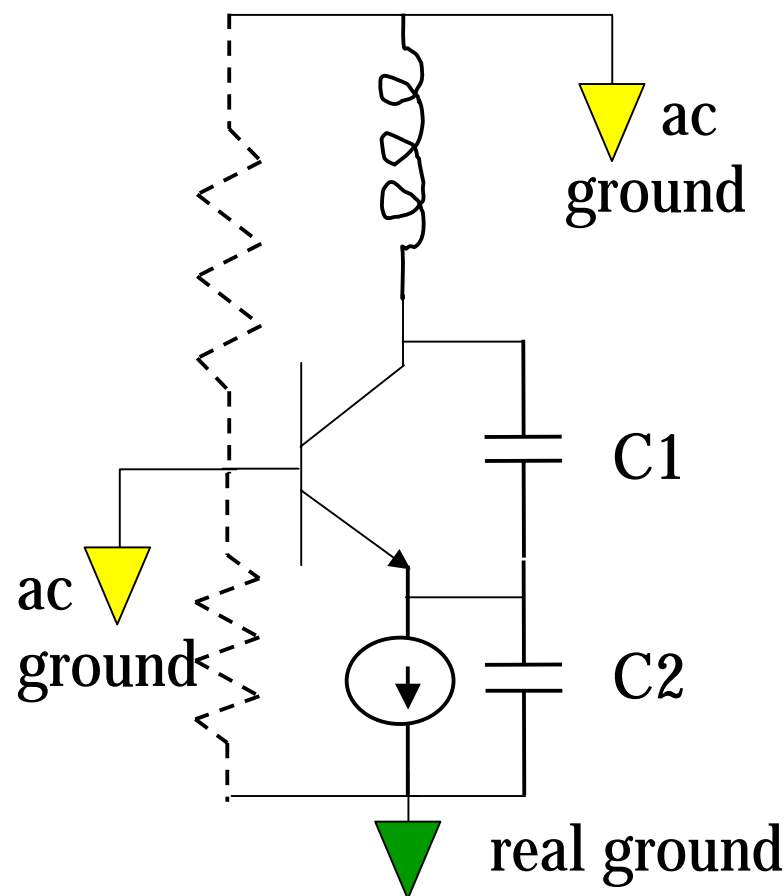
### Bottom-line:


CB=>non-inverting GAIN stage + Cap divider closes loop with  $\phi=0$  (I.e. oscillations)



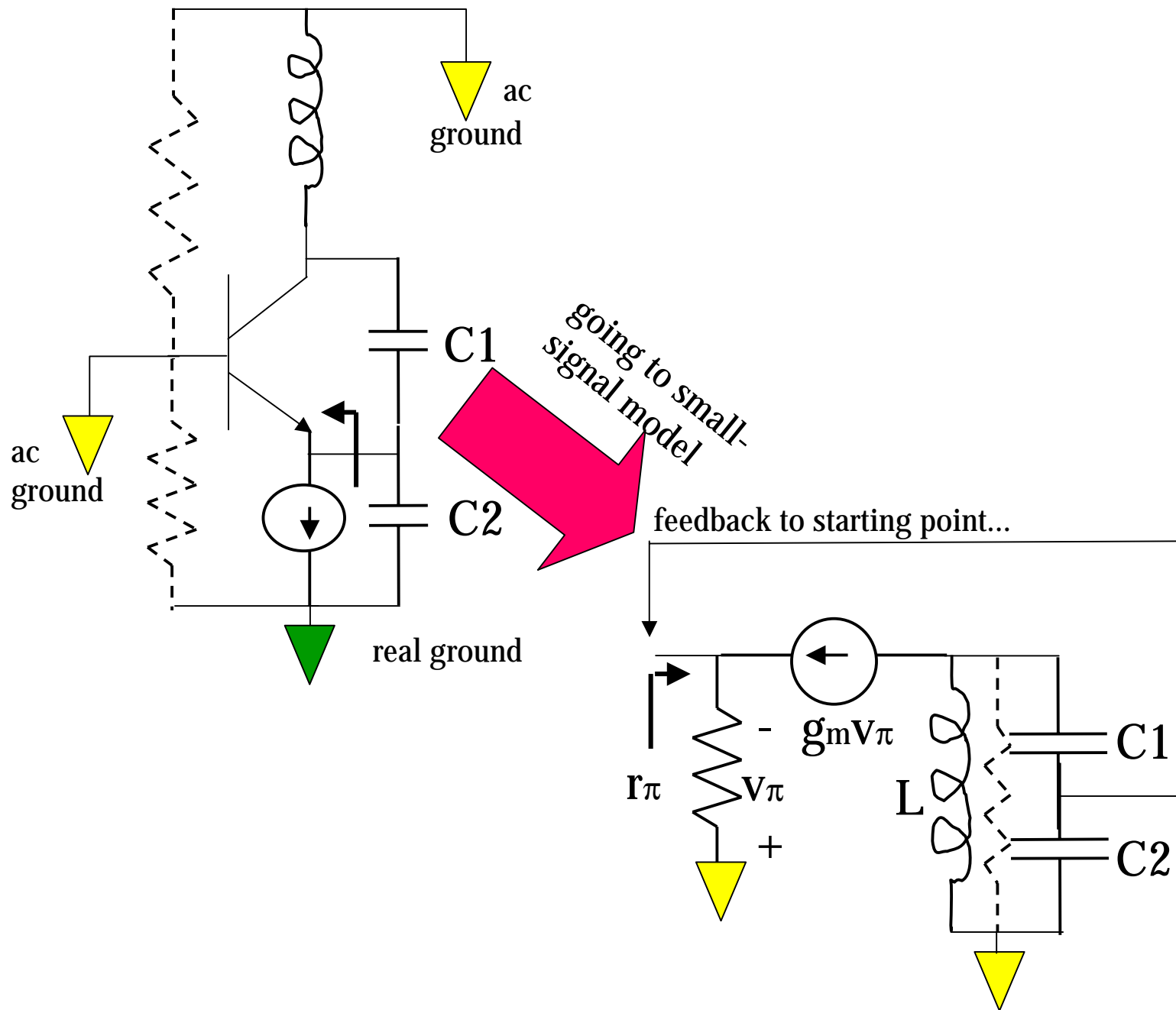

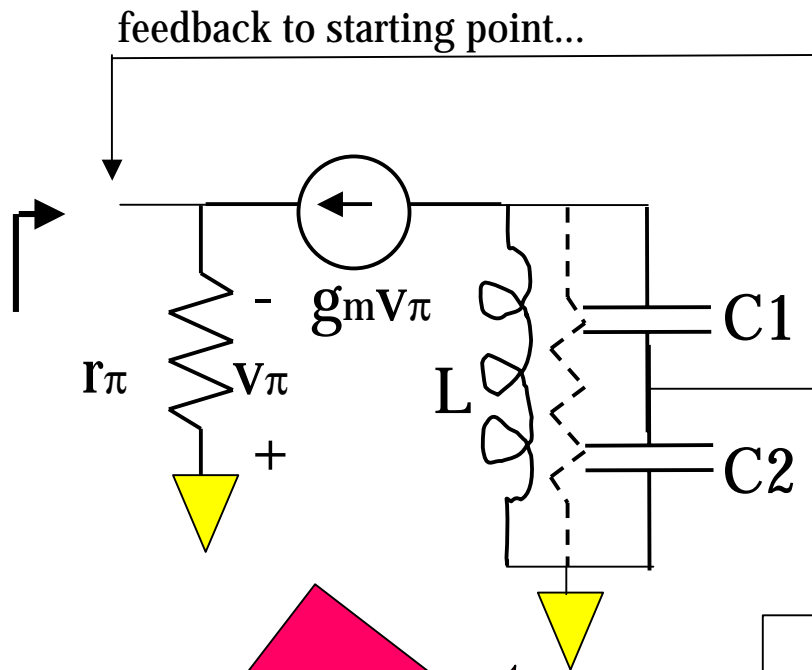

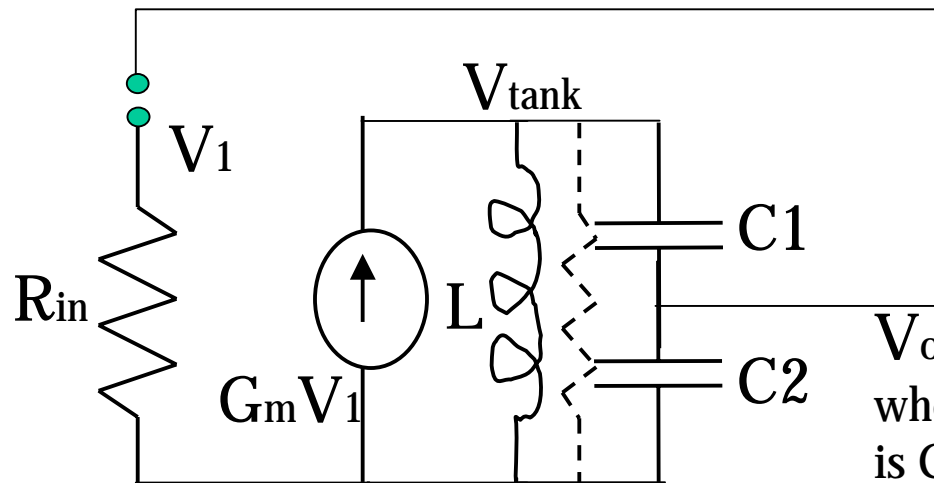And creating an equivalent two-port for transistor (which is written generally...either for small-sig. or equivalent as a large-signal behavior...)



$V_o = n V_{tank}$   
 where "n"  
 is Cap divider

Assume a  $V_1$ :

$$V_{\text{tank}} = +G_m V_1 Z_{\text{tank}}$$

at resonance,  $Z_{\text{tank}} = R_{\text{eq}} = R_{iT} \parallel R$   
(where  $R$  is all other resistances\* and  $R_{iT}$  comes from the impedance Transform of  $R_{\text{in}}$  based on  $C_1$  &  $C_2$ )

$$V_o = n V_{\text{tank}} = [C_1 / (C_1 + C_2)] V_{\text{tank}}$$

and, if  $V_o = V_1$  we will have condition for oscillations

\*Footnote: This notation follows T. Lee (copy from text attached); Krauss uses a different notation:  $R_t = R_L \parallel R_p$  (where  $R_p$  is from inductance  $L$  and  $R_L$  is an actual LOAD) and  $R_i$  includes both the intrinsic transistor ( $1/g_m$ ) and external added resistor  $R_e$

At the highest level, we can use simple feedback theory to emphasize a couple of points:

$$a = G_m R_{eq}$$

$$f = C_1 / (C_1 + C_2)$$

$$af = 1 \rightarrow \text{denominator is zero}$$

Note\*: this doesn't  
Specify where it  
Comes from...

---

\*Footnote: It turns out that, as shown in Fig. 16.6 (T. Lee book) the current flow in the device is highly non-linear (spiked in time as  $V_{BE}$  turns on) and we really can't use normal small-signal parameters for  $G_m$ . How to cope with that problem is discussed in Sect. 16.3.2 of T. Lee text (Ch.16)

This is a highlight  
summary of the T. Lee  
discussion, Ch. 16,  
Section 16.3.4...

Loading

$$\left( \frac{R_{iT}}{R_i} \right)^{\frac{1}{n}} = \frac{1}{n}$$

$$\therefore R_{iT} = \frac{R_i}{n^2} = \frac{1}{n^2 G_m}$$

$$R_{eq} = R \parallel R_{iT} = R \parallel \frac{1}{n^2 G_m}$$

*at..resonance:*

Voltage gain

$$v_{\tan k} = G_m v_1 \left( R \parallel \frac{1}{n^2 G_m} \right)$$

$$v_{\tan k} = (2 I_{bias}) \frac{R}{1 + n^2 G_m R}$$

*the..next..not – so – obvious..step..uses*

Closing the  
Loop... →

$$G_m = \frac{2 I_{bias}}{v_1} = \frac{2 I_{bias}}{n v_{\tan k}}$$

$$v_{\tan k} = \frac{2 I_{bias} R}{1 + \frac{n^2 \cdot R \cdot 2 I_{bias}}{n \cdot v_{\tan k}}} \Rightarrow$$

$$v_{\tan k} + n \cdot R \cdot 2 I_{bias} = 2 I_{bias} R$$

$$\therefore v_{\tan k} = 2 I_{bias} R \cdot (1 - n)$$

*Other..notation:*

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}; \dots \omega = \frac{1}{\sqrt{L C_{eq}}}; \dots n = \frac{C_1}{C_1 + C_2}$$

This is the bottom-line result, giving the final tank voltage in terms of the bias current, R and the voltage divider ration n.

Incidentally, if one were using the notation from Krauss, then R would actually be given by  $R_L || R_p$