

2X2 Quad==4Quad Multiplier

The following are qualitative and conceptual points about 2Q & 4Q Multipliers. Basically Prelab 2 and Lab 2 moves fairly quickly into useful chips that do multiplying. At one level you won't have to struggle with biasing etc. Nonetheless, it is really nice to have a grasp of how things fit together.




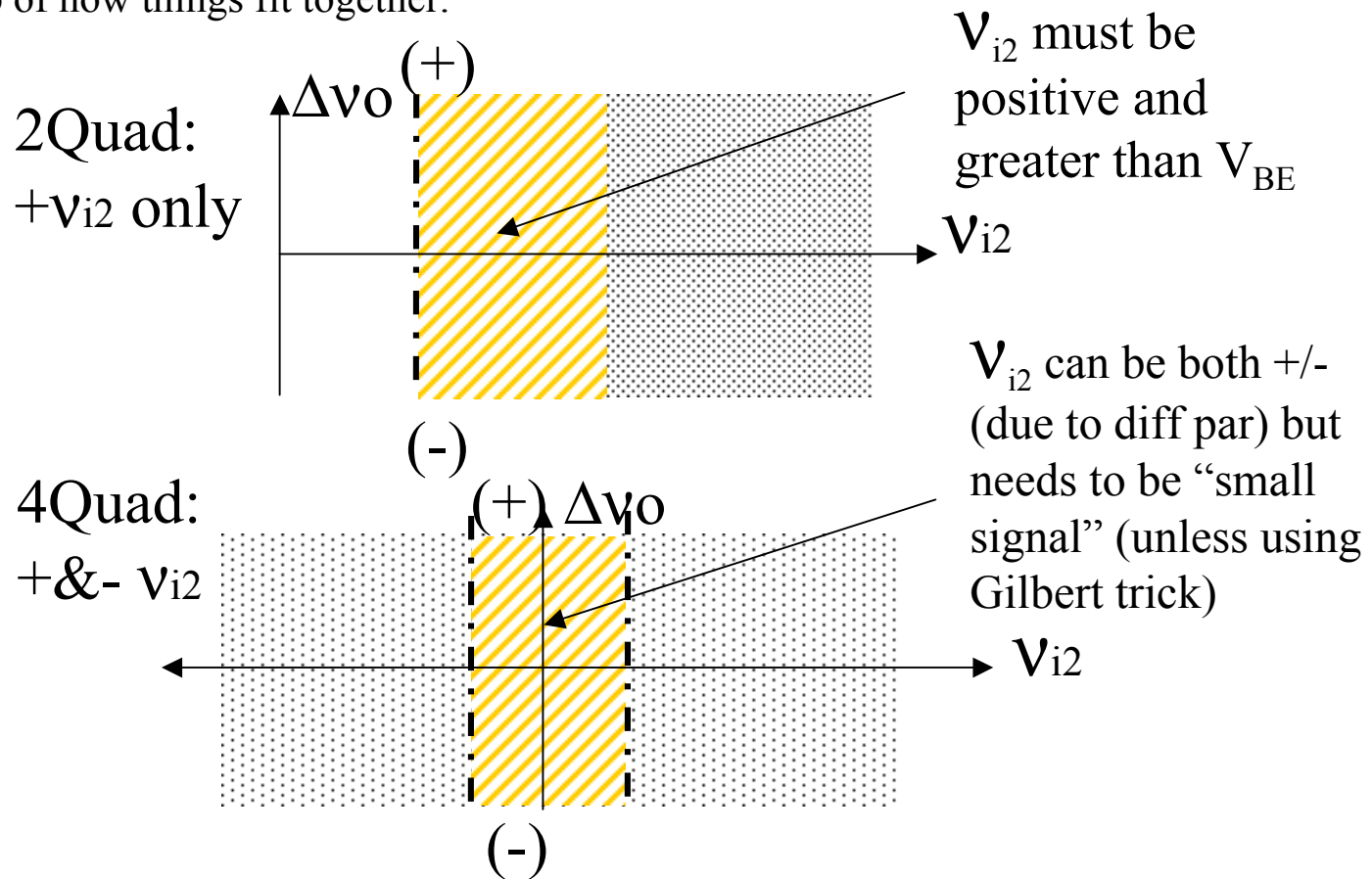
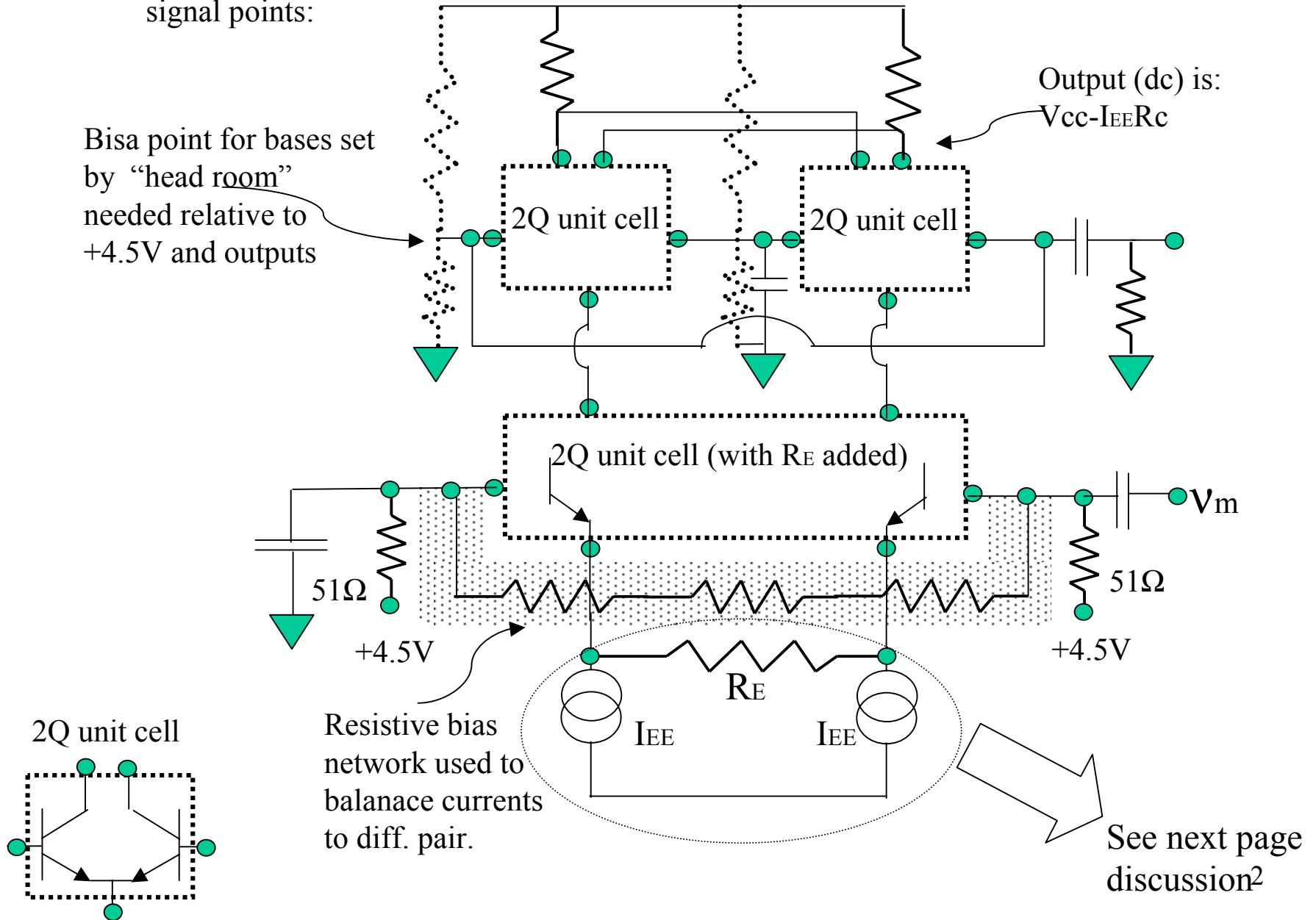


Fig 3 (prelab 2) can be redrawn as follows, primarily to emphasize the symmetry and bias vs signal points:

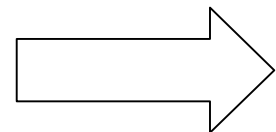


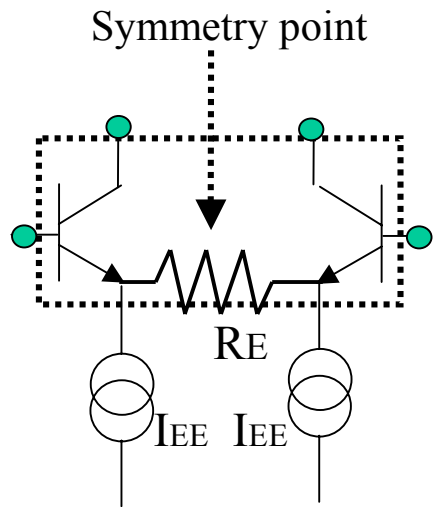

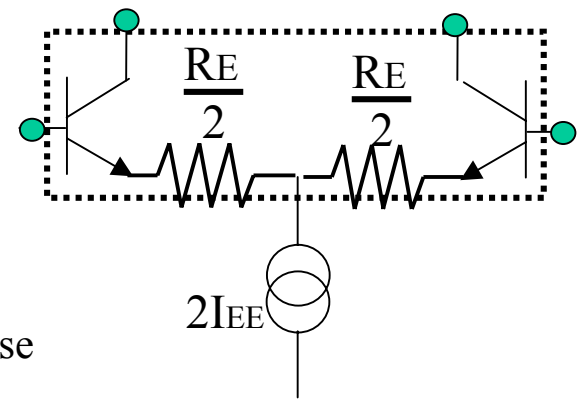Equivalence of these two circuits...both give same input-output per base & collectors



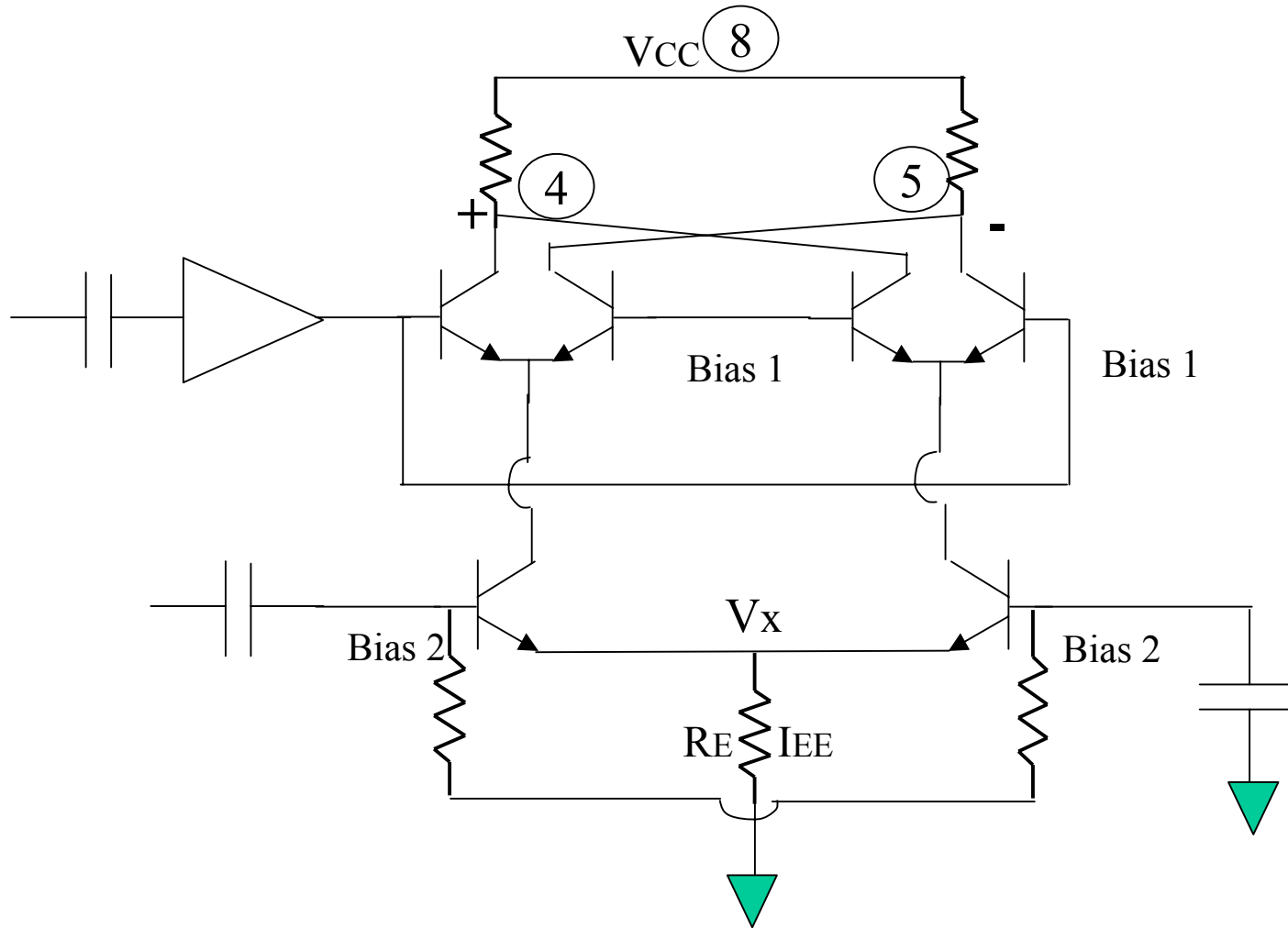Now, assuming all that made sense, look at Lab circuit ala 602:



Where are bias points (i.e. What voltages?) Start from nodes 4 & 5

$$\frac{V_{cc} - V_4}{R_c} = I_1 \quad ; \quad \frac{V_{cc} - V_5}{R_c} = I_2$$

$$I_{EE} = I_1 + I_2$$

If we know $R_E \Rightarrow V_x = I_{EE} R_E$


$$\therefore V_{BIAS2} = V_x + V_{BE}$$

$$V_{BIAS1} \Big|_{\min} = V_{BIAS2} + V_{BE} + V_{CE(sat)}$$


$$V_{BIAS1} \Big|_{\max} = V_4 = V_5$$

Basically, V_{BIAS1} needs to be somewhere between these limits.

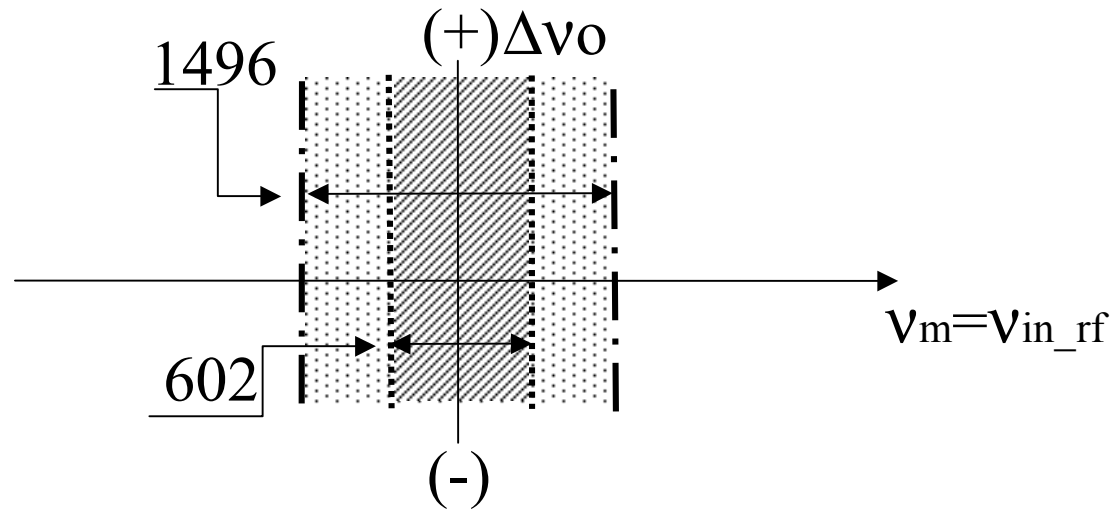Final comments on differences between Fig 3 (Prelab 2; "1496" circuit) and 602:




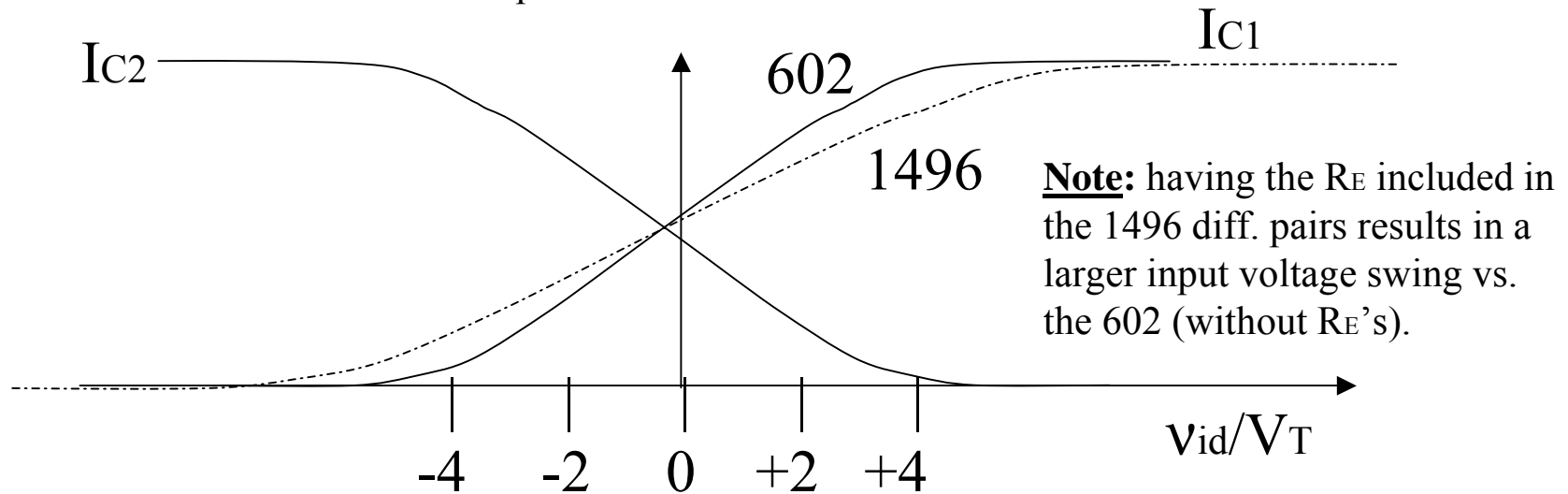Comment: the bottom diff pair limits how much swing at v_m . To understand, look at earlier discussion of differential pair.



Now, time for the down-and-detailed...Four Quad Multiplier:

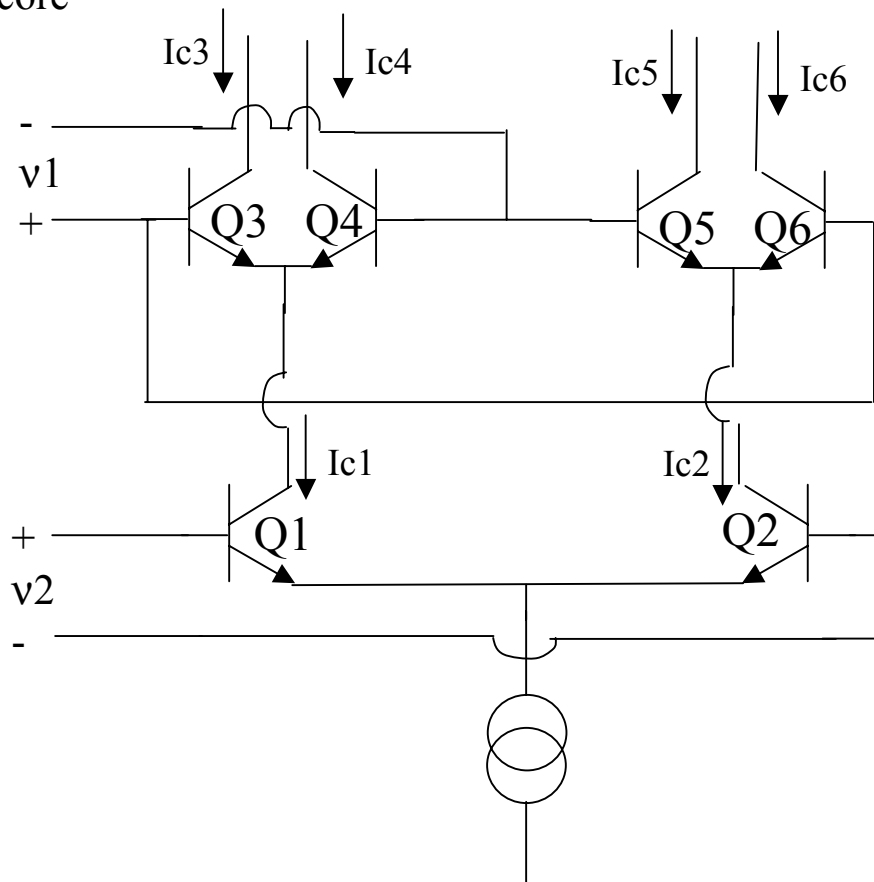Even with the beauty and simplicity of the multiplier with diff. Pair and current source, there are limits (2 quad, linearity, dynamic range...) The following is a fully symmetric 4 Quad "core"



By exact analogy to previous derivation for single diff pair

$$I_{c3} - I_{c4} = \frac{I_{c1}}{1 + e^{-v_1/V_T}} - \frac{I_{c1}}{1 + e^{+v_1/V_T}}$$


$$= \tanh\left(\frac{v_1}{2V_T}\right) \cdot I_{c1} \leftarrow \text{where } \frac{I_{EE}}{1 + e^{-v_2/V_T}}$$

and for Q5 - Q6

$$I_{c5} - I_{c6} = \tanh\left(\frac{v_1}{2V_T}\right) \cdot I_{c2} \leftarrow \frac{I_{EE}}{1 + e^{+v_2/V_T}}$$

Now taking $(I_{c3}-I_{c4})+(I_{c5}-I_{c6})$, the exponential terms involving $\exp\left(\pm \frac{v_2}{V_T}\right)$ Also reduce to tanh:
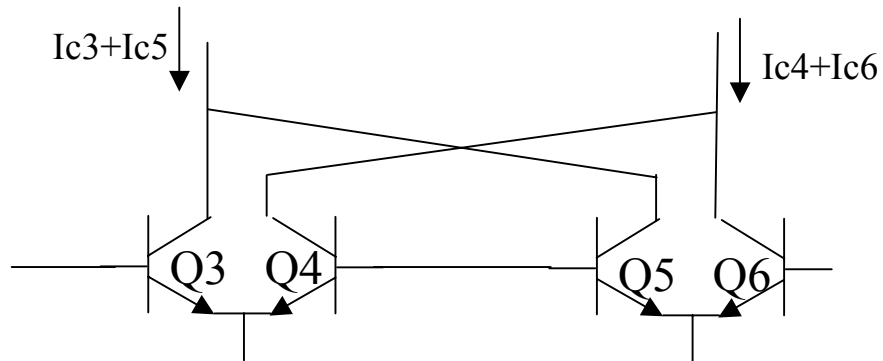
$$(I_{c3} - I_{c4}) + (I_{c5} - I_{c6}) = I_{EE} \tanh\left(\frac{v_1}{2V_T}\right) \cdot \tanh\left(\frac{v_2}{2V_T}\right)$$



The circuit connectivity to actually realize this $\tanh(x) \cdot \tanh(y)$ function is cross-coupled as shown and voltage output $R(I_{c3}+I_{c5})-R(I_{c4}+I_{c6})$

As noted in previous diff pair is equal to (2 Quad) discussions, there are both : limitations due to tanh functions and ways to "fix" and get around them:

- 1) Use small v_1 and v_2 (not always useful)
- 2) "linearize" lower diff pair by adding R_E to each emitter (quite useful)
- 3) "prescale" both x and y arguments (i.e. $x=\tanh^{-1}v_1$ and $y=\tanh^{-1}v_2$)

This last approach is the very elegant (and useful) Gilbert multiplier “with all the trimmings”).

There will be a handout on the fully prescaled Gilbert multiplier (but it will not be discussed further)

Distortion

We will consider two main kinds: harmonic (HD) and intermodulation (IM), lets start with HD and then come back to IM.

$$a \cos(\omega_1 t) \rightarrow A \rightarrow b_1 \cos(\omega_1 t + \phi_1) + b_2 \cos(2\omega_1 t + \phi_2) + b_3 \dots$$

$$HD_2 \equiv \frac{|b_2|}{|b_1|} \quad ; \quad HD_3 \equiv \frac{|b_3|}{|b_1|}$$

$$THD \equiv \frac{[b_2^2 + b_3^2 + \dots]^{1/2}}{|b_1|}$$

Using power series expansion on collector current, expressions for the diff pair:

$$\frac{I_{c2}}{I_{EE}} = \frac{1}{1 + \exp(d)} = \frac{1}{2} - \frac{d}{4} + \frac{1}{48}d^3 - \frac{1}{480}d^5 \dots$$

↑

note: d^2 term is not here!

This is different for the expression (and harmonic terms) we noted in Ch. 4 Krauss for a single CE amplifier)

Using $d = a \cos \omega_1 t$ and doing a bit of math/algebra
(see Mayaram & Pederson, Kluwer '91 p.17)

$$\frac{I_{c2}}{I_{EE}} = b_o^1 + b_1 \cos \omega_1 t + b_2 \cos 2\omega_1 t + b_3 \cos 3\omega_1 t \dots$$

$$b_o^1 = 1/2$$

$$b_3 = \frac{1}{192} \left(\frac{a}{V_T} \right)^3$$

$$b_1 = 1/4 \left(\frac{a}{V_T} - \frac{1}{16} \left(\frac{a}{V_T} \right)^3 \right) \quad \vdots$$

$$b_2 = 0$$

Figure 1.16 (Mayaram & Pederson) shows how these harmonics vary vs v_1/V_T (input signal in normalized units of V_T):

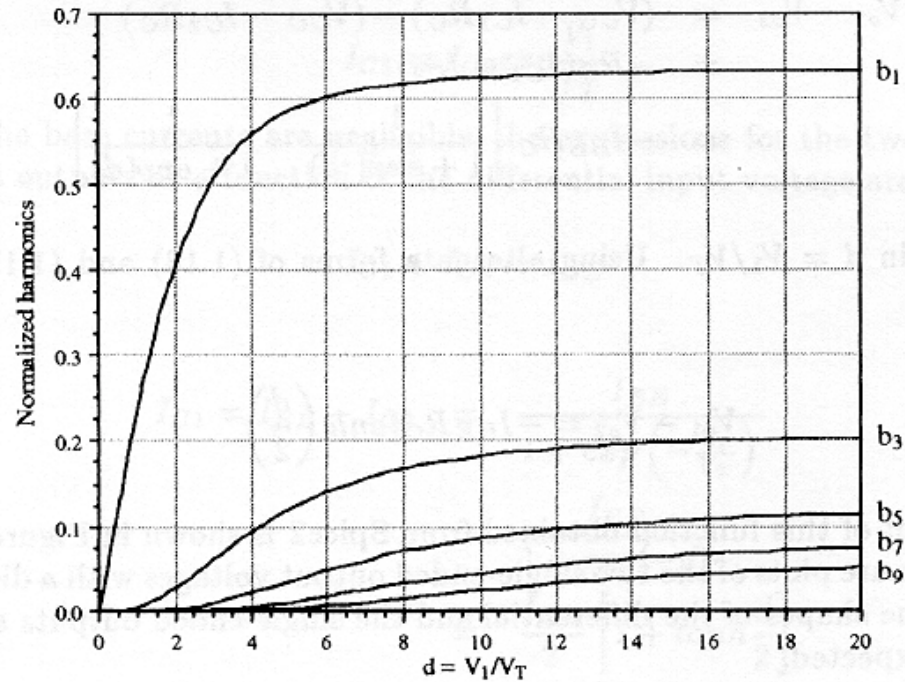


Figure 1.16: Normalized harmonics of the collector current in ECP.

From this figure we can easily estimate $HD_3\dots$ and THD. As noted above, $b_2 = 0 \quad \therefore \quad HD_2 = 0$ (good news for using diff. Pair). Analytically, HD_3 can be expressed:

$$HD_3 \simeq \frac{1}{48} \left(\frac{a}{V_T} \right)^2$$

$$\uparrow \frac{kT}{q}$$

Following a similar procedure for MOS device using the simple current expression:

$$I_D = k'W/L \left[(V_{Gs} - V_{TH})V_{DS} - \frac{1}{2}V_{DS}^2 \right]$$

$$HD_3(MOS) = \frac{1}{32} \left(\frac{a}{V_{GG} - V_{TH}(MOS)} \right)^2$$

If we use a single transistor (common emitter) amplifier, things: 1) get more complex and 2) performance is worse.

$$I_c = I_{CA} e^{v_1/V_T} \quad \text{where} \quad I_{CA} = I_s e^{V_{BE}/V_T}$$

$$\simeq I_{CA} \left[1 + \frac{v_1}{V_T} + \frac{1}{2} \left(\frac{v_1}{V_T} \right)^2 + \frac{1}{6} \left(\frac{v_1}{V_T} \right)^3 \dots \right]$$

Considering the case where $\frac{v_1}{V_T} \equiv d$

$$e^{(d \cos \omega_1 t)} = I_o(d) + 2I_1(d) \cos \omega_1 t + 2I_2(d) \cos 2\omega_1 t + \dots 2I_n(d) \cos n\omega_1 t..$$

Plotting the respective ratios $I_n(d)/I_0(d)$ we see something qualitatively like Fig 1.16 (Mayaram & Pederson) but much more severe quantitatively in terms of HD

Figure 2.6 (Mayaram & Pederson)

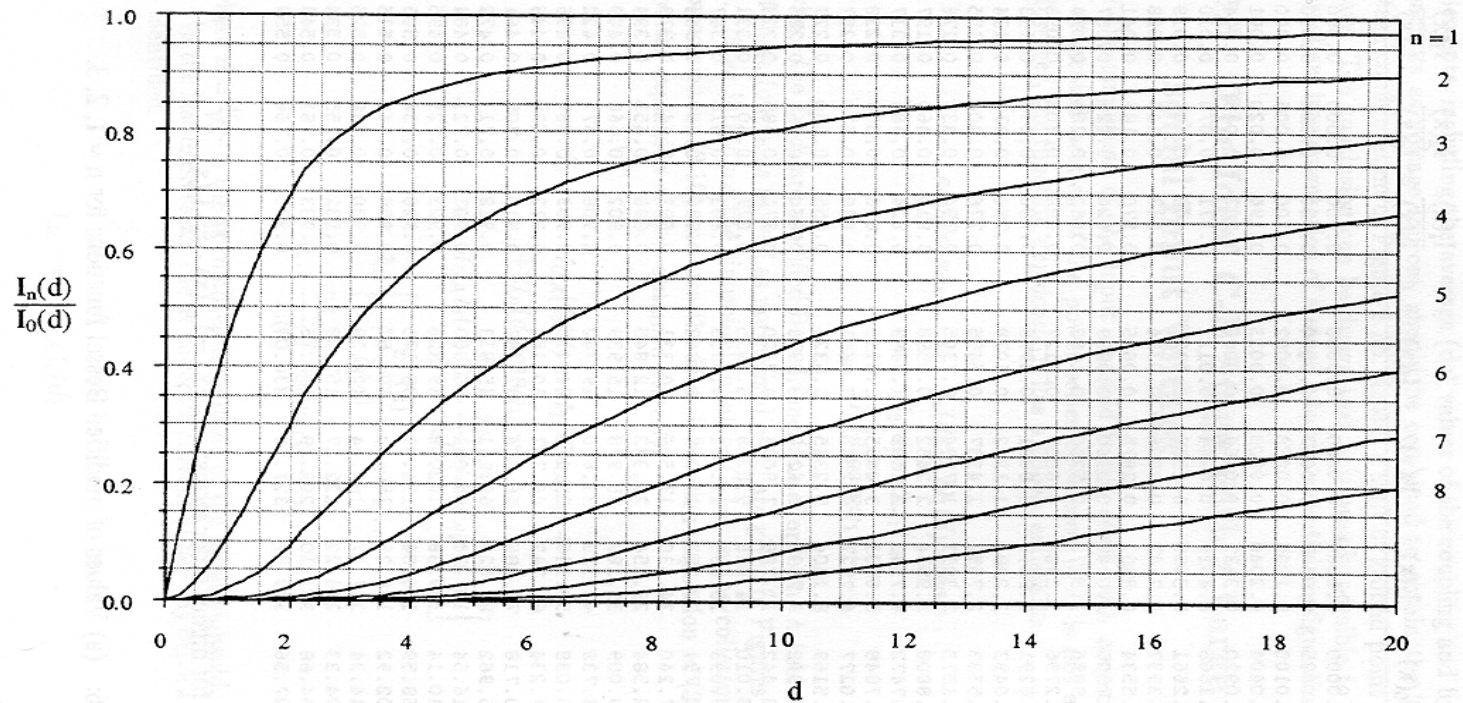


Figure 2.6: (b) Plot of normalized Bessel functions for $n = 1$ to 8.

Intermodulation (IM) distortion arises when multiple frequencies are present

$$v_i = v_{1a} \cos \omega_1 t + v_{2a} \cos \omega_2 t$$

$$v_o = a_1 v_i + a_2 v_i^2 + a_3 v_i^3 + \dots$$

Using v_i in v_o expression gives lots of terms. The primary ones of concern come from 3rd order as follows:.

$$a_3 v_i^3 = \dots a_{32} \cos(\omega_1 t \pm 2\omega_2 t) + a_{33} \cos(2\omega_1 t \pm \omega_2 t)$$

$$a_{32} = \frac{3a_3}{4} V_{1a} V_{2a}^2 \quad a_{33} = \frac{3a_3}{4} V_{1a}^2 V_{2a}$$

Assuming $V_{1a}=V_{2a}$, then approximately

$$IM_3 = \frac{V_o[IM_3]}{a_1 V_{1a}} = \frac{\frac{3}{4} a_3 V_{1a}^3}{a_1 V_{1a}} = \frac{3}{4} \frac{a_3}{a_1} V_{1a}^2$$

There are several basic points to note as well as practical considerations:

- the IM3 grows super linearly
- this means it overtakes the linear gain term (a big problem)
- we need to control output power to avoid such IM distortion problems (see figure and physical interpretation)