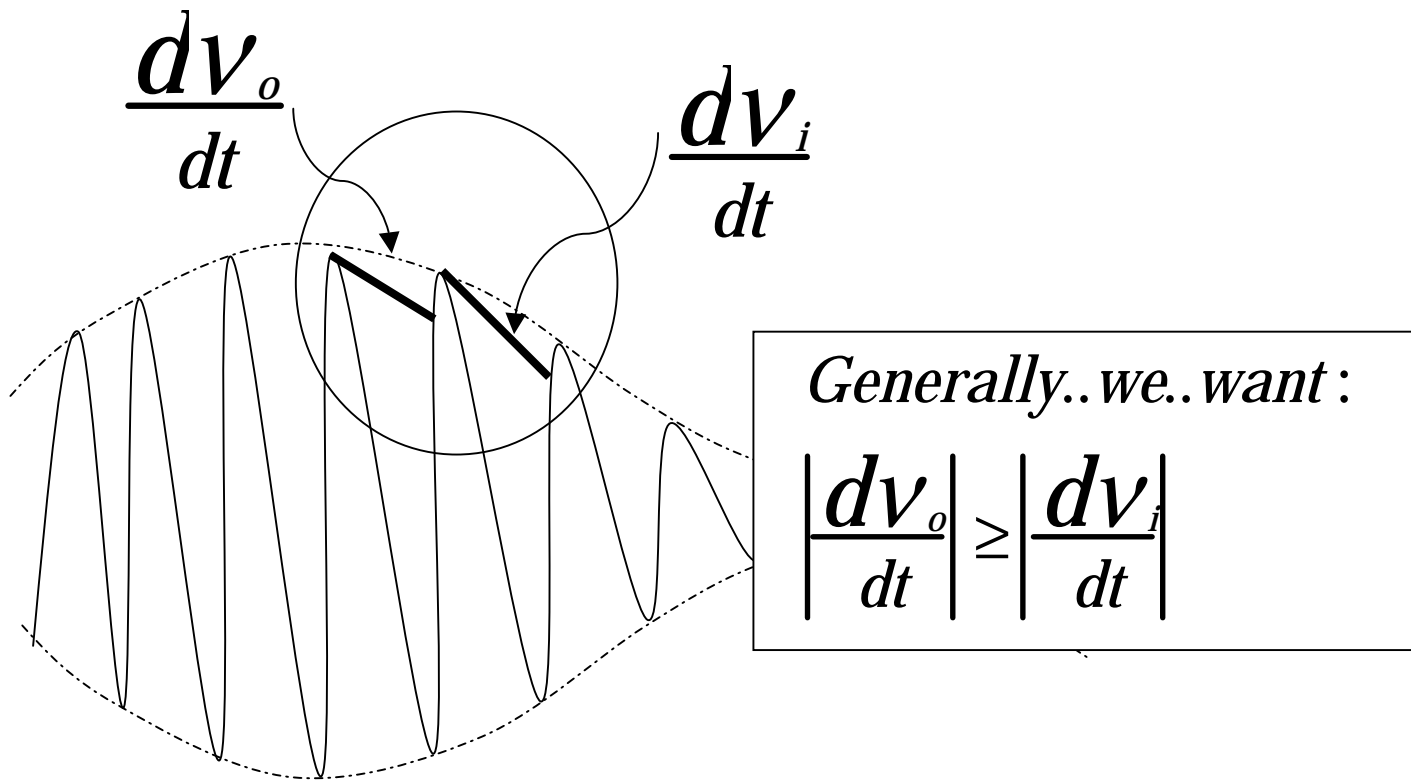


# Highlight (Preview) Summary of:

1) "Optimal" RC and 2) Diode Loading



Outline of Solution:

$$v_i = V_i (1 + m \cos \omega_m t)$$

$$v_o = V e^{-t/T_{RC}}$$

"Derivative inequality" gives

$$\frac{V}{T_{RC}} e^{-t/T_{RC}} \geq V_i m \omega_m \sin \omega_m t$$

Equating  $v_i = v_o$  (at some  $t$ ) gives

$$\frac{1 + m \cos \omega_m t}{T_{RC}} \geq m \omega_m \sin \omega_m t$$


And, rearranging followed by some trigonometry to minimize LHS of inequality...

$$\frac{(1-m^2)^{1/2}}{m} \geq \omega_m T_{RC} \quad \text{and, since } T_{RC} = RC,$$

$$C \leq \frac{(1-m^2)^{1/2}}{m} \frac{1}{\omega_m R} = \frac{\sqrt{\left(\frac{1}{m^2}\right) - 1}}{\omega_m R}$$

← KEY EQUATION

## Diagonal Clipping

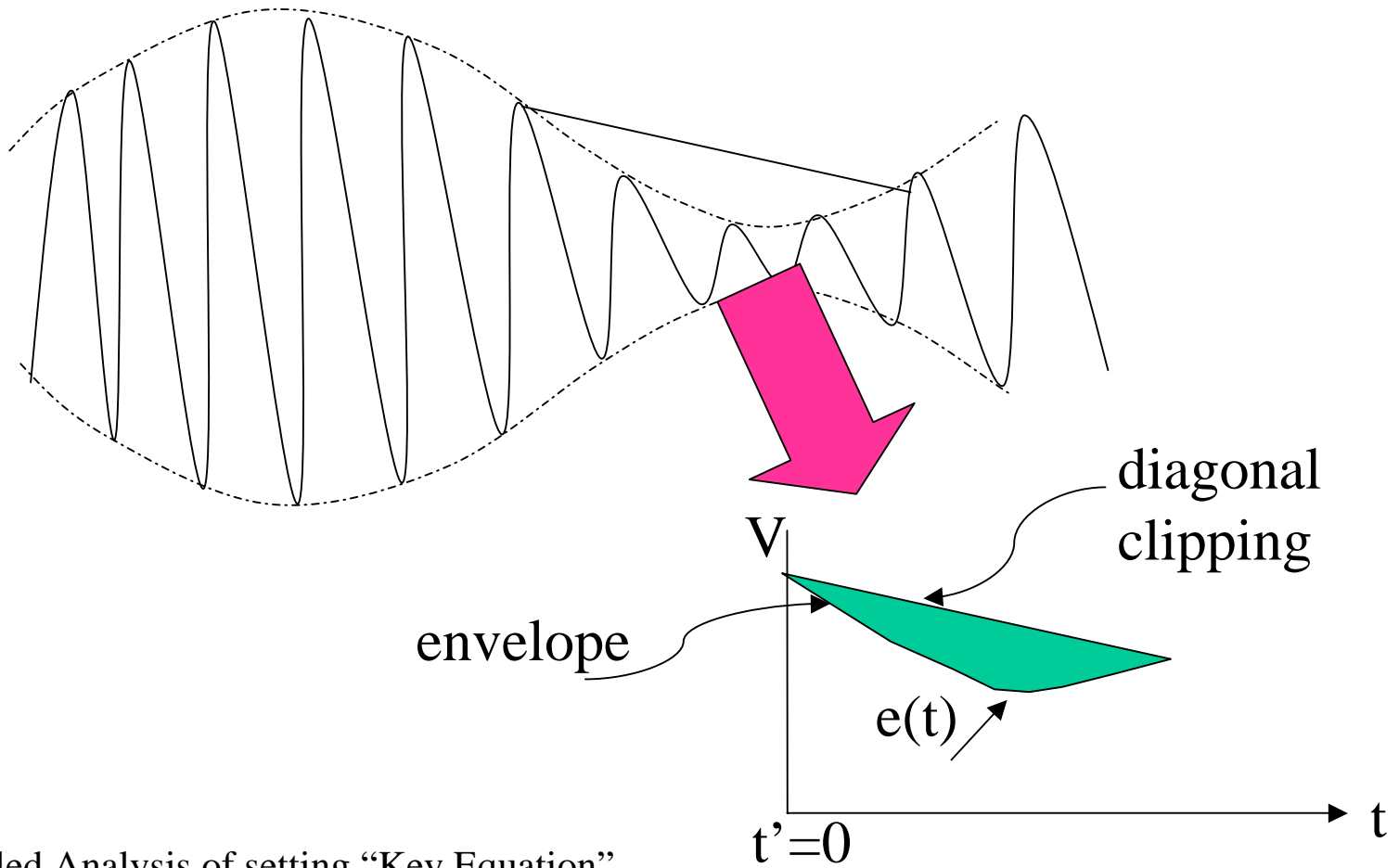

Detailed Analysis of setting “Key Equation”

$$\text{Envelope: } e(t) = Va(1 + m\cos\omega_m t)$$

The voltage across the capacitor when the diode is off is

$$v_o(t) = Ve^{-t'/\tau}, \text{ where } \tau \equiv RC$$

t'=time since diode turn off

To avoid diagonal clipping require  $\left| \frac{dv_o}{dt} \right| \geq \left| \frac{de(t)}{dt} \right|$  at  $t' = 0$  i.e.  $t = t'$

$$\text{or } \frac{dv_o}{dt} \leq \frac{de(t)}{dt} \text{ since slopes are negative \&}$$

sign is included in slope

$$\Rightarrow -\frac{V}{\tau} \leq -V_A m \omega_m \sin \omega_m t'$$

$$\text{or } V_A m \omega_m \sin \omega_m t' \leq \frac{V}{\tau}$$

Note that  $V = V_A (1 + m \cos \omega_m t')$

$$\Rightarrow V_A m \omega_m \sin \omega_m t' \leq \frac{V_A}{\tau} (1 + m \cos \omega_m t')$$

or 
$$\frac{1 + m \cos \omega_m t'}{m \sin \omega_m t'} \geq \omega_m \tau$$

To ensure that this condition is satisfied make

$$\left. \frac{1 + m \cos \omega_m t'}{m \sin \omega_m t'} \right|_{\min} \geq \omega_m \tau$$

To obtain the minimum take derivative w.r.t.  $t'$  and equate to zero, i.e.,

$$-\omega_m \cos \omega_m t' \left( \frac{1 + m \cos \omega_m t'}{m \sin^2 \omega_m t'} \right) - \frac{m \omega_m \sin \omega_m t'}{m \sin \omega_m t'} = 0$$

$$\text{i.e. } -\omega_m \cos \omega_m t' - \underbrace{m \omega_m \cos^2 \omega_m t' - m \omega_m \sin^2 \omega_m t'}_{-m \omega_m} = 0$$

$$\text{i.e. } \cos \omega_m t' = -m$$

$$\Rightarrow \sin \omega_m t' = \sqrt{1 - m^2}$$

$$\therefore \text{minimum value is } \frac{1 - m^2}{m \sqrt{1 - m^2}} = \frac{1}{m} \sqrt{1 - m^2}$$

$$\therefore \frac{1}{m} \sqrt{1 - m^2} \geq \omega_m \tau = \omega_m RC$$

$$\therefore C \leq \frac{1}{R \omega_m} \sqrt{\frac{1 - m^2}{m}}$$


← same "key equation"

Remark


If C is increased above this value diagonal clipping or failure to follow distortion results.

Above notes provided by Prof. Karti MAYARAM of Oregon State Univ.
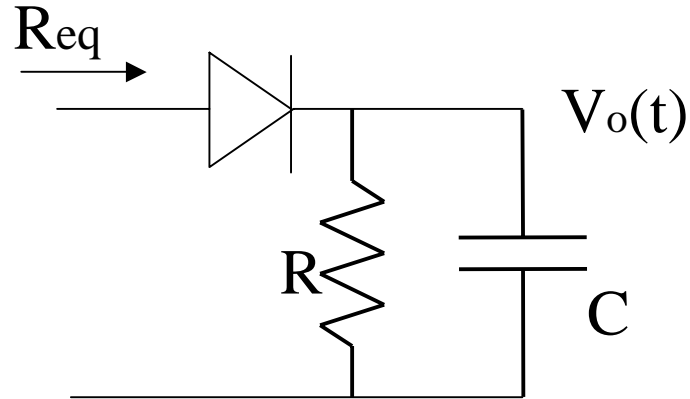
### Equivalent Impedance of Diode/RC Load



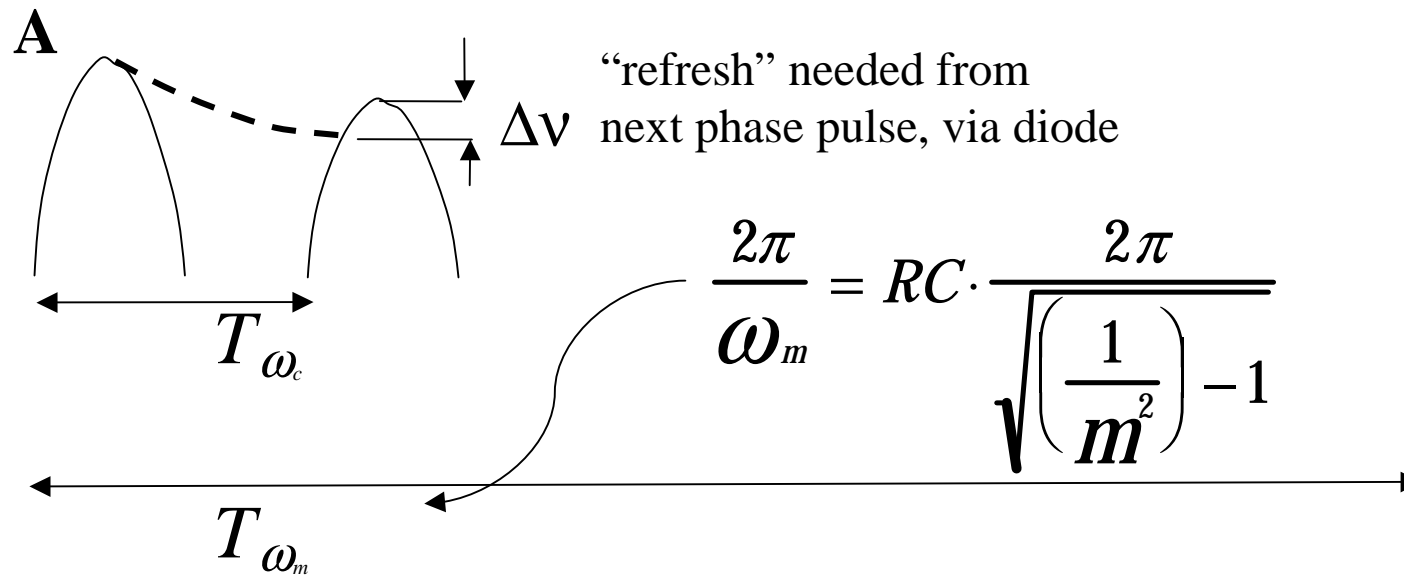What equivalent load is seen by the tank circuit due to diode and RC?



$$v_{out}(t) = Ae^{-t/RC} \approx A\left(1 - \frac{t}{RC}\right)$$

$$\Delta E = \frac{1}{2}C(V_i^2 - V_f^2)$$

$$= \frac{1}{2}C\left(A^2 - A^2\left(1 - \frac{2T_{\omega_c}}{RC} + \frac{T_{\omega_c}^2}{(RC)^2}\right)\right)$$

$$= \frac{1}{2}CA^2\left(\frac{2T_{\omega_c}}{RC} - \frac{T_{\omega_c}^2}{(RC)^2}\right) \text{ and if } T_{\omega_c} \ll RC$$

$$\approx \frac{1}{2}C\left(\frac{2T_{\omega_c}}{RC}\right)A^2$$

From  $R_{eq}$  side  $\Delta E = \frac{1}{2} \frac{A^2}{R_{eq}} T_{\omega_c}$

$$R_{eq} \approx R/2 \text{ wow, simple result!}$$