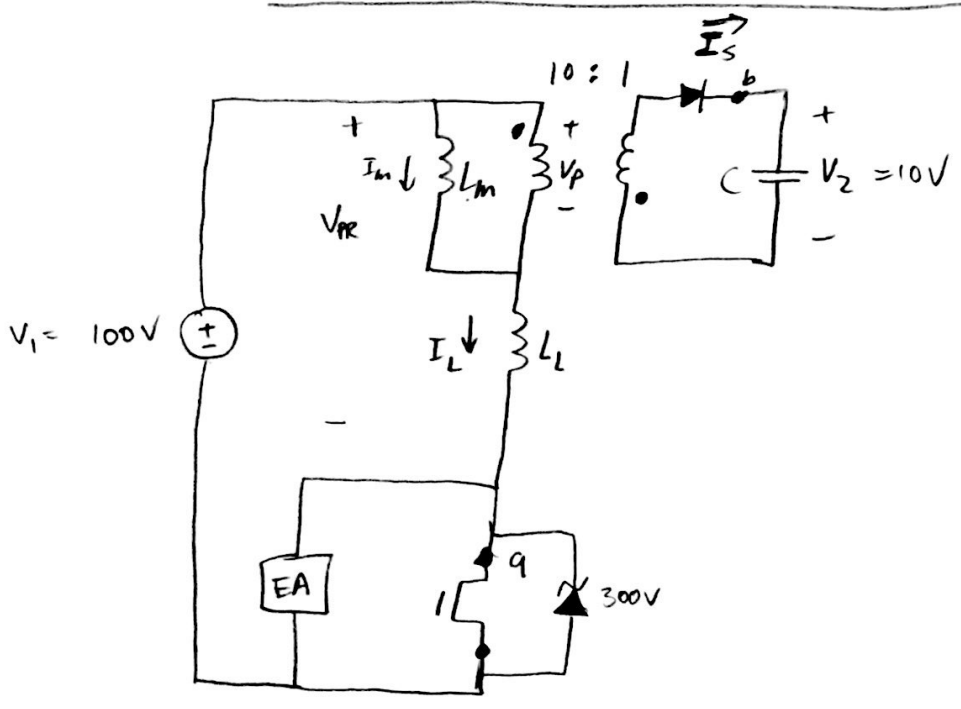


EE 255 HOMEWORK # 5 SOLUTIONS

①



(a) 100kHz, $L_m = 100 \mu\text{H}$, $L_L = 5 \text{mH}$

Output energy = $(10\text{V})(5\text{A})(10\mu\text{s}) = 0.5 \text{mJ/cycle}$.

The peak current through L_m is $I_{\text{peak}} = \frac{V_1}{L_m + L_L} \cdot D_1 T_{\text{cy}}$

The energy stored in L_m must equal 0.5mJ every cycle. Thus:

$$\frac{1}{2} L_m I_{\text{peak}}^2 = 0.5 \text{mJ}, \text{ Thus: } \frac{1}{2} L_m \left(\frac{V_1}{L_m + L_L} \cdot D_1 T_{\text{cy}} \right)^2 = 0.5 \text{mJ}$$

Substituting L_m, L_L, T_{cy} , and V_1 , we solve for $D_1 = 0.332039$

$$(b) \text{Loss}_{L_L} = \frac{1}{2} L_L I_{\text{peak}}^2 = \frac{1}{2} L_L \left(\frac{V_1}{L_m + L_L} \cdot D_1 T_{\text{cy}} \right)^2 = 25 \mu\text{J/cycle} = \text{Loss}_{L_L}$$

$$\text{Efficiency} = \frac{\text{output energy/cycle}}{\text{output energy/cycle} + \text{Loss}_{L_L}} = \frac{500 \mu\text{J}}{525 \mu\text{J}} = \eta = 95.24\%$$

EE 255 HOMEWORK #5 SOLUTIONS


(c) We know $I_{peak} = \left(\frac{V_1}{L_M + L_L} \right) \cdot D_1 T_{cy} = 3.16227 A$

$$\Delta t_{commutation} = \frac{\Delta I}{V_{FET} - V_1 - 10V_2} \cdot L_L = \frac{3.16227 A}{100V} \cdot 50\mu H = \boxed{0.158 \mu s}$$

The voltage during commutation across L_L is the 300V of the avalanche diode less the 100V from the reflected secondary (i.e. $10V_2$), and the 100V supply (i.e. V_1).


(d) 200 kHz, $L_M = 1mH$, $L_L = 0 \mu H$, we know by volt second balancing while ignoring L_L that $V_2 = \frac{ND_2}{1-D_2} V_1$, where $V_2 = 10V$, $V_1 = 100V$, $N = \frac{1}{10}$, so D_2 , or the duty factor across the magnetizing inductance, **must be 0.5**. (With $L_L = 50\mu H$)

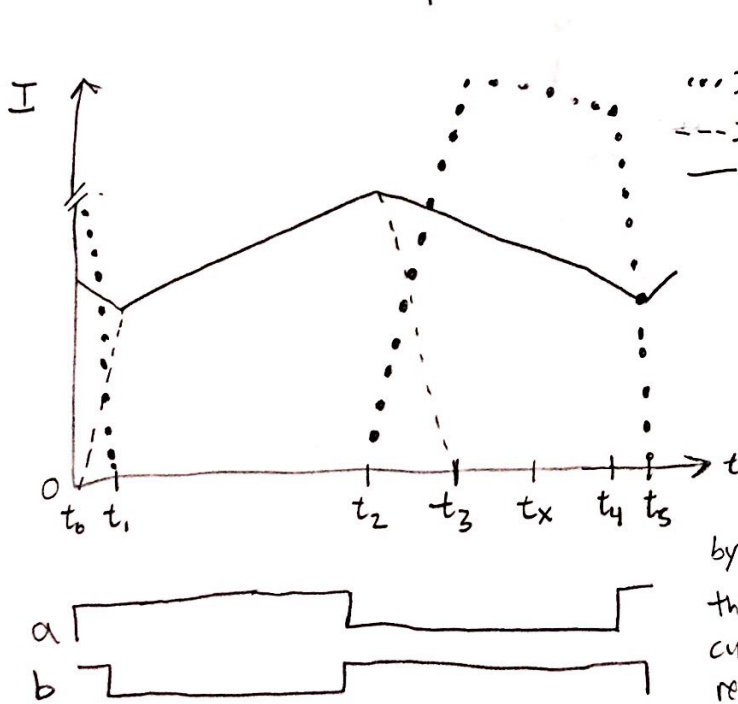(e) in part (e), we have commutation time where both the FET and diode are conducting. Let's draw our expected current curves. As you can see this is quite complicated.



First of all, we know over one cycle the integral of our output current, I_s , is $(5A)(5\mu s) = 25\mu C$. We can break down the I_s curve into three components: from (t_2-t_3) , from (t_3-t_4) , and from (t_4-t_5) . We need to solve for these three times and currents after figuring out our new initial duty factor without commutation time, which can be done with a volt second balance given L_M and L_S create a voltage divider of $\left(\frac{1000}{1050} \right) \cdot 100V = 95.2V$, when "a" is closed. Once we know this, we find the times and currents, by using $\frac{\Delta I}{\Delta t} = \frac{V}{L}$ for the leakage inductance and knowing the area is $25\mu C$. This then sets the magnetizing current. From inspection, we can see that we have to redo all our calculations to converge to our final answer, we thus use LTspice to avoid excessive

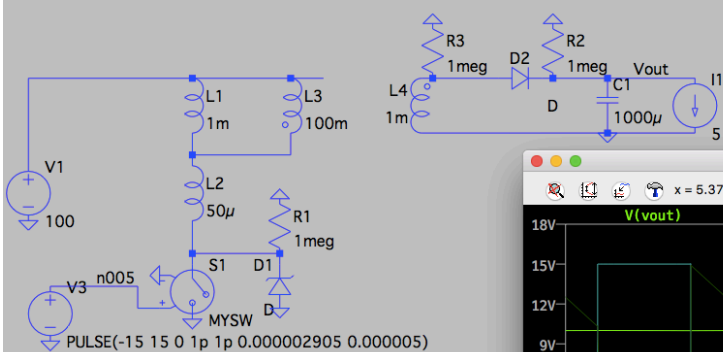hand calculations. we find that a **DF of 0.581** (due to commutation time loss) we meet our specs.



```

.model MYSW SW(Ron=0.0001 Roff=100000k Vt=5)
.model D2 D(Ron=0.01 Roff=1000k Vfwd=0.0)
.model D1 D(Ron=0.01 Roff=10k Vfwd=0.0 Vrev=300)
.tran 15m
.ic V(vout) 10
K1 L3 L4 1

```

