

EE155/255 Green Electronics

Embedded Software
Power Devices
10/2/17

Prof. William Dally
Computer Systems Laboratory
Stanford University

Logistics



- Lab group assignments
 - Go to Canvas and group yourselves – or we will group you
- Homework 1 due Today – by 9am in box outside Sue's office
- Sign up for Lab signoff time
 - Lab 1 must be signed off this week
- Sign up for Piazza
 - piazza.com/stanford/fall2017/ee155ee255
- Discussion sections
 - Fridays 4:30-5:50PM
 - STLC 118

Course at a Glance

No	Date	Topic	HW out	HW in	Lab out	Lab ck	Lab	HW
1	9/25/17	Intro (basic converters)	1		1		Intro to ST32F3	Periodic Steady State
2	9/27/17	Embedded Prog/Power Elect.						
3	10/2/17	Power Electronics - 1 (switches)	2	1	2	1	AC Energy Meter	Power Devices
4	10/4/17	Power Electronics - 2 (circuits)						
5	10/9/17	Photovoltaics	3	2	3	2	PV MPPT	Motor control Matlab
6	10/11/17	Feedback Control						
7	10/16/17	Electric Motors	4	3	4	3	Motor control - Lab/	Feedback
8	10/18/17	Isolated Converters						
9	10/23/17	Solar Day	5/PP	4	5	4	PS	Isolated Converters
10	10/25/17	Magnetics						
11	10/30/17	Soft Switching	6	5/PP	6	5	Magnetics	Magnetics and Inverters
12	11/1/17	Project Discussions						
13	11/6/17	Inverters, Grid, PF, and Batteries		6	P	6	Project	
14	11/8/17	Thermal & EMI						
15	11/13/17	Quiz Review				C1		
16	11/15/17	Grounding, and Debugging						
Q	11/15/17	Quiz - in the evening						
	11/20/17	Thanksgiving Break				C2		
	11/22/17	Thanksgiving Break						
17	11/27/17	Wrapup						
18	11/29/17	Guest Lecture				C3		
19	12/4/17	Guest Lecture						
20	12/6/17	No Class						
	TBD	Project presentations			P			
	12/15/17	Project webpage due						

PSSA in One Slide

- Green energy systems are made from voltage converters
 - PV systems, electric/hybrid cars, wind power, etc...
 - Power path + intelligent control
- Separate behavior into fast and slow
 - Fast – within switching cycle
 - Slow – $f \ll f_{cy}$
- Within cycle solve for **periodic steady state**
 - State variables the same at start and end of cycle.
- For slow transient response
 - Write difference equations
- Buck/Boost Topologies

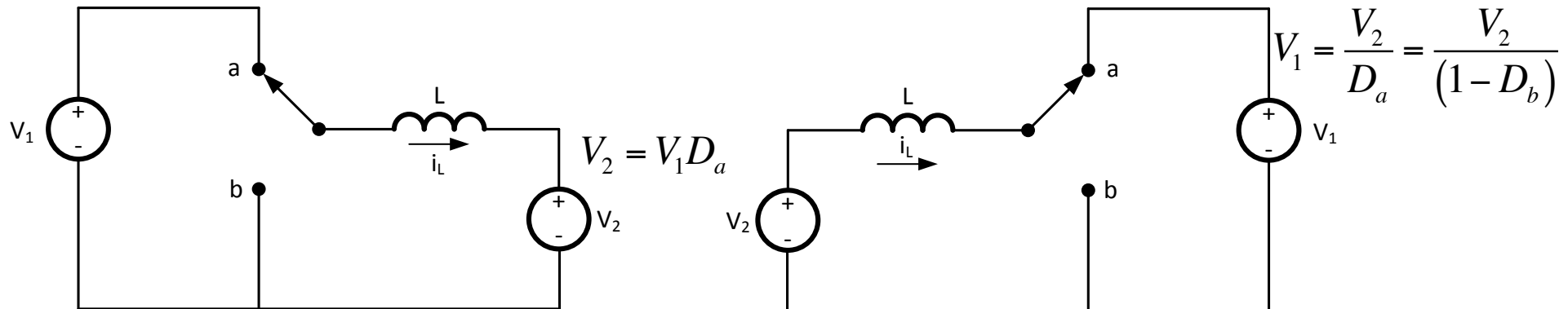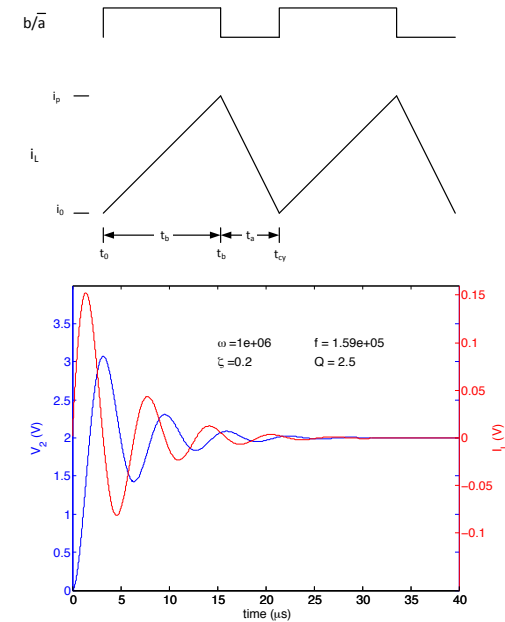


Embedded Software in One Slide

- Real-time, Event driven
 - Timer schedules periodic events (make sure work is done before next event)
 - I/O devices signal completion
- Integer and FP Arithmetic
 - Scale your numbers, avoid divides
- Layered design
 - UI – avoid modes, label buttons, it should be obvious
 - Control – at different frequencies
 - Monitoring and Housekeeping


Organization of Code

- Control
- User Input
- Display
- Monitoring
- Housekeeping

Layered Control: Example Battery Charger

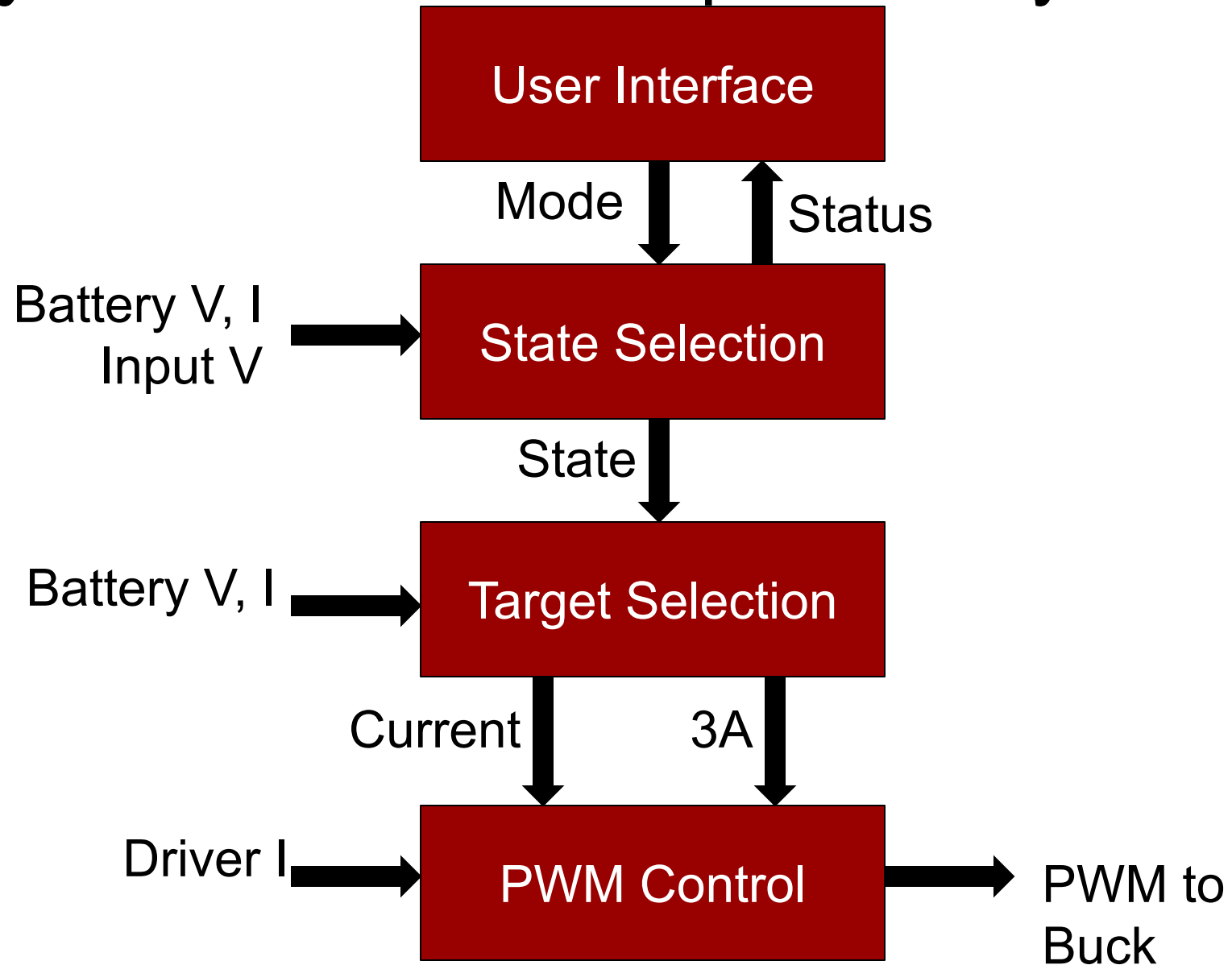

Layered Control: Example Battery Charger

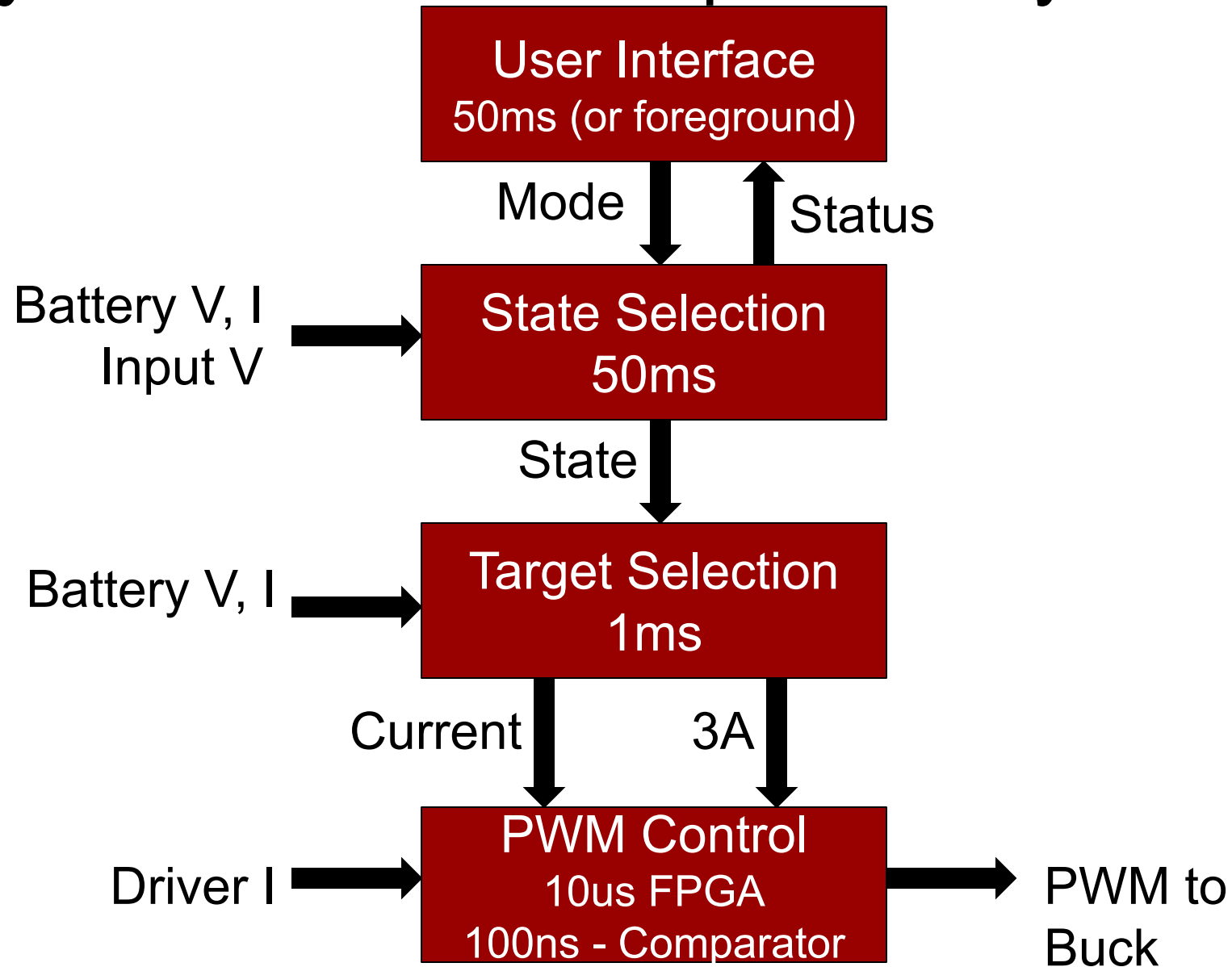



Example Photovoltaic Controller

- Mode selection
 - Line test, Panel test, MPPT, etc...
- Monitors
 - Line (current, voltage, frequency, ...) (anti-islanding)
 - Internal operation (voltages, currents, temps)
 - Panels (current, voltage)
- Maximum Power-Point Tracking
 - Search algorithm for peak power point
- Inverter control
 - Convert 400V DC to 240V AC – in sync with line
- User interface
 - Display status, serial output, network connections, ...

Power Electronics



Part 1 – Power Devices

Real Switches

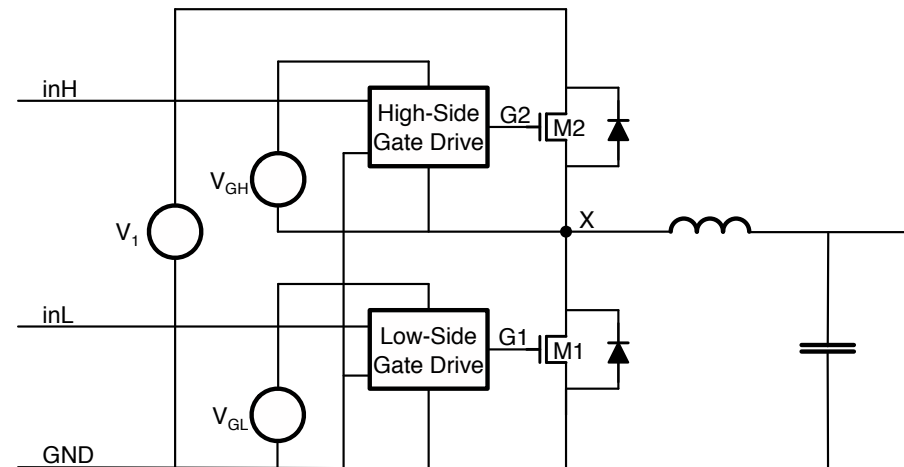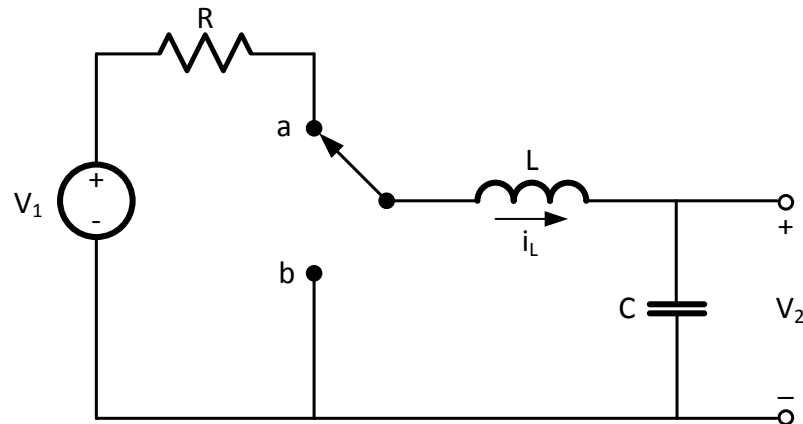


Real Switches

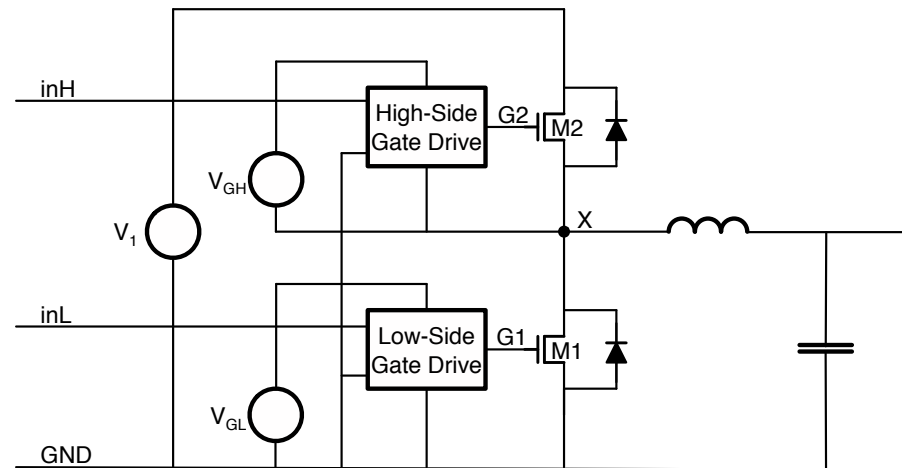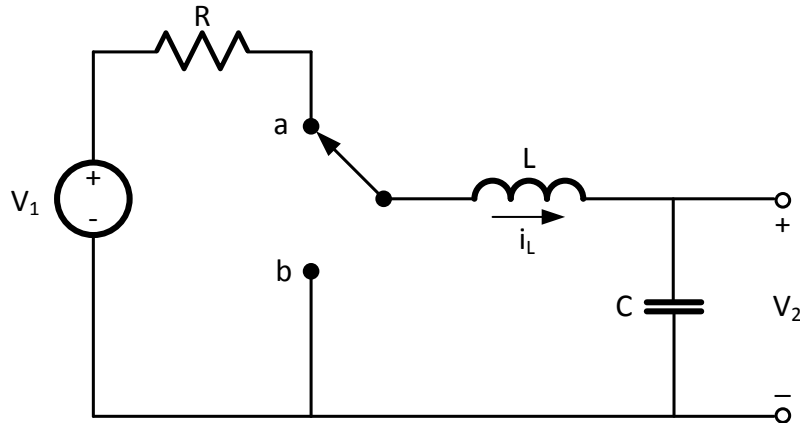- Finite switching time
- Finite voltage blocking
- Non-zero on resistance
- Parasitic L and C
- Need gate-drive supplies



Quick Summary in a Few Pictures

DC I-V Characteristics of On Switches

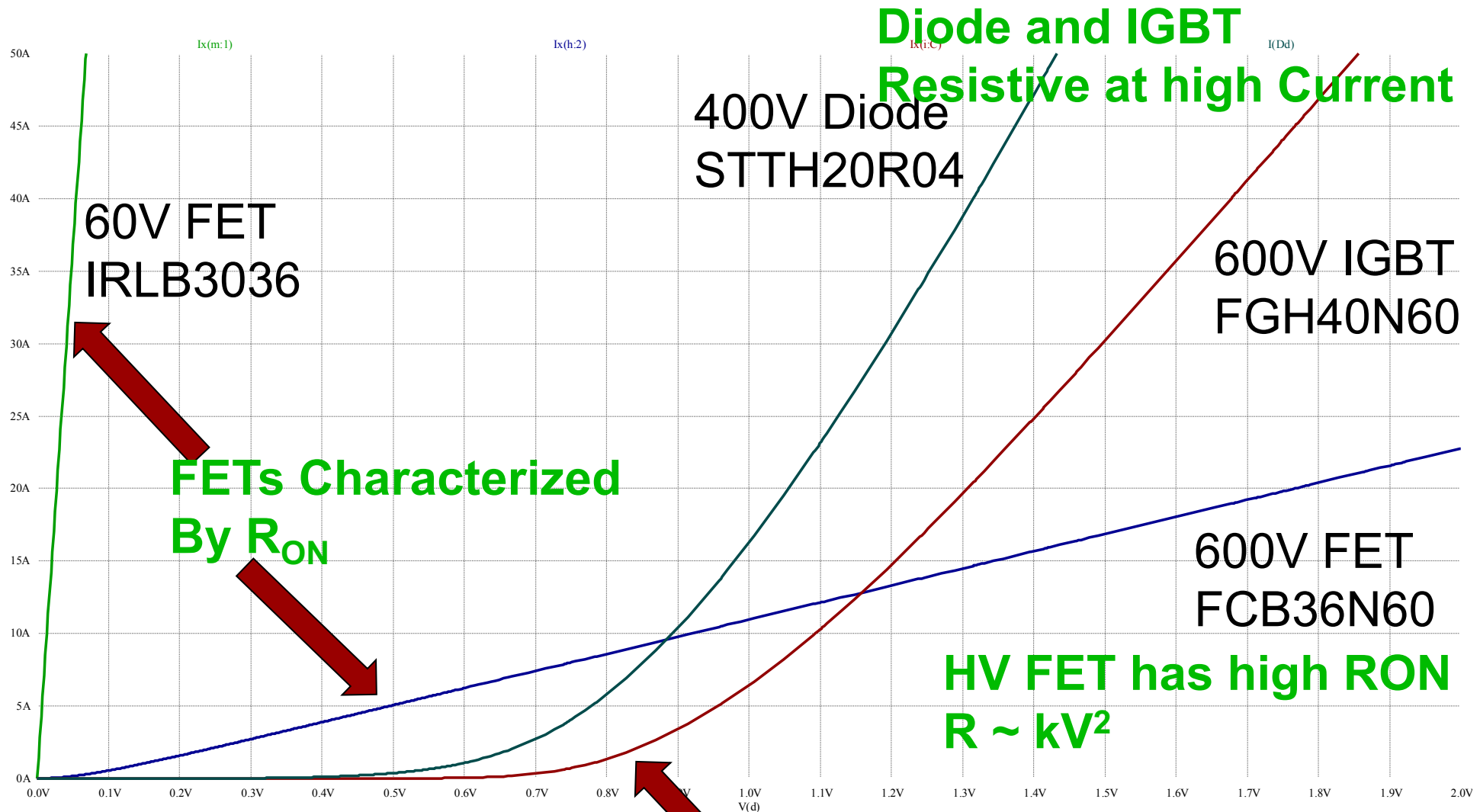

Diode and IGBT

Resistive at high Current

400V Diode
STTH20R04

600V IGBT
FGH40N60

60V FET
IRLB3036


FETs Characterized
By R_{ON}

600V FET
FCB36N60


HV FET has high R_{ON}
 $R \sim kV^2$

IGBT Like a Diode
Little Current Until $\sim 0.7V$


Transient Response of FET and IGBT

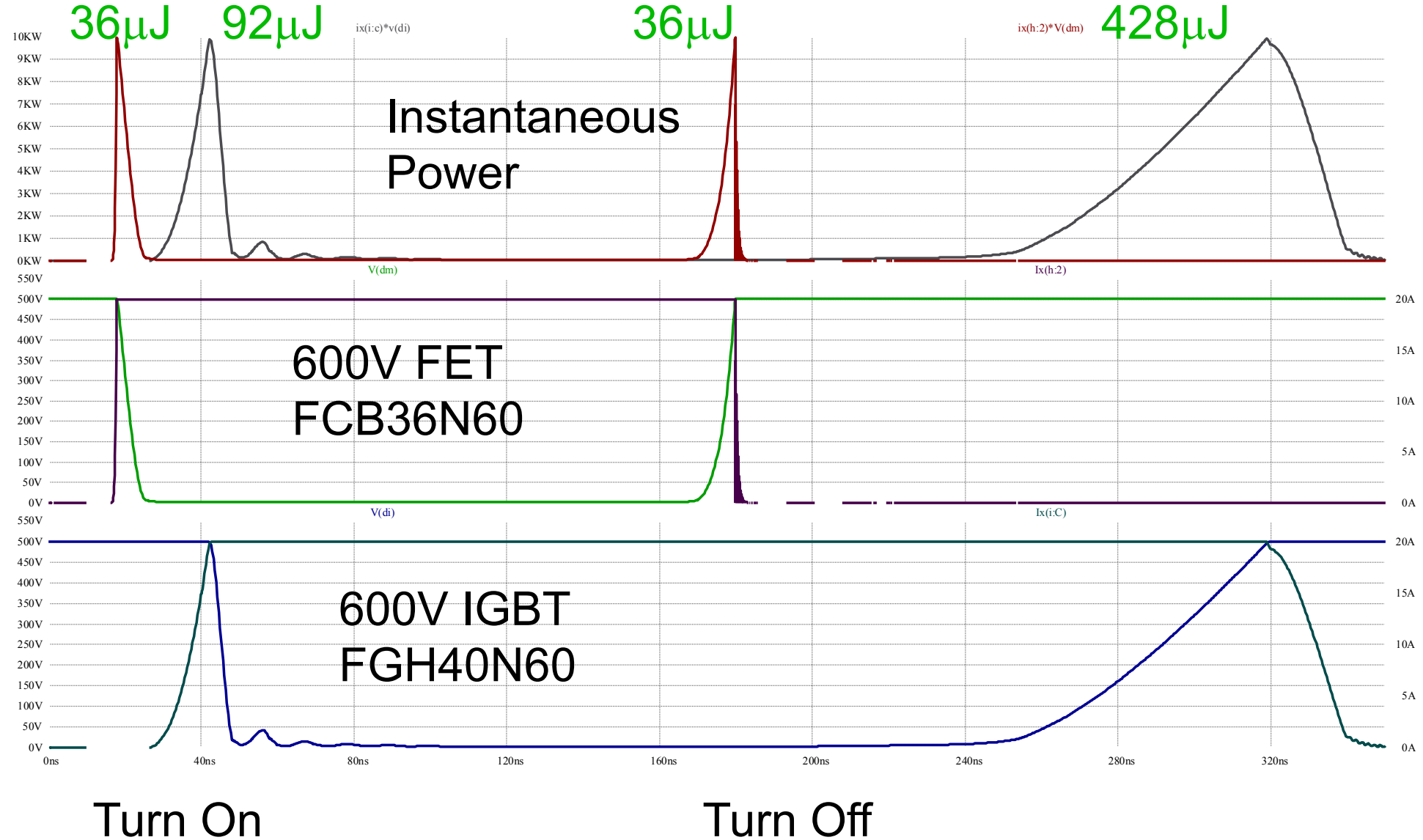


Boost Configuration for Transient Test

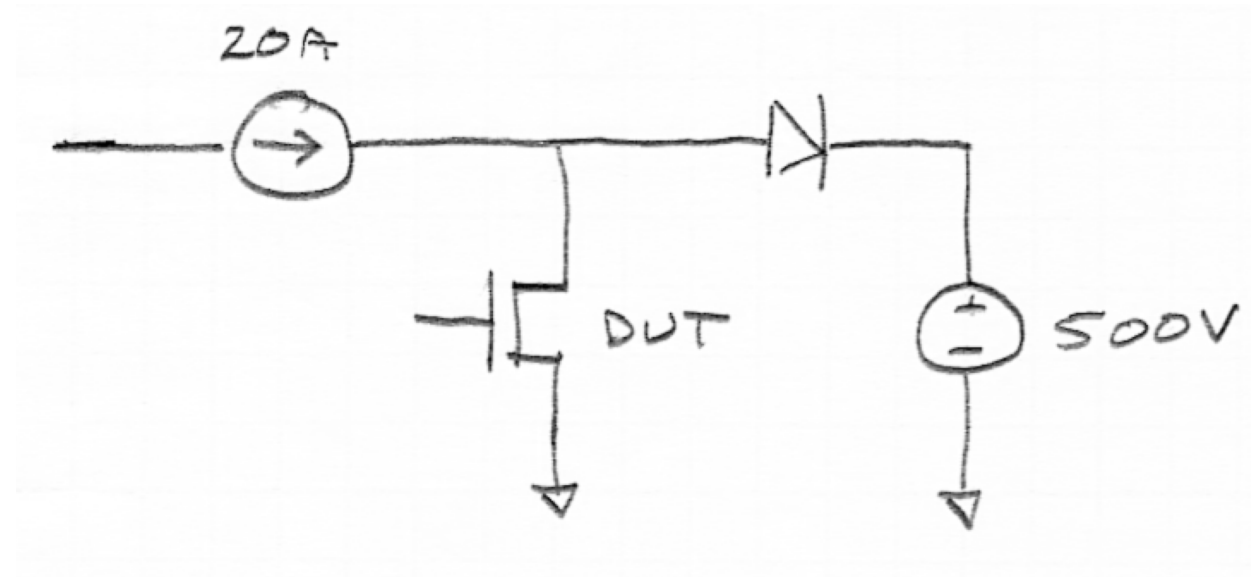

Diode Reverse Recovery



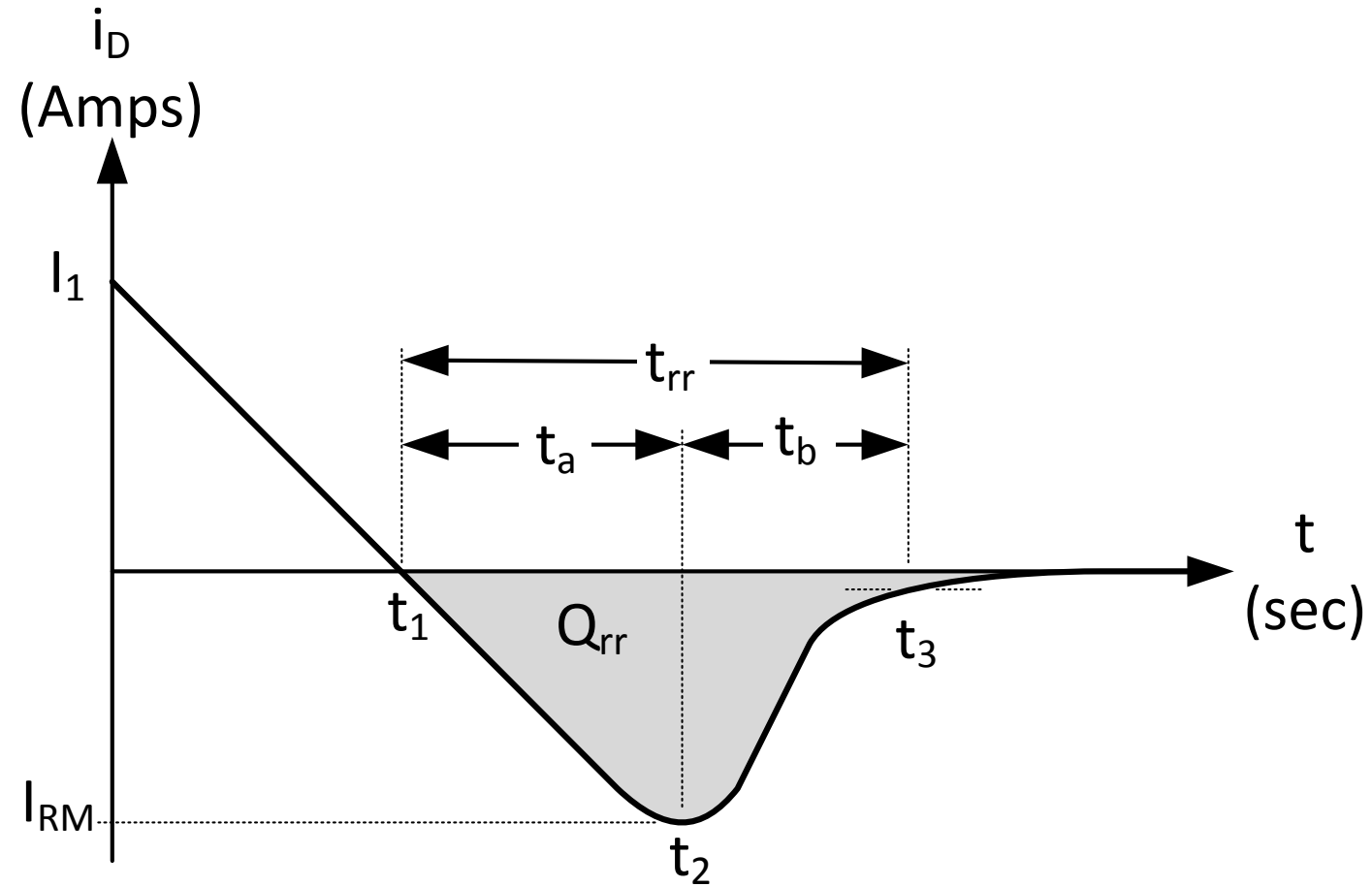


Diode Reverse Recovery

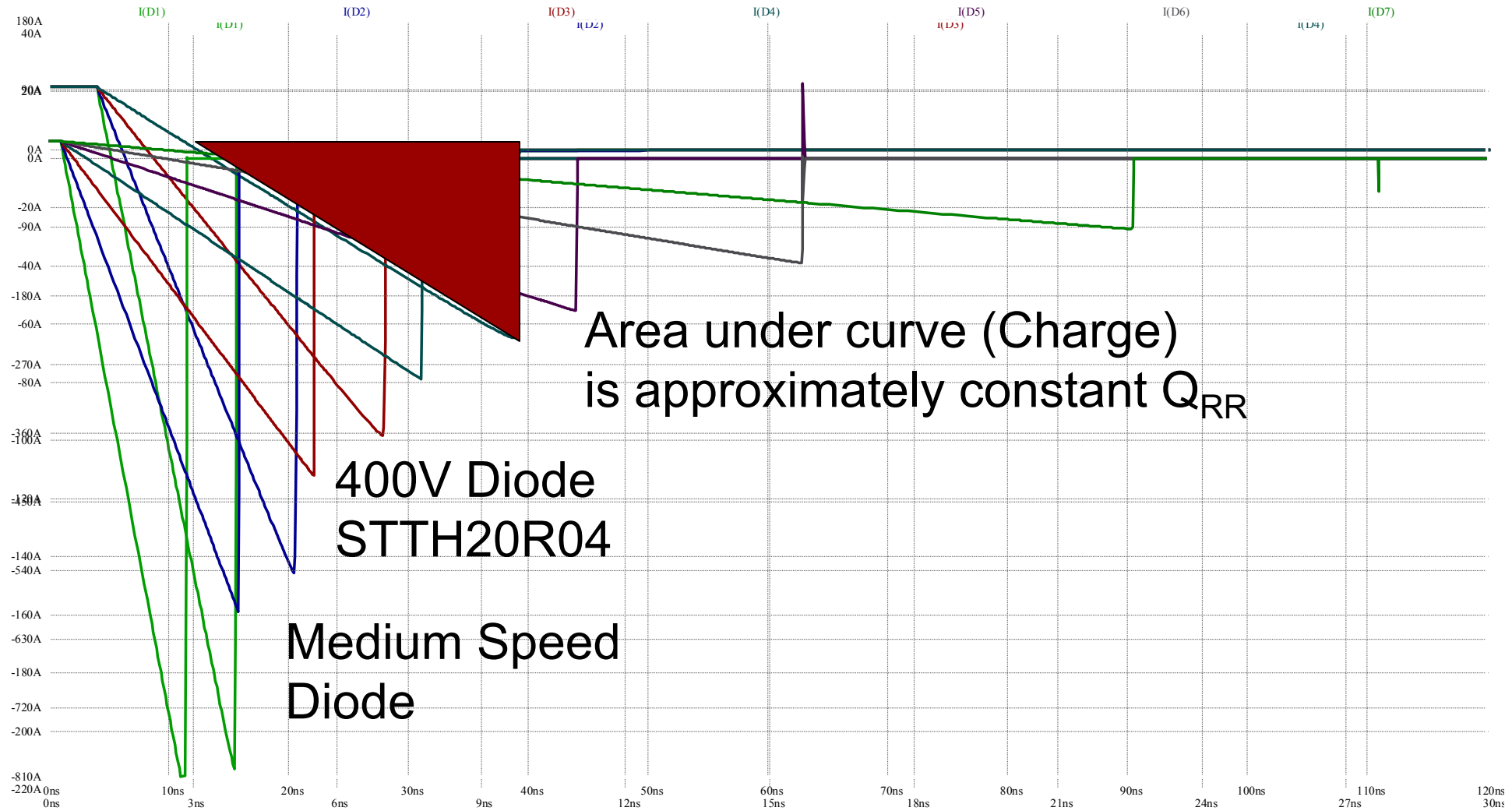

Power MOSFETs


Power MOSFETs are your friends

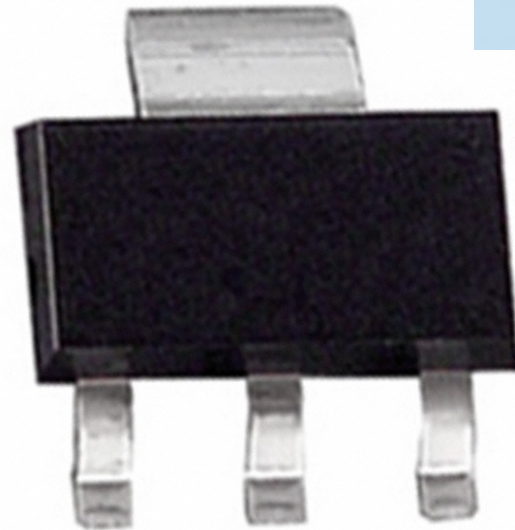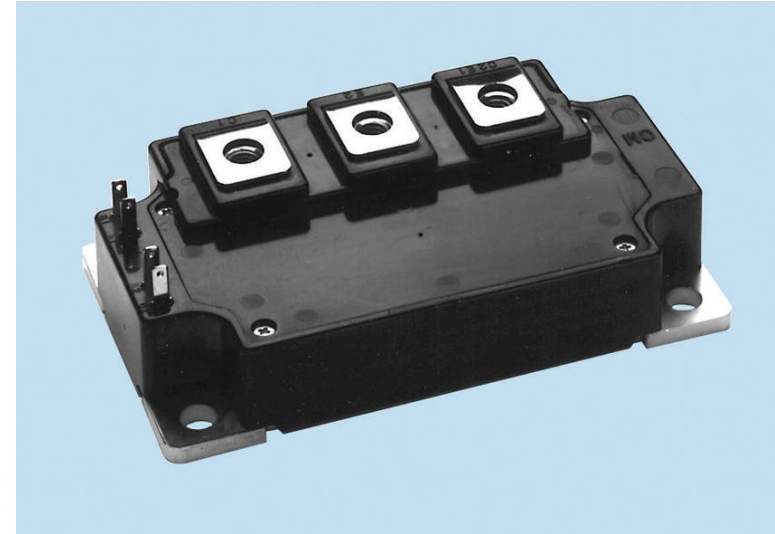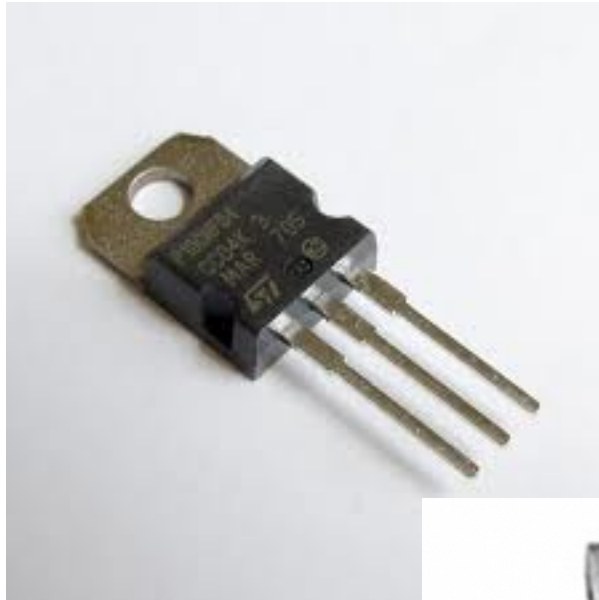




MOSFET Properties

- Fast switching time 10-50ns
 - Low switching losses
- Low conduction losses at low voltages
 - V^2/R of 1-2MW
 - e.g., at 20V $R = 0.4\text{m}\Omega$ (4mV drop at 10A)
 - Typically better than IGBT up to ~400V
- Easily paralleled for lower R_{on} , More I, or easier cooling
- Integral body diode in DMOS FET
- Avalanche breakdown can be used to “snub” overshoot


MOSFETs are Switches

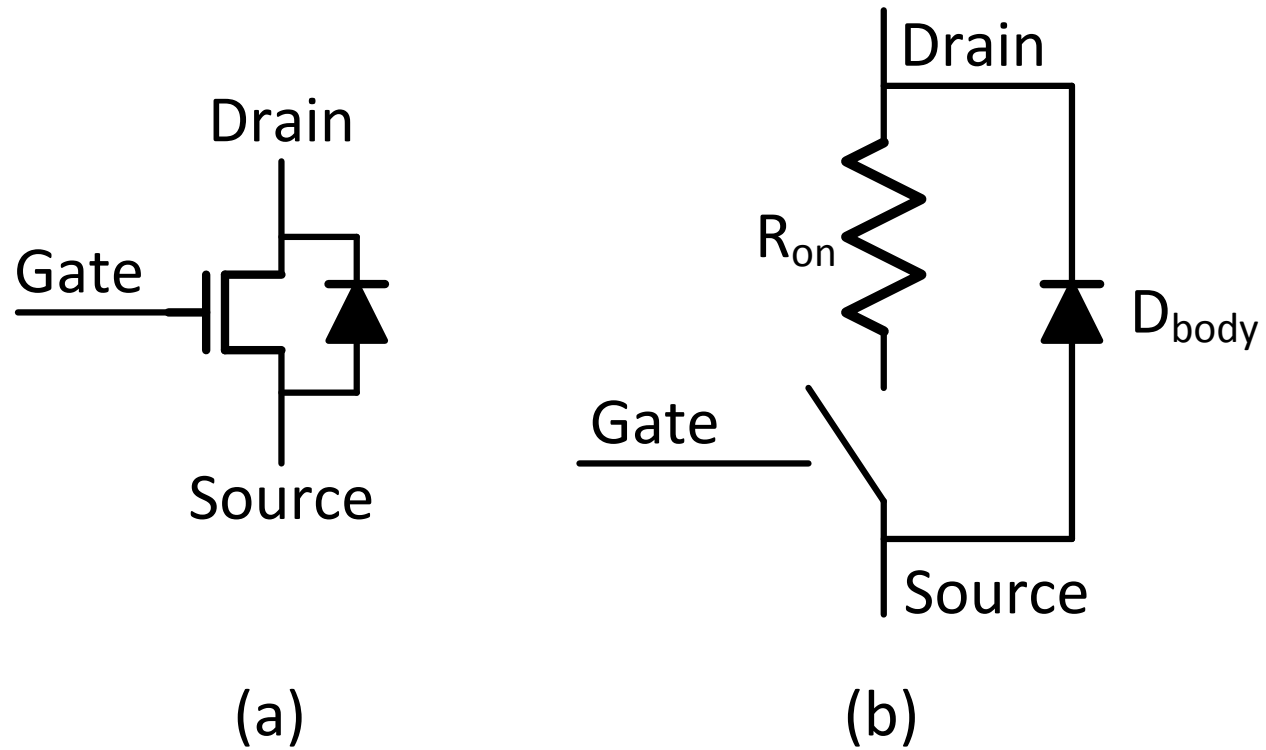


How do they Work

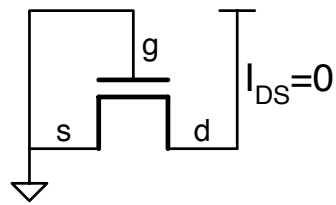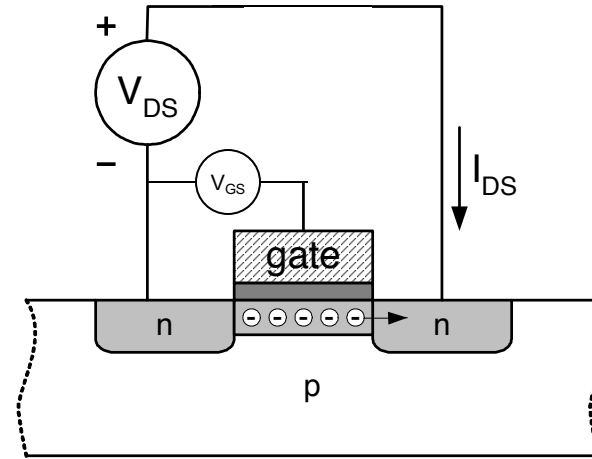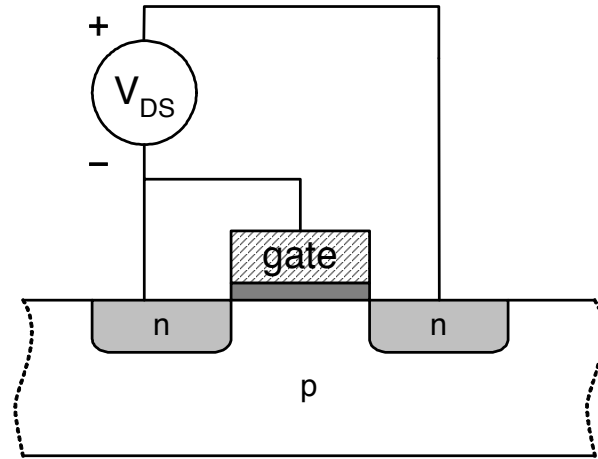

$|g=0$

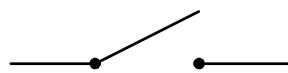

(a)

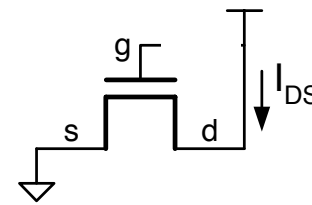


$|g=1$




(b)


Power MOSFET (DMOS) Structure

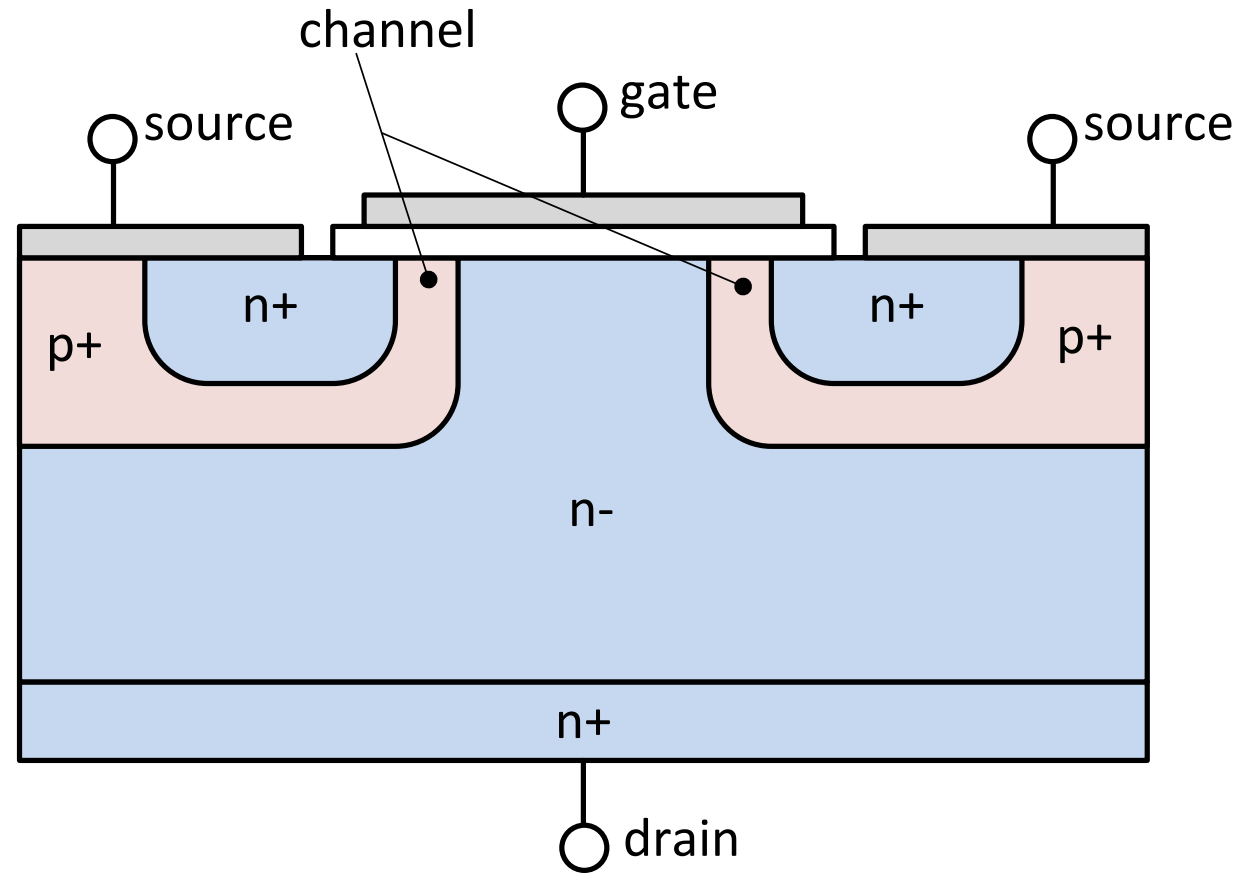

Gate Charge vs V_{GS}

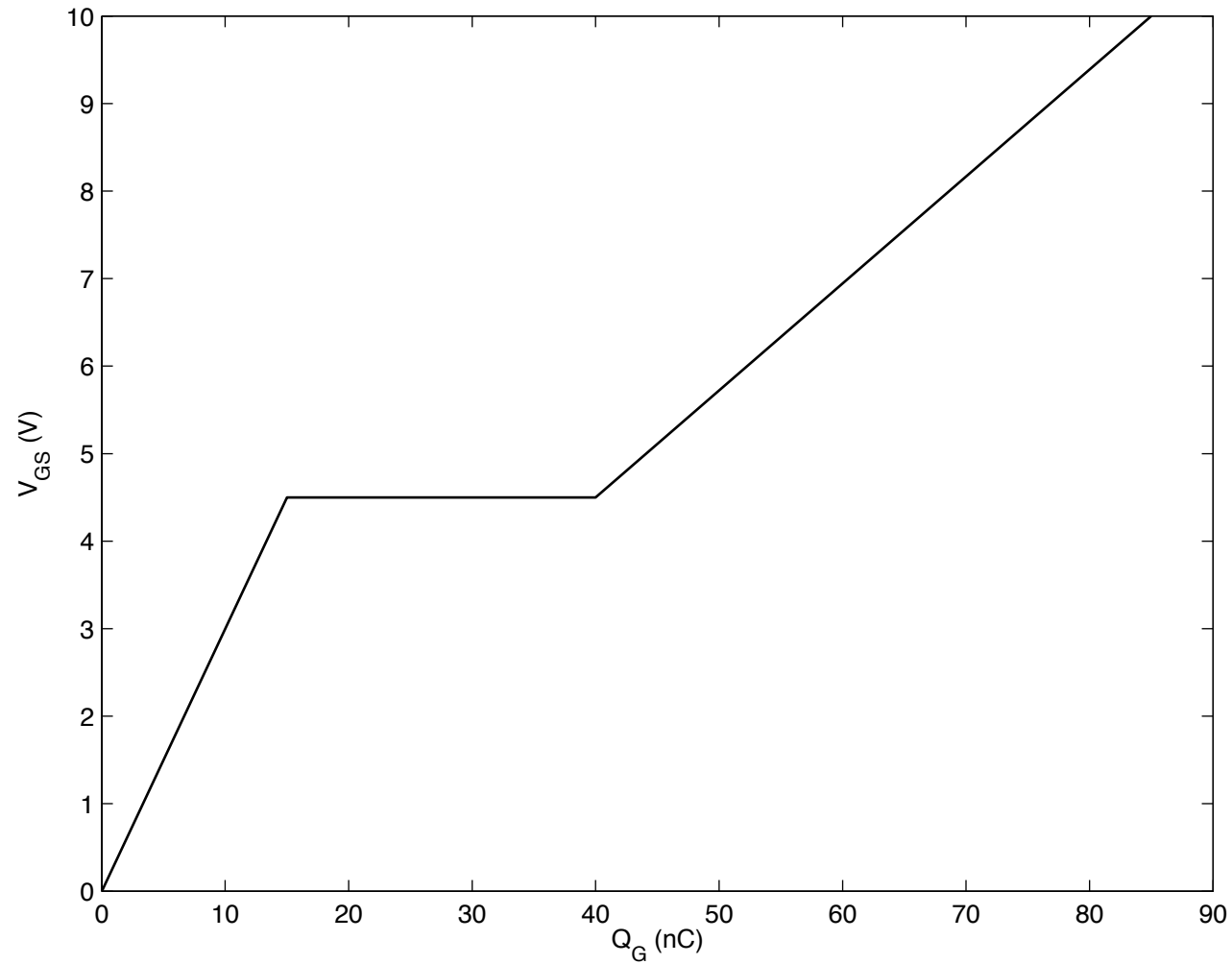


Parasitics

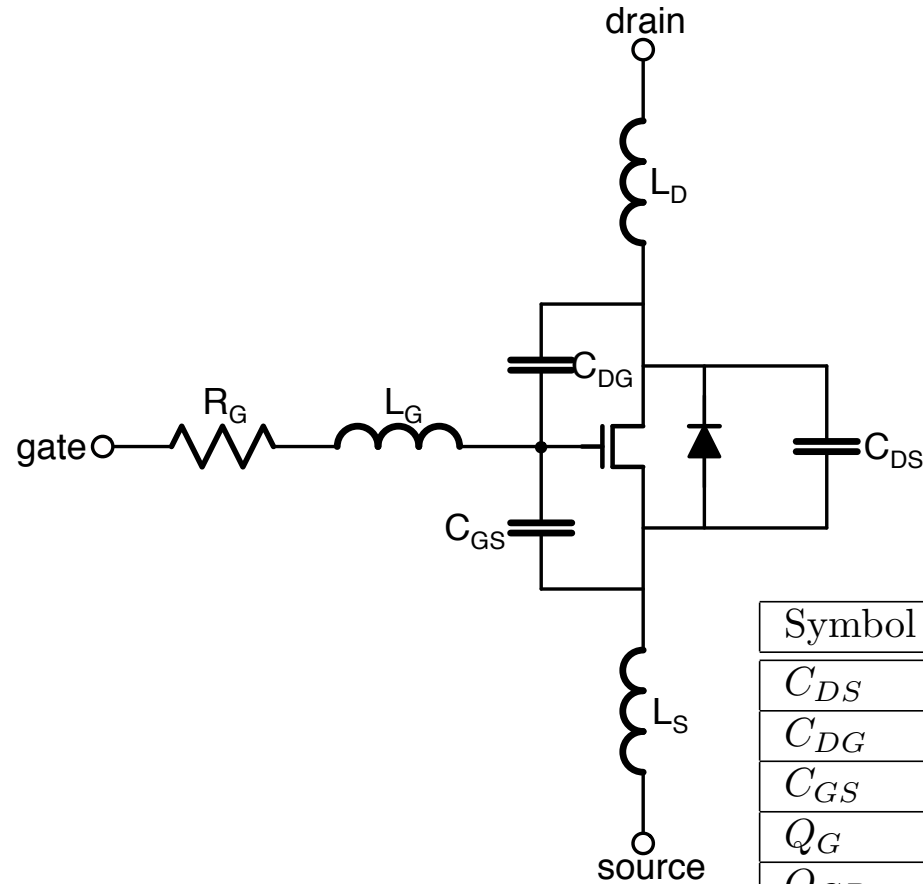

600V 0.1Ω FET
TO220 Package

Symbol	Value	Units	Description
C_{DS}	200	pF	Drain-source capacitance
C_{DG}	70	pF	Drain-gate (Miller) capacitance
C_{GS}	3600	pF	Gate-source capacitance
Q_G	86	nC	Total gate turn-on charge
Q_{GD}	35	nC	Gate-drain turn-on charge
L_S	7	nH	Source inductance
L_D	3	nH	Drain inductance
L_G	7	nH	Gate inductance
R_G	1.5	Ω	Gate resistance

Parasitics

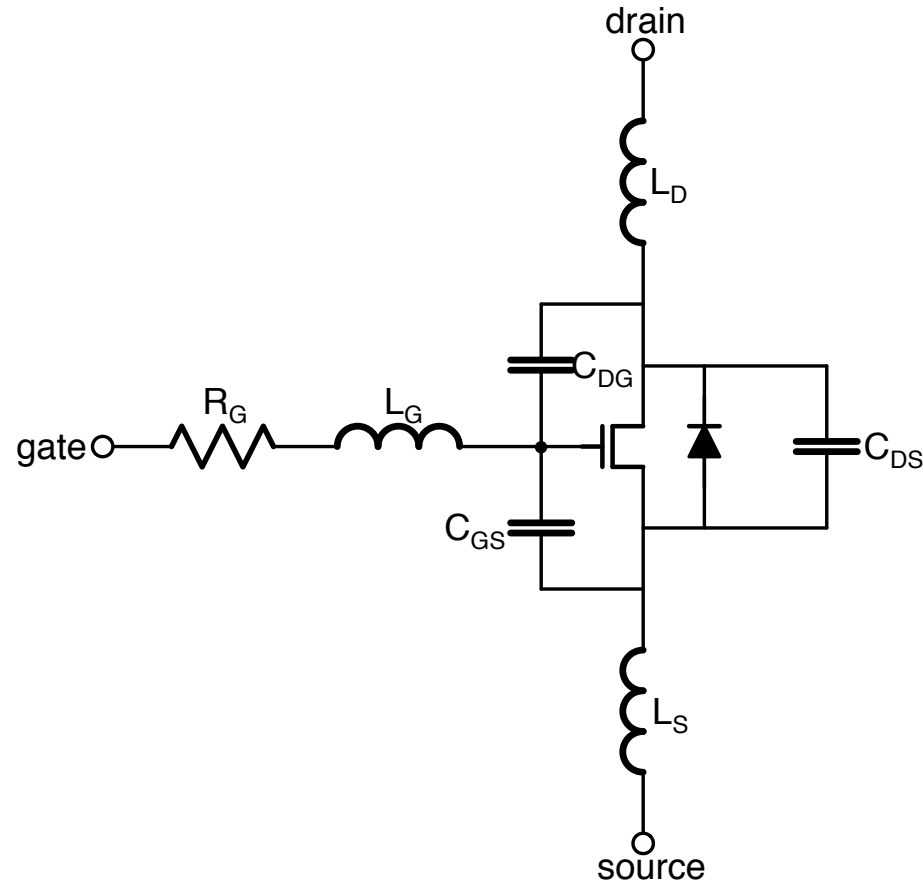

C_{DS} – CV^2 energy

L_D, L_S – I^2L energy


slows switching,
overshoot,

corrupts gate drive

C_{DG} – slows turn on

R_G, L_G – slow device turn-on


Tek

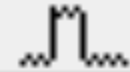

● Acq Complete

M Pos: 91.11µs

MEASURE

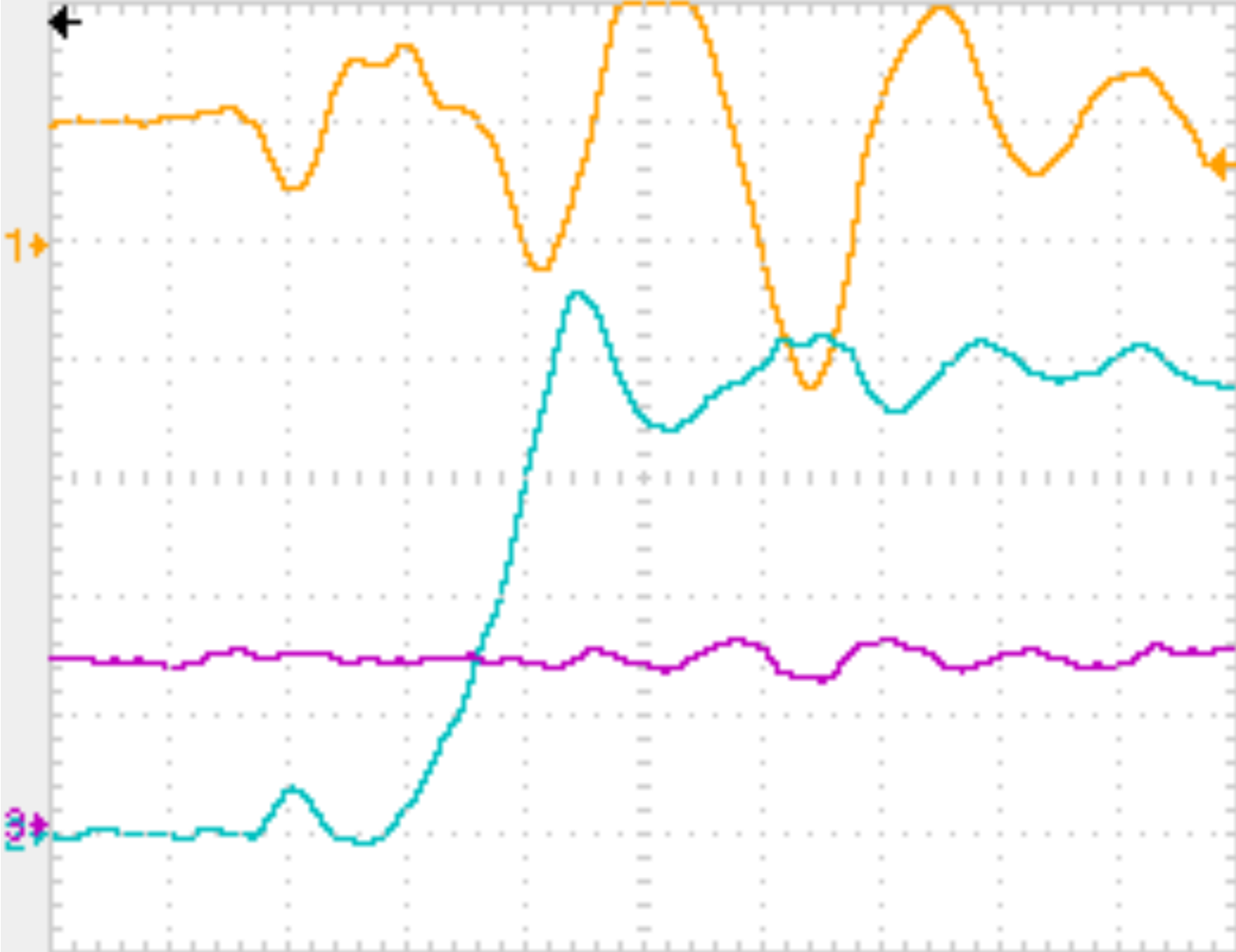

CH2
Rise Time
5.220ns

CH2
Fall Time
?

CH2
Pk-Pk
464V

CH3
Mean
280V

CH2
Pos Width
?

CH1 5.00V

CH2 100V

M 5.00ns

CH1 3.40V

CH3 200V

12-Nov-14 00:50

<10Hz

Typical MOSFETs

Device	20V				GaN	SiC	Units
		IRLB3036	IRFB4227	FCB36N60N	EPC2010	C2M0025120	
V_{DSmax}	20	60	200	600	200	1200	V
R_{on}		1.9	20	81	18	25	m Ω
Q_G		91	70	86	5	161	nC
C_{oss}		1020	460	80	270	220	pF
I_{Dmax}		195	65	36	12	90	A
I_{DM}		1100	260	108	60	250	A
E_{AS}		290	140	1800			mJ
P_{max}		380	330	312		463	W
V^2/R		1.9	2.0	4.4	2.2	58	MW
V^2/RQ_G		21	29	52	440	360	mV/s

Power MOSFETs should be ON or OFF

They are not happy in between

- IRLB3036
- Can handle 60V (when its off)
- Can handle 195A (when its on – if you can cool it)
 - $I^2R = (195)^2(0.002) = 76W$
- But it can't handle 60V and 195A at the same time
 - $P = VI = (60)(195) = 11.7kW$
 - At least not for very long
- Turn them on and off quickly
- Best circuits are “soft switching”
 - Zero-current switching (ZCS) or zero-voltage switching(ZVS) or both.

Power Diodes


Diode Properties

- Self-controlling switch
 - Allows current in one direction
 - Turns off when current reaches zero (in theory)
- Relatively fixed voltage drop independent of current
 - 0.5 to 2.0V
 - High losses at low voltages
- Care required to operate in parallel
 - Current hogging
- Turn-off delay
 - Must clear space charge out of junction
- Turn-on delay
 - Negligible for most fast diodes, but some are problematic


Key Parameters

- Reverse breakdown voltage
- Maximum current
- Reverse recovery time
- Junction capacitance


Diode Reverse Recovery

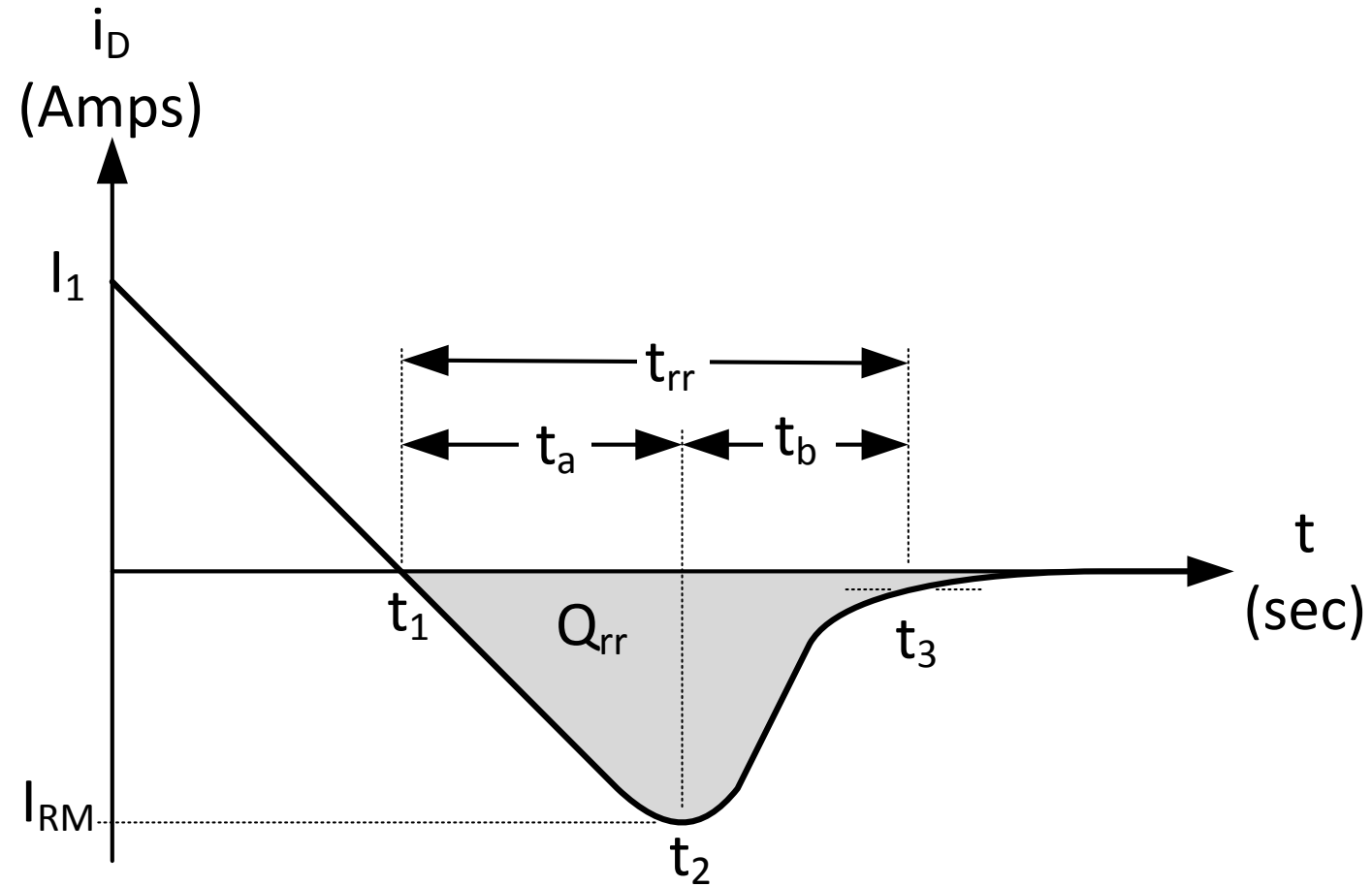


Diode Forward Recovery

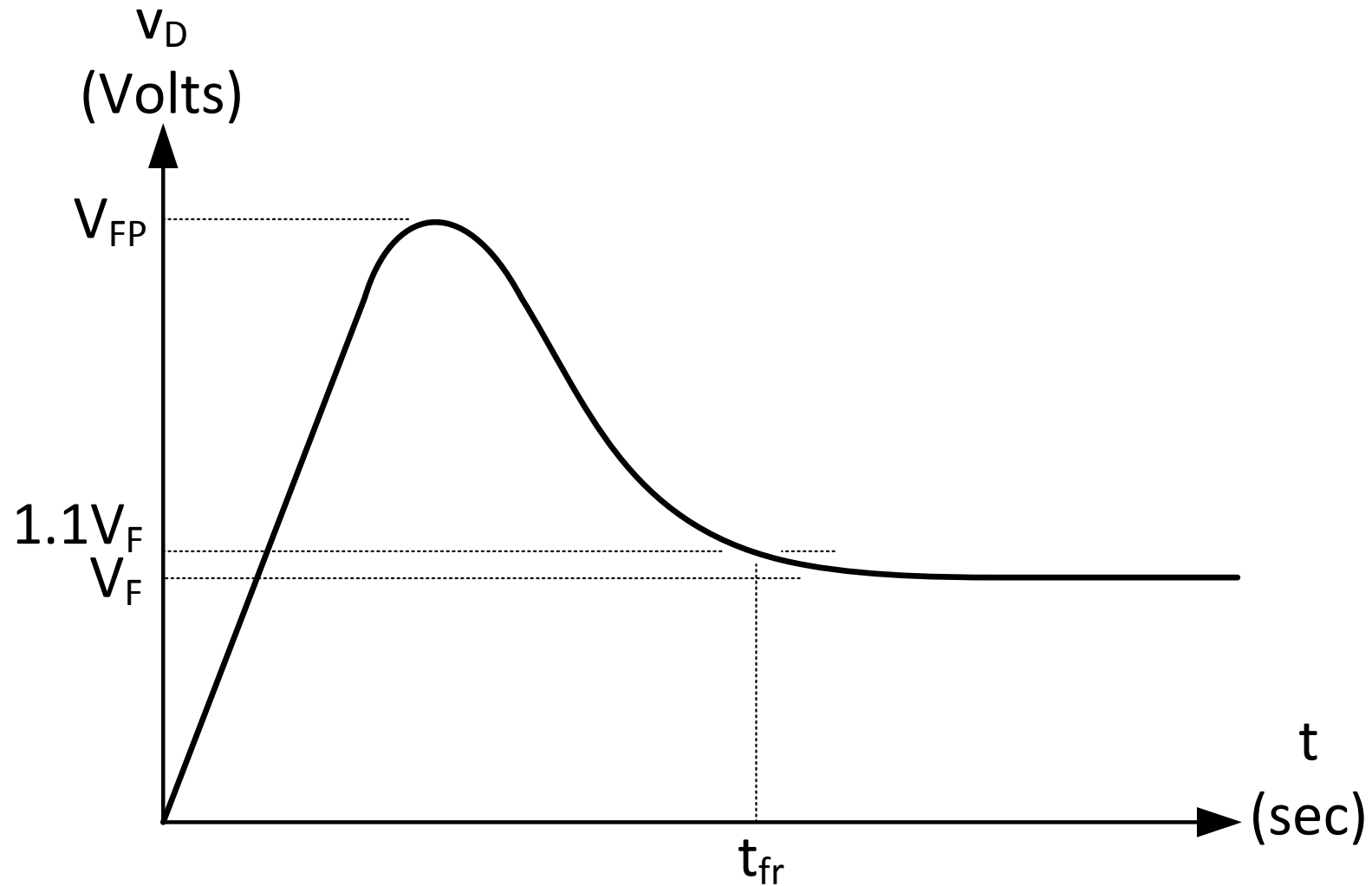

Diode Forward Recovery

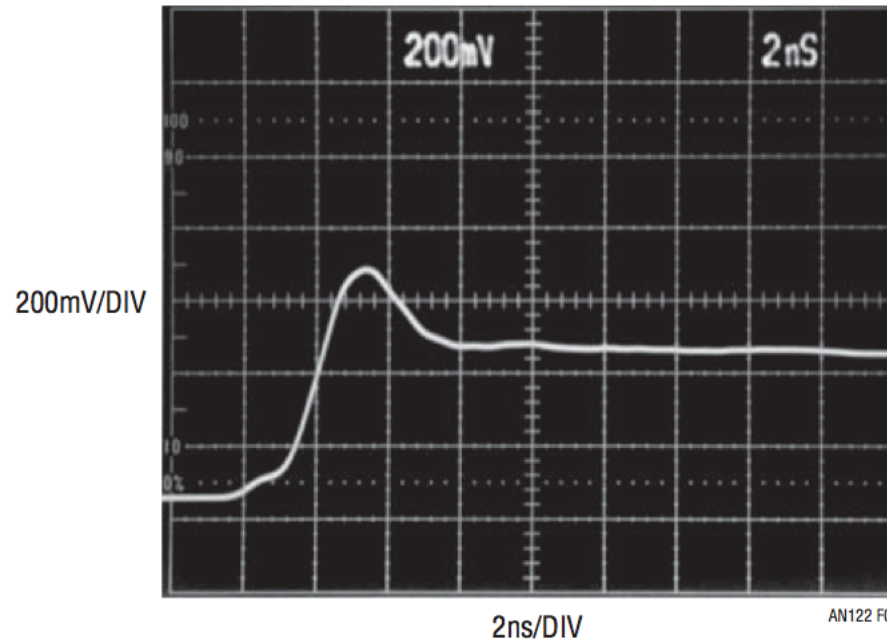


Good Diode

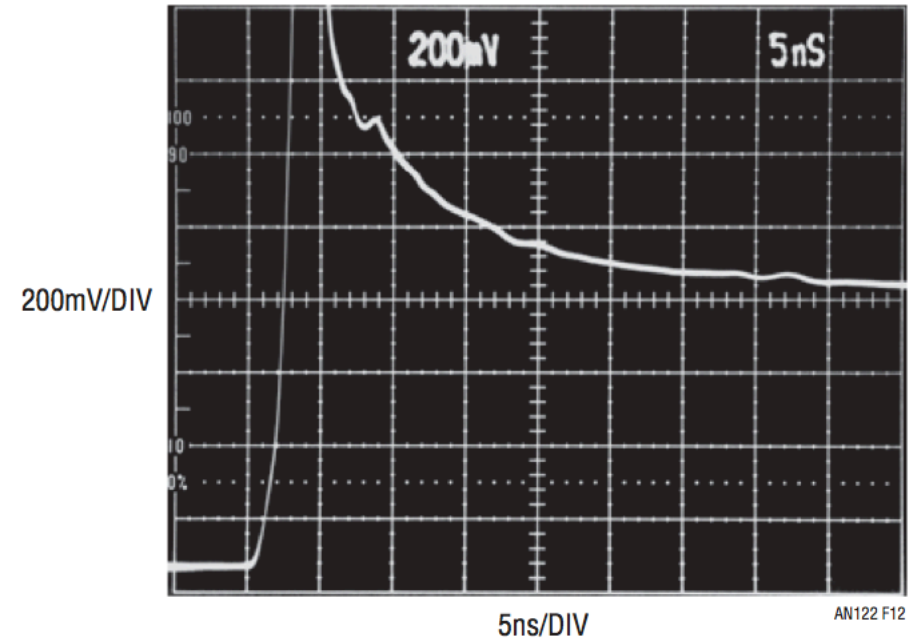




Bad Diode

Two 2A Diodes < One 4A Diode

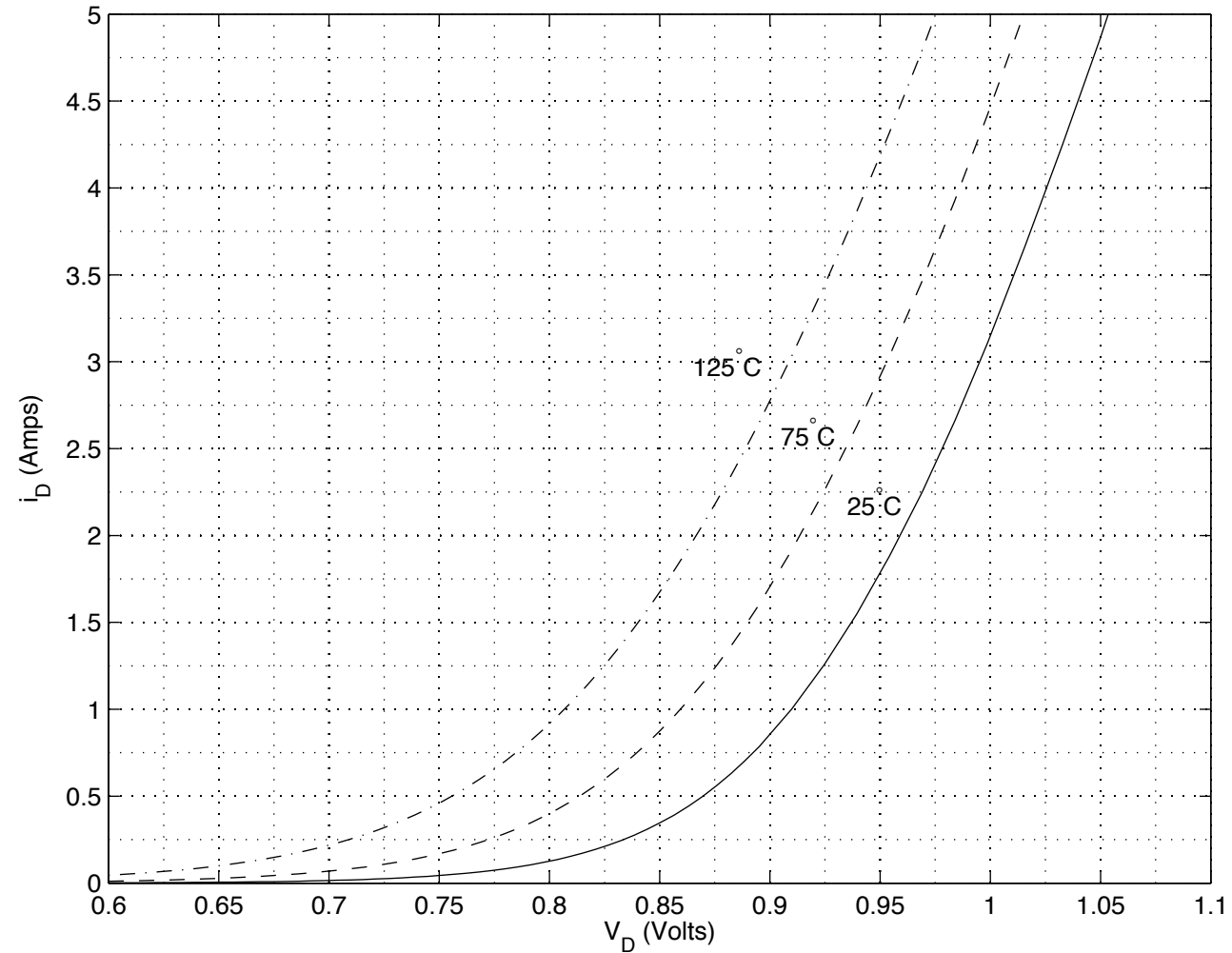


Summary – Power Devices

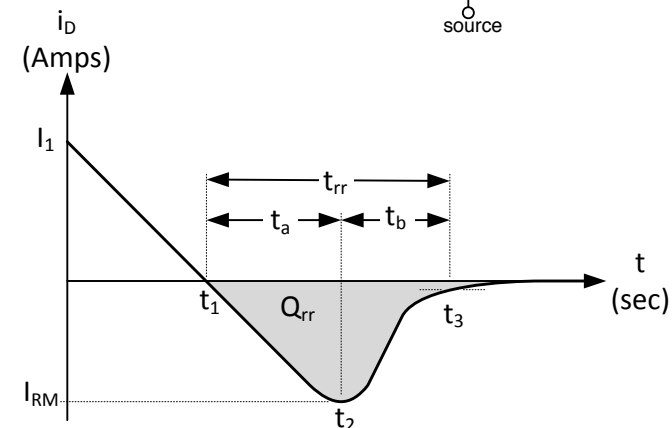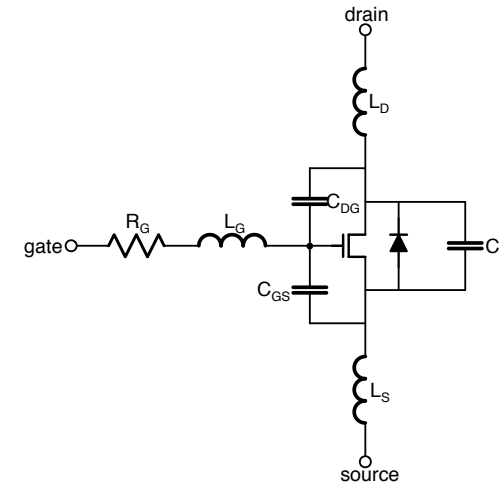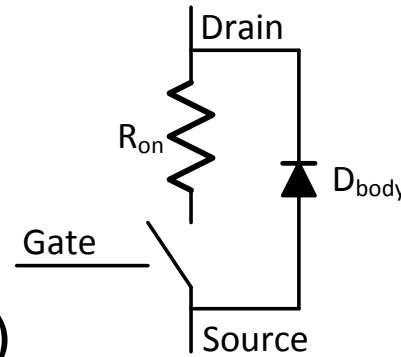- Finite, non-zero
 - Switching time
 - Blocking voltage
 - On-voltage (resistance)
- Parasitics – L and C
- MOSFETs – switches
 - Turn on/off as fast as gate can be charged
 - $R = kV^2$
- Diodes
 - Self-controlled switches
 - Reverse recovery loss Q_{RR}




Power Circuits


Practical Buck Converter

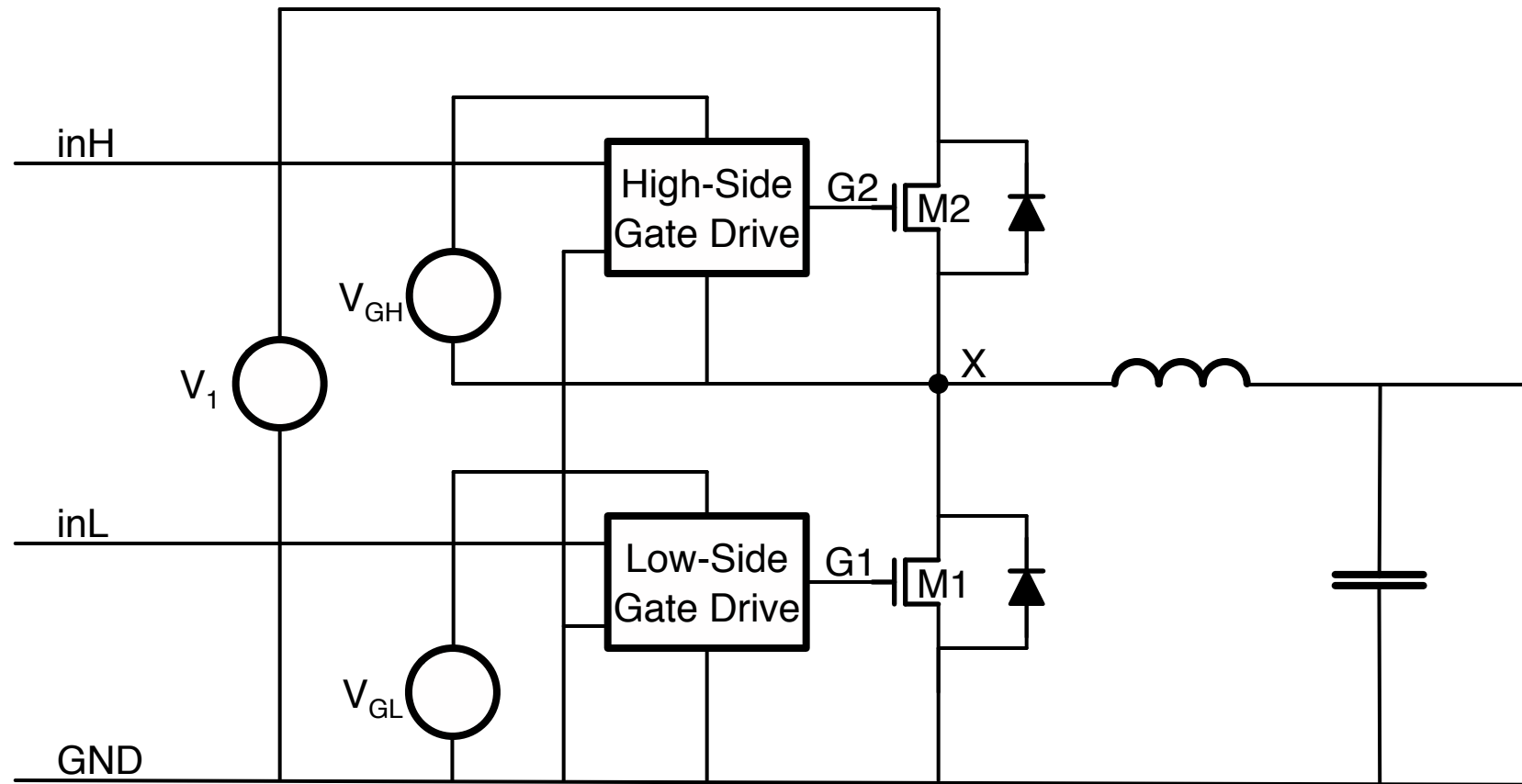

Simple Model

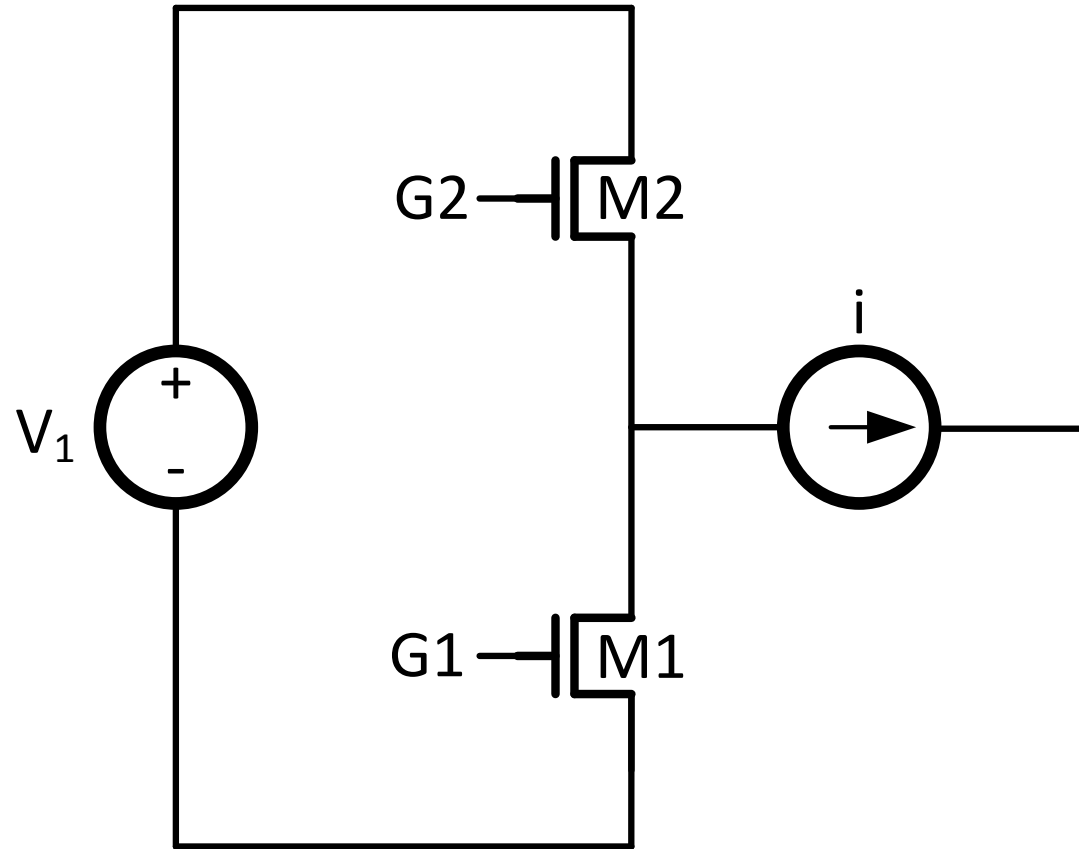

One Switch May be a Diode

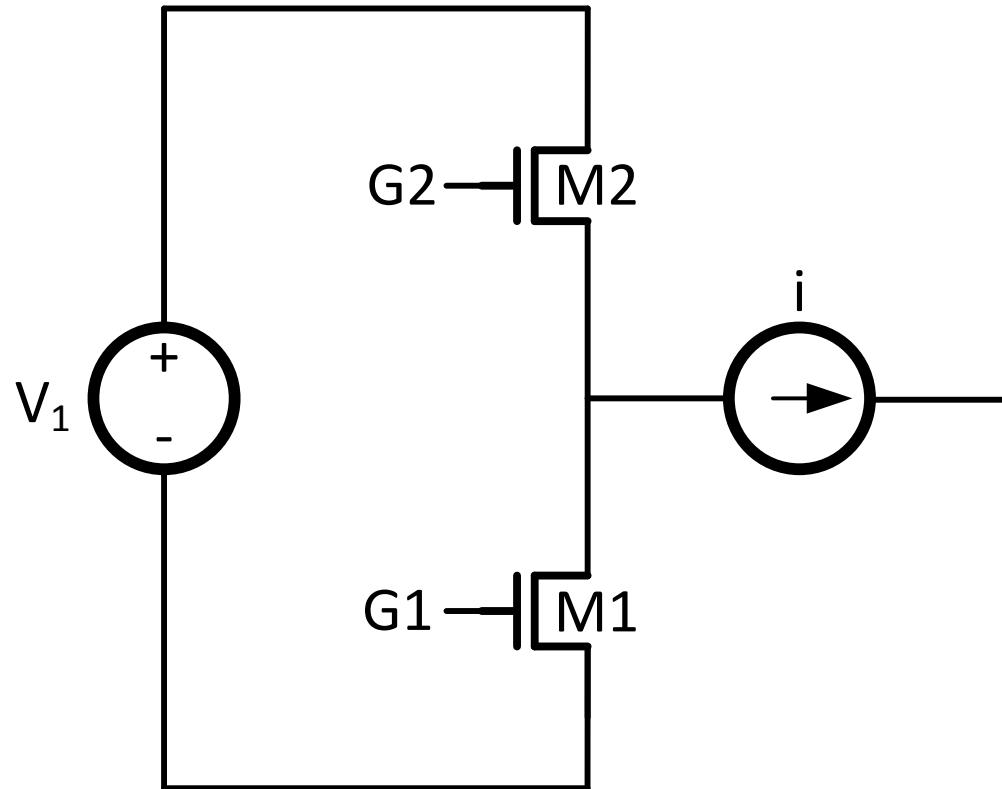


Lower switch for buck

Upper switch for boost


Other switch does most of the work

Synchronous rectification may be used to reduce loss

Turn-On Loss

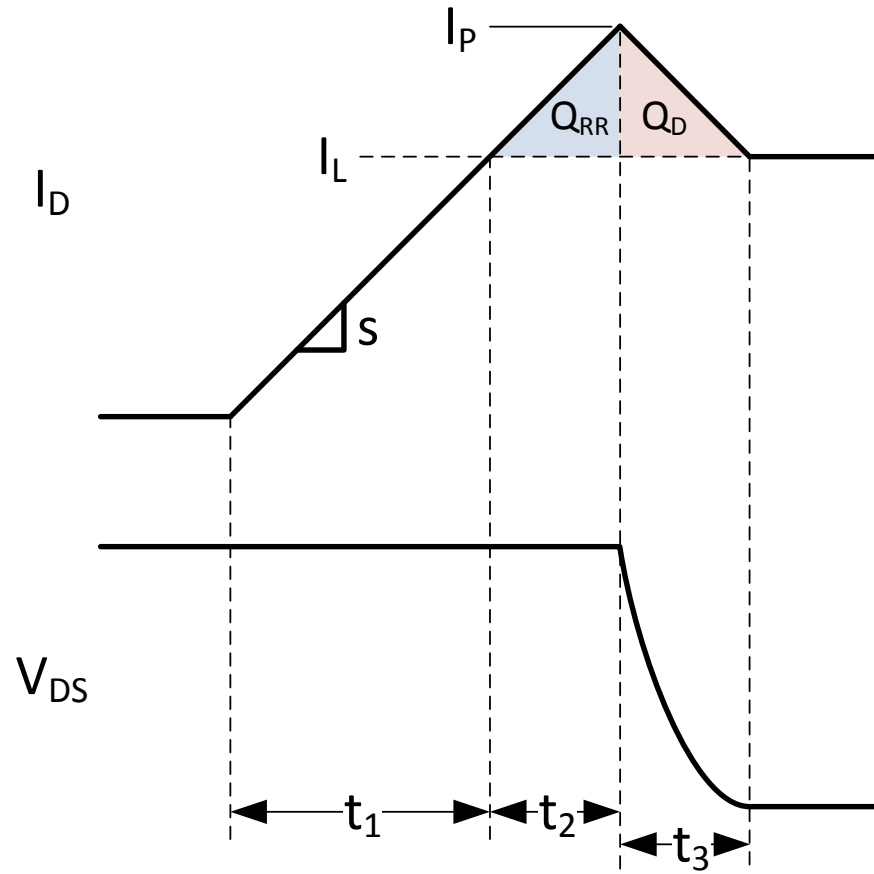

Turn-On Buck w/ Diode

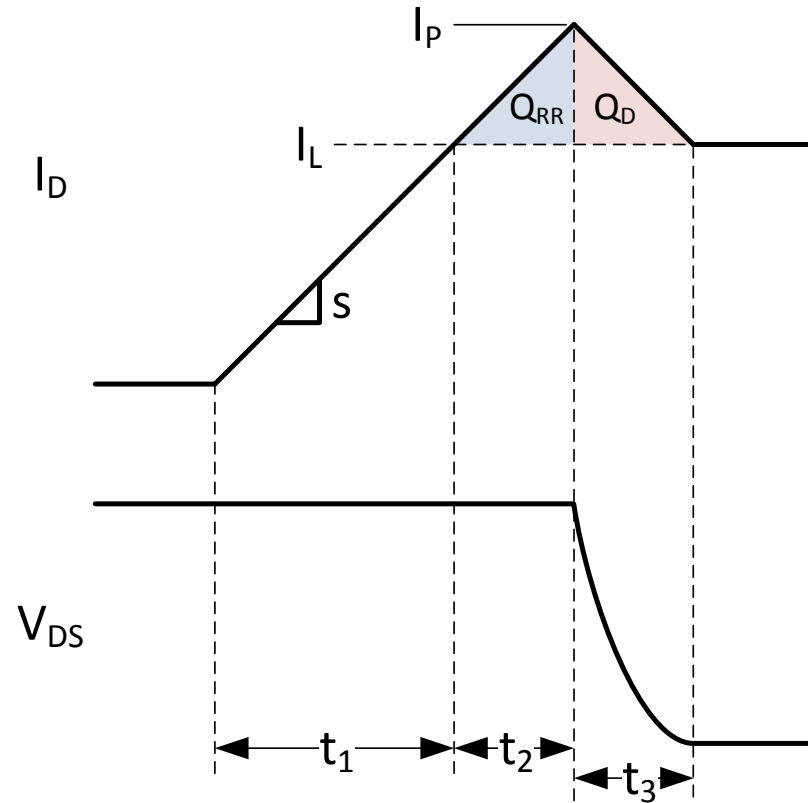


t_1 – ramp current to I_L

t_2 – diode reverse recovery

t_3 – discharge drain
capacitance

Current waveform in t_2 and
 t_3 may vary

Turn-On Buck w/ Diode

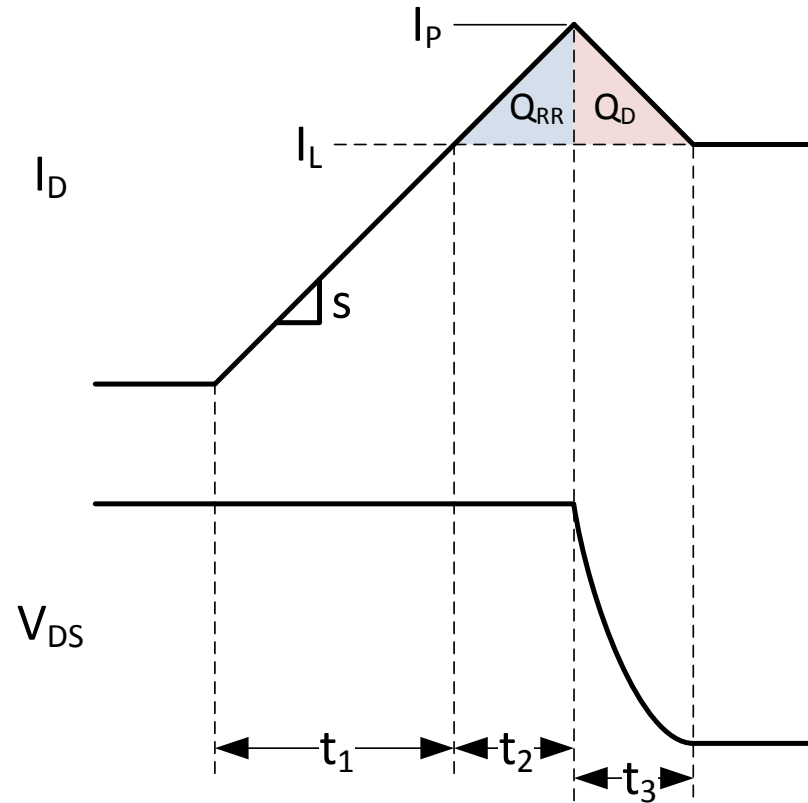

$$t_1 = \frac{I_L}{s}$$

$$E_1 = 0.5V_{DD}I_Lt_1 = \frac{0.5V_{DD}I_L^2}{s}$$

$$t_2 = \sqrt{\frac{2Q_{RR}}{s}}$$


$$E_2 = V_{DD}t_2(I_L + 0.5t_2s)$$

$$t_3 \approx \frac{2I_P}{Q_D} \quad \text{T3 is upside down}$$

$$Q_D \quad \text{T3} = 2Q_d/I_p$$

$$E_3 = 0.5V_{DD}Q_D + 0.33V_{DD}I_Lt_3$$

Turn-Off Buck with Diode

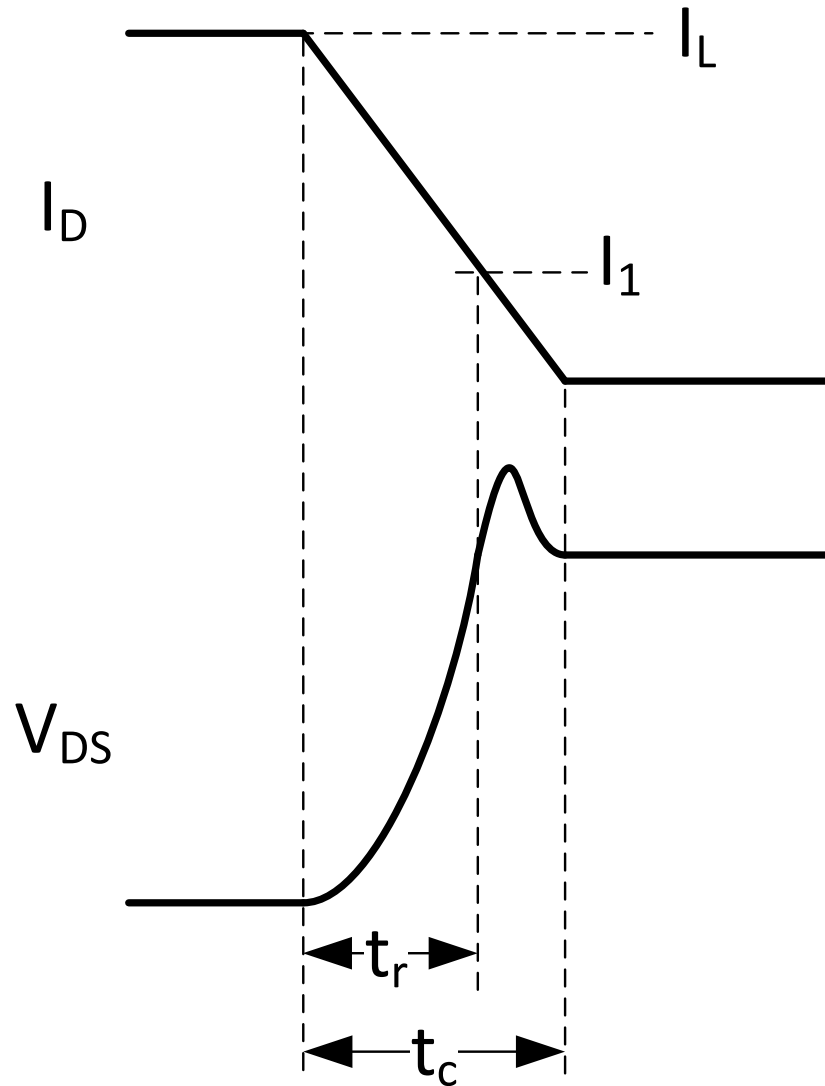


Excess current charges drain node.

Integrate to get switching energy

$$E = V_{DD} t_r \left(\frac{1}{6} I_L + \frac{1}{3} I_1 \right)$$


Turn-Off Buck with Diode

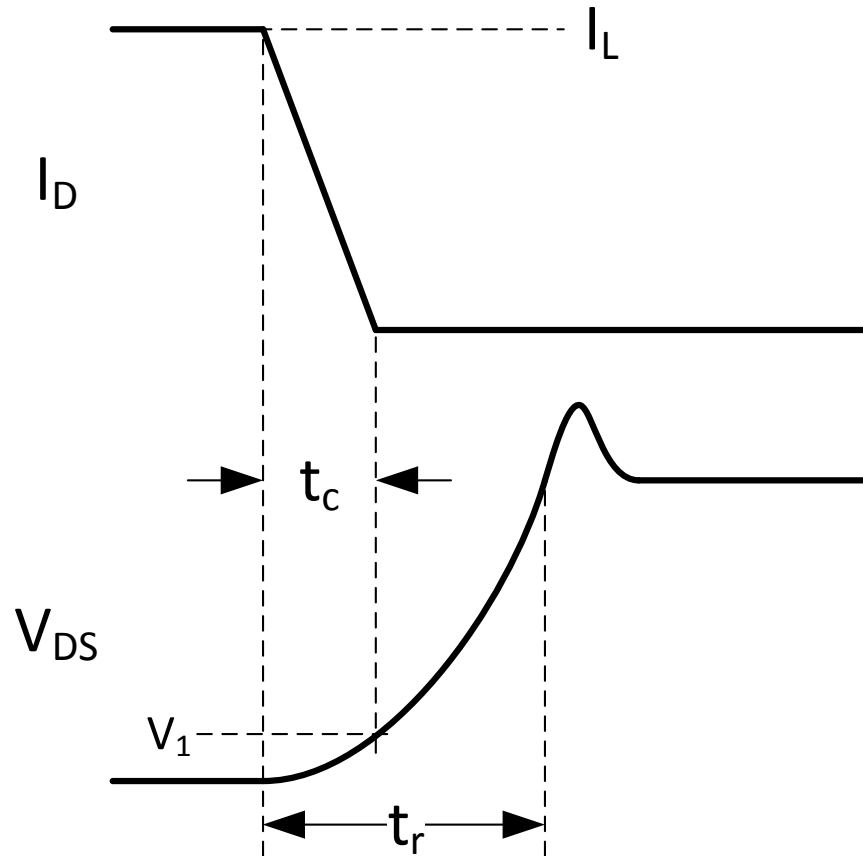

If current ramps faster than
voltage nearly ZVS

$$E = \frac{1}{6} V_1 I_L t_c$$

Parasitic Losses

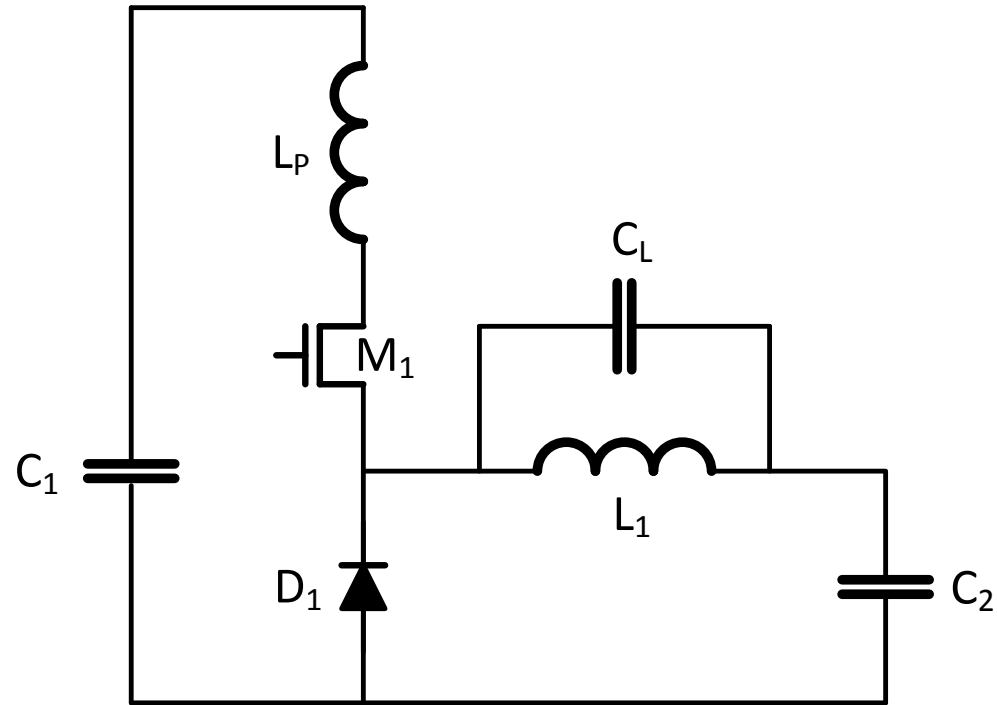


Switching Loss with SPICE


Simulation Setup

- Boost configuration 40A, 50V
- IRLB3036 – 60V, 2m Ω FET

Ideal Diode, No Parasitics

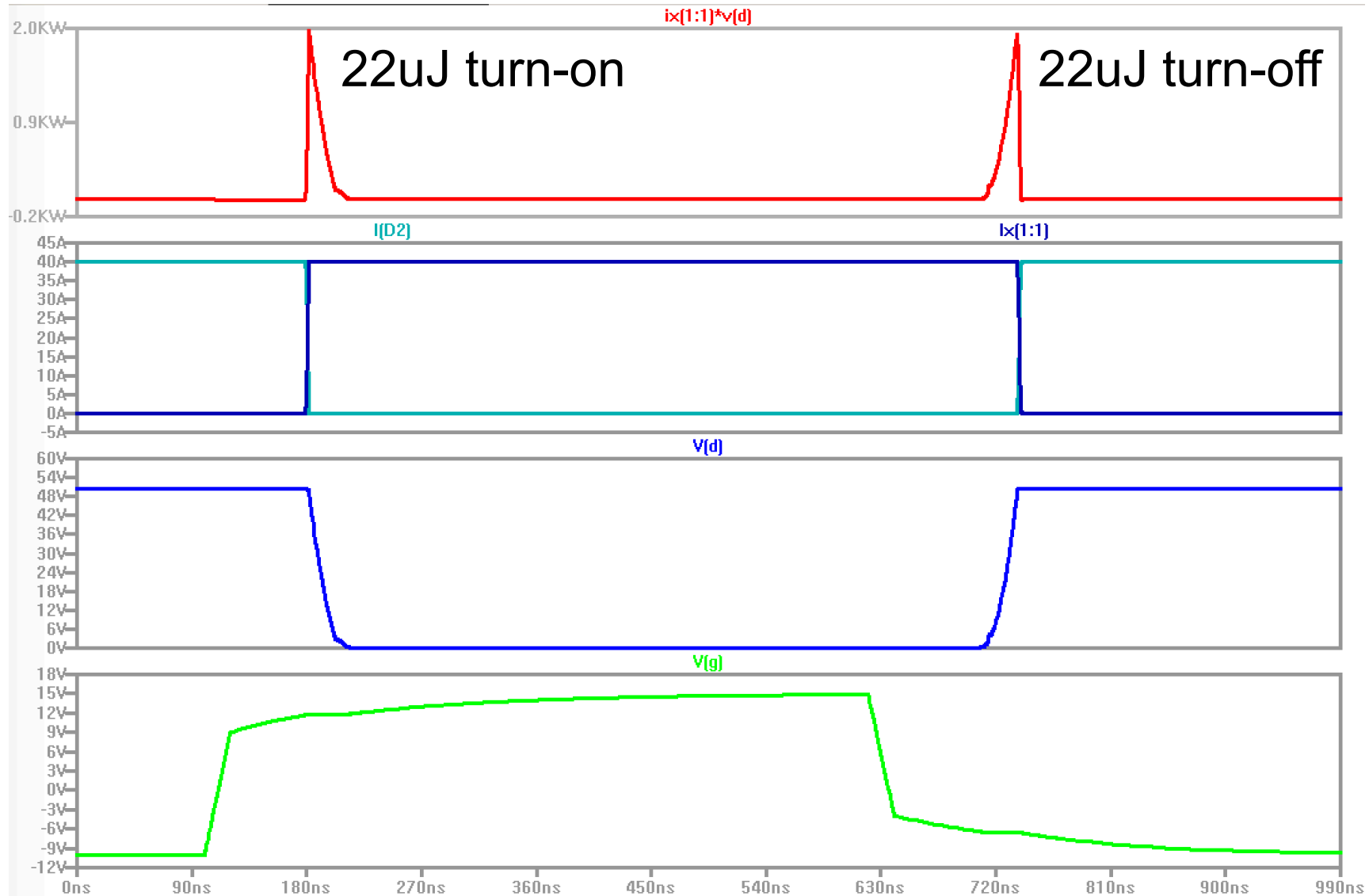


Body Diode of IRLB3036

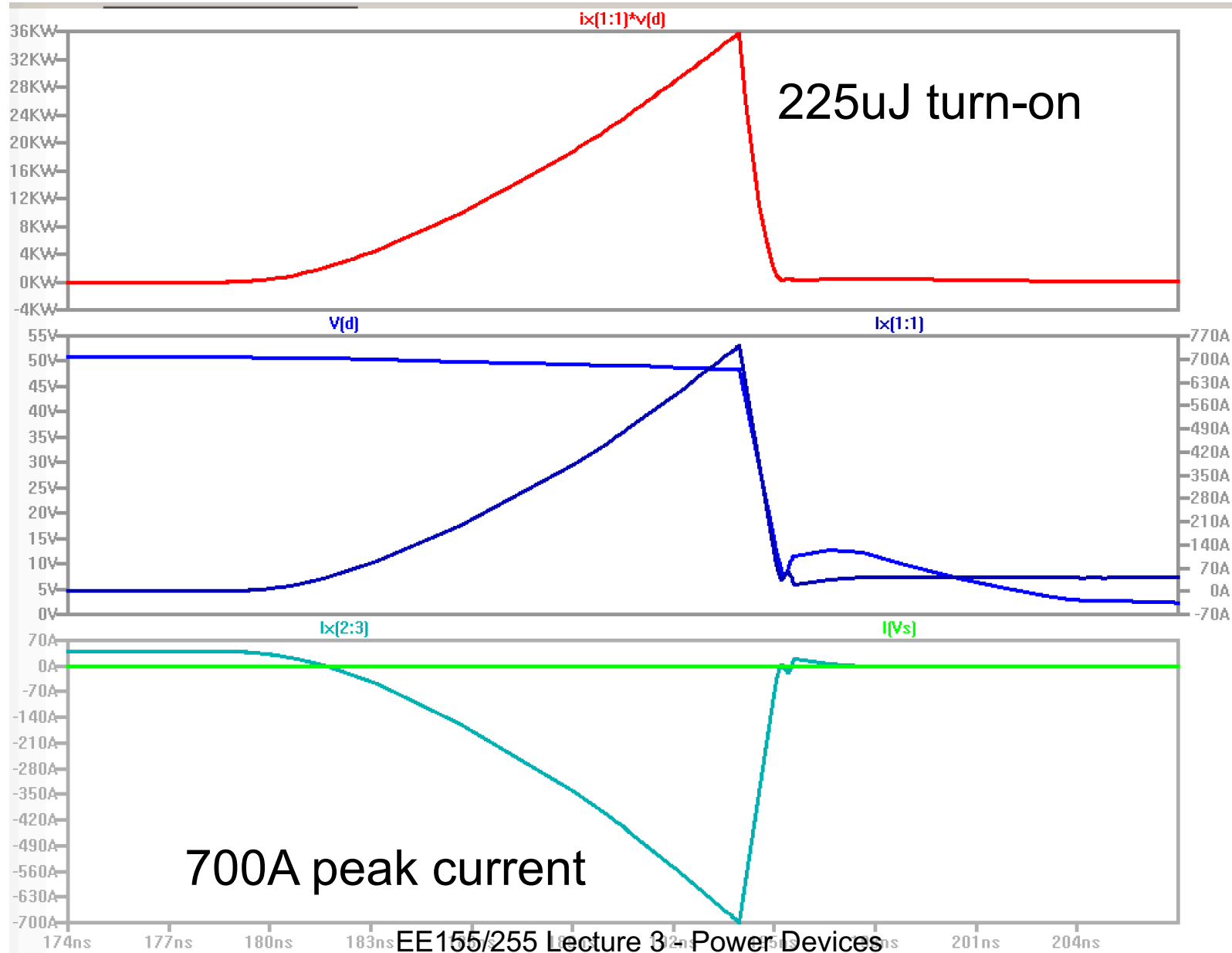


Gate Drive


Gate Driver

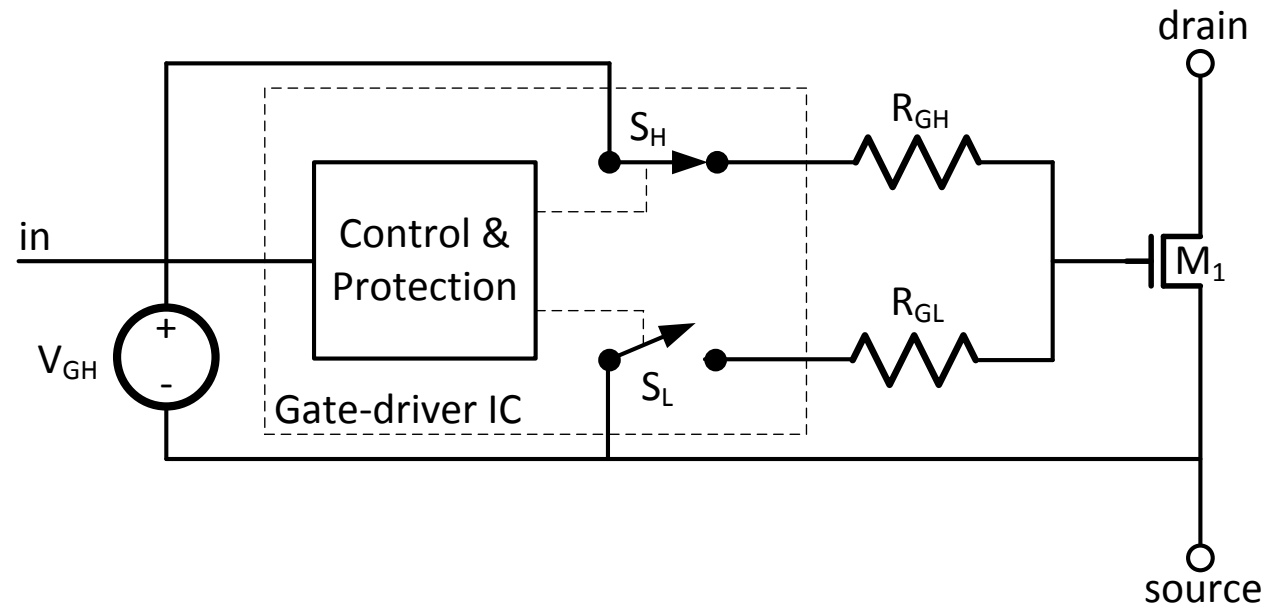

Effect of Miller Cap on Rise Time

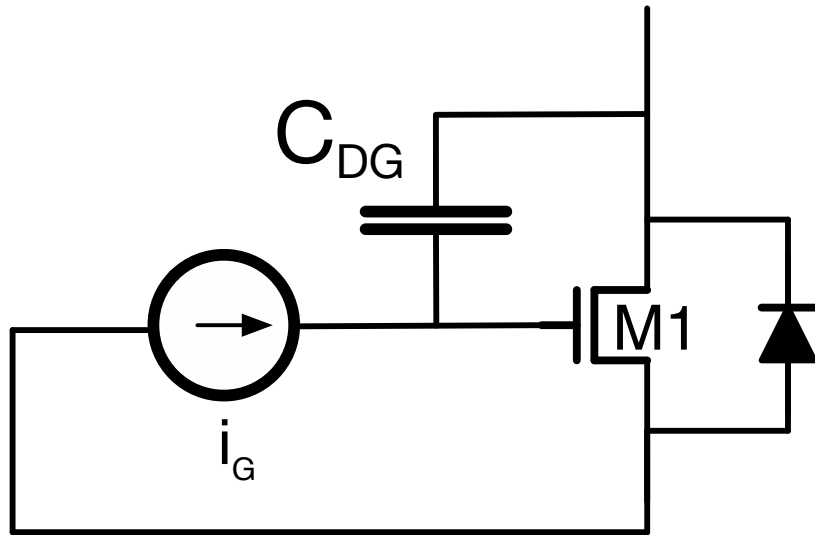

Effect of Miller Cap on Rise Time

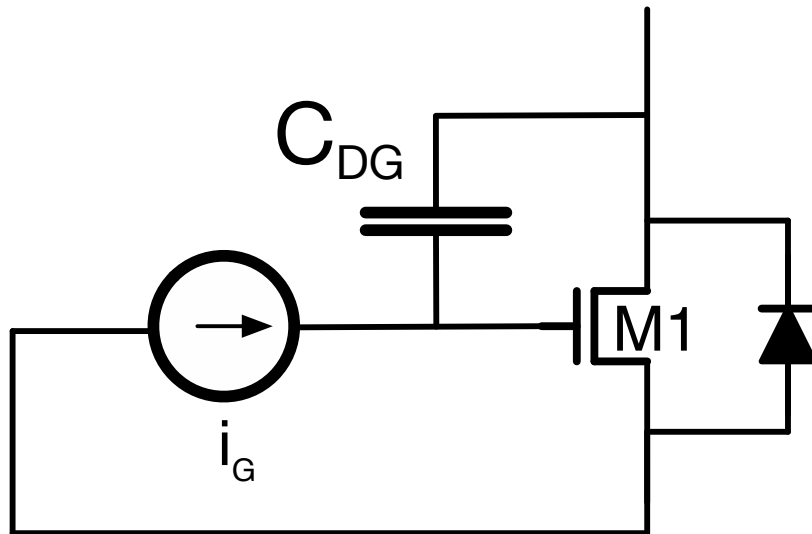


$$\frac{dV_D}{dt} = \frac{i_G}{C_{DG}}$$

$$\Delta t = \frac{\Delta V_D C_{DG}}{i_G}$$


Example: $i = 0.5\text{A}$, $C = 100\text{pF}$, $\Delta V = 400\text{V}$

Bootstrap Supply

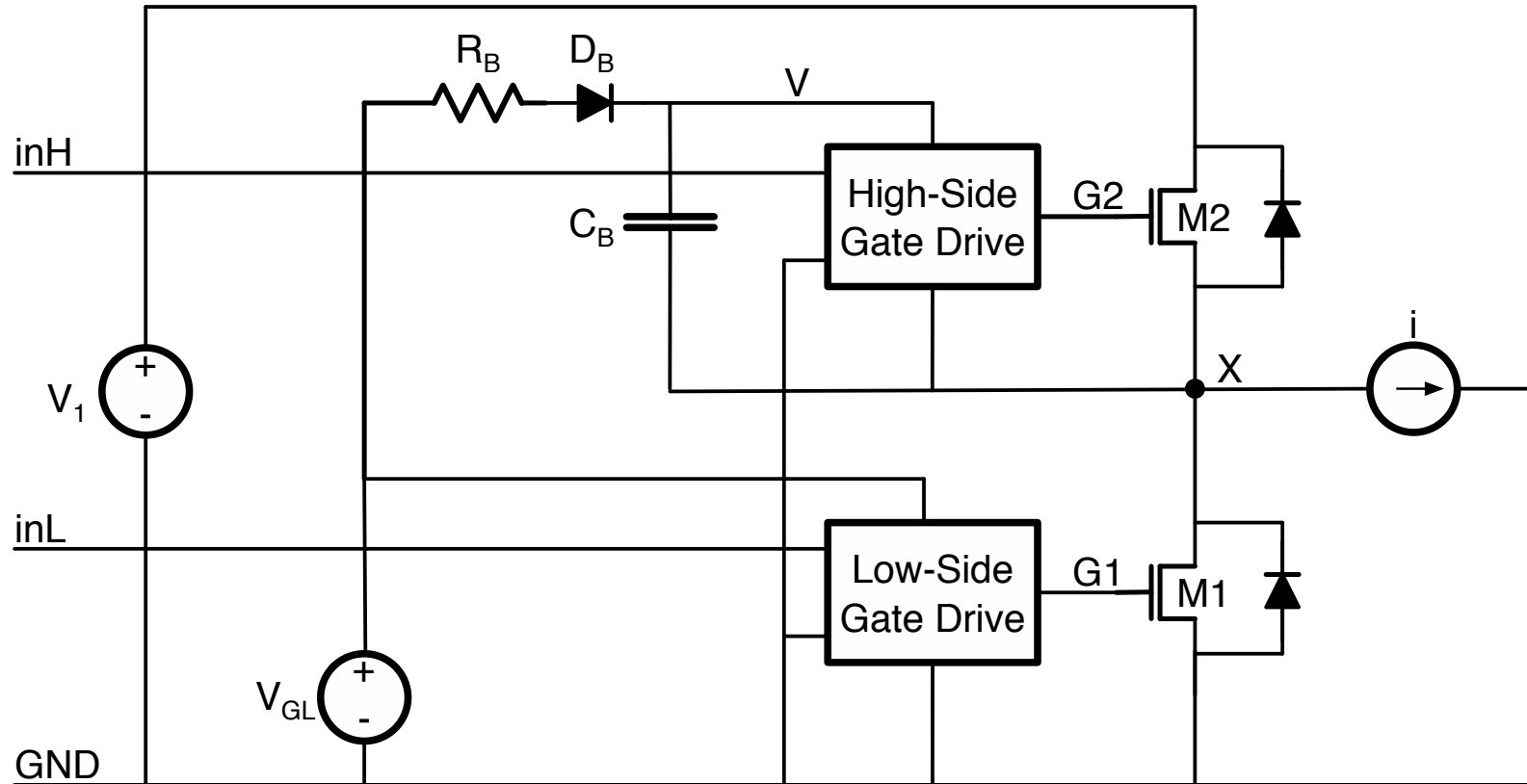


Dead Time


Too Little Dead Time (11.6kW loss)

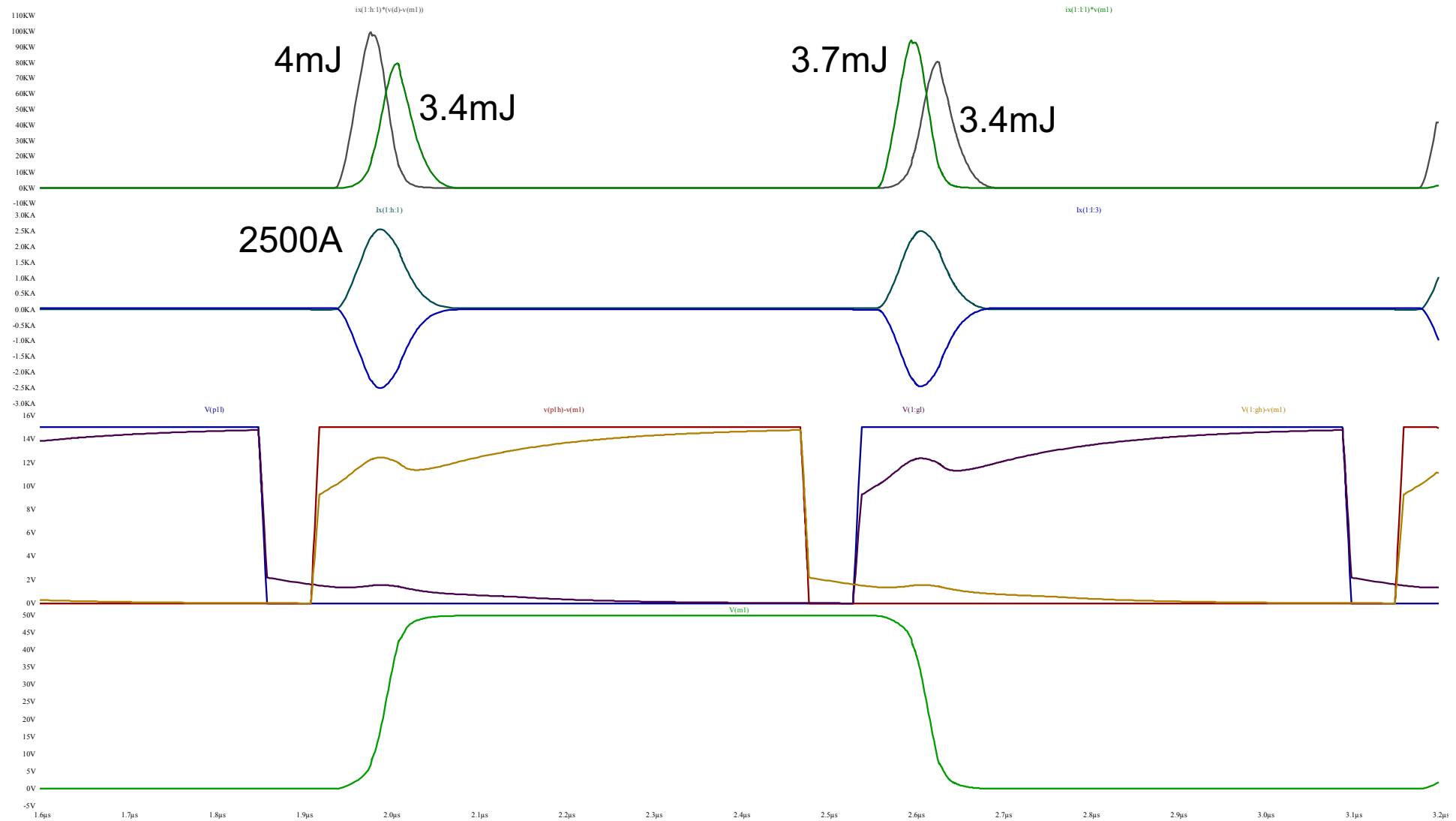

The "Real" Gate Signal

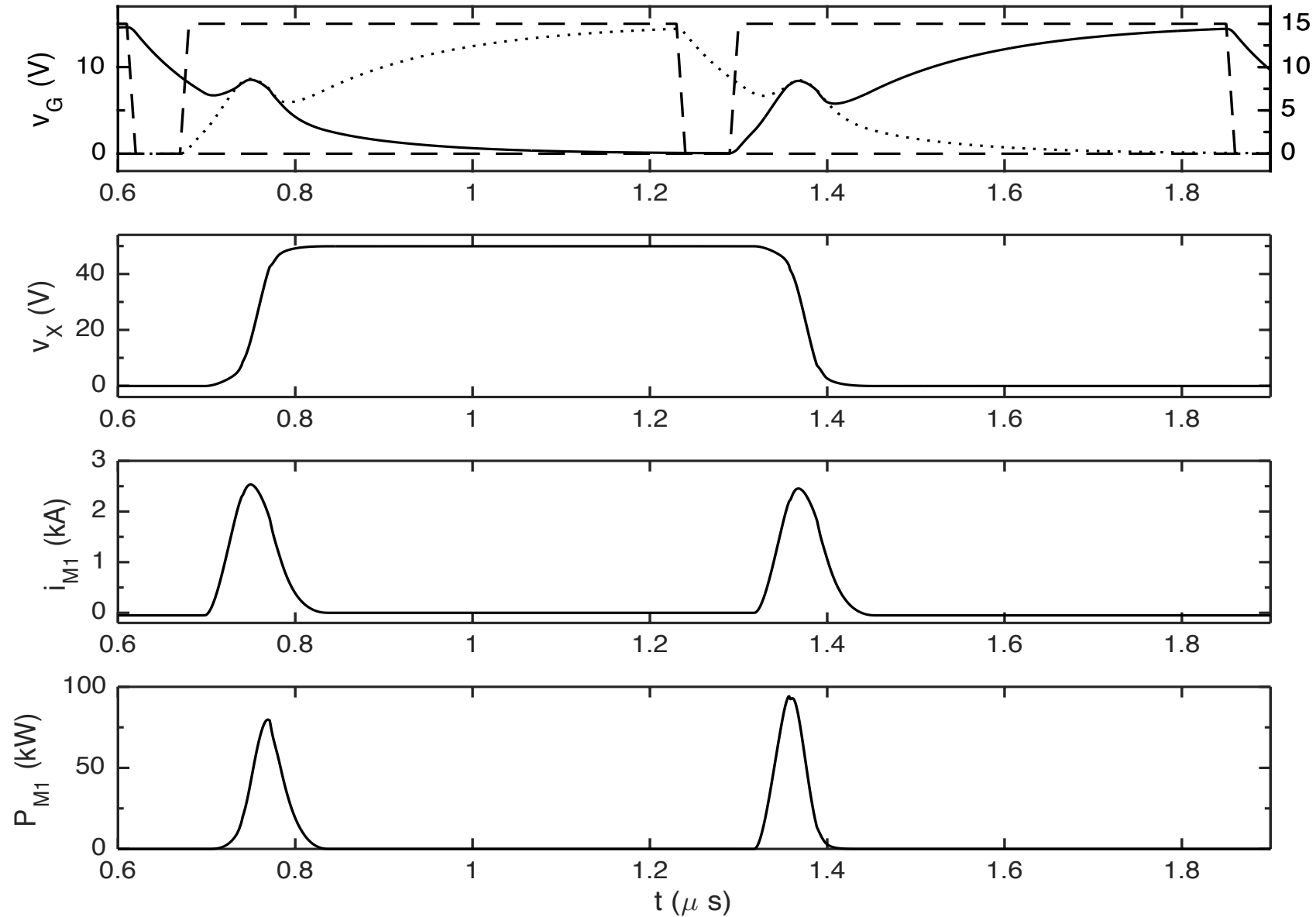


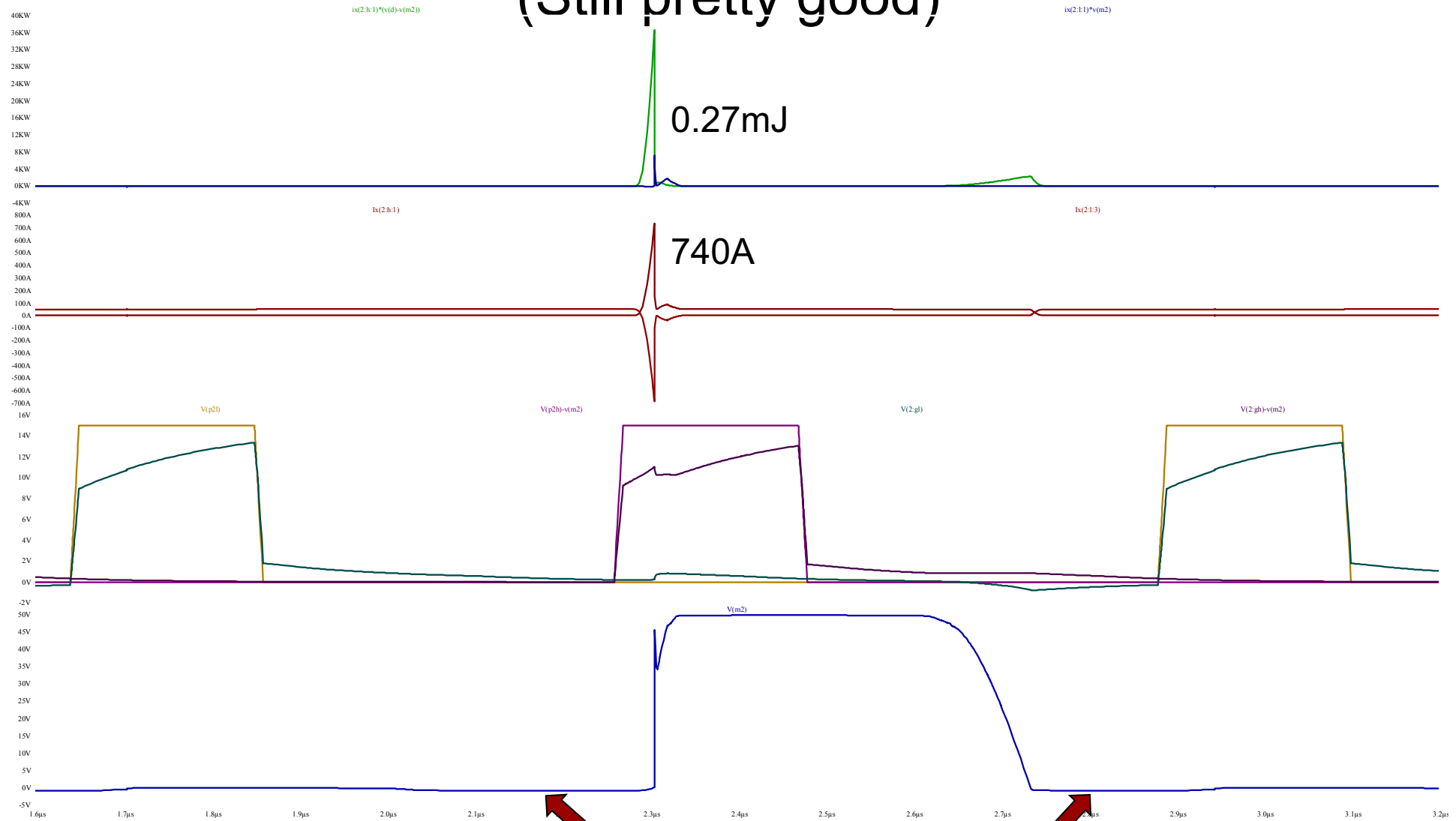Too Much Dead-Time (340W loss) (Still pretty good)



700mV diode drop

Just Right (310W loss)

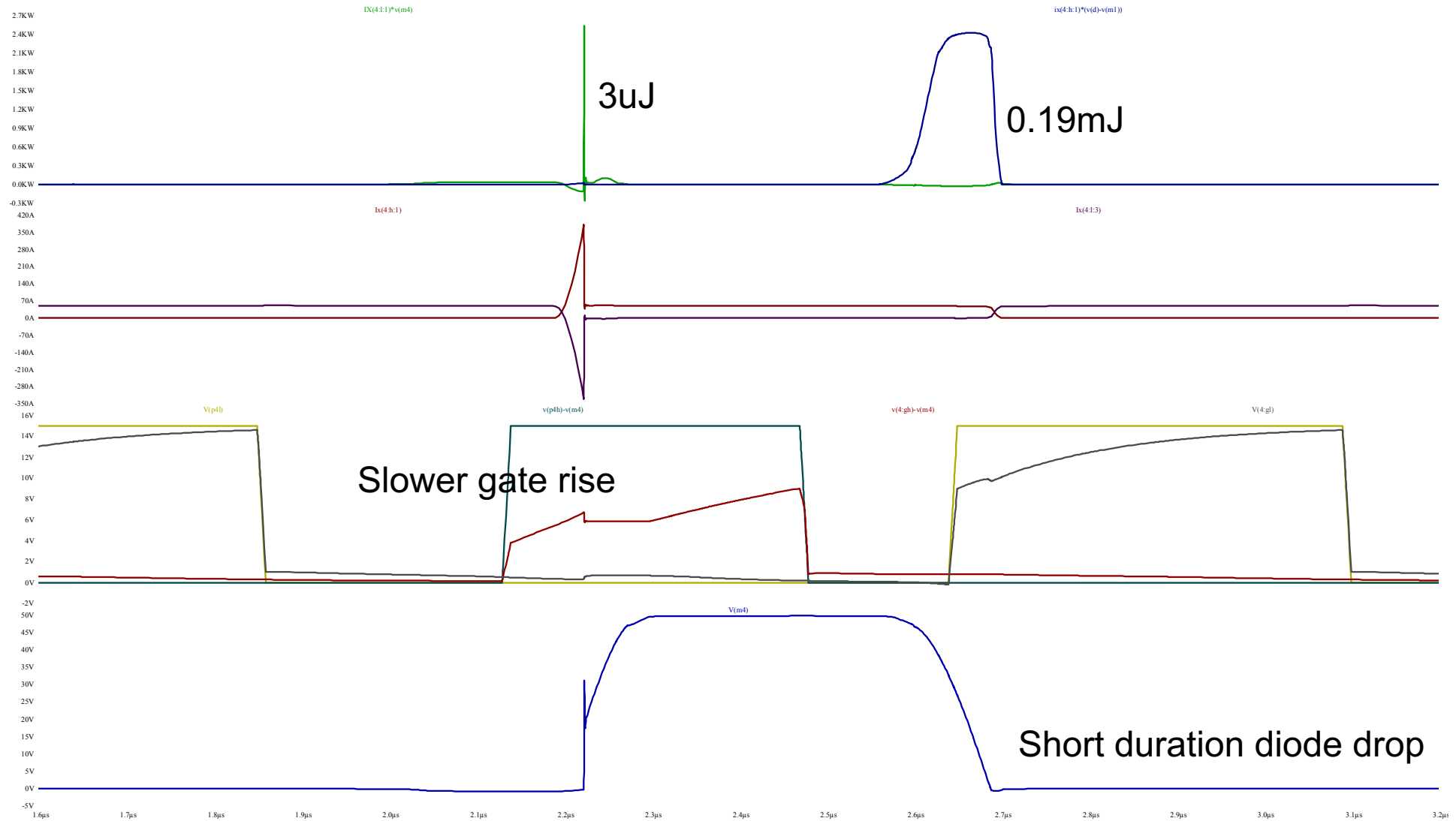


Conduction loss is $I^2R = 50^2 \times 1m \sim 25W$

Too much dead time is better than too little

Snubbers

Dampen Ringing Nodes

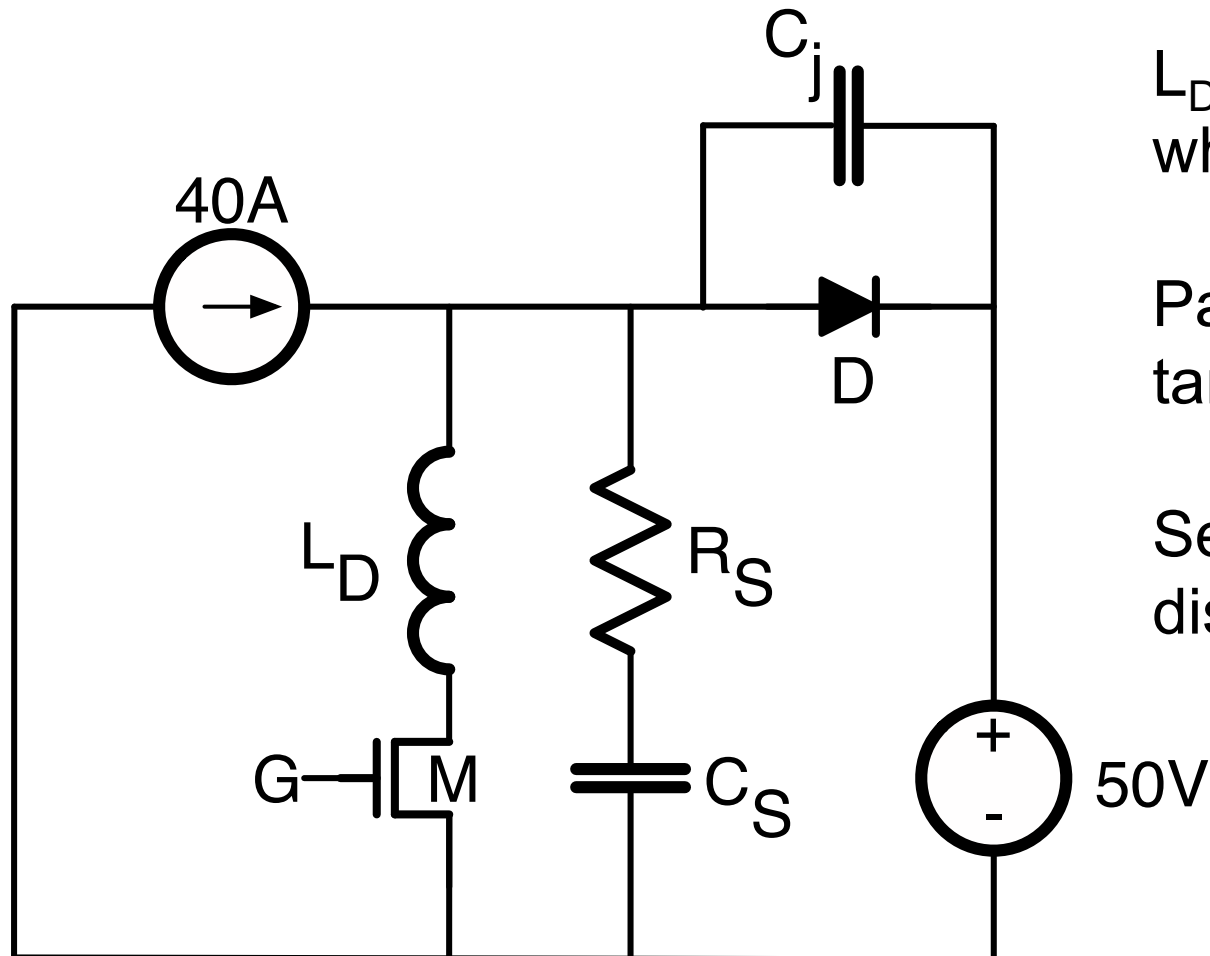


L_D and C_j resonate
when M is on


Parallel R_S dampens
tank

Series C_S limits
dissipation


Inductance on Drain

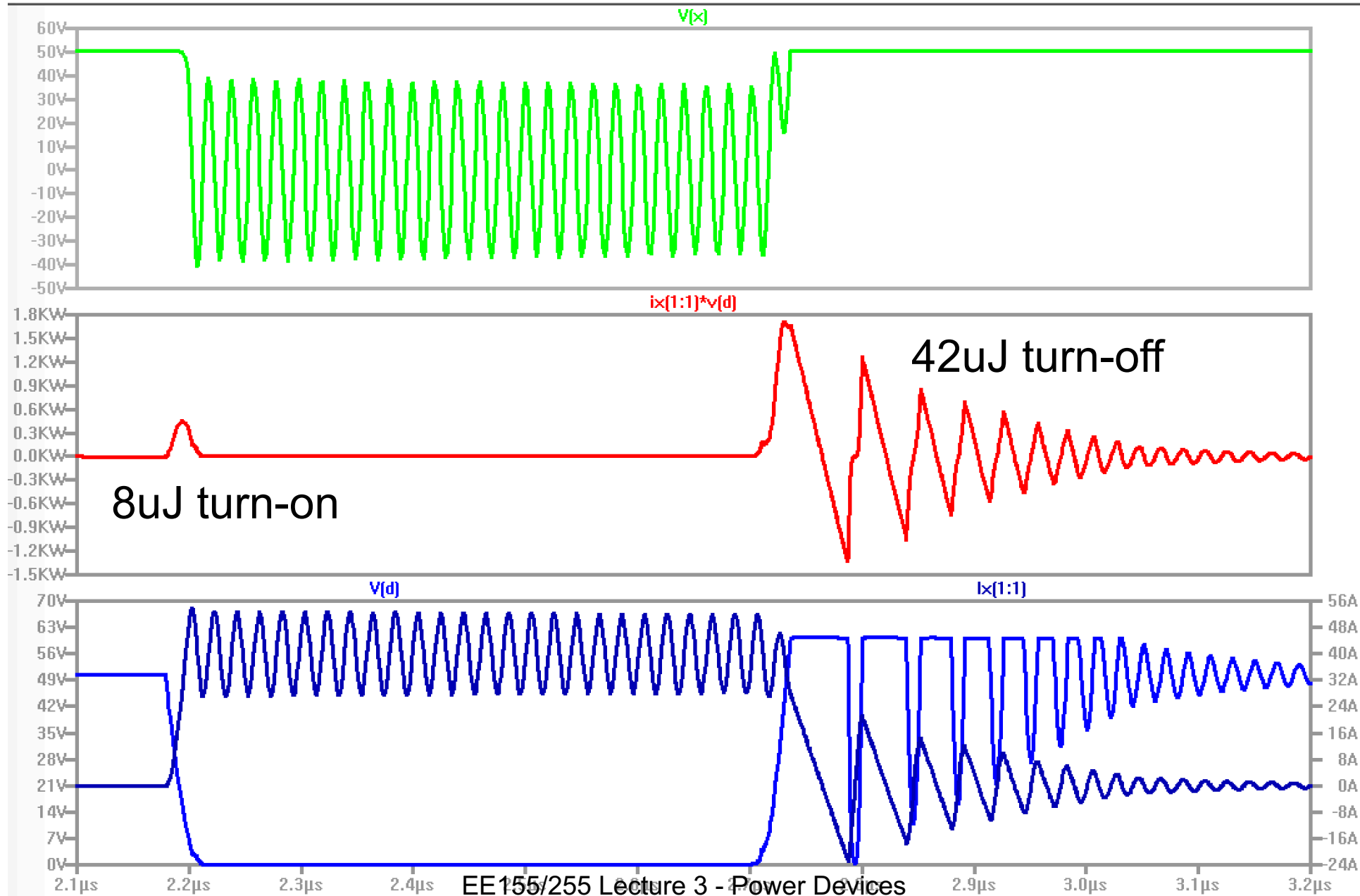

With Snubber (1nF, 5Ω)

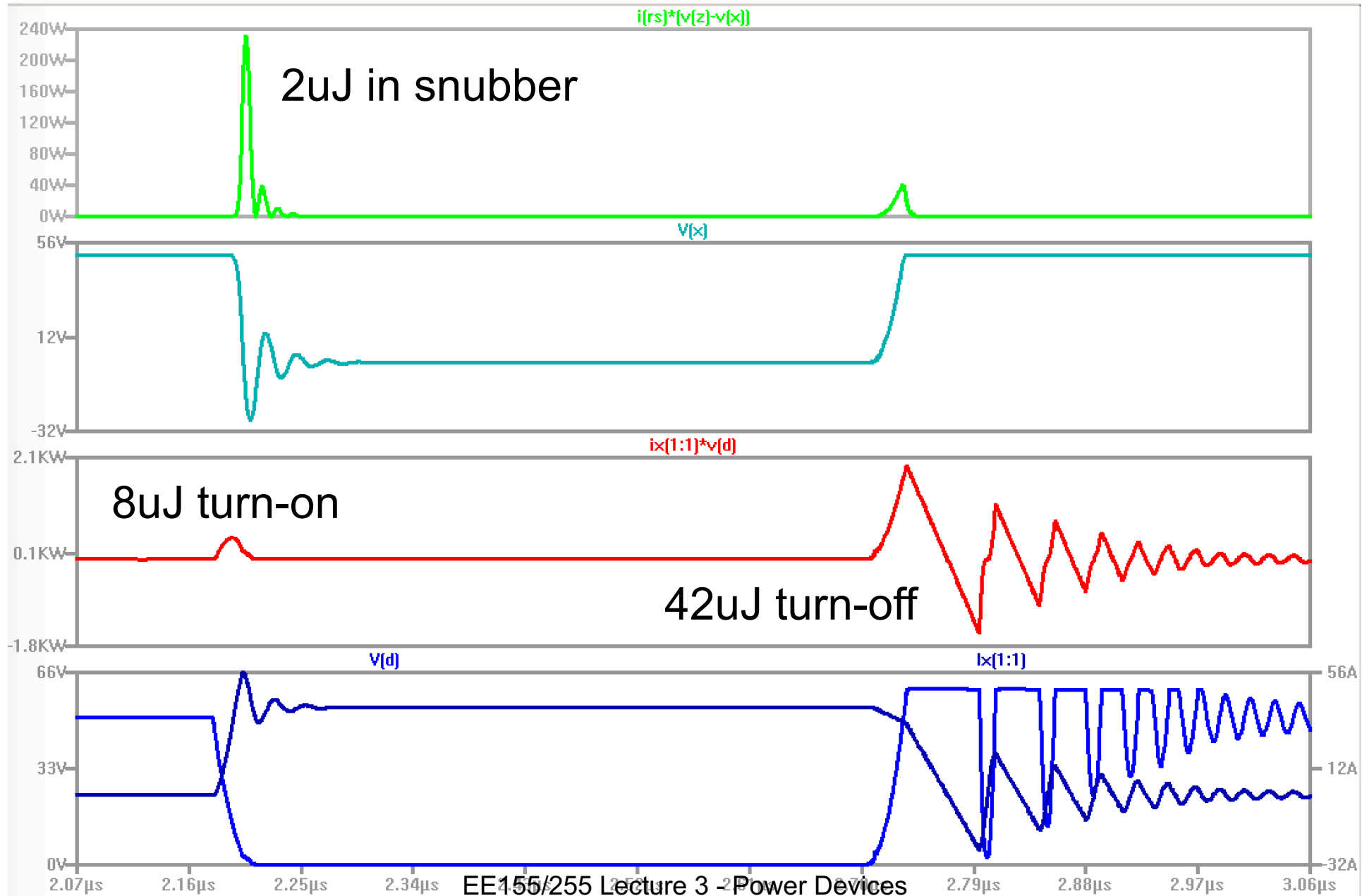

Design Procedure

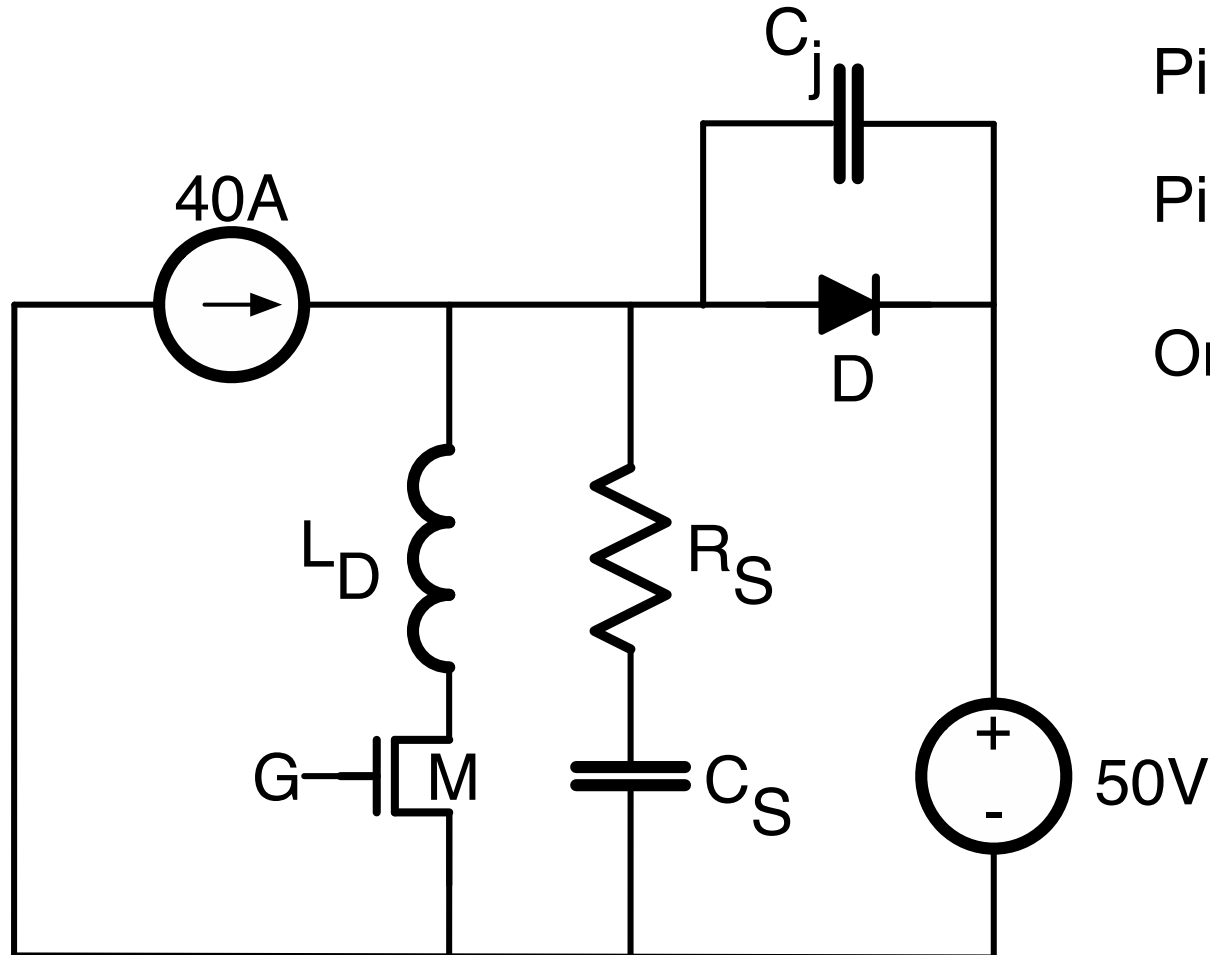

Pick $R_S \sim 1/\omega C_j$


Pick C_S so

$$\tau \geq \pi/\omega$$

Or

$$E_s = C_S V^2/2$$

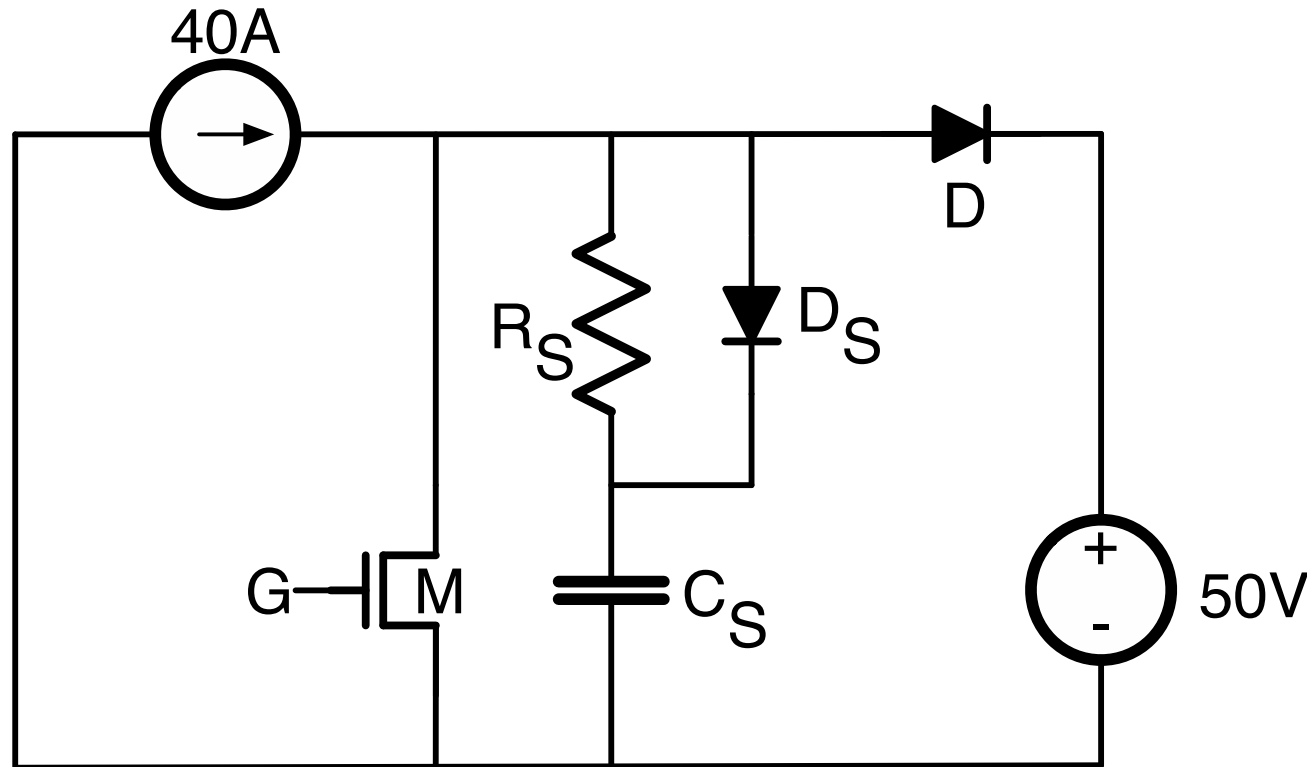Move Turn-Off Dissipation to Passive Device



C_S slows rise time of drain

$C_S V^2 / 2R_S$ dissipated in R_S when C_S discharges


Rarely used today

Other forms slow fall time and rising/falling current

Summary

- Real switches have limitations
 - Conduction losses (R_{ON} for FETs, V_{CE} for IGBTs, Diode drop)
 - Switching losses (finite t_{on} , t_{off} , t_{rr})
 - With current source load, current ramps, then voltage falls
 - And voltage rises before current falls
 - May be dominated by reverse recovery time
 - Complicated by inductance
- Power MOSFETs
 - Switch quickly, have linear I-V, integral diode
- IGBTs
 - Diode-like I-V, slower switching
- Diodes
 - Have reverse recovery time
- Switches operate in pairs
 - For one-way converters, one switch may be a diode
 - Synchronous rectification – make both switches FETs to reduce loss
 - Need “dead time” to avoid “shoot through” current
- Gate-drive circuits control rise and fall times
- Bootstrap supply needed for high-side driver
- Snubbers dampen voltage and current transients

Course at a Glance

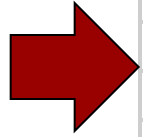

No	Date	Topic	HW out	HW in	Lab out	Lab ck	Lab	HW
1	9/25/17	Intro (basic converters)	1		1		Intro to ST32F3	Periodic Steady State
2	9/27/17	Embedded Prog/Power Elect.						
3	10/2/17	Power Electronics - 1 (switches)	2	1	2	1	AC Energy Meter	Power Devices
4	10/4/17	Power Electronics - 2 (circuits)						
5	10/9/17	Photovoltaics	3	2	3	2	PV MPPT	Motor control Matlab
6	10/11/17	Feedback Control						
7	10/16/17	Electric Motors	4	3	4	3	Motor control - Lab/	Feedback
8	10/18/17	Isolated Converters						
9	10/23/17	Solar Day	5/PP	4	5	4	PS	Isolated Converters
10	10/25/17	Magnetics						
11	10/30/17	Soft Switching	6	5/PP	6	5	Magnetics	Magnetics and Inverters
12	11/1/17	Project Discussions						
13	11/6/17	Inverters, Grid, PF, and Batteries		6	P	6	Project	
14	11/8/17	Thermal & EMI						
15	11/13/17	Quiz Review				C1		
16	11/15/17	Grounding, and Debugging						
Q	11/15/17	Quiz - in the evening						
	11/20/17	Thanksgiving Break				C2		
	11/22/17	Thanksgiving Break						
17	11/27/17	Wrapup						
18	11/29/17	Guest Lecture				C3		
19	12/4/17	Guest Lecture						
20	12/6/17	No Class						
	TBD	Project presentations			P			
	12/15/17	Project webpage due						