

Lecture #4: Programmable Logic Structure

Paul Hartke

Phartke@stanford.edu

Stanford EE121


January 17, 2001

Book Reading

- Chapter 1
- Chapter 2.1-2.6
- Chapter 3.1.-3.7
- Chapter 4.1-4.3, 4.5
- Chapter 5.3, 5.4.1, 5.4.8, 5.5.1, 5.7.0, 5.8.1-5.8.4, 5.9.1-5.9.3, 5.10.1-5.10.7, 5.11.1
 - Know the architectures involved but don't need the TTL equivalents or ABEL/VHDL
- Chapter 10.5-10.6
 - Difference between CPLD and FPGA architecture

How do you drive a LED with CMOS?

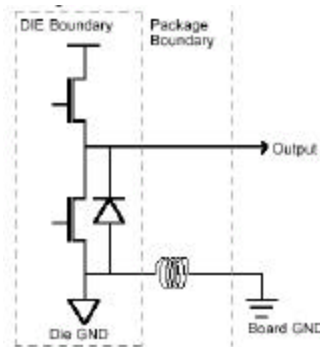- Point is that static power is used.
- Static power is a problem.
- Dynamic power has its issues as well.
- $V=L \cdot di/dt$



Ground Bounce

- Mitigations
 - Internal Bypass Capacitors
 - More Power and Ground Pins
 - Lower Slew Rate of I/O

- More info:

– http://www.idt.com/docs/AN_147.pdf


 


Figure 10, $V_{olv} = 0.7V$ can cause false switching


Mux as way to Implement Logic

- We did this in E40 and it's the same here
- Wired like this, small ROM
- If the inputs are configurable

Then basis for LookUp Table
(LUT) FPGAs

 

Combinational Programmable Logic Devices

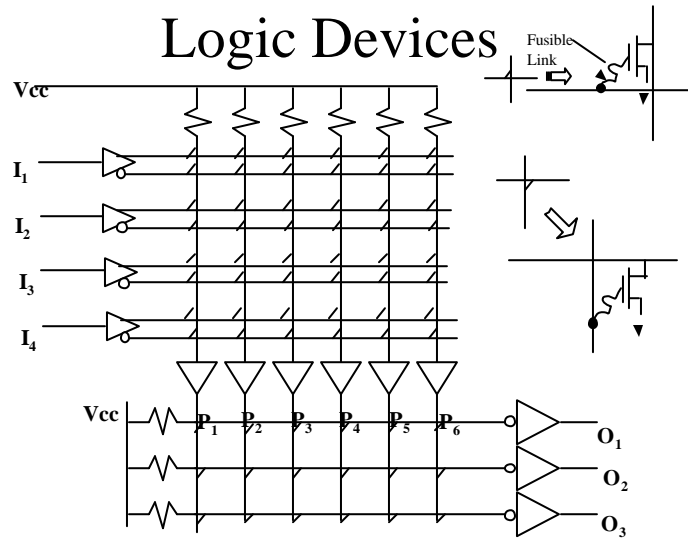


CPLDs (2)

- Burn in the interconnection to create logic
 - Uses wired logic but could be implemented with static CMOS
 - In Eetimes this week, Xilinx announced they are phasing out this architecture.
 - Too much power.

Erasable PLD

 - Replace fuse with re-programmable device
 - Charge can be injected onto the floating gate thus turning the transistor off. The charge will remain on the gate even if the power is turned off. Later, if desired, the charge can be removed. The process is repeatable.




FPGAs

- Field Programmable Gate Arrays have a more general structure but based on these primitives.

FPGA Micro-Architecture


Xilinx Logic Cell Arrays General Chip Architecture:

 - Look Blocks (CLBs)
- IO Blocks (IOBs)
- Wiring Channels
- Other goodies (BlockRam)
- Use Data Books
- <http://xilinx.com/partin>



Wiring Channels

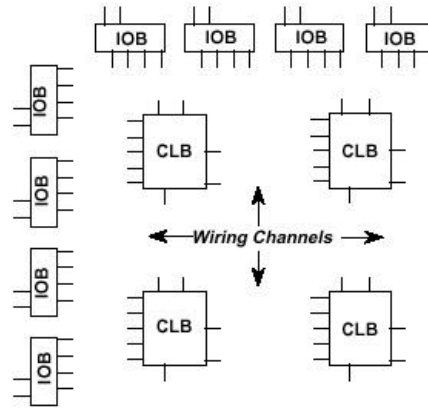- Interconnect Logic created in FPGA to connect up logic
- Reconfigurable
- BIG FPGA feature



CLB Diagram From Data Book

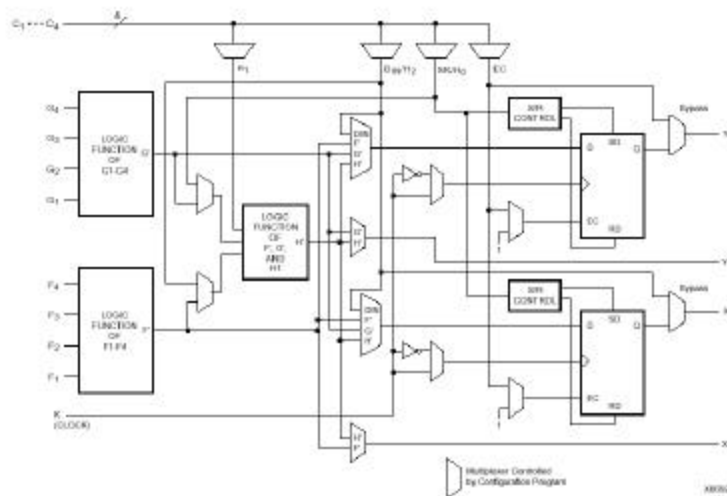


Figure 1: Simplified Block Diagram of XC4000 Series CLB (RAM and Carry Logic functions not shown)

IOB Diagram from Data Book

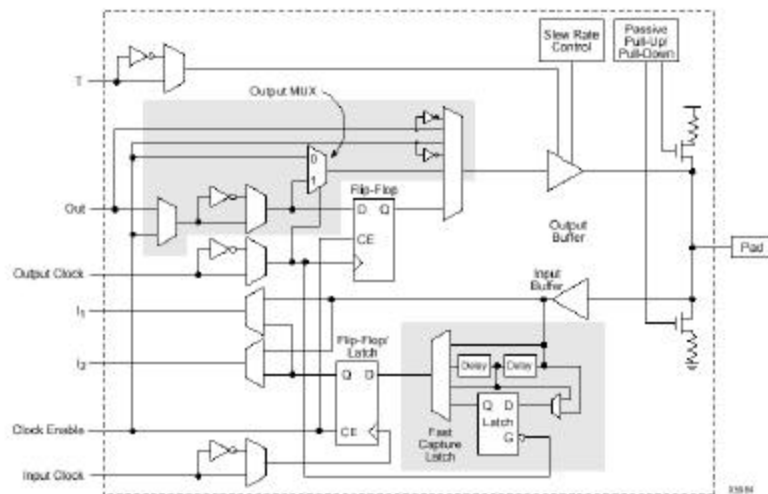


Figure 16: Simplified Block Diagram of XC4000X IOB (shaded areas indicate differences from XC4000E)

IOB Notes

- Note Tristate output driver
- Slew Rate control used to limit edge speed to lower instantaneous power (which affects ground bounce).
- Flip Flop at input so you don't have to drive into interconnect.

Interconnect around CLB

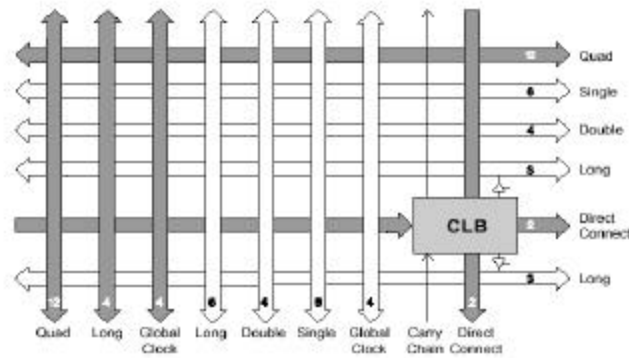


Figure 25: High-Level Routing Diagram of XC4000 Series CLB (shaded arrows indicate XC4000X only)

Programmable Switch Matrix


 


Figure 26: Programmable Switch Matrix (PSM)

More Routing

 

- Common to XC4000E and XC4000X
- XC4000X only
- Programmable Switch Matrix

Figure 27: Detail of Programmable Interconnect Associated with XC4000 Series CLB

Last Routing Slide!! 😊

 


Figure 30: XC4000X Direct Interconnect

Timing Info

- <http://xilinx.com/partinfo/ds005.pdf>
- Use this info to guesstimate how fast design “should” run.

CLB Switching Characteristic Guidelines

Description	Symbol	-3		-2		-1		-09		-00	
		Min	Max	Min	Max	Min	Max	Min	Max	Min	Max
Combinatorial Delays											
F/D inputs to X/Y outputs	T _{FD}		1.8		1.5		1.3		1.2		1.1
F/D inputs via H' to X/Y outputs	T _{FD'}		2.7		2.4		2.2		2.0		1.9
F/D inputs via transparent latch to Q outputs	T _{FDQ}		2.9		2.6		2.2		2.0		1.8
C inputs via SR/H0 via H to X/Y outputs	T _{CH0}		2.5		2.2		2.0		1.8		1.8
C inputs via H1 via H to X/Y outputs	T _{CH1}		2.4		2.1		1.9		1.6		1.5
C inputs via DIN/H2 via H to X/Y outputs	T _{CH2}		2.5		2.2		2.0		1.8		1.8
C inputs via EC, DIN/H2 to YQ, XQ output (bypass)	T _{CAVP}		1.5		1.3		1.1		1.0		0.9

FPGA Figures of Merit

- FPGA operating frequency for your design is hard to predict beforehand.
- Run some micro-benchmarks on different FPGAs to get a feel for their perf and how much logic you can put between flip flops.
- 32 bit fast adder size and speed.

Understand FPGA Architecture

- Look up table (LUT) based with fixed and ***limited*** routing resources.
- So logic is cheap (consider 4 input XOR in VLSI) but wires are very expensive.
- FPGAs are manufactured in the same chip fabs as “high performance” ASICs based on standard CMOS. The tradeoff is easy of design vs performance.
 - Often a good tradeoff.