

# Synchronization in Digital Logic Circuits

Ryan Donohue  
Rdonohue@yahoo.com


## Synchronization: Why care?

- ◆ Digital Abstraction depends on all signals in a system having a valid logic state
- ◆ Therefore, Digital Abstraction depends on reliable synchronization of external events

## The Real World


 
### ◆ Real World does not respect the Digital Abstraction!

- Inputs from the Real World are usually asynchronous to your system clock
- Inputs that come from other synchronous systems are based on a different system clock, which is typically asynchronous to your system clock



  
## Metastability

- ◆ When asynchronous events enter your synchronous system, they can cause bistables to go into metastable states
- ◆ Every real life bistable (such as a D-latch) has a metastable state



## Quick Metastability Review

 

- ◆ Once a FF goes metastable (due to a setup time violation, say) we can't say when it will assume a valid logic level or what level it might eventually assume
- ◆ The only thing we know is that the probability of a FF coming out of a metastable state increases exponentially with time

## Mean Time Between Failures

- ◆ For a FF we can compute its MTBF, which is a figure of merit related to metastability.

$$MTBF(t_r) = \frac{e^{(t_r/t)}}{T_0 f a}$$

$t_r$  resolution time (time since clock edge)  
 $f$  sampling clock frequency  
 $a$  asynchronous event frequency  
 $t$  and  $T_0$  FF parameters

For a typical .25um  
 ASIC library FF

$t_r = 2.3ns$   
 $t = 0.31ns$   
 $T_0 = 9.6as$

For  $f = 100MHz$ ,  
 $a = 1MHz$


MTBF = 20.1 days

## Synchronizer Requirements

- ◆ Synchronizers must be designed to reduce the chances system failure due to metastability
- ◆ Synchronizer requirements
  - Reliable [high MTBF]
  - Low latency [works as quickly as possible]
  - Low power/area impact
 
## Single signal Synchronizer

- ◆ Traditional synchronizer
  - SIG is asynchronous, and META might go metastable from time to time
  - However, as long as META resolves before the next clock period SIG1 should have valid logic levels
  - Place FFs close together to allow maximum time for META to resolve



## Single Synchronizer analysis

- ◆ MTBF of this system is roughly:

$$MTBF(t_r) = \frac{e^{(t_r/t)}}{T_o f a} \times \frac{e^{(t_r/t)}}{T_o f}$$


MTBF =  $9.57 \times 10^{10}$  years  
Age of Earth =  $5 \times 10^9$  years

For a typical .25um  
ASIC library FF

$t_r = 2.3\text{ns}$   
 $t = 0.31\text{ns}$   
 $T_o = 9.6\text{as}$


For  $f = 100\text{MHz}$ ,  
 $a = 1\text{MHz}$

 - ◆ Can increase MTBF by adding more series stages



 
## Flip Flop design is important?

- ◆ Dynamic FFs not suitable for synchronizers since they have no regeneration



CMOS Dynamic FF

 


TSFF (Svenson)

- ◆ Special 'SYNC' FFs should be used for the primary synchronizer if available

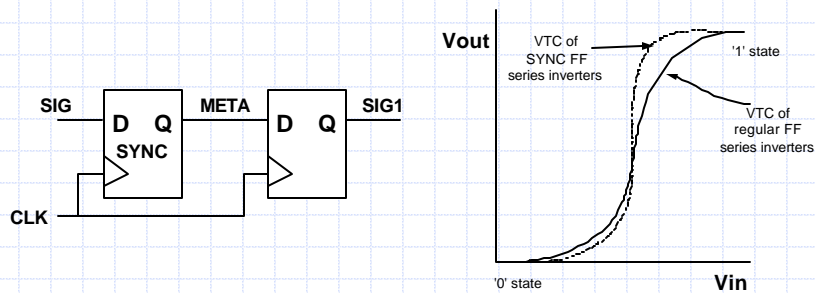
## SYNC Flip Flop

- ◆ SYNC Flip Flops are available in some ASIC libraries
  - Better MTBF characteristics due to high gain in the feedback path
  - Very large (5x regular FF) and very high power



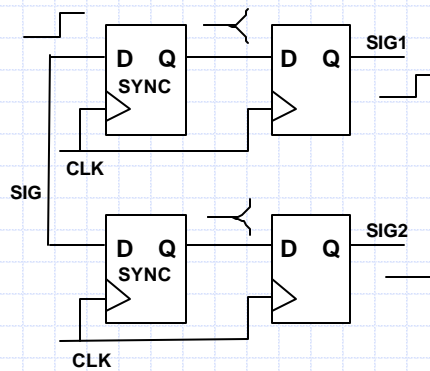
## Synchronization Pitfall

- ◆ Never synchronize the same signal in multiple places! Inconsistency will result!




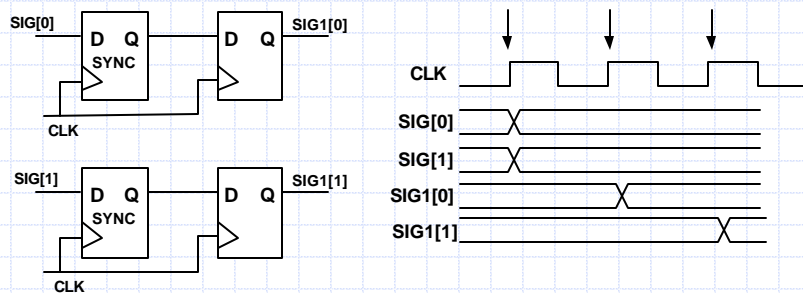
## Bus Synchronization

- ◆ Obvious approach is to use single signal synchronizers on each bit
- ◆ WRONG!



  
## Handshaking is the Answer

- ◆ Need a single point of synchronization for the entire bus


 
## Handshaking Rules

- ◆ Sender outputs data and THEN asserts REQ
- ◆ Receiver latches data and THEN asserts ACK
- ◆ Sender deasserts REQ, will not reassert it until ACK deasserts
- ◆ Receiver sees REQ deasserted, deasserts ACK when ready to continue



## Alternate Handshaking Scheme

- ◆ Previous example is known as 4-phase handshaking
- ◆ 2-phase (or edge based) handshaking is also suitable
  - Sender outputs data and THEN changes state of REQ, will not change state of REQ again until after ACK changes state.
  - Receiver latches data. Once receiver is ready for more it changes state of ACK.
- ◆ 2-phase requires one bit of state be kept on each side of transaction. Used when FFs are inexpensive and reliable reset is available.




## High Bandwidth solutions

- ◆ Handshaking works great, but reduces bandwidth at the clock crossing interface because each piece of data has many cycles of series handshaking.
- ◆ Correctly designed FIFOs can increase bandwidth across the interface and still maintain reliable communication

 
## Abstract FIFO design

- ◆ Ideal dual port FIFO writes with one clock, reads with another
- ◆ FIFO storage provides buffering to help rate match load/unload frequency
- ◆ Flow control needed in case FIFO gets totally full or totally empty



 
## FIFO in detail

- ◆ FIFO of any significant size is implemented using an on-chip SRAM
- ◆ SRAM must be dual-ported for our design [have two independent ports]
- ◆ We will use a write pointer to determine the write address, and a read pointer to determine the read address


 
## FIFO pointer control

- ◆ FIFO is managed as a circular buffer using pointers.
- ◆ First write will occur at address 00h. Next write will occur at 01h. After writing at FFh, next write will wrap to 00h.
- ◆ Reads work the same way. First read will occur at address 00h.



## FIFO pointers and flow control

### ◆ Generation of FULL and EMPTY signals.

- FIFO is FULL when write pointer catches read pointer

```
always @(posedge clk1)
FULL <= (WR_PNTR == RD_PNTR) && ((OLD_WR_PNTR + 1 == RD_PNTR) || FULL)
```

- FIFO is empty when read pointer catches write pointer


```
always @(posedge clk2)
EMPTY <= (WR_PNTR == RD_PNTR) && ((OLD_RD_PNTR + 1 == WR_PNTR) || EMPTY)
```

### ◆ Write pointer and read pointer must never pass each other.

- Write passing read overwrites unread data
- Read passing write re-reads invalid data

## FIFO in detail


### ◆ We have a problem!

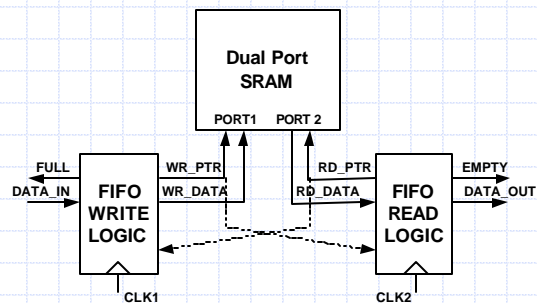

To generate FULL/EMPTY conditions the write logic needs to see the read pointer and the read logic needs to see the write pointer!

 
## Pointer Synchronization

- ◆ Our pointers change in a very specific way (when they change, they increment by 1)
  - Applying a traditional two stage FF synchronizer on each bit of a binary pointer could cause a wildly invalid pointer value to be produced
  - Gray coding the pointer value means at most one bit will change per cycle – we can only be 'off by one'


 
## Pointer Synchronizer

- ◆ Pointer is stored in gray code.
- ◆ A standard single bit synchronizer is used on each bit of PTR\_OUT. At most one bit changes per cycle!
- ◆ We can still do binary math to increment the pointer.



```

module bin2gray (bin,gray);
    parameter SIZE = 4;
    input [SIZE-1:0] bin;
    output [SIZE-1:0] gray;
    reg [SIZE-1:0] gray;


    always @(bin)
        gray = (bin >> 1) ^ bin;
endmodule

module gray2bin (gray,bin);
    parameter SIZE = 4;
    input [SIZE-1:0] gray;
    output [SIZE-1:0] bin;
    reg [SIZE-1:0] bin;


    integer i;
    always @(gray)
        for (i=0; i<SIZE; i=i+1)
            bin[i] = ^(gray >> i);
endmodule
    
```
 
## Pointer Synchronizer pitfall


- ◆ Write and read pointers need to be registered in gray code as shown on previous slide.
- ◆ Don't be tempted to cheat and register pointers in binary. What's wrong with the synchronizer shown below?



## Answer to pitfall

 

 
- ◆ Combinational logic frequently contains hazards at the output (non fully covered Karnaugh map)
- ◆ Avoid this problem by using a registered value of PTR\_IN



## Pointer math pitfall

- ◆ When our pointer synchronizer goes metastable our new pointer value may not be updated until one cycle later.
- ◆ We need to be conservative when generating FULL and EMPTY signals to reflect this.
  - Typically FULL = 1 when WRITE catches READ.  
We need FULL = 1 when WRITE catches READ-1.
  - Typically EMPTY = 1 when READ catches WRITE.  
We need EMPTY = 1 when READ catches WRITE-1.


## Final Synchronizer FIFO Design

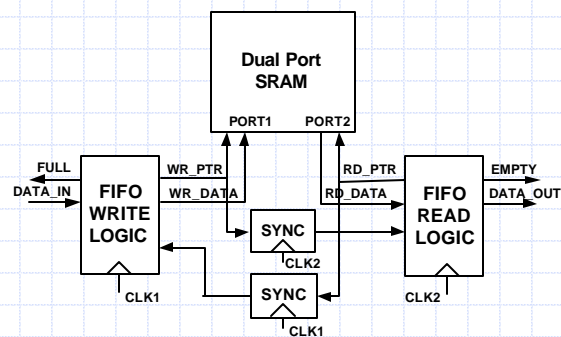

Works for any phase/frequency relationship  
between CLK1 and CLK2
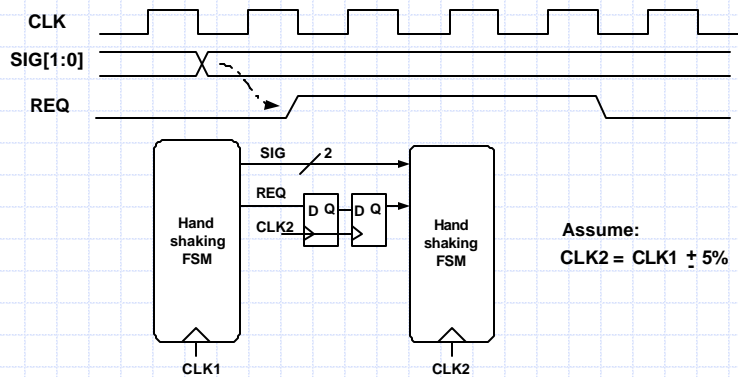
## Mesosynchronous Designs

- ◆ When two systems of bounded frequency need communicate, open loop synchronization circuits can be used (no ACK)



## Mesosynchronous Tradeoffs

- ◆ Benefits to mesosynchronous designs
  - Less synchronization circuitry
  - Synchronizer might have lower latency vs. full 4-phase handshaking
- ◆ Costs of mesosynchronous designs
  - Synchronizer only works at certain frequency ratios (may hamper bringup/debug)
  - Intolerant of spec mistakes (maybe that unload frequency was supposed to be  $\pm 50\%$ !)

## Words to the wise

- ◆ Be wary of synchronizer schemes designed by others
    - Synopsys Designware DW04\_sync multi-bit synchronizer DOES NOT WORK as a synchronizer
    - Synthesizers might use dynamic FFs as synchronizers – they don't know the difference.
    - Auto-placement tools must be told to place synchronizer FF pairs close together
- BE PARANOID

## Conclusions

- ◆ Synchronizers are important. Synchronization failure is deadly and difficult to debug
- ◆ Synchronization requires careful design. Most CAD and logic tools CANNOT catch bad synchronizer designs.
- ◆ Design of synchronizer depends on performance level needed. Basic synchronizer of back-to-back FFs is the core design all others are based on.