

Synchronization in Digital Logic Circuits


Ryan Donohue
Rdonohue@yahoo.com

Synchronization: Why care?

- ◆ Digital Abstraction depends on all signals in a system having a valid logic state
- ◆ Therefore, Digital Abstraction depends on reliable synchronization of external events


The Real World

 - ◆ Real World does not respect the Digital Abstraction!
 - § Inputs from the Real World are usually asynchronous to your system clock
 - § Inputs that come from other synchronous systems are based on a different system clock, which is typically asynchronous to your system clock




Metastability

 - ◆ When asynchronous events enter your synchronous system, they can cause bistables to go into metastable states
- ◆ Every real life bistable (such as a D-latch) has a metastable state



Quick Metastability Review

 

- ◆ Once a FF goes metastable (due to a setup time violation, say) we can't say when it will assume a valid logic level or what level it might eventually assume
- ◆ The only thing we know is that the probability of a FF coming out of a metastable state increases exponentially with time

Mean Time Between Failures

- ◆ For a FF we can compute its MTBF, which is a figure of merit related to metastability.

$$MTBF(t_r) = \frac{e^{(t_r/D)}}{T_o f a}$$

t_r , resolution time (time since clock edge)
 f , sampling clock frequency
 a , asynchronous event frequency
 T_o and T_o , FF parameters

For a typical .25um
 ASIC library FF
 $t_r = 2.3ns$
 $D = 0.31ns$
 $T_o = 9.6as$


For $f = 100MHz$,
 $a = 1MHz$ **MTBF = 20.1 days**

Synchronizer Requirements

- ◆ Synchronizers must be designed to reduce the chances system failure due to metastability
- ◆ Synchronizer requirements
 - § Reliable [high MTBF]
 - § Low latency [works as quickly as possible]
 - § Low power/area impact

Single signal Synchronizer

 - ◆ Traditional synchronizer
 - § SIG is asynchronous, and META might go metastable from time to time
 - § However, as long as META resolves before the next clock period SIG1 should have valid logic levels
 - § Place FFs close together to allow maximum time for META to reslove



Single Synchronizer analysis

- ◆ MTBF of this system is roughly:


$$MTBF(t_s) = \frac{e^{-(t_s/D)}}{T_o f a} \times \frac{e^{-(t_s/D)}}{T_o f}$$

For a typical .25um ASIC library FF

$t_s = 2.3ns$ For $f = 100MHz$,
 $\tau = 0.31ns$ $a = 1MHz$,
 $T_o = 9.6as$


MTBF = 9.57×10^{10} years
 Age of Earth = 5×10^9 years

 - ◆ Can increase MTBF by adding more series stages



Flip Flop design is important?

 
- ◆ Dynamic FFs not suitable for synchronizers since they have no regeneration



- ◆ Special `_SYNC_` FFs should be used for the primary synchronizer if available


SYNC Flip Flop

 - ◆ SYNC Flip Flops are available in some ASIC libraries
 - Better MTBF characteristics due to high gain in the feedback path
 - Very large (5x regular FF) and very high power




Synchronization Pitfall

 - ◆ Never synchronize the same signal in multiple places! Inconsistency will result!





Bus Synchronization

 - ◆ Obvious approach is to use single signal synchronizers on each bit
- ◆ **WRONG!**



Handshaking is the Answer

  - ◆ Need a single point of synchronization for the entire bus



Handshaking Rules

- ◆ Sender outputs data and THEN asserts REQ
- ◆ Receiver latches data and THEN asserts ACK
- ◆ Sender deasserts REQ, will not reassert it until ACK deasserts
- ◆ Receiver sees REQ deasserted, deasserts ACK when ready to continue



Alternate Handshaking Scheme


- ◆ Previous example is known as 4-phase handshaking
- ◆ 2-phase (or edge based) handshaking is also suitable
 - Sender outputs data and THEN changes state of REQ, will not change state of REQ again until after ACK changes state.
 - Receiver latches data. Once receiver is ready for more it changes state of ACK.
- ◆ 2-phase requires one bit of state be kept on each side of transaction. Used when FFs are inexpensive and reliable reset is available.

High Bandwidth solutions

- ◆ Handshaking works great, but reduces bandwidth at the clock crossing interface because each piece of data has many cycles of series handshaking.
- ◆ Correctly designed FIFOs can increase bandwidth across the interface and still maintain reliable communication


Abstract FIFO design

 - ◆ Ideal dual port FIFO writes with one clock, reads with another
- ◆ FIFO storage provides buffering to help rate match load/unload frequency
- ◆ Flow control needed in case FIFO gets totally full or totally empty




FIFO in detail

 - ◆ FIFO of any significant size is implemented using an on-chip SRAM
- ◆ SRAM must be dual-ported for our design [have two independent ports]
- ◆ We will use a write pointer to determine the write address, and a read pointer to determine the read address



FIFO pointer control

 - ◆ FIFO is managed as a circular buffer using pointers.
- ◆ First write will occur at address 00h. Next write will occur at 01h. After writing at FFh, next write will wrap to 00h.
- ◆ Reads work the same way. First read will occur at address 00h.



FIFO pointers and flow control


- ◆ Generation of FULL and EMPTY signals.
 - FIFO is FULL when write pointer catches read pointer


```
always @(posedge clk1)
FULL <= (WR_PNTR == RD_PNTR) && ((OLD_WR_PNTR + 1 == RD_PNTR) || FULL)
```
 - FIFO is empty when read pointer catches write pointer


```
always @(posedge clk2)
EMPTY <= (WR_PNTR == RD_PNTR) && ((OLD_RD_PNTR + 1 == WR_PNTR) || EMPTY)
```
- ◆ Write pointer and read pointer must never pass each other.
 - Write passing read overwrites unread data
 - Read passing write re-reads invalid data

FIFO in detail


- ◆ We have a problem!

 

To generate FULL/EMPTY conditions the write logic needs to see the read pointer and the read logic needs to see the write pointer!


Pointer Synchronization

 - ◆ Our pointers change in a very specific way (when they change, they increment by 1)
 - Applying a traditional two stage FF synchronizer on each bit of a binary pointer could cause a wildly invalid pointer value to be produced
 - Gray coding the pointer value means at most one bit will change per cycle _ we can only be _off by one_



Pointer Synchronizer

 - ◆ Pointer is stored in gray code.
- ◆ A standard single bit synchronizer is used on each bit of PTR_OUT. At most one bit changes per cycle!
- ◆ We can still do binary math to increment the pointer.




```
module bin2gray (bin,gray);
parameter SIZE = 4;
input [SIZE-1:0] bin;
output [SIZE-1:0] gray;
reg [SIZE-1:0] gray;
always @(bin)
gray = (bin >> 1) ^ bin;
endmodule


module gray2bin (gray,bin);
parameter SIZE = 4;
input [SIZE-1:0] gray;
output [SIZE-1:0] bin;
reg [SIZE-1:0] bin;
integer i;
always @(gray)
for (i=0; i<SIZE; i=i+1)
bin[i] = ^(gray >> i);
endmodule
```

Pointer Synchronizer pitfall

 
- ◆ Write and read pointers need to be registered in gray code as shown on previous slide.
- ◆ Don't be tempted to cheat and register pointers in binary. What's wrong with the synchronizer shown below?



Answer to pitfall

 

 
- ◆ Combinational logic frequently contains hazards at the output (non fully covered Karnaugh map)
- ◆ Avoid this problem by using a registered value of PTR_IN



Pointer math pitfall

- ◆ When our pointer synchronizer goes metastable our new pointer value may not be updated until one cycle later.
- ◆ We need to be conservative when generating FULL and EMPTY signals to reflect this.
 - § Typically FULL = 1 when WRITE catches READ. We need FULL = 1 when WRITE catches READ-1.
 - § Typically EMPTY = 1 when READ catches WRITE. We need EMPTY = 1 when READ catches WRITE-1.


Final Synchronizer FIFO

 

Works for any phase/frequency relationship between CLK1 and CLK2

Mesosynchronous Designs

 - ◆ When two systems of bounded frequency need communicate, open loop synchronization circuits can be used (no ACK)



Mesosynchronous Tradeoffs

- ◆ Benefits to mesosynchronous designs
 - § Less synchronization circuitry
 - § Synchronizer might have lower latency vs. full 4-phase handshaking
- ◆ Costs of mesosynchronous designs
 - § Synchronizer only works at certain frequency ratios (may hamper bringup/debug)
 - § Intolerant of spec mistakes (maybe that unload frequency was supposed to be ± 50%!)

Words to the wise

- ◆ Be wary of synchronizer schemes designed by others
 - § Synopsys Designware DW04_sync multi-bit synchronizer DOES NOT WORK as a synchronizer
 - § Synthesizers might use dynamic FFs as synchronizers _ they don't know the difference.
 - § Auto-placement tools must be told to place synchronizer FF pairs close together
- BE PARANOID

Conclusions

- ◆ Synchronizers are important. Synchronization failure is deadly and difficult to debug
- ◆ Synchronization requires careful design. Most CAD and logic tools CANNOT catch bad synchronizer designs.
- ◆ Design of synchronizer depends on performance level needed. Basic synchronizer of back-to-back FFs is the core design all others are based on.