

Lecture #4: Clocking in Synchronous Circuits

Kunle Olukotun
Stanford EE183
January 15, 2003

Tutorial/Verilog Questions?

- Tutorial is done, right?
 - Due at midnight (Fri 1/17/03)
 - Turn in copies of all verilog, copy of “verification” scripts you wrote, corresponding waveforms annotated, FPGA Editor output (use PrtSc and copy to MS Paint), the part of the implementation output that shows the speed and the amount of logic units utilized.
- Check out the tao of EE183 on the web

Course Logistics

- Labs due every two weeks
 - Prelab report due a week before demo
 - Demo due on Fridays at **5pm**
 - Report due by following Monday at midnight

Lab	Pre-Lab Report Due	Demo Due by 5 pm	Final Report Due
1	Jan 17	Jan 24	Jan 27
2	Jan 30	Feb 17	Feb 10
3	Feb 14	Feb 21	Feb 24
4	Feb 28	Mar 7	Mar 10

- All reports are submitted by email using PDF

PreLab

- Encourage you to think about structure of your design before you implement
 - Datapath control decomposition
 - FSM hierarchy and states
 - Better prelab leads to easier implementation
- Worth 2pts of your report
 - Demo: 20 pts
 - Prelab: 2pts
 - Report: 18pts

Lab 1 Questions?

- VGA
- TCGROM
- Sega Game Controller
- Two dual port memories
 - Why?
 - 4Kx1 architecture
- CoreGen

Lab 1: Optional Fun Things

- Display the number of iterations
- Capability to clear the screen
 - Instead of the cheesy (but perfectly fine) board reset
- Capability to start with a random game board
 - LFSR seeded by counter from powerup
- Fastforward
 - Have the next N game states be computed in rapid succession
 - Perhaps use a third BRAM

Lab 1: Known Interesting Initial States

- Some starting states are more interesting than others
 - Have the initialization of the BRAM be one of them.
 - Have multiple ones and switch between them
- Use Memutils.zip to generate the BRAMs init files.
 - <http://groups.yahoo.com/xsboard-users/files>
 - <http://groups.yahoo.com/group/xsboard-users/files/>

Lab 1: Background Image

- When the game state location is off show a background image
 - Have another 64x64 BRAM storing the image and index it the same way as the game board. If the location is vacant then display whatever is in the background image.
 - we only have 10 4kbit BRAMs

Lab 1 Design Structure


- Hierarchy of cooperating FSMs
 - Master control FSM
 - Gamepad FSM
 - VGA FSM
 - Board update FSM
 - Game state FSM
- Datapath elements
 - BRAMCounters
 - Registers
- Make VGA and gamepad modules reusable

Today's Lecture

- Clocking in synchronous systems
 - Skew
 - jitter
 - H clock distribution tree
 - Max path, min path, critical path

FSM Timing

 - Now that we know how to design a state machine, how fast can we make it run?
- The register-to-register performance is the key metric to consider.




Clock Skew

- We have assumed that the clock reaches each DFF simultaneously.
 - It should be no surprise that this assumption is not entirely valid.
- Clock Skew is the non-time varying (static) difference in the clock arrival time at two different DFFs.


Clock Skew

 - The wire propagation delay is non trivial and the difference in arrival times for this type of layout is unacceptable.



H Clock Distribution Tree

 - Make Clock distribution tree in the form of an H so that all flops are equidistant to the root of the tree.
- An FPGA is a very regular structure but for an ASIC, there are a variable number of DFFs in each sector.



Spartan II Skew Data



Spartan-II 2.5V FPGA Family: DC and Switching Characteristics

Clock Distribution Guidelines⁽¹⁾

Symbol	Description	Speed Grade		Units
		-6	-5	
		Max	Max	
GCLK Clock Skew				
T _{GSKIEWIOB}	Global clock skew between IOB flip-flops	0.13	0.14	ns

Notes:

1. These clock distribution delays are provided for guidance only. They reflect the delays encountered in a typical design under worst-case conditions. Precise values for a particular design are provided by the timing analyzer.

Clock Jitter

- Clock Jitter is the time-varying (cycle to cycle) difference in the clock arrival time at the *same* DFF.
- There are many sources of jitter—inaccuracies in the source oscillator, drifting of the Phase Lock Loop (PLL), and crosstalk between the clock and other transitioning signals.

Spartan II Jitter Data

DLL Clock Tolerance, Jitter, and Phase Information


All DLL output jitter and phase specifications were determined through statistical measurement at the package pins using a clock mirror configuration and matched drivers. Figure 1, page 13, provides definitions for various parameters in the table below.

Symbol	Description	F _{CLKIN}	CLKDLLHF		CLKDLL		Units
			Min	Max	Min	Max	
T _{IPTOL}	Input clock period tolerance	-	-	1.0	-	1.0	ns
T _{IJTCC}	Input clock jitter tolerance (cycle-to-cycle)	-	-	±150	-	±300	ps
T _{LOCK}	Time required for DLL to acquire lock	> 60 MHz	-	20	-	20	µs
		50-60 MHz	-	-	-	25	µs
		40-50 MHz	-	-	-	50	µs
		30-40 MHz	-	-	-	90	µs
		25-30 MHz	-	-	-	120	µs
T _{OJITCC}	Output jitter (cycle-to-cycle) for any DLL clock output ⁽¹⁾	-	-	±60	-	±60	ps
T _{PHIO}	Phase offset between CLKIN and CLKO ⁽²⁾	-	-	±100	-	±100	ps
T _{PHOO}	Phase offset between clock outputs on the DLL ⁽³⁾	-	-	±140	-	±140	ps
T _{PHIOM}	Maximum phase difference between CLKIN and CLKO ⁽⁴⁾	-	-	±160	-	±160	ps
T _{PHOOM}	Maximum phase difference between clock outputs on the DLL ⁽⁵⁾	-	-	±200	-	±200	ps

- Notes:**
- Output Jitter** is cycle-to-cycle jitter measured on the DLL output clock, *excluding* input clock jitter.
 - Phase Offset between CLKIN and CLKO** is the worst-case fixed time difference between rising edges of CLKIN and CLKO, *excluding* output jitter and input clock jitter.
 - Phase Offset between Clock Outputs on the DLL** is the worst-case fixed time difference between rising edges of any two DLL outputs, *excluding* Output Jitter and input clock jitter.
 - Maximum Phase Difference between CLKIN and CLKO** is the sum of Output Jitter and Phase Offset between CLKIN and CLKO, or the greatest difference between CLKIN and CLKO rising edges due to DLL alone (*excluding* input clock jitter).
 - Maximum Phase Difference between Clock Outputs on the DLL** is the sum of Output Jitter and Phase Offset between any two DLL clock outputs, or the greatest difference between any two DLL output rising edges due to DLL alone (*excluding* input clock jitter).

 Example Parameters

- DFF values:
 - $T_{clk \rightarrow q} = 1ns, T_{setup} = 1ns, T_{hold} = 1ns$
- Clock skew is max 2ns and jitter is 2ns
- Combinational logic $T_{cl_pdmax} = 10ns,$
 $T_{cl_pdmin} = 1ns$



MaxPath Timing Constraint


- Add up the components that result in the time budget; the period must be greater than this value.
- $T_{\text{clk} \rightarrow \text{q}} + T_{\text{cl_pdmax}} + T_{\text{setup}} + T_{\text{skew}} + T_{\text{jitter}} \leq \text{Clock Period}$
- $1 + 10 + 1 + 2 + 2 \leq \text{Clock Period}$
- $16\text{ns} \leq \text{Clock Period}$
- Max Frequency is 62.5MHz

MinPath Timing Constraint

- Consider what happens when the same clock edge is considered at the far DFF.
- $T_{\text{clk} \rightarrow \text{q}} + T_{\text{cl_pdmin}} \geq T_{\text{skew}} + T_{\text{jitter}} + T_{\text{hold}}$
- $1 + 1 \geq 2 + 2 + 1$
- Whoops!! ☹
- AKA, “Hold-Time Violation”

MinPath and ShiftRegisters

 - Shift Registers can easily fall prey to min path timing violations.
- Fix the violations by increasing delay between Ds and Qs
 - Insert pairs of inverters
- FPGA DFF clk->q is big enough so that MinPath violations are rare.
 - $T_{\text{clk-q}} = 1.0\text{ns}$
 - $T_{\text{hold}} = 0\text{ns}$
 - $T_{\text{skew}} = 0.14\text{ns}$
 - $T_{\text{jitter}} = 0.06\text{ns}$



Impacts

- You can “fix” MaxPath timing constraint violations by slowing down the clock after the circuit is implemented.
- You *cannot* “fix” MinPath timing constraint violations by modifying the clock.

Static Timing Tool

- Longest MaxPath Constraint is called *Critical Path* of design.
 - Find critical path by calculating all the MaxPath constraints of every path in the design and picking the largest.
- Perfect tool for a computer.
 - Xilinx Timing Analyzer is an example of a static timing tool.

Timing Closure Challenges

- When integrate individual blocks that meet timing, the combined system might not meet timing.
- In general have registered outputs from *top-level* blocks.
 - This doesn't solve the problem if the chip is so large/fast that a signal cannot propagate all the way across the chip.
 - Reason that I/Os are always useful to register
 - Not always certain timing budget available on the board.