

Problem 3, part (d): Load-line analysis of CMOS

